

Simulation of Stand-alone Photovoltaic System using Python


Arjun Sanu M, B. Kanoj, Vijaybabu and A. B. Raju

Department of Electrical & Electronics Engineering
B.V.B College of Engineering & Technology, Hubli-31


December 29, 2012




System Block Diagram

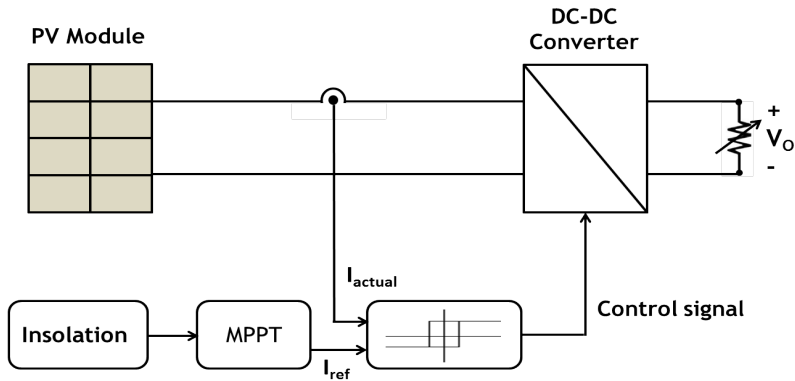


Circuit Diagram

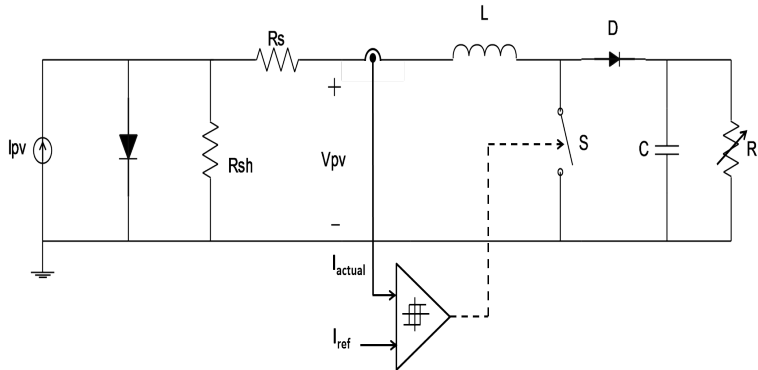

Boost converter

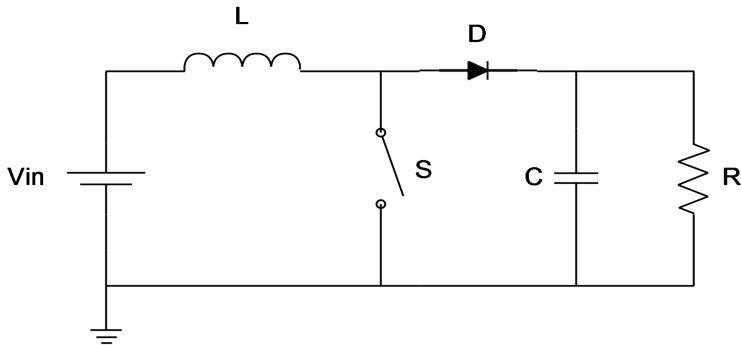


Case 1: when switch is ON

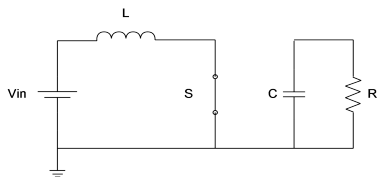
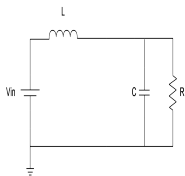
$$\frac{di}{dt} = \frac{1}{L} [V_{in} - (1 - S)V_c]$$





$$\frac{dV_{in}}{dt} = \frac{1}{C} \left[(1 - S)i - \frac{V_c}{R} \right]$$

Principal Symbols

- V_{pv} = PV module voltage
- I_{pv} = PV module current
- I_{ph} = Photo current
- I_{rs} = Reverse saturation current
- n_s = Number of cells connected in series
- n_p = Number of cells connected in parallel
- R_s = Series Resistance
- R_{sh} = Shunt Resistance
- T = Temperature in Kelvin
- B = Ideality factor of the diode
- q = Electron charge (1.602×10^{-19} C)
- K = Boltzmann's constant (1.38×10^{23} J/K)



PV Module: Mathematical Model

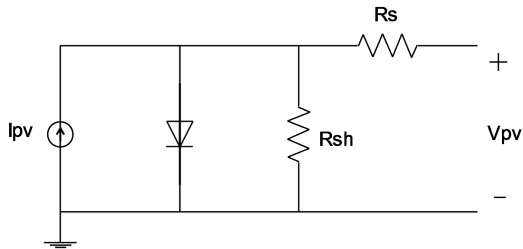


Figure: Typical PV cell

$$V_{pv} = \left(\frac{n_s k T B}{q} \right) * \ln \left[\frac{n_p I_{ph} - I_{pv} + n_p I_{rs}}{I_{rs}} \right] - R_s I_{pv}$$



Electrical Characteristics

| Symbol | Quantity | Value |
|-----------|-----------------------|--------|
| P_{max} | maximum power | 5.0 W |
| V_{max} | Voltage at P_{max} | 17.2 V |
| I_{max} | Current at P_{max} | 0.29 A |
| I_{sc} | Short circuit current | 0.32 A |
| V_{oc} | Open circuit voltage | 21.0 V |



Results

VI characteristics of PV module at different insulations

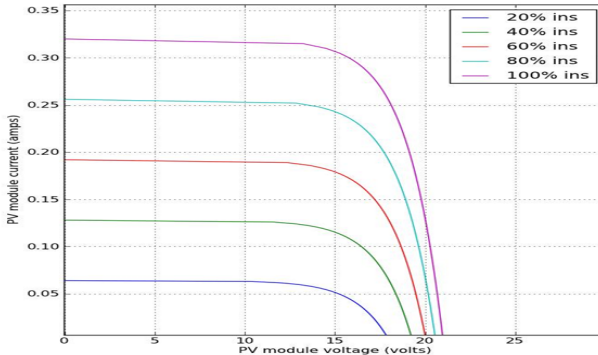


Figure: VI characteristics



Results

Power curves of the PV module at different insolation levels

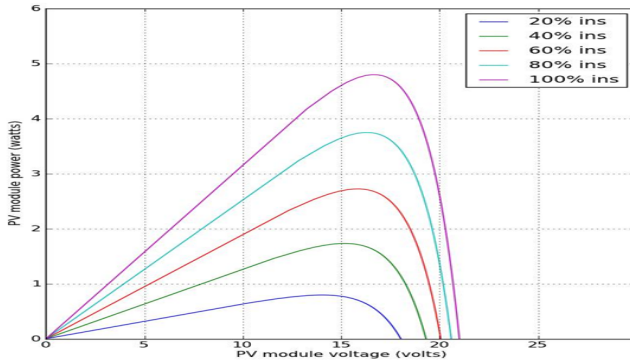



Figure: Power curve



Why Python?

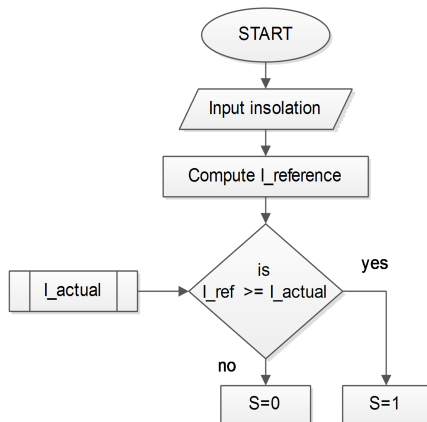- Python has all the features present in the other simulation softwares.
- Free and Open Source.
- Possibility of improving performance comparable to compiled languages.
- Possibility of developing GUI application.





flowchart to generate the switching pulses at MPP




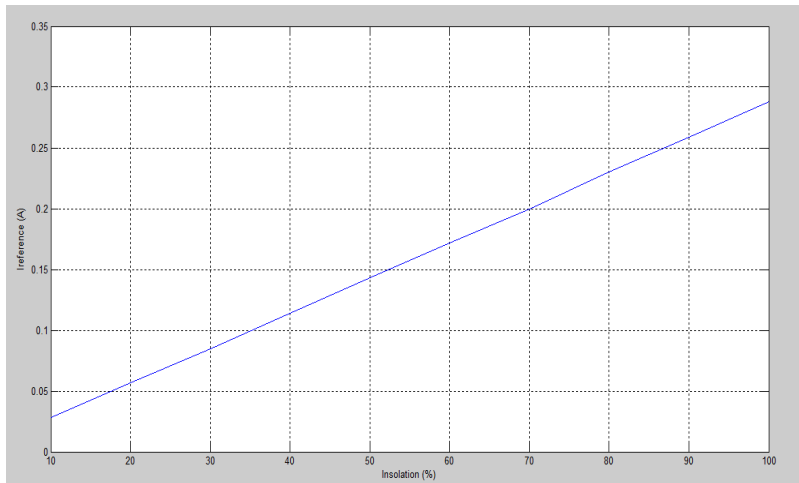


Figure: Plot of Ireference Vs Insolation

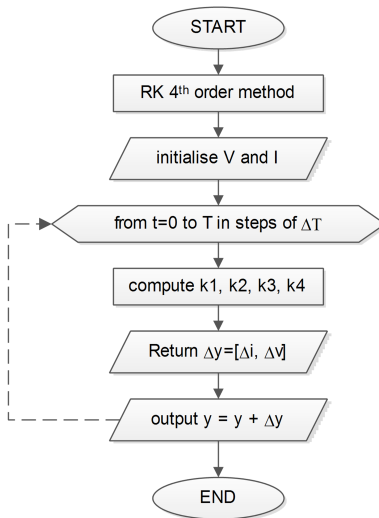





flowchart for system simulation




Results

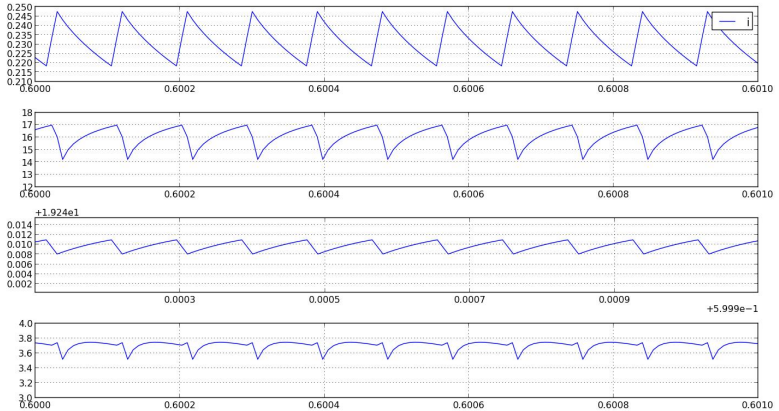

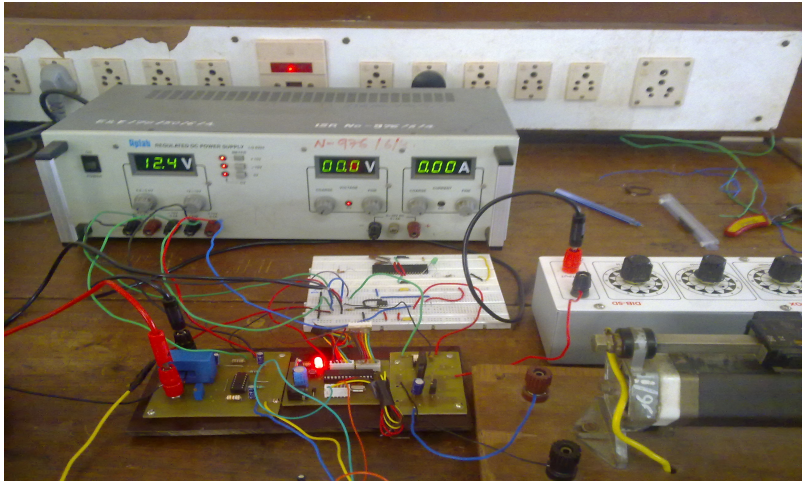

Experimental setup

Results

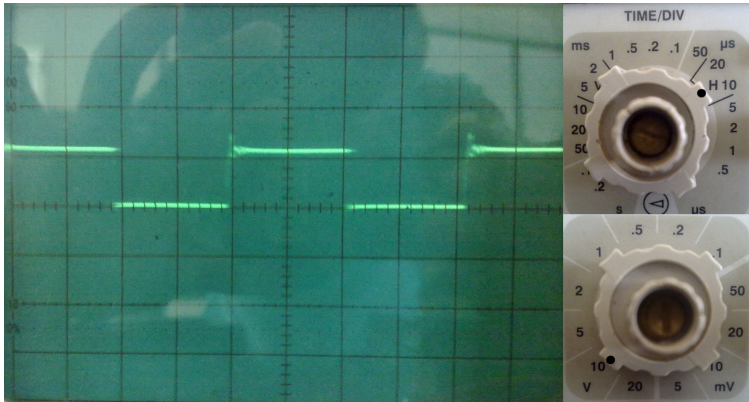


Dutycycle when $R_{load} = 150$ ohms

Conclusion

- The system simulation has been carried out for one value of insolation & hysteresis band control has been used for generating switching pulses.
- Further the simulation can be carried out for different insolation levels.
- MPP tracking algorithms can be implemented.



References

-  E. Koutroulis, K. Kalaitzakis, and N.C.Voulgaris, *Development of a microcontroller-based, photovoltaic maximum power point tracking control system*, IEEE Transactions on Power Electronics, vol.16, no.21, pp. 4654, Jan.2001.



THANK YOU

