

$$r_1 = 4.218139246 \text{ times } r_2$$

if r_2 is 1200ohm

$$r_1 = 5061.767095 \text{ ohm}$$

$$r_2 = 1200 \text{ ohm}$$