

current = 0.000668519ampere

vce = 2.687288889volt

resistance = 690ohm

current = 0.000636011ampere

vce = 2.629556025volt