

$$r_b = 21500\text{ohm}$$

$$r_c = 700\text{ohm}$$

$$r_b \text{ at emitter resistance } 100\text{ohm} = 18950\text{ohm}$$