

base current = 0.0000215ampere

collector current = 0.00215ampere

emitter current = 0.0021715ampere

base current = 0.000025622ampere

collector current = 0.002562189ampere

emitter current = 0.002587811ampere