

$r_b = 630000 \text{ ohm}$

$\text{stability} = 56.50660793$

new point

$i_c = 0.000642045 \text{ ampere}$

$v_{ce} = 8.789772727 \text{ volt}$