

voltage gain = $260 < 180$

voltage gain reduced ce removed

when cb is short circuited the voltage gain increased