

current gain = -48.7804878

input resistance = 990.2439024ohm

voltage gain = -49.26108374

output resistance = 51428.57143ohm

approximate

current gain = -50

input resistance = 1000ohm

voltage gain = -50