

output resistance = 1000ohm

input resistance very low

voltage gain = 19.23076923