

$$r1 = 500\text{ohm}$$

$$\text{effective input resistance} = 1.25\text{r3ohm}$$

$$r2 = 1500\text{ohm}$$

$$\text{voltage gain} = 0.975609756\text{av`}$$