

Output voltage = $-5v_1 + (-2v_2)$