

Output voltage for  $v_i 0.01 = -414.4 \text{ mV}$

Output voltage for  $v_i 0.1 = -473.6 \text{ mV}$

Output voltage for  $v_i 1 = -532.8 \text{ mV}$