

Console

Example 18.1, Page No. = 18.3

Upper limit of current (Ampere) =

264.28571

Lower limit of current (Ampere) =

211.67448

Total resistance at starting (ohm) =

0.9459459

Resistance of each section

r1 (ohm) =

0.1883090

r2 (ohm) =

0.1508224

r3 (ohm) =

0.1207983

r4 (ohm) =

0.0967510

r5 (ohm) =

0.0774908

r6 (ohm) =

0.0620648

r7 (ohm) =

0.0497096

