

For an open link, the input to AND gate is logic 1, whereas for a closed link the corresponding input to the AND gate is same as the voltage applied

at that input, therefore,

$$P(o)=I(o)I(2)'I(3)'I(6)$$