

Result Example-3.3

the base current of given circuit is (in mA):

1.86

the collector current of given circuit is (in mA):

4.95

base current required for the transistor to be in saturation is (in mA):

0.165

the base current is (in mA):

- 2.14