

Result Example-3.7(a)

when  $V(i)=0$ , the transistor T(1) is operating at point B

here  $V(o)$ (in volts)=

5.