

Console

-->//For p1, the 5-A current is out of the positive terminal (or into the negative terminal h

-->

-->// power(p) in watts is given by $p=V*I$

-->

-->// v voltage in volts and i current in Amperes

-->

-->p1=20*-5;

-->

-->disp("p1=")

p1=

-->disp(p1)

- 100.

-->units='Watts W'

units =

Watts W

-->p1=[string(p1) units];

-->disp(p1)

!-100 Watts W !

-->

-->// in watts

-->

-->

```
-->// power in p1 is -100w ie. the supplied power  
-->  
-->//For p2 and p3, the current flows into the positive terminal of the element in each ca  
nce,  
-->  
-->p2=12*5;  
-->  
-->disp("p2=")  
  
p2=  
-->disp(p2)  
  
60.  
  
-->units='Watts W'  
units =  
  
Watts W  
  
-->p2=[string(p2) units];  
  
-->disp(p2)  
  
!60 Watts W !  
  
-->  
-->// in watts  
-->  
-->  
-->  
-->// p2 is 60w absorbed power  
-->  
-->p3=8*6;
```

```

-->

-->disp("p3=")

p3=

-->disp(p3)

48.

-->units='Watts W'
units =

Watts W

-->p3=[string(p3) units];

-->disp(p3)

!48 Watts W !

-->

-->// in watts

-->

-->

-->// p3 is absorbed power

-->

-->//For p4,we should note that the voltage is 8V(positive at the top), the same as the v<
-->for p3, since both the passive element and the dependent source are connected to the<
-->terminals.

-->

-->// i current is 5A

-->

-->p4=8*(-0.2*5);

-->
```

```
-->disp("p4=")

p4=

-->disp(p4)

- 8.

-->units='Watts W'
units =

Watts W

-->p4=[string(p4) units];

-->disp(p4)

!-8 Watts W !

-->

-->// in watts

-->

-->

-->// p4 is -8w supplied power

-->

-->// now...

-->p1=-100;

-->p2=60;

-->p3=48;

-->p4=-8;

-->

-->p0=p1+p2+p3+p4;
```

-->disp(p0)

0.

-->

-->disp("W")

W

-->// in watts W

-->

-->// this shows that total power supplied equals total power absorbed.

-->

-->