

```
//example 3.7//  
//not using nand//  
clc  
//refreshes all variables//  
clear  
//clears the screen//  
disp('in the figure same input is given to NAND gate on both ends.')
```