

```
//example 3.8//  
//not using nor 2 different input//  
clc  
//refreshes all variables//  
clear  
//clears the screen//  
disp('The first two EX-NOR gates implement a two input EX-OR gate using  
two input EX-NOR gates. The second EX-NOR gate here has been wired as a  
NOT circuit. The output of the second gate and the third input are fed  
to the two inputs of the third EX-NOR gates.')
```

```
//result//
```