

```
//example 4.5//
clc
//clears the screen//
clear
//clears all existing variables//
a=1.6;
//when output is LOW, inputs of all gates draw
current individually//
i=5*a;
//input loading factor//
disp(i,'current being sourced when output is
high (in mA) = ')
```