

```
//example 7.4(b)//  
clc  
//clears the screen//  
clear  
//clears all variables//  
disp('Inputs D5 to D7 are the ones that are active; among these, D7 has  
the highest priority. Therefore, the output bits are A=0, B=0 and C=0')
```