

```
//example 7.4(c)//  
clc  
//clears the screen//  
clear  
//clears all variables//  
disp('D7 is active. Since D7 has the highest priority, it will be  
encoded irrespective of the logic status of other inputs. Therefore,  
the output bits are A=0, B=0 and C=0')
```