

Scilab Textbook Companion for  
Transmission Lines And Networks  
by U. Sinha<sup>1</sup>

Created by  
Aakanksha Gupta  
Bachelor of Engineering  
Electrical Engineering  
Thapar University  
College Teacher  
Dr.sunil Kumar Singla  
Cross-Checked by  
Lavitha Pereira

November 24, 2013

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Transmission Lines And Networks

**Author:** U. Sinha

**Publisher:** Satya Prakashan, New Delhi

**Edition:** 5

**Year:** 1987

**ISBN:** 81-7684-017-3

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>5</b>
<b>1 Transmission Lines</b>	<b>13</b>
<b>2 Open and Short Circuited Lines</b>	<b>24</b>
<b>3 Line with any Termination</b>	<b>33</b>
<b>4 Power Lines</b>	<b>45</b>
<b>5 Telegraph and Telephone Lines</b>	<b>49</b>
<b>6 Ultrahigh Frequency Lines</b>	<b>60</b>
<b>7 Waveguides</b>	<b>68</b>
<b>8 Transmission Lines Measurements</b>	<b>72</b>
<b>9 Artificial Lines</b>	<b>74</b>
<b>11 Networks</b>	<b>78</b>
<b>12 Network Theorems</b>	<b>94</b>
<b>13 Network Parameters</b>	<b>109</b>
<b>14 Filters</b>	<b>121</b>
<b>15 Equalizers</b>	<b>137</b>



# List of Scilab Codes

Exa 1.1	Calculating the resistance and inductance and leakage and capacitance per km and velocity of propagation . . . . .	13
Exa 1.2	Calculating the values of the line constants . . . . .	14
Exa 1.3	Determining Zo and a and b . . . . .	14
Exa 1.4	Calculating terminating impedance and attenuation and phase constant . . . . .	15
Exa 1.5	Calculating phase velocity and characteristic impedance and propagation constant and power delivered at receiving end . . . . .	16
Exa 1.6	Calculating characteristic impedance and propagation constant . . . . .	16
Exa 1.7	Calculating Zo and a and b and Vp . . . . .	17
Exa 1.8	Calculating characteristic impedance . . . . .	18
Exa 1.9	Calculating phase velocity and attenuation . . . . .	18
Exa 1.10	Calculating characteristic impedance . . . . .	19
Exa 1.11	Calculating the voltage across load in terms of the sending end voltage . . . . .	19
Exa 1.12	Calculating dc resistance and inductance and capacitance and ac resistance . . . . .	20
Exa 1.13	Calculating per km high and low frequency inductance and capacitance and dc and ac resistance . . . . .	21
Exa 1.14	Calculating line attenuation and velocity of propagation	22
Exa 1.15	Calculating sending and receiving end voltages and currents and power . . . . .	22
Exa 2.1	Calculating Zo . . . . .	24
Exa 2.2	Calculating the line constants . . . . .	24
Exa 2.3	Calculating the received current and voltage . . . . .	25

Exa 2.4	Determining $Z_0$ and $a$ and $b$ and primary constants of line . . . . .	26
Exa 2.5	Calculating the line constants . . . . .	27
Exa 2.6	Calculating $Z_0$ and $P$ and line constants . . . . .	28
Exa 2.7	Calculating the series impedance and shunt admittance per km of line . . . . .	29
Exa 2.8	Calculating $Z_0$ and $a$ and $b$ . . . . .	29
Exa 2.9	Calculating output current when far end is short circuited . . . . .	30
Exa 2.10	Calculating $Z_0$ and $a$ and $b$ . . . . .	31
Exa 2.11	Calculating $Z_0$ and $a$ and $b$ . . . . .	31
Exa 3.1	Calculating sending end voltage . . . . .	33
Exa 3.2	Calculating rms value voltage and current . . . . .	33
Exa 3.3	Calculating the rms value of voltage and current . . . . .	34
Exa 3.4	Calculating the input impedance of line . . . . .	34
Exa 3.5	Calculating sending end impedance . . . . .	35
Exa 3.6	Calculating input impedance . . . . .	35
Exa 3.7	Calculating the value of voltage reflection coefficient . .	36
Exa 3.8	Calculating the ratio of transmitter voltage to receiver voltage . . . . .	36
Exa 3.9	Calculating the value of voltage reflection coefficient . .	37
Exa 3.10	Calculating power delivered at receiving end . . . . .	37
Exa 3.11	Calculating sending end current and receiving end current and voltage and efficiency of transmission . . . . .	38
Exa 3.12	Calculating the resistance and inductance of the series and shunt elements . . . . .	39
Exa 3.13	Determining the characteristic impedance and propagation constant . . . . .	40
Exa 3.14	Calculating voltage and current . . . . .	40
Exa 3.15	Calculating input impedance . . . . .	41
Exa 3.16	Calculating power consumed in load . . . . .	41
Exa 3.17	Calculating the exact and approximate distance to fault .	42
Exa 3.18	Calculating the reflection factor and reflection loss . .	43
Exa 3.19	Calculating reflection coefficient and input impedance .	43
Exa 3.20	Finding reflection loss . . . . .	44
Exa 4.2	Determining equivalent pi network . . . . .	45
Exa 4.3	Calculating inductance per km of line . . . . .	45
Exa 4.4	Calculating characteristic impedance and propagation constant . . . . .	46

Exa 4.5	Calculating inductive reactance . . . . .	46
Exa 4.6	Calculating capacitive susceptance . . . . .	47
Exa 4.7	Determining the capacitance per km and charging current . . . . .	47
Exa 5.1	Calculating decrease in attenuation and cut off frequency	49
Exa 5.2	Calculating Zo and a and b and Vp . . . . .	49
Exa 5.3	Calculating modified Zo and a and Vp . . . . .	50
Exa 5.4	Calculating the phase velocity before and after velocity and decrease in attenuation and cut off frequency . . .	51
Exa 5.5	Calculating attenuation and cut off frequency . . . . .	52
Exa 5.6	Calculating attenuation and highest frequency of transmission . . . . .	52
Exa 5.7	Calculating the value of Zo and a and Vp after loading	53
Exa 5.8	Calculating cut off frequency and attenuation . . . . .	54
Exa 5.9	Calculating Zo and a and b . . . . .	54
Exa 5.10	Calculating length of line for a given attenuation . . .	55
Exa 5.11	Calculating cutoff frequency and attenuation and phase velocity . . . . .	55
Exa 5.12	Finding the value of the loading coil inductance and the interval at which it needs to be placed . . . . .	56
Exa 5.13	Calculating rate of transmission of information . . . . .	57
Exa 5.14	Calculating a and b and cut off frequency . . . . .	57
Exa 5.15	Calculating wavelength of line . . . . .	58
Exa 5.16	Calculating the value of attenuation . . . . .	58
Exa 5.17	Calculating potential at mid point . . . . .	59
Exa 6.1	Calculating complex reflection coefficient and terminal impedance . . . . .	60
Exa 6.2	Calculating value of load impedance . . . . .	61
Exa 6.3	Calculating VSWR and position of voltage minimum nearest to load . . . . .	61
Exa 6.4	Calculating standing wave ratio . . . . .	62
Exa 6.5	Calculating value of load impedance . . . . .	62
Exa 6.11	Calculating point of attachment and length of stub . .	63
Exa 6.14	Calculating point of attachment and length of stub . .	63
Exa 6.15	Calculating point of attachment and length of stub . .	64
Exa 6.17	Calculating the dimensions of a quarter wave line . . .	64
Exa 6.18	Designing a quarter wave transformer . . . . .	65

Exa 6.19	Designing a single stub matching given system to eliminate standing wave ratio . . . . .	65
Exa 6.20	calculating frequency and terminated impedance . . . . .	66
Exa 6.21	Calculating load and input impedance . . . . .	66
Exa 7.1	Calculating critical and guide wavelengths . . . . .	68
Exa 7.2	Finding the value of the dominant mode . . . . .	68
Exa 7.3	Calculating the cut off wavelength and guide wavelength and group and phase velocities and the characteristic wave impedance . . . . .	69
Exa 7.4	Calculating voltage attenuation . . . . .	69
Exa 7.5	Calculating group and phase velocities and phase constant . . . . .	70
Exa 7.6	Calculating cut off frequencies . . . . .	70
Exa 7.7	Calculating cut off wavelength and guide wavelength and characteristic wave impedance . . . . .	71
Exa 8.1	Calculating the value of load impedance . . . . .	72
Exa 8.2	Calculating insertion loss . . . . .	72
Exa 8.3	Calculating insertion loss . . . . .	73
Exa 9.1	Designing an artificial line . . . . .	74
Exa 9.2	Designing an artificial line . . . . .	75
Exa 9.3	Designing a delay line using T section . . . . .	75
Exa 9.4	Designing an artificial line . . . . .	76
Exa 11.1	Calculating image and iterative impedance . . . . .	78
Exa 11.2	Calculating iterative impedance . . . . .	79
Exa 11.3	Calculating iterative and image impedance . . . . .	79
Exa 11.4	Calculating image and iterative impedances and transfer constants . . . . .	80
Exa 11.5	Computing the insertion ratio and loss . . . . .	81
Exa 11.6	Determining the components of a symmetrical T section network . . . . .	82
Exa 11.7	Calculating current . . . . .	82
Exa 11.8	Calculating characteristic impedance . . . . .	82
Exa 11.9	Designing a L section . . . . .	83
Exa 11.10	Designing a reactive T network . . . . .	84
Exa 11.11	Determining the equivalent T network . . . . .	84
Exa 11.12	Finding the elements of the arms of a loss less T network . . . . .	85
Exa 11.13	Determining the image and iterative impedance and equivalent T network . . . . .	85

Exa 11.14	Calculating the characteristic impedance and propagation function of given network . . . . .	86
Exa 11.15	Calculating characteristic impedance and propagation function . . . . .	87
Exa 11.16	Designing a L matching loss less network . . . . .	88
Exa 11.17	Calculating different losses and total insertion loss . . .	88
Exa 11.18	Calculating the elements of a L section network . . . .	89
Exa 11.19	Calculating image impedance and transfer constant . .	90
Exa 11.20	Calculating reduction in power . . . . .	91
Exa 11.21	Calculating characteristic impedance and attenuation constant and phase shift constant . . . . .	91
Exa 11.22	Calculating image impedance and propagation constant and elements of T network . . . . .	92
Exa 12.1	Finding the rms value of current . . . . .	94
Exa 12.2	Calculating voltage . . . . .	94
Exa 12.3	Calculating current . . . . .	95
Exa 12.5	Determining Thevenins equivalent generator . . . . .	95
Exa 12.6	Determining Thevenins equivalent circuit . . . . .	96
Exa 12.7	Deriving the equivalent voltage generator circuit . . .	96
Exa 12.8	Determining the Nortons equivalent circuit . . . . .	97
Exa 12.9	Obtaining Nortons equivalent circuit . . . . .	98
Exa 12.10	Verifying reciprocity theorem . . . . .	98
Exa 12.11	Calculating value of compensation source . . . . .	98
Exa 12.12	Calculating power in load and turns ratio for maximum power transfer . . . . .	99
Exa 12.13	Determining value of maximum power . . . . .	99
Exa 12.14	Calculating value of R and X which result in maximum power transfer and value of maximum power transferred .	100
Exa 12.17	Calculating effective resistance of coil and inductance of the effective resistance . . . . .	100
Exa 12.19	Determining the elements of a series type Foster network	101
Exa 12.20	Determining the elements of series type Foster network	102
Exa 12.21	Finding current . . . . .	103
Exa 12.22	Using Thevenins theorem to calculate power . . . .	103
Exa 12.23	Finding Thevenins equivalent generator . . . . .	103
Exa 12.25	Determining the value of load impedance for which maximum power is consumed in load and the corresponding power . . . . .	104

Exa 12.26	Determining Thevenins equivalent circuit . . . . .	104
Exa 12.27	Calculating current . . . . .	105
Exa 12.28	Using Millmans theorem to find current and voltage .	105
Exa 12.29	Verifying Tellegens theorem . . . . .	106
Exa 12.30	Verifying Tellegens theorem . . . . .	106
Exa 12.31	Finding current . . . . .	107
Exa 12.32	Calculating current and voltage using Thevenins theorem	108
Exa 13.1	Determining z and y parameters . . . . .	109
Exa 13.2	Obtaining the open circuit impedance parameters . .	110
Exa 13.3	Finding driving point and transfer impedances and loop equations and voltage . . . . .	110
Exa 13.4	Computing y parameters . . . . .	111
Exa 13.5	Finding the z parameters . . . . .	111
Exa 13.6	Computing h parameters . . . . .	112
Exa 13.7	Calculating transmission parameters and loop equations	113
Exa 13.8	Obtaining the transmission parameters . . . . .	113
Exa 13.9	Calculating input impedance . . . . .	114
Exa 13.10	Finding ABCD parameters and the equivalent T network	115
Exa 13.11	Obtaining the parameters Ya and Yb and Yc . . . .	115
Exa 13.12	Finding the equivalent pi network . . . . .	116
Exa 13.13	Obtaining the z and y and ABCD parameters and the equivalent pi network . . . . .	116
Exa 13.14	Finding y parameters . . . . .	117
Exa 13.15	Determining the ABCD parameters and image impedance	118
Exa 13.17	Determining the open and short circuit impedance .	119
Exa 13.18	Calculating y parameters . . . . .	119
Exa 13.19	Determining the image impedances . . . . .	120
Exa 14.1	Calculating values of inductor and capacitor . . . .	121
Exa 14.2	Calculating cut off frequency and attenuation and phase shift . . . . .	121
Exa 14.3	Calculating value of L and C . . . . .	122
Exa 14.4	Determining iterative impedance and cut off frequency and ratio of output voltage to input voltage . . . . .	122
Exa 14.5	Determining the elements of a prototype HP T section filter . . . . .	123
Exa 14.6	Calculating frequency . . . . .	123
Exa 14.7	Designing a m derived T section low pass filter . . .	124
Exa 14.8	Designing an m derived T section high pass filter . . .	124

Exa 14.9	Designing a low pass filter . . . . .	125
Exa 14.10	Designing a high pass composite filter . . . . .	126
Exa 14.11	Designing a high pass filter and finding the frequency of peak attenuation . . . . .	127
Exa 14.12	Designing a low pass composite filter . . . . .	128
Exa 14.13	Designing a prototype band pass filter . . . . .	129
Exa 14.14	Designing a prototype T section of a band pass filter .	129
Exa 14.15	Designing a m derived low pass filter . . . . .	130
Exa 14.16	Determining the values of shun arm of network . . . . .	131
Exa 14.17	Designing a low pass composite filter . . . . .	131
Exa 14.18	Determining the cut off frequency and characteristic impedance . . . . .	132
Exa 14.19	Designing a low pass composite filter . . . . .	133
Exa 14.20	Determining the second resonance frequency . . . . .	134
Exa 14.21	Computing the values of elements of filter . . . . .	134
Exa 14.22	Calculating bandwidth . . . . .	135
Exa 14.23	Finding the values of the elements of a prototype filter	135
Exa 15.4	Finding the elements of the lattice . . . . .	137
Exa 15.5	Calculating values of L and C . . . . .	137
Exa 15.6	Calculating characteristic impedance and the components of the shunt arm of equalizer . . . . .	138
Exa 15.10	Calculating value of R and L . . . . .	138
Exa 15.11	Designing a constant resistance equalizer . . . . .	139
Exa 15.12	Designing a constant resistance equalizer . . . . .	139
Exa 15.13	Designing a lattice equalizer . . . . .	140
Exa 16.1	Designing a symmetrical bridge T network . . . . .	142
Exa 16.2	Designing a T pad attenuator . . . . .	142
Exa 16.3	Designing a T type attenuator . . . . .	143
Exa 16.4	Designing an attenuator and determining its equivalent T structure . . . . .	143
Exa 16.5	Finding the elements of the arm of a T section symmetrical resistive attenuator . . . . .	144
Exa 16.6	Calculating the characteristic and attenuation per section of an attenuator . . . . .	144
Exa 16.7	Determining the resistance value of a T type attenuator pad . . . . .	145
Exa 16.8	Finding the elements of a balanced T pad . . . . .	145
Exa 16.9	Designing L type attenuator . . . . .	146

Exa 16.10	Designing a T pad . . . . .	146
Exa 16.11	Designing an unbalance pi attenuator . . . . .	147
Exa 16.12	Designing a T attenuator . . . . .	147
Exa 16.13	Designing a ladder attenuator . . . . .	148
Exa 16.14	Designing an attenuator . . . . .	148
Exa 16.15	Designing a balanced attenuator . . . . .	149
Exa 16.16	Finding the attenuation and the values of the shunt resistance of an H type attenuator . . . . .	149
Exa 16.17	Designing a L type attenuator . . . . .	150
Exa 16.18	Designing a minimum loss pad . . . . .	150

# Chapter 1

## Transmission Lines

**Scilab code Exa 1.1** Calculating the resistance and inductance and leakage and capacitance per km and velocity of propagation

```
1 clear;
2 clc;
3 Zo=710* exp(%i*(-%pi/(180/16)));f=1000;
4 w=2*%pi*f;
5 a=.01;b=.035;
6 P=a+%i*b;
7 Z=Zo*P;
8 R=real(Z);
9 r=round(R*100)/100;
10 printf(' -Resistance R = %f ohms/km\n',r);
11 L=((imag(Z))/w)*10^3;
12 l=round(L*100)/100;
13 printf(' -Inductance L = %f mH/km\n',l);
14 Y=P/Zo;
15 G=real(Y);
16 printf(' -Conductance G = %f mhos/km\n',-G);
17 C=((imag(Y))/w)*10^6;
18 c=round(C*1000)/1000;
19 printf(' -Capacitance C = %f microfarads/km\n',c);
20 Vp=round(w*1000/(b*10^5))/1000;
```

```
21 printf( '-Velocity of propagation Vp = %f * 10^5 km/
sec ',Vp);
```

---

### Scilab code Exa 1.2 Calculating the values of the line constants

```
1 clear;
2 clc;
3 Zo=2039.6;f=800; //value of Zo as taken in solution
4 P=0.054* exp(%i*(%pi/(180/87.9)));
5 w=2*pi*f;
6 Z=Zo*P;
7 R=real(Z);
8 printf( '-Resistance R = %f ohms/km\n',R);
9 L=(imag(Z))/w;
10 printf( '-Inductance L = %f mH/km\n',L*(10^3));
11 Y=P/Zo;
12 G=real(Y);
13 printf( '-Conductance G = %f micromhos/km\n',G*(10^6)
);
14 C=((imag(Y))/w)*(10^6);c=round(C*10000)/10000
15 printf( '-Capacitance C = %f microfarads/km\n',c);
```

---

### Scilab code Exa 1.3 Determining Zo and a and b

```
1 clear;
2 clc;
3 R=10;L=.0037;f=1000;G=.4*(10^-6);C=.0083*(10^-6);
4 w=2*pi*f;
5 Z=R+(%i*w*L);
6 Y=G+(%i*w*C);
7 Zo=sqrt(Z/Y);
8 C=round(real(Zo));
9 D=round(imag(Zo));
```

```

10 printf( '-Zo = %f + j(%f) ohms\n' ,C,D);
11 P=sqrt(Z*Y);
12 a=real(P);
13 a1=round(a*10000)/10000;
14 printf( '-Attenuation constant a = %f neper/km\n' ,a1)
15 ;
15 b=imag(P);
16 b1=round(b*10000)/10000;
17 printf( '-Phase constant b = %f radians/km' ,b1);

```

---

**Scilab code Exa 1.4** Calculating terminating impedance and attenuation and phase constant

```

1 clear;
2 clc;
3 f=1000;R=6;L=.0022;G=.25*(10^-6);C=.005*(10^-6);l
=100;
4 //value of C as taken in solution
5 w=2*pi*f;
6 Z=R+(%i*w*L);
7 Y=G+(%i*w*C);
8 Zo=sqrt(Z/Y);
9 C=real(Zo);
10 D=imag(Zo);
11 printf( '(i) Terminating impedance for which there
will be no reflection is Zo = %f /-%f ohms\n' ,fix
(abs(Zo)),round(((atan(imag(Zo),real(Zo))*180/%pi
)*10)/10));
12 P=sqrt(Z*Y);
13 a=real(P);
14 b=imag(P);
15 a1=a*l*8.66;
16 printf( '(ii)(a) Attenuation suffered while travelling
= %f db\n' ,a1);
17 Vp=(w/b)*(10^-5);v=round(Vp*100)/100;

```

```
18 printf( '( i )( b ) Phase velocity Vp = %f * 10^5 km/sec \
n' , v );
```

---

**Scilab code Exa 1.5** Calculating phase velocity and characteristic impedance and propagation constant and power delivered at receiving end

```
1 clear;
2 clc;
3 f=1000; R=10.4; L=.0037; G=.8*(10^-6); C=.00835*(10^-6);
4 l=1000; Vs=1;
5 w=2*pi*f;
6 Z=R+round((%i*w*L));
7 Y=G+(%i*w*C);
8 Zo=sqrt(Z/Y);
9 printf( '-Characteristic impedance is Zo = %f /-%f
ohms\n' , fix(abs(Zo)), round(((atan(imag(Zo),real(
Zo))*180/pi))));
```

10 P=sqrt(Z\*Y);

```
11 printf( '-Propagation constant P = %f + j(%f)\n' , fix(
real(P)*10^4)/10^4, round(imag(P)*10^4)/10^4);
12 b=imag(P);
13 Is=Vs/Zo; Vp=(w/b)*(10^-5); v=round(Vp*100)/100;
14 printf( '-Phase velocity Vp = %f * 10^5 km/sec\n' , v);
15 Ir=Is*exp(-P*l);
16 P=((abs(Ir))^2)*real(Zo);
17 printf( "-Power delivered at receiving end = %f micro
-watt" , P*(10^6));
```

---

**Scilab code Exa 1.6** Calculating characteristic impedance and propagation constant

```
1 clear;
```

```

2 clc;
3 f=5000/(2*pi);R=196;C=.09*(10^-6);L=.71*(10^-3);G
    =0;
4 //value of C as taken in solution
5 w=2*pi*f;
6 Z=R+(%i*w*L);
7 Y=G+(%i*w*C);
8 Zo=sqrt(Z/Y);
9 printf("-Characteristic impedance is Zo = %f /-%f
    ohms\n",fix(abs(Zo)),round(((atan(imag(Zo),real(
    Zo))*180/pi))*10)/10);
10 P=sqrt(Z*Y);F=fix(abs(P)*100)/100;
11 printf("-Propagation constant P = %f /-%f ohms\n",F
    ,((atan(imag(P),real(P))*180/pi)));
12 //the difference in result is due to erroneous
    value in textbook.
13 disp("The difference in result is due to erroneous
    value in textbook")

```

---

### Scilab code Exa 1.7 Calculating Zo and a and b and Vp

```

1 clc;
2 R=10.4;L=3.666*(10^-3);G=.08*(10^-6);C
    =.00835*(10^-6);w=5000;
3 //value of L and C as taken in solution
4 Z=R+(%i*w*L);
5 Y=G+%i*w*C;
6 Zo=sqrt(Z/Y);
7 printf("-Zo = %f /-%f ohms\n",fix(abs(Zo)),round((
    atan(imag(Zo),real(Zo))*180/pi))*10)/10);
8 P=sqrt(Z*Y);
9 a=real(P);
10 b=imag(P);
11 printf("-Attenuation constant a = %f neper/km\n",a);
12 printf("-Phase constant b = %f radians/km\n",b);

```

```

13 Vp=(w/b)*(10^-5);v=round(Vp*1000)/1000;
14 printf ('( ii )(b) Phase velocity Vp = %f * 10^5 km/sec \
n ',v);
15 //the difference in result of Zo is due to erroneous
   value in textbook.
16 disp("The difference in result of Zo is due to
   erroneous value in textbook")

```

---

### Scilab code Exa 1.8 Calculating characteristic impedance

```

1 clear;
2 clc;
3 R=65;L=1.6*(10^-3);C=.1*(10^-6);G=2.25*(10^-6);f
   =800;
4 w=5000;
5 Z=R+round(%i*w*L);
6 Y=G+%i*w*C;
7 Zo=sqrt(Z/Y);
8 printf ('-Characteristic impedance is Zo = %f / -%f
   ohms\n',(abs(Zo)),(((atan(imag(Zo),real(Zo))*180/
   %pi))));
```

---

### Scilab code Exa 1.9 Calculating phase velocity and attenuation

```

1 clear;
2 clc;
3 R=6;L=2*(10^-3);G=.5*(10^-6);C=.005*(10^-6);f=1000;l
   =100;
4 w=2*pi*f;
5 Z=R+(%i*w*L);
6 Y=G+%i*w*C;
7 Zo=sqrt(Z/Y);
8 P=sqrt(Z*Y);
```

---

```

9 a=real(P);
10 b=imag(P);
11 a1=fix(a*8.66*1*10^3)/10^3;
12 printf("-Attenuation suffered while travelling = %f
           db\n",a1);
13 Vp=fix(w/b)/10^3;
14 printf("-Phase velocity Vp = %f km/sec",Vp );

```

---

### Scilab code Exa 1.10 Calculating characteristic impedance

---

```

1 clc;
2 R=20;L=10*(10^-3);ins=0.1*(10^6);C=.1*(10^-6);w
   =5000; //ins=insulation resistance
3 G=1/ins;
4 Z=R+(%i*w*L);
5 Y=G+%i*w*C;
6 Zo=sqrt(Z/Y);
7 C=real(Zo);
8 D=imag(Zo);
9 printf('Input impedance Zo = %f /-%f ohms\n',(abs(Zo)
   )),round(((atan(imag(Zo),real(Zo))*180/%pi))*10)
   /10);
10 //the difference in result of Zo is due to erroneous
    value in textbook.
11 disp("The difference in result of Zo is due to
    erroneous value in textbook")

```

---

### Scilab code Exa 1.11 Calculating the voltage across load in terms of the sending end voltage

---

```

1 clear;
2 clc;
3 x=1;l=12;V=0.1;

```

```

4 V1=1-V;
5 //V1=ratio of voltage at 1km from the sending end to
   the voltage at sending end
6 P=-log(V1);
7 V2=exp(-P*1);
8 x=V2*100;x1=round(x*100)/100;
9 //x=ratio of voltage across the load impedance to
   the voltage at sending end
10 printf("Voltage across the load impedance is %f
           percentage of the sending end voltage",x1);

```

---

**Scilab code Exa 1.12** Calculating dc resistance and inductance and capacitance and ac resistance

```

1 clear;
2 clc;
3 a=.1;d=30;Ur=1;s=5.57*(10^7);e=1;f=30000;
4 //ur= relative magnetic permeability of conductor
   material ,
5 //s=conductivity of material
6 //e=relative dielectric constant of the material
7 L=(Ur+9.21*log10(d/a))*10^-7;
8 printf("-Inductance L = %f mH/km\n",L*10^3);
9 C=12.07*e/(log10(d/a));
10 printf("-Capacitance C = %f micromicrofarads/km\n",
        round(C*100)/100);
11 Rdc=2/(%pi*a*a*10^-2*10^-2*s);
12 Rdc1=Rdc*10^3;
13 printf("-D.C. resistance of line Rdc = %f ohms/km\n",
        round(Rdc1*100)/100);
14 Uo=4*%pi*10^-7;
15 //Uo=absolute permeability
16 Rac=(1/(a*10^-2))*(sqrt(f*Uo/(%pi*s)));
17 Rac1=Rac*10^3;
18 printf("-A.C. resistance of line = %f ohms/km",round(

```

```

    Rac1*100)/100);
19 //the difference in result of inductance and
   capacitance is due to erroneous value in textbook
   .
20 disp("The difference in result of inductance and
   capacitance is due to erroneous value in textbook
   ")

```

---

**Scilab code Exa 1.13** Calculating per km high and low frequency inductance and capacitance and dc and ac resistance

```

1 clear;
2 clc;
3 a=0.2;b=0.8;c=1;
4 a1=a*10^-2;b1=b*10^-2;c1=c*10^-2;s=5.57*(10^7);e
   =2.5;f=100*(10^3);
5 //e=relative dielectric constant of the material
6 //s=conductivity of copper
7 eo=(1/(36*pi))*10^-9;
8 Uo=4*pi*10^-7;
9 //Uo=absolute permeability
10 Llf=((((Uo/(2*pi))*log(b1/a1))+((Uo/(8*pi))*(((4*
      c1^4)/(((c1^2)-(b1^2))^2))*log(c1/b1))-((2*c1^2)
      /((c1^2)-(b1^2)))))*10^3;
11 printf("-Low frequency inductance = %f mH/km\n",
   round(Llf*(10^3)*10000)/10000);
12 Lhf=((Uo/(2*pi))*log(b1/a1))*10^3;
13 printf("-High frequency inductance = %f mH/km\n",
   round(Lhf*(10^3)*1000)/1000);
14 C=(2*pi*eo*e/(log(b1/a1)))*10^3;
15 printf("-Capacitance = %f microfarads/km\n",round(C
   *(10^6)*10000)/10000);
16 Rdc=((1/(\pi*s))*((1/(a1^2))+(1/((c1^2)-(b1^2)))))*
   *10^3;
17 printf("-D.c. resistance = %f ohms/km\n",round(Rdc

```

```

        *1000)/1000);
18 Rac=((sqrt(f*Uo/(4*pi*s)))*((1/a1)+(1/b1)))*10^3;
19 printf("-A.c. resistance = %f ohms/km",round(Rac*100)
/100);

```

---

**Scilab code Exa 1.14** Calculating line attenuation and velocity of propagation

```

1 clear;
2 clc;
3 Vd=10;l=2;b=20;f=796;
4 w=2*pi*f;
5 //Vd=voltage drop(in percentage),b=phase change(in
degrees)
6 V=(100-Vd)/100; //V=Vr/Vs;
7 a=(20*log10(1/V))/l;
8 printf("(i) Attenuation = %f db/km\n",round(a*1000)
/1000);
9 b1=(b/l)*(pi/180); //b1=phase constant/km(in
radians)
10 Vp=w/b1;
11 printf("(ii) The velocity of propagation = %d km/sec"
,Vp);

```

---

**Scilab code Exa 1.15** Calculating sending and receiving end voltages and currents and power

```

1 clear;
2 clc;
3 l=200;Vg=10;Zg=500;Zs=683-(%i*138);P=0.0074+(%i
*0.0356);Zo=Zs;
4 Is=Vg/(Zg+Zs);
5 modIs=abs(Is);

```

```

6 printf("-Sending end current = %f mA\n", round(modIs
    *(10^3)*100)/100);
7 Vs=Is*Zs;
8 modVs=abs(Vs);
9 printf("-Sending end voltge = %f V r.m.s.\n", round(
    modVs*100)/100);
10 Rs=real(Zs);
11 Ps=((modIs)^2)*Rs;
12 printf("-Sending end power = %f mW\n", round(Ps
    *(10^3)*100)/100);
13 Vr=modVs*exp(-P*l);
14 A=imag(-P*l);
15 printf("-Receiving end voltage = %f / - %f V\n", round(
    (abs(Vr)*100)/100,A));
16 Zr=Zs;
17 Ir=Vr/Zr;
18 modIr=abs(Ir);
19 printf("-Receiving end current = %f mA\n", round(
    modIr*(10^3)*100)/100);
20 Rr=Rs;
21 Pr=((modIr)^2)*Rr;
22 printf("-Receiving end power = %f mW", fix(Pr*(10^3)
    *100)/100);

```

---

# Chapter 2

## Open and Short Circuited Lines

**Scilab code Exa 2.1** Calculating  $Z_o$

```
1 clc;
2  $Z_{oc}=900*\exp\left(\frac{j\pi}{180/30}\right)$ ;  $Z_{sc}=400*\exp\left(\frac{j\pi}{180/10}\right)$ ;  $f=1.6*10^3$ ;
3  $Z_o=\sqrt{Z_{oc} \cdot Z_{sc}}$ ;
4  $A=\text{real}(Z_o)$ ;
5  $B=\text{imag}(Z_o)$ ;
6 printf(" $Z_o = %f + %f$  ohms", abs( $Z_o$ ), atan( $B/A$ )*180/ $\pi$ );
```

---

**Scilab code Exa 2.2** Calculating the line constants

```
1 clear;
2 clc;
3  $f=796$ ;  $Z_{oc}=328*\exp\left(\frac{j\pi}{180/29.2}\right)$ ;  $Z_{sc}=1548*\exp\left(\frac{j\pi}{180/6.8}\right)$ ;  $l=50$ ;
4  $Z_o=\sqrt{Z_{oc} \cdot Z_{sc}}$ ;
5  $C=\text{real}(Z_o)$ ;
6  $D=\text{imag}(Z_o)$ ;
```

```

7 printf("-Zo = %f / - %f ohms\n", fix(abs(Zo)), atan(D, C
) *180/%pi);
8 w=2*%pi*f;
9 Z1=sqrt(Zsc/Zoc);
10 A=real(Z1);
11 B=imag(Z1);
12 D=(1+A+(%i*B))/(1-(A+(%i*B)));
13 r=abs(D);
14 theta=atan((imag(D))/(real(D)))-%pi;
15 n=1;
16 P=(1/(2*1))*((log(r))+(%i*(theta+(2*n*%pi))));
17 E=real(P);
18 F=imag(P);
19 printf("-P = %f / - %f\n", round(abs(P)*10000)/10000,
round(atan(F,E)*180*100/%pi)/100);
20 Z=P*Zo;
21 R=real(Z);
22 L=(imag(Z))/w;
23 printf("-R = %f ohms/km\n", round(R*100)/100);
24 printf("-L = %f mH/km\n", round(L*(10^3)*100)/100);
25 Y=P/Zo;
26 G=real(Y);
27 C=(imag(Y))/w;
28 printf("-G = %f micro-mhos/km\n", round(G*(10^6)));
29 printf("-C = %f microfarads/km", round(C*(10^6)
*10000)/10000);

```

---

**Scilab code Exa 2.3** Calculating the received current and voltage

```

1 clear;
2 clc;
3 Zo=600; a=0.1; b=0.05; x=10; Is=20*(10^-3);
4 Vr=0;
5 printf("-Receiving end voltage Vr=0 because the
receiving end has been short circuited\n");

```

```

6 P=a+(%i*b);
7 Ir=Is/(cosh(10*P));
8 A=real(Ir);
9 B=imag(Ir);
10 printf("-Received current is Ir = %f /- %f mA ", 
    round(abs(Ir)*(10^3)*100)/100,fix(atan(B,A)
    *180*10/%pi)/10);

```

---

**Scilab code Exa 2.4** Determining Zo and a and b and primary constants of line

```

1 clear;
2 clc;
3 Zoc=1930*exp(%i*(%pi/(180/68.9)));Zsc=1308*exp(%i*(-
    %pi/(180/76.2)));l=8;w=5000;
4 Zo=sqrt(Zoc*Zsc);
5 C=real(Zo);
6 D=imag(Zo);
7 printf("-Zo = %f /- %f ohms\n",round(abs(Zo)),round(
    atan(D,C)*180*100/%pi)/100);
8 Z1=sqrt(Zsc/Zoc);
9 A=round(real(Z1)*1000)/1000;
10 B=round(imag(Z1)*1000)/1000;
11 D=(1+A+(%i*B))/(1-(A+(%i*B)));K=round((1+A+(%i*B))
    *100)/100;J=round((1-(A+(%i*B)))*10)/10;
12 phi1=atan(imag(K),real(K))+(%pi/4);
13 phi2=atan(imag(J),real(J));
14 phi3=phi1-phi2;
15 P=(1/(2*8))*(log(round(abs(K/J)*10)/10)+(%i*(round(
    phi3*10)/10+(6.28)))); 
16 printf(" -a = %f neper/km\n",fix(real(P)*100)/100);
17 printf(" -b = %f radians/km\n",fix(imag(P)*1000)
    /1000);
18 Z=P*Zo;
19 R=real(Z);

```

```

20 L=(imag(Z))/w;
21 printf(" -R = %f ohms/km\n", round(R*1000)/1000);
22 printf(" -L = %f mH/km\n", round(L*(10^6))/1000);
23 Y=P/Zo;
24 G=real(Y);
25 C=(imag(Y))/w;
26 printf(" -G = %f micro-mhos/km\n", -round(G*(10^9))
    /1000);
27 printf(" -C = %f microfarads/km", round(C*(10^9))
    /1000);
28 //the difference in result is due to erroneous
    value in textbook.
29 disp("The difference in result is due to erroneous
    value in textbook")

```

---

### Scilab code Exa 2.5 Calculating the line constants

```

1 clear;
2 clc;
3 w=5000; Zoc=1300*exp(%i*(%pi/(180/80))); Zsc=3200*exp(
    %i*(-%pi/(180/80))); l=40;
4 Zo=sqrt(Zoc*Zsc);
5 Z1=sqrt(Zsc/Zoc);
6 A=real(Z1);
7 B=imag(Z1);
8 D=(1+A+(%i*B))/(1-(A+(%i*B))); K=(1+A+(%i*B)); J=(1-(A
    +(%i*B)));
9 r=round(abs(D)*1000)/1000;
10 theta=round(atan((imag(D))/(real(D)))*10)/10;
11 P=(1/(2*l))*((log(r))+(%i*(theta+6.28)));
12 b=imag(P);
13 Z=P*Zo;
14 R=real(Z);
15 L=(imag(Z))/w;
16 printf("R = %f ohms\n", fix(R*100)/100);

```

```

17 printf(" L = %f mH/km\n", round(L*(10^6))/1000);
18 Y=P/Zo;
19 G=real(Y);
20 C=(imag(Y))/w;
21 printf(" G = %f micro-mhos/km\n", round(G*(10^8))
    /100);
22 printf(" C = %f micro-farads/km\n", round(C*(10^9))
    /1000);
23 //the difference in result of L and C is due to
    erroneous value in textbook.
24 disp("The difference in result of L and C is due to
    erroneous value in textbook")

```

---

**Scilab code Exa 2.6** Calculating Zo and P and line constants

```

1 clear;
2 clc;
3 Zoc=286*exp(%i*(-%pi/(180/40)));Zsc=1520*exp(%i* (%pi
    /(180/16)));l=50;f=700;
4 w=2*%pi*f;
5 Zo=sqrt(Zoc*Zsc);
6 S=real(Zo);
7 T=imag(Zo);
8 printf("-Characteristic impedance of transmission
    line is Zo = %f /- %f ohms\n", round(abs(Zo)*100)
    /100, atan(T,S)*180/%pi);
9 A=atanh(sqrt(Zsc/Zoc));
10 P=A/l;
11 U=real(P);
12 V=imag(P);
13 printf("-Propagation constant = %f /- %f\n", fix(abs(
    P)*1000)/1000, round(atan(V,U)*180*100/%pi)/100)
14 Z=P*Zo;
15 R=real(Z);
16 L=(imag(Z))/w;

```

```

17 printf("-R = %f ohms/km\n", round(R*100)/100);
18 printf("-L = %f mH/km\n", fix(L*(10^3)*100)/100);
19 Y=P/Zo;
20 G=real(Y);
21 C=(imag(Y))/w;
22 printf("-G = %f micromhos/km\n", fix(G*(10^6)*100)
    /100);
23 printf("-C = %f microfarads/km", fix(C*(10^6)*10^5)
    /10^5);

```

---

**Scilab code Exa 2.7** Calculating the series impedance and shunt admittance per km of line

```

1 clear;
2 clc;
3 Zoc=2500*exp(%i*(-%pi/(180/70)));Zsc=49*exp(%i* (%pi
    /(180/25)));l=1;
4 f=(8000)/(2*%pi);
5 w=2*%pi*f;
6 Zo=sqrt(Zoc*Zsc);
7 A=atanh(sqrt(Zsc/Zoc));
8 P=A/l;
9 P1=P*l/1000;
10 Z=P1*Zo;
11 printf("Series impedance of line is Z = %f /- %f
    ohms/km\n",round(abs(Z)*1000)/1000,atan(imag(Z),
    real(Z))*180/%pi);
12 Y=P1/Zo;
13 printf("Shunt admittance of line is Y = %f /- %f
    mhos/km",round(abs(Y)*10^6*10)/10,atan(imag(Y),
    real(Y))*180/%pi);

```

---

**Scilab code Exa 2.8** Calculating Zo and a and b

```

1 clear;
2 clc;
3 Zoc=2000*exp(%i*(-%pi/(180/80)));Zsc=20*exp(%i*(%pi
    /(180/20));l=0.5;w=10000;
4 // value of length of cable as taken in solution
5 Zo=sqrt(Zoc*Zsc);
6 C=real(Zo);
7 D=imag(Zo);
8 printf("-Zo = %f / - %f ohms\n",abs(Zo),atan(D,C)
    *180/%pi);
9 A=atanh(sqrt(Zsc/Zoc));
10 P=A/l;
11 a=real(P);
12 printf("-a = %f neper/km\n",fix(a*10000)/10000);
13 b=imag(P);
14 printf("-b = %f henry/km",round(b*10000)/10000);

```

---

**Scilab code Exa 2.9** Calculating output current when far end is short circuited

```

1 clear;
2 clc;
3 Vs=1;f=1000;l=150;Zo=692*exp(%i*(-%pi/(180/12)));a
    =0.0047;b=0.022;Vr=0;
4 P=a+(%i*b);
5 Ir=1/(Zo*sinh((a*l)+(b*l)));
6 C=real(Ir);
7 D=imag(Ir);
8 printf("Output current (in amperes)= %f / - %f mA",
    round(abs(Ir)*10^6)/1000,atan(D,C)*180/%pi);
9 //the difference in result is due to erroneous
    value in textbook.
10 disp("The difference in result is due to erroneous
    value in textbook")

```

---

### Scilab code Exa 2.10 Calculating Zo and a and b

```
1 clear;
2 clc;
3 f=20*(10^6);l=32;Zsc=17+(%i*19.4);Zoc=115-(%i*138);
4 Zo=sqrt(Zoc*Zsc);
5 X=real(Zo);
6 Y=imag(Zo);
7 printf("-Characteristic impedance = %f / - %f ohms\n"
    ,round(abs(Zo)),round(atan(Y,X)*180*10/%pi)/10);
8 Z1=sqrt(Zsc/Zoc);
9 A=real(Z1);
10 B=imag(Z1);
11 D=(1+A+(%i*B))/(1-(A+(%i*B)));
12 r=sqrt(((real(D))^2)+((imag(D))^2));
13 theta=atan((imag(D))/(real(D)));
14 n=6;
15 P=(1/(2*l))*((log(r))+(%i*(theta+(2*n*pi))));
16 b=imag(P);
17 a=real(P);
18 printf("-Attenuation factor = %f neper/m\n",round(a
    *10000)/10000);
19 printf("-Phase propagation factor = %f radians/m",
    round(b*100)/100);
```

---

### Scilab code Exa 2.11 Calculating Zo and a and b

```
1 clear;
2 clc;
3 f=20*(10^6);Zoc=1390;Zsc=4.61;l=5;
4 lo=(3*(10^8))/f; //lo=wavelength
5 Zo=sqrt(Zoc*Zsc);
```

```
6 printf("-Characteristic impedance = %f ohms\n", round
(Zo));
7 er=(lo/l)^2; //er=relative permittivity of
dielectric
8 printf("-Relative permittivity of dielectric = %f\n"
,er);
9 P=fix(((atanh(sqrt(Zsc/Zoc))/l)*10000)/10000;
10 a=P*8.686;
11 printf("-a = %f db/m\n", fix(a*10000)/10000);
12 Vp=(3*(10^8))/(sqrt(er)*10^8);
13 printf("-Velocity of propagation = %f * 10^8 m/sec",
Vp);
14 //the difference in result of attenuation constant
is due to erroneous value in textbook.
15 disp("The difference in result of the value of
attenuation constant is due to erroneous value in
textbook")
```

---

# Chapter 3

## Line with any Termination

**Scilab code Exa 3.1** Calculating sending end voltage

```
1 clear;
2 clc;
3 l=10; a=0.03; b=0.03; Vr=4; f=1000;
4 P=a+(%i*b);
5 Vs=Vr*(exp(P*l));
6 C=real(Vs);
7 D=imag(Vs);
8 printf("Sending end voltage is Vs = %f /- %f volts",
fix(abs(Vs)*100)/100,round(atan(D,C)*180/%pi));
```

---

**Scilab code Exa 3.2** Calculating rms value voltage and current

```
1 clear;
2 clc;
3 Zo=50; Vr=10; Ir=0; a=0;
4 B=%pi/4;
5 V=(Vr*cos(B))+(%i*(Ir*Zo*sin(B)));
6 I=(Ir*cos(B))+(%i*((Vr*sin(B))/Zo));
```

```

7 C=real(I);
8 D=imag(I);
9 printf("-R.m.s. voltage at the required distance is V
      = %f volts\n", round((V)*100)/100);
10 printf("-R.m.s. current at required distance is I =
        %f /_ %f Amps", round(abs(I)*1000)/1000, atan(D,C)
           *180/%pi);

```

---

**Scilab code Exa 3.3** Calculating the rms value of voltage and current

```

1 clc;
2 Zo=500*exp(%i*(-%pi/(180/43)));l=10;P=0.07+(%i*0.08)
   ;Vs=5;
3 V=Vs*(exp(-P*l));
4 I=V/Zo;
5 C=real(V);
6 D=imag(V);
7 E=real(I)*(10^3);
8 F=imag(I)*(10^3);
9 printf("-R.m.s. voltage at the required distance is V
      = %f /_ %f V\n", round(abs(V)*10)/10, round(atan(D
           ,C)*180*10/%pi)/10);
10 printf("-R.m.s. current at required distance is I =
        %f/_ %f mA", round(abs(I)*10^3), round(atan(F,E)
           *180*10/%pi)/10);

```

---

**Scilab code Exa 3.4** Calculating the input impedance of line

```

1 clear;
2 clc;
3 Zo=710*exp(%i*(%pi/(180/14)));l=100;P=0.007+(%i
   *0.028);Zr=300;

```

```

4 K=round(sinh(P*l)*100)/100; J=round(cosh(P*l)*100)
   /100;
5 Zin=Zo*((Zr*J)+(Zo*K))/((Zo*J)+(Zr*K));
6 C=real(Zin);
7 D=imag(Zin);
8 printf("Input impedance of line is Zin = %f / - %f
   ohms", abs(Zin), round(atan(D,C)*180*10/%pi)/10);
9 A=((Zr*J)+(Zo*K));
10 B=((Zo*J)+(Zr*K));
11 //the difference in result is due to erroneous
   value in textbook.
12 disp("The difference in result is due to erroneous
   value in textbook")

```

---

**Scilab code Exa 3.5** Calculating sending end impedance

```

1 clear;
2 clc;
3 Zo=55; Zr=115+(%i*75); n=1.183;
4 //value of Zr as taken in solution
5 m=(2*%pi*n)-(2*%pi);
6 Zin=Zo*(Zr+(%i*Zo*tan(m)))/(Zo+(%i*Zr*tan(m)));
7 C=real(Zin);
8 D=imag(Zin);
9 printf("Sending end impedance is Zin = %f + j(%f)
   ohms", fix(C*10)/10, fix(D*10)/10);

```

---

**Scilab code Exa 3.6** Calculating input impedance

```

1 clear;
2 clc;
3 Zo=50*exp(-%i*(%pi/(180/5))); a=0.001; b=%pi/1.8; Vr
   =0.5*exp(%i*(%pi/(180/30)));

```

```

4 l=100;x=4; //Vr=voltage reflection coefficient
5 modVr=abs(Vr);
6 A=modVr*exp(-2*a*(l-x));
7 Zin=Zo*(1+A)/(1-A);
8 C=real(Zin);
9 D=imag(Zin);
10 printf("Input impedance of transmission line = %f /_
    %f ohms",fix(abs(Zin)*100)/100,atan(D,C)*180/%pi
    );

```

---

**Scilab code Exa 3.7** Calculating the value of voltage reflection coefficient

```

1 clear;
2 clc;
3 Ka=0.2*exp(%i*(-%pi/(180/30)));d=1/12;
4 Kb=Ka/exp(%i*%pi*4*d);
5 printf("Desired value of voltage reflection
    coefficient = %f / %f",abs(Kb),atan(imag(Kb),
    real(Kb))*180/%pi);

```

---

**Scilab code Exa 3.8** Calculating the ratio of transmitter voltage to receiver voltage

```

1 clear;
2 clc;
3 Zo=710*exp(%i*(-%pi/(180/16)));a=0.01;b=0.035;l=100;
    Zr=300;
4 P=a+(%i*b);
5 V=(cosh(P*l))+((Zo/Zr)*sinh(P*l)); //V=Vs/Vr
6 modV=abs(V);
7 V1=log(modV)*8.686;
8 V2=log(modV);

```

```

9 printf("-Ratio of the transmitter voltage and the
    receiver voltage in nepers = %f\n", round((V2)
    *100)/100);
10 printf("-Ratio of the transmitter voltage and the
    receiver voltage in decibels = %f\n", round((V1)
    *100)/100);

```

---

**Scilab code Exa 3.9** Calculating the value of voltage reflection coefficient

```

1 clear;
2 clc;
3 Zo=692*exp(%i*(-%pi/(180/12 )));Zr=200;l=100;V=1;f
    =1000;
4 K=(Zr-Zo)/(Zr+Zo);
5 C=real(K);
6 D=imag(K);
7 printf("Voltage reflection coefficient = %f /_ %f",
    round(abs(K)*100)/100,round(atan(D,C)*180*10/%pi)
    /10);

```

---

**Scilab code Exa 3.10** Calculating power delivered at receiving end

```

1 clear;
2 clc;
3 f=1000;l=1000;R=10.4;L=0.00367;G=0.8*(10^-6);C
    =0.00835*(10^-6);Es=10;
4 // value of Es as taken in solution
5 w=2*%pi*f;
6 Z=R+round((%i*w*L));
7 Y=G+(%i*w*C);
8 Zo=sqrt(Z/Y);
9 P=sqrt(Z*Y);
10 Is=Es/Zo;

```

```

11 Ir=Is*exp(-P*l);
12 P=((abs(Ir))^2)*real(Zo);
13 printf("-Power delivered at receiving end = %f micro
    -watt",P*(10^6));
14 //the difference in result is due to erroneous
    value in textbook.
15 disp("The difference in result is due to erroneous
    value in textbook")

```

---

**Scilab code Exa 3.11** Calculating sending end current and receiving end current and voltage and efficiency of transmission

```

1 clear;
2 clc;
3 l=50; Zo=692*exp(%i*(-%pi/(180/12))); a=0.00755; b
    =0.0355; Zr=300; f=1000; Vs=10;
4 P=a+(%i*b);
5 Zin=Zo*((Zr*cosh(P*l))+(Zo*sinh(P*l)))/((Zo*cosh(P*l)
    ))+(Zr*sinh(P*l)));
6 Is=Vs/Zin*(10)^-1;
7 A=real(Is);
8 B=imag(Is);
9 printf("-Sending end current = %f /_ %f Amp\n",round
    (abs(Is)*10^5)/10^5,round(atan(B,A)*180*10/%pi)
    /10);
10 Vr=Vs*((cosh(P*l))-((Zo*sinh(P*l))/Zin));
11 C=real(Vr);
12 D=imag(Vr);
13 printf("-Receiving end voltage = %f /_ %f volts\n",
    round(abs(Vr)*10)/10,round(atan(D,C)*180/%pi));
14 Ir=Vr/Zr;
15 E=real(Ir);
16 F=imag(Ir);
17 printf("-Receiving end current = %f /_ %f Amp\n",
    round(abs(Ir)*1000)/1000,round(atan(F,E)*180/%pi))

```

```

        );
18 modIr=abs(Ir);
19 Rr=Zr;
20 Pr=((modIr)^2)*Rr;
21 theta=atan((imag(Zin))/(real(Zin)));
22 modIs=abs(Is);
23 Ps=Vs*modIs*cos(theta);
24 n=(Pr/Ps)*10;
25 printf("-Efficiency of transmission (in percentage)=
    %f", round(n));

```

---

**Scilab code Exa 3.12** Calculating the resistance and inductance of the series and shunt elements

```

1 clear;
2 clc;
3 l=10; Zo=280*exp(-%i*(%pi/(180/30))); P=0.08*exp(%i*(
    %pi/(180/40))); f=5000/(2*pi);
4 w=2*pi*f;
5 Z1=Zo*tanh(P*l/2);
6 Rs=real(Z1);
7 Ls=imag(Z1)/w;
8 printf("-Resistance of series element = %f ohms\n",
    fix(Rs));
9 printf("-Inductance of series element = %f mH\n",
    round(Ls*(10^3)*100)/100);
10 Z2=Zo/(sinh(P*l));
11 Rsh=real(Z2);
12 Csh=-imag(Z2)/w;
13 printf("-Resistance of shunt element = %f ohms\n",
    round(Rsh*10)/10);
14 printf("-Capacitance of shunt element = %f
    microfarads", fix(Csh*1000)/1000);

```

---

**Scilab code Exa 3.13** Determining the characteristic impedance and propagation constant

```
1 clear;
2 clc;
3 l=5; f=5000/(2*pi); Rs=175; Ls=10*(10^-3); Rsh=270; Csh
   =0.2*(10^-6);
4 w=2*pi*f;
5 Z1=(Rs+(%i*w*Ls)); //Z1=Z1/2
6 Z2=Rsh-(%i/(w*Csh));
7 t=sqrt((Z1)/((Z1)+(2*Z2)));
8 P=2*(atanh(t))/l;
9 A=real(P);
10 B=imag(P);
11 printf("Propagation constant = %f + %f per loop km\
n",round(A*100)/100,round(B*100)/100);
12 Zo=Z1/(tanh((P*l)/2));
13 C=real(Zo);
14 D=imag(Zo);
15 printf("Characteristic impedance = %f /- %f ohms",
   round(abs(Zo)*1000)/1000,round(atan(D,C)*180/pi)
   );
16 //the difference in result is due to erroneous
   value in textbook.
17 disp("The difference in result is due to erroneous
   value in textbook")
```

---

**Scilab code Exa 3.14** Calculating voltage and current

```
1 clear;
2 clc;
3 a=0; Zo=50; Vr=100; l=50; y=10; Ir=0; f=20*(10^6);
```

```

4 lo=300/f; //lo=lambda
5 b=2*pi/lo;
6 P=a+(%i*b);
7 V=(Vr*cosh(P*y))+(Ir*Zo*sinh(P*y));
8 printf("-Voltage at the required point = %f /- %f
    volts\n", abs(V), atan(imag(V),real(V))*180/pi);
9 I=((Vr/Zo)*sinh(P*y))+(Ir*cosh(P*y));
10 A=real(I);
11 B=imag(I);
12 printf("-Current at required point = %f /- %f Amps",
    round(abs(I)*1000)/1000, atan(B,A)*180/pi);

```

---

**Scilab code Exa 3.15** Calculating input impedance

```

1 clear;
2 clc;
3 Zo=600; Zr=%i*150; l=0.25; f=300*(10^6);
4 lo=300/f; //lo=lambda
5 b=2*pi/lo;
6 Zin=Zo*Zr/Zr;
7 A=real(Zin);
8 B=imag(Zin);
9 printf("Zin = %f + j (%f) ohms" ,A ,B);

```

---

**Scilab code Exa 3.16** Calculating power consumed in load

```

1 clear;
2 clc;
3 f=7.5*(10^3); R=2.6; L=2.4*(10^-3); C=.0078*(10^-6); G
    = .11*(10^-6); l=50; Vs=10;
4 w=2*pi*f;
5 Z=R+(%i*w*L);
6 Y=G+(%i*w*C);

```

```

7 Zo=sqrt(Z/Y);
8 P=sqrt(Z*Y);
9 Is=Vs/Zo;
10 Ir=Is*(exp(-P*l));
11 Ir1=abs(Ir);
12 Rr=real(Zo);
13 Pr=Ir1*Ir1*Rr;
14 printf("Power consumed in load is Pr = %f mW", round(
    Pr*(10^3)*10)/10);
15 //the difference in result is due to erroneous
   value in textbook.
16 disp("The difference in result is due to erroneous
   value in textbook")

```

---

**Scilab code Exa 3.17** Calculating the exact and approximate distance to fault

```

1 clear;
2 clc;
3 R=10.4;L=0.0036;C=0.0083*(10^-6);G=0;f1=1420;f2
   =1860;
4 Favg=(f1+f2)/2;
5 w=2*pi*Favg;
6 Z=R+(%i*w*L);
7 Y=G+(%i*w*C);
8 P=sqrt(Z*Y);
9 a=real(P);
10 b=imag(P);
11 v=w/b;
12 d=v/(2*(f2-f1));
13 printf("-Approximate distance = %f km\n", round(d));
14 w1=2*pi*f1;
15 Z1=R+(%i*w1*L);
16 Y1=G+(%i*w1*C);
17 P1=sqrt(Z1*Y1);

```

```

18 a1=real(P1);
19 b1=imag(P1);
20 v1=w1/b1;
21 w2=2*pi*f2;
22 Z2=R+(%i*w2*L);
23 Y2=G+(%i*w2*C);
24 P2=sqrt(Z2*Y2);
25 a2=real(P2);
26 b2=imag(P2);
27 v2=w2/b2;
28 D=(v1*v2)/(2*((v1*f2)-(v2*f1)));
29 printf("-Exact distance = %f km",round(D*10)/10);

```

---

**Scilab code Exa 3.18** Calculating the reflection factor and reflection loss

```

1 clear;
2 clc;
3 Z1=300; Zo=650*exp(%i*(-%pi/(180/12))); Z2=Zo;
4 Z=Z1+Z2;
5 K=(2*sqrt(Z1*abs(Z2)))/abs(Z);
6 printf("-Reflection factor = %f\n", round(K*1000)
    /1000);
7 L=20*(log10(1/K));
8 printf("-Reflection loss = %f db", round(L*100)/100);
9 //the difference in result of reflection loss is due
    to erroneous value in textbook.
10 disp("The difference in result of reflection loss is
        due to erroneous value in textbook")

```

---

**Scilab code Exa 3.19** Calculating reflection coefficient and input impedance

```

1 clear;
2 clc;

```

```

3 Zo=600;a=0.01;b=0.03;l=100;Zr=200;
4 P=a+(%i*b);
5 K=(Zr-Zo)/(Zr+Zo);
6 printf(" Reflection coefficient = %f / - %f\n",abs(K)
      ,atan(imag(K),real(K))*180/pi);
7 k=((abs(K))*exp(-2*P*l));
8 b=(1+k)/(1-k);
9 Zin=Zo*b;
10 C=real(Zin);
11 D=imag(Zin);
12 printf("Input impedance Zin = %f + j(%f) ohms",round
      (C*1000)/1000,round(D*100)/100);
13 //Zin has been wrongly calculated in the book

```

---

### Scilab code Exa 3.20 Finding reflection loss

```

1 clc;
2 Zo=632.8;Zr=80;
3 F=20*log10((2*Zr*Zo)/(Zo+Zr));
4 printf(" Reflection loss = %f db",round(F*100)/100);
5 //the difference in result is due to erroneous
   value in textbook.
6 disp("The difference in result is due to erroneous
   value in textbook")

```

---

# Chapter 4

## Power Lines

**Scilab code Exa 4.2** Determining equivalent pi network

```
1 clear;
2 clc
3 l=225; Zo=401-(%i*29); P=(0.148+(%i*2.06))*(10^-3);
4 Zs=Zo*sinh(P*l);
5 A=real(Zs);
6 B=imag(Zs);
7 printf("-Series branch of the equivalent network
        will have the impedance = %f + j(%f) ohms\n",
        round(A), round(B));
8 Zsh=Zo*cOTH(P*l/2);
9 C=real(Zsh);
10 D=imag(Zsh);
11 printf("-Shunt branch of the equivalent network will
        have the impedance = j(%f) ohms", round(D))
```

---

**Scilab code Exa 4.3** Calculating inductance per km of line

```
1 clear;
```

```

2 clc;
3 r=1.25; d1=75; d2=150;
4 r1=0.7718*r;
5 ds=nthroot((r1*r1*d1*d1),4);
6 dm=sqrt(d2*(sqrt((d2*d2)+(d1*d1)))); 
7 L=0.9212*log10(dm/ds);
8 printf("Total loop inductance = %f mH/loop km",round
(L*100)/100);

```

---

**Scilab code Exa 4.4** Calculating characteristic impedance and propagation constant

```

1 clear;
2 clc;
3 l=440; L=2.2*(10^-3); C=0.0136*(10^-6); R=0.120; G=0; f
    =60;
4 w=2*pi*f;
5 Z=R+(%i*w*L);
6 Y=G+(%i*w*C);
7 Zo=sqrt(Z/Y);
8 A=real(Zo);
9 B=imag(Zo);
10 printf("-Characteristic impedance = %f + j(%f) ohms\
n", round(A), round(B));
11 P=sqrt(Z*Y);
12 E=real(P)*10^4;
13 F=imag(P)*10^3;
14 printf("-Propagation constant = %f * 10^-4 + j(%f) *
10^-3 per km", fix(E*100)/100, fix(F*100)/100);

```

---

**Scilab code Exa 4.5** Calculating inductive reactance

```
1 clear;
```

```

2 clc;
3 f=50; r=5*(10^-3); x=.5; y=3; z=4.5; t=6; s=5;
4 r1=0.7788*r; // r1=CMR
5 Dab=round(sqrt((y^2)+(x^2))*1000)/1000;
6 Dab1=round(sqrt((y^2)+(s^2))*1000)/1000;
7 Daa=sqrt((t^2)+(z^2));
8 Dab2=Dab;
9 Dab3=Dab1;
10 dab=round(nthroot((Dab1*Dab3*Dab*Dab2),4)*100)/100;
11 dca=fix(nthroot((t*t*z*z),4)*100)/100;
12 ds1=nthroot((r1*r1*7.5*7.5),4);
13 ds2=nthroot((r1*r1*5.5*5.5),4);
14 ds3=ds1;
15 ds=round(nthroot((ds1*ds2*ds3),3)*1000)/1000;
16 La=fix(0.4606*log10(dca/ds)*100)/100;
17 X=2*3*f*La*10^-3;
18 printf("Inductive reactance = %f ohm/km/phase",X);

```

---

#### Scilab code Exa 4.6 Calculating capacitive susceptance

```

1 clear;
2 clc;
3 dia=2*(10^-2); f=50; d=3.5;
4 r=dia/2;
5 Cab=0.01207/(log10(d/r))*(10^-6);
6 Xc=1/(2*pi*f*Cab);
7 Bc=(1/Xc)*10^6;
8 printf("Capacitive susceptance per km = %f * 10^-6  
mho/km", round(Bc*100)/100);

```

---

#### Scilab code Exa 4.7 Determining the capacitance per km and charging current

```

1 clear;
2 clc;
3 dia=2*(10^-2); f=50; d1=3.5; V=66000;
4 r=dia/2;
5 Cn1=0.02414/(log10(d1/r))*(10^-6);
6 printf("(a) Capacitance per km = %f microfarads/km, to
neutral\n", fix(Cn1*(10^6)*10^5)/10^5);
7 Vn=V/sqrt(3);
8 Ic1=Vn*2*pi*f*Cn1;
9 printf("\tCharging current = %f mA/km\n", fix(Ic1
*(10^3)*10)/10);
10 d1=3.5; d2=4.5; d3=5.5;
11 Deq=nthroot(d1*d2*d3,3);
12 Cn2=0.02414/(log10(Deq/r))*(10^-6);
13 printf("(b) Capacitance per km = %f microfarads/km, to
neutral\n", fix(Cn2*(10^6)*10^5)/10^5);
14 Ic2=Vn*2*pi*f*Cn2;
15 printf("\tCharging current = %f mA/km", round(Ic2
*(10^3)));

```

---

# Chapter 5

## Telegraph and Telephone Lines

**Scilab code Exa 5.1** Calculating decrease in attenuation and cut off frequency

```
1 clear;
2 clc;
3 R=28; C=0.04*(10^-6); G=0; L=0; f=1600; s=2000; r=3.7; l
   =88*(10^-3);
4 Rc=R+(r/(s*(10^-3)));
5 Lc=L+(l/(s*(10^-3)));
6 Fc=1/(%pi*(sqrt(Lc*C)));
7 printf("-Cutoff frequency = %f Hz\n", round(Fc));
8 w=2*%pi*f;
9 a=sqrt(w*C*R/2);
10 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
11 A=(a-al)*8.686;
12 printf("-Decrease in attenuation = %f db/km", round(A
   *100)/100);
```

---

**Scilab code Exa 5.2** Calculating Zo and a and b and Vp

```

1 clear;
2 clc;
3 R=10.15;L=3.93*(10^-3);G=0.29*(10^-6);C
    =0.008*(10^-6);w=5000;r=7.3;l=246*(10^-3);
4 s=7.88;
5 Rc=R+(r/s);
6 Lc=L+(l/s);
7 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
8 printf("-a = %f neper/km\n",round(al*10000)/10000);
9 b=w*(sqrt(Lc*C));
10 printf("-b = %f radians/km\n",round(b*10^4)/10^4);
11 lo=2*pi/b; //lo=lambda
12 printf("-lo = %f km\n",round(lo*100)/100);
13 Vp=(w/b)*10^-4;
14 printf("-Vp = %f * 10^4 km/sec\n",round(Vp*100)/100)
    ;
15 Zo=(sqrt(Lc/C))*10^-3;
16 printf("-Zo = %f * 10^3 ohms",fix(Zo*100)/100);

```

---

**Scilab code Exa 5.3** Calculating modified Zo and a and Vp

```

1 clear;
2 clc;
3 R=10.4;L=3.67*(10^-3);G=0.8*(10^-6);C
    =0.00835*(10^-6);w=5000;r=7.3;l=246*(10^-3);
4 s=7.88;
5 Rc=R+(r/s);
6 Lc=L+(l/s);
7 Z=fix((Rc+(%i*w*Lc))*100)/100;
8 Y=G+(%i*w*C);
9 Zo=sqrt(Z/Y);
10 A=real(Zo);
11 B=imag(Zo);
12 P=sqrt(Z*Y);
13 a=real(P);

```

```

14 b=imag(P);
15 Vp=w/b;
16 phi=(round(atan(imag(Z),real(Z))*180*10/%pi)/10)-
    round(atan(imag(Y),real(Y))*180*10/%pi)/10;
17 printf("(i) Using exact method Zo = %f /- %f ohms\n",
    round(abs(Zo)),phi);
18 printf("\t\tta = %f neper/km\n",round(a*10^4)/10^4)
    ;
19 printf("\t\ttVp = %f * 10^4 km/sec\n",round(Vp
    *10^-2)/10^2);
20 Zo1=sqrt(Lc/C);
21 printf("(ii) Using approximate methos Zo = %f ohms\n"
    ,round(Zo1));
22 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
23 printf("\t\tta = %f neper/km\n",round(al*10^5)
    /10^5);
24 b1=w*(sqrt(Lc*C));
25 Vp1=1/(sqrt(Lc*C));
26 printf("\t\ttVp = %f * 10^4 km/sec\n",round(Vp1
    *10^-2)/10^2);

```

---

**Scilab code Exa 5.4** Calculating the phase velocity before and after velocity and decrease in attenuation and cut off frequency

```

1 clear;
2 clc;
3 R=10; C=0.04*(10^-6); L=0; G=0; f=1000; l=100*(10^-3); r
    =12; d=0.9;
4 w=2*pi*f;
5 a=sqrt(w*C*R/2);
6 b=sqrt(w*C*R/2);
7 Vp=(w/b)*10^-5;
8 printf("-Phase velocity before loading = %f * 10^5
    km/sec\n",fix(Vp*10)/10);
9 Rc=R+(r/d);

```

```

10 Lc=L+(1/d);
11 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
12 Vpl=(1/(sqrt(Lc*C)))*10^-4;
13 printf("-Phase velocity after loading = %f * 10^4 km
/sec\n",Vpl);
14 A=a-al;
15 printf("-Decrease in attenuation = %f neper/km\n",
round(A*10000)/10000);
16 Fc=1/(%pi*(sqrt(Lc*C*d)));
17 printf("-Cutoff frequency = %f kHz",round(Fc*(10^-3)
*1000)/1000);

```

---

**Scilab code Exa 5.5** Calculating attenuation and cut off frequency

```

1 clear;
2 clc;
3 R=40; C=0.06*(10^-6); L=0; G=0; r=15; l=80*(10^-3); d=1.2;
    f=(5/(2*pi))*10^3;
4 Rc=R+(r/d);
5 Lc=L+(1/d)
6 w=2*pi*f;
7 Z=Rc+(%i*w*Lc);
8 Y=G+(%i*w*C);
9 P=sqrt(Z*Y);
10 a=real(P);
11 printf("(a) Attenuation constant a = %f neper/km\n",
round(a*1000)/1000);
12 Fc=1/(%pi*(sqrt(l*C*d)));
13 printf("(b) Cutoff frequency = %f kHz",round(Fc
*(10^-3)*1000)/1000);

```

---

**Scilab code Exa 5.6** Calculating attenuation and highest frequency of transmission

```

1 clear;
2 clc;
3 R=25; C=0.04*(10^-6); L=0.6*(10^-3); G=0; l=45*(10^-3); r
    =20; d=1; f=1000;
4 Rc=R+(r/d);
5 Lc=L+(l/d)
6 w=2*pi*f;
7 Z=Rc+(%i*w*Lc);
8 Y=G+(%i*w*C);
9 P=sqrt(Z*Y);
10 a=real(P);
11 printf("-Attenuation per km line = %f neper/km\n",
    round(a*10^5)/10^5);
12 Fc=1/(%pi*(sqrt(Lc*C*d)));
13 printf("-Highest frequency of transmission will be
    cutoff frequency = %f kHz", round(Fc*(10^-3)*10^3)
    /10^3);

```

---

**Scilab code Exa 5.7** Calculating the value of  $Z_0$  and  $a$  and  $V_p$  after loading

```

1 clear;
2 clc;
3 R=42.1; L=1*(10^-3); G=1.5*(10^-6); C=0.062*(10^-6); f
    =796; r=2.7; l=31*(10^-3);
4 d=1.135;
5 Rc=R+(r/d);
6 Lc=round((L+(l/d))*1000)/1000;
7 Zo=sqrt(Lc/C);
8 printf("-Zo after loading = %f ohms\n", round(Zo));
9 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
10 printf("-a after loading = %f neper/km\n", round(al
    *10^4)/10^4);
11 Vp=1/(sqrt(Lc*C));
12 printf("-Approximate value of Vp = %f km/sec", fix(Vp)

```

```
) );
```

---

### Scilab code Exa 5.8 Calculating cut off frequency and attenuation

```
1 clear;
2 clc;
3 R=30; L=0; G=0; C=7000*(10^-12); f=3/(2*pi)*(10^3); r
    =35; l=70*(10^-3);
4 d=1;
5 Rc=R+(r/d);
6 Lc=L+(l/d);
7 Fc=1/(%pi*(sqrt(Lc*C*d)));
8 printf("-Approximate value of highest frequency = %f
kHz\n", round(Fc*(10^-3)*100)/100);
9 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
10 printf("-Approximate value of attenuation per km
after = %f neper/km", round(al*10^4)/10^4);
```

---

### Scilab code Exa 5.9 Calculating Zo and a and b

```
1 clear;
2 clc;
3 R=44; L=0.001; G=1*(10^-6); C=0.065*(10^-6); f=1600; r
    =3.7; l=88*(10^-3);
4 d=1.136;
5 w=2*pi*f;
6 Rc=R+(r/d);
7 Lc=L+(l/d);
8 Zo=sqrt(Lc/C);
9 printf("-Approximate value of Zo = %f ohms\n", round(
    Zo*100)/100);
10 al=(((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C)))*8.686;
```

```

11 printf("-Approximate value of a = %f db/km\n",fix(al
    *1000)/1000);
12 b=w*(sqrt(Lc*C));
13 printf("-Approximate value of b = %f radians/km",fix
    (b*1000)/1000);
14 //the difference in result of Zo is due to erroneous
    value in textbook.
15 disp("The difference in result of Zo is due to
    erroneous value in textbook")

```

---

**Scilab code Exa 5.10** Calculating length of line for a given attenuation

```

1 clear;
2 clc;
3 a=0.005;f=1000;al=0.05;att=10 //att=given
    attenuation in db
4 lo=att/(a*8.686);
5 printf("-For the open wire line the required length
    is lo = %f km\n",round(lo*10)/10);
6 lc=att/(al*8.686);
7 printf("-For the cable the required length is lc =
    %f km",fix(lc*100)/100);

```

---

**Scilab code Exa 5.11** Calculating cutoff frequency and attenuation and phase velocity

```

1 clear;
2 clc;
3 R=20;C=0.03*(10^-6);L=0;G=0;r=18.2;l=78*(10^-3);d
    =2.1;f=3000/(2*pi);
4 Rc=R+(r/d);
5 Lc=L+(l/d);
6 Fc=1/(%pi*(sqrt(Lc*C*d)));

```

```

7 printf("( i ) Cutoff frequency = %f kHz\n", round(Fc
     *(10^-3)*100)/100);
8 al=((Rc/2)*sqrt(C/Lc))+((G/2)*sqrt(Lc/C));
9 printf("( ii ) Attenuation per km = %f neper/km\n", fix(
     al*10000)/10000);
10 Vp1=(1/(sqrt(Lc*C)))*10^-4;
11 printf("( iii ) Phase velocity = %f * 10^4 km/sec", fix(
     Vp1*1000)/1000);
12 //the difference in result of attenuation per km and
   phase velocity is due to erroneous value in
   textbook.
13 disp("The difference in result of attenuation per km
   and phase velocity is due to erroneous value in
   textbook")

```

---

**Scilab code Exa 5.12** Finding the value of the loading coil inductance and the interval at which it needs to be placed

```

1 clear;
2 clc;
3 R=80; C=0.06*(10^-6); L=0; G=0; f=2500; al=0.04; ratio=40;
4 fc=2*f;
5 //ratio=ratio off resistance to inductance of
   loading coil
6 A=2/(3.14*3.14*C*4*f*f); //A=Lc*d
7 B=al/(%pi*f*1.414*C/2);
8 C=%pi*f*1.414*C/2;
9 y=poly([ratio*C*100*A -al*100 80*100*C], "x", "coeff");
10 a=roots(y);
11 b=round(a(1,1)*100)/100;
12 Lo=round((A/b)*1000)/1000;
13 printf("Adding %f Henry coils at intervals of %f km
   is the practical and economically possible
   solution.", Lo, b)

```

---

**Scilab code Exa 5.13** Calculating rate of transmission of information

```
1 clear;
2 clc;
3 B=3000; //B=band width
4 D=30; //D=ratio of signal power to noise power in db
5 P=10^(D/10); // P=converting D into a numerical
                 ratio
6 A=fix(log2(1+P)*100)/100
7 C=B*A;
8 printf("Rate of transmission of information = %f
           bits/sec",C);
```

---

**Scilab code Exa 5.14** Calculating a and b and cut off frequency

```
1 clear;
2 clc;
3 R=55; L=0.6*(10^-3); G=1*(10^-6); C=0.04*(10^-6); f=800;
      r=8; l=0.1; d=2.5; //value of l/loading coil
      inductance) as taken in solution
4 w=2*pi*f;
5 Z=round(R+(%i*w*L));
6 Y=G+(%i*w*C);
7 Zo=sqrt(Z/Y);
8 P=round(sqrt(Z*Y)*10^4)/10^4;
9 Zc=r+(%i*w*l);
10 A=fix(((cosh(P*d))+(Zc*(sinh(P*d))/(2*Zo)))*10^3)
     /10^3;
11 P1=(acosh(A))/d;
12 al=real(P1);
13 bl=imag(P1);
```

```

14 printf("New value of attenuation constant = %f neper
        /km\n", round(al*100)/100);
15 printf(" New value of phase constant = %f rad/km\n",
        round(bl*1000)/1000);
16 Lc=L+(1/(d*10^3));
17 Fc=1/(3.14*(sqrt(Lc*C*d)));
18 printf(" Cutoff frequency = %f * 10^4 Hz", round(Fc
        *10^-2)/10^2);
19 //the difference in result is due to erroneous
    value in textbook.
20 disp("The difference in result is due to erroneous
    value in textbook")

```

---

**Scilab code Exa 5.15** Calculating wavelength of line

```

1 clear;
2 clc;
3 R=10;C=0.008*(10^-6);l=60; //value of R as taken in
    solution
4 Rt=R*l; //Rt=total resistance
5 Ct=C*l; //Ct=total capacitance
6 f=1600 //assumption
7 w=2*pi*f;
8 b=sqrt(f*Rt*Ct/2);
9 lo=2*pi/b;
10 printf("Wavelength of line = %f metres",fix(lo*100)
        /100);

```

---

**Scilab code Exa 5.16** Calculating the value of attenuation

```

1 clear;
2 clc;

```

```

3 R=45;L=1.2*(10^-3);G=5*(10^-6);C=0.065*(10^-6);w
    =20000;l=22*(10^-3);s=1.1;
4 pf=0.005 // pf=power factor // value of pf as taken in
    solution
5 r=pf*w*L;
6 Rc=R+(r/s);
7 Lc=L+(l/s);
8 P=sqrt((Rc+(%i*w*Lc))*(G+(%i*w*C)));
9 theta=round(atan(imag(P),real(P))*180/%pi);
10 a=abs(P)*cos(theta*%pi/180);
11 printf("Attenuation constant of line = %f neper/km",
    fix(a*10^4)/10^4);

```

---

**Scilab code Exa 5.17** Calculating potential at mid point

```

1 clear;
2 clc;
3 l=100;R=10;G=10^-5;Vs=40;Zr=0;
4 Zo=sqrt(R/G);
5 P=sqrt(R*G);
6 Zin=Zo*(Zr+(Zo*tanh(P*l)))/(Zo+(Zr*tanh(P*l)));
7 Is=Vs/Zin;
8 V=(Vs*(cosh(P*l)))-(Is*Zo*(sinh(P*l)));
9Vm=2*V;
10 printf("Potential at mid point = %f volts",Vm);
11 //the difference in result is due to erroneous
    value in textbook.
12 disp("The difference in result is due to erroneous
    value in textbook")

```

---

# Chapter 6

## Ultrahigh Frequency Lines

**Scilab code Exa 6.1** Calculating complex reflection coefficient and terminal impedance

```
1 clear;
2 clc;
3 f=200*(10^6);s=4.48;ymin=6;Zo=300; //s=standing wave
   ratio
4 lo=300/(f*(10^-6)); //where f is in megahertz ,lo=
   wavelength of wave in air
5 b=2*pi/lo;
6 phi=(2*b*ymin*(10^-2))-%pi;
7 ampK=(s-1)/(s+1); //ampK=amplitude of the reflection
   coefficient
8 K=ampK*(exp(%i*phi));
9 A=real(K);
10 B=imag(K);
11 printf("-Complex reflection coefficient= %f / - %f\n"
   ,round(abs(K)*1000)/1000,round(atan(B,A)*180/%pi)
   );
12 ZR=(Zo*(1+K))/(1-K);
13 C=real(ZR);
14 D=imag(ZR);
15 printf("-Terminating impedance of line = %f / - %f
```

```
ohms" ,abs(ZR) ,round(atan(D,C)*180*10/%pi)/10);
```

---

**Scilab code Exa 6.2** Calculating value of load impedance

```
1 clear;
2 clc;
3 Zo=75;s=3;d=1/5;
4 B=2*%pi*d; //B=b*ymax where ymax=position of the
               current maxima which is 1/5th
               wavelength away from the load(here)
5 phi=2*B;
6 ampK=(s-1)/(s+1); //ampK=amplitude of the reflection
                      coefficient
7 K=ampK*(exp(%i*phi));
8 ZR=round(((Zo*(1+K))*100)/100)/(round((1-K)*1000)
   /1000);
9 C=real(ZR);
10 D=imag(ZR);
11 printf("Load impedance = %f /- %f ohms",round(abs(ZR)
   )*10)/10,round(atan(imag(ZR),real(ZR))*180*100/
   %pi)/100);
12 //the difference in result is due to erroneous
   value in textbook.
13 disp("The difference in result is due to erroneous
   value in textbook")
```

---

**Scilab code Exa 6.3** Calculating VSWR and position of voltage minimum nearest to load

```
1 clear;
2 clc;
3 Zo=50;f=300*(10^6);ZR=50+(%i*50);
```

```

4 lo=300/(f*(10^-6)); //where f is in megahertz ,lo=
    wavelength of wave in air
5 K=(ZR-Zo)/(ZR+Zo);
6 ampK=sqrt((real(K)^2)+(imag(K)^2));
7 S=(1+ampK)/(1-ampK);
8 printf("-VSWR = %f\n",round(S*100)/100);
9 phi=atan(imag(K)/real(K));
10 ymax=phi*lo/(2*2*pi);
11 ymin=ymax+(lo/4);
12 printf("-Position of voltage minimum nearest load =
    %f metres",round(ymin*10000)/10000);

```

---

#### Scilab code Exa 6.4 Calculating standing wave ratio

```

1 clear;
2 clc;
3 Zo=400; ZRa=70, ZRb=800; ZRc=650-(%i*475);
4 Ka=(ZRa-Zo)/(ZRa+Zo);
5 ampKa=sqrt((real(Ka)^2)+(imag(Ka)^2));
6 Sa=(1+ampKa)/(1-ampKa);
7 printf("(a) Standing wave ratio = %f\n",round(Sa*100)
    /100);
8 Kb=(ZRb-Zo)/(ZRb+Zo);
9 ampKb=sqrt((real(Kb)^2)+(imag(Kb)^2));
10 Sb=(1+ampKb)/(1-ampKb);
11 printf("(b) Standing wave ratio = %f\n",Sb);
12 Kc=(ZRc-Zo)/(ZRc+Zo);
13 ampKc=sqrt((real(Kc)^2)+(imag(Kc)^2));
14 Sc=(1+ampKc)/(1-ampKc);
15 printf("(c) Standing wave ratio = %f",round(Sc*1000)
    /1000);

```

---

#### Scilab code Exa 6.5 Calculating value of load impedance

```

1 clear;
2 clc;
3 s=2; f=300*(10^6); lo=1; ymin=0.8; //lo=wavelength
4 ampK=(s-1)/(s+1);
5 b=2*pi/lo;
6 phi=(2*b*ymin)-pi;
7 K=ampK*(exp(%i*pi));
8 Zr=(1+K)/(1-K);
9 A=real(Zr);
10 B=imag(Zr);
11 printf("Value of load impedance = %f /- %f ohms",
    round(abs(Zr)*10)/10,fix(atan(B,A)*180*100/pi)
    /100);
12 //the difference in result is due to erroneous
    value in textbook.
13 disp("The difference in result is due to erroneous
    value in textbook")

```

---

**Scilab code Exa 6.11** Calculating point of attachment and length of stub

```

1 clear;
2 clc;
3 ZR=100; Zo=600; f=100*(10^6);
4 lo=300/(f*(10^-6)); //lo=wavelength
5 Ls=(lo/(2*pi))*(atan(sqrt(ZR/Zo)));
6 printf("-Point of attachment = %f cms\n",round(Ls
    *(10^2)*10)/10)
7 Lt=(lo/(2*pi))*(%pi+(atan((sqrt(ZR*Zo))/(ZR-Zo))));
8 printf("-Length of the short circuited stub = %f cms
    ",round(Lt*(10^2)));

```

---

**Scilab code Exa 6.14** Calculating point of attachment and length of stub

```

1 clear;
2 clc;
3 f=10^9;K=0.5*exp(%i*(30)/(180/%pi));
4 lo=300/(f*(10^-6)); //lo=wavelength
5 ampK=abs(K);
6 phi=atan(imag(K)/real(K));
7 Ls=(lo/(4*pi))*(phi+pi-acos(ampK));
8 printf("-Position of stub = %f cm\n",Ls*(10^2));
9 Lt=(lo/(2*pi))*(atan(sqrt(1-(ampK*ampK)))/(2*ampK))
    ;
10 printf("-Length of the stub = %f cm",round(Lt*(10^2)
    *100)/100);

```

---

**Scilab code Exa 6.15** Calculating point of attachment and length of stub

```

1 clear;
2 clc;
3 Zo=400;ZR=200-(%i*100);lo=3; //lo=wavelength
4 //value os Zo as taken in solution
5 K=(ZR-Zo)/(ZR+Zo);
6 ampK=abs(K);
7 phi=%pi + atan(imag(K)/real(K));
8 Ls=(lo/(4*pi))*(phi+pi-acos(ampK));
9 printf("Shortest distance from the lead to the stub
        location = %f metres\n",round(Ls*100)/100);
10 Lt=(lo/(2*pi))*(atan(sqrt(1-(ampK*ampK)))/(2*ampK))
    ;
11 printf("Length of the short circuited stub = %f
        metres",fix(Lt*10)/10);

```

---

**Scilab code Exa 6.17** Calculating the dimensions of a quarter wave line

```
1 clear;
```

```

2 clc;
3 ZR=300; s=9; d=0.1
4 r=d/2;
5 Zof=276*log10(s/r);
6 Zoq=sqrt(ZR*Zof);
7 do=(s*2)/10^(Zoq/276);
8 printf("Diameter of wire used = %f cm",fix(do*10)
    /10);

```

---

**Scilab code Exa 6.18** Designing a quarter wave transformer

```

1 clear;
2 clc;
3 Zin=36; Zt=500; f=40; x=0.97
4 Zo=sqrt(Zin*Zt);
5 A=10^(Zo/276);
6 lo=300/f;
7 l1=lo*x/4;
8 printf("The characteristic impedance of the
    transmission line = %f ohms\n",round(Zo));
9 printf("The spacing between the conductors shud be
    %f times the radius of the conductor\n",round(A))
    ;
10 printf("The length of the quarter wavelength
    transformer must be %f metres",round(l1*100)/100)
    ;

```

---

**Scilab code Exa 6.19** Designing a single stub matching given system to eliminate standing wave ratio

```

1 clear;
2 clc;
3 f=150; S=4.48; Ymin=6*(10^-2);

```

```

4 lo=300/(f); //lo=wavelength
5 b=(2*pi)/lo;
6 phi=round(((2*b*Ymin)-pi)*100)/100;
7 phi1=-phi;
8 ampK=round(((S-1)/(S+1))*10)/10;
9 Ls=(lo/(4*pi))*(phi1+pi-round(acos(ampK)));
10 printf("Point of attachment = %f cm\n",round(Ls
    *(10^4))/100);
11 Lt=(lo/(2*pi))*(atan(sqrt(1+(ampK*ampK)))/(2*ampK))
    ;
12 printf("Length of the stub = %f cm",round(Lt*(10^4))
    /100);
13 //the difference in result is due to erroneous
    value in textbook.
14 disp("The difference in result is due to erroneous
    value in textbook")

```

---

**Scilab code Exa 6.20** calculating frequency and terminated impedance

```

1 clear;
2 clc;
3 s=3.3; Zo=300; l=15;
4 ampK=round(((s-1)/(s+1))*100)/100;
5 Zr=Zo*(1+ampK)/(1-ampK);
6 printf("-Terminated impedance = %f ohms\n",fix(Zr));
7 lo=(2*2*pi*l*(10^-2))/pi; //lo=wavelength
8 f=300/lo;
9 printf("-Frequency = %f MHz",f);

```

---

**Scilab code Exa 6.21** Calculating load and input impedance

```

1 clear;
2 clc;

```

```

3 Ymin=18*(10^-2);S=2.5;dmin=20*(10^-2);l=52*(10^-2);
   Zo=300;
4 //dmin=distance between adjacent voltage minimas
5 ampK=round(((S-1)/(S+1))*100)/100;
6 ZR=fix(Zo*(1+ampK)/(1-ampK));
7 printf("Input impedance = %f ohms\n",ZR);
8 lo=2*dmin; //lo=wavelength
9 b=(2*pi)/lo;
10 phi=(2*b*Ymin)-pi;
11 theta=-fix(phi-(2*b*l));
12 Zm=Zo*(round((1+(ampK*exp(%i*theta)))*100)/100)/(
   round((1-(ampK*exp(%i*theta)))*100)/100);
13 printf("Load impedance = %f + j(%f) ohms",round(real
   (Zm*100))/100,round(imag(Zm*100))/100);
14 //the difference in result is due to erroneous
   value in textbook.
15 disp("The difference in result is due to erroneous
   value in textbook")

```

---

# Chapter 7

## Waveguides

**Scilab code Exa 7.1** Calculating critical and guide wavelengths

```
1 clear;
2 clc;
3 c=3*(10^8);
4 f=3000*(10^8);
5 lo=c/f;
6 l=lo*(10^4);
7 m=1;n=0;a=7.62;
8 lc=2*a;
9 printf("-Critical wavelength = %f cm\n",lc);
10 lg=sqrt((1*l*lc*lc)/((lc*lc)-(l*l)));
11 printf("-Guide wavelength = %f cm",round(lg*10)/10);
```

---

**Scilab code Exa 7.2** Finding the value of the dominant mode

```
1 clear;
2 clc
3 a=3;
4 lc=2*a;
```

```

5 Zs=500;n=377;c=3*(10^8);
6 lo=sqrt(1-((n/Zs)^2))*lc;
7 f=c/lo;
8 f1=f/(10^7);
9 printf("Frequency of dominant mode = %f GHz",round(
    f1*100)/100);

```

---

**Scilab code Exa 7.3** Calculating the cut off wavelength and guide wavelength and group and phase velocities and the characteristic wave impedance

```

1 clear;
2 clc
3 a=4.5;b=3;f=9*(10^9);c=3*(10^8);n=377
4 lo=c/f;
5 l=lo*(10^2);
6 lc=2*a;
7 printf("(i) Cutoff wavelength = %f cm\n",lc);
8 lg=l /(sqrt(1-((l/lc)^2)));
9 printf("(ii) Guide wavelength = %f cm\n",fix(lg*100)
    /100);
10 Vp=(lg/l)*c*10^-8;
11 printf("(iii) Phase velocity = %f * 10^8 m/sec\n",fix
    (Vp*100)/100);
12 Vg=(l/lg)*c*10^-8;
13 printf(" Group velocity = %f * 10^8 m/sec\n",round
    (Vg*100)/100);
14 Z=n/(sqrt(1-((l/lc)^2)));
15 printf("(iv) Characteristic impedance = %f ohm",fix(Z
));

```

---

**Scilab code Exa 7.4** Calculating voltage attenuation

```
1 clear;
```

```

2 clc;
3 a=1; c=3*(10^8); f=(10^9); d=25;
4 lc=2*a;
5 lo=c/f;
6 l=lo/(10^2);
7 att=(54.55/lc)*d;
8 printf("Total attenuation = %f db", round(att*100)
    /100);
9 //the difference in result is due to erroneous
   value in textbook.
10 disp("The difference in result is due to erroneous
      value in textbook")

```

---

**Scilab code Exa 7.5** Calculating group and phase velocities and phase constant

```

1 clear;
2 clc;
3 c=3*(10^8); f=3000*(10^6); a=.0722;
4 lo=c/f;
5 lc=2*a;
6 lg=lo/(sqrt(1-((lo/lc)^2)));
7 Vp=(lg/lo)*c*10^-8;
8 printf("-Phase velocity Vp = %f * 10^8 m/sec\n",
    round(Vp*10)/10);
9 Vg=(lo/lg)*c*10^-8;
10 printf("-Group velocity Vg = %f * 10^8 m/sec\n",
    round(Vg*10)/10);
11 b=(2*pi)/lg;
12 printf("-Phase constant = %f radians/m", round(b));

```

---

**Scilab code Exa 7.6** Calculating cut off frequencies

```

1 clear;
2 clc
3 d=5; c=3*(10^8) ;
4 lo=1.706*d;
5 f=c/lo;
6 ff=f/(10^7);
7 printf("( i ) Cutoff frequency for TE11 = %f GHz\n",
     round(ff*100)/100);
8 l=1.306*d;
9 fc=c/l;
10 ffc=fc/(10^7);
11 printf("( ii ) Cutoff frequency for TE01 = %f GHz" ,
     round(ffc*10)/10);

```

---

**Scilab code Exa 7.7** Calculating cut off wavelength and guide wavelength and characteristic wave impedance

```

1 clear;
2 clc;
3 c=3*(10^8); f=8*(10^9); r=2.5; h=1.84; n=377;
4 l=c/f;
5 lo=l*(10^2);
6 lc=2*pi*r/h;
7 printf("-Cutoff wavelength = %f cm\n", round(lc*100)
    /100);
8 lp=lo/(sqrt(1-((lo/lc)^2)));
9 printf("-Guide wavelength = %f cm\n", round(lp*100)
    /100);
10 Zo=n/(sqrt(1-((lo/lc)^2)));
11 printf("-Characteristic wave impedance = %f ohm", fix
    (Zo*10)/10);

```

---

# Chapter 8

## Transmission Lines Measurements

**Scilab code Exa 8.1** Calculating the value of load impedance

```
1 clear;
2 clc;
3 K=0.5*exp(%i*(30)/(180/%pi));
4 Zo=100;
5 Zl=Zo*(1+K)/(1-K);
6 A=real(Zl);
7 B=imag(Zl);
8 printf("Load impedance = %f /- %f ohms",fix(abs(Zl))
    ,round(atan(B,A)*180/%pi));
```

---

**Scilab code Exa 8.2** Calculating insertion loss

```
1 clear;
2 clc;
3 P1=67;P2=30;
4 L=10*log10(P1/P2);
```

```
5 printf("Insertion loss = %f db",fix(L*100)/100);
```

---

### Scilab code Exa 8.3 Calculating insertion loss

```
1 clear;
2 clc;
3 S=2;
4 Lr=10*log10(((S+1)^2)/(4*S));
5 Ld=10*log10((S+1)/(S-1));
6 L=Ld+Lr;
7 printf("Insertion loss = %f db",round(L*100)/100);
8 //the difference in result is due to erroneous
   value in textbook.
9 disp("The difference in result is due to erroneous
   value in textbook")
```

---

# Chapter 9

## Artificial Lines

Scilab code Exa 9.1 Designing an artificial line

```
1 clear;
2 clc;
3 R=10.4;L=3.67*(10^-3);G=0.8*(10^-6);C
    =0.00835*(10^-6);bmax=0.1;
4 f=5.5*(10^3); //artificial line will be designed fr
    highest frequency of operation
5 w=2*%pi*f;
6 Z=R+(%i*w*L);
7 Y=G+(%i*w*C);
8 P=sqrt(Z*Y);
9 b=imag(P);
10 l=bmax/b;
11 Zs=Z*l/2;
12 Zsh=1/(Y*l);
13 Zr=Y*l;
14 R1=real(Zs);
15 printf("-R1/2 = %f ohms\n",round(R1*10)/10);
16 L1=imag(Zs)/w;
17 printf("-L1/2 = %f mH\n",fix(L1*(10^3)*100)/100);
18 C2=imag(Zr)/w;
19 printf("-C2 = %f microfarads\n",fix(C2*(10^6)*10^4))
```

```

        /10^4);
20 G2=real(Zr);
21 R2=1/(round(G2*10^6*10)/10);
22 printf("-R2 = %f m ohms",R2);

```

---

### Scilab code Exa 9.2 Designing an artificial line

```

1 clear;
2 clc;
3 R=16.64;L=5.87*(10^-3);G=1.28*(10^-6);C
    =0.0134*(10^-6);bmax=0.1;f2=5500;f1=30;
4 w=2*pi*f2;
5 Z=R+(%i*w*L);
6 Y=G+(%i*w*C);
7 P=fix(sqrt(Z*Y)*10^4)/10^4;
8 a=-f1*((-3*real(P)*real(P)*imag(P))-((imag(P))^3))
    /24;
9 a1=round(a*1000)/1000;
10 v=sqrt(bmax/a1);
11 l=f1/v;
12 R1=R*f1/(2*l);
13 L1=L*f1*10^3/(2*l);
14 C1=C*f1*10^6/l;
15 G1=G*f1/l;
16 Rg=1/G1;
17 printf("The elements of the artificial line are:\n")
    ;
18 printf(" R/2 = %f ohms\n",fix(R1*100)/100);
19 printf(" L/2 = %f mH\n",fix(L1*100)/100);
20 printf(" C = %f microfarads\n",fix(C1*1000)/1000);
21 printf(" Rg = %f k ohms\n",round((Rg*0.1)/100));

```

---

### Scilab code Exa 9.3 Designing a delay line using T section

```

1 clear;
2 clc;
3 Ro=500; Td=1*(10^-6); Tr=0.3*(10^-6);
4 n=1.1*((Td/Tr)^(3/2));
5 N=round(n);
6 printf("-Number of T-sections required = %f\n",N);
7 C=Td/(1.07*N*Ro);
8 printf("-C = %f microfarads\n",C*(10^6));
9 L=(Ro*Td)/(1.07*n);
10 printf("-L = %f mH",L*(10^3));
11 //the difference in result of L is due to erroneous
   value in textbook.
12 disp("The difference in result of L is due to
   erroneous value in textbook")

```

---

### Scilab code Exa 9.4 Designing an artificial line

```

1 clear;
2 clc;
3 R=10.4; L=3.66*(10^-3); G=0.8*(10^-6); C
   =0.00835*(10^-6); bmax=0.1; s=7.88; f=5000; w=2*pi*f
   ;
4 Z=R+(%i*w*L);
5 Y=G+(%i*w*C);
6 P=sqrt(Z*Y);
7 b=imag(P);
8 lmax=bmax/b;
9 l=s/20; //l<lmax
10 Zs=Z*l/2;
11 Zsh=1/(Y*l);
12 Zr=Y*l;
13 R1=real(Zs);
14 printf("-R1 = %f ohms\n",round(R1*100)/100);
15 L1=imag(Zs)/w;
16 printf("-L1 = %f mH\n",round(L1*(10^3)*100)/100);

```

```
17 C2=imag(Zr)/w;  
18 printf("-C2 = %f microfarads\n",C2*(10^6));  
19 G2=real(Zr);  
20 printf("-G2 = %f micromhos",G2*(10^6));
```

---

# Chapter 11

## Networks

Scilab code Exa 11.1 Calculating image and iterative impedance

```
1 clear;
2 clc;
3 Za=200;
4 Zb=400;
5 Zc=500;
6 Zi1=sqrt((Za+Zc)*((Za*Zc)+(Za*Zb)+(Zc*Zb))/(Zb+Zc));
7 printf("(a) Image impedance Zi1 = %f ohms\n",round(
    Zi1*10)/10);
8 Zi2=sqrt((Zb+Zc)*((Za*Zc)+(Za*Zb)+(Zc*Zb))/(Za+Zc));
9 printf(" Image impedance Zi2 = %f ohms\n",round(Zi2
));
10 Zt1=(1/2)*((Za-Zb)+sqrt(((Za-Zb)^2)+(4*((Za*Zb)+(Za*
    Zc)+(Zb*Zc)))));
11 printf("(b) Iterative impedances Zt1 = %f ohms\n",
    round(Zt1*10)/10);
12 Zt2=(1/2)*((Zb-Za)+sqrt(((Zb-Za)^2)+(4*((Za*Zb)+(Za*
    Zc)+(Zb*Zc)))));
13 printf(" Iterative impedances Zt2 = %f ohms",round(
    Zt2*10)/10);
```

---

### Scilab code Exa 11.2 Calculating iterative impedance

```
1 clear;
2 clc;
3 Za=%i*200; Zc=-%i*500;
4 Zt1=(Za/2)+(%sqrt((Za*Za/4)+(Za*Zc)));
5 A=real(Zt1);
6 B=imag(Zt1);
7 printf("Iterative impedances Zt1 = %d + j(%d) ohms\n"
    ",A,B);
8 Zt2=(-Za/2)+(%sqrt((Za*Za/4)+(Za*Zc)));
9 C=real(Zt2);
10 D=imag(Zt2);
11 printf("Iterative impedances Zt2 = %d + j(%d) ohms",
    C,D);
```

---

### Scilab code Exa 11.3 Calculating iterative and image impedance

```
1 clear;
2 clc;
3 Z1=30+(%i*7.5); Z2=50+(%i*10); Z3=-%i*3229;
4 Za=Z1; Zb=Z2; Zc=Z3;
5 a=Za+Zc;
6 b=Zb+Zc;
7 s=(Za*Zb)+(Zb*Zc)+(Zc*Za);
8 Zi1=%sqrt(a*s/b);
9 printf("Image impedances Zi1 = %f /_ %f ohms\n",
    round(abs(Zi1)*10)/10,round(atan(imag(Zi1)),real(
    Zi1))*180*100/%pi)/100);
10 Zi2=%sqrt(b*s/a);
11 printf(" Image impedances Zi1 = %f /_ %f ohms\n",
    round(abs(Zi2)*10)/10,round(atan(imag(Zi2)),real(
```

```

    Zi2))*180*100/%pi)/100);
12 Zt1=(1/2)*((Za-Zb)+sqrt(((Za-Zb)^2)+(4*s)));
13 printf(" Iterative impedances Zt1 = %f + j(%f) ohms\
n",round(real(Zt1)*100)/100,round(imag(Zt1)*100)
/100);
14 Zt2=(1/2)*((Zb-Za)+sqrt(((Za-Zb)^2)+(4*s)));
15 printf(" Iterative impedances Zt1 = %f + j(%f) ohms\
n",round(real(Zt2)*100)/100,round(imag(Zt2)*100)
/100);
16 //the difference in result is due to erroneous
   value in textbook.
17 disp("The difference in result is due to erroneous
   value in textbook")

```

---

**Scilab code Exa 11.4** Calculating image and iterative impedances and transfer constants

```

1 clear;
2 clc;
3 Za=%i*300;Zc=-%i*700;
4 Zoc1=Za+Zc;
5 Zsc1=Za;
6 Zoc2=Zc;
7 Zsc2=(Za*Zc)/(Za+Zc);
8 Zi1=sqrt(Zoc1*Zsc1);
9 printf("-Image impedance Zi1 = %f ohms\n",round(Zi1)
 );
10 Zi2=sqrt(Zoc2*Zsc2);
11 printf("-Image impedance Zi2 (in ohms)= %f ohms\n",
   round(Zi2));
12 Zt1=(Za/2)+(sqrt((Za*Za/4)+(Za*Zc)));
13 A=real(Zt1)
14 B=imag(Zt1);
15 printf("-Iterative impedance Zt1 = %f + j(%f) ohms\
n",
   round(A),B);

```

```

16 Zt2=(-Za/2)+(sqrt((Za*Za/4)+(Za*Zc))) ;
17 C=real(Zt2) ;
18 D=imag(Zt2) ;
19 printf("-Iterative impedance Zt2 = %f + j(%f) ohms\n"
      ,round(C),D) ;
20 I=(1+(sqrt(Zsc1/Zoc1)))/(1-(sqrt(Zsc1/Zoc1))) ;
21 Qi=(log(I))/2 ;
22 E=real(Qi) ;
23 F=imag(Qi) ;
24 printf("-Image transfer constant = %f + j(%f)\n",E,
      round(F*1000)/1000) ;
25 I1=(Zt1+Zc) ;
26 I2=Zc ;
27 Q2=log(I1/I2) ;
28 G=real(Q2) ;
29 H=imag(Q2) ;
30 printf("-Iterative transfer constant = %f +j(%f)" ,G ,
      round(H*180*10/%pi)/10) ;

```

---

**Scilab code Exa 11.5** Computing the insertion ratio and loss

```

1 clear ;
2 clc ;
3 Zg=100;Zl=500;b=63.4;a=0;
4 theta=a+(%i*b);
5 Fr=2*(sqrt(Zg*Zl))/(Zg+Zl) ;
6 IR=Fr*exp(theta) ;
7 A=real(IR) ;
8 B=imag(IR) ;
9 printf("-Insertion ratio = %f / - %f\n",fix(abs(IR)
      *100)/100,theta/%i) ;
10 IL=-20*log10(Fr) ;
11 printf("-Insertion loss = %f db",round(IL*10)/10) ;

```

---

**Scilab code Exa 11.6** Determining the components of a symmetrical T section network

```
1 clear;
2 clc;
3 Zoc=800;Zsc=600;
4 R2=sqrt((Zoc*Zoc)-(Zsc*Zoc));
5 R1=2*(Zoc-R2);
6 printf("The components of the network are:\n");
7 printf(" R1/2 = %d ohms\n",R1/2);
8 printf(" R2 = %d ohms",R2);
```

---

**Scilab code Exa 11.7** Calculating current

```
1 clear;
2 clc;
3 Z1=20;Z2=10;Vrms=10;
4 Zot=sqrt(((Z1*Z1)/4)+(Z1*Z2));
5 I=Vrms/Zot;
6 a=[30 27.32;1 -3.732];
7 b=[0.577;0];
8 b=inv(a)*b;
9 printf("Current flowing through the terminating
impedance = %f mA",round(b(2,1)*(10^4)*100)/100);
```

---

**Scilab code Exa 11.8** Calculating characteristic impedance

```
1 clear;
2 clc;
```

```

3 Z1=50+(%i*125);Z2=200-(%i*100);
4 Zot=sqrt((Z1/4)*(Z1+(4*Z2)));
5 A=real(Zot);
6 B=imag(Zot);
7 printf("Characteristic impedance = %f + j(%f) ohms",
       round(A),round(B*100)/100);

```

## Scilab code Exa 11.9 Designing a L section

**Scilab code Exa 11.10** Designing a reactive T network

```
1 clear;
2 clc; //solved using the value of w used in the
      solution
3 Rl=1000;Xg=250+(%i*200);w=2*(10^6);
4 Rg=real(Xg);
5 X1=sqrt(Rg*Rl);
6 X2=X1;
7 X3=X1;
8 C3=1/(w*X3);
9 printf("-C3 = %d pf\n",C3*(10^12));
10 L1=X1/w;
11 printf("-L1 = %d micro-henry\n",L1*(10^6));
12 L2=X2/w;
13 Xc=-%i*imag(Xg);
14 X21=X2+(Xc/%i);
15 L21=X21/w;
16 printf("-L2 = %d micro-henry",L21*(10^6));
```

---

**Scilab code Exa 11.11** Determining the equivalent T network

```
1 clear;
2 clc;
3 Zin=400+(%i*4000);Zout1=100+(%i*1000);Zout2=38+(%i
      *380);
4 Zoc1=Zin;Zoc2=Zout1;Zsc2=Zout2;
5 Z3=sqrt(Zoc1*(Zoc2-Zsc2));
6 Z1=Zoc1-Z3;
7 Z2=Zoc2-Z3;
8 A=real(Z1);
9 B=imag(Z1);
```

```

10 C=real(Z2);
11 D=imag(Z2);
12 E=real(Z3);
13 F=imag(Z3);
14 printf("-Z1 = %f + j (%f) ohms\n", round(A*10)/10,
        round(B*10)/10);
15 printf("-Z2 = %f + j (%f) ohms\n", fix(C*10)/10, fix(D)
        );
16 printf("-Z3 = %f + j (%f) ohms\n", fix(E*10)/10, fix(F)
        );

```

---

**Scilab code Exa 11.12** Finding the elements of the arms of a loss less T network

```

1 clear;
2 clc;
3 w=5*(10^6); Rg=800; Rl=200; b=-12;
4 X3=-(sqrt(Rg*Rl))/sin(b*pi/180);
5 L3=X3/w;
6 X1=(-Rg/tan(b*pi/180))+((sqrt(Rg*Rl)/sin(b*pi/180)
    ));
7 L1=X1/w;
8 X2=(-Rl/tan(b*pi/180))+((sqrt(Rg*Rl)/sin(b*pi/180)
    ));
9 C2=-1/(X2*w);
10 printf("-L3 = %f micro-henry\n", fix(L3*(10^6)));
11 printf("-L1 = %f micro-henry\n", fix(L1*(10^6)));
12 printf("-C2 = %f pf", round(C2*(10^12)));

```

---

**Scilab code Exa 11.13** Determining the image and iterative impedance and equivalent T network

```
1 clear;
```

```

2 clc;
3 Ya=40*(10^-3); Yb=50*(10^-3); Yc=20*(10^-3);
4 Za=1/Ya; Zb=1/Yb; Zc=1/Yc;
5 Z1=Zb*Zc/(Za+Zb+Zc);
6 Z2=Za*Zc/(Za+Zb+Zc);
7 Z3=Zb*Za/(Za+Zb+Zc);
8 Zi1=sqrt(((Z3+Z1)/(Z3+Z2))*((Z1*Z2)+(Z2*Z3)+(Z1*Z3)))
    );
9 printf("(a) Zi1 = %f ohms\n", round(Zi1));
10 Zi2=sqrt(((Z3+Z2)/(Z3+Z1))*((Z1*Z2)+(Z2*Z3)+(Z1*Z3)))
    );
11 printf("    Zi2 = %f ohms\n", round(Zi2*100)/100);
12 Zt1=(1/2)*((Z1-Z2)+sqrt(((Z1-Z2)^2)+(4*((Z1*Z2)+(Z2
    *Z3)+(Z1*Z3))))));
13 printf("    Zt1 = %f ohms\n", fix(Zt1*100)/100);
14 Zt2=(1/2)*((Z2-Z1)+sqrt(((Z1-Z2)^2)+(4*((Z1*Z2)+(Z2
    *Z3)+(Z1*Z3)))));
15 printf("    Zt2 = %f ohms\n\n", fix(Zt2*100)/100);
16 Zb1=Za*Zb/(Za+Zb);
17 Z11=Zb*Zc/(Zb+Zc+Zb1);
18 Z21=Zb1*Zc/(Zb+Zc+Zb1);
19 Z31=Zb1*Zb/(Zb+Zc+Zb1);
20 Zr=Zc+Z21;
21 Zs=Z21+Zb;
22 Z12=Z31*Zs/(Z31+Zr+Za);
23 Z22=Zr*Za/(Z31+Zr+Za);
24 Z32=Z31*Za/(Z31+Zr+Za);
25 Z121=Z12+Z11;
26 printf("    The desired T network will be as:\n");
27 printf("    Z1 = %f ohms\n", round(Z121*100)/100);
28 printf("    Z2 = %f ohms\n", fix(Z22*10)/10);
29 printf("    Z3 = %f ohms\n", round(Z32*10^4)/10^4);

```

---

**Scilab code Exa 11.14** Calculating the characteristic impedance and propagation function of given network

```

1 clear;
2 clc;
3 L=20*(10^-3);C=0.064*(10^-6);f=400;
4 w=2*pi*f;
5 Z1=round(2*i*w*L*10)/10;
6 Z2=1/(i*w*C);
7 Zo=sqrt((Z1*Z1/4)+(Z1*Z2));
8 printf("Characteristic impedance = %f ohms\n",round(
    Zo*100)/100);
9 Pf=(1+(Z1/(2*Z2)));
10 printf(" Propagation constant = %f",round(Pf*100)
    /100);
11 //the difference in result is due to erroneous
    value in textbook.
12 disp("The difference in result is due to erroneous
    value in textbook")

```

---

**Scilab code Exa 11.15** Calculating characteristic impedance and propagation function

```

1 clear;
2 clc;
3 Za=300;Zc=600;R=1000;
4 Zi1=sqrt((Za*Za)+(Za*Zc));
5 Zi2=Za*Zc/sqrt((Za*Za)+(Za*Zc));
6 Zt1=(Za/2)+sqrt((Za*Za/4)+(Za*Zc));
7 Zt2=(-Za/2)+sqrt((Za*Za/4)+(Za*Zc));
8 printf("The image impedances are:\n");
9 printf("Zi1 = %f ohms\n",round(Zi1*10)/10);
10 printf(" Zi2 = %f ohms\n",round(Zi2*10)/10);
11 printf(" Zt1 = %f ohms\n",Zt1);
12 printf(" Zt2 = %f ohms\n",Zt2);
13 I=((R+Zt1+Zt2)*(R+Zt1)/(Zt1))-Zt1)*(1/(R+R));
14 Ir=20*log10(round((I*1000))/1000);
15 printf(" Insertion loss = %f db",Ir);

```

---

**Scilab code Exa 11.16** Designing a L matching loss less network

```
1 clear;
2 clc;
3 Rg=100; Rl=50; f=5*(10^6);
4 w=2*pi*f;
5 X21=sqrt(Rl*(Rg-Rl));
6 X22=-X21;
7 X31=-Rg*sqrt(Rl/(Rg-Rl));
8 X32=-X31;
9 L2=X21/w;
10 printf("(i) X2 is inductive and X3 is capacitive
           where\n   X2=L2 = %f microhenry\n", round(L2*(10^6)
           *1000)/1000);
11 C2=-1/(w*X31);
12 printf("   X3=C3 = %f pf\n", round(C2*(10^12)*10)/10);
13 L31=X32/w;
14 printf("(ii) X3 is inductive and X2 is capacitive
           where\n   X3=L3 = %f microhenry\n", round(L31
           *(10^6)*1000)/1000);
15 C21=-1/(w*X22);
16 printf("   X2=C2 = %f pf", round(C21*(10^12)));
```

---

**Scilab code Exa 11.17** Calculating different losses and total insertion loss

```
1 clear;
2 clc;
3 Zl=100; Zsh=500; Zg=300;
4 Zoc=Zl+Zsh;
5 Zsc=Zl+(1/((1/Zl)+(1/Zsh)));
6 Zi1=sqrt(Zoc*Zsc);
```

```

7 Zi2=Zi1;
8 theta=atanh(sqrt(Zsc/Zoc));
9 att=theta*8.686;
10 printf("-Attenuation loss = %f db\n",round(att*10)
    /10);
11 inp=20*log10(round((Zi1+Zg))/(2*sqrt(Zi1*Zg)));
12 printf("-Loss due to mismatch at the input = %f db\n"
    ",round(inp*100)/100);
13 out=20*log10((Zi2+Zl)/(2*(sqrt(Zi2*Zl)))); 
14 printf("-Loss due to mismatch at output = %f db\n",
    round(out*100)/100);
15 Ki1=(Zi1-Zg)/(Zi1+Zg);
16 Ki2=(Zi2-Zl)/(Zi2+Zl);
17 inte=-20*log10(1-(Ki1*Ki2*exp(-2*theta)));
18 printf("-Loss due to interaction = %f db\n",fix(inte
    *100)/100);
19 ext=20*log10((Zg+Zl)/(2*sqrt(Zg*Zl)));
20 printf("-External reflection loss = %f db\n",round(
    ext*100)/100);
21 tot=att+inp+out-inte-ext;
22 printf("-Total insertion loss = %f db\n",fix(tot
    *100)/100);

```

---

**Scilab code Exa 11.18** Calculating the elements of a L section network

```

1 clear;
2 clc;
3 Rg=8000;Zl=500+(%i*500);f=5*(10^6);
4 //value of f as taken in solution
5 w=2*%pi*f;
6 Xc=-%i*imag(Zl);
7 Rl=real(Zl);
8 X21=sqrt(Rl*(Rg-Rl));
9 X22=-X21;
10 X31=-Rg*sqrt(Rg/(Rg-Rl));

```

```

11 X32=-X31;
12 X2a=X21+(Xc/%i);
13 L2a=X2a/w;
14 C3a=-1/(w*X31);
15 printf("(a)X2 is inductive and X3 is capacitive
           where\n      X2=L2 = %f mH\n", round(L2a*(10^3)*1000)
           /1000);
16 printf("      X3=C3 = %f pf\n", round(C3a*(10^12)*1000)
           /1000);
17 X2b=X22+(Xc/%i);
18 C2b=-1/(w*X2b);
19 L3b=X32/w;
20 printf("(b)X2 is capacitive and X3 is inductive
           where\n      X2=C2 = %f pf\n", round(C2b*(10^12)*100)
           /100);
21 printf("      X3=L3 = %f mH", round(L3b*(10^3)*1000)
           /1000);

```

---

**Scilab code Exa 11.19** Calculating image impedance and transfer constant

```

1 clear;
2 clc;
3 Zoc1=-%i*400; Zoc2=-%i*600; Zsc1=%i*267; Zsc2=%i*400;
4 A=Zoc1/Zsc1;
5 B=Zoc2/Zsc2;
6 printf("(a) Since Zoc1/Zsc1 = Zoc2/Zsc2 = %f the
           results are consistant\n", round(A*10)/10);
7 Zi1=sqrt(Zoc1*Zsc1);
8 Zi2=sqrt(Zoc2*Zsc2);
9 printf("The image impedances are:\n Zi1 = %f ohms\n
           Zi2 = %f ohms\n", round(Zi1*10)/10, round(Zi2*10)
           /10);
10 C=(1+sqrt(B))/(1-sqrt(B));
11 phi=round(atan(imag(C), real(C))*180*10/%pi)/10;
12 theta=round(%i*phi*%pi*1000/(2*180))/1000;

```

```
13 printf("Image transfer constant = j %f",theta/%i);
```

---

**Scilab code Exa 11.20** Calculating reduction in power

```
1 clear;
2 clc;
3 Zg=300; Zi=400; Zi1=600; theta=10;
4 thetai=theta/8.686;
5 Zi2=Zi1;
6 Ir=thetai + log(((Zi1+Zg)/(2*sqrt(Zi1*Zg)))*((Zi1+Zi)
    /(2*sqrt(Zi1*Zi)))*((Zi+Zg)/(2*sqrt(Zi*Zg)))
    *((1-((Zg-Zi1)/(Zg+Zi1))*((Zi-Zi1)/(Zi+Zi1))*exp
    (-2*thetai))));;
7 Ir1=(round(Ir*10)/10)*8.686;
8 printf("The reduction in power will be = %f db",
    round(Ir1*100)/100);
```

---

**Scilab code Exa 11.21** Calculating characteristic impedance and attenuation constant and phase shift constant

```
1 clear;
2 clc;
3 R1=200; L1=100*(10^-3); R2=200; L2=100*(10^-3); C2
    =2.5*(10^-6); w=2000;
4 Z1=R1+(%i*w*L1);
5 Z2=1/(%i*w*C2);
6 Zoc=Z1+Z2;
7 Zsc=Z1+(1/((1/Z1)+(1/Z2)));
8 Zo=sqrt(Zoc*Zsc);
9 printf("-Characteristic impedance = %f ohms\n",round
    (Zo));
10 P=atanh(sqrt(Zsc/Zoc));
11 a=real(P);
```

```

12 printf("-Attenuation constant = %f nepers\n", round(a
   *100)/100);
13 b=(imag(P))*180/%pi;
14 printf("-Phase shift constant = %d degrees",b);

```

---

**Scilab code Exa 11.22** Calculating image impedance and propagation constant and elements of T network

```

1 clear;
2 clc;
3 Z1o=1260*(exp(%i*30/(180/(%pi))));Z2o=2430*(exp(-%i
   *34/(180/(%pi))));
4 Z1s=318*(exp(%i*72/(180/(%pi))));Z2s=613*(exp(%i
   *8/(180/(%pi))));
5 Zi1=sqrt(Z1o*Z1s);
6 A=real(Zi1);
7 B=imag(Zi1);
8 printf("(i)Image impedance Zi1 = %f / - %f ohms\n",
   round(abs(Zi1)),atan(B,A)*180/%pi);
9 Zi2=sqrt(Z2o*Z2s);
10 C=real(Zi2);
11 D=imag(Zi2);
12 printf(" Image impedance Zi2 = %f / - %f ohms\n",
   round(abs(Zi2)),atan(D,C)*180/%pi);
13 Z3=sqrt(Z2o*(round(Z1o)-round(Z1s)));
14 Z1=Z1o-Z3;
15 Z2=Z2o-Z3;
16
17 P=atanh(sqrt(Z1s/Z1o));
18 printf("(ii)Propagation constant = %f / - %f\n",
   round(abs(P*100))/100,round(atan(imag(P),real(P))
   *100)/100);
19 printf("(iii)The elements of the T network are:\n")
   ;
20 printf("      Z1 = %f + j(%f) ohms\n",round(real(Z1)))

```

```
    , round(imag(z1)));
21 printf("      Z2 = %f + j(%f) ohms\n", round(real(z2))
    , round(imag(z2)));
22 printf("      Z3 = %f + j(%f) ohms", round(real(z3)),
    round(imag(z3)));
```

---

# Chapter 12

## Network Theorems

**Scilab code Exa 12.1** Finding the rms value of current

```
1 clear;
2 clc;
3 w=2*pi*(10^6);C=100*(10^-12);V=10;L=100*(10^-6);
4 Zc=1/(w*C);
5 Ic=(V/sqrt(2))/Zc;
6 printf("-R.m.s. value of current flowing through
    capacitor C = %f mA\n",round(Ic*(10^3)*100)/100);
7 Zl=w*L;
8 Il=(V/sqrt(2))/Zl;
9 printf("-R.m.s. value of current flowing through
    inductor L = %f mA",fix(Il*(10^3)*10)/10);
```

---

**Scilab code Exa 12.2** Calculating voltage

```
1 clear;
2 clc;
3 Z1=10;Z2=5;Z3=2;I1=2;I2=4;
4 Vab1=I1*(1/((1/Z2)+(1/(Z1+Z3))));
```

```

5 I5=I2*Z3/(Z1+Z2+Z3); //I5=current through the 5 ohm
    resistor
6 Vab2=Z2*I5;
7 Vab=Vab1+Vab2;
8 printf("Vab = %f volts", round(Vab*100)/100);

```

---

### Scilab code Exa 12.3 Calculating current

```

1 clear;
2 clc;
3 R1=5; R2=%i*5; R3=3+(%i*4); V1=50*exp(%i*90/(180/%pi));
    V2=50;
4 Z1=R1+(1/((1/R2)+(1/R3)));
5 I1=V1/Z1;
6 Iz1=I1*R2/(R2+R3);
7 Z2=R2+(1/((1/R1)+(1/R3)));
8 I2=V2/Z2;
9 Iz2=-I2*R1/(R1+R3);
10 Iz=Iz1+Iz2;
11 printf("Total current in the (3+j4)ohm branch = %f /
    - %f Amp", round(abs(Iz)*10)/10, round(atan(imag(Iz)
    ), real(Iz))*180*10/%pi)/10);

```

---

### Scilab code Exa 12.5 Determining Thevenins equivalent generator

```

1 clear;
2 clc;
3 Isc=10; Voc=120; Rl=8; Il=6;
4 Zeq=Voc/Isc; //Zeq=impedance of the equivalent
    thevenin's generator Z=R+jX
5 t=Voc/Isc; //(R^2)+(X^2)=(t^2)
6 R=((Voc/Il)^2)-(t^2)-(Rl^2))/(2*Rl);
7 X=sqrt((t^2)-(R^2));

```

```
8 printf("The equivalent Thevenin generator has an emf  
      of %d volts and an internal impedance of (%d +  
      j%d) ohms" ,Voc ,R ,X);
```

---

### Scilab code Exa 12.6 Determining Thevenins equivalent circuit

```
1 clear;  
2 clc;  
3 V=10; R1=5; R2=%i*5; R3=3+(%i*4);  
4 Zab=R2+(1/((1/R1)+(1/R3)));  
5 A=real(Zab);  
6 B=imag(Zab);  
7 I=V/(R1+R3);  
8 Voc=I*R3;  
9 C=real(Voc);  
10 D=imag(Voc);  
11 printf("The equivalent Thevenin circuit has an emf  
      of %f /- %f volts and an internal impedance of (  
      %f + j%f) ohms" ,fix(abs(Voc)*100)/100,fix(atan(D,  
      C)*180/%pi),A,B);
```

---

### Scilab code Exa 12.7 Deriving the equivalent voltage generator circuit

```
1 clear;  
2 clc;  
3 Voc=150; Rl=10; Il=2.65; Isc=3;  
4 t=Voc/Isc; // (R^2)+(X^2)=(t^2)  
5 R=((Voc/Il)^2)-(t^2)-(Rl^2)/(2*Rl);  
6 X=sqrt((t^2)-(R^2));  
7 printf("-The equivalent voltage generator circuit  
      has an emf of %d volts and an internal impedance  
      of (%f + j%f) ohms\n" ,Voc ,fix(R*100)/100,round(X  
      *100)/100);
```

```

8 if X>0 then
9     printf("-Since X has a positive value the
10    circuit will be inductive");
11 else
12     disp("-Since X has a negative value the circuit
13    will be capacitive");
14 end

```

---

**Scilab code Exa 12.8** Determining the Nortons equivalent circuit

```

1 clear;
2 clc;
3 Za=-%i*5; Zb=5+(%i*5); V=50; Z1=5-(%i*5); Z2=10;
4 Isc=V/Za;
5 A=real(Isc);
6 B=imag(Isc);
7 printf("-Short circuit current = %d / - %d Amps\n",
8     abs(Isc), atan(B,A)*180/%pi);
9 Zab=1/((1/Za)+(1/Zb));
10 C=real(Zab);
11 D=imag(Zab);
12 printf("-Equivalent impedance = %d + j (%d) ohms\n", C
13     ,D);
14 I1=Isc*(Zab/(Zab+Z1));
15 E=real(I1);
16 F=imag(I1);
17 printf("-Current through impedance Z1(=5-j5) = %d / -
18     %d Amps\n", abs(I1), atan(F,E)*180/%pi);
19 I2=Isc*(Zab/(Zab+Z2));
20 G=real(I2);
21 H=imag(I2);
22 printf("-Current through impedance Z2(=10) = %f / -
23     %f Amps", round(abs(I2)*100)/100, round(atn(H,G)
24     *100*180/%pi)/100);

```

---

**Scilab code Exa 12.9** Obtaining Nortons equivalent circuit

```
1 clear;
2 clc;
3 V1=10; V2=20; R1=5; R2=15;
4 Isc=(V1/R1)+(V2/R2);
5 Zab=1/((1/R2)+(1/R1));
6 printf("-Short circuit current = %f Amp\n", round(Isc
    *100)/100);
7 printf("-Equivalent impedance = %f ohm", Zab);
```

---

**Scilab code Exa 12.10** Verifying reciprocity theorem

```
1 clear;
2 clc;
3 I=5*exp(%i*(90)/(180/%pi)); Z1=5+(%i*5); Z2=2; Z3=-%i
    *2;
4 I2=I*Z1/(Z1+Z2+Z3);
5 V2=I2*Z3;
6 I1=I*Z3/(Z1+Z2+Z3);
7 V1=I1*Z1;
8 printf("The reciprocity theorem has been verified.")
```

---

**Scilab code Exa 12.11** Calculating value of compensation source

```
1 clear;
2 clc;
3 Z1=%i*10; Z2=3+(%i*4); Z=5; V=20;
```

```

4 Zeq=1/((1/Z1)+(1/Z2));
5 Zi=Z+Zeq;
6 I=V/Zi;
7 Vc=I*Zeq;
8 A=real(Vc);
9 B=imag(Vc);
10 printf("Compensation source Vc = %f /- %f volts",
         round(abs(Vc)*10)/10,round(atan(B,A)*180*10/%pi)
         /10);

```

---

**Scilab code Exa 12.12** Calculating power in load and turns ratio for maximum power transfer

```

1 clear;
2 clc;
3 Zg=10000;Zl=24+(%i*7);Vrms=100;
4 Rl=real(Zl);
5 Xl=imag(Zl);
6 Zeq=sqrt(((Rl+Zg)^2)+((Xl)^2));
7 Irms=Vrms/Zeq;
8 P=Irms*Irms*Rl;
9 printf("(i)Power in the load if connected directly
        to the generator = %f mW\n",round(P*(10^3)*10)
        /10);
10 ampZl=sqrt((Rl*Rl)+(Xl*Xl));
11 n=1/sqrt(ampZl/Zg);
12 printf("(ii)The desired turn ratio of transformer is
        1:%d\n",n);
13 P1=Vrms*Vrms/(4*Zg);
14 printf("(iii)Power transferred under ideal load
        conditions =%f mW",P1*(10^3));

```

---

**Scilab code Exa 12.13** Determining value of maximum power

```

1 clear;
2 clc;
3 Zg=10+(%i*20);V=50;
4 Rg=real(Zg);Xg=imag(Zg);
5 ampZg=sqrt((Rg*Rg)+(Xg*Xg));
6 Rl=ampZg;
7 I=V/(Zg+Rl);
8 ampI=round(sqrt((real(I))^2+(imag(I))^2)*100)/100;
9 P=ampI*ampI*round(Rl*10)/10;
10 printf("Power delivered to the load = %f Watt",round
(P*10)/10);

```

---

**Scilab code Exa 12.14** Calculating value of R and X which result in maximum power transfer and value of maximum power transferred

```

1 clear;
2 clc;
3 V=50*exp(%i*45/(180/%pi));Z1=3;Z2=2+(%i*10);Xl=2;
4 Voc=V*Z2/(Z1+Z2);
5 Zab=1/((1/Z1)+(1/Z2));
6 Zg=Zab
7 Rl1=Zg-(%i*Xl);
8 Rl=abs(Rl1);
9 Z=Zab+Rl-(%i*Xl);
10 I1=Voc/Z;
11 I=abs(I1);
12 P=I*I*Rl;
13 printf("-Rl = %f ohms\n",round(Rl*100)/100);
14 printf("-Xl = %f ohms\n",Xl);
15 printf("-Maximum power delivered to load = %f Watts"
,round(P));

```

---

**Scilab code Exa 12.17** Calculating effective resistance of coil and inductance of the effective resistance

```
1 clear;
2 clc;
3 f=5*(10^6);C=400*(10^-12);R=10*(10^3);
4 w=2*pi*f;
5 L=2/(w*w*C);
6 r=1/(w*w*C*C*R);
7 printf("-Effective resistance of the coil = %f ohms\n",round(r*100)/100);
8 printf("-Inductance of effective resistance of the
coil = %f mH",round(L*(10^3)*1000)/1000);
```

---

**Scilab code Exa 12.19** Determining the elements of a series type Foster network

```
1 clear;
2 clc;
3 w1=2*(10^6);w2=3*(10^6);w3=4*(10^6);w=1*(10^6);Z=%i
*100;
4 F=((w*w)-(w2*w2))/(((w*w)-(w1*w1))*((w*w)-(w3*w3)));
5 H=Z/(%i*w*F);H1=round(H*10^-8*100)/(100*10^-8);
6 A=((w1*w1)-(w2*w2))/((w1*w1)-(w3*w3));
7 B=((w3*w3)-(w2*w2))/((w3*w3)-(w1*w1));
8 C2=-1/(H1*A);
9 printf("Elements of the series type Foster network
are:\n");
10 printf("-C2 = %f pf\n",fix(C2*(10^12)))
11 L2=1/(w1*w1*C2);
12 printf("-L2 = %f microhenry\n",round(L2*(10^6)*10)
/10);
13 C4=-1/(H1*B);
14 printf("-C4 = %f pf\n",fix(C4*(10^12)));
15 L4=1/(w3*w3*C4);
```

```
16 printf("-L4 = %f microhenry", round(L4*(10^6)*10)/10)
;
```

---

**Scilab code Exa 12.20** Determining the elements of series type Foster network

```
1 clear;
2 clc;
3 w1=1000; w2=1500; w3=2000; w4=3000; w5=5000; w=100; Z=%i
    *100;
4 F=((w*w)-(w2*w2))*((w*w)-(w4*w4))/(((w*w)-(w1*w1))
    *((w*w)-(w3*w3))*((w*w)-(w5*w5)));
5 H=Z/(%i*w*F);
6 A=((w1*w1)-(w2*w2))*((w1*w1)-(w4*w4))/(((w1*w1)-(w3*
    w3))*((w1*w1)-(w5*w5)));
7 B=((w3*w3)-(w2*w2))*((w3*w3)-(w4*w4))/(((w3*w3)-(w5*
    w5))*((w3*w3)-(w1*w1)));
8 C=((w5*w5)-(w2*w2))*((w5*w5)-(w4*w4))/(((w5*w5)-(w1*
    w1))*((w5*w5)-(w3*w3)));
9 C2=-1/(H*A);
10 printf("-C2 = %f microfarads\n", round(C2*(10^6)*100)
    /100);
11 L2=1/(w1*w1*C2);
12 printf("-L2 = %f henry\n", round(L2*100)/100);
13 C4=-1/(H*B);
14 printf("-C4 = %f microfarads\n", round(C4*(10^6)*100)
    /100);
15 L4=1/(w3*w3*C4);
16 printf("-L4 = %f henry\n", round(L4*100)/100);
17 C6=-1/(H*C);
18 L6=1/(w5*w5*C6);
19 printf("-C6 = %f microfarads\n", round(L6*100)/100);
20 printf("-L6 = %f henry\n", round(C6*(10^6)*100)/100)
```

---

**Scilab code Exa 12.21** Finding current

```
1 clear;
2 clc;
3 V=10; Rl=10; Z1=5; Z2=5;
4 Zab=1/((1/Z1)+(1/Z2));
5 I1=V/(Z1+Z2);
6 Voc=I1*Z1;
7 I=Voc/(Zab+Rl);
8 printf("Current in the 10 ohm resistor = %d mA", I
    *(10^3));
```

---

**Scilab code Exa 12.22** Using Thevenins theorem to calculate power

```
1 clear;
2 clc;
3 Rl=10; V=100; Z1=-%i*30; Z2=-%i*30; Z3=20+(%i*10);
4 I=V/(Z1+Z2);
5 Voc=I*Z2;
6 Zab=1/((1/Z1)+(1/Z2))+Z3;
7 Z=Zab+Rl;
8 I1=Voc/Z;
9 ampI1=sqrt(real(I1)^2+imag(I1)^2);
10 P1=ampI1*ampI1*Rl;
11 printf("Power in the load = %f Watts", round(P1*100)
    /100);
```

---

**Scilab code Exa 12.23** Finding Thevenins equivalent generator

```

1 clear;
2 clc;
3 V=100; R1=10; R2=10; R3=10; R4=10;
4 I=V/(R1+R2);
5 Vab=I*R2;
6 Zab=1/((1/R1)+(1/R2));
7 V1=Vab*R4/(Zab+R3+R4);
8 Z1=1/((1/(Zab+R3))+(1/R4));
9 printf("The equivalent Thevenin circuit has an emf
        of %d volts and an internal impedance of %f ohms"
        ,V1,Z1);

```

---

**Scilab code Exa 12.25** Determining the value of load impedance for which maximum power is consumed in load and the corresponding power

```

1 clear;
2 clc;
3 V=100; Z1=20; Z2=-%i*100; Z3=100;
4 Zab=1/((1/(Z2))+(1/Z3));
5 Voc=V*Z3/(Z2+Z3);
6 I=Voc/(Zab+Voc);
7 P=(abs(I))^2 * real(Zab);
8 Z=conj(Zab);
9 A=real(Z);
10 B=imag(Z);
11 printf("Value of load value for maximum power = %d +
           j(%d) ohms\n",A,B);
12 printf(" Maximum Power = %d Watts",P);

```

---

**Scilab code Exa 12.26** Determining Thevenins equivalent circuit

```

1 clear;
2 clc;

```

```

3 V=100;R1=50;R2=60;R3=40;R4=60;R5=40;
4 Rac=1/((1/(R2+R3))+(1/(R4+R5)));
5 Rt=Rac+R1;
6 I=V/Rt;
7 V1=I*R1;
8 Vac=V-V1;
9 Vab=R2*Vac/(R2+R3);
10 Vad=R5*Vac/(R4+R5);
11 Vbd=Vab-Vad;
12 Voc=Vbd;
13 R1y=R5*R1/(R1+R4+R5);
14 R2y=R1*R4/(R1+R4+R5);
15 R3y=R4*R5/(R1+R4+R5);
16 Rbd=R3y+(1/((1/(R1y+R2))+(1/(R2y+R3)))) ;
17 printf("The equivalent Thevenin circuit has an emf
          of %d volts and an internal impedance of %d ohms"
          ,Vbd,Rbd);

```

---

### Scilab code Exa 12.27 Calculating current

```

1 clear;
2 clc;
3 V1=6;V2=6;R1=2;R2=1;R3=2;
4 Y1=1/R1;Y2=1/R2;
5Vm=((V1*Y1)+(V2*Y2))/(Y1+Y2);
6 Zm=1/(Y1+Y2);
7 I=Vm/(Zm+R3);
8 printf("Current in resistor R3 = %f Amp" ,I);

```

---

### Scilab code Exa 12.28 Using Millmans theorem to find current and voltage

```
1 clear;
```

```

2 clc;
3 V1=5; V2=4; R1=5; R2=4; I3=1; R3=10; R4=5;
4 V3=I3*R3;
5 Y1=1/R1; Y2=1/R2; Y3=1/R3;
6 V4=((V1*Y1)+(V2*Y2)+(V3*Y3))/(Y1+Y2+Y3);
7 I4=V4/R4;
8 printf("Voltage across resistor R4 = %f volts\n",V4)
      ;
9 printf("Current in resistor R4 = %f Amp",I4);
10 //the difference in result is due to erroneous
    value in textbook.
11 disp("The difference in result is due to erroneous
    value in textbook")

```

---

### Scilab code Exa 12.29 Verifying Tellegens theorem

```

1 clear;
2 clc;
3 V=120; R1=6; R2=8; R3=3; R4=5;
4 a=[7 -4;-1 2];
5 b=[60;0];
6 b=inv(a)*b;
7 I1=b(1,1);
8 I2=b(2,1);
9 VI1=(R1*I1)+(R2*(I1-I2))-V;
10 printf("Summation V*I for first loop = %d\n",VI1);
11 VI2=(R3*I2)+(R4*I2)-(R2*(I1-I2));
12 printf("Summation V*I for second loop = %d\n",VI2);
13 printf("Hence Tellegens theorem has been verified .")
      ;

```

---

### Scilab code Exa 12.30 Verifying Tellegens theorem

```

1 clear;
2 clc;
3 V1=4; V2=2; V3=2; V4=3; V5=-1; V6=-5; i1=2; i2=2; i3=4; i4
   =-2; i5=-6; i6=4;
4 Va=V2+V3-V1;
5 printf("V2+V3-V1= %d volts\n",Va);
6 Vb=V2+V4+V6;
7 printf("V2+V4+V6= %d volts\n",Vb);
8 Vc=V4+V5-V3;
9 printf("V4+V5-V6= %d volts\n",Vc);
10 printf("-Hence KVL is satisfied for all three loops
PQ TU, PR YX and QR ST respectively.\n\n");
11 Ia=i1+i2-i6;
12 printf("i1+i2-i6= %d Amp\n",Ia);
13 Ib=i3+i4-i2;
14 printf("i3+i4-i2= %d Amp\n",Ib);
15 Ic=i5+i6-i4;
16 printf("i5+i6-i2= %d Amp\n",Ic);
17 printf("-Hence KCL is satisfied at all three nodes P
,Q and R respectively.\n\n");
18 VI=(V1*i1)+(V2*i2)+(V3*i3)+(V4*i4)+(V5*i5)+(V6*i6);
19 printf("-Summation V*I= %d\n\n",VI);
20 printf("-This proves Tellegens theorem.");

```

---

### Scilab code Exa 12.31 Finding current

```

1 clear;
2 clc;
3 Vrms=10; R1=5; Z1=20; Z2=20; Z3=10; Z4=10;
4 Zab=(1/((1/Z1)+(1/Z2)))+(1/((1/Z3)+(1/Z4)));
5 Voc=R1;
6 I=Voc/(Zab+R1);
7 printf("Current I = %f Amps",I);

```

---

**Scilab code Exa 12.32** Calculating current and voltage using Thevenins theorem

```
1 clear;
2 clc;
3 I1=6; I2=8; R1=4; R2=4; R3=6; R4=4; Rl=3;
4 V1=I1*R1; V2=I2*R4;
5 Voc1=V1*(R3+R4)/(R1+R2+R3+R4);
6 Voc2=V2*(R1+R2)/(R1+R2+R3+R4);
7 Voc=Voc1+Voc2;
8 Zab=1/((1/(R1+R2))+(1/(R3+R4)));
9 I1=Voc/(Zab+Rl);
10 printf("-i1 = %f Amp\n", round(I1*10)/10);
11 el=I1*Rl;
12 printf("-el = %f volts", round(el*10)/10);
```

---

# Chapter 13

## Network Parameters

**Scilab code Exa 13.1** Determining z and y parameters

```
1 clear;
2 clc;
3 Z1=%i*20;Z2=%i*25;Z3=30;
4 Z11=Z1+Z3; //Z11=V1/I1 when I2=0
5 Z12=Z3; //Z12=V1/I2 when I1=0
6 Z21=Z3; //Z21=V2/I1 when I2=0
7 Z22=Z2+Z3; //Z22=V2/I2 when I1=0
8 printf("(a)The z-parameters are\n");
9 printf(" Z11 = %f + j(%f) ohms\n",real(Z11),imag(
    Z11));
10 printf(" Z12 = %f ohms\n",Z12);
11 printf(" Z21 = %f ohms\n",Z21);
12 printf(" Z22 = %f + j(%f) ohms\n",real(Z22),imag(
    Z22));
13 deltaz=(Z11*Z22)-(Z12*Z21);
14 y11=Z22/deltaz;
15 y12=-Z12/deltaz;
16 y21=-Z21/deltaz;
17 y22=Z11/deltaz;
18
19 printf("(b)The y-parameters are\n");
```

---

```

20 printf(" y11 = %f + j (%f) mhos\n",real(y11),imag(
21   y11));
21 printf(" y12 = %f + j (%f) mhos\n",real(y12),imag(
22   y12));
22 printf(" y21 = %f + j (%f) mhos\n",real(y21),imag(
23   y21));
23 printf(" y22 = %f + j (%f) mhos\n",real(y22),imag(
      y22));

```

---

**Scilab code Exa 13.2** Obtaining the open circuit impedance parameters

---

```

1 clear;
2 clc;
3 L=1;C=1;R=1;
4 printf("z11 = s + %d ohms\n",C);
5 printf(" z21 = %d ohms\n",C);
6 printf(" z22 = 1/s + %d ohms\n",C);
7 printf(" z12 = %d ohms\n",C);

```

---

**Scilab code Exa 13.3** Finding driving point and transfer impedances and loop equations and voltage

---

```

1 clear;
2 clc;
3 Voc2=100;I1=10;V2=25;
4 Voc1=100;I2=20;V1=50;
5 z11=Voc1/I1;
6 z21=V2/I1;
7 z22=Voc2/I2;
8 z12=V1/I2;
9 printf("(a)The driving point impedances are:\n");
10 printf(" z11 = %f ohms\n",z11);
11 printf(" z22 = %f ohms\n",z22);

```

---

```

12 printf(" The transfer impedances are :\n");
13 printf(" z12 = %f ohms\n",z12);
14 printf(" z21 = %f ohms\n\n",z21);
15 printf(" The loop equations are :\n");
16 printf(" V1= %f*I1 + %f*I2\n",z11,z12);
17 printf(" V2= %f*I1+ %f*I2\n\n",z21,z22);
18 Rl=10;
19 a=[z11 z12 ; z21 (z22+Rl)];
20 b=[100 ; 0];
21 b=inv(a)*b;
22 I2=b(2,1);
23 V1=-I2*Rl;
24 printf("(b) Voltage across resistor = %f volts",round
(V1*10)/10);

```

---

### Scilab code Exa 13.4 Computing y parameters

```

1 clear;
2 clc;
3 z11=10;z22=12;z12=5;z21=5;
4 deltaz=(z11*z22)-(z12*z21);
5 y11=z22/deltaz;
6 printf("The y-parameters are :\n");
7 printf("-y11 = %f mho\n",round(y11*10^4)/10^4);
8 y22=z11/deltaz;
9 printf("-y22 = %f mho\n",round(y22*10^4)/10^4);
10 y12=-z12/deltaz;
11 printf("-y12 = %f mho\n",round(y12*10^3)/10^3);
12 y21=y12;
13 printf("-y21 = %f mho",round(y21*10^3)/10^3);

```

---

### Scilab code Exa 13.5 Finding the z parameters

```

1 clear;
2 clc;
3 Y1=1; Y2=1; Y3=2; V3=3;
4 Z1=1/Y1; Z2=1/Y2; Z3=1/Y3;
5 V1=1; I1=-1;
6 z11=V1/I1;
7 V2=1; I2=3;
8 z22=V2/I2;
9 z21=V2/I1;
10 printf("z11 = %f ohms\n",z11);
11 printf(" z22 = %f ohms\n",z22);
12 printf(" z21 = %f ohms\n",z21);
13 printf(" z11 = %f ohms\n",0);

```

---

### Scilab code Exa 13.6 Computing h parameters

```

1 clear;
2 clc;
3 Vs1=25; Is1=1; Is2=2; //values with output terminal
    short circuited
4 Vo1=10; Vo2=50; Io2=2; //values with input terminal
    open circuited
5 Vs2=0;
6 h11=Vs1/Is1;
7 printf("The h-parameters are:\n");
8 printf("-h11 = %f ohms\n",h11); //with output
    terminals short circuited
9 h21=Is2/Is1;
10 printf("-h21 = %f\n",h21); //with input terminals
    open circuited
11 h12=Vo1/Vo2;
12 printf("-h12 = %f\n",h12); //with input terminals
    open circuited
13 h22=Io2/Vo2;
14 printf("-h22 = %f mho",h22); //with output terminals

```

```

        short circuited
15 //the difference in result of h22 is due to
   erroneous value in textbook.
16 disp("The difference in result of h22 is due to
   erroneous value in textbook")

```

---

**Scilab code Exa 13.7** Calculating transmission parameters and loop equations

```

1 clear;
2 clc;
3 z11=40;z22=30;z12=20;z21=20;
4 deltaz=(z11*z22)-(z12*z21);
5 A=z11/z12;
6 printf("The transmission parameters are:\n");
7 printf(" A = %f\n",A);
8 B=deltaz/z21;
9 printf(" B = %f ohms\n",B);
10 C=1/z21;
11 printf(" C = %f mho\n",C);
12 D=z22/z21;
13 printf(" D = %f\n",D);
14 printf(" The network equations using z-parameter are
   \n");
15 printf(" V1 = %fI1 + %fI2\n",z11,z12);
16 printf(" V2 = %fI1 + %fI2\n",z21,z22);
17 printf(" The network equations using ABCD parameter
   are\n");
18 printf(" V1 = %fV2 - %fI2\n",A,B);
19 printf(" I1 = %fV2 - %fI2\n",C,D);

```

---

**Scilab code Exa 13.8** Obtaining the transmission parameters

```

1 clear;
2 clc;
3 V1=1; R1=1; R2=2; R3=1; R4=2; I2=0;
4 //I2=0 because port 2-2' has been open circuited
5 a=[R1+R2 -R2;-2 5];
6 b=[1;0];
7 b=inv(a)*b;
8 I1=b(1,1);
9 I3=b(2,1);
10 V2=I3*R4;
11 A=V1/V2;
12 C=I1/V2;
13 V21=0; //because port 2-2' has been short circuited
14 c=[3 -2;-2 3];
15 d=[1;0];
16 d=inv(c)*d;
17 I11=d(1,1);
18 I21=d(2,1);
19 B=V1/I21;
20 D=I11/I21;
21 R=(A*D)-(B*C);
22 printf("The transmission parameters are:\n");
23 printf(" A = %f\n",A);
24 printf(" B = %f ohms\n",B);
25 printf(" C = %f mhos\n",C);
26 printf(" D = %f\n\n",D);
27 printf(" AD-BC = %f . Hence the circuit is
reciprocal.",R);

```

---

### Scilab code Exa 13.9 Calculating input impedance

```

1 clear;
2 clc;
3 Rl=3; z11=5; z12=2; z21=2; z22=1;
4 Zi=z11-(z12/z21);

```

```
5 printf("Input impedance = %f ohms", Zi);
```

---

**Scilab code Exa 13.10** Finding ABCD parameters and the equivalent T network

```
1 clear;
2 clc;
3 z11=10; z22=20; z12=5; z21=5;
4 deltaz=(z11*z22)-(z12*z21);
5 A=z11/z12;
6 printf("(a) The ABCD parameters are:\n");
7 printf(" A = %f\n",A);
8 B=deltaz/z21;
9 printf(" B = %f ohms\n",B);
10 C=1/z12;
11 printf(" C = %f mho\n",C);
12 D=z22/z21;
13 printf(" D = %f\n\n",D);
14 Z3=z21;
15 Z1=z11-Z3;
16 Z2=z22-Z3;
17 printf("(b) The equivalent T-network:\n");
18 printf(" Z1 = %f ohms\n",Z1);
19 printf(" Z2 = %f ohms\n",Z2);
20 printf(" Z13 = %f ohms\n",Z3);
```

---

**Scilab code Exa 13.11** Obtaining the parameters Ya and Yb and Yc

```
1 clear;
2 clc;
3 V1=10; I1=2.5; I2a=-0.5; // values with terminals 3-4
    short-circuited
```

```

4 V2=V1; I2b=1.5; // values with terminals 1–2 short
                     circuited
5 Yb=-I2a/V1;
6 Ya=(I1/V1)-Yb;
7 Yc=(I2b/V2)-Yb;
8 printf("-Ya = %f mho\n", Ya);
9 printf("-Yb = %f mhp\n", Yb);
10 printf("-Yc = %f mho", Yc);

```

---

**Scilab code Exa 13.12** Finding the equivalent pi network

```

1 clear;
2 clc;
3 Za=2; Zb=2.5; Zc=5;
4 Ya=1/Za; Yb=1/Zb; Yc=1/Zc;
5 Y1=(Ya*Yc)/(Ya+Yb+Yc);
6 Z1=1/Y1;
7 Y2=(Yb*Yc)/(Ya+Yb+Yc);
8 Z2=1/Y2;
9 Y3=(Ya*Yb)/(Ya+Yb+Yc);
10 Z3=1/Y3;
11 printf("The equivalent pi network is: \n");
12 printf(" Z1 = %f ohms\n", Z1);
13 printf(" Z2 = %f ohms\n", Z2);
14 printf(" Z3 = %f ohms\n", Z3);

```

---

**Scilab code Exa 13.13** Obtaining the z and y and ABCD parameters and the equivalent pi network

```

1 clear;
2 clc;
3 y11=0.5; y12=-0.2; y21=-0.2; y22=1;
4 Y2=-y12;

```

```

5 Y1=y11-Y2;
6 Y3=y22-Y2;
7 deltay=(y11*y22)-(y12*y21);
8 z11=y22/deltay;
9 z22=y11/deltay;
10 z12=y12/deltay;
11 z21=z12;
12 A=-y22/y12;
13 B=-1/y12;
14 C=-deltay/y12;
15 D=-y11/y12;
16 printf("The y parameters are\n");
17 printf(" y11 = %f mho\n",y11);
18 printf(" y12 = %f mho\n",y12);
19 printf(" y21 = %f mho\n",y21);
20 printf(" y22 = %f mho\n\n",y22);
21 printf(" The z parameters are\n");
22 printf(" z11 = %f ohm\n",round(z11*1000)/1000);
23 printf(" z12 = %f ohm\n",round(z12*10^4)/10^4);
24 printf(" z21 = %f ohm\n",round(z21*10^4)/10^4);
25 printf(" z22 = %f ohm\n\n",round(z22*1000)/1000);
26 printf(" The ABCD parametrs are\n");
27 printf(" A = %f\n",A);
28 printf(" B = %f ohm\n",B);
29 printf(" C = %f mho\n",C);
30 printf(" D = %f\n\n",D);
31 printf(" The equivalent pi network is\n");
32 printf(" Y1 = %f mho\n",Y1);
33 printf(" Y2 = %f mho\n",Y2);
34 printf(" Y3 = %f mho",Y3);

```

---

### Scilab code Exa 13.14 Finding y parameters

```

1 clear;
2 clc;

```

```

3 Y1=1;Y2=2;Y3=1;
4 y11=Y1+Y2;
5 y12=-Y2;
6 y21=y12;
7 y22=Y2+Y3;
8 Y11=y11+y11;
9 Y12=y12+y12;
10 Y21=Y12;
11 Y22=y22+y22;
12 printf("The y-parameters are:\n");
13 printf(" Y11 = %f mho\n",Y11);
14 printf(" Y12 = %f mho\n",Y12);
15 printf(" Y21 = %f mho\n",Y21);
16 printf(" Y22 = %f mho\n",Y22);

```

---

**Scilab code Exa 13.15** Determining the ABCD parameters and image impedance

```

1 clear;
2 clc;
3 Za=10;Zb=10;Zc=5;
4 Ya=1/Za;Yb=1/Zb;Yc=1/Zc;
5 A=1+(Za*Yb);
6 printf("The ABCD parameters are:\n");
7 printf(" A = %f\n",A);
8 B=Za+Zb+(Za*Zb*Yc);
9 printf(" B = %f ohm\n",B);
10 C=Yc;
11 printf(" C = %f mho\n",C);
12 D=1+(Zb*Yc);
13 printf(" D = %f \n\n",D);
14 Zi1=sqrt((A*B)/(C*D));
15 printf(" Image impedances of the two port network
are:\n");
16 printf(" Zi1 = %f ohms\n",round(Zi1*10)/10);
17 Zi2=sqrt((D*B)/(A*C));

```

```
18 printf(" Zi2 = %f ohms" ,round(Zi2*100)/100);
```

---

### Scilab code Exa 13.17 Determining the open and short circuit impedance

```
1 clear;
2 clc;
3 R1=2;R2=1;R3=1;R4=2;
4 A=[R1+R2 R2 -R4;R2 R2+R4 R4;-R1 R1 R4+R3+R1];
5 B=det(A);
6 C=[1 R2 -R1;0 R2+R1 R1;0 R4 R4+R3+R1];
7 D=det(C);
8 E=[1 -R1;0 R4+R3+R1];
9 F=[R2+R1 -R1;-R1 R4+R3+R1];
10 G=[R4+R2 0 -R4;R1 1 R4;-R4 0 R4+R2];
11 H=[1 R1;0 R4+R3+R1];
12 I=[R2+R1 R1;R1 R4+R3+R1];
13 printf("Z1s = %d/%d ohms\n",B,D);
14 printf(" Z1o = %d/%d ohms\n",det(F),det(E));
15 printf(" Z2s = %d/%d ohms\n",det(A),det(C));
16 printf(" Z2o = %d/%d ohms\n",det(I),det(H));
```

---

### Scilab code Exa 13.18 Calculating y parameters

```
1 clear;
2 clc;
3 R1=2;R2=1;R3=2;R4=1;R5=2;
4 R3=R3/2;
5 z11=R2+R1;
6 z22=R3+R2;
7 z12=R2;
8 z21=R2;
9 Z11=z11+z11;
10 Z12=z12+z12;
```

```
11 Z21=z21+z21;
12 Z22=z22+z22;
13 deltaZ=(Z11*Z22)-(Z12*Z21);
14 y11=Z22/deltaZ;
15 y12=-Z12/deltaZ;
16 y21=y12;
17 y22=Z11/deltaZ;
18 printf("The y-parameters are:\n");
19 printf("-y11 = %f mho\n",y11);
20 printf("-y12 = %f mho\n",y12);
21 printf("-y21 = %f mho\n",y21);
22 printf("-y22 = %f mho\n",y22);
```

---

### Scilab code Exa 13.19 Determining the image impedances

```
1 clear;
2 clc;
3 R1=3;R2=2;R3=2;
4 A=(R3+R3+R2+R2)/(R1+R3+R1+R2);
5 Zi1=sqrt((R2*(R1+R3)+(R1*R2))/A);
6 printf("Zi1 = %f ohms\n",round(Zi1*10)/10);
7 Zi2=R2+(R3*(R1+Zi1)/(R3+R1+Zi1));
8 printf(" Zi2 = %f ohms\n",round(Zi2*10)/10);
```

---

# Chapter 14

## Filters

**Scilab code Exa 14.1** Calculating values of inductor and capacitor

```
1 clear;
2 clc;
3 Rk=600;fc=3000;
4 L=Rk/(%pi*fc);
5 printf("-Desired value of inductor L = %f mH\n",
       round(L*(10^3)*10)/10);
6 C=1/(%pi*Rk*fc);
7 printf("-Desired value of capacitor C = %f
       microfarads",round(C*(10^6)*10^4)/10^4);
```

---

**Scilab code Exa 14.2** Calculating cut off frequency and attenuation and phase shift

```
1 clear;
2 clc;
3 L=20*(10^-3);C=0.32*(10^-6);f=15*(10^3);
4 fc=(1/(3.14*(sqrt(L*C))));;
5 printf("Cutoff frequency fc = %f kHz\n",fix(fc*0.1)
       /100);
```

```

6 Rk=sqrt(L/C);
7 printf(" Value of nominal terminating impedance Rk =
    %f ohms\n",fix(Rk*10)/10);
8 a=2*(acosh(f/fc));
9 printf(" Value of attenuation a = %f db\n",fix(a
    *8.686*100)/100);
10 printf(" Phase shift of the low pass filter = pi
    radians");

```

---

### Scilab code Exa 14.3 Calculating value of L and C

```

1 clear;
2 clc;
3 fc=10*(10^3);Rk=600;
4 L=Rk/(4*pi*fc);
5 printf("-Value of L = %f mH\n",fix(L*(10^3)*10^3)
    /10^3);
6 C=1/(4*pi*fc*Rk);
7 printf("-Value of C = %f microfarads",fix(C*(10^6)
    *10^5)/10^5);

```

---

### Scilab code Exa 14.4 Determining iterative impedance and cut off frequency and ratio of output voltage to input voltage

```

1 clear;
2 clc;
3 L=60*(10^-3);C=0.2*(10^-6);
4 fc=1/(%pi*(sqrt(L*C)));
5 printf("(i)Cut off frequency fc for the low pass
    filter = %f kHz\n\n",round(fc*(10^-1))/100);
6 fa=1000;
7 Za=(sqrt(L/C))*(sqrt(1-((fa/fc)^2)));

```

```

8 printf(” (ii) Iterative impedance at f=1 KHz = %f
      ohms\n”,fix(Za));
9 fb=5000;
10 Zb=(sqrt(L/C))*(sqrt(1-((fb/fc)^2)));
11 printf(” Iterative impedance at f=5 KHz = j (%f)
      ohms\n\n”,fix(Zb/%i));
12 aa=0; //attenuation at frequency fa
13 ba=2*(asind(fa/fc)); //phase shift at frequency fa
14 ab=2*acosh(fb/fc); //attenuation at frequency fb
15 bb=180; //attenuation at frequency fb
16 V1=exp(aa); //V1=(Vin/Vout) at frequency of 1kHz
17 V2=exp(ab); //V2=(Vin/Vout) at frequency of 5kHz
18 printf(” (iii) At 5kHz, the voltage ratio = %f and
      phase difference = %f degrees\n”,round(V2*10)/10,
      bb);
19 printf(” At 1kHz, the voltage ratio = %f and
      phase difference = %f degrees\n”,V1,fix(ba*10)
      /10);

```

---

**Scilab code Exa 14.5** Determining the elements of a prototype HP T section filter

```

1 clear;
2 clc;
3 fc=1000;Rk=600;
4 L=Rk/(4*pi*fc);
5 C=1/(4*pi*fc*Rk);
6 printf(”Thus, the series elements are two capacitors
      of value %f microfarad each and shunt inductance
      of value %f mH.”,round(C*(10^3)*10^6)/10^5,fix(L
      *(10^3)*100)/100);

```

---

**Scilab code Exa 14.6** Calculating frequency

```

1 clear;
2 clc;
3 a=1.15;
4 F=cosh(a/2);
5 printf("The frequency at which low pass filter will
    have an attenuation 10 db will be %f times the cut
    off frequency", round(F*100)/100);

```

---

**Scilab code Exa 14.7** Designing a m derived T section low pass filter

```

1 clear;
2 clc;
3 Rk=600; fc=1000; fi=1050;
4 L0=Rk/(%pi*fc);
5 C0=1/(%pi*fc*Rk);
6 m=round(sqrt(1-((fc/fi)^2))*10)/10;
7 L1=m*L0/2;
8 printf("-mL/2 = %f mH\n", round(L1*(10^3)*100)/100);
9 C=m*C0;
10 printf("-mC = %f microfarads\n", round(C*(10^6)*1000)
    /1000);
11 L2=L0*((1-(m*m))/(4*m));
12 printf("(1-m^2)L/(4m) = %f mH", L2*(10^3));
13 //the difference in result is due to erroneous value
    in textbook.
14 disp("The difference in result is due to erroneous
    value in textbook")

```

---

**Scilab code Exa 14.8** Designing an m derived T section high pass filter

```

1 clear;
2 clc;
3 fc=20*(10^3); Rk=600; m=0.6;

```

```

4 L0=Rk/(4*pi*fc);
5 C0=1/(4*pi*fc*Rk);
6 C1=2*C0/m;
7 printf("-2C/m = %f microfarads\n", round(C1*(10^6)
     *1000)/1000);
8 L=L0/m;
9 printf("-L/m = %f mH\n", round(L*(10^3)*100)/100)
10 C2=C0*((4*m)/(1-(m*m)));
11 printf("-4mC/(1-m^2) = %f microfarads", round(C2
     *(10^6)*1000)/1000);

```

---

### Scilab code Exa 14.9 Designing a low pass filter

```

1 clear;
2 clc;
3 fc=2000; fi=2050; Rk=500; // fi=frequency at which
      infinite attenuation occurs
4 L0=Rk/(%pi*fc);
5 C0=1/(%pi*fc*Rk);
6 printf("The elements of the constant-K L.P. are :\n")
    ;
7 printf(" L = %f mH\n", fix(L0*(10^3)*10)/10);
8 printf(" C = %f microfarads\n\n", fix(C0*(10^6)
     *1000)/1000);
9 m1=round(sqrt(1-((fc/fi)^2))*100)/100;
10 L1=m1*L0/2;
11 L2=(1-(m1*m1))*L0/(4*m1);
12 C1=m1*C0;
13 printf("The elements of the m-derived L.P.T. filter
      are :\n");
14 printf(" mL/2 = %f mH\n", fix(L1*(10^3)*100)/100);
15 printf(" mC = %f microfarads\n", fix(C1*(10^6)*100
     /100));
16 printf(" (1-m^2)L/4m = %f mH\n\n", fix(L2*(10^3)
     *100)/100);

```

```

17 m2=0.6;
18 L3=m2*L0/2;
19 L4=(1-(m2*m2))*L0/(4*m2);
20 C2=m2*C0;
21 printf("The elements of the terminating half
    sections m-derived L.P.T. filter are:\n");
22 printf(" mL/2 = %f mH\n",fix(L3*(10^3)*10)/10);
23 printf(" mC = %f microfarads\n",fix(C2*(10^6)
    *10000)/10000);
24 printf(" (1-m^2)L/4m = %f mH\n\n",fix(L4*(10^3)*10)
    /10);
25 printf("The complete composite filter is constructed
    by using the constant-K in cascade with the
    short-cut of m-derived section and terminating
    half section");

```

---

### Scilab code Exa 14.10 Designing a high pass composite filter

```

1 clear;
2 clc;
3 fc=1.2*(10^3);fi=1.1*(10^3);Rk=600; // fi=frequency
    at which infinite attenuation occurs
4 L0=Rk/(4*pi*fc);
5 C0=1/(4*pi*fc*Rk);
6 printf("The elements of the constant-K H.P. are:\n")
    ;
7 printf(" L = %f mH\n",fix(L0*(10^3)*100)/100);
8 printf(" C = %f microfarads\n\n",fix(C0*(10^6)*100)
    /100);
9 m1=round(sqrt(1-((fi/fc)^2))*10)/10;
10 C1=2*C0/m1;
11 L1=L0/m1;
12 C2=4*m1*C0/(1-(m1*m1));
13 printf("The elements of the m-derived H.P.T. filter
    are:\n");

```

```

14 printf(" 2C/m = %f microfarads\n", fix(C1*(10^6)
   *100)/100);
15 printf(" L/m = %f mH\n", round(L1*(10^3)*10)/10);
16 printf(" 4mC/(1-m^2) = %f microfarads\n\n", fix(C2
   *(10^6)*100)/100);
17 m2=0.6;
18 C3=2*C0/m2;
19 L2=L0/m2;
20 C4=4*m2*C0/(1-(m2*m2));
21 printf("The elements of the terminating half section
   m-derived H.P.T. filter are:\n");
22 printf(" 2C/m = %f microfarads\n", round(C3*(10^6)
   *100)/100);
23 printf(" L/m = %f mH\n", round(L2*(10^3)*100)/100);
24 printf(" 4mC/(1-m^2) = %f microfarads\n\n", round(C4
   *(10^6)*100)/100);
25 printf("The complete composite filter is constructed
   by using the constant-K in cascade with the
   sharp-cut off m-derived section and terminating
   half section");

```

---

**Scilab code Exa 14.11** Designing a high pass filter and finding the frequency of peak attenuation

```

1 clear;
2 clc;
3 fc=1*(10^6); Rk=75; m=0.6;
4 L0=Rk/(4*pi*fc);
5 C0=1/(4*pi*fc*Rk);
6 printf("The elements of the prototype T-section H.P.
   are:\n");
7 printf("  L = %f mH\n", round(L0*(10^3)*1000)/1000);
8 printf("  C = %f picofarads\n\n", round(C0*(10^12)));
9 C1=2*C0/m;
10 L1=L0/m;

```

```

11 C2=4*m*C0/(1-(m*m));
12 printf(" The elements of the terminating half
           section m-derived H.P.T. filter are:\n");
13 printf(" 2C/m = %f picofarads\n",fix(C1*(10^12)));
14 printf(" L/m = %f mH\n",round(L1*(10^6))/1000);
15 printf(" Cshunt = %f picofarads\n\n",round(C2
           *(10^12)));
16 fi=fc*sqrt(1-(m*m));
17 printf(" Frequency of peak attenuation = %d kHz",fi
           *(10^-3));

```

---

### Scilab code Exa 14.12 Designing a low pass composite filter

```

1 clear;
2 clc;
3 Rk=500; fc=1000; fi1=1065; fi2=1250;
4 L0=Rk/(%pi*fc);
5 C0=1/(%pi*fc*Rk);
6 printf("The elements of the constant-K L.P. are:\n")
      ;
7 printf("  L = %f mH\n",round(L0*(10^3)));
8 printf("  C = %f microfarads\n\n",round(C0*(10^6)
      *100)/100);
9 m1=0.4
10 L1=m1*L0/2;
11 L2=(1-(m1*m1))*L0/(4*m1);
12 C1=m1*C0;
13 printf("The elements of the m-derived L.P.T. filter
           are:\n");
14 printf(" mL/2 = %f mH\n",round(L1*(10^3)*10)/10);
15 printf(" mC = %f microfarads\n",round(C1*(10^6)
      *1000)/1000);
16 printf(" (1-m^2)L/4m = %f mH\n",fix(L2*(10^3)*10)
      /10);
17 m2=sqrt(1-((fc/fi2)^2));

```

```

18 L3=m2*L0/2;
19 L4=(1-(m2*m2))*L0/(4*m2);
20 C2=m2*C0;
21 printf("The elements of the terminating half
sections m-derived L.P.T. filter are:\n");
22 printf(" mL/2 = %f mH\n",fix(L3*(10^3)*10)/10);
23 printf(" C = %f microfarads\n",round(C2*(10^6)
*1000)/1000);
24 printf(" Lshunt = %f mH\n\n",fix(L4*(10^3)*10)/10);
25 printf("The complete composite filter is constructed
by using the constant-K in cascade with the
short-cut of m-derived section and terminating
half section");

```

---

### Scilab code Exa 14.13 Designing a prototype band pass filter

```

1 clear;
2 clc;
3 f1=1000;f2=4000;Rk=600;
4 C1=(f2-f1)/(4*pi*Rk*f1*f2);
5 L1=Rk/(%pi*(f2-f1));
6 C2=1/(%pi*Rk*(f2-f1));
7 L2=Rk*(f2-f1)/(4*pi*f1*f2);
8 printf("The elements of the prototype band pass
filter are:\n");
9 printf(" L1 = %f mH\n",fix(L1*(10^5))/100);
10 printf(" C1 = %f microfarads\n",round(C1*(10^11))
/10^5);
11 printf(" L2 = %f mH\n",round(L2*(10^4))/10);
12 printf(" C2 = %f microfarads",round(C2*(10^10))
/10^4);

```

---

**Scilab code Exa 14.14** Designing a prototype T section of a band pass filter

```
1 clear;
2 clc;
3 f1=12000;f2=16000;Rk=600;
4 C1=(f2-f1)/(4*pi*Rk*f1*f2);
5 L1=Rk/(%pi*(f2-f1));
6 C2=1/(%pi*Rk*(f2-f1));
7 L2=Rk*(f2-f1)/(4*pi*f1*f2);
8 printf("The elements of the prototype band pass
filter are:\n");
9 printf(" L1 = %f mH\n",round(L1*(10^5))/100);
10 printf(" C1 = %f picofarads\n",round(C1*(10^12)));
11 printf(" L2 = %f mH\n",L2*(10^3));
12 printf(" C2 = %f microfarads",C2*(10^6));
13 //the difference in result of L2 and C2 is due to
erroneous value in textbook.
14 disp("The difference in result of C2 and L2 is due
to erroneous value in textbook")
```

---

**Scilab code Exa 14.15** Designing a m derived low pass filter

```
1 clear;
2 clc;
3 fc=5000;fi=1.25*fc;Rk=600; // fi=frequency at which
infinite attenuation occurs
4 L0=Rk/(%pi*fc);
5 C0=1/(%pi*fc*Rk);
6 m=sqrt(1-((fc/fi)^2));
7 L1=m*L0/2;
8 L2=(1-(m*m))*L0/(4*m);
9 C1=m*C0;
10 printf("The elements of the m-derived L.P.T. filter
are:\n");
```

---

```

11 printf(" mL/2 = %f mH\n",round(L1*(10^5))/100);
12 printf(" mC = %f microfarads\n",fix(C1*(10^10))
13 printf(" (1-m^2)L/4m = %f mH",round(L2*(10^4))/10);

```

---

**Scilab code Exa 14.16** Determining the values of shun arm of network

---

```

1 clear;
2 clc;
3 L=0.5*(10^-3);C=0.01*(10^-6);Rk=600;
4 L1=2*L;
5 C1=C/2;
6 L2=Rk*Rk*C1;
7 C2=L1/(Rk*Rk);
8 printf("The elements of the shunt arm will be an
         inductance of %f mH in parallel with a
         capacitance of %f microfarads",L2*(10^3),round(C2
         *(10^10))/10^4);

```

---

**Scilab code Exa 14.17** Designing a low pass composite filter

---

```

1 clear;
2 clc;
3 fc=2400;fi=2500;Rk=600; // fi=frequency at which
                           infinite attenuation occurs
4 L0=Rk/(3.14*fc);
5 C0=1/(3.14*fc*Rk);
6 printf("The elements of the constant-K L.P. are:\n")
       ;
7 printf(" L = %f mH\n",round(L0*(10^5))/100);
8 printf(" C = %f microfarads\n\n",round(C0*(10^10))
       /10^4);
9 m1=sqrt(1-((fc/fi)^2));

```

---

```

10 L1=m1*L0/2;
11 L2=(1-(m1*m1))*L0/(4*m1);
12 C1=m1*C0;
13 printf("The elements of the m-derived L.P.T. filter
           are:\n");
14 printf(" mL/2 = %f mH\n", round(L1*(10^5))/100);
15 printf(" mC = %f microfarads\n", round(C1*(10^10))
           /10^4);
16 printf(" (1-m^2)L/4m = %f mH\n\n", round(L2*(10^5))
           /100);
17 m2=0.6;
18 L3=m2*L0/2;
19 L4=(1-(m2*m2))*L0/(2*m2);
20 C2=m2*C0/2;
21 printf("The elements of the terminating half
           sections m-derived L.P.T. filter are:\n");
22 printf(" mL/2 = %f mH\n", round(L3*(10^5))/100);
23 printf(" mC/2 = %f microfarads\n", round(C2*(10^10))
           /10^4);
24 printf(" (1-m^2)L/2m = %f mH\n\n", fix(L4*(10^5))
           /100);
25 printf("The complete composite filter is constructed
           by using the constant-K in cascade with the
           short-cut of m-derived section and terminating
           half section");

```

---

**Scilab code Exa 14.18** Determining the cut off frequency and characteristic impedance

```

1 clear;
2 clc;
3 C0=1*(10^-6); L0=10*(10^-3);
4 C=C0/2;
5 L=L0;
6 Rk1=sqrt(L/C);

```

```

7 fc1=1/(4*pi*sqrt(L*C));
8 printf("The cut-off frequency( high pass ) = %f Hz\n",
    round(fc1));
9 printf(" The characteristic impedance( high pass ) =
    %f ohms\n\n",round(Rk1*10)/10);
10 C1=C0*2;
11 Rk2=sqrt(L/C1);
12 fc2=1/(%pi*sqrt(L*C1));
13 printf(" The cut-off frequency( low pass ) = %f Hz\n",
    fix(fc2));
14 printf(" The characteristic impedance( low pass ) = %f
    ohms",fix(Rk2*10)/10);

```

---

### Scilab code Exa 14.19 Designing a low pass composite filter

```

1 clear;
2 clc;
3 Rk=500;fc=4000;fi=5000; // fi=frequency at which
    infinite attenuation occurs
4 L0=Rk/(%pi*fc);
5 C0=1/(%pi*fc*Rk);
6 printf("The elements of the constant-K L.P. are:\n")
    ;
7 printf(" L = %f mH\n",round(L0*(10^4))/10);
8 printf(" C = %f microfarads\n\n",round(C0*(10^9))
    /1000);
9 m1=sqrt(1-((fc/fi)^2));
10 L1=m1*L0/2;
11 L2=(1-(m1*m1))*L0/(4*m1);
12 C1=m1*C0;
13 printf("The elements of the m-derived L.P.T. filter
    are:\n");
14 printf(" mL/2 = %f mH\n",round(L1*(10^5))/100);
15 printf(" C = %f microfarads\n",round(C1*(10^10))
    /10^4);

```

```

16 printf(" Lshunt = %f mH\n\n", round(L2*(10^5))/100);
17 m2=0.6;
18 L3=m2*L0/2;
19 L4=(1-(m2*m2))*L0/(2*m2);
20 C2=m2*C0/2;
21 printf("The elements of the terminating half
sections m-derived L.P.T. filter are:\n");
22 printf(" Lseris = %f mH\n", round(L3*(10^5))/100);
23 printf(" C = %f microfarads\n", round(C2*(10^10))
/10^4);
24 printf(" Lshunt = %f mH\n\n", round(L4*(10^5))/100);
25 printf("The complete composite filter is constructed
by using the constant-K in cascade with the
short-cut of m-derived section and terminating
half section");
26 //the difference in result of the elements of the m
derived L.P. T section is due to erroneous value
in textbook.
27 disp("The difference in result of the elements of
the m derived L.P. T section is due to erroneous
value in textbook")

```

---

**Scilab code Exa 14.20** Determining the second resonance frequency

```

1 clear;
2 clc;
3 fr=1*(10^6);C=0.04*(10^-12);C1=6*(10^-12);
4 fa=fr*(1+(C/(2*C1)));
5 printf("The second resonance frequency = %f MHz",
round(fa*(10^-2))/10^4);

```

---

**Scilab code Exa 14.21** Computing the values of elements of filter

```

1 clear;
2 clc;
3 Rk=600; f1=120*(10^3); f2=123*(10^3);
4 C1=(f2-f1)/(4*pi*Rk*f1*f2);
5 L1=Rk/(pi*(f2-f1));
6 C2=L1/(Rk*Rk);
7 L2=Rk*(f2-f1)/(4*pi*f1*f2);
8 printf("The elements of the T-type constant k band
    pass filter are:\n");
9 printf(" L1 = %f mH\n",fix((L1)*(10^4))/10);
10 printf(" C1 = %f picofarads\n",fix((C1)*(10^14))
    /100);
11 printf(" L2 = %f microhenry\n",fix((L2)*(10^7))/10);
12 printf(" C2 = %f microfarads",round((C2)*(10^9))
    /1000);

```

---

### Scilab code Exa 14.22 Calculating bandwidth

```

1 clear;
2 clc;
3 C=1/100; fo=1000; //C=C1/C2
4 //value of fo as taken in solution
5 f1=fo*((sqrt(C+1))-sqrt(C));
6 f2=fo*((sqrt(C+1))+sqrt(C));
7 BW=f2-f1;
8 printf(" Bandwidth = %d Hz", (BW));

```

---

### Scilab code Exa 14.23 Finding the values of the elements of a prototype filter

```

1 clear;
2 clc;
3 Ro=600; f=120; fo=1500; //f=f2-f1

```

```

4 F=f0*f0; //F=f1*f2
5 l1=Ro/(2*pi*f);
6 c1=round(f*10^11/(2*Ro*pi*F))/10^5;
7 c2=round(1*10^8/(%pi*Ro*f))/100;
8 l2=Ro*f/(4*pi*F);
9 n=(1/2)*(sqrt(((2*c2/(c1/2))+9)-1));
10 C1=((2*n)-1)*c1*10^-6/(2*n);
11 C2=c1*10^-6/n;
12 L=n*n*l2;
13 C3=c2*10^-6/(n*n);
14 printf("The elements of the filter are:\n");
15 printf(" (2n-1)C1/n = %f microfarads\n",fix(C1
    *(10^9))/1000);
16 printf(" 2C1/n = %f microfarads\n",fix((C2)*(10^10))
    /10^4);
17 printf(" (n^2)L2 = %f H\n",round(L*10)/10);
18 printf(" C2/(n^2) = %f microfards",round((C3)*(10^9)
    )/1000);

```

---

# Chapter 15

## Equalizers

**Scilab code Exa 15.4** Finding the elements of the lattice

```
1 clear;
2 clc;
3 R0=600;R1=400;L=40*(10^-3);
4 R2=R0*R0/R1;
5 printf("-Other arm of lattice equalizer will have a
      resistance of R2 = %f ohms\n",R2);
6 C=L/(R0*R0);
7 printf(" -R2 resistance will be in parallel with a
      capacitance of C = %f microfarads",round(C*(10^8)
      )/100);
```

---

**Scilab code Exa 15.5** Calculating values of L and C

```
1 clear;
2 clc;
3 R=600;f=4000;
4 a=3;
5 w=2*pi*f;
```

---

```

6 C=sqrt((exp(2*3*0.115)-1)/(4*w*w*R*R));
7 printf("-C = %f microfarads\n", round(C*(10^9))/1000)
    ;
8 L=2*C*R*R;
9 printf(" -L = %f mH", fix(L*(10^5))/100);

```

---

**Scilab code Exa 15.6** Calculating characteristic impedance and the components of the shunt arm of equalizer

---

```

1 clear;
2 clc;
3 R1=1000;C1=0.0212*(10^-6);R2=250;
4 R0=sqrt(R1*R2);
5 printf("Characteristic impedance of line = %f ohms\n
    ",R0);
6 L2=C1*R0*R0;
7 printf("Components of the shunt arm are inductance
        of %f mH in parallel with a given resistance of
        %f ohms.",L2*(10^3),R0);

```

---

**Scilab code Exa 15.10** Calculating value of R and L

---

```

1 clear;
2 clc;
3 R1=1;C=0.05;R0=1;
4 R2=R0*R0/R1;
5 printf("-Series arm will have a resistance R2 = %f
        ohms\n",R2);
6 L=C*R0*R0;
7 printf(" -Value of inductance in parallel with R2 =
        %f henry",L);

```

---

### Scilab code Exa 15.11 Designing a constant resistance equalizer

```
1 clear;
2 clc;
3 f=500; Ro=400; f1=50; D1=17;
4 M1=10^(D1/10);
5 D2=4; f2=2500;
6 M2=10^(D2/10);
7 B=sqrt(((f1*f1*(M1-1))-(f2*f2*(M2-1)))/(M2-M1));
8 A=sqrt((B*B*M2)+(f2*f2*(M2-1)));
9 L11=Ro/(%pi*(A+B));
10 L12=Ro/(%pi*(A-B));
11 R11=L11*%pi*(A-B);
12 R12=L12*%pi*(A+B);
13 R21=Ro*Ro/R11;
14 R22=Ro*Ro/R12;
15 C21=L11/(Ro*Ro);
16 C22=L12/(Ro*Ro);
17 printf("The designed equalizer will have the
        configuration :\n");
18 printf(" I . R1 = %f ohms , C2 = %f microfarads , R2 =
        %f ohms , L1 = %f mH\n",round(R11),round(C21
        *(10^9))/1000,fix(R21),round(L11*(10^4))/10);
19 printf(" II . R1 = %f ohms , C2 = %f microfarads , R2 =
        %f ohms , L1 = %f mH\n",fix(R12),round(C22
        *(10^9))/1000,round(R22),round(L12*(10^3)));
20 M=((A*A)+(f*f))/((B*B)+(f*f));
21 F=10*log10(M);
22 printf(" Loss aat 500Hz = %f db",fix(F*10)/10);
```

---

### Scilab code Exa 15.12 Designing a constant resistance equalizer

```

1 clear;
2 clc;
3 R0=600;D=10;b=10/6;fr=8.5*(10^3);
4 k=round((10^(D/20)*100))/100;
5 fb=fr/b;
6 Cb=1/(2*pi*fb*R0);
7 Lb=R0/(2*pi*fb);
8 printf("The desired bridged-T constant resistance
equalizer will be as:\n");
9 printf("-Ro = %f ohms\n",R0);
10 L1=Lb*((k-1)/sqrt(k))*(((b*b)-1)/(b*b));
11 printf("-L1 = %f Henry\n",round(L1*10^4)/10^4);
12 C1=Cb*(sqrt(k)/(k-1))*(1/((b*b)-1));
13 printf("-C1 = %f microfarads\n",round(C1*(10^10))
/10^4);
14 L2=Lb*((sqrt(k))/(k-1))*(1/((b*b)-1));
15 printf("-L2 = %f Henry\n",round(L2*10^5)/10^5);
16 C2=Cb*((k-1)/sqrt(k))*(((b*b)-1)/(b*b));
17 printf("-C2 = %f microfarads\n",round(C2*(10^10))
/10^4);
18 R1=R0*(k-1);
19 printf("-R1 = %f ohms\n",round(R1));
20 R2=R0/(k-1);
21 printf("-R2 = %f ohms",round(R2));

```

---

### Scilab code Exa 15.13 Designing a lattice equalizer

```

1 clear;
2 clc;
3 f1=200;f2=2400;Li=2.6;Lc1=0.494;Lc2=1.949;Ro=600;
4 //Li=total insertion loss
5 //value of f1 as taken in solution
6 //Lc=cable loss
7 Le1=Li-Lc1; //Le=equalizer loss
8 Le2=Li-Lc2;

```

```

9 M1=fix(exp(2*Le1));
10 M2=round(exp(2*Le2)*100)/100;
11 Q=((f2*f2*(M2-1))-(f1*f1*(M1-1)))/(M1-M2);
12 P=(f1*f1*(M1-1))+(M1*Q);
13 R11b=Ro*(sqrt(P)+sqrt(Q))/(sqrt(P)-sqrt(Q));
14 R21b=Ro*Ro/R11b;
15 L12b=Ro/(%pi*(sqrt(P)-sqrt(Q)));
16 C22b=L12b/(Ro*Ro);
17 L12a=Ro/(%pi*(sqrt(P)+sqrt(Q)));
18 R11a=Ro*(sqrt(P)-sqrt(Q))/(sqrt(P)+sqrt(Q));
19 R21a=Ro*Ro/R11a;
20 C22a=L12a/(Ro*Ro);
21 printf("The required equalizer will have the
         following configuration:\n");
22 printf("I. R11 = %f ohms\n",fix(R11a));
23 printf("-L12 = %f mH\n",round(L12a*(10^4))/10);
24 printf("-R21 = %f ohms\n",round(R21a));
25 printf("-C22 = %f microfarads\n\n",round(C22a*(10^9)
         )/10^3);
26 printf("II. R11 = %f ohms\n",round(R11b));
27 printf("-L12 = %f mH\n",fix(L12b*(10^4))/10);
28 printf("-R21 = %f ohms\n",round(R21b*100)/100);
29 printf("-C22 = %f microfarads",fix(C22b*(10^9))
         /10^3);

```

---

# Chapter 16

## Attenuators

**Scilab code Exa 16.1** Designing a symmetrical bridge T network

```
1 clear;
2 clc;
3 D=40; Ro=600;
4 N=10^(D/20);
5 R3=Ro*(N-1);
6 R2=Ro/(N-1);
7 R1=Ro;
8 printf("R1 = %f ohms\n",R1);
9 printf(" R2 = %f ohms\n",round(R2*100)/100);
10 printf(" R3 = %f k ohms\n",R3*(10^-3));
```

---

**Scilab code Exa 16.2** Designing a T pad attenuator

```
1 clear;
2 clc;
3 D=20; Ro=600;
4 N=10^(D/20);
5 R1=Ro*(N-1)/(N+1);
```

```
6 R2=R0*2*N/((N*N)-1);
7 printf("R1 = %f ohms\n", round(R1*10)/10);
8 printf(" R2 = %f ohms\n", round(R2*10)/10);
```

---

**Scilab code Exa 16.3** Designing a T type attenuator

```
1 clear;
2 clc;
3 D=20; R0=75;
4 N=10^(D/20);
5 R1=R0*(N-1)/(N+1);
6 R2=R0*2*N/((N*N)-1);
7 printf("R1 = %f ohms\n", round(R1*100)/100);
8 printf(" R2 = %f ohms\n", round(R2*100)/100);
```

---

**Scilab code Exa 16.4** Designing an attenuator and determining its equivalent T structure

```
1 clear;
2 clc;
3 D=20; R0=500;
4 N=10^(D/20);
5 R1=R0*(N-1)/(N+1);
6 R2=R0*(N+1)/(N-1);
7 printf("The elements of the attenuator are:\n");
8 printf("R1 = %f ohms\n", round(R1*100)/100);
9 printf(" R2 = %f ohms\n", round(R2*100)/100);
10 r1=R1;
11 r2=(R2-R1)/2;
12 printf("The equivalent T structure of the designed
        lattice:\n");
13 printf(" R1 = %f ohms\n", round(r1*100)/100);
14 printf(" R2 = %f ohms\n", round(r2*100)/100);
```

---

**Scilab code Exa 16.5** Finding the elements of the arm of a T section symmetrical resistive attenuator

```
1 clear;
2 clc;
3 D=15; Ro=75;
4 N=10^(D/20);
5 R1=Ro*(N-1)/(N+1);
6 R2=Ro*2*N/((N*N)-1);
7 printf("The arms of the T section will contain:\n");
8 printf(" R1 = %f ohms\n",round(R1*100)/100);
9 printf(" R2 = %f ohms\n",round(R2*100)/100);
10 //the difference in result of R1 is due to erroneous
    value in textbook.
11 disp("The difference in result of R1 is due to
    erroneous value in textbook")
```

---

**Scilab code Exa 16.6** Calculating the characteristic and attenuation per section of an attenuator

```
1 clear;
2 clc;
3 R1=175; R2=350;
4 y=poly([1 -3 1],"N","coeff");
5 f=roots(y);
6 N=f(1,1);
7 D=20*log10(N);
8 Ro=R1*(N+1)/(N-1);
9 printf("The characteristic impedance of T attenuator
    = %f ohms and its attenuation per section is %f
    db",round(Ro*10)/10,round(D*100)/100);
```

---

**Scilab code Exa 16.7** Determining the resistance value of a T type attenuator pad

```
1 clear;
2 clc;
3 D=40; Ri1=70; Ri2=600;
4 Ai=D*0.115;
5 R3=(sqrt(Ri1*Ri2))/sinh(Ai);
6 R2=(Ri2/tanh(Ai))-R3;
7 R1=(Ri1/tanh(Ai))-R3;
8 printf("The desired elements of T-pad are:\n");
9 printf(" R1 = %f ohms\n", round(R1*100)/100);
10 printf(" R2 = %f ohms\n", round(R2));
11 printf(" R3 = %f ohms\n", round(R3*100)/100);
```

---

**Scilab code Exa 16.8** Finding the elements of a balanced T pad

```
1 clear;
2 clc;
3 D=10; Ri1=150; Ri2=75;
4 Ai=D*0.115;
5 R3=(sqrt(Ri1*Ri2))/sinh(Ai);
6 R2=(Ri2/tanh(Ai))-R3;
7 R1=(Ri1/tanh(Ai))-R3;
8 printf("The desired elements of T-pad are:\n");
9 printf(" R1 = %f ohms\n", round(R1*100)/100);
10 printf(" R2 = %f ohms\n", round(R2*10)/10);
11 printf(" R3= %f ohms\n\n", fix(R3*100)/100);
12 R2a=sqrt((Ri1*Ri2*Ri2)/(Ri1-Ri2));
13 R1a=sqrt(Ri1*(Ri1-Ri2));
14 printf("The minimum loss pad will be a L attenuator
:\n");
```

```
15 printf(" R1 = %f ohms\n",round(R1a));
16 printf(" R2 = %f ohms\n",round(R2a));
```

---

### Scilab code Exa 16.9 Designing L type attenuator

```
1 clear;
2 clc;
3 Ri1=500;D=15;
4 N=10^(D/20);N1=fix(N*1000)/1000;
5 R2=Ri1/(N1-1);
6 R1=Ri1*(1-(1/N));
7 printf("The series arm of the L attenuator is %f
         ohms, while its shunt arm is %f ohms",round(R1),
         round(R2));
8 //the difference in result of R2 is due to erroneous
     value in textbook.
9 disp("The difference in result of R2 is due to
     erroneous value in textbook")
```

---

### Scilab code Exa 16.10 Designing a T pad

```
1 clear;
2 clc;
3 Ri1=50;Ri2=200;p=5;
4 d=p/100;
5 Ai=atanh(1/(1+d));A=fix(Ai*100)/100;
6 R3=(sqrt(Ri1*Ri2))/sinh(A);
7 R2=(Ri2/tanh(A))-R3;
8 R1=(Ri1/tanh(A))-R3;
9 printf("The desired elements of T-pad are:\n");
10 printf(" R1 = %f ohms\n",round(R1));
11 printf(" R2 = %f ohms\n",fix(R2*10)/10);
12 printf(" R3 = %f ohms\n",round(R3*10)/10);
```

---

### Scilab code Exa 16.11 Designing an unbalances pi attenuator

```
1 clear;
2 clc;
3 D=20;Ri1=200;Ri2=500;
4 Ai=D*0.115;
5 Gi1=1/Ri1;Gi2=1/Ri2;
6 G3=(sqrt(Gi1*Gi2))/sinh(Ai);
7 G2=(Gi2/tanh(Ai))-G3;
8 G1=(Gi1/tanh(Ai))-G3;
9 R3=1/G3;R2=1/G2;R1=1/G1;
10 printf("The desired pi attenuator will be:\n");
11 printf(" R1 = %f ohms\n",round(R1*10)/10);
12 printf(" R2 = %f ohms\n",round(R2*10)/10);
13 printf(" R3 = %f ohms\n",round(R3));
14 //the difference in result of R3 is due to erroneous
   value in textbook.
15 disp("The difference in result of R3 is due to
erroneous value in textbook")
```

---

### Scilab code Exa 16.12 Designing a T attenuator

```
1 clear;
2 clc;
3 R1=500;R2=110;
4 Ro=sqrt((2*2*R1*R1/4)+(2*R1*R2));
5 a=acosh(1+(2*R1/(2*R2)));
6 Ri1=Ro;Ri2=150;Ai=round(a*10)/10;
7 R3=(sqrt(Ri1*Ri2))/(fix(sinh(Ai)*100)/100);
8 R2=(Ri2/(round(tanh(Ai)*10^4)/10^4))-(fix(R3*100)
   /100);
```

```
9 R1=(Ri1/(round(tanh(Ai)*10^4)/10^4))-R3;
10 printf("The desired elements of the attenuator are:\n");
11 printf("R1 = %f ohms\n",fix(R1*100)/100);
12 printf("R2 = %f ohms\n",fix(R2*100)/100);
13 printf("R3 = %f ohms\n",fix(R3*100)/100);
```

---

### Scilab code Exa 16.13 Designing a ladder attenuator

```
1 clear;
2 clc;
3 Ro=600;D=5;
4 N=10^(D/20);
5 R1=Ro*(N+1)/(N-1);
6 R2=Ro*((N*N)-1)/(2*N);
7 printf("The desired ladder attenuator will be:\n");
8 printf("R1 = %f ohms\n",round(R1));
9 printf("R2 = %f ohms\n",round(R2));
10 //the difference in result of R1 is due to erroneous
    value in textbook.
11 disp("The difference in result of R1 is due to
    erroneous value in textbook")
```

---

### Scilab code Exa 16.14 Designing an attenuator

```
1 clear;
2 clc;
3 d=12;Ro=500;
4 D=(d-3)/3;
5 N=round(10^(D/20)*1000)/1000;
6 R1=Ro*(N+1)/(N-1);
7 R2=Ro*(round((N*N))-1)/(2*N);
8 printf("The desired attenuator will be:\n");
```

```

9 printf("R1 = %f ohms\n",round(R1));
10 printf("R2 = %f ohms\n",round(R2));
11 //the difference in result of R1 is due to erroneous
   value in textbook.
12 disp("The difference in result of R1 is due to
   erroneous value in textbook")

```

---

**Scilab code Exa 16.15** Designing a balanced attenuator

```

1 clear;
2 clc;
3 d1=0; d2=5; d3=10; d4=15; d5=20; Ro=600;
4 printf("For 0 db loss:\n");
5 printf("  R1 = 0\n  R2 = infinite\n\n");
6 n=4;
7 for i=1:n
8     N=10^(5*i/20);
9     R2=Ro*(N-1);
10    R1=Ro/(N-1);
11    printf("\n For %d db loss:\n",5*i);
12    printf("  R1=%f\n",round(R1));
13    printf("  R2=%f\n",round(R2));
14 end

```

---

**Scilab code Exa 16.16** Finding the attenuation and the values of the shunt resistance of an H type attenuator

```

1 clear;
2 clc;
3 Ro=600; R1=240;
4 R2=((Ro*Ro)-(4*R1*R1))/(4*R1);
5 d=acosh(1+(2*R1/R2));
6 printf("Value of shunt resistance = %d ohm\n",R2);

```

```
7 printf(" Attenuation = %f db" ,round(d*8.686*10)/10);
```

---

### Scilab code Exa 16.17 Designing a L type attenuator

```
1 clear;
2 clc;
3 Ri1=500;d=15;
4 P=d/8.686;
5 N=exp(P);
6 R1=Ri1*(1-(1/N));
7 R2=Ri1/(N-1);
8 printf("The desired attenuator will be:\n");
9 printf(" R1 = %f ohms\n" ,round(R1));
10 printf(" R2 = %f ohms\n" ,round(R2));
```

---

### Scilab code Exa 16.18 Designing a minimum loss pad

```
1 clear;
2 clc;
3 Ri1=72;Ri2=52;
4 R1=Ri1*sqrt(1-(Ri2/Ri1));
5 R2=Ri2*sqrt(1-(Ri2/Ri1));
6 x=sqrt(Ri1/Ri2);
7 L=20*log10(x+(sqrt((x*x)-1)));
8 printf("The desired elements will be:\n");
9 printf(" R1 = %f ohms\n" ,round(R1));
10 printf(" R2 = %f ohms\n" ,fix(R2*10)/10);
11 printf(" Value of loss produced by the network = %f
db" ,round(L));
```

---