

Scilab Textbook Companion for  
Electronic Circuit Analysis And Design  
by D. A. Neamen<sup>1</sup>

Created by  
Priya Apte  
Electrical  
Electrical Engineering  
Indian Institute of Technology Patna  
College Teacher  
NA  
Cross-Checked by  
Ganesh R

August 10, 2013

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electronic Circuit Analysis And Design

**Author:** D. A. Neamen

**Publisher:** McGraw-Hill Education

**Edition:** 2

**Year:** 2001

**ISBN:** 0256119198

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>5</b>
<b>1 Semiconductor materials and diodes</b>	<b>12</b>
<b>2 Diode Circuits</b>	<b>19</b>
<b>3 The Bipolar Junction Transistor</b>	<b>25</b>
<b>4 Basic BJT Amplifiers</b>	<b>37</b>
<b>5 The Field Effect Transistor</b>	<b>44</b>
<b>6 Basic FET Amplifier</b>	<b>54</b>
<b>7 Frequency Response</b>	<b>66</b>
<b>8 Ouput Stages and Power Amplifier</b>	<b>80</b>
<b>9 The Ideal Operational Amplifier</b>	<b>86</b>
<b>10 Integrated Circuit Biasing and Active Loads</b>	<b>88</b>
<b>11 Differential and Multistage Amplifier</b>	<b>96</b>
<b>12 Feedback and Stability</b>	<b>107</b>
<b>13 Operational Amplifier Circuits</b>	<b>114</b>
<b>14 Nonideal Effects in Operational Amplifier Circuits</b>	<b>125</b>

<b>15 Applications and Design of Integrated Circuits</b>	<b>130</b>
<b>16 MOSFET Digital Circuits</b>	<b>136</b>
<b>17 Bipolar Digital Circuits</b>	<b>142</b>

# List of Scilab Codes

Exa 1.1	Calculate intrinsic carrier concentration in silicon . . .	12
Exa 1.2	Calculate thermal equilibrium electron and hole concentrations . . . . .	12
Exa 1.3	Calculate the built in potential barrier of a pn junction	13
Exa 1.4	Calculate the junction capacitance of a pn junction . .	13
Exa 1.5	Determine the diode current in pn junction . . . . .	14
Exa 1.6	Determine the diode voltage and current . . . . .	15
Exa 1.7	Determine the diode voltage and current . . . . .	16
Exa 1.9	Analysing the circuit . . . . .	16
Exa 1.10	Calculate currents in a circuit . . . . .	17
Exa 1.11	Design the value of resistance required to limit the current in given circuit . . . . .	17
Exa 2.1	Compare voltages and the transformer turns ratio in two full wave rectifier circuits . . . . .	19
Exa 2.2	Determine the capacitance required to yield a particular ripple voltage . . . . .	20
Exa 2.3	Design a full wave rectifier . . . . .	21
Exa 2.5	Determine the percent regulation of a voltage regulator	22
Exa 2.8	Determine the output voltage and diode currents . . .	22
Exa 2.10	Calculate the photocurrent generated in a photodiode	23
Exa 2.11	Determine the value of R required to limit the current in circuit . . . . .	23
Exa 3.1	Calculate the collector and emitter currents . . . . .	25
Exa 3.2	Calculate the breakdown voltage of a transistor . . . .	25
Exa 3.3	Calculate the base collector and emitter currents and ce voltage for common emitter circuit . . . . .	26
Exa 3.4	Analyse the common emitter circuit with pnp transistor	26
Exa 3.5	Calculate the currents and voltages in a circuit . . . .	27

Exa 3.6	Calculate the characteristics of a circuit containing an emitter resistor . . . . .	28
Exa 3.7	Calculate the characteristics of a circuit . . . . .	29
Exa 3.9	Calculate the characteristics of an npn bipolar circuit .	30
Exa 3.10	Calculate the currents output voltage and power dissipation . . . . .	31
Exa 3.13	Design the circuit . . . . .	32
Exa 3.14	Analyze a circuit using voltage divider bias circuit and determine the change in Q point . . . . .	32
Exa 3.15	Design a bias stable circuit . . . . .	34
Exa 3.16	Determine the currents in a two transistor current source	34
Exa 3.17	Calculate the dc voltages at each node and the dc currents through the elements in multistage circuit . . .	35
Exa 4.1	Calculate the small signal voltage gain of a bipolar transistor . . . . .	37
Exa 4.2	Determine the small signal voltage gain . . . . .	38
Exa 4.4	Determine the small signal voltage gain . . . . .	38
Exa 4.5	Determine the small signal voltage gain of a common emitter circuit . . . . .	39
Exa 4.7	Determine the small signal voltage gain of a common emitter circuit . . . . .	40
Exa 4.8	Determine the dc and ac load lines . . . . .	41
Exa 4.9	Determine the maximum symmetrical swing . . . . .	42
Exa 4.10	Calculate the small signal voltage gain of an emitter circuit . . . . .	42
Exa 5.1	Calculate the current in an n channel MOSFET . . . .	44
Exa 5.2	Determine the source to drain voltage required to bias p channel MOSFET . . . . .	44
Exa 5.3	Calculate the drain current and drain to source voltage of circuit . . . . .	45
Exa 5.4	Calculate the drain current and drain to source voltage of circuit . . . . .	45
Exa 5.6	Design the dc bias of a MOSFET circuit to produce specified drain current . . . . .	46
Exa 5.7	Design a MOSFET circuit biased with a constant current source . . . . .	47
Exa 5.8	Calculate the characteristics of a circuit containing an enhancement load device . . . . .	48

Exa 5.10	Calculate the characteristics of a circuit containing a depletion load device . . . . .	48
Exa 5.11	Determine the dc transistor currents and voltages in a circuit containing a depletion load device . . . . .	49
Exa 5.13	Determine the currents and voltages in a MOSFET constant current source . . . . .	49
Exa 5.14	Design the size of a power MOSFET to meet the specification of particular switch application . . . . .	50
Exa 5.16	Calculate $I_d$ and $V_{ds}$ in an n channel pn JFET . . . . .	51
Exa 5.17	Design the dc bias of a JFET circuit . . . . .	51
Exa 5.19	Calculate the quiscent current and voltage values . . . . .	52
Exa 5.20	Design a circuit with an enhancement mode MESFET . . . . .	52
Exa 6.1	Calculate the transconductance of an n chennel MOSFET . . . . .	54
Exa 6.2	Determine the small signal voltage gain of a MOSFET . . . . .	54
Exa 6.3	Determine the small signal voltage gain and input and output resistance of a commoon source amplifier . . . . .	55
Exa 6.4	Design the bias of a MOSFET such that the Q point is in the middle of saturation . . . . .	56
Exa 6.6	Determine the small signal voltage gain of a circuit . . . . .	57
Exa 6.7	Determine the small signal voltage gain of a circuit . . . . .	58
Exa 6.9	Calculate the output resistance of a source follower circuit . . . . .	59
Exa 6.11	Design the small signal voltage gain of an NMOS amplifier . . . . .	59
Exa 6.12	Determine the small signal voltage gain of a circuit . . . . .	60
Exa 6.13	Determine the small signal voltage gain of a circuit . . . . .	61
Exa 6.14	Design the biasing of a multistage MOSFET . . . . .	61
Exa 6.15	Design the biasing of cascade circuit . . . . .	62
Exa 6.17	Determine the small signal voltage gain of a circuit . . . . .	63
Exa 6.18	Determine the small signal voltage gain of a circuit . . . . .	64
Exa 6.19	Design a JFET source folllower . . . . .	65
Exa 7.1	Determine the corner frequencies and maximum magnitude asymptotes . . . . .	66
Exa 7.2	Determine the corner frequencies and bandwidth . . . . .	67
Exa 7.3	Determine the corner frequencies and maximum gain . . . . .	67
Exa 7.4	Design the circuit . . . . .	68
Exa 7.5	Determine 3dB frequency . . . . .	69

Exa 7.6	Determine the corner frequencies and maximum gain . . . . .	70
Exa 7.7	Determine the mid gain corner frequencies and bandwidth of a circuit . . . . .	70
Exa 7.8	Determine the corner frequencies and limiting horizontal asymptotes . . . . .	72
Exa 7.9	Determine 3dB frequency . . . . .	73
Exa 7.10	Calculate bandwidth and capacitance . . . . .	73
Exa 7.12	Determine the unity gain bandwidth . . . . .	74
Exa 7.13	Determine the Miller capacitance and cutoff frequency	74
Exa 7.14	Determine the upper corner frequency and midband gain	75
Exa 7.15	Determine the upper corner frequency and midband gain	76
Exa 7.16	Determine the upper corner frequency and midband gain	77
Exa 7.17	Determine the frequency of a zero and a pole . . . . .	78
Exa 8.2	Determine the maximum power dissipation . . . . .	80
Exa 8.3	Determine the maximum safe power dissipation . . . . .	81
Exa 8.7	Determine the required biasing in MOSFET class AB	81
Exa 8.8	Design a transformer coupled emitter follower amplifier	82
Exa 8.9	Design the class AB output stage . . . . .	83
Exa 8.11	Determine the currents and the current gain . . . . .	84
Exa 9.5	Determine a load current in a voltage to current converter	86
Exa 9.9	Determine the time constant . . . . .	87
Exa 10.1	Design a two transistor current source . . . . .	88
Exa 10.2	Determine the change in load current . . . . .	88
Exa 10.4	Design a Widlar current source . . . . .	89
Exa 10.5	Determine the change in load current . . . . .	90
Exa 10.6	Design a generalized current mirror . . . . .	91
Exa 10.7	Design a MOSFET current source . . . . .	91
Exa 10.8	Compare the output resistances . . . . .	92
Exa 10.9	Determine the currents and voltages . . . . .	92
Exa 10.10	Calculate the open circuit voltage gain . . . . .	93
Exa 10.11	Calculate the small signal voltage gain . . . . .	94
Exa 10.12	Calculate the small signal voltage gain . . . . .	94
Exa 11.1	Determine the quiescent collector current and collector emitter voltage . . . . .	96
Exa 11.3	Determine the differential and common mode gains . . . . .	97
Exa 11.7	Determine the CMRR of a differential amplifier . . . . .	97
Exa 11.8	Design a bipolar source . . . . .	98

Exa 11.9	Determine the differential and common mode input resistance . . . . .	98
Exa 11.10	Calculate the dc characteristics of a MOSFET diff amp . . . . .	99
Exa 11.11	Compare the forward transconductance . . . . .	100
Exa 11.12	Determine the differential mode voltage gain common mode voltage gain CMRR . . . . .	100
Exa 11.13	Determine the differential mode voltage gain . . . . .	101
Exa 11.15	Determine the differential mode voltage gain . . . . .	102
Exa 11.16	Calculate the input resistance and the small signal voltage gain . . . . .	102
Exa 11.17	Calculate the output resistance . . . . .	103
Exa 11.19	Determine the differential mode voltage gain . . . . .	104
Exa 11.20	Determine the zero and pole frequencies . . . . .	105
Exa 12.1	Calculate the feedback transfer function . . . . .	107
Exa 12.2	Calculate the percent change in the closed loop gain $A_f$ . . . . .	107
Exa 12.3	Determine the bandwidth of a feedback amplifier . . . . .	108
Exa 12.5	Determine the input resistance and output resistance . . . . .	108
Exa 12.6	Determine the input resistance and output resistance . . . . .	109
Exa 12.7	Determine the expected input resistance . . . . .	109
Exa 12.11	Determine the transconductance gain of a transistor feedback circuit . . . . .	110
Exa 12.16	Determine the loop gain . . . . .	111
Exa 12.19	Determine the stability of an amplifier . . . . .	112
Exa 12.22	Determine the shift in the 3dB frequency . . . . .	112
Exa 12.23	Determine the shift in the 3dB frequency . . . . .	112
Exa 13.1	Calculate the dc currents . . . . .	114
Exa 13.2	Calculate the bias currents . . . . .	115
Exa 13.3	Calculate the bias currents . . . . .	115
Exa 13.4	Determine the small signal differential voltage gain . . . . .	116
Exa 13.5	Determine the small signal voltage gain . . . . .	118
Exa 13.6	Calculate the output resistance . . . . .	119
Exa 13.7	Determine the dominant pole frequency of the 741 op amp . . . . .	120
Exa 13.9	Determine the small signal voltage gain . . . . .	120
Exa 13.10	Determine the differential mode voltage gain . . . . .	121
Exa 13.12	Determine the small signal voltage gain . . . . .	122
Exa 13.13	Determine the small signal voltage gain . . . . .	123

Exa 13.14	Determine the dominant pole frequency and unity gain bandwidth . . . . .	123
Exa 14.2	Determine the closed loop input resistance . . . . .	125
Exa 14.3	Determine the closed loop input resistance . . . . .	125
Exa 14.5	Determine the unity gain bandwidth and the closed loop gain . . . . .	126
Exa 14.6	Calculate the slew rate of the 741 op amp . . . . .	126
Exa 14.7	Determine the small signal bandwidth of an amplifier and full power bandwidth . . . . .	127
Exa 14.8	Calculate the offset voltage in bipolar diff amp . . . . .	127
Exa 14.10	Calculate the offset voltage in MOSFET diff amp . . . . .	127
Exa 14.11	Determine the range of voltage produced by an offset voltage compensation network . . . . .	128
Exa 14.13	Determine the bias current effect . . . . .	128
Exa 15.2	Determine the clock frequency . . . . .	130
Exa 15.3	Design a one pole low pass switched capacitor filter . . . . .	130
Exa 15.4	Determine the oscillation frequency and required amplifier gain . . . . .	131
Exa 15.6	Determine the hysteresis width of a particular Schmitt trigger . . . . .	131
Exa 15.7	Design a Schmitt trigger circuit . . . . .	132
Exa 15.10	Design the 555IC as a monostable multivibrator . . . . .	132
Exa 15.13	Design the supply voltage . . . . .	133
Exa 15.14	Determine the output resistance and load regulation . . . . .	133
Exa 15.15	Determine the output resistance and variation in output voltage . . . . .	133
Exa 15.16	Determine the bias current temperature compensated reference voltage and required resistor . . . . .	134
Exa 16.3	Design the aspect ratio and determine the power dissipation . . . . .	136
Exa 16.4	Design the aspect ratio and determine the power dissipation . . . . .	137
Exa 16.5	Determine the noise margin of an inverter with enhancement load . . . . .	137
Exa 16.9	Determine the critical voltage on the voltage transfer curve of a CMOS inverter . . . . .	138
Exa 16.10	Calculate the power dissipation in CMOS inverter . . . . .	139
Exa 16.11	Determine the noise margins of a CMOS inverter . . . . .	139

Exa 16.15	Determine the currents voltages and power dissipation in two NMOS SPAM cells . . . . .	140
Exa 17.1	Calculate the currents and voltages in the basic differential amplifier circuit used as digital circuit . . . . .	142
Exa 17.2	Calculate the currents resistors and logic 0 values in the basic ECL logic gate . . . . .	143
Exa 17.3	Design the reference position of the ECL circuit . . . . .	144
Exa 17.4	Calculate the power dissipated in the ECL logic circuit	145
Exa 17.5	Calculate minimum fanout of ECL logic gate . . . . .	145
Exa 17.7	Analyze the modified ECL logic gate . . . . .	146
Exa 17.9	Calculate the currents and voltages for the basic TTL NAND circuit . . . . .	147
Exa 17.11	Determine the currents in a Schottky transistor . . . . .	148
Exa 17.12	Calculate the power dissipation in a low power Schottky TTL circuit . . . . .	149

# Chapter 1

## Semiconductor materials and diodes

**Scilab code Exa 1.1** Calculate intrinsic carrier concentration in silicon

```
1 clear;
2 clc;
3 //Example 1.1
4 T=300; //(( K )temperature)
5 //for silicon
6 B=5.23*10^(15); //Constant ( per centimeter cube
    degree kelvin )
7 Eg=1.1; //bandgap energy in electrovolt (eV)
8 k=86*10^(-6); //Boltzmann's constant (eV per degree
    kelvin )
9 n_i=B*T^(3/2)*exp(-Eg/(2*k*T)); //intrinsic carrier
    concentration
10 printf('intrinsic carrier concentration=%f cm^-3' ,
    n_i);
```

---

**Scilab code Exa 1.2** Calculate thermal equilibrium electron and hole concentrations

```

1 clear;
2 clc;
3 //Example 1.2
4 T=300; //( K ) Given Temperature
5 Nd=10^16; //(cm^-3) Donor concentration
6 n_i=1.5*10^10; //(cm^-3) intrinsic carrier
    concentration
7 //since Nd>>n_i
8 n_o=10^16; //(cm^-3) electron concentration
9 //by using formula :: n_i^2=n_o*p_o
10 p_o=(n_i)^2/Nd; //hole concentration
11 printf ('\nelectron concentration=%e cm^-3',n_o);
12 printf ('\n hole concentration =%e cm^-3',p_o);

```

---

**Scilab code Exa 1.3** Calculate the built in potential barrier of a pn junction

```

1 clear;
2 clc;
3 //Example1.3
4 T=300; //( K ) Given Temperature
5 Na=10^16; //(cm^-3) Acceptor concentration in p region
6 Nd=10^17; //(cm^-3) Donor concentration in n region
7 n_i=1.5*10^10; //(cm^-3) intrinsic carrier
    concentration
8 V_T=0.026; //(Volt) terminal voltage
9 //built-in potential
10 V_bi=V_T*log(Na*Nd/(n_i)^2);
11 printf ('\nthe built-in potential=%f V',V_bi)

```

---

**Scilab code Exa 1.4** Calculate the junction capacitance of a pn junction

```
1 clear;
```

```

2 clc;
3 //Example 1.4
4 T=300; //( K ) Given Temperature
5 Na=10^16; //(cm^-3) Acceptor concentration in p region
6 Nd=10^15; //(cm^-3) Donor concentration in n region
7 n_i=1.5*10^10; //(cm^-3) intrinsic carrier
    concentration
8 C_jo=0.5; //(pF) junction capacitance at zero applied
    voltage
9 V_T=0.026; //(Volt) terminal voltage
10 //built-in potential
11 V_bi=V_T*log(Na*Nd/(n_i)^2);
12 disp(V_bi,"the built-in potential(V)")
13 //the junction capacitance for
14 V_R=1; //(V) reverse bias voltage
15 Cj=C_jo*(1+V_R/V_bi)^(-1/2);
16 printf ('\nthe junction capacitance for V_R=1V=%f pF\
    ',Cj)
17 V_R=5; //(V) reverse bias voltage
18 Cj=C_jo*(1+V_R/V_bi)^(-1/2);
19 printf ('\nthe junction capacitance for V_R=5V =%f pF
    ',Cj)

```

---

**Scilab code Exa 1.5** Determine the diode current in pn junction

```

1 clear;
2 clc;
3 //Example 1.5
4 T=300; //( K ) Given Temperature
5 V_T=0.026; //(Volt) terminal voltage
6 Is=10^-11; //(mA) reverse bias saturation current
7 n=1; //emission coefficient
8 v_D=+0.7; //(V) applied voltage
9 //pn junction is forward biased
10 i_D=Is*(exp(v_D/V_T)-1); //diode current

```

```

11 printf ('\n diode current=%f mA\n', i_D)
12 v_D=-0.7; // (V) pn junction is reverse biased
13 Is=10^-14 //A;
14 i_D=Is*(exp(v_D/V_T)-1); // diode current
15 printf ('\n diode current=%e A', i_D)

```

---

**Scilab code Exa 1.6** Determine the diode voltage and current

```

1 clear;
2 clc;
3 //Example 1.6
4 Is=10^-13; // (A) reverse saturation current
5 V_PS=5; // (V) applied voltage
6 R=2; // (KOhm) Resistance in circuit
7 V_T=0.026; // (Volt) terminal voltage
8 //V_PS=Is*R*(exp(V_D/V_T)-1)+V_D
9 //5=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
10 // let right side of equation be x=(10^-13)*(2000)*(
    exp(V_D/V_T)-1)+V_D
11 V_D=0.6; // (V)
12 x=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
13 // so the equation is not balanced
14 V_D=0.65; // (V)
15 x=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
16 // again equation is not balanced . solution for V_D
    is between 0.6V and 0.65V
17 V_D=0.619; // (V)
18 x=(10^-13)*(2000)*(exp(V_D/V_T)-1)+V_D
19 // essentially equal to the value of the left side of
    the equation i.e 5V
20 printf ('\n diode voltage=%f V', V_D)
21 I_D=(V_PS-V_D)/R; // (A) diode current
22 printf ('\n the diode current=%f mA', I_D)

```

---

**Scilab code Exa 1.7** Determine the diode voltage and current

```
1 clear;
2 clc;
3 //Example 1.7
4 //piecewise linear diode parameters
5 V_Y=0.6; //(V)
6 r_f=0.010; //(KOhm)
7 V_PS=5; //(V) applied voltage
8 R=2; //(KOhm) Resistance in circuit
9 I_D=(V_PS-V_Y)/(R+r_f); //(A) diode current
10 printf ('\nthe diode current=%f mA\n', I_D)
11 V_D=V_Y+I_D*r_f; //(V) diode voltage
12 printf ('\ndiode voltage=%f V', V_D)
```

---

**Scilab code Exa 1.9** Analysing the circuit

```
1 clear;
2 clc;
3 //Example 1.9
4 //circuit and diode parameters
5 V_PS=5; //(V)
6 R=5; //(KOhm)
7 V_Y=0.6; //(V)
8 V_T=0.026; //(Volt) terminal voltage
9 v_i=0.1 /*sin (wt) Volt
10 //dc analysis
11 I_DQ=(V_PS-V_Y)/R;
12 printf ('\ndc quiescent current=%f mA\n', I_DQ)
13 V_O=I_DQ*R;
14 printf ('\ndc output voltage=%f V\n', V_O)
15 //ac analysis
```

```

16 V_PS=0;
17 //Kirchhoff voltage law equation becomes
18 //v_i=i_d*r_d+i_d*R
19 r_d=V_T/I_DQ//(Ohm) small signal diode diffusion
   resistance
20 i_d=v_i/(r_d+R); //ac diode current
21 printf ('\nac diode current=%fsin(wt) A\n',i_d)
22
23 v_o=i_d*R; //ac output voltage
24 printf ('\nac output voltage=%fsin(wt) V',v_o)

```

---

**Scilab code Exa 1.10** Calculate currents in a circuit

```

1 clear;
2 clc;
3 //Example 1.10
4 V_Y=0.7;//(V) cut in voltage for pn junction
5 r_f=0;
6 V_PS=4;//(V)
7 R1=4,R2=4//(KOhm) from given circuit
8 I1=(V_PS-V_Y)/R1;
9 printf ('\ncurrent through pn junction diode=%.3f mA\n',
   I1)
10 V_Y=0.3;//(V) cut in voltage for Schottky diode
11 I2=(V_PS-V_Y)/R2;
12 printf ('\ncurrent through Schottky diode=%.3f mA\n',
   I2)

```

---

**Scilab code Exa 1.11** Design the value of resistance required to limit the current in given circuit

```

1 clear;
2 clc;

```

```
3 //Example 1.11
4 V_Z=5.6; // (V) Zener diode breakdown voltage
5 r_z=0; // (Ohm) Zener resistance
6 I=3; // (mA) current in the diode
7 V_PS=10; // (V)
8 // I=(V_PS-V_Z)/R
9 R=(V_PS-V_Z)/I;
10 printf ('\n resistance=%f KOhm\n',R)
```

---

# Chapter 2

## Diode Circuits

**Scilab code Exa 2.1** Compare voltages and the transformer turns ratio in two full wave rectifier circuits

```
1 clear;
2 clc;
3 //Example 2.1
4 v_I=120; //(V) rms primary input
5 v_o=9; //(V) peak output voltage
6 V_Y=0.7; //(V) diode cut in voltage
7 //for center-tapped transformer circuit in fig.2.6(a)
8 v_S=v_o+V_Y//(V) peak value of secondary voltage
9 printf('\npeak value of secondary voltage=%f V\n',v_S)
10 v_S_rms=v_S/sqrt(2)//for a sinusoidal signal rms
   value of v_S
11 printf('\nrms value of v_S=%f V\n',v_S_rms)
12 //let turns ratio of the primary to secondary
   winding be x=N1/N2
13 x=v_I/v_S_rms;
14 printf('\nturns ratio=%f \n',x)
15 //for the bridge circuit in fig.2.7(a)
16 v_Sb=v_o+2*V_Y;//(V) peak value of secondary voltage
```

```

17 printf ('\npeak value of secondary voltage=%f V\n', v_Sb)
18 v_S_rms=v_Sb/sqrt(2); //for a sinusoidal signal rms
    value of v_S
19 printf ('\nrms value of v_S=%f V\n', v_S_rms)
20 //let turns ratio of the primary to secondary
    winding be x=N1/N2
21 x=v_I/v_S_rms;
22 printf ('\nturns ratio=%f\n',x)
23 //for center tapped rectifier
24 PIV=2*v_S-V_Y;
25 printf ('\npeak inverse voltage of a diode=%f V\n', PIV)
26 //for the bridge rectifier peak inverse voltage of a
    diode
27 PIV=v_Sb-V_Y;
28 printf ('\npeak inverse voltage of a diode=%f V\n', PIV)
29 //advantage of bridge rectifier over center tapped
    rectifier is it requies only half of the turns

```

---

**Scilab code Exa 2.2** Determine the capacitance required to yield a particular ripple voltage

```

1 clear;
2 clc;
3 //Example 2.2
4 // full wave rectifier circuit with 60Hz input signal
5 V_M=10; //(V)peak output voltage
6 R=0.01; //(MOhm)output load resistance
7 f=60; //Hz
8 V_r=0.2; //(V)ripple voltage
9 C=V_M/(2*f*R*V_r); //capacitance
10 printf ('\ncapacitance=%f microF\n',C)

```

---

### Scilab code Exa 2.3 Design a full wave rectifier

```
1 clear;
2 clc;
3 //Example 2.3
4 V_0=12; //(V) peak output voltage
5 I_L=0.12; //(A) current delivered to the load
6 R=V_0/I_L;
7 printf ('\n effective load resistance=%f Ohm\n',R)
8 V_Y=0.7; //(V) diode cut in voltage
9 v_S=V_0+2*V_Y;
10 printf ('\n peak value of v_S=%f V\n',v_S)
11 v_Srms=v_S/sqrt(2);
12 printf ('\n rms voltage=%f V\n',v_Srms)
13 //let x=N1/N2
14 Vin=120; //(V) input line voltage
15 x=Vin/v_Srms;
16 printf ('\n turns ratio=%f \n',x)
17 VM=12; //(V)
18 Vr=5/100*VM;
19 printf ('\n ripple voltage=%f V\n',Vr)
20 f=60; //(Hz) input frequency
21 C=VM/(2*R*Vr*f);
22 printf ('\n filter capacitance=%f F\n',C)
23 i_Dmax=(VM/R)*(1+2*pi*sqrt(VM/(2*Vr)));
24 printf ('\n peak diode current=%f A\n',i_Dmax)
25 R=0.1; //Kohm
26 i_Davg=(1/(2*pi))*sqrt(2*Vr/VM)*((VM/R)*(1+pi*sqrt
    (VM/(2*Vr))));
27 printf ('\n average diode current=%f mA\n',i_Davg)
28 PIV=v_S-V_Y;
29 printf ('\n peak inverse voltage=%f V\n',PIV)
```

---

**Scilab code Exa 2.5** Determine the percent regulation of a voltage regulator

```

1 clear;
2 clc;
3 //Example 2.5
4 rZ=4; //(Ohm) Zener resistance
5 V_Lnom=9; //(V) nominal output voltage
6 Izmax=0.3; //(A) maximum zener diode current
7 Izmin=0.03; //(A) minimum zener diode current
8 V_Lmax=V_Lnom+Izmax*rZ
9 V_Lmin=V_Lnom+Izmin*rZ
10 //percent regulation R
11 R=((V_Lmax-V_Lmin)/V_Lnom)*100;
12 printf('npercent regulation=%0.1f \n',R)

```

---

**Scilab code Exa 2.8** Determine the output voltage and diode currents

```

1 clear;
2 clc;
3 //Example 2.8
4 R1=5; R2=10; //(KOhm)
5 V_Y=0.7; //(V) diode cut in voltage
6 V1=5; V2=-5; //(V)
7 vt=0; //(V)
8 //asssuming initially diode D1 is off
9 //iR1=iD2=iR2=V1-V2-V_Y/(R1+R2)
10 iD2=(V1-V2-V_Y)/(R1+R2);
11 printf('ndiode current=%0.2f mA\n',iD2)
12 iR1=iD2;
13 vo=V1-iR1*R1;
14 printf('noutput voltage=%0.2f V\n',vo)

```

```

15 v=vo-V_Y; //v=v'
16 printf ('\\nVoltage=%0.1f V\\n' ,v)
17 vt=4; //(V) fig .2.33
18 //both D1 and D2 are on
19 vo==vt;
20 vo=4;
21 iD2=(V1-vo)/R1;
22 printf ('\\ndiode current=%0.2f mA\\n' ,iD2)
23 iR1==iD2;
24 v=vo-V_Y;
25 printf ('\\nV=%0.2f V\\n' ,v)
26 iR2=(v-V2)/R2;
27 printf ('\\niR2=%0.2f mA\\n' ,iR2)
28 iD1=iR2-iD2;
29 printf ('\\nCurrent through D1=%0.2f mA\\n' ,iD1)

```

---

**Scilab code Exa 2.10** Calculate the photocurrent generated in a photodiode

```

1 clear;
2 clc;
3 //Example 2.10
4 n=1; //quantum efficiency
5 A=10^-2; //cm^2 junction area
6 p=5*10^17; //cm^-2-s^-1 incident photon flux
7 e=1.6*10^-16; //charge of an electron
8 Iph=n*e*p*A;
9 printf ('\\nphotocurrent=%0.1f mA\\n' ,Iph)

```

---

**Scilab code Exa 2.11** Determine the value of R required to limit the current in circuit

```
1 clear;
```

```
2 clc;
3 //Example 2.11
4 I=0.01; // (A) diode current
5 V_Y=1.7; // (V) forward bias voltage drop
6 Vt=0.2; // (V)
7 R=(5-V_Y-Vt)/I;
8 printf ('\n resistance=%0.1 f Ohm',R)
```

---

# Chapter 3

## The Bipolar Junction Transistor

**Scilab code Exa 3.1** Calculate the collector and emitter currents

```
1 clear;
2 clc;
3 //Example 3.1
4 //let beta be "b"
5 b=150; //common emitter current gain
6 iB=15*10^-3; //(mA) base current
7 //assume transistor biased in forward active mode
8 iC=b*iB;
9 printf ('\ncollector current=%.2f mA\n',iC)
10 iE=(1+b)*iB;
11 printf ('\nemitter current=% .2f mA\n',iE)
12 a=b/(1+b);
13 printf ('\ncommon base current gain=% .3f \n',a)
```

---

**Scilab code Exa 3.2** Calculate the breakdown voltage of a transistor

```

1 clear;
2 clc;
3 //Example 3.2
4 b=100; //common emitter current gain
5 BVcbo=120; //(V) break down voltage of the B-C
    junction
6 n=3; //empirical constant
7 BVceo=BVcbo/(b)^(1/n);
8 printf ('\nbreakdown voltage=%f V\n',BVceo)

```

---

**Scilab code Exa 3.3** Calculate the base collector and emitter currents and ce voltage for common emitter circuit

```

1 clear;
2 clc;
3 //Example 3.3
4 Vbb=4; //(V)
5 Rb=220//(KOhm) ;
6 Rc=2;//(KOhm)
7 Vcc=10; //(V)
8 Vbe=0.7;//(V)
9 b=200;
10 //from fig .3.19(b)
11 Ib=(Vbb-Vbe)/Rb;
12 printf ('\nbase current=%f mA\n',Ib)
13 Ic=b*Ib;
14 printf ('\ncollector current=%f mA\n',Ic)
15 Ie=(1+b)*Ib;
16 printf ('\nemitter current=%f mA\n',Ie)
17 Vce=Vcc-Ic*Rc;
18 printf ('\ncollector emitter voltage=%f V\n',Vce)

```

---

**Scilab code Exa 3.4** Analyse the common emitter circuit with pnp transistor

```
1 clear;
2 clc;
3 //Example 3.4
4 Vbb=1.5; //(V)
5 Rb=580; //(KOhm)
6 Veb=0.6; //(V)
7 Vcc=5; //(V)
8 b=100;
9 //writing Kirchhoff voltage law equation around E-B
   loop
10 Ib=(Vcc-Veb-Vbb)/Rb;
11 printf ('\nbase current=%.3f mA\n', Ib)
12 Ic=b*Ib;
13 printf ('\ncollector current=%.2f mA\n', Ic)
14 Ie=(1+b)*Ib;
15 printf ('\nemitter current=%.3f mA\n', Ie)
16 Vec=(1/2)*Vcc;
17 printf ('\nce voltage=%.2f V\n', Vec)
18 Rc=(Vcc-Vec)/Ic;
19 printf ('\ncollector resistance=%.f KOhm\n', Rc)
```

---

**Scilab code Exa 3.5** Calculate the currents and voltages in a circuit

```
1 clear;
2 clc;
3 //Example 3.5
4 b=100;
5 Vbe=0.7; //(V)
6 Vce=0.2; //(V)
7 Vbb=8; //(v)
8 Rb=220; //(KOhm)
9 Ib=(Vbb-Vbe)/Rb
```

```

10 printf ('\nbase current=%f mA\n', Ib)
11 //transistor in active region
12 Ic=b*Ib;
13 printf ('\ncollector current=%.3f mA\n', Ic)
14 Vcc=10; //(V)
15 Rc=4; //(KOhm)
16 Vce=Vcc-Ic*Rc;
17 printf ('\ncollector emitter voltage=%.2f V\n', Vce)
18 //saturation
19 Vce=0.2; //(V)
20 Ic=(Vcc-Vce)/Rc;
21 printf ('\nsaturation collector current=%.2f mA\n', Ic
    )
22 x=Ic/Ib
23 //which is <b
24 Ie=Ic+Ib;
25 printf ('\nemitter current=%f mA\n', Ie)

```

---

**Scilab code Exa 3.6** Calculate the characteristics of a circuit containing an emitter resistor

```

1 clear;
2 clc;
3 //Example 3.6
4 Vbe=0.7;
5 b=75;
6 //Q point values::
7 //using KVL eq around the B-E loop
8 //Vbb=Ib*Re+Vbe+Ie*Re
9 //assuming transistor is in forward biased mode we
   can write Ie=(1+b)*Ib
10 Vbb=6;
11 Rb=25; //KOhm
12 Re=0.6; //KOhm
13 Ib=(Vbb-Vbe)/(Rb+(1+b)*Re);

```

```

14 printf ('\nbase current=%f mA\n', Ib)
15 Ic=b*Ib;
16 printf ('\ncollector current=%0.2f mA\n', Ic)
17 Ie=(1+b)*Ib;
18 printf ('\nemitter current=%0.2f mA\n', Ie)
19 Vcc=12;
20 Rc=0.4;
21 Vce=Vcc-Ic*Rc-Ie*Re;
22 printf ('\ncollector emitter voltage=%0.2f V\n', Vce)
23 //load line::
24 //using KVL law around C-E loop
25 //Vce=Vcc-(Ic*(Rc+((1+B)/B)*Re));
26 Ic=[0,12,5.63]
27 Vce=12-Ic*1;
28 xset ('window',1)
29 plot2d(Vce,Ic,style=3)
30 title("load line")
31 xlabel("Vce")
32 ylabel("Ic")

```

---

### Scilab code Exa 3.7 Calculate the characteristics of a circuit

```

1 clear;
2 clc;
3 //Example 3.7
4 Vbe=0.65;
5 Vcc=5;
6 Rc=0.5; //KOhm
7 b=100;
8 V1=-5;
9 Re=1; //KOhm
10 // Q-point values :: writing KVL eq around B-E loop
11 Ie=(-V1-Vbe)/Re;
12 printf ('\nemitter current=%0.2f mA\n', Ie)
13 Ib=(Ie/(1+b));

```

```

14 printf ('\nbase current=%f mA\n', Ib)
15 Ic=(b/(1+b))*Ie;
16 printf ('\ncollector current=%0.2f mA\n', Ic)
17 Vce=Vcc-Ic*Rc-Ie*Re-V1;
18 printf ('\ncollector emitter voltage=%f V\n', Vce)
19 //load line::
20 //Vce=Vcc-V1-(Ic*(Rc+((1+B)/B)*Re));
21 Vce=[0,2,,3.5,4,6,8,10]
22 Ic=(10-Vce)/1.51;
23 xset ('window',1)
24 plot2d(Vce,Ic,style=3,rect=[0,0,10,8])
25 title("load line")
26 xlabel("Vce")
27 ylabel("Ic")

```

---

**Scilab code Exa 3.9** Calculate the characteristics of an npn bipolar circuit

```

1 clear;
2 clc;
3 //Example 3.9
4 b=100;
5 Vbe=0.7;
6 V1=-5;
7 V2=12;
8 Rb=10;
9 Re=5;
10 Rc=5;
11 Rl=5;
12 //Q point values:: using KVL eq around B-E loop
13 Ib=-(V1+Vbe)/(Rb+(1+b)*Re);
14 printf ('\nbase current=%f mA\n', Ib)
15 Ic=b*Ib;
16 printf ('\ncollector current=%f mA\n', Ic)
17 Ie=(1+b)*Ib;
18 printf ('\nemitter current=%f mA\n', Ie)

```

```

19 // at collector node we can write  $I_c = (V_2 - V_o) / R_c - V_o / R_l$ 
20  $V_o = (V_2 / R_c - I_c) * R_c * R_l / (R_c + R_l);$ 
21 printf( '\noutput voltage=%0.3f V\n' ,  $V_o$  )
22  $V_{ce} = V_o - I_e * R_e - V_1;$ 
23 printf( '\ncollector emitter voltage=%f V\n' ,  $V_{ce}$  )
24 // load line::
25  $R_{th} = R_l * R_c / (R_l + R_c);$ 
26 printf( '\nThevenin equivalent resistance=%f KOhm\n' ,
 $R_{th}$  )
27  $V_{th} = (R_l / (R_l + R_c)) * V_2;$ 
28 printf( '\nThevenin equivalent voltage=%f V\n' ,  $V_{th}$  )
29 // fig.3.36(c) KVL law
30 //  $V_{ce} = 6 - V_1 - I_c * R_{th} - I_e * R_e;$ 
31  $V_{ce} = [0, 2, 4.7, 3.5, 4, 6, 8, 10]$ 
32  $I_c = (11 - V_{ce}) / 7.5;$ 
33 xset( 'window' , 1)
34 plot2d(  $V_{ce}$  ,  $I_c$  , style=3 , rect=[0, 0, 12, 2] )
35 title("load line")
36 xlabel("Vce")
37 ylabel("Ic")

```

---

**Scilab code Exa 3.10** Calculate the currents output voltage and power dissipation

```

1 clear;
2 clc;
3 //Example 3.10
4  $R_b = 0.24;$ 
5  $V_{cc} = 12;$ 
6  $V_{be} = 0.7;$ 
7  $V_{ce} = 0.1;$ 
8  $b = 75;$ 
9  $R_c = 5; //Ohm$ 
10 //for  $V_t = 0$  , transistor is cut off ,  $I_b = I_c = 0$ ,  $V_o = V_{cc} = 12$ 
   V, power dissipation is zero

```

```

11 Vt=12; // (V)
12 Ib=(Vt-Vbe)/Rb;
13 printf ('\nbase current=%0.3f mA\n', Ib)
14 Ic=(Vcc-Vce)/Rc;
15 printf ('\ncollector current=%0.2f A\n', Ic)
16 Ib=0.0471; //A
17 x=Ic/Ib
18 //since Ic/Ib<b transistor is in saturation
19 //Vo==Vcc;
20 Vo=0.1;
21 printf ('\noutput voltage=%0.2f V\n', Vo)
22 P=Ic*Vce+Ib*Vbe;
23 printf ('\npower dissipation=%0.3f W\n', P)

```

---

**Scilab code Exa 3.13** Design the circuit

```

1 clear;
2 clc;
3 //Example 3.13
4 b=100;
5 Vcc=12;
6 Vbe=0.7;
7 Icq=1; //mA
8 Vceq=6;
9 Rc=(Vcc-Vceq)/Icq;
10 printf ('\ncollector resistance=%.3f KOhms\n', Rc)
11 Ibq=Icq/b;
12 printf ('\nbase current=%0.3f mA\n', Ibq)
13 Rb=(Vcc-Vbe)/Ibq;
14 printf ('\nbase resistance=%0.3f KOhms\n', Rb)

```

---

**Scilab code Exa 3.14** Analyze a circuit using voltage divider bias circuit and determine the change in Q point

```

1 clear;
2 clc;
3 //Example 3.14
4 R1=56;
5 R2=12.2;
6 Rc=2;
7 Re=.4;
8 Vcc=10;
9 Vbe=0.7;
10 b=100;
11 //fig.3.53(b)
12 Rth=R2*R1/(R1+R2);
13 printf ('\nThevenin rquivalent resistance=%0.1f KOhm\
n',Rth)
14 Vth=(R2/(R1+R2))*Vcc;
15 printf ('\nThevenin equivalent voltage=%0.2f V\n',Vth
)
16 Ibq=(Vth-Vbe)/(Rth+(1+b)*Re);
17 printf ('\nbase current=%f mA\n',Ibq)
18 Icq=b*Ibq;
19 printf ('\ncollector current=%.3f mA\n',Icq)
20 Ieq=(1+b)*Ibq;
21 printf ('\nemitter current=% .2f mA\n',Ieq)
22 Vceq=Vcc-Icq*Rc-Ieq*Re;
23 printf ('\ncollector emitter voltage=% .3f V\n',Vceq)
24 b=[50,100,150]
25 for x=b
26 Ibq=(Vth-Vbe)/(Rth+(1+x)*Re);
27 disp ("Ibeq ,Iceq ,Ieq ,Vceq")
28 disp (Ibq)
29 Icq=x*Ibq;
30 disp (Icq)
31 Ieq=(1+x)*Ibq;
32 disp (Ieq)
33 Vceq=Vcc-Icq*Rc-Ieq*Re;
34 disp (Vceq)
35 disp ("")
36 end

```

---

### Scilab code Exa 3.15 Design a bias stable circuit

```
1 clear;
2 clc;
3 //Example 3.15
4 Vcc=5;
5 Rc=1; //KOhm
6 Vbe=0.7;
7 b=120;
8 Vceq=3;
9 Re=.510;
10 Icq=(Vcc-Vceq)/(Rc+Re);
11 printf ('\ncollector current=%.3f mA\n',Icq)
12 Ibq=Icq/b;
13 printf ('\nbase current=%0.3f mA\n',Ibq)
14 //for bias stable circuit
15 Rth=0.1*(1+b)*Re;
16 printf ('\nThevenin rquivalent resistance=%.1f KOhm\n
      ',Rth)
17 //Ibq=(Vth-Vbe)/(Rth+(1+b)*Re)
18 Vth=Ibq*(Rth+(1+b)*Re)+Vbe;
19 printf ('\nThevenin equivalent voltage=%.2f V\n',Vth)
20 //Vth=(R2/(R1+R2))*Vcc
21 //let x=(R2/(R1+R2))
22 x=Vth/Vcc
23 //Rth=6050=R1*x
24 R1=6.05/x;
25 printf ('\nR1=%.1f KOhms\n',R1)
26 R2=x*R1/(1-x);
27 printf ('\nR2=%.1f KOhms\n',R2)
```

---

**Scilab code Exa 3.16** Determine the currents in a two transistor current source

```
1 clear;
2 clc;
3 //Example 3.16
4 R1=10;
5 b=50;
6 Vbe=0.7;
7 V1=-5;
8 I1=-(V1+Vbe)/R1;
9 printf ('\nreference current=%.3f mA\n', I1)
10 Iq=I1/(1+2/b);
11 printf ('\nbias current=%.3f mA\n', Iq)
12 //Ib=Ib1=Ib2
13 Ib=Iq/b;
14 printf ('\nbase current=%f mA\n', Ib)
```

---

**Scilab code Exa 3.17** Calculate the dc voltages at each node and the dc currents through the elements in multistage circuit

```
1 clear;
2 clc;
3 //Example 3.17
4 Vbe=0.7;
5 Vcc=10;
6 V2=5;
7 b=100;
8 R1=100;
9 R2=50;
10 Re1=2;
11 Rth=R2*R1/(R1+R2);
12 printf ('\nThevenin equivalent resistance=%.1f KOhm\n', Rth)
13 Vth=(R2/(R1+R2))*Vcc-V2;
```

```

14 printf ('\nThevenin equivalent voltage=%f V\n',Vth)
15 //Vth=Ib1*Rth+Vbe+Ie1*Re1-5 and Ie1=(1+b)*Ib1
16 Ib1=(Vth+5-Vbe)/(Rth+(1+b)*Re1);
17 printf ('\nIb1=%f mA\n',Ib1)
18 Ic1=b*Ib1;
19 printf ('\nIc1=%f mA\n',Ic1)
20 Ie1=(1+b)*Ib1;
21 printf ('\nIe1=%f mA\n',Ie1)
22 //summing the currents at the collector of Q1,Ir1+
    Ib2=Ic1
23 //(5-Vc1)/Rc1+Ib2=Ic1
24 //also Ib2=Ie2/(1+b)=(5-(Vc1+0.7))/(1+b)*Re2
25 Rc1=5;
26 Re1=2;
27 Re2=2;
28 Rc2=1.5;
29 Vc1=Rc1*(1+b)*Re2*((5/Rc1)+(4.3/((1+b)*Re2))-Ic1)
    /(((1+b)*Re2)+Rc1);
30 printf ('\nVc1=%f V\n',Vc1)
31 Ir1=(5-Vc1)/Rc1;
32 printf ('\nIr1=%f mA\n',Ir1)
33 Ve2=Vc1+Vbe;
34 printf ('\nVe2=%f V\n',Ve2)
35 Ie2=(5-Ve2)/Re1;
36 printf ('\nIe2=%f mA\n',Ie2)
37 Ic2=Ie2*b/(1+b);
38 printf ('\nIc2=%f mA\n',Ic2)
39 Ib2=Ie2/(1+b);
40 printf ('\nIb2=%f mA\n',Ib2)
41 Ve1=Ie1*Re1-5;
42 printf ('\nVe1=%f V\n',Ve1)
43 Vc2=Ic2*Rc2-5;
44 printf ('\nVc2=%f V\n',Vc2)
45 Vce1=Vc1-Ve1;
46 printf ('\nVce1=%f V\n',Vce1)
47 Vec2=Ve2-Vc2;
48 printf ('\nVec2=%f V\n',Vec2)

```

---

# Chapter 4

## Basic BJT Amplifiers

**Scilab code Exa 4.1** Calculate the small signal voltage gain of a bipolar transistor

```
1 clear;
2 clc;
3 //Example 4.1
4 b=100;
5 Vcc=12;
6 Vbe=0.7;
7 Rc=6;
8 Rb=50;
9 Vbb=1.2;
10 //dc solution
11 Ibq=(Vbb-Vbe)/Rb;
12 printf ('\nbase current=%.3f mA\n',Ibq)
13 Icq=b*Ibq;
14 printf ('\ncollector current=%.3f mA\n',Icq)
15 Vceq=Vcc-Icq*Rc;
16 printf ('\ncollector emitter voltage=%.2f V\n',Vceq)
17 //transistor is forward biased
18 //ac solution
19 V_T=0.026; //(V)
20 //small signal hybrid pi parameters
```

```

21 r_pi=b*V_T/Icq;
22 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
23 g_m=Icq/V_T;
24 printf ('\ntransconductance=%f mA/V\n',g_m)
25 //Av=Vo/Vs=-(g_m*Rc)*r_pi/(r_pi+Rb)
26 Av=-(g_m*Rc)*r_pi/(r_pi+Rb);
27 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

**Scilab code Exa 4.2** Determine the small signal voltage gain

```

1 clear;
2 clc;
3 //Example 4.2
4 V_pi=50; //(V)
5 Icq=1; //(mA)
6 ro=V_pi/Icq;
7 printf ('\nsmall signal output resistance=%f KOhm\n',
     ,ro)
8 Rc=6;
9 g_m=38.5;
10 r_pi=2.6;
11 Rb=50;
12 Av=-(g_m)*(Rc*ro/(Rc+ro))*r_pi/(r_pi+Rb);
13 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

**Scilab code Exa 4.4** Determine the small signal voltage gain

```

1 clear;
2 clc;
3 //Example 4.4
4 b=100;
5 Vbe=0.7;
6 Va=100;

```

```

7 V_T=0.026; // (V)
8 //from dc analysis
9 Icq=0.95;
10 Vceq=6.31;
11 //ac analysis
12 r_pi=b*V_T/Icq;
13 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
14 g_m=Icq/V_T;
15 printf ('\ntransconductance=%f mA/V\n',g_m)
16 Rs=0.5;
17 Rc=6;
18 ro=Va/Icq;
19 printf ('\nro=%f KOhm\n',ro)
20 Av=-g_m*(5.9*r_pi/(5.9+r_pi))/((5.9*r_pi/(r_pi+5.9))
    +Rs)*ro*Rc/(ro+Rc);
21 printf ('\nsmall signal voltage gain=%f \n',Av)
22 Ri=5.9*r_pi/(r_pi+5.9);
23 printf ('\ninput resistance=%f KOhm\n',Ri)
24 Ro=ro*Rc/(ro+Rc);
25 printf ('\noutput resistance=%f KOhm\n',Ro)

```

---

**Scilab code Exa 4.5** Determine the small signal voltage gain of a common emitter circuit

```

1 clear;
2 clc;
3 //Example 4.5
4 b=100;
5 Vbe=0.7;
6 Rc=2;
7 Rs=0.5;
8 Icq=2.16;
9 V_T=0.026; // (V)
10 Vceq=4.8
11 //ac solution

```

```

12 r_pi=b*V_T/Icq;
13 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
14 g_m=Icq/V_T;
15 printf ('\ntransconductance=%f mA/V\n',g_m)
16 //since Va=infinity , ro=Va/Icq is also infinity
17 Re=0.4;
18 Rib=r_pi+(1+b)*Re;
19 printf ('\ninput resistance to the base=%f KOhm\n',
        Rib)
20 //Ri=R1||R2||Rib
21 Ri=10*Rib/(10+Rib);
22 printf ('\ninput resistance to the amplifier=%f
          KOhm\n',Ri)
23 Av=-(1/(r_pi+(1+b)*Re))*b*Rc*Ri/(Ri+Rs);
24 printf ('\nsmall signal voltage gain=%f \n',Av)
25 //by approximate expression
26 Av=-Rc/Re;
27 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

**Scilab code Exa 4.7** Determine the small signal voltage gain of a common emitter circuit

```

1 clear;
2 clc;
3 //Example 4.7
4 Iq=0.5;
5 b=120;
6 Va=80;
7 V_T=0.026; //(V)
8 rc=120; //small signal collector resistance (KOhm)
9 //Icq=Iq
10 Icq=0.5;
11 g_m=Icq/V_T;
12 printf ('\ntransconductance=%f mA/V\n',g_m)
13 ro=Va/Icq;

```

```

14 printf ('\nsmall signal output resistance=%f KOhm\n
      ,ro)
15 Av=-g_m*ro*rc/(ro+rc);
16 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

**Scilab code Exa 4.8** Determine the dc and ac load lines

```

1 clear;
2 clc;
3 //Example 4.8
4 b=150; Veb=0.7;
5 //dc solution
6 V2=10;
7 V1=-10;
8 V_T=0.026; //(V)
9 Rc=5;
10 Rb=50;
11 Re=10;
12 Ibq=(V2-Veb)/(Rb+(1+b)*Re);
13 printf ('\nbase current=%f mA\n',Ibq)
14 Icq=b*Ibq;
15 printf ('\ncollector current=%f mA\n',Icq)
16 Ieq=(1+b)*Ibq;
17 printf ('\nemitter current=%f mA\n',Ieq)
18 Vecq=V2-V1-Icq*Rc-Ieq*Re;
19 printf ('\nemitter collector voltage=%f V\n',Vecq)
20 //ac solution
21 r_pi=b*V_T/Icq;
22 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
23 g_m=Icq/V_T;
24 printf ('\ntransconductance =%fmA/V\n',g_m)
25 //since Va=infinity ,ro=Va/Icq is also infinity

```

---

**Scilab code Exa 4.9** Determine the maximum symmetrical swing

```
1 clear;
2 clc;
3 //Example 4.9
4 Ic=0.894;
5 i_C=2*Ic;
6 printf('\nmaximum possible symmetrical peak to peak
    ac collector current=%f mA\n',i_C)
7 Rc=5;
8 Rl=2;
9 vo=i_C*Rc*Rl/(Rc+Rl);
10 printf('\nmaximum possible symmetrical peak to peak
    output voltage=%f V\n',vo)
11 iC=Ic+i_C*1/2;
12 printf('\nmaximum instantaneous collector current=%
    .3 f mA\n',iC)
```

---

**Scilab code Exa 4.10** Calculate the small signal voltage gain of an emitter circuit

```
1 clear;
2 clc;
3 //Example 4.10
4 b=100;
5 Vbe=0.7;
6 V_T=0.026; //(V)
7 Re=2;
8 R1=50;
9 R2=50;
10 Rs=0.5;
11 Va=80;
12 //by dc analysis
13 Icq=0.793;
14 Vceq=3.4;
```

```

15 r_pi=b*V_T/Icq;
16 printf ('\nsmall signal resistance=%f KOhm\n',r_pi)
17 g_m=Icq/V_T;
18 printf ('\ntransconductance=%f mA/V\n',g_m)
19 ro=Va/Icq;
20 printf ('\nsmall signal output resistance=%f KOhm\n
      ',ro)
21 Rib=r_pi+(1+b)*Re*ro/(ro+Re);
22 printf ('\ninput resistance to the base=%f KOhm\n',
      Rib)
23 //Ri=R1||R2||Rib
24 x=R1*R2/(R1+R2);
25 Ri=x*Rib/(x+Rib);
26 printf ('\nRi=%f KOhm\n',Ri)
27 y=ro*Re/(ro+Re);
28 Av=(1/(r_pi+(1+b)*y))*(1+b)*y*Ri/(Ri+Rs);
29 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

# Chapter 5

## The Field Effect Transistor

**Scilab code Exa 5.1** Calculate the current in an n channel MOSFET

```
1 clear;
2 clc;
3 //Example 5.1
4 Vtn=0.75; //(V)
5 W=40*10^-6; //(cm)
6 L=4*10^-6; //(cm)
7 u=650; //(cm)
8 Iox=450*10^-11;
9 e=3.9*8.86*10^-14;
10 Kn=W*u*e/(2*L*Iox);
11 printf ('\nconduction parameter=%f mA/V^2\n',Kn)
12 Vgs=2*Vtn;
13 i_D=Kn*(Vgs-Vtn)^2;
14 printf ('\ndrain current=%f mA\n',i_D)
```

---

**Scilab code Exa 5.2** Determine the source to drain voltage required to bias p channel MOSFET

```

1 clear;
2 clc;
3 //Example 5.2
4 Kp=0.2; // (mA/V^2)
5 Vtp=0.5;
6 iD=0.5;
7 Vsg=sqrt(iD/Kp)-Vtp;
8 printf ('\nVgs=%f V\n',Vsg)
9 //to bias in p channel MOSFET
10 Vsd=Vsg+Vtp;
11 printf ('\nVsd=%f V\n',Vsd)

```

---

**Scilab code Exa 5.3** Calculate the drain current and drain to source voltage of circuit

```

1 clear;
2 clc;
3 //Example 5.3
4 R1=30;
5 R2=20;
6 RD=20;
7 Vdd=5;
8 Vtn=1;
9 Kn=0.1;
10 Vgs=R2*Vdd/(R1+R2);
11 printf ('\nVgs=%f V\n',Vgs)
12 I_D=Kn*(Vgs-Vtn)^2;
13 printf ('\nthe drain current=%f mA\n',I_D)
14 Vds=Vdd-I_D*RD;
15 printf ('\ndrain to source voltage=%f V\n',Vds)

```

---

**Scilab code Exa 5.4** Calculate the drain current and drain to source voltage of circuit

```

1 clear;
2 clc;
3 //Example 5.4
4 R1=50;
5 R2=50;
6 RD=7.5;
7 Vdd=5;
8 Vtp=-0.8;
9 Vg=2.5;
10 Kp=0.2;
11 Vo=R2*Vdd/(R1+R2);
12 printf ('\nVo=%f V\n',Vo)
13 Vsg=Vdd-Vg;
14 printf ('\nsource to gate voltage=%f V\n',Vsg)
15 I_D=Kp*(Vsg+Vtp)^2;
16 printf ('\nthe drain current=%f mA\n',I_D)
17 Vsd=Vdd-I_D*RD;
18 printf ('\nsource to drain voltage=%f V\n',Vsd)

```

---

**Scilab code Exa 5.6** Design the dc bias of a MOSFET circuit to produce specified drain current

```

1 clear;
2 clc;
3 //Example 5.6
4 Vtn=2;
5 Kn=80*10^-3;
6 //x=W/L
7 x=4;
8 I_D=0.5;
9 //I_D=Kn*x*((Vgs-Vtn)^2)/2;
10 Vgs=sqrt(I_D*2/(Kn*x))+2;
11 printf ('\nVgs=%f V\n',Vgs)
12 //y=R1+R2
13 Rs=2;

```

```

14 y=10/0.05;
15 printf ('\\nR1+R2=% .2 f Kohm\\n' ,y)
16 //Vgs=Vg-Vs=(R2/(R1+R2)*10-5)-I_D*Rs+5
17 R2=(y/10)*(Vgs+I_D*Rs);
18 printf ('\\nR2=% .2 f KOhm\\n' ,R2)
19 R1=y-R2;
20 printf ('\\nR1=% .2 f KOhm\\n' ,R1)

```

---

**Scilab code Exa 5.7** Design a MOSFET circuit biased with a constant current source

```

1 clear;
2 clc;
3 //Example 5.7
4 Vtn=0.8;
5 Kn=80;
6 //x=W/L
7 x=3;
8 I_D=250;
9 Vd=2.5;
10 //I_D=Kn/2*x*(Vgs-Vtn)^2
11 Vgs=sqrt(I_D*2/(Kn*x))+Vtn;
12 printf ('\\nVgs=% .3 f V\\n' ,Vgs)
13 Vs=-Vgs
14 //I_D=(5-Vd)/Rd
15 Rd=(5-Vd)/I_D;
16 printf ('\\nRd=% .2 f KOhm\\n' ,Rd)
17 Vds=Vd-Vs;
18 printf ('\\nVds=% .2 f V\\n' ,Vds)
19 Vdssat=Vgs-Vtn
20 //since Vds>Vdssat transistor is biased in
      saturation region

```

---

**Scilab code Exa 5.8** Calculate the characteristics of a circuit containing an enhancement load device

```
1 clear;
2 clc;
3 //Example 5.8
4 Vtn=0.8;
5 Kn=0.05;
6 //I_D=Kn*(Vgs-Vtn)^2
7 //Vds=Vgs=5-I_D*Rs
8 //combining these two equations we obtain 0.5(Vgs)
     ^2+0.2Vgs-4.68
9 Vgs=poly(0,'Vgs')
10 p=poly([-4.68 0.2 0.5], 'Vgs', 'c')
11 printf('\npossible solutions ::%.3f V\n', roots(p))
12 //assuming transistor is conducting ,Vgs must be
     greater than threshold voltage
13 Vgs=2.87;
14 I_D=Kn*(Vgs-Vtn)^2;
15 printf ('\ndrain current=% .3f mA\n', I_D)
```

---

**Scilab code Exa 5.10** Calculate the characteristics of a circuit containing a depletion load device

```
1 clear;
2 clc;
3 //Example 5.10
4 Vtn=-2;
5 Kn=0.1;
6 Vdd=5;
7 Rs=5;
8 Vgs=0;
9 I_D=Kn*(Vgs-Vtn)^2;
10 printf ('\ndrain current=% .3f mA\n', I_D)
11 Vds=Vdd-I_D*Rs;
```

```
12 printf ('\n dc drain to source voltage=%f V\n', Vds)
13 Vdssat=Vgs-Vtn
14 //since Vds>Vdssat transisyor is biased in
    saturation region
```

---

**Scilab code Exa 5.11** Determine the dc transistor currents and voltages in a circuit containing a depletion load device

```
1 clear;
2 clc;
3 //Example 5.11
4 Vtnd=1;
5 Vtnl=-2;
6 Knd=50;
7 Knl=10;
8 Vt=5;
9 Vo=poly(0, 'Vo')
10 p=poly([4 -40 5], 'Vo', 'c')
11 printf ('\npossible solutions ::%f V\n', roots(p))
12 //since output voltage cannot be greater than supply
    voltage 5V
13 Vo=0.1; //(V)
14 I_D=Knl*(-Vtnl)^2;
15 printf ('\n drain current=%f microA\n', I_D)
```

---

**Scilab code Exa 5.13** Determine the currents and voltages in a MOSFET constant current source

```
1 clear;
2 clc;
3 //Example 5.13
4 Kn1=0.2;
5 Kn2=0.1;
```

```

6 Kn3=0.1;
7 Kn4=0.1;
8 Vtn1=1;
9 Vtn2=1;
10 Vtn3=1;
11 Vtn4=1;
12 V2=-5;
13 Vgs3=(sqrt(Kn4/Kn3)*(-V2-Vtn4)+Vtn3)/(1+sqrt(Kn4/Kn3
    ));
14 printf ('\nVgs3=%f V\n',Vgs3)
15 Iq=Kn3*(Vgs3-Vtn3)^2;
16 printf ('\nbias current=%f mA\n',Iq)
17 Vgs1=sqrt(Iq/Kn1)+Vtn1;
18 printf ('\ngate to source voltage on M1=%f V\n',
    Vgs1)
19 Vds2=-V2-Vgs1;
20 printf ('\ndrain to source voltage on M2=%f V\n',
    Vds2)
21 Vgs2=Vgs3;
22 Vdssat=Vgs2-Vtn2
23 //since Vds2>Vdssat M2 is biased in saturation
    region

```

---

**Scilab code Exa 5.14** Design the size of a power MOSFET to meet the specification of particular switch application

```

1 clear;
2 clc;
3 //Example 5.14
4 I_D=0.5;
5 Vds=6;
6 Kn=80*10^-6;
7 Vgs=5;
8 Vtn=1;
9 //x=W/L

```

```

10 x=I_D*(Kn*(Vgs-Vtn)^2);
11 disp(x,"W/L ")
12 //maximum power dissipation in transistor
13 Pmax=Vds*I_D;
14 printf('\nmaximum power dissipation in transistor=%
.3 f W\n',Pmax)

```

---

**Scilab code Exa 5.16** Calculate Id and Vds in an n channel pn JFET

```

1 clear;
2 clc;
3 //Example 5.16
4 Idss=2; //(mA) saturation current
5 Vp=-3.5;//(V) pinch off voltage
6 Vgs=[0 Vp/4 Vp/2]
7 I_D=Idss*(1-Vgs/Vp)^2;
8 disp(I_D,"I_D (A)")
9 Vds=Vgs-Vp;
10 disp(Vds,"Vdssat (V)")

```

---

**Scilab code Exa 5.17** Design the dc bias of a JFET circuit

```

1 clear;
2 clc;
3 //Example 5.17
4 Idss=5; //mA
5 Vp=-4;
6 Vdd=10;
7 I_D=2;
8 Vds=6;
9 //I_D=Idss*(1-Vgs/Vp)^2
10 Vgs=(1-sqrt(I_D/Idss))*Vp;
11 printf ('\nVgs=% .2 f V\n',Vgs)

```

```

12 Rs=-Vgs/I_D;
13 printf ('\nRs=%f KOhm\n',Rs)
14 Rd=(Vdd-Vds-I_D*Rs)/I_D;
15 printf ('\nRd=%f KOhm\n',Rd)
16 Vgs-Vp
17 // since Vds>Vgs-Vp JFET is biased in saturation

```

---

**Scilab code Exa 5.19** Calculate the quiscent current and voltage values

```

1 clear;
2 clc;
3 //Example 5.19
4 Idss=2.5;
5 Vp=2.5;
6 I_D=0.8;
7 //I_D=Iq=0.8*10^-3=(Vd-(-9))/Rd
8 Vd=0.8*4-9;
9 printf ('\nVd =%fV\n',Vd)
10 //I_D=Idss*(1-Vgs/Vp)^2;
11 Vgs=(1-sqrt(I_D/Idss))*Vp;
12 printf ('\nVgs =%fV\n',Vgs)
13 Vs=1-Vgs;
14 printf ('\nVs=%f V\n',Vs)
15 Vsd=Vs-Vd;
16 printf ('\nVsd=%f V\n',Vsd)
17 Vp-Vgs
18 // since Vsd>Vp-Vgs JFET is biased in saturation

```

---

**Scilab code Exa 5.20** Design a circuit with an enhancement mode MES-FET

```

1 clear;
2 clc;

```

```

3 //Example 5.20
4 Vtn=0.24;
5 Kn=1.1;
6 //x=R1+R2=50000
7 x=50;
8 Vgs=0.5;
9 Vds=2.5;
10 Vdd=4;
11 Rd=6.7;
12 I_D=Kn*(Vgs-Vtn)^2;
13 printf( '\ndrain current=%f mA\n' , I_D)
14 Vd=Vdd-I_D*Rd;
15 printf( '\nvoltage at drain=%f V\n' , Vd)
16 Vs=Vd-Vds;
17 printf( '\nvoltage at source =%f fV\n' , Vs)
18 Rs=Vs/I_D;
19 printf( '\nsource resistance =%f KOhm\n' , Rs)
20 Vg=Vgs+Vs;
21 printf( '\nvoltage at the gate=%f V\n' , Vg)
22 //Vg=R2*Vdd/(R2+R1)
23 R2=Vg*x/Vdd;
24 printf( '\nR2=%f KOhm\n' , R2)
25 R1=x-R2;
26 printf( '\nR1=%f KOhm\n' , R1)
27 Vgs-Vtn
28 //since Vds>Vgs-Vtn transistor is biased in
    saturation

```

---

# Chapter 6

## Basic FET Amplifier

**Scilab code Exa 6.1** Calculate the transconductance of an n chennel MOS-FET

```
1 clear;
2 clc;
3 //Example 6.1
4 Vtn=1;
5 //let x= u_n*Cox*1/2
6 x=20*10^-3;
7 //let y=W/L
8 y=40;
9 I_D=1;
10 Kn=x*y;
11 printf('nconduction parameter=%f mA/V^2\n',Kn)
12 g_m=2*sqrt(Kn*I_D);
13 printf('ntransconductance=%f mA/V\n',g_m)
```

---

**Scilab code Exa 6.2** Determine the small signal voltage gain of a MOS-FET

```

1 clear;
2 clc;
3 //Example 6.2
4 Vgsq=2.12;
5 Vdd=5;
6 Rd=2.5;
7 Vtn=1;
8 Kn=0.8;
9 //let lambda=y
10 y=0.02; //V^-1
11 Idq=Kn*(Vgsq-Vtn)^2;
12 printf ('\n drain current=%.3f mA\n', Idq)
13 Vdsq=Vdd-Idq*Rd;
14 printf ('\n drain to source voltage=% .3f V\n', Vdsq)
15 Vgs=1.82;
16 Vgs-Vtn
17 //since Vdsq>Vgs-Vtn transistor is biased in
   saturation
18 g_m=2*Kn*(Vgsq-Vtn);
19 printf ('\n transconductance=% .3f mA/V\n', g_m)
20 ro=(y*Idq)^-1;
21 printf ('\n output resistance=% .2f KOhm\n', ro)
22 Av=-g_m*ro*Rd/(ro+Rd);
23 printf ('\n small signal voltage gain=% .2f\n', Av)

```

---

**Scilab code Exa 6.3** Determine the small signal voltage gain and input and output resistance of a common source amplifier

```

1 clear;
2 clc;
3 //Example 6.3
4 Vdd=10;
5 R1=70.9; // (Kohm)
6 R2=29.1; // (Kohm)
7 Rd=5; // (Kohm)

```

```

8 Vtn=1.5;
9 Kn=0.5; // (mA/V^2)
10 //lambda=y
11 y=0.01; //V^-1
12 Rsi=4; //(Kohm)
13 Vgsq=Vdd*R2/(R1+R2);
14 printf ('\ngate to source voltage=%f V\n',Vgsq)
15 Idq=Kn*(Vgsq-Vtn)^2;
16 printf ('\ndrain current=%f mA\n', Idq)
17 Vdsq=Vdd-Idq*Rd;
18 printf ('\ndrain to source voltage=%f V\n',Vdsq)
19 g_m=2*Kn*(Vgsq-Vtn);
20 printf ('\ntransconductance=%f mA/V\n',g_m)
21 ro=(y*Idq)^-1;
22 printf ('\noutput resistance=%f KOhm\n',ro)
23 Ri=R1*R2/(R1+R2);
24 printf ('\namplifier input resistance=%f Kohm\n',Ri
)
25 Av=-g_m*(ro*Rd/(ro+Rd))*Ri/(Ri+Rsi);
26 printf ('\nsmall signal voltage gain=%f\n',Av)
27 printf ('\namplifier input resistance=%f Kohm\n',Ri
)
28 Ro=Rd*ro/(Rd+ro);
29 printf ('\namplifier output resistance=%f Kohm\n',
Ro)

```

---

**Scilab code Exa 6.4** Design the bias of a MOSFET such that the Q point is in the middle of saturation

```

1 clear;
2 clc;
3 //Example 6.4
4 Vtn=1;
5 Kn=1; // (mA/V^2)
6 //lambda=y

```

```

7 y=0.015; //V^-1
8 Ri=100; // (Kohm)
9 Idq=2; //(mA)
10 Idt=4; //(mA)
11 //Idt=4=Kn*( Vgst-Vtn ) ^2
12 Vgst=sqrt( Idt/Kn)+Vtn;
13 printf( '\nVgst=%f V\n',Vgst)
14 Vdst=Vgst-Vtn;
15 printf( '\nVdst=%f V\n',Vdst)
16 Vdd=12;
17 Vdsq=7;
18 Rd=(Vdd-Vdsq)/Idq;
19 printf( '\nRd =%.2f Kohm\n',Rd)
20 Vgsq=sqrt( Idq/Kn)+Vtn;
21 printf( '\nVgsq=%f V\n',Vgsq)
22 R1=Ri*Vdd/Vgsq;
23 printf( '\nR1=%f Kohm\n',R1)
24 R2=Ri*R1/(R1-Ri);
25 printf( '\nR2=%f Kohm\n',R2)
26 g_m=2*Kn*(Vgsq-Vtn);
27 printf( '\ntransconductance=%f mA/V\n',g_m)
28 ro=(y*Idq)^-1;
29 printf( '\noutput resistance=%f Kohm\n',ro)
30 Av=-g_m*(ro*Rd/(ro+Rd));
31 printf( '\nsmall signal voltage gain=%f\n',Av)

```

---

**Scilab code Exa 6.6** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.6
4 Vtn=0.8;
5 Kn=1; //(mA/V^2)
6 Idq=0.5;
7 Vdd=5;

```

```

8 Rd=7; // (Kohm)
9 Vgsq=sqrt(Idq/Kn)+Vtn;
10 printf ('\nVgsq=%f V\n',Vgsq)
11 Vs=-Vgsq
12 Vdsq=Vdd-Idq*Rd-Vs;
13 printf ('\nVdsq=%f V\n',Vdsq)
14 g_m=2*Kn*(Vgsq-Vtn);
15 printf ('\ntransconductance=%f mA/V\n',g_m)
16 Av=-g_m*Rd;
17 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

**Scilab code Exa 6.7** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.7
4 Vdd=12;
5 R1=162;
6 R2=463;
7 Rs=0.75;
8 Kn=4;
9 Vtn=1.5;
10 //lambda=y
11 y=0.01;
12 Rsi=4;
13 Idq=7.97;
14 Vgsq=2.91;
15 g_m=2*Kn*(Vgsq-Vtn);
16 printf ('\ntransconductance=%f mA/V\n',g_m)
17 ro=(y*Idq)^-1;
18 printf ('\noutput resistance=%f KOhm\n',ro)
19 Ri=R1*R2/(R1+R2);
20 printf ('\namplifier input resistance=%f Kohm\n',Ri
)
21 x=Rs*ro/(Rs+ro);

```

```
22 Av=g_m*x*(Ri/(Ri+Rs))/((1+g_m*x));
23 printf ('\n small signal voltage gain=%.2f\n',Av)
```

---

**Scilab code Exa 6.9** Calculate the output resistance of a source follower circuit

```
1 clear;
2 clc;
3 //Example 6.9
4 Rs=750; //Ohm
5 ro=12500;
6 g_m=11.3*10^-3;
7 x=1/g_m;
8 y=x*Rs/(x+Rs);
9 Ro=y*ro/(y+ro);
10 printf ('\n output resistance=%.3f ohm\n',Ro)
```

---

**Scilab code Exa 6.11** Design the small signal voltage gain of an NMOS amplifier

```
1 clear;
2 clc;
3 //Example 6.11
4 Vtnd=1;
5 Vtnl=1;
6 Kn=30;
7 // let W/L=x
8 xl=1;
9 Vdd=5;
10 Av=10;
11 //Av=sqrt (xd/xl)
12 xd=(Av)^2*xl;
```

```

13 printf ('\nwidth to length ratio of driver transistor
    =%.2f\n', xd)
14 Knd=xd*Kn*0.001/2;
15 Knl=xl*Kn*0.001/2;
16 printf ('\nconduction parameter Knd=% .2f mA/V^2\n',
    Knd)
17 printf ('\nconduction parameter Knl=% .3f mA/V^2\n',
    Knl)
18 //Vgsd-Vtnd=(Vdd-Vtnl)-sqrt (Knd/Knl)*(Vgsd-Vtnd)
19 y=sqrt (Knd/Knl);
20 Vgsd=(y+5)/(1+y);
21 printf ('\nVgsd=% .2f V\n', Vgsd)
22 Vdsd=Vgsd-1;
23 printf ('\nVdsd=% .2f V\n', Vdsd)

```

---

**Scilab code Exa 6.12** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.12
4 Vtnd=0.8;
5 Vtnl=-1.5;
6 Knd=1;
7 Knl=0.2;
8 //lambda=y
9 yd=0.01;
10 yl=0.01;
11 Idq=0.2;
12 gmd=2*sqrt (Knd*Idq);
13 printf ('\ntransconductance of the driver=% .3f mA/V\n',
    , gmd)
14 roD=1/(yd*Idq);
15 printf ('\noutput resistances=% .2f Kohm\n', roD)
16 Av=-gmd*roD/2;
17 printf ('\nsmall signal voltage gain=% .2f \n', Av)

```

---

**Scilab code Exa 6.13** Determine the small signal voltage gain of a circuit

```
1 clear;
2 clc;
3 //Example 6.13
4 Vtn=0.8;
5 Vtp=-0.8;
6 Kn=80*10^-3;
7 Kp=40*10^-3;
8 //x=W/L
9 xn=15;
10 xp=10;
11 //lambda=y
12 yn=0.01;
13 yp=0.01;
14 Ibias=0.2;
15 gm=2*sqrt(Kn*xn*Ibias/2);
16 printf ('\ntransconductance of the NMOS driver=%f
mA/V^2\n',gm)
17 ron=1/(yn*Ibias);
18 printf ('\noutput resistances=%f Kohm\n',ron)
19 Av=-gm*ron/2;
20 printf ('\nsmall signal voltage gain=%f \n',Av)
```

---

**Scilab code Exa 6.14** Design the biasing of a multistage MOSFET

```
1 clear;
2 clc;
3 //Example 6.14
4 Kn1=500*10^-3;
5 Kn2=200*10^-3;
```

```

6 Vtn1=1.2;
7 Vtn2=Vtn1;
8 Idq1=0.2;
9 Idq2=0.5;
10 Vdsq1=6;
11 Vdsq2=6;
12 Ri=100;
13 Rsi=4;
14 Rs2=(10-Vdsq2)/Idq2;
15 printf ('\nRs2=%f KOhm\n',Rs2)
16 Vgs2=sqrt(Idq2/Kn2)+Vtn2;
17 printf ('\ngate to source voltage for M2=%f V\n',
           Vgs2)
18 Vs2=-1;
19 Vg2=Vs2+Vgs2;
20 printf ('\ngate voltage of M2=%f V\n',Vg2)
21 Vg1=Vg2;
22 Rd1=(5-Vg1)/Idq1;
23 printf ('\nresistor Rd1=%f KOhm\n',Rd1)
24 Vs1=Vg1-Vdsq1;
25 printf ('\nsource voltage of M1=%f KOhm\n',Vs1)
26 Rs1=(Vs1+5)/Idq1;
27 printf ('\nresistor Rs1=%f KOhm\n',Rs1)
28 Vgs1=sqrt(Idq1/Kn1)+Vtn1;
29 printf ('\ngate to source voltage for M1=%f V\n',
           Vgs1)
30 R1=Ri*10/(Vgs1+Idq1*Rs1);
31 printf ('\nR1=%f KOhm\n',R1)
32 //Ri=R1*R2/(R1+R2)
33 R2=Ri*R1/(R1-Ri);
34 printf ('\nR2=%f KOhm\n',R2)

```

---

**Scilab code Exa 6.15** Design the biasing of cascade circuit

```
1 clear;
```

```

2 clc;
3 //Example 6.15
4 Vtn1=1.2;
5 Vtn2=1.2;
6 Kn1=0.8;
7 Kn2=0.8;
8 //x=R1+R2+R3=300
9 x=300;
10 Rs=10;
11 Idq=0.4;
12 Vdsq1=2.5;
13 Vdsq2=2.5;
14 Vs1=Idq*Rs-5;
15 printf ('\n dc voltage at source of M1=%f V\n',Vs1)
16 Vgs=sqrt(Idq/Kn1)+Vtn1;
17 printf ('\n gate to source voltage=%f V\n',Vgs)
18 R3=(Vgs+Vs1)*x/5;
19 printf ('\n R3=%f KOhm\n',R3)
20 Vs2=Vdsq2+Vs1;
21 printf ('\n voltage at source of M2=%f V\n',Vs2)
22 //y=R2+R3
23 y=(Vgs+Vs2)*x/5;
24 printf ('\n R2+R3=%f KOhm\n',y)
25 R2=150;
26 R1=x-y;
27 printf ('\n R1=%f KOhm\n',R1)
28 R3=y-R2;
29 printf ('\n R3=%f KOhm\n',R3)
30 Vd2=Vdsq2+Vs2;
31 printf ('\n voltage at drain of M2 =%f V\n',Vd2)
32 Rd=(5-Vd2)/Idq;
33 printf ('\n drain resistance=%f KOhm\n',Rd)

```

---

**Scilab code Exa 6.17** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.17
4 Kn=0.8;
5 Vtn=1.2;
6 Vgs=1.91;
7 Rd=2.5;
8 gm=2*Kn*(Vgs-Vtn);
9 printf ('\ntransconductance=%f mA/V\n',gm)
10 Av=-gm*Rd;
11 printf ('\nsmall signal voltage gain=%f \n',Av)

```

---

**Scilab code Exa 6.18** Determine the small signal voltage gain of a circuit

```

1 clear;
2 clc;
3 //Example 6.18
4 //Determine the small signal voltage gain of a
      circuit in fig.6.55
5 Idss=12;
6 Vp=-4;
7 //lambda=y
8 y=0.008;
9 Vgssq=poly(0,'Vgssq');
10 p=poly([26.4 17.2 2.025],'Vgssq','c')
11 printf ('\nroots=%f\n',roots(p))
12 Vgssq=-2.01
13 Idq=Idss*(1-Vgssq/Vp)^2;
14 printf ('\nquiescent drain current=%f mA\n',Idq)
15 gm=(-2*Idss/Vp)*(1-Vgssq/Vp);
16 printf ('\ntransconductance=%f mA/V\n',gm)
17 ro=(1/(y*Idq));
18 printf ('\noutput resistance=%f KOhm\n',ro)
19 Rd=2.7;
20 Rl=4;

```

```
21 x=Rd*Rl/(Rd+Rl);
22 Av=-gm*ro*x/(ro+x);
23 printf ('\nsmall signal voltage gain=%f \n',Av)
```

---

**Scilab code Exa 6.19** Design a JFET source follower

```
1 clear;
2 clc;
3 //Example 6.19
4 Idss=12;
5 Vp=-4;
6 Rl=10;
7 //lambda=y
8 y=0.01;
9 Av=0.9;
10 //gm=(-2*Idss/Vp)*(1-Vgs/Vp)
11 gm=2;
12 Vgs=(1+gm*Vp/(2*Idss))*Vp;
13 printf ('\n gate to source voltage=%f V\n',Vgs)
14 Idq=Idss*(1-Vgs/Vp)^2;
15 printf ('\n quiescent drain current=%f mA\n',Idq)
16 Rs=(-Vgs+10)/Idq;
17 printf ('\nRs=%f KOhm\n',Rs)
18 ro=(1/(y*Idq));
19 printf ('\noutput resistance=%f KOhm\n',ro)
20 x=Rl*ro/(Rl+ro);
21 t=x*Rs/(x+Rs);
22 Av=gm*t/(1+gm*t);
23 printf ('\nsmall signal voltage gain=%f \n',Av)
```

---

# Chapter 7

## Frequency Response

**Scilab code Exa 7.1** Determine the corner frequencies and maximum magnitude asymptotes

```
1 clear;
2 clc;
3 //Example 7.1
4 Rs=1000;
5 Rp=10000;
6 Cs=1*10^-6;
7 Cp=3*10^-12;
8 Ts=(Rs+Rp)*Cs;
9 printf ('\ntime constant=%.3f s\n',Ts)
10 f=1/(2*pi*Ts);
11 printf ('\ncorner frequency=%.2f Hz\n',f)
12 x=20*log10(Rp/(Rp+Rs));
13 printf ('\nmaximum magnitude =%.3fdB\n',x)
14 Rp=10; //KOhm
15 Rs=1; //Kohm
16 Cp=3; //pF
17 Tp=Cp*Rs*Rp/(Rs+Rp);
18 printf ('\ntime constant=%.3f ns\n',Tp)
19 Tp=2.73*10^-3; //micro sec
20 f=1/(2*pi*Tp);
```

```
21 printf ('\ncorner frequency =%.2fMHz\n',f)
```

---

**Scilab code Exa 7.2** Determine the corner frequencies and bandwidth

```
1 clear;
2 clc;
3 //Example 7.2
4 Rs=1000;
5 Rp=10000;
6 Cs=1*10^-6;
7 Cp=3*10^-12;
8 Ts=(Rs+Rp)*Cs;
9 printf ('\nopen circuit time constant=%.3f s\n',Ts)
10 Rs=1; //KOhm
11 Rp=10; //KOhm
12 Cp=3; //pF
13 Tp=Cp*Rs*Rp/(Rs+Rp);
14 printf ('\nshort circuit time constant=%.3f ns\n',Tp)
15 fL=1/(2*pi*Ts);
16 printf ('\ncorner frequency fL=%.2f Hz\n',fL)
17 Tp=2.73*10^-3; //microsec
18 fH=1/(2*pi*Tp);
19 printf ('\ncorner frequency fH=%.3f MHz\n',fH)
20 fL=14.5*10^-6; //MHz
21 fbw=fH-fL;
22 printf ('\nbandwidth =%.3fMHz\n',fbw)
```

---

**Scilab code Exa 7.3** Determine the corner frequencies and maximum gain

```
1 clear;
2 clc;
3 //Example 7.3
4 R1=51.2;
```

```

5 R2=9.6;
6 Rc=2;
7 Re=.4;
8 Rsi=.1;
9 Vt=0.026;
10 Cc=1;
11 Vcc=10;
12 Vbe=0.7;
13 b=100;
14 Rb=8.08;
15 Icq=1.81;
16 gm=Icq/Vt;
17 printf ('\ntransconductance=%f mA/V\n',gm)
18 r=b*Vt/Icq;
19 printf ('\ndiffusion resistance=%f KOhm\n',r)
20 x=r+(1+b)*Re;
21 y=x*R2/(x+R2);
22 Ri=y*R1/(R1+y);
23 printf ('\ninput resistance=%f KOhm\n',Ri)
24 Ts=(Rsi+Ri)*Cc;
25 printf ('\ntime constant=%f ms\n',Ts)
26 Ts=6.87*10^-3; //Sec
27 fL=1/(2*pi*Ts);
28 printf ('\ncorner frequency fL=%f Hz\n',fL)
29 Rib=r+(1+b)*Re;
30 printf ('\nRib=%f KOhm\n',Rib)
31 Av=(gm*r*Rc/(Rsi+Ri))*Rb/(Rb+Rib);
32 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

### Scilab code Exa 7.4 Design the circuit

```

1 clear;
2 clc;
3 //Example 7.4
4 fL=20*10^-3; //KHz

```

```

5 Rd=6.7;
6 Rl=10;
7 Ts=1/(2*pi*fL);
8 printf ('\ntime constant=%f ms\n',Ts)
9 Cc=Ts/(Rd+Rl);
10 printf ('\ncoupling capacitance=%f microF\n',Cc)

```

---

### Scilab code Exa 7.5 Determine 3dB frequency

```

1 clear;
2 clc;
3 //Example 7.5
4 b=100;
5 Vbe=0.7;
6 Rs=500;
7 Rb=100000;
8 Re=10000;
9 Rl=10000;
10 Va=120;
11 Ccc2=1*10^-6;
12 Icq=0.838*0.001;
13 r=3100; //small signal parameter
14 gm=32.2*0.001;
15 ro=143000;
16 x=(r+Rs*Rb/(Rs+Rb))/(1+b);
17 y=ro*x/(ro+x);
18 Ro=Re*y/(Re+y);
19 printf ('\noutput resistance of emitter=%f Ohm\n',
Ro)
20 Ts=(Ro+Rl)*Ccc2;
21 printf ('\ntime constant=%f s\n',Ts)
22 fL=1/(2*pi*Ts);
23 printf ('\n3dB frequency=%f Hz\n',fL)

```

---

**Scilab code Exa 7.6** Determine the corner frequencies and maximum gain

```
1 clear;
2 clc;
3 //Example 7.6
4 Rs=3.2;
5 Rd=10;
6 Rl=20;
7 Cl=10;
8 Vtp=-2;
9 Kp=0.25;
10 Idq=0.5;
11 Vsgq=3.41;
12 Vsdq=3.41;
13 gm=2*Kp*(Vsgq+Vtp);
14 printf ('\ntransconductance =%.3fmA/V\n',gm)
15 Tp=Cl*Rd*Rl/(Rd+Rl);
16 printf ('\ntime constant=%.3f ns\n',Tp)
17 Tp=66.7*10^-3; //micro sec
18 fH=1/(2*pi*Tp);
19 printf ('\ncorner frequency=%.2f MHz\n',fH)
20 Av=(gm*Rd*Rl/(Rd+Rl))/(1+gm*Rs);
21 printf ('\nmaximum small signal voltage gain=%.2f\n',
Av)
```

---

**Scilab code Exa 7.7** Determine the mid gain corner frequencies and bandwidth of a circuit

```
1 clear;
2 clc;
3 //Example 7.7
4 Vbe=0.7;
```

```

5 b=100;
6 Re=.5;
7 Rc=5;
8 Rl=10;
9 R1=40;
10 Cc=10;
11 R2=5.7;
12 Rs=.1;
13 Vt=0.026;
14 Icq=0.99;
15 gm=Icq/Vt;
16 printf ('\ntransconductance=%f mA/V\n',gm)
17 r=b*Vt/Icq;
18 printf ('\ndiffusion resistance=%f KOhm\n',r)
19 Ri=r+(1+b)*Re;
20 printf ('\ninput resistance=%f KOhm\n',Ri)
21 x=Rc*Rl/(Rc+Rl);
22 y=R1*R2/(R1+R2);
23 t=y*Ri/(y+Ri);
24 Av=gm*r*x*(y/(y+Ri))*(1/(Rs+t));
25 printf ('\nmaximum small signal voltage gain=%f\n',
           Av)
26 Ts=(Rs+t)*Cc;
27 printf ('\ntime constant=%f ms\n',Ts)
28 Ts=46.6*0.001; //sec
29 C1=15;
30 Tp=x*C1;
31 printf ('\ntime constant=%f ns\n',Tp)
32 fL=1/(2*pi*Ts);
33 printf ('\nlower corner frequency=%f Hz\n',fL)
34 Tp=50*10^-3; //micro sec
35 fH=1/(2*pi*Tp);
36 printf ('\nupper corner frequency=%f MHz\n',fH)
37 fL=3.4*10^-6; //MHz
38 fbw=fH-fL;
39 printf ('\nbandwidth =%f MHz\n',fbw)

```

---

**Scilab code Exa 7.8** Determine the corner frequencies and limiting horizontal asymptotes

```

1 clear;
2 clc;
3 //Example 7.8
4 Re=4;
5 Rc=2;
6 Rs=0.5;
7 Vt=0.026;
8 Ce=1*10^-3;
9 V1=5;
10 Icq=1.06;
11 V2=-5;
12 b=100;
13 Vbe=0.7;
14 gm=Icq/Vt;
15 printf ('\ntransconductance =%.2fmA/V\n',gm)
16 r=b*Vt/Icq;
17 printf ('\ndiffusion resistance=%.2f KOhm\n',r)
18 Ta=Re*Ce;
19 printf ('\ntime constant Ta=%ef s\n',Ta)
20 Tb=(Re*Ce*(Rs+r))/(Rs+r+(1+b)*Re);
21 printf ('\ntime constant Tb=%e s\n',Tb)
22 fA=1/(2*pi*Ta);
23 printf ('\ncorner frequency =%.2fHz\n',fA)
24 Tb=2.9*0.01; //msec
25 fB=1/(2*pi*Tb);
26 printf ('\ncorner frequency =%.2fkHz\n',fB)
27 Av=(gm*r*Rc)/(Rs+r+(1+b)*Re);
28 printf ('\nlimiting low frequency horizontal
           asymptote=%.2f\n',Av)
29 Av=gm*r*Rc/(Rs+r);
30 printf ('\nnlimiting high frequency horizontal
           asymptote=%.2f\n',Av)

```

asymptote=% .2 f \n , Av)

---

### Scilab code Exa 7.9 Determine 3dB frequency

```
1 clear;
2 clc;
3 //Example 7.9
4 r=2600;
5 C1=2*10^-6;
6 C2=0.1*10^-6;
7 fB=1/(2*pi*r*(C1+C2));
8 printf('n3dB frequency=% .2 f MHz\n',fB)
```

---

### Scilab code Exa 7.10 Calculate bandwidth and capacitance

```
1 clear;
2 clc;
3 //Example 7.10
4 fT=500;
5 Ic=1;
6 b=100;
7 Vt=0.026;
8 C2=0.3*10^-12;
9 fB=fT/b;
10 printf('nbandwidth=% .3 f MHz\n',fB)
11 gm=Ic/Vt;
12 printf('ntransconductance=% .3 f mA/V\n',gm)
13 fT=500000000;
14 gm=38.5*0.001;
15 C1=gm/(fT*2*pi)-C2;
16 printf('ncapacitance =%3.2 eF\n',C1)
```

---

**Scilab code Exa 7.12** Determine the unity gain bandwidth

```
1 clear;
2 clc;
3 //Example 7.12
4 Kn=0.25;
5 Vtn=1;
6 Cgd=0.04*10^-3;
7 Cgs=0.2*10^-3;
8 Vgs=3;
9 gm=2*Kn*(Vgs-Vtn);
10 printf('ntransconductance =%.3fmA/V\n',gm)
11 fT=gm/(2*pi*(Cgd+Cgs));
12 printf('nunity gain bandwidth=%.f MHz\n',fT)
```

---

**Scilab code Exa 7.13** Determine the Miller capacitance and cutoff frequency

```
1 clear;
2 clc;
3 //Example 7.13
4 gm=1;
5 Cgd=0.04;
6 Rl=10;
7 Cgs=0.2;
8 Cm=Cgd*(1+gm*Rl);
9 printf('nMiller capacitance=%f pF\n',Cm)
10 Cm=0.44*0.001;//nF
11 Cgs=0.2*0.001;//nF
12 fT=gm/(2*pi*(Cgs+Cm));
13 printf('ncutoff frequency=%f MHz\n',fT)
```

---

**Scilab code Exa 7.14** Determine the upper corner frequency and midband gain

```
1 clear;
2 clc;
3 //Example 7.14
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 Rb=40;
8 R2=5.72;
9 Re=0.5;
10 Rc=5;
11 Rl=10;
12 b=150;
13 Vbe=0.7;
14 C1=35*10^-3;
15 C2=4;
16 Vt=0.026;
17 Icq=1.02;
18 r=b*Vt/Icq;
19 printf ('\n small signal parameter = %.2f KOhm\n', r)
20 gm=Icq/Vt;
21 printf ('\n transconductance = %.3f mA/V\n', gm)
22 Cm=C2*(1+gm*Rc*Rl/(Rc+Rl));
23 printf ('\n Miller capacitance = %.3f pF\n', Cm)
24 Cm=527*10^-3;
25 x=Rb*Rs/(Rb+Rs);
26 y=r*x/(r+x);
27 fH=1/(2*pi*y*(C1+Cm));
28 printf ('\n upper corner frequency = %.2f MHz\n', fH)
29 t=Rb*r/(Rb+r);
30 p=Rc*Rl/(Rc+Rl);
31 Av=gm*p*t/(t+Rs);
```

```
32 printf( '\nmidband gain=%f\n' ,Av)
```

---

**Scilab code Exa 7.15** Determine the upper corner frequency and midband gain

```
1 clear;
2 clc;
3 //Example 7.15
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 R1=40;
8 R2=5.72;
9 Re=0.5;
10 Rc=5;
11 Rl=10;
12 b=150;
13 Vbe=0.7;
14 C1=35;
15 C2=4;
16 Vt=0.026;
17 Icq=1.02;
18 gm=39.2;
19 r=3.82;
20 x=Re*Rs/(Re+Rs);
21 t=r/(1+b);
22 y=t*x/(t+x);
23 Tp=y*C1;
24 printf( '\ntime constant=%f ns\n' ,Tp)
25 Tp=0.679*10^-3; //micro sec
26 f=1/(2*pi*Tp);
27 printf( '\nupper frequency =%f fMHz\n' ,f)
28 T=C2*Rc*Rl/(Rc+Rl);
29 printf( '\ntime constant=%f ns\n' ,T)
30 T=13.3*10^-3; //micro sec
```

```

31 f=1/(2*pi*T);
32 printf ('\nupper frequency=%f MHz\n',f)
33 x=Rc*Rl/(Rc+Rl);
34 y=Re*t/(Re+t);
35 Av=gm*x*(y/(y+Rs));
36 printf ('\nmidband voltage gain=%f \n',Av)

```

---

**Scilab code Exa 7.16** Determine the upper corner frequency and midband gain

```

1 clear;
2 clc;
3 //Example 7.16
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 R1=42.5;
8 R2=20.5;
9 R3=28.3;
10 Re=5.4;
11 Rc=5;
12 Rl=10;
13 b=150;
14 Vbe=0.7;
15 C1=35;
16 C2=4;
17 Vt=0.026;
18 Icq=1.02;
19 gm=39.2;
20 r=3.820;
21 Rb=R2*R3/(R2+R3);
22 x=Rb*r/(Rb+r);
23 y=Rs*x/(x+Rs);
24 Tp=y*(C1+2*C2);
25 printf ('\n time constant=%f ns\n',Tp)

```

```

26 Tp=Tp*10^-3; //micro sec
27 f=1/(2*pi*Tp);
28 printf ('\n3dB frequency =%0.3fMHz\n',f)
29 T=C2*Rc*Rl/(Rc+Rl);
30 printf ('\n time constant=%0.2f ns\n',T)
31 T=T*0.001; //micro sec
32 f=1/(2*pi*T);
33 printf ('\n upper frequency=%0.3f MHz\n',f)
34 x=Rc*Rl/(Rc+Rl);
35 y=Rb*r/(Rb+r);
36 Av=gm*x*(y/(y+Rs));
37 printf ('\n midband voltage gain=%0. f \n',Av)

```

---

**Scilab code Exa 7.17** Determine the frequency of a zero and a pole

```

1 clear;
2 clc;
3 //Example 7.17
4 V1=5;
5 V=-5;
6 Rs=0.1;
7 R1=40;
8 R2=5.720;
9 Re=0.5;
10 Rc=5;
11 Rl=10;
12 b=150;
13 Vbe=0.7;
14 C1=35;
15 C2=4;
16 Vt=0.026;
17 Icq=1.02;
18 gm=39.2;
19 r=3.820;
20 t=r/(1+b);

```

```
21 t=t*0.001;
22 f=1/(2*pi*C1*t);
23 printf ('\nthe zero occurs at this frequency=%.2f MHz
24 \n',f)
24 x=1+gm*Re*R1/(Re+R1);
25 Rb=R1*R2/(R1+R2)
26 d=x*r;
27 y=d*Rb/(d+Rb);
28 t=y*Rs/(y+Rs);
29 Tp=t*(C2+C1/x);
30 printf ('\n time constant=%.2f ns\n',Tp)
31 Tp=Tp*10^-3; //micro sec
32 f=1/(2*pi*Tp);
33 printf ('\n3dB frequency=%.f MHz\n',f)
```

---

# Chapter 8

## Ouput Stages and Power Amplifier

**Scilab code Exa 8.2** Determine the maximum power dissipation

```
1 clear;
2 clc;
3 //Example 8.1
4 //let thermal resistance parameters be R
5 Rdcase=1.75; //degree celsius per watt
6 Rcsnk=1; //degree celsius per watt
7 Rsamb=5; //degree celsius per watt
8 Rcamb=50; //degree celsius per watt
9 Tamb=30; //ambient temperature
10 Tjmax=150; //maximum junction temperature
11 Tdev=150; //device temperature
12 //when no heat sink is used
13 P=(Tjmax-Tamb)/(Rdcase+Rcamb);
14 printf ('\nmaximum power dissipation=%f W\n',P)
15 //when heat sink is used
16 P=(Tjmax-Tamb)/(Rdcase+Rcsnk+Rsamb);
17 printf ('\nmaximum power dissipation=%f W\n',P)
```

---

**Scilab code Exa 8.3** Determine the maximum safe power dissipation

```
1 clear;
2 clc;
3 //Example 8.3
4 Rcsnk=1; //degree celsius per watt
5 Rsamb=5; //degree celsius per watt
6 Tjmax=175; //maximum junction temperature
7 Toc=25;
8 Tamb=25;
9 Pr=20; //rated power W
10 Rdcase=(Tjmax-Toc)/Pr;
11 printf ('\ndevice to case thermal resistance=%f C
/W\n',Rdcase)
12 P=(Tjmax-Tamb)/(Rdcase+Rcsnk+Rsamb);
13 printf ('\nmaximum power dissipation=%f W\n',P)
```

---

**Scilab code Exa 8.7** Determine the required biasing in MOSFET class AB

```
1 clear;
2 clc;
3 //Example 8.7
4 Vdd=10;
5 Rl=20;
6 K=0.2;
7 Vt=1;
8 vo=5;
9 iL=vo/20;
10 printf ('\niL=%f A\n',iL)
11 Idq=0.05;
12 //Idq=K*(Vbb/2-Vt)
13 Vbb=(sqrt(Idq/K)+1)*2;
```

```

14 printf( '\nVbb=%f V\n' ,Vbb)
15 iD=iL;
16 Vgsn=sqrt(iD/K)+Vt;
17 printf( '\nVgsn=%f V\n' ,Vgsn)
18 Vsgp=Vbb-Vgsn;
19 printf( '\nVsgp=%f V\n' ,Vsgp)
20 vi=vo+Vgsn-Vbb/2;
21 printf( '\ninput voltage=%f V\n' ,vi)

```

---

**Scilab code Exa 8.8** Design a transformer coupled emitter follower amplifier

```

1 clear;
2 clc;
3 //Example 8.8
4 Vcc=24;
5 Rl=8;
6 P=5;
7 Vbe=0.7;
8 b=100;
9 Vp=sqrt(2*Rl*P);
10 printf( '\npeak output voltage=%f V\n' ,Vp)
11 Ip=Vp/Rl;
12 printf( '\npeak output current =%f mA\n' ,Ip)
13 a=0.9*Vcc/Vp;
14 printf( '\nalpha=%f\n' ,a)
15 Icq=Ip/(0.9*a);
16 printf( '\nIcq=%f A\n' ,Icq)
17 Pq=Vcc*Icq;
18 printf( '\nmaximum power dissipated in the transistor
    =%f W\n' ,Pq)
19 Ibq=Icq/b;
20 Ibq=Ibq*1000; //mA
21 printf( '\nbase current Ibq=%f mA\n' ,Ibq)
22 Rth=2.500;

```

```

23 //Vth=Vcc*Rth/R1 and Vth=Ibq*Rth+Vbe
24 R1=Vcc*Rth/(Ibq*Rth+Vbe);
25 printf ('\nR1=%f KOhm\n',R1)
26 R2=Rth*R1/(R1-Rth);
27 printf ('\nR2=%f KOhm\n',R2)

```

---

### Scilab code Exa 8.9 Design the class AB output stage

```

1 clear;
2 clc;
3 //Example 8.9
4 Iso=3*10^-14;
5 Isq=10^-13;
6 b=75;
7 Vt=0.026;
8 Rl=8;
9 P=5;
10 Vp=sqrt(2*Rl*P);
11 printf ('\npeak voltage Vp=%f V\n',Vp)
12 Vcc=Vp/0.8;
13 printf ('\nsupply voltage=%f V\n',Vcc)
14 Ien=Vp/Rl;
15 printf ('\nemitter current=%f A\n',Ien)
16 Ibn=Ien/(1+b);
17 Ibn=Ibn*1000; //mA
18 printf ('\nbase current=%f mA\n',Ibn)
19 iD=0.020;
20 Vbb=2*Vt*log(iD/Iso);
21 printf ('\nVbb=%f V\n',Vbb)
22 Icq=Isq*exp((Vbb/2)/Vt);
23 Icq=Icq*1000; //mA
24 printf ('\nquiescent collector current=%f mA\n',Icq)
25 Ibias=20; //mA
26 iD=Ibias-Ibn;

```

```

27 printf ('\n drain current=%f mA\n', iD)
28 iD=iD*0.001; //A
29 Vbb=2*Vt*log(iD/Iso);
30 printf ('\n Vbb=%f V\n', Vbb)
31 Icn=1.12;
32 Vben=Vt*log(Icn/Isq);
33 printf ('\n B-E voltage of Qn=%f V\n', Vben)
34 Vebp=Vbb-Vben;
35 printf ('\n emitter base voltage of Qp=%f V\n', Vebp)
36 Icp=Isq*exp(Vebp/Vt);
37 Icp=Icp*1000; //mA
38 printf ('\n Icp=%f mA\n', Icp)

```

---

**Scilab code Exa 8.11** Determine the currents and the current gain

```

1 clear;
2 clc;
3 //Example 8.11
4 R1=2; //KOhm
5 R2=R1;
6 Rl=.1; //KOhm
7 b=60;
8 Vbe=0.6;
9 Veb=0.6;
10 V1=15;
11 V2=V1;
12 iR1=(V1-Vbe)/R1;
13 //iR1=iR2=iE1=iE2
14 printf ('\n iR1=%f mA\n', iR1)
15 vo=10;
16 io=vo/Rl;
17 printf ('\n output current=%f mA\n', io)
18 iB3=100/61;
19 printf ('\n iB3=%f mA\n', iB3)
20 iR1=(V1-(10+Vbe))/R1;

```

```
21 printf( '\ncurrent in R1=%f mA\n' , iR1)
22 iE1=iR1-iB3;
23 printf( '\niE1=%f mA\n' , iE1)
24 iB1=iE1/(1+b);
25 iB1=iB1*1000; //micro A
26 printf( '\niB1=%f microA\n' , iB1)
27 iE2=(10-0.6+15)/R1;
28 printf( '\niE2=%f mA\n' , iE2)
29 iB2=iE2/(1+b);
30 iB2=iB2*1000;
31 printf( '\niB2=%f microA\n' , iB2)
32 Ii=iB2-iB1;
33 printf( '\ninput current=%f microA\n' , Ii)
34 Ii=Ii*0.001; //mA
35 Ai=io/Ii;
36 printf( '\ncurrent gain=%f\n' , Ai)
37 Ai=(1+b)*R1/(2*R1);
38 printf( '\npredicted current gain=%f\n' , Ai)
```

---

# Chapter 9

## The Ideal Operational Amplifier

**Scilab code Exa 9.5** Determine a load current in a voltage to current converter

```
1 clear;
2 clc;
3 //Example 9.5
4 Zl=0.1;
5 R1=10;
6 R2=1;
7 R3=1;
8 Rf=10;
9 Vt=-5;
10 iL=-Vt/R2;
11 printf ('\nload current=%.3 f mA\n',iL)
12 vL=iL*Zl;
13 printf ('\nvoltage across the load=%.2 f V\n',vL)
14 i4=vL/R2;
15 printf ('\ni4=%.3 f mA\n',i4)
16 i3=i4+iL;
17 printf ('\ni3=%.3 f mA\n',i3)
18 Vo=i3*R3+vL;
```

```
19 printf( '\noutput voltage=%f V\n' ,Vo)
20 i1=Vt/R1;
21 i2=i1;
22 printf( '\ni1=%f mA\n' ,i1)
23 printf( '\ni2=%f mA\n' ,i2)
```

---

**Scilab code Exa 9.9** Determine the time constant

```
1 clear;
2 clc;
3 //Example 9.9
4 //Vo=(-1/R1*C2)*integrate((-1)dt)
5 x=integrate('(-1)', 't', 0, 1)
6 Vo=10;
7 //let y=R1*C2
8 y=-x/Vo;
9 printf( '\nR1C2=%f ms\n' ,y)
```

---

# Chapter 10

## Integrated Circuit Biasing and Active Loads

**Scilab code Exa 10.1** Design a two transistor current source

```
1 clear;
2 clc;
3 //Example 10.1
4 Vbe=0.6; //(V)
5 b=100;
6 V1=5;
7 Io=200; //micro A
8 Iref=Io*(1+2/b);
9 printf ('\nreference current=%f microA\n',Iref)
10 Iref=Iref*0.001; //mA
11 R1=(V1-Vbe)/Iref;
12 printf ('\nR1=%f KOhm\n',R1)
```

---

**Scilab code Exa 10.2** Determine the change in load current

```
1 clear;
```

```

2  clc;
3 //Example 10.2
4 V1=5;
5 V2=-5;
6 R1=9.3;
7 b=50;
8 Vbe=0.7;
9 Va=80;
10 Iref=(V1-Vbe-V2)/R1;
11 printf ('\nreference current =%.3fmA\n',Iref)
12 Io=Iref/(1+2/b);
13 printf ('\noutput current=%f fmA\n',Io)
14 ro=Va/Io;
15 printf ('\nsmall signal output resistance=%f KOhm\n',
           ,ro)
16 //dIo=dVce2/ro
17 Vce2=0.7;
18 dIo=(V1-Vce2)/ro;
19 printf ('\nchange in load current=%f mA\n',dIo)
20 x=dIo/Io;
21 x=x*100;
22 printf ('\npercent change in output current=%f \n',
           x)

```

---

#### Scilab code Exa 10.4 Design a Widlar current source

```

1 clear;
2 clc;
3 //Example 10.4
4 Iref=1;
5 Io=12*10^-3;
6 V1=5;
7 V2=-5;
8 Vt=0.026;
9 Vbe=0.7;

```

```

10 R1=(V1-Vbe-V2)/Iref;
11 printf ('\nResistance R1 =%.2fKOhm\n',R1)
12 Re=(Vt/Io)*log(Iref/Io);
13 printf ('\nResistance Re =%.2fKOhm\n',Re)
14 Vbe=Io*Re;
15 printf ('\ndifference between two B-E voltages=% .2f V
    \n',Vbe)

```

---

**Scilab code Exa 10.5** Determine the change in load current

```

1 clear;
2 clc;
3 //Example 10.5
4 V1=5;
5 V2=-5;
6 R1=9.3;
7 Re=9.580;
8 Vt=0.026;
9 b=100;
10 Vbe=0.7;
11 Va=80;
12 Io=12;
13 ro2=Va/Io;
14 printf ('\nsmall signal collector resistance=% .2f
    MOhm\n',ro2)
15 Io=12*0.001; //mA
16 gm2=Io/Vt;
17 printf ('\ntransconductance=% .3f mA/V\n',gm2)
18 r=b*Vt/Io;
19 printf ('\nResistance=% .2f KOhm\n',r)
20 Ro=ro2*(1+gm2*Re*r/(Re+r));
21 printf ('\noutput resistance=% .2f MOhm\n',Ro)
22 dVc2=4;
23 dIo=dVc2/Ro;
24 printf ('\nchange in load current=% .3f microA\n',dIo)

```

```
25 Io=12; //micro A
26 x=dIo/Io;
27 x=x*100;
28 printf ('\npercent change in output current =%.4f\n', x)
```

---

**Scilab code Exa 10.6** Design a generalized current mirror

```
1 clear;
2 clc;
3 //Example 10.6
4 V1=5;
5 V2=-5;
6 Vbe=0.6;
7 Veb=0.6;
8 Iq2=400*10^-3; //mA
9 Iref=200*10^-3; //mA
10 Iq1=Iref;
11 Iq3=Iq1;
12 Iq4=600*10^-6;
13 R1=(V1-Veb-Vbe-V2)/Iref;
14 printf ('\nResistance R1=%f KOhm\n', R1)
```

---

**Scilab code Exa 10.7** Design a MOSFET current source

```
1 clear;
2 clc;
3 //Example 10.7
4 //uox*Cox/2=x
5 x=20*10^-6; //A/V^2
6 Vtn=1;
7 V1=5;
8 V2=0;
```

```

9 Iref=0.25*10^-3;
10 Io=0.1*10^-3;
11 Vgs2=1.85;
12 // let y=W/L
13 y2=Io/(x*(Vgs2-Vtn)^2);
14 printf ('\nwidth per length 2=%f\n',y2)
15 y1=Iref/(x*(Vgs2-Vtn)^2);
16 printf ('\nwidth per length 1=%f\n',y1)
17 Vgs1=Vgs2;
18 Vgs3=V1-V2-Vgs1;
19 printf ('\nVgs3=%f V\n',Vgs3)
20 y3=Iref/(x*(Vgs3-Vtn)^2);
21 printf ('\nwidth per length 3=%f\n',y3)

```

---

**Scilab code Exa 10.8** Compare the output resistances

```

1 clear;
2 clc;
3 //Example 10.8
4 Iref=100;
5 Io=Iref;
6 //lambda=y
7 y=0.01;
8 gm=0.5*10^+3;
9 ro=1/(y*Iref);
10 printf ('\noutput resistance=%f MOhm\n',ro)
11 ro2=1;
12 ro4=1;
13 Ro=ro4+ro2*(1+gm*ro4);
14 printf ('\noutput resistance of cascode circuit=%f
MOhm\n',Ro)

```

---

**Scilab code Exa 10.9** Determine the currents and voltages

```

1 clear;
2 clc;
3 //Example 10.9
4 Idss1=2;
5 Idss2=1;
6 Vp1=-1.5;
7 Vp2=Vp1;
8 //lambda=y
9 y1=0.05;
10 y2=y1;
11 V2=-5;
12 Vds=1.5;
13 Vsmin=Vds+V2;
14 printf ('\nminimum value of Vs=%f V\n',Vsmin)
15 Io=Idss2*(1+y1*Vds);
16 printf ('\noutput current=%f mA\n',Io)
17 Vgs1=(1-sqrt(Io/Idss1))*Vp1;
18 printf ('\ngate to source voltage of Q1=%f V\n',
Vgs1)
19 V1=Vgs1+Vsmin;
20 printf ('\nV1=%f V\n',V1)

```

---

**Scilab code Exa 10.10** Calculate the open circuit voltage gain

```

1 clear;
2 clc;
3 //Example 10.10
4 Vt=0.026;
5 Van=120;
6 Vap=80;
7 Av=-(1/Vt)/(1/Van+1/Vap);
8 printf ('\nsmall signal open circuit voltage gain=%f
f\n',Av)

```

---

**Scilab code Exa 10.11** Calculate the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 10.11
4 Van=120;
5 Vap=80;
6 Vt=0.026;
7 Ico=0.001;
8 //Rl=infinity
9 Av=-(1/Vt)/(1/Van+1/Vap);
10 printf ('\nsmall signal open circuit voltage gain=%.\n2
           f\n',Av)
11 Rl=100;
12 Av1=-(1/Vt)/(1/Van+1/Vap+1/Rl);
13 printf ('\nsmall signal open circuit voltage gain=%.\n2
           f\n',Av1)
14 Rl=10;
15 Av2=-(1/Vt)/(1/Van+1/Vap+1/Rl);
16 printf ('\nsmall signal open circuit voltage gain=%.\n2
           f\n',Av2)
```

---

**Scilab code Exa 10.12** Calculate the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 10.12
4 //lambda=y
5 yn=0.01;
6 yp=0.01;
7 Vtn=1;
8 Kn=1;
```

```

9 Iref=0.5;
10 gm=2*sqrt(Kn*Iref);
11 printf ('\ntransconductance =%.2fmA/V\n',gm)
12 go=yn*Iref;
13 printf ('\nsmall signal transistor conductance=%f
mA/V\n',go)
14 go2=go;
15 // for Rl=infinity
16 Av=-gm/(go+go2);
17 printf ('\nvoltage gain=%f \n',Av)
18 Rl=100; //Kohm
19 gl=0.01;
20 Av=-gm/(go+gl+go2);
21 printf ('\nvoltage gain=%f \n',Av)

```

---

# Chapter 11

## Differential and Multistage Amplifier

**Scilab code Exa 11.1** Determine the quiescent collector current and collector emitter voltage

```
1 clear;
2 clc;
3 //Example 11.1
4 V1=10;
5 V2=-10;
6 Iq=1;
7 Rc=10;
8 Vbe=0.7;
9 iC1=Iq/2;
10 iC2=iC1;
11 printf ('\ncollector currents =%.2fmA\n',iC1)
12 Vc1=V1-iC1*Rc;
13 Vc2=Vc1;
14 printf ('\ncollector voltages =%.2fV\n',Vc1)
15 Vcm=0;
16 Ve=Vcm-Vbe;
17 Vce1=Vc1-Ve;
18 printf ('\ncollector emitter voltage=% .2 f V\n',Vce1)
```

```

19 Vcm=-5;
20 Ve=Vcm-Vbe;
21 Vce1=Vc1-Ve;
22 printf ('\n collector emitter voltage =%.2fV\n',Vce1)
23 Vcm=5;
24 Ve=Vcm-Vbe;
25 Vce1=Vc1-Ve;
26 printf ('\n collector emitter voltage=% .2f V\n',Vce1)

```

---

**Scilab code Exa 11.3** Determine the differential and common mode gains

```

1 clear;
2 clc;
3 //Example 11.3
4 V1=10;
5 V2=-10;
6 Iq=0.8*10^-3;
7 Rc=12000;
8 Ro=25000;
9 b=100;
10 Vt=0.026;
11 Ad=Iq*Rc/(4*Vt);
12 printf ('\n differential gain=% .3f\n',Ad)
13 Acm=-(Iq*Rc/(2*Vt))/(1+(1+b)*Iq*Ro/(Vt*b));
14 printf ('\n common mode gain=% .3f\n',Acm)

```

---

**Scilab code Exa 11.7** Determine the CMRR of a differential amplifier

```

1 clear;
2 clc;
3 //Example 11.7
4 Ad=92.3;
5 Acm=0.237; //mod of Acm

```

```
6 CMRR=Ad/Acm;
7 printf ('\ncommon mode rejection ratio=%.2f\n',CMRR)
8 CMRRdB=20*log10(CMRR);
9 printf ('\nCMRR in decibels=%.2f dB\n',CMRRdB)
```

---

**Scilab code Exa 11.8** Design a bipolar source

```
1 clear;
2 clc;
3 //Example 11.8
4 CMRRdB=90; //dB
5 CMRR=3.16*10^4;
6 b=100;
7 Vt=0.026;
8 Iq=0.8;
9 Ro=(2*CMRR-1)*Vt*b/((1+b)*Iq);
10 Ro=Ro*10^-3; //Mohm
11 disp(Ro,"output resistance (MOhm)")
```

---

**Scilab code Exa 11.9** Determine the differential and common mode input resistance

```
1 clear;
2 clc;
3 //Example 11.9
4 b=100;
5 Vbe=0.7;
6 Va=100;
7 Vt=0.026;
8 Iref=0.5;
9 Iq=Iref;
10 I1=Iq/2
11 Icq=I1;
```

```

12 r=b*Vt/Icq;
13 printf ('\nsmall signal parameter=%f KOhm\n',r)
14 ro=Va/Icq;
15 printf ('\nro=%f KOhm\n',ro)
16 Ro=Va/Iq;
17 printf ('\noutput resistance of Q4=%f KOhm\n',Ro)
18 Rid=2*r;
19 printf ('\ndifferential mode input resistance =%f
fKOhm\n',Rid)
20 Ricm=(1+b)*(Ro*ro/2)/(Ro+ro/2);
21 Ricm=Ricm*0.001; //Mohm
22 printf ('\ncommon mode input resistance=%f MOhm\n',
Ricm)

```

---

**Scilab code Exa 11.10** Calculate the dc characteristics of a MOSFET diff amp

```

1 clear;
2 clc;
3 //Example 11.10
4 Kn1=0.1;
5 Kn2=Kn1;
6 Kn3=0.1;
7 Kn4=Kn3;
8 R1=30;
9 Vtn=1;
10 Rd=16;
11 // I1=(20-Vgs4)/R1 and I1=Kn3*(Vgs4-Vtn)^2
12 Vgs4=poly(0,'Vgs4')
13 p=poly([-1 -17 9],'Vgs4','c')
14 printf ('\nroots=%fV\n',roots(p))
15 Vgs4=2.40;
16 I1=(20-Vgs4)/R1;
17 printf ('\nI1=%f mA\n',I1)
18 Iq=I1;

```

```

19 Id1=Iq/2;
20 printf ('\nId1 and Id2 =%.2fmA\n', Id1)
21 Vgs1=sqrt(Id1/Kn1)+Vtn;
22 printf ('\nVgs1 and Vgs2 =%.2fV\n', Vgs1)
23 vo1=10-Id1*Rd;
24 printf ('\nvo1 and vo2=%.2f V\n', vo1)
25 Vds1=Vgs1-Vtn;
26 printf ('\nVds1=Vds2=Vds1(sat)=%.2f V\n', Vds1)
27 Vcm=vo1-Vds1+Vgs1;
28 printf ('\nVcm max=%.2f V\n', Vcm)
29 Vds4=Vgs4-Vtn;
30 printf ('\nVds4=%.2f V\n', Vds4)
31 Vcm2=Vgs1+Vds4-10;
32 printf ('\nVcm min=%.2fV\n', Vcm2)

```

---

**Scilab code Exa 11.11** Compare the forward transconductance

```

1 clear;
2 clc;
3 //Example 11.11
4 Kn=0.5;
5 Iq=1;
6 Vt=0.026;
7 //transconductance of the MOSFET
8 gm=2*sqrt(Kn*Iq/2);
9 printf ('\ntransconductance=%.3f mA/V\n', gm)
10 //transconductance of the bipolar transistor
11 gm=Iq/(2*Vt);
12 printf ('\ntransconductance=%.3f mA/V\n', gm)

```

---

**Scilab code Exa 11.12** Determine the differential mode voltage gain common mode voltage gain CMRR

```

1 clear;
2 clc;
3 //Example 11.12
4 Iq=0.587;
5 Kn=1;
6 Rd=16;
7 //lambda=y
8 y=0.01;
9 Ro=1/(y*Iq);
10 printf ('\noutput resistance =%.2fKOhm\n',Ro)
11 Ad=sqrt(Kn*Iq/2)*Rd;
12 printf ('\ndifferential mode voltage gain=% .2f \n',Ad
    )
13 Acm=-sqrt(2*Kn*Iq)*Rd/(1+2*sqrt(2*Kn*Iq)*Ro);
14 printf ('\ncommon mode voltage gain=% .2f \n',Acm)
15 CMRR=20*log10(-Ad/Acm);
16 printf ('\ncommon mode rejection ratio=% .2f dB\n',
    CMRR)

```

---

**Scilab code Exa 11.13** Determine the differential mode voltage gain

```

1 clear;
2 clc;
3 //Example 11.13
4 Iq=0.2;
5 Va=100;
6 Va2=Va;
7 Va4=Va;
8 Rl=100;
9 Vt=0.026;
10 Ad=(1/Vt)/(1/Va2+1/Va4);
11 printf ('\nopen circuit voltage gain=% .2f \n',Ad)
12 Ad=(Iq/(2*Vt))/(Iq/(2*Va2)+Iq/(2*Va4)+1/Rl);
13 printf ('\nvoltage gain=% .2f \n',Ad)

```

---

**Scilab code Exa 11.15** Determine the differential mode voltage gain

```
1 clear;
2 clc;
3 //Example 11.15
4 Kn=0.2;
5 Idq=0.1;
6 ro4=1000; //Kohm
7 ro6=1000; //KOhm
8 ro2=ro4;
9 //lambda=y
10 y=0.01;
11 gm=2*sqrt(Kn*Idq);
12 printf ('\ntransconductance=%f mA/V\n',gm)
13 ro=1/(y*Idq);
14 printf ('\noutput resistance=%f f KOhm\n',ro)
15 Ro=ro4+ro6*(1+gm*ro);
16 Ro=Ro*0.001; //Mohm
17 printf ('\noutput resistance of the cascode active
load=%f fMohm\n',Ro)
18 Ro=Ro*1000; //KOhm
19 Ad=gm*ro2*Ro/(ro4+Ro);
20 printf ('\ndifferential mode voltage gain=%f\n',Ad)
```

---

**Scilab code Exa 11.16** Calculate the input resistance and the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 11.16
4 Iq=0.2;
5 Ic1=Iq;
```

```

6 Icb=1;
7 R4=10;
8 R3=0.2;
9 b=100;
10 Va=100;
11 Vt=0.026;
12 Ri=2*(1+b)*b*Vt/Iq;
13 Ri=Ri*0.001; //MOhm
14 printf ('\ninput resistance=%f MOhm\n',Ri)
15 R11=b*Vt/Iq;
16 printf ('\nresistance R11=%f KOhm\n',R11)
17 Re=R11*R3/(R11+R3);
18 printf ('\nRe=%f KOhm\n',Re)
19 gm11=Iq/Vt;
20 printf ('\ngm11=%f mA/V\n',gm11)
21 ro11=Va/Iq;
22 printf ('\nro11 =%f fKOhm\n',ro11)
23 Rc11=ro11*(1+gm11*Re);
24 Rc11=Rc11*0.001; //MOhm
25 printf ('\nRc11=%f MOhm\n',Rc11)
26 r8=b*Vt/Icb;
27 printf ('\nresistance=%f fKOhm\n',r8)
28 //answer of following given in the book is wrong
29 Rb8=r8+(1+b)*R4;
30 Rb8=Rb8*0.001; //MOhm
31 printf ('\nRb8 =%f fMOhm\n',Rb8)
32 R17=Rc11*Rb8/(Rc11+Rb8);
33 printf ('\nR17=%f MOhm\n',R17)
34 Av=Iq*R17/(2*Vt);
35 printf ('\nsmall signal voltage gain=%f\n',Av)

```

---

**Scilab code Exa 11.17** Calculate the output resistance

```

1 clear;
2 clc;

```

```

3 //Example 11.17
4 Va=100;
5 R4=10;
6 b=100;
7 Rc11=1.26*10^3;
8 r8=2.6;
9 Iq=0.2;
10 Rc7=Va/Iq;
11 printf ('\nRc7=%f KOhm\n',Rc7)
12 Z=Rc11*Rc7/(Rc11+Rc7);
13 printf ('\nZ=%f KOhm\n',Z)
14 x=(r8+Z)/(1+b);
15 Ro=R4*x/(R4+x);
16 printf ('\noutput resistance=%f KOhm\n',Ro)

```

---

**Scilab code Exa 11.19** Determine the differential mode voltage gain

```

1 clear;
2 clc;
3 //Example 11.19
4 b=100;
5 Vt=0.026;
6 Rc=20;
7 Ir4=0.4;
8 Iq=Ir4;
9 Ir6=Ir4;
10 r4=b*Vt/Ir4;
11 printf ('\nr4=%f KOhm\n',r4)
12 r3=b^2*Vt/Ir4;
13 printf ('\nr3=%f KOhm\n',r3)
14 Ri2=r3+(1+b)*r4;
15 printf ('\ninput resistance=%f KOhm\n',Ri2)
16 gm=Iq/(2*Vt);
17 printf ('\ntransconductance=%f mA/V\n',gm)
18 Ad1=gm*Rc*Ri2/(2*(Rc+Ri2));

```

```

19 printf ('\n gain of differential amplifier stage=%f\n\
20 n', Ad1)
21 r5=b*Vt/Ir6;
22 printf ('\n r5=%f fKOhm\n', r5)
23 Ir7=2;
24 r6=b*Vt/Ir7;
25 printf ('\n r6=%f f KOhm\n', r6)
26 R6=16.5;
27 R7=5;
28 Ri3=r5+(1+b)*(R6+r6+(1+b)*R7);
29 Ri3=Ri3*0.001; //MOhm
30 printf ('\n Ri3=%f f MOhm\n', Ri3)
31 Rs=5;
32 A2=Ir4*Rs/(2*Vt);
33 printf ('\n voltage gain A2=%f\n', A2)
34 A3=1; //vo/vo3
35 Ad=Ad1*A2*A3;
36 printf ('\n small signal voltage gain=%f\n', Ad)

```

---

**Scilab code Exa 11.20** Determine the zero and pole frequencies

```

1 clear;
2 clc;
3 //Example 11.20
4 Ro=10000000;
5 Co=1*10^-12;
6 Rb=500;
7 r=10000;
8 b=100;
9 f=1/(2*pi*Ro*Co);
10 f=f*0.001; //KHz
11 printf ('\n frequency of the zero=%f f KHz\n', f)
12 Req=Ro*(1+Rb/r)/(1+Rb/r+2*(1+b)*Ro/r);
13 printf ('\n Req=%f Ohm\n', Req)
14 f=1/(2*pi*Req*Co);

```

```
15 f=f*10^-9; //GHz
16 printf( '\nfrequency of the pole=%f GHz\n', f)
```

---

# Chapter 12

## Feedback and Stability

**Scilab code Exa 12.1** Calculate the feedback transfer function

```
1 clear;
2 clc;
3 //Example 12.1
4 A=10^5; //open loop gain
5 Af=50; //closed loop gain
6 b=(A/Af-1)/A;
7 printf ('\nfeedback transfer function=%f\n',b)
8 A=-10^5;
9 Af=-50;
10 b=(A/Af-1)/A;
11 printf ('\nfeedback transfer function=%f\n',b)
```

---

**Scilab code Exa 12.2** Calculate the percent change in the closed loop gain  
Af

```
1 clear;
2 clc;
3 //Example 12.2
```

```

4 A=10^5;
5 Af=50;
6 b=0.019999;
7 dA=10^4;
8 dAf=Af*dA/(A*(1+b*A));
9 printf ('\n dAf=%e\n',dAf)
10 //x=dAf/Af
11 x=dAf/Af;
12 x=x*100;
13 printf ('\n percent change dAf/Af=%f\n',x)

```

---

**Scilab code Exa 12.3** Determine the bandwidth of a feedback amplifier

```

1 clear;
2 clc;
3 //Example 12.3
4 Ao=10^4;
5 wh=2*pi*100; // rad/s
6 Af=50;
7 //x=(1+bAo)
8 x=Ao/Af;
9 printf ('\n(1+bAo)=%f\n',x)
10 wfh=wh*x;
11 printf ('\n closed loop bandwidth=%f\n',wfh)

```

---

**Scilab code Exa 12.5** Determine the input resistance and output resistance

```

1 clear;
2 clc;
3 //Example 12.5
4 Av=10^5;
5 Avf=50;

```

```

6 Rf=10; //Kohm
7 Ro=20000; //Ohm
8 //x=(1+bvAv)
9 x=Av/Avf;
10 printf( '\n(1+bvAv)=%e\n' ,x)
11 Rif=Rf*x;
12 Rif=Rif*0.001; //MOhm
13 printf( '\ninput resistance=%.2f MOhm\n' ,Rif)
14 Rof=Ro/x;
15 printf( '\noutput resistance=%.2f Ohm\n' ,Rof)

```

---

**Scilab code Exa 12.6** Determine the input resistance and output resistance

```

1 clear;
2 clc;
3 //Example 12.6
4 Af=10^5;
5 Aif=50;
6 Rf=10000;
7 Ro=20;
8 //x=(1+biAi)
9 x=Af/Aif;
10 printf( '\n(1+biAi)=%e\n' ,x)
11 Rif=Rf/x;
12 printf( '\ninput resistance =%.2f Ohm\n' ,Rif)
13 Rof=Ro*x;
14 Rof=Rof*0.001; //Mohm
15 printf( '\noutput resistance=%.2f MOhm\n' ,Rof)

```

---

**Scilab code Exa 12.7** Determine the expected input resistance

```
1 clear;
```

```

2 clc;
3 //Example 12.7
4 Ri=50;
5 R1=10;
6 R2=90;
7 Av=10^4;
8 bv=1/(1+R2/R1);
9 printf ('\nfeedback transfer function=%f\n',bv)
10 Rif=Ri*(1+bv*Av);
11 Rif=Rif*0.001; //Mohm
12 printf ('\ninput resistance=%f MOhm\n',Rif)

```

---

**Scilab code Exa 12.11** Determine the transconductance gain of a transistor feedback circuit

```

1 clear;
2 clc;
3 //Example 12.11
4 hFE=100; //transistor parameter
5 Vbe=0.7;
6 Vcc=10;
7 R1=55;
8 R2=12;
9 Re=1;
10 Rc=4;
11 Rl=4;
12 Icq=0.983;
13 Vceq=5.08;
14 Vt=0.026;
15 r=hFE*Vt/Icq;
16 printf ('\nsmall signal parameter resistance=%f
    KOhm\n',r)
17 gm=Icq/Vt;
18 printf ('\ntransconductance=%f mA/V\n',gm)
19 Agf=-gm*(Rc/(Rc+Rl))/(1+Re*(gm+1/r));

```

```

20 printf ('\ntransconductance transfer function=%f mA
/V\n',Agf)
21 //as first approximation
22 Agf2=-1/Re;
23 printf ('\nAgf=%f mA/V\n',Agf2)
24 Avf=Agf*Rl;
25 printf ('\nvoltage gain=%f\n',Avf)

```

---

**Scilab code Exa 12.16** Determine the loop gain

```

1 clear;
2 clc;
3 //Example 12.15
4 //Determine the loop gain fig12.45(a)
5 hFE=100;
6 Vbe=0.7;
7 Icq=0.492;
8 r=5.28;
9 gm=18.9;
10 Rs=10;
11 R1=51;
12 R2=5.5;
13 Re=0.500;
14 Rc=10;
15 Rf=82;
16 x=r*R2/(r+R2);
17 y=R1*x/(x+R1);
18 t=Rs*y/(y+Rs);
19 Req=t;
20 printf ('\nequivalent resistance=%f KOhm\n',t)
21 T=gm*Rc*Req/(Rc+Rf+Req);
22 printf ('\nthe loop gain=%f\n',T)

```

---

**Scilab code Exa 12.19** Determine the stability of an amplifier

```
1 clear;
2 clc;
3 //Example 12.19
4 //T=b*100/(sqrt(1+(f/10^5)^2)) angle=-3tan^-1(f/10^5)
5 //stable at f180 at which phase becomes -180 degrees
6 //-3*atan(f180/10^5)=-180
7 f180=tand(180/3)*10^5;
8 printf ('\n frequency at -180 degree=%ef Hz\n',f180)
9 b=0.2;
10 T=b*100/(sqrt(1+(f180/10^5)^2))^3;
11 printf ('\nmagnitude of the loop gain=%.2f\n',T)
12 b=0.02;
13 T=b*100/(sqrt(1+(f180/10^5)^2))^3;
14 printf ('\nmagnitude of the loop gain=%.2f\n',T)
```

---

**Scilab code Exa 12.22** Determine the shift in the 3dB frequency

```
1 clear;
2 clc;
3 //Example 12.22
4 Ao=10^6;
5 fPD=0.010; //KHz
6 b=0.01;
7 Af=Ao/(1+b*Ao);
8 printf ('\n low frequency closed loop gain=%.2f\n',Af)
9 fc=fPD*(1+b*Ao);
10 printf ('\n closed loop 3dB frequency=%.2f KHz\n',fc)
```

---

**Scilab code Exa 12.23** Determine the shift in the 3dB frequency

```
1 clear;
```

```
2 clc;
3 //Example 12.23
4 A=10^3;
5 Cf=30*10^-12; //feedback capacitor (F)
6 R2=5*10^5;
7 Cm=Cf*(1+A);
8 printf ('\nMiller capacitance=%e F\n',Cm)
9 fp=1/(2*pi*R2*Cm);
10 printf ('\ndominant pole frequency =%.2 fHz\n',fp)
```

---

# Chapter 13

## Operational Amplifier Circuits

**Scilab code Exa 13.1** Calculate the dc currents

```
1 clear;
2 clc;
3 //Example 13.1
4 V1=15; //positive supply voltage
5 V2=-15; //negative supply voltage
6 Veb12=0.6;
7 Vbe11=0.6;
8 Rs=40;
9 Iref=(V1-V2-Veb12-Vbe11)/Rs;
10 printf ('\nreference current=%.2f mA\n',Iref)
11 Ic10=19;
12 Ic1=Ic10/2;
13 printf ('\nIc1=Ic2=Ic3=Ic4= %.3f microA \n',Ic1)
14 Ic1=Ic1*0.001; //mA
15 Vbe7=0.6;
16 Vbe6=0.6;
17 Ic6=Ic1;
18 R2=1;
19 Vc6=Vbe7+Vbe6+Ic6*R2+V2;
20 printf ('\nvoltage at collector of Q6=%.2f V\n',Vc6)
```

---

**Scilab code Exa 13.2** Calculate the bias currents

```
1 clear;
2 clc;
3 //Example 13.2
4 Iref=0.72;
5 Ic17=0.75*Iref;
6 printf ('\ncollector currents in Q17=%f mA\n',Ic17)
7 b=200;
8 Ib17=Ic17/b;
9 Ie17=Ic17;
10 R8=0.100;
11 Vbe17=0.6;
12 R9=50;
13 Ic16=Ib17+(Ie17*R8+Vbe17)/R9;
14 Ic16=Ic16*1000;
15 printf ('\ncollector current in Q16=%f microA\n',
           Ic16)
```

---

**Scilab code Exa 13.3** Calculate the bias currents

```
1 clear;
2 clc;
3 //Example 13.3
4 Is1=10^-14; //reverse saturation currents for Q18 Q19
5 Is2=3*10^-14; //reverse saturation currents for Q14
                 Q20
6 Iref=0.72;
7 Vt=0.026;
8 Ic13a=0.25*Iref;
9 printf ('\nIc13a=%f mA\n',Ic13a)
10 Vbe19=0.6;
```

```

11 R10=50;
12 Ir1o=Vbe19/R10;
13 printf ('\ncurrent in Ro=%f mA\n',Ir1o)
14 Ic19=Ic13a-Ir1o;
15 printf ('\ncurrent in Q19 =%.3fmA\n',Ic19)
16 Ic19=Ic19*0.001; //A
17 Vbe19=Vt*log(Ic19/Is1);
18 printf ('\nB-E voltage of Q19=%f V\n',Vbe19)
19 b=200;
20 Ic19=Ic19*10^6; //micro A
21 Iv19=Ic19*1000;
22 Ib18=Ic19/b;
23 Ir1o=Ir1o*1000;
24 printf ('\nbase current in Q18=%f microA\n',Ib18)
25 Ic18=Ir1o+Ib18;
26 printf ('\n currents in Q18=%f microA\n',Ic18)
27 Ic18=Ic18*10^-6;
28 Vbe18=Vt*log(Ic18/Is1);
29 printf ('\nB-E voltage of Q18=%f V\n',Vbe18)
30 Vbb=Vbe18+Vbe19;
31 printf ('\nvoltage difference Vbb=%f V\n',Vbb)
32 Ic14=Is2*exp(Vbb/(2*Vt));
33 Ic14=Ic14*10^6; //micro A
34 printf ('\n quiescent currents in Q14 and Q20 =%.
fmicroA\n',Ic14)

```

---

**Scilab code Exa 13.4** Determine the small signal differential voltage gain

```

1 clear;
2 clc;
3 //Example 13.4
4 b=200;
5 Va=50
6 Vt=0.026;
7 R2=1;

```

```

8 Ic6=0.0095;
9 Ic4=Ic6;
10 Ic16=0.0158;
11 Ic17=0.54;
12 r17=b*Vt/Ic17;
13 printf ('\ninput resistance to gain stage=%.2 f KOhm\n',
14 ,r17)
14 R9=50;
15 R8=0.100;
16 x=r17+(1+b)*R8;
17 Re=x*R9/(x+R9);
18 printf ('\nRe=%0.3 f KOhm\n',Re)
19 r16=b*Vt/Ic16;
20 printf ('\nr16=%0.2 f KOhm\n',r16)
21 Ri2=r16+(1+b)*Re;
22 Ri2=Ri2*0.001; //MOhm
23 printf ('\nRi2=%0.2 f KOhm\n',Ri2)
24 r6=b*Vt/Ic6;
25 printf ('\nresistance of the active load=%0.2 f KOhm\n',
26 ,r6)
26 gm=Ic6/Vt;
27 printf ('\ntransconductance =%.3 fmA/V\n',gm)
28 ro6=Va/Ic6;
29 ro6=ro6*0.001; //MOhm
30 printf ('\nro6=%0.2 f MOhm\n',ro6)
31 R=ro6*(1+gm*R2*r6/(R2+r6));
32 printf ('\nneffective resistance of active load=%0.2 f
33 MOhm\n',R)
33 ro4=Va/Ic4;
34 ro4=ro4*0.001; //Mohm
35 printf ('\nResistance ro4=%0.2 f KOhm\n',ro4)
36 Icq=9.5;
37 x=Ri2*R/(R+Ri2);
38 y=ro4*x/(ro4+x);
39 Ad=-y*Icq/Vt;
40 printf ('\nsmall signal differential voltage gain=%0.2
41 f\n',Ad)

```

---

**Scilab code Exa 13.5** Determine the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 13.5
4 bp=50;
5 bn=200;
6 Va=50;
7 R9=50;
8 R8=0.100;
9 Rl=2;
10 Vt=0.026;
11 Ri2=4070;
12 Ic20=0.138;
13 r20=bp*Vt/Ic20;
14 printf ('\n r20=%f KOhm\n',r20)
15 R20=r20+(1+bp)*Rl;
16 printf ('\n R20=%f KOhm\n',R20)
17 Ic13A=0.18;
18 R19=Va/Ic13A;
19 printf ('\n R19=%f KOhm\n',R19)
20 r22=bp*Vt/Ic13A;
21 printf ('\n r22=%f KOhm\n',r22)
22 Ri3=r22+(1+bp)*R19*R20/(R19+R20);
23 Ri3=Ri3*0.001; //MOhm
24 printf ('\n input resistance to the output stage=%f
    MOhm\n',Ri3)
25 Ic13B=0.54;
26 R=Va/Ic13B;
27 printf ('\n effective resistance of the active load=%
    .2 f KOhm\n',R)
28 Ic17=Ic13B;
29 R17=Va/Ic17;
30 printf ('\n output resistance Ro17 =%f KOhm\n',R17)
```

```

31 Ri3=Ri3*1000; //KOhm
32 r17=9.63;
33 x=R17*Ri3/(Ri3+R17);
34 y=x*R/(R+x);
35 A=-bn*R9*(1+bn)*y/(Ri2*(R9+r17+(1+bn)*R8));
36 printf ('\nsmall signal voltage gain=%f\n',A)

```

---

### Scilab code Exa 13.6 Calculate the output resistance

```

1 clear;
2 clc;
3 //Example 13.6
4 Ic20=2;
5 bn=200;
6 bp=50;
7 Va=50;
8 r17=9.63;
9 r22=7.22;
10 R20=0.260;
11 gm17=20.8;
12 ro17=92.6;
13 Ro13B=92.6;
14 R8=0.100;
15 Rc17=ro17*(1+gm17*R8*r17/(R8+r17));
16 printf ('\nRc17=%f KOhm\n',Rc17)
17 Rc22=(r22+Rc17*Ro13B/(Rc17+Ro13B))/(1+bp);
18 printf ('\nRc22=%f KOhm\n',Rc22)
19 Ic13A=0.18;
20 Rc19=Va/Ic13A;
21 printf ('\nRc19=%f KOhm\n',Rc19)
22 Rc20=(R20+Rc22*Rc19/(Rc22+Rc19))/(1+bp);
23 printf ('\nRc20=%f KOhm\n',Rc20)
24 Rc20=Rc20*1000; //Ohm
25 R3=22;
26 Ro=R3+Rc20;

```

```
27 printf ('\noutput resistance=%f Ohm\n', Ro)
```

---

**Scilab code Exa 13.7** Determine the dominant pole frequency of the 741 op amp

```
1 clear;
2 clc;
3 //Example 13.7
4 Av2=285;
5 C1=30;
6 Ci=C1*(1+Av2);
7 printf ('\ninput capacitance=%f pF\n', Ci)
8 R12=4.07;
9 Ract=7.18;
10 ro4=5.26;
11 Ro1=Ract*ro4/(Ract+ro4);
12 printf ('\ngate stage input resistance=%fMOhm \n', Ro1)
13 Req=Ro1*R12/(R12+Ro1);
14 printf ('\nequivalent resistance=%f MOhm\n', Req)
15 Req=Req*10^6; //Ohm
16 Ci=Ci*10^-12; //F
17 fPD=1/(2*pi*Req*Ci);
18 printf ('\ndominant pole frequency =%fHz\n', fPD)
```

---

**Scilab code Exa 13.9** Determine the small signal voltage gain

```
1 clear;
2 clc;
3 //Example 13.9
4 //lambda=y
5 y=0.02;
6 //W/L=x and u*Cox/2=t
```

```

7 x=12.5;
8 t=10;
9 Kp1=x*t;
10 printf ('\nconduction parameters of M1 and M2=%.
           fmicroA/V^2\n',Kp1)
11 Kp1=Kp1*0.001; //mA/V^2
12 Id=0.0199;
13 ro2=1/(y*Id);
14 ro2=ro2*0.001; //Mohm
15 printf ('\noutput resistance=%.2f MOhm\n',ro2)
16 Iq=0.0397;
17 ro2=ro2*1000; //Kohm
18 ro4=ro2;
19 Ad=sqrt(2*Kp1*Iq)*ro2*ro4/(ro2+ro4);
20 printf ('\nthe gain of input stage=%.2f \n',Ad)
21 Kn7=0.250;
22 Id7=Iq;
23 gm7=2*sqrt(Kn7*Id7)
24 printf ('\ntransconductance of M7=% .2f mA/V\n',gm7)
25 ro7=1/(y*Id7);
26 ro7=ro7*0.001;
27 printf ('\noutput resistance of M7 and M8 =%.2fMOhm\n
           ',ro7)
28 ro7=ro7*1000; //Kohm
29 ro8=ro7;
30 Av2=gm7*ro7*ro8/(ro7+ro8);
31 printf ('\ngain of the second stage=% .2f\n',Av2)
32 Av=Ad*Av2;
33 printf ('\noverall voltage gain=% .2f\n',Av)

```

---

**Scilab code Exa 13.10** Determine the differential mode voltage gain

```

1 clear;
2 clc;
3 //Example 13.10

```

```

4 Iref=100;
5 Kn=80;
6 Kp=40;
7 //W/L=x
8 x=25;
9 //lambda=y
10 y=0.02;
11 Id=Iref/2;
12 gm1=2*sqrt(Kp*x*Id/2);
13 printf ('\ntransconductance gm1=gm8=%f microA/V\n', gm1)
14 gm6=2*sqrt(Kn*x*Id/2);
15 printf ('\ntransconductance=%f microA/V\n', gm6)
16 r01=1/(y*Id);
17 r08=r01;
18 r06=r01;
19 r010=r01;
20 printf ('\noutput resistance r01=r08=r06=r010=%f MOhm\n', r01)
21 Id4=Iref;
22 r04=1/(y*Id4);
23 printf ('\nro4=%f MOhm\n', r04)
24 Ro8=gm1*r08*r010;
25 printf ('\ncomposite output resistances =%f MOhm\n', Ro8)
26 Ro6=gm6*r06*r04*r01/(r04+r01);
27 printf ('\ncomposite output resistances=%f MOhm\n', Ro6)
28 Ad=gm1*Ro6*Ro8/(Ro6+Ro8);
29 printf ('\ndifferential voltage gain=%f\n', Ad)

```

---

**Scilab code Exa 13.12** Determine the small signal voltage gain

```

1 clear;
2clc;

```

```

3 //Example 13.12
4 Kp=0.6;
5 bn=200;
6 Va=50;
7 Vt=0.026;
8 Ic13=0.20;
9 Ri2=bn*Vt/Ic13;
10 printf ('\ninput resistance to the gain stage=%.2f
           KOhm\n',Ri2)
11 Iq5=Ic13;
12 Ad=sqrt(2*Kp*Iq5)*Ri2;
13 printf ('\nsmall signal voltage gain=%.2f\n',Ad)

```

---

**Scilab code Exa 13.13** Determine the small signal voltage gain

```

1 clear;
2 clc;
3 //Example 13.13
4 Va=150;
5 Vt=0.026;
6 Ic13=0.2;
7 gm13=Ic13/Vt;
8 printf ('\ntransconductance=%.2f mA/V\n',gm13)
9 ro13=Va/Ic13;
10 printf ('\noutput resistance=%.2f KOhm\n',ro13)
11 Av2=gm13*ro13;
12 printf ('\nvoltage gain=%.2f \n',Av2)

```

---

**Scilab code Exa 13.14** Determine the dominant pole frequency and unity gain bandwidth

```

1 clear;
2 clc;

```

```
3 //Example 13.14
4 Av2=5768;
5 C1=12;
6 Ci=C1*(1+Av2);
7 printf ('\n effective input capacitance=%f pF\n',Ci)
8 Ri2=26000; //gain stage input resistance (Ohm)
9 Ci=Ci*10^-12; //F
10 fPD=1/(2*pi*Ri2*Ci);
11 printf ('\n dominant pole frequency=%f Hz\n',fPD)
12 Av=73254;
13 fT=fPD*Av;
14 fT=fT*10^-6; //MHz
15 printf ('\n unity gain bandwidth=%f MHz\n',fT)
```

---

# Chapter 14

## Nonideal Effects in Operational Amplifier Circuits

**Scilab code Exa 14.2** Determine the closed loop input resistance

```
1 clear;
2 clc;
3 //Example 14.2
4 R2=10000;
5 Ri=10000;
6 Aol=10^5;
7 Rif=1/(1/Ri+(1+Aol)/R2);
8 printf ('\nclosed loop input resistance =%.2fOhm\n',Rif)
```

---

**Scilab code Exa 14.3** Determine the closed loop input resistance

```
1 clear;
2 clc;
3 //Example 14.3
4 Aol=10^5;
```

```

5 Ri=10;
6 R1=10;
7 R2=R1;
8 Rif=(Ri*(1+Ao1)+R2*(1+Ri/R1))/(1+R2/R1);
9 Rif=Rif*0.001; //Mohm
10 printf ('\ninput resistance =%.fMOhm\n',Rif)

```

---

**Scilab code Exa 14.5** Determine the unity gain bandwidth and the closed loop gain

```

1 clear;
2 clc;
3 //Example 14.5
4 Ao=2*10^5;
5 fPD=5;
6 fT=fPD*Ao;
7 printf ('\nunity gain bandwidth=%e Hz\n',fT)
8 f3dB=20*10^3;
9 Acl=fT/f3dB;
10 printf ('\nclosed loop gain=%.2f\n',Acl)

```

---

**Scilab code Exa 14.6** Calculate the slew rate of the 741 op amp

```

1 clear;
2 clc;
3 //Example 14.6
4 Iq=19*10^-6;
5 C1=30*10^-12;
6 SR=Iq/C1;
7 SR=SR*10^-6;
8 printf ('\nslew rate=%.2f V/micros\n',SR)

```

---

**Scilab code Exa 14.7** Determine the small signal bandwidth of an amplifier and full power bandwidth

```
1 clear;
2 clc;
3 //Example 14.7
4 fT=1000; //KHz
5 Aclo=10;
6 SR=1*10^3;
7 Vpo=10;
8 f3dB=fT/Aclo;
9 printf ('\nsmall signal closed loop bandwidth=%f f
          KHz\n',f3dB)
10 fmax=SR/(2*pi*Vpo);
11 printf ('\nfull power bandwidth=%f f KHz\n',fmax)
```

---

**Scilab code Exa 14.8** Calculate the offset voltage in bipolar diff amp

```
1 clear;
2 clc;
3 //Example 14.8
4 Is1=10^-14;
5 Is2=1.05*10^-14;
6 Vt=0.026;
7 Vos=Vt*log(Is2/Is1);
8 printf ('\nthe offset voltage =%fV\n',Vos)
```

---

**Scilab code Exa 14.10** Calculate the offset voltage in MOSFET diff amp

```

1 clear;
2 clc;
3 //Example 14.10
4 Kn1=105;
5 Kn2=100;
6 Iq=200;
7 dKn=Kn1-Kn2;
8 printf ('\ndifference in conduction parameter=%.2f
           microA/V^2\n',dKn)
9 Kn=(Kn1+Kn2)/2;
10 printf ('\naverage of the conduction parameter=%.2f
            microA/V^2\n',Kn)
11 Vos=sqrt(Iq/(2*Kn))*dKn/(2*Kn);
12 printf ('\noffset voltage=%f V\n',Vos)

```

---

**Scilab code Exa 14.11** Determine the range of voltage produced by an offset voltage compensation network

```

1 clear;
2 clc;
3 //Example 14.11
4 Rs=100;
5 R4=100000;
6 R3=100000;
7 V1=15;
8 V2=-15;
9 Vy=Rs*V1/(Rs+R4);
10 Vy=Vy*1000; //mV
11 printf ('\nVoltage Vy =%.2fmV\n',Vy)

```

---

**Scilab code Exa 14.13** Determine the bias current effect

```
1 clear;
```

```
2 clc;
3 //Example 14.13
4 R1=10;
5 R2=100;
6 Ib1=1.1*10^-3;
7 Ib2=1*10^-3;
8 vo=Ib1*R2;
9 printf ('\noutput voltage =%.2fV\n',vo)
10 R3=R1*R2/(R1+R2);
11 printf ('\nR3=% .2f KOhm\n',R3)
12 vo=R2*(Ib1-Ib2);
13 printf ('\noutput voltage=% .2f V\n',vo)
```

---

# Chapter 15

## Applications and Design of Integrated Circuits

**Scilab code Exa 15.2** Determine the clock frequency

```
1 clear;
2 clc;
3 //Example 15.2
4 C=20*10^-6;
5 Req=1000;
6 fC=1/(C*Req);
7 printf ('\n clock frequency =%.2fKHz\n', fC)
```

---

**Scilab code Exa 15.3** Design a one pole low pass switched capacitor filter

```
1 clear;
2 clc;
3 //Example 15.3
4 fC=10000;
5 f3dB=1000;
6 //x=C2/C1
```

```
7 x=2*pi*f3dB/fC;
8 printf('n capacitances C2/C1=%f\n',x)
```

---

**Scilab code Exa 15.4** Determine the oscillation frequency and required amplifier gain

```
1 clear;
2 clc;
3 //Example 15.4
4 C=0.1*10^-6;
5 R=1000;
6 fo=1/(2*pi*R*C*sqrt(3));
7 printf('the oscillation frequency =%.2f Hz\n',fo)
8 //minimum amplifier gain=8
9 R=1; //KOhm
10 R2=8*R;
11 printf('R2=%.f KOhm\n',R2)
```

---

**Scilab code Exa 15.6** Determine the hysteresis width of a particular Schmitt trigger

```
1 clear;
2 clc;
3 //Example 15.6
4 R1=10000;
5 R2=90000;
6 Vh=10;
7 Vl=-10;
8 Vth=R1*Vh/(R1+R2);
9 printf('upper crossover voltage=%f V\n',Vth)
10 Vtl=R1*Vl/(R1+R2);
11 printf('lower crossover voltage=%f V\n',Vtl)
12 x=Vth-Vtl;
```

```
13 printf( '\n hysteresis width =%.fV\n' ,x)
```

---

**Scilab code Exa 15.7** Design a Schmitt trigger circuit

```
1 clear;
2 clc;
3 //Example 15.7
4 Vs=2;
5 Vh=15;
6 Vl=-15;
7 //hysteresis width=x
8 x=60*0.001; //(V)
9 //Vth-Vtl=(R1/(R1+R2))*(Vh-Vl)
10 //R2/R=y
11 y=(Vh-Vl)/x-1;
12 printf( '\nR2/R1=% .2 f \n' ,y)
13 Vref=(1+1/y)*Vs;
14 printf( '\nreference voltage=% .4 f V\n' ,Vref)
```

---

**Scilab code Exa 15.10** Design the 555IC as a monostable multivibrator

```
1 clear;
2 clc;
3 //Example 15.10
4 C=15*10^-9;
5 T=100*10^-6; //(s) time
6 R=T/(1.1*C);
7 R=R*0.001; //Kohm
8 printf( '\nResistance R=% .2 f KOhm\n' ,R)
```

---

**Scilab code Exa 15.13** Design the supply voltage

```
1 clear;
2 clc;
3 //Example 15.13
4 Rl=10; //load resistance
5 P1=20; //power delivered to the load
6 Ps=20; //(W)
7 Vp=sqrt(2*Rl*P1);
8 printf ('\npeak output voltage=%.2f V\n',Vp)
9 Ip=Vp/Rl;
10 printf ('\npeak load current =%.2fA\n',Ip)
11 Vs=%pi*Rl*Ps/Vp;
12 printf ('\nrequired supply voltage=%.2f V\n',Vs)
```

---

**Scilab code Exa 15.14** Determine the output resistance and load regulation

```
1 clear;
2 clc;
3 //Example 15.14
4 Vonl=5;
5 Vofl=4.96;
6 I1=0.005;
7 I2=1.5;
8 dVo=Vonl-Vofl;
9 dIo=I1-I2;
10 Rvf=-dVo/dIo;
11 printf ('\noutput resistance=%f Ohm\n',Rvf)
12 LR=100*(Vonl-Vofl)/Vonl;
13 printf ('\nload regulation =%.2f\n',LR)
```

---

**Scilab code Exa 15.15** Determine the output resistance and variation in output voltage

```
1 clear;
2 clc;
3 //Example 15.15
4 Aol=1000;
5 Vref=5;
6 Vo=10;
7 Io=0.1*0.001;
8 Vt=0.026;
9 Rof=2*Vt*Vo/(Io*Vref*Aol);
10 printf ('\noutput resistance=%.2 f mOhm\n',Rof)
11 //dVo/Vo=V and dIo/Io=I
12 //V=-I*2*Vt/(Vref*Aol)
13 //V/I=x
14 x=-2*Vt/(Vref*Aol);
15 printf ('\npercent change=%.2 e\n',x)
```

---

**Scilab code Exa 15.16** Determine the bias current temperature compensated reference voltage and required resistor

```
1 clear;
2 clc;
3 //Example 15.16
4 Vz=6.3;
5 Vbe=0.6;
6 Veb=0.6;
7 Vo=8;
8 R1=3.9;
9 R2=3.4;
10 R3=0.576;
11 Ic3=(Vz-3*Vbe)/(R1+R2+R3);
12 printf ('\nbias current =%.3 f mA\n',Ic3)
13 Vb7=Ic3*R1+2*Vbe;
```

```
14 printf( '\ntemperature compensated reference voltage=\n' %.2f V\n', Vb7)\n15 R13=2.23;\n16 R12=R13*Vo/Vb7-R13;\n17 printf( '\nR12=% .2f KOhm\n', R12)
```

---

# Chapter 16

## MOSFET Digital Circuits

**Scilab code Exa 16.3** Design the aspect ratio and determine the power dissipation

```
1 clear;
2 clc;
3 //Example 16.3
4 Vdd=5;
5 Vtnd=0.8;
6 Vtnl=0.8;
7 Kn=35;
8 Vo=0.1;
9 Vi=4.2;
10 //W/L=Y
11 yl=0.5;
12 //Kd/Kl=x
13 x=(Vdd-Vo-Vtnl)^2/(2*Vo*(Vi-Vtnd)-Vo^2);
14 printf ('\nKd/Kl=%f\n',x)
15 //Kd/Kl=yd/yl
16 yd=12.6
17 yl=0.5
18 iD=Kn*yl*(Vdd-Vo-Vtnl)^2/2;
19 printf ('\n drain current =%.2f microA\n',iD)
20 P=iD*Vdd;
```

```
21 printf( '\n power dissipation=% .2f microW\n' ,P)
```

---

**Scilab code Exa 16.4** Design the aspect ratio and determine the power dissipation

```
1 clear;
2 clc;
3 //Example 16.4
4 Vdd=5;
5 Vtnd=0.8;
6 Vtnl=-2;
7 Kn=35;
8 Vo=0.1;
9 Vi=5;
10 //W/L=Y
11 yl=0.5;
12 //Kd/Kl=x
13 x=(-Vtnl)^2/(2*Vo*(Vi-Vtnd)-Vo^2);
14 printf( '\n Kd/Kl=% .2f\n' ,x)
15 //Kd/Kl=yd/yl
16 yd=2.41
17 yl=0.5
18 iD=Kn*yl*(-Vtnl)^2/2;
19 printf( '\n drain current=% .2f microA\n' ,iD)
20 P=iD*Vdd;
21 printf( '\n power dissipation =% .2f microW\n' ,P)
```

---

**Scilab code Exa 16.5** Determine the noise margin of an inverter with enhancement load

```
1 clear;
2 clc;
3 //Example 16.5
```

```

4 Voh=4.2;
5 Vol=0.1;
6 //x=Kd/Kl
7 x=25.1;
8 Vdd=5;
9 Vtnl=0.8;
10 Vohu=4.2;
11 Vil=0.8;
12 Vtnd=0.8;
13 Vih=Vtnd+(Vdd-Vtnl)/x*((1+2*x)/sqrt(1+3*x)-1);
14 printf ('\nVih=% .2f V\n',Vih)
15 Volu=(Vdd-Vtnl+x*(Vih-Vtnd))/(1+2*x);
16 printf ('\noutput voltage corresponding to Vih=% .3f V
          \n',Volu)
17 NMl=Vil-Volu;
18 printf ('\nnoise margin=%0.3f V\n',NMl)
19 NMh=Vohu-Vih;
20 printf ('\nnoise margin=% .3f V\n',NMh)

```

---

**Scilab code Exa 16.9** Determine the critical voltage on the voltage transfer curve of a CMOS inverter

```

1 clear;
2 clc;
3 //Example 16.9
4 Vdd=5;
5 Vtn=1;
6 Vtp=-1;
7 //Kn=Kp hence Kn/Kp=x=1;
8 x=1;
9 Vit=(Vdd+Vtp+sqrt(x)*Vtn)/(1+sqrt(x));
10 printf ('\ninput voltage=% .2f V\n',Vit)
11 Vipt=Vit;
12 Vopt=Vipt-Vtp;
13 printf ('\noutput voltage at the transition point for

```

```

PMOS =%.2fV\n', Vopt)
14 Vint=Vit;
15 Vont=Vint-Vtn;
16 printf ('\noutput voltage at the transition point for
    NMOS=% .2f V\n', Vont)
17 Vdd=10;
18 Vit=(Vdd+Vtp+sqrt(x)*Vtn)/(1+sqrt(x));
19 printf ('\ninput voltage =%.2fV\n', Vit)
20 Vipt=Vit;
21 Vint=Vit;
22 Vopt=Vipt-Vtp;
23 printf ('\noutput voltage at the transition point for
    PMOS =%.2fV\n', Vopt)
24 Vont=Vint-Vtn;
25 printf ('\noutput voltage at the transition point for
    NMOS =%.2fV\n', Vont)

```

---

**Scilab code Exa 16.10** Calculate the power dissipation in CMOS inverter

```

1 clear;
2 clc;
3 //Example 16.10
4 Cl=2*10^-6;
5 Vdd=5;
6 f=100000;
7 P=f*Cl*Vdd^2;
8 printf ('\npower dissipation in the CMOS inverter=% .3
    f microW\n', P)

```

---

**Scilab code Exa 16.11** Determine the noise margins of a CMOS inverter

```

1 clear;
2 clc;

```

```

3 //Example 16.11
4 Vtn=1;
5 Vtp=-1;
6 Vdd=5;
7 Vth=1;
8 Vil=Vtn+3*(Vdd+Vtp-Vth)/8;
9 printf ('\ninput voltage at the transition points Vil
    =%.3f V\n',Vil)
10 Vih=Vtn+5*(Vdd+Vtp-Vtn)/8;
11 printf ('\ninput voltage at the transition points Vih
    =%.3fV\n',Vih)
12 Vohu=1*(2*Vil+Vdd-Vtn-Vtp)/2;
13 printf ('\noutput voltage =%.3f V\n',Vohu)
14 Volu=1*(2*Vih-Vdd-Vtn-Vtp)/2;
15 printf ('\noutput voltage =%.2f V\n',Volu)
16 NML=Vil-Volu;
17 printf ('\nnoise margin =%.3f V\n',NML)
18 NMH=Vohu-Vih;
19 printf ('\nnoise margin=% .3f V\n',NML)

```

---

**Scilab code Exa 16.15** Determine the currents voltages and power dissipation in two NMOS SPAM cells

```

1 clear;
2 clc;
3 //Example 16.15
4 Vdd=3;
5 Kn=60;
6 Vtnd=0.5;
7 //W/L=x
8 xd=2;
9 Vtnl=-1;
10 xl=0.5;
11 R=2; //(MOhm)
12 Vgsl=0;

```

```

13 //solution with Depletion load
14 iD=Kn*xl*(Vgs1-Vtn1)^2/2;
15 printf ('\n drain currents in M1 and M3 =%.fmicroA\n',
16 iD)
16 P=iD*Vdd;
17 printf ('\n power dissipation in the circuit=%f
18 microW\n',P)
18 //iD=Kn/2*x*(2*Vgsd-Vtnd)Vdsd-Vdsd^2
19 Q=poly(0,'Q');
20 p=poly([0.25 -5 1], 'Q', 'c');
21 roots(p)
22 disp("Q=50.5 (mV)")
23 //solution with Resistor load
24 //(Vdd-Q)/R=Kn/2*xd*(2*Vgsd-Vtnd)Q-Q^2
25 Q=poly(0,'Q');
26 p=poly([3 -599 120], 'Q', 'c');
27 roots(p)
28 Q=0.005;
29 disp("Q=5 (mV)")
30 iD=(Vdd-Q)/R;
31 printf ('\n drain current =%.2f microA\n',iD)
32 P=iD*Vdd;
33 printf ('\n power dissipation in the circuit =%.2f
microW\n',P)

```

---

# Chapter 17

## Bipolar Digital Circuits

**Scilab code Exa 17.1** Calculate the currents and voltages in the basic differential amplifier circuit used as digital circuit

```
1 clear;
2 clc;
3 //Example 17.1
4 V1=5;
5 V2=-5;
6 Rc1=1;
7 Rc2=Rc1;
8 Rc=Rc1;
9 Re=2.150;
10 v2=0;
11 //for v1=0
12 vE=-0.7;
13 iE=(vE-V2)/Re;
14 printf ('\nemitter current=%.3f mA\n', iE)
15 iC=1;
16 Vcc=5;
17 vo1=Vcc-iC*Rc;
18 printf ('\nvo1=vo2=%.f V\n', vo1)
19 //for v2=-1
20 vE=-0.7;
```

```

21 iE=2;
22 iC2=2;
23 vo1=5;
24 vo2=Vcc-iC2*Rc;
25 printf ('\\nvo2=%f V\\n',vo2)
26 v1=1;
27 Vbe=0.7;
28 vE=v1-Vbe;
29 iE=(vE-V2)/Re;
30 printf ('\\nemitter current =%.3fmA\\n',iE)
31 iC1=iE;
32 vo1=Vcc-iC1*Rc;
33 printf ('\\nvo1=%f V\\n',vo1)
34 vo2=Vcc

```

---

**Scilab code Exa 17.2** Calculate the currents resistors and logic 0 values in the basic ECL logic gate

```

1 clear;
2 clc;
3 //Example 17.2
4 Vx=-0.7;
5 Vy=Vx;
6 Vbe=0.7;
7 V2=-5.2;
8 Re=1.180;
9 vE=Vx-Vbe;
10 printf ('\\nemitter voltage =%.2fV\\n',vE)
11 iE=(vE-V2)/Re;
12 printf ('\\nemitter current=%f mA\\n',iE)
13 Icxy=iE;
14 vo1=-0.7;
15 Rc1=-vo1/Icxy;
16 printf ('\\nRc1=%f KOhm\\n',Rc1)
17 Vnor=vo1-Vbe;

```

```

18 printf( '\nNOR output logic 0 value=%f V\n' ,Vnor)
19 Vr=(vo1+Vnor)/2;
20 vE=Vr-Vbe;
21 printf( '\nvE=%f V\n' ,vE)
22 iE=(vE-V2)/Re;
23 printf( '\niE=%f mA\n' ,iE)
24 vo2=-0.7;
25 iC2=iE;
26 Rc2=-vo2/iC2;
27 printf( '\nRc2=%f KOhm\n' ,Rc2)
28 Vor=vo2-Vbe;
29 printf( '\nNOR logic 0 value is=%f V\n' ,Vor)

```

---

**Scilab code Exa 17.3** Design the reference position of the ECL circuit

```

1 clear;
2 clc;
3 //Example 17.3
4 Vr=-1.05;
5 Vbe=0.7;
6 Vb5=Vr+Vbe;
7 printf( '\nVb5 =%fV\n' ,Vb5)
8 R1=0.250;
9 i1=-Vb5/R1;
10 printf( '\ni1=%f mA\n' ,i1)
11 Vy=0.7;
12 V2=-5.2;
13 // let R1+R2=x
14 x=(-2*Vy-V2)/i1;
15 R2=x-R1;
16 printf( '\nR2=%f KOhm\n' ,R2)
17 iS=i1;
18 Rs=(Vr-V2)/iS;
19 printf( '\nRs=%f KOhm\n' ,Rs)

```

---

**Scilab code Exa 17.4** Calculate the power dissipated in the ECL logic circuit

```
1 clear;
2 clc;
3 //Example 17.4
4 Vx=-0.7;
5 Vy=-0.7;
6 iCxy=3.22; // (mA)
7 iCR=0;
8 i5=1.40;
9 i1=1.40;
10 Vor=-0.7;
11 R4=1.500;
12 Vnor=-1.4;
13 V2=-5.2;
14 R3=1.500;
15 i3=(Vor-V2)/R3;
16 printf ('\n current i3=%.2f mA\n',i3)
17 i4=(Vnor-V2)/R4;
18 printf ('\n current i4 =%.2fmA\n',i4)
19 P=(iCxy+iCR+i5+i1+i3+i4)*(0-V2);
20 printf ('\n power dissipation=%.2f mW\n',P)
```

---

**Scilab code Exa 17.5** Calculate minimum fanout of ECL logic gate

```
1 clear;
2 clc;
3 //Example 17.5
4 b=50;
5 V2=-5.2;
6 Vbe=0.7;
```

```

7  Rc2=0.240;
8  Vor=-0.75;
9  Re=1.180;
10 iE=(Vor-Vbe-V2)/Re;
11 printf ('\nemitter current=%f mA\n', iE)
12 iB=iE/(1+b);
13 iB=iB*1000; //micro A
14 printf ('\ninput base current=%f microA\n', iB)
15 R3=1.500;
16 i3=(Vor-V2)/R3;
17 printf ('\ni3=%f mA\n', i3)
18 iB=iB*0.001; //mA
19 N=(-(Vor+Vbe)*(1+b)/(Rc2)-i3)/iB;
20 printf ('\nN=%f\n', N)

```

---

### Scilab code Exa 17.7 Analyze the modified ECL logic gate

```

1 clear;
2 clc;
3 //Example 17.7
4 Vcc=1.7;
5 Re=0.008; //mohm
6 Rc=0.008; //mohm
7 Vy=0.4;
8 Vbe=0.7;
9 Vor=Vcc //logic 1
10 Vor=Vcc-Vy //logic 0
11 Vr=1.5;
12 iE=(Vr-Vbe)/Re;
13 printf ('\nemitter current=%f microA\n', iE)
14 iR=Vy/Rc;
15 printf ('\nmaximum current in Rc =%f microA\n', iR)
16 iD=iE-iR;
17 printf ('\ncurrent through the diode=%f microA\n',
           iD)

```

```

18 P=iE*Vcc;
19 printf ('\n power dissipation=% .2f microW\n',P)
20 Vv=1.7;
21 iE=(Vv-Vbe)/Re;
22 printf ('\niE =% .2f microA\n',iE)
23 P=iE*Vcc;
24 printf ('\n power dissipation =% .2f microW\n',P)

```

---

**Scilab code Exa 17.9** Calculate the currents and voltages for the basic TTL NAND circuit

```

1 clear;
2 clc;
3 //Example 17.9
4 bf=25;
5 b=bf;
6 br=0.1;
7 Vcc=5;
8 R1=4;
9 Vbc=0.7;
10 Vy=0.1;
11 Vx=0.1;
12 R2=1.6;
13 Vbe=0.8;
14 Rc=4;
15 Vce=0.1;
16 vB2=Vx+Vce;
17 printf ('\nvB2=% .2f V\n',vB2)
18 vB1=Vx+Vbe;
19 printf ('\nbbase voltage=% .2f V\n',vB1)
20 i1=(Vcc-vB1)/R1;
21 printf ('\ncurrent i1=% .2f mA\n',i1)
22 vB1=Vbe+Vbe+Vbc;
23 printf ('\nvB1=% .2f V\n',vB1)
24 vC2=Vbe+Vce;

```

```

25 printf ('\ncollector voltage=%f V\n',vC2)
26 i1=(Vcc-vB1)/R1;
27 printf ('\ncurrent i1 =%.2fmA\n',i1)
28 iB2=(1+2*br)*i1;
29 printf ('\niB2=%.2f mA\n',iB2)
30 i2=(Vcc-vC2)/R2;
31 printf ('\ni2 =%.2fmA\n',i2)
32 iE2=i2+iB2;
33 printf ('\niE2=%.2f mA\n',iE2)
34 Rb=1;
35 i4=Vbe/Rb;
36 printf ('\ncurrent in the pull down resistor=%f mA\
n',i4)
37 iBo=iE2-i4;
38 printf ('\nbase drive to the output transistor=%f
mA\n',iBo)
39 i1=(Vcc-Vce)/Rc;
40 printf ('\ni1=%f mA\n',i1)

```

---

**Scilab code Exa 17.11** Determine the currents in a Schottky transistor

```

1 clear;
2 clc;
3 //Example 17.11
4 b=25;
5 iB=1;
6 iC=2;
7 ic=(iB+iC)/(1+1/b);
8 printf ('\nninternal collector current=%f mA\n',ic)
9 ib=ic/b;
10 printf ('\nninternal base current =%.3fmA\n',ib)
11 iD=iB-ib;
12 printf ('\nSchottky diode current=%f mA\n',iD)
13 iC=20;
14 ic=(iB+iC)/(1+1/b);

```

```

15 printf ('\ninternal collector current=%f mA\n',ic)
16 ib=ic/b;
17 printf ('\ninternal base current =%fmA\n',ib)
18 iD=iB-ib;
19 printf ('\nSchottky diode current=%f mA\n',iD)

```

---

**Scilab code Exa 17.12** Calculate the power dissipation in a low power Schottky TTL circuit

```

1 clear;
2 clc;
3 //Example 17.12
4 Vy=0.3;
5 Vbe=0.7;
6 vx=0.4;
7 R2=8;
8 Vce=0.4;
9 Vcc=5;
10 b=25;
11 Vce=0.4;
12 Vbe1=0.7;
13 Vbe2=0.7;
14 Vcc=5;
15 R1=20;
16 v1=Vce+Vy;
17 i1=(Vcc-v1)/R1;
18 printf ('\ni1=%f mA\n',i1)
19 P1=i1*(Vcc-vx);
20 printf ('\npower dissipation=%f mW\n',P1)
21 v1=Vbe1+Vbe2;
22 printf ('\nv1=%f V\n',v1)
23 vC2=Vbe1+Vce;
24 printf ('\nvoltage vC2 =%f V\n',vC2)
25 i1=(Vcc-v1)/R1;
26 printf ('\ncurrent i1 =%fmA\n',i1)

```

```
27 i2=(Vcc-vC2)/R2;
28 printf ('\n current i2 =%.3fmA\n',i2)
29 P=(i1+i2)*Vcc;
30 printf ('\n power dissipation for high input condition
=%.3f mW\n',P)
```

---