

Scilab Textbook Companion for  
Basic Electrical Engineering  
by C. L. Wadhwa<sup>1</sup>

Created by  
Manoj A  
B.Tech Third Year  
Electrical Engineering  
National Institute of Technology, Karnataka.  
College Teacher  
Debasisha Jena  
Cross-Checked by  
Ganesh R

July 4, 2014

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Basic Electrical Engineering

**Author:** C. L. Wadhwa

**Publisher:** New Age International Ltd.

**Edition:** 4

**Year:** 2007

**ISBN:** 978-81-224-2947-3

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 AC Circuits</b>	<b>13</b>
<b>2 Network Theory</b>	<b>60</b>
<b>3 Three Phase Supply</b>	<b>90</b>
<b>4 Basic Instruments</b>	<b>103</b>
<b>5 Transformer</b>	<b>110</b>
<b>6 DC Machines</b>	<b>136</b>
<b>7 Three Phase Synchronous Machines</b>	<b>155</b>
<b>8 Three Phase Induction Motors</b>	<b>162</b>
<b>10 Power System</b>	<b>181</b>
<b>11 Domestic Wiring</b>	<b>186</b>
<b>12 DC Circuits</b>	<b>192</b>
<b>13 Electromagnetic Induction</b>	<b>216</b>

# List of Scilab Codes

Exa 1.1	To calculate frequency and instantaneous voltage and time of a voltage wave . . . . .	13
Exa 1.2	To find the current and power . . . . .	14
Exa 1.3	To find the current and power of a capacitive circuit .	15
Exa 1.4	To find the frequency in the RLC Circuit at a phase angle of 45 degrees . . . . .	16
Exa 1.5	To find the inductance of a choke to operate a 120V 500W lamp at 230V . . . . .	17
Exa 1.6	Determine the value of the circuit components . . . .	19
Exa 1.7	To determine circuit impedance and current in a parallel connection of a resistor and capacitor . . . . .	20
Exa 1.8	To find the current and impedance and admittance of the circuit . . . . .	21
Exa 1.9	Maximum current and frequency at which it occurs and respective voltages . . . . .	21
Exa 1.10	RLC circuit problems on resonace . . . . .	22
Exa 1.11	RLC circuit problems with quality factor . . . . .	24
Exa 1.12	RLC circuit problem to find the resonance frequency and impedance magnitude . . . . .	25
Exa 1.13	Series Resonace of a RLC circuit with 2 coils . . . .	26
Exa 1.14	Series Resonance in RLC circuit to find inductance and power . . . . .	27
Exa 1.15	Determine the current in parallel branches and supply current . . . . .	28
Exa 1.16	Determine the original and loaded circuit bandwidth .	30
Exa 1.17	Expression for the sum of energy stored by inductor and capacitor connected in series at resonance . . . . .	31

Exa 1.18	Expression for the sum of energy stored by inductor and capacitor connected in parallel at resonance . . . . .	32
Exa 1.19	To determine bandwidth and half power frequencies . .	32
Exa 1.20	Determine the frequency of resonance and Max value of $R_c$ at resonance . . . . .	33
Exa 1.21	To determine $R_l$ for which resonance can take place . .	34
Exa 1.22	To find the resistor for a given Q factor . . . . .	35
Exa 1.23	Find the flux density . . . . .	36
Exa 1.24	Find the number of ampere turns . . . . .	37
Exa 1.25	To find current in the 600 turn exciting coil . . . . .	38
Exa 1.26	Find the current required to develop a flux of given mWb	39
Exa 1.27	Determine the inductance of individual winding . . . . .	40
Exa 1.28	Determine the inductance of a three coil system . . . . .	41
Exa 1.29	To determine the parameters of an alternating current of 50Hz frequency . . . . .	41
Exa 1.30	Determine the resultant current for two alternating currents . . . . .	42
Exa 1.31	To determine the sum and difference of two alternating voltage sources . . . . .	43
Exa 1.32	Determine the parameters of the circuit and power and pf . . . . .	44
Exa 1.33	Determine circuit paramters of an iron coil . . . . .	45
Exa 1.34	Determine the phase angle between 220V main and the current . . . . .	46
Exa 1.35	To determine the coil parameters with resistance of 5 ohms . . . . .	47
Exa 1.36	Determine the resonant frequency and the source current	47
Exa 1.37	Determine Circuit parameters for a circuit with a current source . . . . .	49
Exa 1.38	Determine the instantaneous energy stored in the capacitor and inductor . . . . .	50
Exa 1.39	To determine the current through all the branches of the given network . . . . .	52
Exa 1.40	To determine parameters to operate the relay . . . . .	54
Exa 1.41	To determine the parameters of a toroid . . . . .	55
Exa 1.42	Determine the magnetic flux for a toriod . . . . .	57
Exa 1.43	To determine the magnetic parameters of a steel ring .	58
Exa 2.1	To determine the current using loop analysis . . . . .	60

Exa 2.2	To calculate current in each branch using loop analysis	61
Exa 2.3	To calculate current in each branch using loop analysis and point voltages in a given network . . . . .	63
Exa 2.4	To calculate current from a battery and pd across points A and B . . . . .	65
Exa 2.5	Determine Current through branch AB of the given network . . . . .	67
Exa 2.6	Determine the current in the branches of the network using nodal analysis . . . . .	67
Exa 2.7	To Calculate current in all branches of the network shown using nodal analysis . . . . .	69
Exa 2.8	Conversion to current source and nodal analysis . . . . .	70
Exa 2.9	Superposition Principle to determine current in branch	71
Exa 2.10	Using thevenin theorem determine current through 2 ohm resistor . . . . .	72
Exa 2.11	To find the current through the branch AB . . . . .	74
Exa 2.12	Determine current through various values of RL . . . . .	75
Exa 2.13	Current through AB using Nortons theorem . . . . .	76
Exa 2.14	To determine current in RL using nortons theorem . . . . .	77
Exa 2.15	To find current across 2ohm resistor using nortons theorem . . . . .	78
Exa 2.16	To determine the current in the 2 ohm resistor using superposition theorem . . . . .	79
Exa 2.17	To determine the value of RL for Max power transfer . . . . .	80
Exa 2.18	Star to delta conversion of a circuit . . . . .	81
Exa 2.19	Star Equivalent of the delta circuit . . . . .	82
Exa 2.20	To determine equivalent resistance using star delta transformation . . . . .	83
Exa 2.21	Determine current through branch AB using loop and nodal analysis . . . . .	84
Exa 2.22	Current through 2 ohm resistor given a current source	86
Exa 2.23	To find voltage v and current through 3 ohm resistor using nodal analysis . . . . .	87
Exa 2.24	Determine the current through 10 ohm resistor using thevenins circuit . . . . .	88
Exa 3.1	To determine the parameters of a balanced 3 phase star connected to a resistive load . . . . .	90

Exa 3.2	To determine the parameters of a balanced 3 phase star connected to an impedance . . . . .	91
Exa 3.3	To determine the potential of the star point and line currents . . . . .	92
Exa 3.4	To determine the line currents if one inductor is short circuited . . . . .	93
Exa 3.5	To find line current and pf and powers of a balanced delta load . . . . .	94
Exa 3.6	To find Line currents and star connected resistors for the same power . . . . .	95
Exa 3.7	Reduction in load when one resistor is removed . . . . .	97
Exa 3.8	To measure power by two wattmeter method . . . . .	98
Exa 3.9	To find power using two wattmeter method of a circuit with non reactive resistances . . . . .	99
Exa 3.10	Two wattmeter power dertermimation for a delta system	101
Exa 4.1	Torque on the coil at a current of 1mA . . . . .	103
Exa 4.2	To find the deflection produced by 200V . . . . .	104
Exa 4.3	Reading on ammeters when their shunts are interchanged	104
Exa 4.4	To create an instrument that measures voltages and currents upto a rated value . . . . .	105
Exa 4.5	To determine the range and current and deflection at various conditions . . . . .	106
Exa 4.6	Error calculation . . . . .	107
Exa 4.7	Dynamometer wattmeter power calculation of the load	108
Exa 4.8	Percentage error calculation in a wattmeter . . . . .	109
Exa 5.1	To find flux density in the core and induced emf in the secondary winding . . . . .	110
Exa 5.2	To calculate the number of turns per limb on the high and low voltage sides . . . . .	111
Exa 5.3	To calculate resistance of primary in terms of secondary and vice versa . . . . .	112
Exa 5.4	Total resitance and total copper loss at full load . . . . .	113
Exa 5.5	Voltage regulation at a pf lagging . . . . .	114
Exa 5.6	Regulation at lagging leading and unity power factors	116
Exa 5.7	Calculate the circuit parameters of a transformer using OC and SC tests . . . . .	117
Exa 5.8	To calculate terminal voltage and current and efficiency	118
Exa 5.9	Regulation at full load pf lag . . . . .	120

Exa 5.10	Calculate efficiency on unity pf at different cases . . . . .	121
Exa 5.11	Calcualte efficiencies at various loads . . . . .	122
Exa 5.12	To determine all day efficiency . . . . .	123
Exa 5.13	Calculating Efficiency using Sumpner test . . . . .	124
Exa 5.14	To determine the ratio of weights of copper . . . . .	125
Exa 5.15	To find voltage ratio and output . . . . .	125
Exa 5.16	Determine primary and secondary voltages and current . . . . .	126
Exa 5.17	Equivalent resistance and leakage reactance wrt primary . . . . .	127
Exa 5.18	To determine Input current and voltage during SC test . . . . .	128
Exa 5.19	To determine the load for max efficiency at two power factors . . . . .	129
Exa 5.20	To determine the max regulation and the pf at which it occurs . . . . .	131
Exa 5.21	To calculate secondary terminal voltage and full load efficiency at unity pf . . . . .	132
Exa 6.1	To Determine the useful flux per pole . . . . .	136
Exa 6.2	Determine the EMF generated . . . . .	136
Exa 6.3	Determine the EMF generated in a wave winding . . . . .	137
Exa 6.4	Ratio of speeds of a generator and motor . . . . .	137
Exa 6.5	Calculate Load Current in a shunt generator . . . . .	138
Exa 6.6	Useful Flux per pole on no load shunt motor . . . . .	139
Exa 6.7	To find efficiency and useful torque . . . . .	139
Exa 6.8	Speed calculation of series motor . . . . .	140
Exa 6.9	Parameters calculated due to armature reaction . . . . .	141
Exa 6.10	Number of conductors of compensating winding . . . . .	142
Exa 6.11	Swinburne test on a dc shunt motor . . . . .	143
Exa 6.12	Speed of a belt driven shunt generator . . . . .	145
Exa 6.13	Voltage between feeder and bus bar in a series generator . . . . .	145
Exa 6.14	Induced EMF and Armature current in a long shunt compound generator . . . . .	146
Exa 6.15	Speed at 50A considering armature reaction of a shunt motor . . . . .	147
Exa 6.16	Speed of shunt motor taking 50kW input . . . . .	148
Exa 6.17	Useful torque and efficiency of a shunt motor . . . . .	149
Exa 6.18	Total torque developed in a 4 pole shunt motor . . . . .	150
Exa 6.19	EMF and copper losses of a Shunt Motor . . . . .	150
Exa 6.20	Current taken by a motor at 90 percent efficiency . . . . .	151
Exa 6.21	Rated torque calculation by resistance addition . . . . .	152

Exa 6.22	Efficiency at full load . . . . .	153
Exa 7.1	Power delivered to 3 phase synchronous motor . . . . .	155
Exa 7.2	New plant pf and percent decrease in line current . . . . .	156
Exa 7.3	kVAr rating of a synchronous condenser . . . . .	157
Exa 7.4	Calculate E per phase and Current and pf . . . . .	158
Exa 7.5	Voltage Regulation of a 3 Phase alternator . . . . .	159
Exa 7.6	Internal Voltage drop in an alternator . . . . .	160
Exa 8.1	Find the percentage slip and poles of the motor . . . . .	162
Exa 8.2	To calculate motor speed and its slip . . . . .	163
Exa 8.3	To Calculate Parameters of a 3 phase 4 pole induction machine . . . . .	163
Exa 8.4	Calculation of slip from losses . . . . .	165
Exa 8.5	apping of an auto transformer to limit current in squirrel cage motor . . . . .	166
Exa 8.6	To find the total mechanical power and rotor copper loss . . . . .	167
Exa 8.7	To determine the starting torque and current using different starters . . . . .	168
Exa 8.8	To actual rotor speed and the rotor frequency at 3 percent slip . . . . .	169
Exa 8.9	To determine the various parameters of a 3 phase 400V 6 poles Induction Motor . . . . .	170
Exa 8.10	To determine parameters of an 3 phase delta connected 4 pole induction motor . . . . .	171
Exa 8.11	Determine the shaft power of 6 pole Induction Motor . .	172
Exa 8.12	Motor parameters at a load power factor . . . . .	173
Exa 8.13	To determine the auto tranformer ratio and starting torque . . . . .	174
Exa 8.14	To determine the starting torque in terms of full load torque . . . . .	175
Exa 8.15	Stator input of 3 phase 4 pole induction motor . . . . .	175
Exa 8.16	Motor parameters of a 6 pole motor with 40 hp mechanical power . . . . .	176
Exa 8.17	To determine parameters of 4 pole induction motor considering circuit parameters . . . . .	177
Exa 8.18	Stator Current and pf and efficiency of a motor operating at rated slip . . . . .	179
Exa 10.1	Determine the additional load which can be supplied .	181

Exa 10.2	Pf at which the slow machine will work . . . . .	182
Exa 10.3	Determine the load and pf of the other machine . . . . .	182
Exa 10.4	Determine the value of a shunt capacitor . . . . .	183
Exa 10.5	Calculate the inductance of a choke to enable the lamp . . . . .	184
Exa 11.1	Determine the size of the conductor for power and lighting circuit . . . . .	186
Exa 11.2	Determine the size of the conductor at 25 m distance . . . . .	189
Exa 11.3	Size of conductor to be used for wiring a 10 kW 400V 3 Phase induction motor . . . . .	190
Exa 12.1	To Compute the number of electrons . . . . .	192
Exa 12.2	Computing the Average lighting current . . . . .	192
Exa 12.3	To Calculate the average voltage . . . . .	193
Exa 12.4	Calculating resistance . . . . .	193
Exa 12.5	Current Calculation using ohms law . . . . .	194
Exa 12.6	Determination of conductance in a short circuit . . . . .	194
Exa 12.7	Power Rating Calculation . . . . .	195
Exa 12.8	To calculate current ratings and maximum voltage of a rated resistor . . . . .	195
Exa 12.9	Determine the output power of the motor . . . . .	196
Exa 12.10	Calculation of Current and power dissipated in resistors connected in series . . . . .	197
Exa 12.11	To find the value of the unknown resistance in the series of resistances in a circuit . . . . .	198
Exa 12.12	To Compute the resistance when operating voltage is altered . . . . .	200
Exa 12.13	To Determine the voltage and branch currents in a circuit with resistors connected in parallel . . . . .	200
Exa 12.14	To determine resistances in parallel . . . . .	201
Exa 12.15	To determine the currents in parallel branches of a network . . . . .	202
Exa 12.16	To determine current through each resistor in series and parallel combinational circuit . . . . .	203
Exa 12.17	To calculate current in each branch of the given network . . . . .	204
Exa 12.18	To determine the current using loop analysis . . . . .	205
Exa 12.19	To calculate current in each branch using loop analysis . . . . .	207
Exa 12.20	To calculate current in each branch using loop analysis and point voltages in a given network . . . . .	208

Exa 12.21	To calculate current from a battery and pd across points A and B . . . . .	211
Exa 12.22	Determine Current through branch AB of the given network . . . . .	212
Exa 12.23	Determine the current in the branches of the network using nodal analysis . . . . .	213
Exa 12.24	To Calculate current in all branches of the network shown using nodal analysis . . . . .	214
Exa 13.1	Computing Induced EMF . . . . .	216
Exa 13.2	Computing Instantaneous Induced EMF . . . . .	217
Exa 13.3	EMF Induced between wing tips . . . . .	218
Exa 13.4	EMF generated due to a bar magnet . . . . .	218
Exa 13.5	EMF induced between two coils in a circular iron core . . . . .	219
Exa 13.6	Force on the conductor due to a uniform magentic field . . . . .	220
Exa 13.7	To determine force between single phase bus bars . . . . .	220
Exa 13.8	To Compute the Maximum Induced EMF . . . . .	221
Exa 13.9	Compute Inductance and EMF induced . . . . .	222
Exa 13.10	Change in Inductance . . . . .	222
Exa 13.11	Computation of Current . . . . .	223
Exa 13.12	To determine Mutual and Self Inductances . . . . .	223
Exa 13.13	Computation of Mutual and self inductance in coils . . . . .	224
Exa 13.14	EMF induced in coils parallel to each other . . . . .	225
Exa 13.15	To Compute the maximum flux set by an coil . . . . .	226
Exa 13.16	Compute Loss of energy . . . . .	227
Exa 13.17	Determining Hysteresis loss . . . . .	228
Exa 13.18	Compute the Loss per Kg at a particular frequency . . . . .	229
Exa 13.19	Theory Based Proof relation between self mutual inductances . . . . .	229

# List of Figures

5.1 To calculate secondary terminal voltage and full load efficiency at unity pf . . . . .	132
11.1 Determine the size of the conductor for power and lighting circuit . . . . .	187
11.2 Determine the size of the conductor at 25 m distance . . . . .	188
11.3 Size of conductor to be used for wiring a 10 kW 400V 3 Phase induction motor . . . . .	190

# Chapter 1

## AC Circuits

**Scilab code Exa 1.1** To calculate frequency and instantaneous voltage and time of a voltage wave

```
1 // To calculate frequency , instantaneous voltage and
   time of a voltage wave
2
3 clc;
4 clear;
5
6 // The volatage eqaution is v= 0.02 sin (4000t + 30(
   degrees));
7
8
9 Vm=0.02;
10
11 deff( 'a=vol(b)' , 'a=Vm*sind(((4000*b)*(180/%pi))+30) '
   ); // Function for voltage equation
12
13 t=320*(10^-6);
14
15 w=4000; // angular frequency
16
17 // General expression for voltage is given by V=Vm
```

```

        sin ()(2*pi*f*t)+theta)
18 // Comparing both the eqautions we get 2*pi*f=4000
19
20 f=w/(2*%pi);
21
22 v=vol(t);
23
24 // 360 degrees is equal to 1/f s.
25
26 //Refer the diagram with this code to understand
   better.
27 // 30 degrees is
28
29 t30=30/(f*360);
30
31 disp('Hz',f,'The frequency of the voltage wave =')
32 disp('V',v,'The instantaneous voltage at t= 320
   micro seconds =')
33
34 disp('s',t30,'The time represented by 30 degrees
   phase difference =')

```

---

**Scilab code Exa 1.2** To find the current and power

```

1 // To find the current and power
2
3 clc;
4 clear;
5
6 Z=10+20*%i;
7
8 V=120;
9
10 I=V/Z;
11

```

```

12 theta=atand(imag(I)/real(I));
13
14 P=V*abs(I)*cosd(theta);
15
16 disp('A',I,'The current flowing through the given
      impedance =')
17 disp('watt',P,'The real power delivered to the
      impedance =')

```

---

**Scilab code Exa 1.3** To find the current and power of a capacitive circuit

```

1 // To find the current and power of a capacitive
   circuit
2
3 clc;
4 clear;
5
6 Z=10-25*i;
7
8 V=15;
9
10 I=V/Z;
11
12 theta=atand(imag(I)/real(I));
13
14 Pr=V*abs(I)*cosd(theta);
15 Pq=V*abs(I)*sind(theta);
16
17 disp('A',I,'The current flowing through the given
      impedance =')
18 disp('watt',Pr,'The real power loss of the
      capacitive impedance =')
19 disp('Var',-Pq,'The reactive power of the capacitive
      circuit =')// Negative sign indicates power
      generated.

```

---

**Scilab code Exa 1.4** To find the frequency in the RLC Circuit at a phase angle of 45 degrees

```
1 // To find the frequency in the RLC Circuit at a
   phase angle of 45 degrees
2
3 clc;
4 clear;
5
6 R=100;
7 L=2;
8 C=20*(10^-6);
9
10 f1=poly([0 1], 'f1 ', 'c ');
11 f2=poly([0 1], 'f2 ', 'c ');
12 w1=2*pi*f1;
13 w2=2*pi*f2;
14
15 //To achieve a phase angle of 45 degrees , the
   difference between Xl and Xc should be equal to R
16
17 // We have two different situations
18
19 Xl1=L*w1;
20 Xc1=1/(w1*C);
21
22 Xl2=L*w2;
23 Xc2=1/(w2*C);
24
25 cs1=Xl1-Xc1-R;
26 cs2=Xc2-Xl2-R;
27
28 f1=roots(cs1(2));
29 f2=roots(cs2(2));
```

```

30
31 //To find the suitable roots and to differentiate
   between positive and negative roots.
32
33 a=sqrt(f1(1));
34 b=sqrt(f1(2));
35 c=sqrt(f2(1));
36 d=sqrt(f2(2));
37
38 if(imag(a))
39     f1=f1(2);
40 end
41
42 if(imag(b))
43     f1=f1(1);
44 end
45
46 if(imag(c))
47     f2=f2(2);
48 end
49
50 if(imag(d))
51     f2=f2(1);
52 end
53
54 disp('The frequencies at which the phase angle is 45
      degrees are')
55
56 disp('Hz ',f2,' f2 = ', 'Hz ',f1,' f1 = ')

```

---

**Scilab code Exa 1.5** To find the inductance of a choke to operate a 120V 500W lamp at 230V

```

1 // To find the inductance of a choke to operate a
   120V 500W lamp at 230V

```

```

2
3 clc;
4 clear;
5
6 V=120;
7 W=500;
8 Rl=(V^2)/W;
9 I=W/V; // Circuit Current
10
11 // Q of a choke means the ratio of its inductive
   reactance to its resistance
12
13 Q=2;
14 f=60;
15 w=2*pi*f;
16
17 Vs=230; // Supply Voltage
18
19 Xcir=230/I;
20
21 L=poly([0 1], 'L', 'c');
22
23 Xl=w*L;
24
25 Rc=Xl/2; // Q utilised
26
27 // total resistance
28
29 Rt=Rl+Rc;
30
31
32 ind=(Rt^2)+(Xl^2)-(Xcir^2); // Characteristic
   equation to find L
33
34 L=roots(ind);
35
36 disp(ind, 'The Characteristic equation to find L is ')
37

```

```

38 if(imag(sqrt(L(1))))
39     L=L(2);
40 else
41     L=L(1);
42 end
43
44
45 disp('H',L,'The inductance of the choke coil = ')

```

---

**Scilab code Exa 1.6** Determine the value of the circuit components

```

1 // Determine the value of the circuit components
2
3 clc;
4 clear;
5
6 Z=10-(30*%i);
7
8 f=1*(10^6);
9
10 Y=1/Z;
11
12 G=real(Y);
13 B=imag(Y);
14
15 // G= 1/R
16 // B= wC
17
18
19 w=2*%pi*f;
20
21 R=1/G;
22
23 C=B/(w);
24

```

```
25 cap=abs((10^9)*C)/(10^9);  
26  
27 disp('ohms',R,'The resistance of the circuit =')  
28 disp('nF',cap,'The capacitance of the circuit =')
```

---

**Scilab code Exa 1.7** To determine circuit impedance and current in a parallel connection of a resistor and capacitor

```
1 // To determine circuit impedance and current in a  
    parallel connection of a resistor and capacitor.  
2  
3 clc;  
4 clear;  
5  
6 R=4700;  
7 V=240;  
8 f=60;  
9 w=2*pi*f;  
10 C=2*(10^-6);  
11 Xc=-(1/(C*w))*%i; // Reactance in polar form  
12  
13 Ir=V/R;  
14 Ic=V/Xc;  
15  
16 I=Ir+Ic; // Total current  
17  
18 Z=V/I;  
19  
20 theta=atand(imag(Z)/real(Z));  
21  
22 mprintf('Impedance of the circuit = %f / - %f ohms',  
          abs(Z),theta)
```

---

**Scilab code Exa 1.8** To find the current and impedance and admittance of the circuit

```
1 //To find the current and impedance and admittance
   of the circuit
2
3 clc;
4 clear;
5
6 R=25;
7 Xl=50*%i;
8 Z1=R+Xl;
9
10 Z2=-40*%i;
11
12 V=100;
13
14 Zeq=(Z1*Z2)/(Z1+Z2);
15
16 Y=1/Zeq;
17
18 I=V*Y;
19
20 mprintf('The Current of the circuit = %f /- %f A \n',
   ,abs(I),atand(imag(I)/real(I)))
21 mprintf('The Impedance of the circuit = %f /- %f
   ohms \n',abs(Zeq),atand(imag(Zeq)/real(Zeq)))
22 mprintf('The Admittance of the circuit = %f /- %f
   siemens \n',abs(Y),atand(imag(Y)/real(Y)))
```

---

**Scilab code Exa 1.9** Maximum current and frequency at which it occurs and respective voltages

```
1 // Maximum current and frequncy at which it occurs
   and respective voltages
```

```

2
3 clc;
4 clear;
5
6 R=5;
7 L=4*(10^-3);
8 C=0.1*(10^-6);
9 V=10;
10
11 w0=1/(sqrt(L*C));
12
13 Ir=V/R;
14
15 Vl=w0*L*Ir;
16
17 Vc=Ir/(w0*C);
18
19 mprintf('The Maximum Current at resonance = %f A \n'
           ,Ir)
20 mprintf('The frequency for resonance = %f rad/sec \n'
           ,w0)
21 mprintf('The voltage magnitude across the inductor =
           %f V \n',Vl)
22 mprintf('The voltage magnitude across the capacitor
           = %f V \n',Vc)

```

---

### Scilab code Exa 1.10 RLC circuit problems on resonace

```

1 // RLC circuit problems on resonace
2
3 clc;
4 clear;
5
6 R=6.28;
7 L=20*(10^-3);

```

```

8 f=5*(10^3) ;
9
10 w=2*pi*f ;
11
12 C=1/(L*(w^2)) ;
13
14 Xc=1/(w*C) ;
15 Xl=L*w ;
16
17 Vc=5 ;
18
19 Z=Xc+R+Xl ;
20
21 I=Vc/Xc // Total current
22
23 V=I*R ;
24
25 // frequency is inversely proportional to square
   root of capacitance
26 // So if C is halved; f will increase square root of
   2 times more.
27
28 fn=sqrt(2)*f ;
29
30 Xln=2*pi*fn*L ;
31
32 Q=Xln/R ;
33
34 //Note under resonance conditions Vl and Vc are much
   greater than the supply voltage .
35
36 mprintf('i) The value of capacitor = %f micro F \n',
   ,(10^6)*C)
37 mprintf('ii) The supply voltage = %f V \n',V)
38 mprintf('iii) The frequency of resonance when C is
   halved = %f Hz \n',fn)
39 mprintf('      The Q of the new circuit = %f \n',Q)

```

---

### Scilab code Exa 1.11 RLC circuit problems with quality factor

```
1 // RLC circuit problems with quality factor
2
3 clc;
4 clear;
5
6 C=320*(10^-12);
7 Q=50;
8 f0=175*(10^3);
9 w0=2*pi*f0;
10
11 L=1/(C*(w0^2));
12
13 R=w0*L/Q;
14
15 Xc=1/(C*w0);
16 Xl=L*w0;
17
18 V=0.85;
19
20 I=V/R;
21
22 Vc=I*Xc;
23
24 bw=f0/Q;
25
26 mprintf('The inductance for resonance =%f m H \n',
27 ,(10^3)*L);
28 mprintf('The current flowing in the circuit at
29 resonance =%f m A \n',(10^3)*I);
30 mprintf('The voltage across the capacitor at
31 resonance =%f V \n',Vc);
32 mprintf('The bandwidth of the circuit =%f Hz \n',bw)
```

;

---

**Scilab code Exa 1.12** RLC circuit problem to find the resonance frequency and impedance magnitude

```
1 // RLC circuit problem to find the resonance
   frequency and impedance magnitude
2
3 clc;
4 clear;
5
6 R=10;
7 L=100*(10^-3);
8 C=0.01*(10^-6);
9
10 f0=1/((2*pi)*(sqrt(L*C)));
11 // New frequencies according to the problem
   statement
12 f1=f0-1000;
13 f2=f0+1000;
14
15 w1=2*pi*f1;
16 w2=2*pi*f2;
17
18 Xl1=w1*L;
19 Xc1=1/(w1*C);
20
21 Xl2=w2*L;
22 Xc2=1/(C*w2);
23
24 Z1=sqrt((R^2)+((Xl1-Xc1)^2));
25 Z2=sqrt((R^2)+((Xl2-Xc2)^2));
26
27 mprintf('The Impedance magnitude at 1KHz below
   resonance (Capacitive) =%f ohms \n',Z1)
```

```
28 mprintf('The Impedance magnitude at 1KHz above  
resonance (Inductive) =%f ohms \n',Z2)
```

---

**Scilab code Exa 1.13** Series Resonace of a RLC circuit with 2 coils

```
1 // Series Resonace of a RLC circuit with 2 coils.  
2  
3 clc;  
4 clear;  
5  
6 R1=0.5;  
7 R2=1.5;  
8 R3=0.5;  
9 C1=6*(10^-6);  
10 C2=12*(10^-6);  
11 L1=25*(10^-3);  
12 L2=15*(10^-3);  
13  
14 // Both the coils are connected in series  
15  
16 Req=R1+R2+R3;  
17  
18 Leq=L1+L2;  
19  
20 Ceq=(C1*C2)/(C1+C2);  
21  
22 f=1/((2*pi)*sqrt(Leq*Ceq));  
23  
24 Q=2*pi*f*Leq/Req;  
25  
26 Q1=2*pi*f*L1/(R1+R3);  
27 Q2=2*pi*f*L2/R2;  
28  
29 mprintf('i) The frequency of resonance = %f Hz or Wo  
= %f rad/sec \n',f,2*pi*f)
```

```

30 mprintf('ii) Q of the circuit = %f \n',Q)// The
      total resistance should be considered , Error in
      the textbook
31 mprintf('iii) Q of coil 1 is %f and Q of coil 2 is
      %f \n',Q1,Q2)

```

---

**Scilab code Exa 1.14** Series Resonance in RLC circuit to find inductance and power

```

1 // Series Resonance in RLC circuit to find inductance
      and power
2
3 clc;
4 clear;
5
6 R=5;
7 C=50*(10^-6);
8 f0=100;
9 w=2*pi*f0;
10
11 L=1/(C*(w^2));
12
13 V=200;
14 Xc=1/(C*w);
15 Xl=L*w;
16
17 I=V/R;
18
19 P=(I^2)*R;
20
21 Vc=I*Xc;
22
23 Zc=R+(Xl*%i);
24
25 Vz=I*(Zc);

```

```

26
27 Q0=X1/R;
28
29 bw=f0/Q0;
30
31 printf('a) The inductance of the coil = %f mH \n',
32     ,(10^3)*L)
32 printf('b) The power delivered to the coil = %f kW \
33 n',(10^-3)*P)
33 printf('c) The voltage magnitude across the
34 capacitor = %f V \n The voltage magnitude of the
34 coil = %f V \n',Vc,abs(Vz)) // Magnitudes with at
34 most accuracy
34 printf('d) The bandwidth of the circuit = %f \n',bw)

```

---

**Scilab code Exa 1.15** Determine the current in parallel branches and supply current

```

1 //Determine the current in parallel branches and
   supply current
2
3 clc;
4 clear;
5
6 Xl=%i*100; // Inductance
7 R=10; // Resistance
8 V=10;
9 Xco=-%i*100;
10
11 Q=abs(Xl)/R;
12
13 Z0=Q*abs(Xco);
14 I0=V/Z0;
15
16 Ic=V/Xco;

```

```

17 I1=V/X1;
18
19 Pi=V*I0; // Power Input
20
21 Pc=(I0^2)*10; // Copper Loss
22
23 // Frequency reduced to fo/2
24
25 X11=X1/2; // New Inductive reactance at half the
               initial frequency
26 Xco1=Xco*2; // New Capacitative reactance at half
                 the initial frequency
27
28 Z1=R+X11; // Net impedance of the branch containing
               Resistance and inductor
29
30 Znet= Z1*Xco1/(Xco1+Z1); // Net Impedance of the
               circuit
31
32 I1=V/Znet; // Net Current for reduced frequency
33
34 ti1=atand(imag(I1)/real(I1)); // Phase Angle
35
36 // Frequency increased to 2fo
37
38 X12=2*X1; // New Inductive reactance at double the
               initial frequency
39 Xco2=Xco/2; // New Capacitative reactance at double
                 the initial frequency
40 Z2=R+X12; // Net impedance of the branch containing
               resistance and inductor
41
42 Zt=Z2*Xco2/(Z2+Xco2); // Net Impedance of the circuit
43
44 I2=V/Zt; // Net Current
45
46 ti2=atand(imag(I2)/real(I2));
47

```

```

48 printf('a) The Current flowing in the inductor =')
49 disp('mA',I1*1000)
50 printf(' The current flowing in the capacitor =')
51 disp('mA',Ic*1000)
52 printf(' The supply current = %g mA\n \n',I0
      *1000)
53 printf('b) The current for half the intial
      frequency = %g/_%g mA\n',abs(I1)*1000,ti1)
54 printf(' The current for double the intial
      frequency = %g/_%g mA\n',abs(I2)*1000,ti2)

```

---

**Scilab code Exa 1.16** Determine the original and loaded circuit bandwidth

```

1 // Determine the original and loaded circuit
   bandwidth
2
3 clc;
4 clear;
5
6 f0=1000*(10^3);
7 V=5;
8 Q=50;
9 Xl=2*(10^3);
10 Xc0=2*(10^3);
11 R1=40*(10^3); // Branch near the source
12 R2=Q*Xl; // Branch with both the inductor and
   resistance
13
14 Z0=Q*Xc0;
15
16 bw=f0/Q; // Original Bandwidth
17
18 // Considering loading resistance
19
20 Reff= R1*R2/(R1+R2);

```

```

21 Qd=Reff/Xc0;
22
23 bw1=f0/Qd; // Bandwidth with loading resistance
24
25 printf('The original bandwidth = %g kHz\n',bw/1000)
26 printf('The loaded circuit bandwidth = %g kHz\n',bw1
    /1000)

```

---

**Scilab code Exa 1.17** Expression for the sum of energy stored by inductor and capacitor connected in series at resonance

```

1 // Expression for the sum of energy stored by
   inductor and capacitor connected in series at
   resonance
2
3 clc;
4 clear;
5
6 printf(' i= Im*cos(w0)*t\n')
7 printf(' The energy stored is L*(i^2)/2 = L*(Im^2)*(
      cos(w0*t)^2) \n\n')
8
9 printf(' The energy stored in the capacitor (q^2)/2C
      = 1/2C * (Im^2)*[integration of i wrt dt from 0
      to t]^2 \n')
10 printf('           = 1/2C * (Im^2) *[integration
      of cos(w0*t) wrt dt from 0 to t]^2\n')
11 printf('           = 1/2C * (Im^2) *[ (sin(w0*t)/w0
      ) limits 0 to t]^2\n')
12 printf('           = (Im^2)/2 * L * (sin(w0*t)^2)\n
      n\n')
13 printf('Therefore total energy = L*(Im^2)/2 * [ (cos(
      w0*t)^2)+(sin(w0*t)^2)]\n')
14 printf('           = (Im^2)*L/2\n')
15 printf('           = L*(I^2)\n')

```

---

**Scilab code Exa 1.18** Expression for the sum of energy stored by inductor and capacitor connected in parallel at resonance

```
1 // Expression for the sum of energy stored by
   inductor and capacitor connected in parallel at
   resonance
2
3 clc;
4 clear;
5
6 printf('v = Vm * cos(w0*t)\n')
7 printf('The energy stored by the capacitor = C*(Vm
   ^2)*(cos(w0*t)^2)\n')
8 printf('The energy stored by the inductor = L*(i^2)
   /2\n')
9 printf('v = L *(di/dt)\n di = v*dt/L\n (i^2) = [
   integration of (v/L) wrt dt from 0 to t]^2 \n')
10 printf('      = (Vm^2)/(L^2) * (sin(w0*t)^2)/(w0^2) =
   (Vm/L)^2 * (sin(w0*t)^2) * LC\n')
11 printf('      = (Vm^2)*C*(sin(w0*t)^2)/L \n')
12 printf(' Energy = L*(i^2)/2 = (Vm^2)*C*(sin(w0*t)^2)
   *L/(L*2)\n')
13 printf('      = C/2 * (Vm^2)*(sin(w0*t)^2)\n')
14 printf(' Therefore total energy = C*(Vm^2)/2 = C*(V
   ^2)\n')
```

---

**Scilab code Exa 1.19** To determine bandwidth and half power frequencies

```
1 // To determine bandwidth and half power frequencies
2
3 clc;
```

```

4 clear;
5
6 R=50;
7 f=750; // Frequency
8 w0=(2*pi*f);
9 L=10*(10^-3);
10 I=1; // Maximum Current
11
12 Q=w0*L/R;
13
14 bw=f/Q;
15
16 a=(f^2); // let a = f1*f2
17 b= bw; // let b = f2-f1
18 c=sqrt((b^2)+(4*a)); // let c = f2+f1
19
20 f2=(b+c)/2;
21 f1=(c-b)/2;
22
23 printf('The bandwidth = %g Hz\n',bw)
24 printf('The half frequencies are f1 = %g Hz and f2 =
    %g Hz\n',f1,f2)

```

---

**Scilab code Exa 1.20** Determine the frequency of resonance and Max value of  $R_c$  at resonance

```

1 // Determine the frequency of resonance and Max
   value of  $R_c$  at resonance
2
3 clc;
4 clear;
5
6 Rl=6;
7 L=1*(10^-3);
8 Rc=4;

```

```

9 C=20*(10^-6);
10
11 w0=(1/(sqrt(L*C)))*(sqrt(((Rl^2)-(L/C))/((Rc^2)-(L/C
    ))));
12
13 Rcm=abs(sqrt(L/C));
14
15 printf(' The frequency of resonance = %g rad/sec\n',w0)
16 printf(' The Maximum value of Rc = %g ohms \n',Rcm)

```

---

**Scilab code Exa 1.21** To determine Rl for which resonance can take place

```

1 // To determine Rl for which resonance can take
   place
2
3 clc;
4 clear;
5
6 Rl=poly(0,'Rl');
7 Rc=5;
8 Xc=6;
9 Xl=15;
10
11 x=((Rl^2)+(Xl^2))*Xc-((Rc^2)+(Xc^2))*Xl;
12
13 Rl=roots(x);
14
15 disp(x)
16
17 printf('The above eqaution must be eqauted to zero
      to get Rl \n')
18
19 disp(Rl)

```

```
20
21 printf('The above eqaution leads to imaginary roots
      which is not possible , hence no value of Rl can
      bring resonance in the circuit at the given
      condition \n' )
```

---

**Scilab code Exa 1.22** To find the resistor for a given Q factor

```
1 //To find the resistor for a given Q factor
2
3 clc;
4 clear;
5
6 f0=600*(10^3);
7 bw=50*(10^3); // Bandwidth
8
9 L=1.3*(10^-3); // Inductance
10
11 Q=30;
12
13 Xl=2*pi*f0*L; // Inductive Reactance
14
15 Xco=Xl; // At resonance Xl= Xco
16
17 Zto=Q*Xco;
18
19 Qd=f0/bw; // Required Q for the circuit
20
21 Zdto= Qd*Xco; // The equivalent input resistance
      required
22
23 Rd=poly(0, 'Rd');
24
25 x=(Zdto*(Zto+Rd))-(Zto*Rd); // Characteristic
      equation to the shunt resistance
```

```

26
27 Rd=roots(x); // Shunt resistance
28
29 printf('The resistance that is to be connected
           across the coil = %g k ohms\n',Rd/1000)

```

---

**Scilab code Exa 1.23** Find the flux density

```

1 //Find the flux density
2
3 clc;
4 clear;
5
6 l=50*(10^-2); // Mean length
7 m0=4*pi*(10^-7); // Constant (Permeability of air)
8 ag=1*(10^-3); // Air Gap
9 mr=300; // Relative permeability
10 N=200; // No of turns
11 I=1; // Current
12 A=poly(0,'A');// Area
13
14 Rel=l/(m0*mr*A); //Reluctance of the substance
15
16 Relag=ag/(m0*A); // Air gap reluctance
17
18 MMF=N*I;
19
20 Relt=Rel+Relag; // Total reluctance
21
22 phi=MMF/Relt;//Flux
23
24 B=phi/A;
25
26 // To get the numerical value of the flux density as
   the polynomial denominator doesn't divide

```

```

27
28 x=B(2)-A;
29 x=roots(x);
30
31 y=B(3)-A;
32 y=roots(y);
33
34 B=x/y;
35
36 printf('The flux density = %g mWb/(m^2)\n',B*1000)

```

---

**Scilab code Exa 1.24** Find the number of ampere turns

```

1 //Find the number of ampere turns
2
3 clc;
4 clear;
5
6 l=30*(10^-2); // Length of an iron path
7 lag=2*(10^-3); //Length of air gap
8 B=0.8; // Flux density
9 H=700;
10 m0=(4*pi)*(10^-7);
11 mr=B/(m0*H);
12
13 A=poly(0,'A');//Area of the iron path
14
15 R1=l/(m0*mr*A);
16 R2=lag/(m0*A);
17 R=R1+R2;
18
19 phi=B*A;//Flux
20
21 NI=phi*R;
22

```

```

23 //To find numerical value
24 y=NI-A;
25
26 NI=roots(y(2));
27
28 //The answer in the textbook contains Round off
   error
29 printf('The number of turns necessary to produce a
   flux density of 0.8T in the air gap = %g AT\n',NI)

```

---

**Scilab code Exa 1.25** To find current in the 600 turn exciting coil

```

1 //To find current in the 600 turn exciting coil
2
3 clc;
4 clear;
5
6 N=600;
7 mr=800;
8 m0=4*pi*(10^-7);
9
10 phi=100*(10^-6); // Flux in air gap
11
12 l1=10*(10^-2);
13 l2=18*(10^-2);
14 lg=2*(10^-3); // Air gap length
15 Ac=(6.25)*(10^-4); // Central limb area
16 As=3*(10^-4); // Side limb area
17
18 Ra=lg/(m0*Ac);
19 Ri=l1/(mr*m0*Ac);
20
21 R=l2/(m0*mr*As);
22

```

```

23 Rt=Ra+Ri; // Total reluctance of the central limb
24
25 AT1=Rt*phi; // MMF or Ampere turns for the central
   limb
26 AT2=R*phi/2; // MMF, Two identical limbs hence flux
   becomes half and only one limb is considered
27
28 AT=AT1+AT2; // Total MMF
29
30 I=AT/N; // Current in the 600 turns
31
32 printf('The current flowing in the 600 turns
   exciting coil = %g A\n',I)

```

---

**Scilab code Exa 1.26** Find the current required to develop a flux of given mWb

```

1 // Find the current required to develop a flux of
   1.6 mWb
2
3 clc;
4 clear;
5
6 B=1;
7 H=900;
8 m0=4*pi*(10^-7);
9 mr=B/(m0*H);
10
11 //lengths
12 lg=1*(10^-3); // Air gap
13 lc=24*(10^-2); // Central Limb
14 la=60*(10^-2); // Side limbs
15
16 //area
17 A=4*4*(10^-4);

```

```

18
19 phi=1.6*(10^-3); // Flux
20
21 //Reluctances
22 Ra=lg/(m0*A); // Air gap
23 Rc=lc/(m0*mr*A); // Central limb
24 Rs=la/(m0*mr*A); // One side limbs
25
26 //mmf
27 AT1=(Ra+Rc)*phi; // Central limb
28 AT2=Rs*phi/2; // One of the side limb
29 AT=AT1+AT2; // Total
30
31 N=680; //Turns
32
33 I=AT/N;
34
35 printf('The current the current required to produce
           a total flux of 1.6 mWb = %g A\n',I)

```

---

**Scilab code Exa 1.27** Determine the inductance of individual winding

```

1 //Determine the inductance of individual winding
2
3 clc;
4 clear;
5
6 La=15; // Self inductance of first coil
7 Lb=16; // Self inductance of second coil
8 M=-8; // Since the flux from both coils oppose each
          other
9
10 L1=La+M;
11 L2=Lb+M;
12

```

```
13 L=L1*L2/(L1+L2);
14
15 printf('The inductance of the individual windings
      are %g H and %g H respectively.\n',L1,L2)
16 printf('The equivalent inductance between the
      terminals is %g H\n',L)
```

---

**Scilab code Exa 1.28** Determine the inductance of a three coil system

```
1 //Determine the inductance of a three coil system
2
3 clc;
4 clear;
5 //Self inductances of A B C
6 L1=25;
7 L2=30;
8 L3=35;
9
10 //Mutual inductances of AB BC CA
11 M12=10; //Flux assist each other
12 M23=-15; //Flux oppose each other
13 M31=-10; //Flux oppose each other
14
15 La=L1+M12+M31;
16 Lb=L2+M12+M23;
17 Lc=L3+M31+M23;
18
19 Leq=1/(((La*Lb)+(Lb*Lc)+(Lc*La))/(La*Lb*Lc));
20
21 printf('The equivalent inductance for a three coil
      system = %g H\n',Leq)
```

---

**Scilab code Exa 1.29** To determine the parameters of an alternating current of 50Hz frequency

```
1 // To determine the parameters of an alternating
   current of 50Hz frequency
2
3 clc;
4 clear;
5
6 f=50;
7 Im=20;
8 w=2*pi*f;
9 t=1/100;
10 It=10;
11 Irms=Im/(sqrt(2));
12 Iav=0; //Full Cycle
13 t10=asin(It/Im)/w; // time taken to rach 10A
14
15 Ih=Im*sin(w*t); // Current at 1/100 sec
16
17 printf('i) The general ecpresion is i(t) = %g sin
   %gt\n',Im,w)
18 printf('ii) The instantaneous value at t= 1/100 sec
   is %g A\n',floor(Ih*10)/10)
19 printf('iii) The time taken to reach 10A for the
   first time = %g s\n',t10)
20 printf('iv) The average and the rms value of current
   is %g A and %g A respectively\n',Iav,Irms)
```

---

**Scilab code Exa 1.30** Determine the resultant current for two alternating currents

```
1 //Determine the resultant current for two
   alternating currents
2
```

```

3  clc;
4  clear;
5
6  ti1=30;
7  ti2=45;
8
9  i1=20*(expm(%i*pi/6));
10 i2=40*(expm(%i*pi/4));
11
12 i=i1+i2;
13
14 ti=atand(imag(i)/real(i));
15
16 printf('The resultant current = %g sin(314t + %g(
    degrees)) A\n',abs(i),ti)
17 printf('           Or %g/-%g A\n',abs(i),ti)

```

---

**Scilab code Exa 1.31** To determine the sum and difference of two alternating voltage sources

```

1 //To determine the sum and difference of two
   alternating voltage sources
2
3 clc;
4 clear;
5
6 //Phase angles
7 tv1=0;
8 tv2=-%pi/6;
9
10 //Taking v1 as reference voltage
11 v1=110*(expm(%i*tv1));
12 v2=80*(expm(%i*tv2));
13
14 Vs=v1+v2; //Sum

```

```

15 Vd=v1-v2; // Difference
16
17 ts=atand(imag(Vs)/real(Vs));
18 td=atand(imag(Vd)/real(Vd));
19
20 printf('i) The sum = %g sin(wt + (%g(degrees))) V\n',
21 ,abs(Vs),ts)
21 printf('i) The difference = %g sin(wt + (%g(degrees)
22 )) V\n',abs(Vd),td)

```

---

**Scilab code Exa 1.32** Determine the parameters of the circuit and power and pf

```

1 // Determine the parameters of the circuit and power
2 // and pf
3 clc;
4 clear;
5
6 tv=30; //Phase angle for voltage
7 ti=-30; // Phase angle for current
8 t=tv-ti; //Phase difference between v and i
9
10 //Keeping i as reference , Voltage leads current by t
11 // angle
12 i=10*(expm(%i*0));
13 v=230*(expm(%i*%pi*t/180));
14
15 z=v/i;
16
17 R=real(z);
18 X=imag(z);
19
20 P=abs(v)*abs(i)*cosd(t)/2; // rms values of voltage

```

```

        and current
21
22 printf('The circuit parameters are \n')
23 printf('Resistance = %g ohms\nReactance = %g ohms\n\
24 n',R,X)
25 printf('The Power consumed = %g W\n',P)
26 printf('p.f of the circuit = %g\n',cosd(t))

```

---

**Scilab code Exa 1.33** Determine circuit paramters of an iron coil

```

1 //Determine circuit paramters of an iron coil
2
3 clc;
4 clear;
5
6 f=50; // Frequency
7 Vdc=40; //DC Voltage source
8 Idc=5; // Current drawn from DC Voltage source
9 Vac=200; // AC Voltage Source
10 Iac=5; // Current drawn form AC Voltage source
11 P=500; // Power Consumed by ac supply
12
13 R=Vdc/Idc; // Resistance of the coil
14 Z=Vac/Iac; // Impedance of the coil
15
16 Pc=(Iac^2)*R; //Power loss in ohmic resistance
17
18 Pil=P-Pc; // Iron loss
19
20 Reff=P/(Iac^2); // Effective resistance of the coil
21
22 Xl=sqrt((Z^2)-(Reff^2)); // Reactance of the coil
23
24 L=Xl/(2*pi*f); // Inductance of the coil
25

```

```
26 pf=P/(Vac*Iac);
27
28 printf('i) The impedance = %g ohms\n',Z)
29 printf('ii) The iron loss = %g W\n',Pil)
30 printf('iii) The inductance of the coil = %g H\n',L)
31 printf('iv) p.f of the coil = %g\n',pf)
```

---

**Scilab code Exa 1.34** Determine the phase angle between 220V main and the current

```
1 //Determine the phase angle between 220V main and
   the current
2
3 clc;
4 clear;
5
6 f=50; //Frequency of AC Mains
7 Vni=100; //Voltage for non inductive load
8 Ini=10; // Current drawn by a non inductive load
9 Rni=Vni/Ini; // Resistance of an non inductive load
10 Vac=220; // Supply from AC Mains
11
12 Z=Vac/Ini;
13
14 X=sqrt((Z^2)-(Rni^2));
15
16 phi=atand(X/Rni); // Phase Angle
17
18 L=X/(2*pi*f); //Inductance
19
20 printf('The inductance of a reactor to be connected
      in series = %g H\n',L)
21 printf('The phase angle between the 220V mains and
      the current = %g degrees\n',phi)
```

---

**Scilab code Exa 1.35** To determine the coil parameters with resistance of 5 ohms

```
1 //To determine the coil parameters with resistance
   of 5 ohms
2
3 clc;
4 clear;
5 //Parameters of the coil
6 R=5; // Resistance
7 I=10; // Current flowing
8 V=200; // Voltage across
9 f=50; // Frequency of operation
10 P=750; //Total Power Dissipated
11
12 Pc=(I^2)*R; // Copper Loss
13 Pil=P-Pc; // Iron Loss
14
15 Z=V/I; // Impedance
16
17 X=sqrt((Z^2)-(R^2)); //Reactance
18
19 L=X/(2*pi*f); // Inductance
20
21 pf=P/(V*I); // Power Factor
22
23 printf('i The iron loss = %g W\n',Pil)
24 printf('ii ) The inductance at the given value of
   current = %g H\n',L)
25 printf('iii ) p.f = %g\n',pf)
```

---

**Scilab code Exa 1.36** Determine the resonant frequency and the source current

```
1 // Determine the resonant frequency and the source
   current
2
3 clc;
4 clear;
5
6 L=0.24; // Inductance
7 Rl=150;
8 Rc=100;
9 C=3*(10^-6); // Capacitance
10 f=50;
11 w=2*pi*f;
12 V=200; // Source voltage
13
14 fs=1/(2*pi*sqrt(L*C)); // Frequency at the time of
   series connection
15
16 f0=fs*sqrt(((Rl^2)-(L/C))/((Rc^2)-(L/C))) // Resonant
   frequency
17
18 //Taking voltage as the reference
19
20 Xl=L*w; // Inductive reactance
21 Xc=1/(C*w); // Capacitive reactance
22
23 Ra=Rl+(%i*Xl); // Effective resistance of inductive
   branch
24 Rb=Rc-(%i*Xc); // Effective resistance of capacitive
   branch
25
26 Reff=Ra*Rb/(Ra+Rb); // Effective Resistance
27 Tr=atand(imag(Reff)/real(Reff)); // Phase Angle
28
29 I=V/Reff; // Source current
30 Ti=atand(imag(I)/real(I)) // Phase angle
```

```

31
32 printf('The resonant frequency = %g Hz\n',f0)
33 printf('The source current = %g/%g A\n',abs(I),Ti)
34 printf('The input impedance = %g/%g ohms\n',abs(
    Reff),Tr)

```

---

**Scilab code Exa 1.37** Determine Circuit parameters for a circuit with a current source

```

1 // Determine Circuit parameters for a circuit with a
   current source
2
3 clc;
4 clear;
5
6 I=2.5*(10^-3); // Current Source
7 R=100; // Resistance of the coil
8 L=1*(10^-3); // Inductance of the coil
9 fr=600*(10^3); // Resonance frequency
10 R2=60*(10^3); // Resistance in parallel with the
    coil
11 wr=2*pi*fr; // Angular Resonance frequency
12
13 Q=wr*L/R; // For the coil
14
15 C=1/((wr^2)*L); // Capacitance in the circuit
16 Xc0=1/(wr*C);
17
18 Recc=Q*Xc0; // Equivalent resistance of coil and
    capacitor
19
20 Req=R*Recc/(R+Recc); // Equivalent resistance of the
    circuit
21
22 Qcir=wr*Req*C; // For the circuit

```

```

23
24 bw=fr/Qcir; // Bandwidth of the circuit
25
26 v=I*Req;
27
28 MaxE=C*(v^2); // Maximum energy stored by the
                  capacitor
29
30 Pdr=(I^2)*Req; // Power dissipated in the resistor
31
32
33 // Textbook calculation for Equivalent resistance of
      C and Coil is wrong
34
35 printf('a) Q of the coil = %g\n',Q)
36 printf('b) Capacitance C = %g pF\n',C*(10^12))
37 printf('c) Q of the circuit = %g\n',Qcir)
38 printf('d) Bandwidth of the circuit = %g kHz\n',bw
      /1000)
39 printf('e) Maximum Energy stored in the capacitor =
      %g pJ\n',MaxE*(10^12))
40 printf('f) Power Dissipated in the resistor = %g mW\
      n',Pdr*1000)

```

---

**Scilab code Exa 1.38** Determine the instantaneous energy stored in the capacitor and inductor

```

1 // Determine the instantaneous energy stored in the
   capacitor and inductor
2
3 clc;
4 clear;
5
6 Vc=20*sqrt(2);
7 C=2; // Capacitor

```

```

8 L=1; // Inductor
9 w=poly(0, 'w');
10
11 // Impedances in order from left to right (as a
   function of w)
12 R1=%i*w;
13 R2=1/(2*%i*w); // Top
14 R3=1; // Bottom
15
16 Rp=R2*R3/(R2+R3); // Effective resistance of the
   parallel path
17
18 Reff=R1+Rp; // Effective resistance
19
20 Reff(2)=Reff(2)*conj(Reff(3));
21 Reff(3)=Reff(3)*conj(Reff(3));
22
23 R=imag(Reff(2))/Reff(3); // Imaginary part of the
   above equation
24
25 //From the above equation we get five roots , three
   are zero and we take the positive value
26 w=roots(R(2));
27 w=abs(w(2)); // Numerical Value
28
29 // Impedances in order from left to right (Numerical
   Value)
30 R1=%i*w;
31 R2=1/(2*%i*w); // Top
32 R3=1; // Bottom
33
34 Vcrms=Vc/sqrt(2);
35
36 // Taking Vc as reference
37
38 Ic=Vcrms/R2; // Current through Capacitor
39 Ir=Vcrms/R3; // Current through Resistor
40

```

```

41 I1=Ic+Ir; // Rms value of Current through Inductor
42 t1=atand(imag(I1)/real(I1)); // Phase angle of
    Inductor Current
43
44 I1max=abs(I1)*sqrt(2); // Maximum Current
45
46 Einst=C*(Vc^2)/2; // Magnitude of Instantaneous energy
    stored
47
48 Ein=L*(abs(I1max)^2)/2; // Energy through the
    inductor
49 Er=(Ir^2)*R3; // Loss in the resistor
50
51 Q0= w*Ein*(1+(1/sqrt(2)))/Er; // Q of the circuit
52
53 printf('a) Instantaneous Energy Stored in Capacitor =
    %g (sin(%gt)^2) \n',Einst,w)
54 printf(' Instantaneous Energy Stored in Inductor =
    %g (sin( %gt + %g)^2) \n',Ein,w,t1)
55 printf('b) Q of the circuit = %g \n',Q0)

```

---

**Scilab code Exa 1.39** To determine the current through all the branches of the given network

```

1 //To determine the current through all the branches
    of the given network
2
3 clc;
4 clear;
5
6 L=1;
7 R=1*(10^3);
8 C=400*(10^-6);
9 i=2; // 2 cos 50t
10

```

```

11 w0=1/(sqrt(L*C));
12
13 v=i*R; // Voltage across the source
14
15 Xl=%i*w0*L; // Inductive reactance
16 Xc=-%i/(C*w0); // Capacitive reactance
17
18 I1=v/Xl; // Inductor current
19 Ic=v/Xc; // Capacitor Current
20
21 //Condition to check if angle is 90
22 if(real(I1)==0)
23     if(imag(I1)>0)
24         tl=atand(%inf);
25     else
26         tl=-1*atand(%inf);
27     end
28
29 else
30     tl=atand(imag(I1)/real(I1));
31 end
32
33 //Condition to check if angle is 90
34 if(real(Ic)==0)
35     if(imag(Ic)>0)
36         tc=atand(%inf);
37     else
38         tc=-1*atand(%inf);
39     end
40
41 else
42     tc=atand(imag(Ic)/real(Ic));
43 end
44
45 printf('The Current through the resistor is %g cos(
        %g)t A\n',i,w0)
46 printf('The Current through the inductor is %g cos(
        %gt + (%g)) A\n',abs(I1),w0,t1)

```

```
47 printf('The Current through the capacitor is %g cos( %gt + (%g)) A\n',abs(Ic),w0,tc)
```

---

**Scilab code Exa 1.40** To determine parameters to operate the relay

```
1 //To determine parameters to operate the relay
2
3 clc;
4 clear;
5
6 N=500; // No of turns
7 l=400*(10^-3); // Mean Core length
8 lg=1*(10^-3); // Air Gap length
9 B=0.8; // Flux density required to operate the relay
10 m0=4*pi*(10^-7); // permeability of free space
11 H=500; // Magentic Field Intensity
12
13 mmfc=H*l; // mmf for the core
14 mmfg=2*lg*B/(m0); // mmf of the air gap
15
16 tmmf=mmfc+mmfg; // Total mmf
17
18 Iop=tmmf/N; // Operating current for the relay
19
20 m=B/H; // Permeability
21
22 mr=m/m0; // Relative permeability
23
24 // When gap is zero
25
26 mmf=mmfc; // Total mmf required
27
28 I=mmf/N; // Current when the gap is zero
29
30 printf('i) The current required to operate the relay
```

```

= %g A\n',Iop)
31 printf('ii)Wrt the Core , The permeability = %g and
      Relative permeability = %g \n',m,Mr)
32 printf('iii) The current required when gap is zero =
      %g A \n',I)

```

---

**Scilab code Exa 1.41** To determine the parameters of a toroid

```

1 // To determine the parameters of a toroid
2
3 clc;
4 clear;
5
6 //Arc length of different materials
7 lni=0.3; // nickel iron alloy
8 lss=0.2;//Silicon Steel
9 lcs=0.1;//Cast steel
10
11 A=1*(10^-3); // Area of cross section of Toroid
12
13 N=100; // Hundred Turns
14
15 phi=6*(10^-4); // Flux
16 B=0.6; // Flux densities
17 m0=4*pi*(10^-7);
18
19 //Field intensities
20 Hni=10; // Ni alloy
21 Hss=77;// Si Steel
22 Hcs=270; // CAst steel
23
24 mmf=(Hni*lni)+(Hss*lss)+(Hcs*lcs); // Total mmf
25
26 B=phi/A;
27

```

```

28 I=mmf/N;
29
30 //P = Permeability , RP = Relative permeability
31
32 //For Nickel Alloy
33 mni=B/Hni; // P
34 mrni=mni/m0; // RP
35
36 //For Si Steel
37 mss=B/Hss; //P
38 mrss=mss/m0; // RP
39
40 //For Cast Steel
41 mcs=B/Hcs; //P
42 mrcts=mcs/m0; // RP
43
44 deff( 'x=rel(y,z)', 'x=(y*z)/phi'); // Function to
     find out Reluctance
45
46 //Reluctances
47 Rni=rel(Hni,lni);
48 Rss=rel(Hss,lss);
49 Rcs=rel(Hcs,lcs);
50
51 printf('i) The mmf required to establish a magnetic
      flux of 6 *(10^-4) Wb = %g AT\n',mmf)
52 printf('ii) The Current through the coil = %g A\n',I
      )
53 printf('iii) Relative permeability and reluctance of
      each ferro magnetic material\n')
54 printf('    Nickel Iron alloy is %g and %g ohms \n',
      mrni,Rni)
55 printf('    Silicon Steel is %g and %g ohms \n',mrss
      ,Rss)
56 printf('    Cast Steel is %g and %g ohms \n',mrcts,
      Rcs)

```

---

**Scilab code Exa 1.42** Determine the magnetic flux for a toriod

```
1 //Determine the magnetic flux for a toriod
2
3 clc;
4 clear;
5
6 //Arc length of different materials
7 lni=0.3; // nickel iron alloy
8 lss=0.2;//Silicon Steel
9 lcs=0.1;//Cast steel
10
11 //Field intensities
12 Hni=10; // Ni alloy
13 Hss=77; // Si Steel
14 Hcs=270; // Cast steel
15
16 con=6*(10^-4); // Gives Constant reluctances
17
18 deff( 'x=rel(y,z)' , 'x=(y*z)/con' ); // Function to
     find out Reluctance
19
20 //Reluctances
21 Rni=rel(Hni,lni); // Note that the textbook has a
     wrong value calculated for the nickel alloy
     reluctance
22 Rss=rel(Hss,lss);
23 Rcs=rel(Hcs,lcs);
24
25 mmf=35; // Applied mmf
26
27 phi=mmf/(Rni+Rss+Rcs); // Magnetic flux produced
28
29 printf('The approximate magnetic flux produced = %g
```

Wb\ n ', phi)

---

**Scilab code Exa 1.43** To determine the magnetic parameters of a steel ring

```
1 //To determine the magnetic parameters of a steel
   ring
2
3 clc;
4 clear;
5
6 d=30*(10^-2); // Mean diameter
7 m0=4*pi*(10^-7);
8 lg=1*(10^-3); //Air Gap length
9 r=(2*(10^-2))/2; // radius of the circular part of
   the air gap
10 Ag=%pi*r*r; // Area of the air gap
11 N=600; // No of turns
12 I=2.5; // Current
13
14 Ip=40/100; // Iron path usage
15 Agp=1-Ip; // Air gap usage
16
17 mmf=N*I;
18 mmfs=Ip*mmf; // mmf required for the steel
19 mmfg=Agp*mmf; // mmf required for the air gap
20
21 Rg=lg/(m0*Ag); // Reluctance of the air gap
22
23 phi=mmfg/Rg; // Flux through the gap
24
25 Rs=mmfs/phi; // Reluctance of steel
26 Rt=Rs+Rg; // Total reluctance
27 B=phi/Ag; // Flux density of air
28
```

```
29 printf('i) mmf of air gap and steel ring = %gAT and  
    %gAT\n',mmfg,mmfs)  
30 printf('ii) Magnetic flux = %g mWb\n',phi*1000)  
31 printf('iii) Reluctance = %g M ohms \n',Rt/(10^6))  
32 printf('iv) Flux density = %g T\n',B)
```

---

# Chapter 2

## Network Theory

**Scilab code Exa 2.1** To determine the current using loop analysis

```
1 // To determine the current using loop analysis
2
3 clc;
4 clear;
5
6 // MESH Equations
7 //6*i1 -2*i2=30
8 // -2*i1 +6*i2=-40
9
10 R=[6 -2;-2 6];
11 E=[30; -40];
12
13 //The Loop Currents
14
15 I=inv(R)*E; // Matrix Method to solve for two
               unknowns in two equations.
16
17 i1=I(1);
18 i2=I(2);
19 i3=i1-i2;
20
```

```

21 disp('A',i2,'i2 =', 'A',i1,'i1 =', 'The Calculated
      Loop Currents are')
22
23 disp('The Negative sign indicates that the assumed
      direction of flow of current should be reversed.
      ')
24
25 if(i1<0);
26     i1=abs(i1);
27 end
28
29 if(i2<0);
30     i2=abs(i2);
31 end
32
33 disp('A',i1,'The Current through 4 ohm resistor on
      the 30V side =')
34 disp('A',i2,'The Current through 4 ohm resistor on
      the 40V side =')
35 disp('A',i3,'The Current through 2 ohm resistor =')

```

---

**Scilab code Exa 2.2** To calculate current in each branch using loop analysis

```

1 // To calculate current in each branch using loop
   analysis .
2
3 clc;
4 clear;
5
6 // MESH Equations for the given network .
7 // 3*i1 - i2 + 0*i3 = 11
8 // -i1 + 10*i2 - 2*i3 = 0
9 // 0*i1 + -2*i2 + 5*i3 = 13
10

```

```

11 // Voltage supplies are 11V and 13V
12
13 R=[3 -1 0;-1 10 -2; 0 -2 5];
14 E=[11;0;13];
15
16 // Loop Currents
17
18 I=inv(R)*E;
19
20 i1=I(1);
21 i2=I(2);
22 i3=I(3);
23
24 ia=i1-i2; // Assumed direction from Mesh 1
25 ib=i2-i3; // Assumed direction from Mesh 2
26
27 disp('A',ib,'ib (through 2 resistor between 7 ohm
      and 3 ohm resistor) =','A',ia,'ia (through 1 ohm
      resistor) =','A',i3,'i3 =','A',i2,'i2 =','A',i1,
      'i1 =','The Calculated Loop Currents are')
28
29 disp('The Negative sign indicates that the assumed
      direction of flow of current should be reversed',
      )
30
31 // To obtain the magnitude of direction.
32
33 if(i1<0)
34     i1=abs(i1);
35 end
36 if(i2<0)
37     i2=abs(i2);
38 end
39 if(i3<0)
40     i3=abs(i3);
41 end
42 if(ia<0)
43     ia=abs(ia);

```

```

44 end
45 if(ib<0)
46     ib=abs(ib);
47 end
48
49 disp('A',i1,'The Current through 2 ohm resistor on
    the 11V side =')
50 disp('A',i2,'The Current through 7 ohm resistor =')
51 disp('A',i3,'The Current through 3 ohm resistor on
    the 13V side =')
52 disp('A',ia,'The Current through 1 ohm resistor =')
53 disp('A',ib,'The Current through 2 ohm resistor
    between the 7 and 3 ohm resistors =')

```

---

**Scilab code Exa 2.3** To calculate current in each branch using loop analysis and point voltages in a given network

```

1 // To calculate current in each branch using loop
    analysis and point voltages in a given network.
2
3 clc;
4 clear;
5
6 // MESH Equations for the given network.
7 // 3.95*i1 - 3.75*i2 + 0*i3 = 120
8 // -3.75*i1 + 9.5*i2 - 5.45*i3 = 0
9 // 0*i1 - 5.45*i2 + 5.55*i3 = -110
10
11 // Positive of 120V DC supply connected to 0.2 ohm
    resistor
12 // Positive of 110 DC supply connected to 0.1 ohm
    resistor
13
14 // Voltage supplies are 120V and 110V
15

```

```

16 R=[3.95 -3.75 0;-3.75 9.5 -5.45; 0 -5.45 5.55];
17 E=[120;0;-110];
18
19 R1=abs(R(2)); // Resistor carrying ia
20 R2=abs(R(8)); // Resistor carrying ib
21
22 // Loop Currents
23
24 I=inv(R)*E;
25
26 i1=I(1);
27 i2=I(2);
28 i3=I(3);
29
30 ia=i1-i2; // Assumed direction from Mesh 1
31 ib=i2-i3; // Assumed direction from Mesh 2
32
33 // Using Nodal Analysis to find V1 and V2.
34 V1=R1*ia;
35 V2=R2*ib;
36
37 disp('A',ib,'ib (through 2 resistor between 7 ohm
      and 3 ohm resistor) =', 'A',ia,'ia (through 1 ohm
      resistor) =', 'A',i3,'i3 =', 'A',i2,'i2 =', 'A',i1,
      'i1 =', 'The Calculated Loop Currents are')
38
39 disp('The Negative sign indicates that the assumed
      direction of flow of current should be reversed',
      )
40
41 // To obtain the magnitude of direction.
42
43 if(i1<0)
44     i1=abs(i1);
45 end
46 if(i2<0)
47     i2=abs(i2);
48 end

```

```

49 if(i3<0)
50     i3=abs(i3);
51 end
52 if(ia<0)
53     ia=abs(ia);
54 end
55 if(ib<0)
56     ib=abs(ib);
57 end
58
59 disp('A',i1,'The Current through 0.2 ohm resistor on
      the 120V side =')
60 disp('A',i2,'The Current through 0.3 ohm resistor ='
      )
61 disp('A',i3,'The Current through 0.1 ohm resistor on
      the 110V side =')
62 disp('A',ia,'The Current through 3.75 ohm resistor ='
      ')
63 disp('A',ib,'The Current through 5.45 ohm resistor ='
      ')
64
65 disp('V',V1,'The voltage V1 =')
66 disp('V',V2,'The voltage V2 =')

```

---

**Scilab code Exa 2.4** To calculate current from a battery and pd across points A and B

```

1 // To calculate current from a battery and pd across
   points A and B
2
3 clc;
4 clear;
5
6 // Resistances in the given network
7 R1=4;

```

```

8 R2=2;
9 R3=3;
10 R4=6;
11 R5=8;
12
13 // MESH Equations
14 //9*i1 -5*i2=10
15 // -5*i1+19*i2=0
16
17 // Supply voltage 10V
18
19 R=[(R1+R2+R3) -(R2+R3); -(R2+R3) (R2+R3+R4+R5)];
20 V=[10;0];
21
22 //Loop Currents
23 I=inv(R)*V;
24
25 i1=I(1);
26 i2=I(2);
27
28 i3=i1-i2; // From Mesh 1
29
30 // Point Voltages
31 Va=i3*R3;
32 Vb=i2*R5;
33
34 disp('amperes',abs(i1), 'The current through 4 ohm
      resistor and the battery =')
35 disp('amperes',abs(i2), 'The current through 6 ohm
      and 8 ohm resistors =')
36 disp('amperes',abs(i3), 'The current through 2 ohm
      and 3 ohm resistors =')
37
38 disp('volts',abs(Va), 'The voltage at point A =')
39 disp('volts',abs(Vb), 'The voltage at point B =')
40 disp('volts',(Va-Vb), 'The voltage across Points A
      and B =')

```

---

**Scilab code Exa 2.5** Determine Current through branch AB of the given network

```
1 // Determine Current through branch AB of the given
   network
2
3 clc;
4 clear;
5
6 // MESH Equations
7 // 4*i1 -2*i2 +0*i3=10
8 // -2*i1 +6*i2 -2*i3=0
9 //0*i1 -2*i2 +6*i3=0
10
11 //Supply Voltage is 10V (Note printing mistake)
12
13 R=[4 -2 0;-2 6 -2; 0 -2 6];
14 V=[10;0;0];
15
16 // Loop Currents
17
18 I=inv(R)*V;
19
20 i1=I(1);
21 i2=I(2);
22 i3=I(3);
23
24 disp('amperes',abs(i2), 'The current through branch
      AB of the network =')
```

---

**Scilab code Exa 2.6** Determine the current in the branches of the network using nodal analysis

```

1 // Determine the current in the branches of the
   network using nodal analysis
2
3 clc;
4 clear;
5
6 // Supply voltages
7 V1=30;
8 V2=40;
9
10 // Resistances in the network
11 R1=4;
12 R2=2;
13 R3=4;
14
15 Vb=poly([0 1] , 'Vb' , 'c');
16
17 AD=(V1-Vb)/R1;
18 BD=(V2-Vb)/R3;
19 CD=Vb/R2;
20
21 X=AD+BD-CD;
22
23 disp('The Characteristic Equation to find Vb is')
24
25 disp(CD , '=' , AD , '      + ' , BD)
26
27 Vb=roots(X); // Stores the numerical value of Vb
28
29 i1=(V1-Vb)/R1;
30 i2=(V2-Vb)/R3;
31 i3=Vb/R2;
32
33 disp('amperes' , i1 , 'Current through 4 ohm resistor on
   the 30V supply side =')
34 disp('amperes' , i2 , 'Current through 4 ohm resistor on
   the 40V supply side =')
35 disp('amperes' , i3 , 'Current through 2 ohm resistor ='
```

)

---

**Scilab code Exa 2.7** To Calculate current in all branches of the network shown using nodal analysis

```
1 // To Calculate current in all branches of the
   network shown using nodal analysis
2
3 clc;
4 clear;
5
6 // Nodal Equations
7 //13*Va-4*Vb=300
8 // -Va+4*Vb=120
9
10 X=[13 -4;-1 4];
11 V=[300;120];
12
13 E=inv(X)*V;
14
15 Va=E(1);
16 Vb=E(2);
17
18 i1=(100-Va)/20;
19 i2=(Va-Vb)/15;
20 i3=(Va/10);
21 i4=(Vb/10);
22 i5=(80-Vb)/10;
23
24 disp('V',Vb,' Voltage Vb = ','V',Va,' Voltage Va = ')
25
26 disp('The Branch Currents as calculated are')
27 disp(i5,'i5',i4,'i4',i3,'i3',i2,'i2',i1,'i1')
28 disp(' amperes respectively')
```

```

30 disp('The Negative sign indicates that the assumed
      direction of flow of current must be reversed')
31
32 disp('amperes',abs(i1), 'The Current through 20 ohm
      resistor on the 100V side =')
33 disp('amperes',abs(i2), 'The Current through 15 ohm
      resistor =')
34 disp('amperes',abs(i3), 'The Current through 10 ohm
      resistor (AE) =')
35 disp('amperes',abs(i4), 'The Current through 10 ohm
      resistor (BE) =')
36 disp('amperes',abs(i5), 'The Current through 10 ohm
      resistor on the 80V side =')

```

---

### Scilab code Exa 2.8 Conversion to current source and nodal analysis

```

1 // Conversion to current source and nodal analysis
2
3 clc;
4 clear;
5
6 // Nodal Equations
7 // 1.5*Va-0.5*Vb+0*Vc=5
8 // 0.5*Va-1.5*Vb+0.5*Vc=0
9 // 0*Va-0.5*Vb+1*Vc=0
10
11 Y=[1.5 -0.5 0;0.5 -1.5 0.5; 0 -0.5 1]; // Admittance
      matrix
12 I=[5;0;0];
13 V=inv(Y)*I;
14
15 Va=V(1);
16 Vb=V(2);
17 Vc=V(3);
18

```

```

19 Vab=Va-Vb;
20
21 disp('V',Va,'Voltage at node A =')
22 disp('V',Vb,'Voltage at node B =')
23 disp('V',Vc,'Voltage at node C =')
24
25 disp('V',Vab,'The voltage across AB in the circuit =')
26 disp('A',Vab/2,'The current in branch AB in the
circuit =')

```

---

**Scilab code Exa 2.9** Superposition Principle to determine current in branch

```

1 // Superposition Principle to determine current in
branch
2
3 clc;
4 clear;
5
6 //Order of resistances from left to right in the
circuit
7 r1=2;
8 r2=12;
9 r3=1;
10 r4=2;
11 r5=3;
12
13 V1=2;
14 V2=4;
15
16 // We now short circuit by removing one source and
consider the rest of the circuit
17 // Hence we will have two cases
18
19 //Case 1 4V supply removed and shorted

```

```

20
21 // Resistances between respective nodes .
22 rab1=(r4*r5)/(r4+r5);
23 rac1=rab1+r3;
24 rcd1=(rac1*r2)/(rac1+r2);
25
26 Reff1=rcd1+r1; // Effective resistance in case 1
27
28 I1=V1/Reff1; // Current from the 2V source
29
30 Iac1=I1*(r2/(r2+rac1));
31 Iab1=Iac1*(r5/(r5+r4)); // Current in AB from 2V
    source
32
33 // Case 2 2V supply removed and shorted
34
35 // Resistances between respective nodes .
36 rcd2=(r1*r2)/(r1+r2);
37 rac2=rcd2+r3;
38 rab2=(rac2*r4)/(rac2+r4);
39
40 Reff2=rab2+r5; // Effective resistance in case 2
41
42 I2=V2/Reff2; // Current from the 4V source
43
44 Iab2=I2*(rac2/(rac2+r4)); // Current in AB from 4V
    source
45
46 Iab=Iab1+Iab2; // Combined Current in AB from both
    the sources
47
48 disp(' amperes ',Iab,'The Current through AB (2 ohm
    resistor ) =')

```

---

**Scilab code Exa 2.10** Using thevenin theorem determine current through 2 ohm resistor

```
1 // Using thevenin theorem determine current through 2
   ohm resistor
2
3 clc;
4 clear;
5
6 // Characteristic equation to find Vth
7 // 14i1+12i2 = 2
8 // 12i1+16i2 = 4
9
10 // Resistors in the circuit in order from the 2V
    side
11 R1=2;
12 R2=12;
13 R3=1;
14 R4=3;
15
16 // Voltage Sources
17 V1=2;
18 V2=4;
19
20 Z=[14 12; 12 16]; // Resistance Matrix
21 V=[V1; V2]; // Voltage Matrix
22
23 I=inv(Z)*V; // Current Matrix
24
25 i1=I(1);
26 i2=I(2);
27
28 Vth=V2-(i2*R4);
29
30 Reff= R3 +((R1*R2)/(R1+R2));
31
32 Zth= Reff*R4/(Reff+R4);
33
```

```

34 Z1=2; // Resistor Connected between AB
35
36 Current = Vth/(Zth+Z1); // Current Through 2 ohm
    resistor
37
38 printf('The Current through 2 ohm resistor connected
    across AB = %g A\n', Current)

```

---

**Scilab code Exa 2.11** To find the current through the branch AB

```

1 //To find the current through the branch AB
2
3 clc;
4 clear;
5
6 Z1=2; // Resistor Across AB
7
8 // Voltage Sources
9 V1=20;
10 V2=10;
11
12 // Resistances in order as seen from 20 V side
    excluding the resistance between A and B
13 R1=2;
14 R2=2;
15 R3=2;
16 R4=4;
17 R5=4;
18
19 // Characteristic Equation
20 //10i1-4i2 =10
21 // -4i1+8i2 =10
22
23 Z=[10 -4; -4 8]; // Resistance Matrix
24 V=[10;10]; // Effective Voltages Matrix

```

```

25 I=inv(Z)*V; // Current Matrix
26 i1=I(1);
27 i2=I(2);
28
29 Vth=V1-(i1*(R1+R2));
30
31 Reff=R4*R5/(R4+R5); // Effective resistance of R4
    and R5 (Parallel)
32 Rt1=Reff+R3; // Effective Resistance on right side
    of AB
33 Rt2=R1+R2; // Effective Resistance on left side of
    AB
34 Zth=Rt1*Rt2/(Rt1+Rt2);
35
36 Current= Vth/(Zl+Zth); // Current Through branch AB
37
38 printf('The Current through branch AB = %g A\n',
    Current)

```

---

**Scilab code Exa 2.12** Determine current through various values of RL

```

1 // Determine current through various values of RL
2
3 clc;
4 clear;
5
6 Rl=[0 2 5]; // Resistance Vector
7
8 // Resistances of the circuit in order from the 40V
    side.
9 R1=4;
10 R2=6;
11 R3=5;
12
13 // Voltage Source

```

```

14 V=40;
15
16 i=V/(R1+R2);
17
18 Vth=i*R2;
19
20 Rth=R3+(R1*R2/(R1+R2));
21
22 Cur=(Rth+R1)/Vth; // Reciprocal of current
23
24 printf(' The Current through the Resistance RL = %g,
           %g ohm is %g A, %g A, %g A respectively \n',
           R1(1),R1(2),R1(3),1/Cur(1),1/Cur(2),1/Cur(3))

```

---

**Scilab code Exa 2.13** Current through AB using Nortons theorem

```

1 // Current through AB using Nortons theorem
2
3 clc;
4 clear;
5
6 // Resistances in order from the 2V side
7 R1=2;
8 R2=12;
9 R3=1;
10 R4=3;
11
12 // Voltage Sources
13 V1=2;
14 V2=4;
15
16 // Using Superposition principle
17 Iab1=V2/R4;
18 I1=V1/(R1+(R2*R3/(R2+R3))); // Current drawn from 2V
                                 supply

```

```

19 Iab2=I1*R2/(R1+R2);
20
21 Iab=Iab1+Iab2; // Current source
22
23 Reff= R3 +((R1*R2)/(R1+R2));
24
25 Zth= Reff*R4/(Reff+R4);
26
27 Zl=2; // Resistor Connected between AB
28
29 Current=Iab*(Zth/(Zth+2)); // Current through branch
   AB
30
31 // Errorless Calculation , In the textbook
   approximations are done
32 printf('The Current through 2 ohm resistor in branch
   AB = %g A\n',Current)

```

---

**Scilab code Exa 2.14** To determine current in RL using nortons theorem

```

1 //To determine current in RL using nortons theorem
2
3 clc;
4 clear;
5
6 // Resistances of the circuit in order from the 40V
   side .
7 R1=4;
8 R2=6;
9 R3=5;
10
11 // Voltage Source
12 V=40;
13
14 I=V/(R1+(R2*R3/(R2+R3)));

```

```

15
16 Ieq=I*(R2/(R2+R3));
17
18 Rth=R3+(R1*R2/(R1+R2));
19
20 Rl=[0 2 5];
21
22 Req=Rth+Rl; // Sum of resistances of Rth and each of
    Rl
23
24 //Currents for different values of Rl
25 I0=Ieq*Rth/Req(1);
26 I2=Ieq*Rth/Req(2);
27 I5=Ieq*Rth/Req(3);
28
29 printf('The Current through the resistance RL = %g
    ohms is %g A\n',Rl(1),I0)
30 printf('The Current through the resistance RL = %g
    ohms is %g A\n',Rl(2),I2)
31 printf('The Current through the resistance RL = %g
    ohms is %g A\n',Rl(3),I5)

```

---

**Scilab code Exa 2.15** To find current across 2ohm resistor using nortons theorem

```

1 // To find current across 2ohm resistor using
    nortons theorem
2
3 clc;
4 clear;
5
6 Z1=2; // Resistor Across AB
7
8 // Voltage Sources
9 V1=20;

```

```

10 V2=10;
11
12 // Resistances in order as seen from 20 V side
   excuding the resistance between A and B
13 R1=2;
14 R2=2;
15 R3=2;
16 R4=4;
17 R5=4;
18
19 Reff=R4*R5/(R4+R5); // Effective resistance of R4
   and R5 (Parallel)
20 Rt1=Reff+R3; // Effective Resistance on right side
   of AB
21 Rt2=R1+R2; // Effective Resistance on left side of
   AB
22 Zth=Rt1*Rt2/(Rt1+Rt2);
23
24 // Using superposition theorem
25 Iab1=V1/(R1+R2); // Current supplied to AB from 20V
   source
26 I1=V2/(R4+(R3*R5/(R3+R5))); // Current supplied from
   10V source to the network
27 Iab2=I1*(R5/(R3+R5)); // Current supplied to AB from
   10V Source
28
29 Iab=Iab1+Iab2; // Current Source
30
31 I=Iab*(Zth/(Zth+Z1));
32
33 printf('The current through branch AB flowing in the
   2 ohm resistor = %g A\n',I)

```

---

**Scilab code Exa 2.16** To determine the current in the 2 ohm resistor using superposition theorem

```

1 // To determine the current in the 2 ohm resistor
   using superposition theorem
2
3 clc;
4 clear;
5
6 // Voltage Sources
7 V1=5;
8 V2=10;
9
10 // Since both Voltage sources are connected in
    parallel and are unequal
11 R1=%inf; // As seen by 5V Source
12 R2=%inf; // As seen by 10V Source
13
14 I1=V1/R1; // Current Drawn from 5V supply
15 I2=V2/R2; // Current Drawn from 10V supply
16
17 I=I1+I2; // Current through 2 ohms resistor
18
19 printf('The Current flowing in the 2 ohm resistor =
    %g A\n',I)

```

---

**Scilab code Exa 2.17** To determine the value of RL for Max power transfer

```

1 //To determine the value of RL for Max power
   transfer
2
3 clc;
4 clear;
5
6 Vs=10/sqrt(2); // RMS Value of Voltage
7
8 // Resistances of the circuit from the Source side

```

```

9 R1=10;
10 R2=15;
11 R3=20;
12 R4=5;
13 R5=10;
14
15 Ref1=R3+(R1*R2/(R1+R2));
16 Ref2=R5+(Ref1*R4/(Ref1+R4));
17
18 Rab=Ref2;
19
20 // Characteristic Loop Equation of the first two
   loops for current flowing in clockwise direction
21 //25i1-15i2 = 10/(2^0.5)
22 // -15i1+40i2 = 0
23
24 Z=[10 25;-15 40];
25 V=[Vs;0];
26 I=inv(Z)*V;
27 i1=I(1);
28 i2=I(2);
29
30 Vth=i2*R4;
31
32 Powtrns=(Vth^2)/(4*Rab);
33
34 printf('The value of resistance RL for maximum power
         transfer = %g ohms\n',Rab)
35 printf('The value of power transferred = %g mW\n',
         Powtrns*1000)

```

---

**Scilab code Exa 2.18** Star to delta conversion of a circuit

```

1 //Star to delta conversion of a circuit
2

```

```

3  clc;
4  clear;
5
6  Zp=5;
7  Zq=10;
8  Zr=%i*10;
9
10 Zpq=((Zp*Zq)+(Zq*Zr)+(Zr*Zp))/Zr;
11 Zqr=((Zp*Zq)+(Zq*Zr)+(Zr*Zp))/Zp;
12 Zrp=((Zp*Zq)+(Zq*Zr)+(Zr*Zp))/Zq;
13
14 printf(' Delta Equivalent : \n')
15 printf(' Zpq = %g + j(%g) ohm \n', real(Zpq), imag(Zpq)
        ))
16 printf(' Zqr = %g + j(%g) ohm \n', real(Zqr), imag(Zqr
        ))
17 printf(' Zrp = %g + j(%g) ohm \n', real(Zrp), imag(Zrp
        ))

```

---

### Scilab code Exa 2.19 Star Equivalent of the delta circuit

```

1 // Star Equivalent of the delta circuit
2
3 clc;
4 clear;
5
6 Z12=%i*5;
7 Z23=%i*-5;
8 Z31=%i*5;
9
10 Z1=(Z12*Z31)/(Z12+Z23+Z31);
11 Z2=(Z12*Z23)/(Z12+Z23+Z31);
12 Z3=(Z23*Z31)/(Z12+Z23+Z31);
13
14 printf('Star Equivalent :\n')

```

```
15 disp('ohms',Z1,'Z1 =')
16 disp('ohms',Z2,'Z2 =')
17 disp('ohms',Z3,'Z3 =')
```

---

**Scilab code Exa 2.20** To determine equivalent resistance using star delta transformation

```
1 //To determine equivalent resistance using star-
   delta transformation
2
3 clc;
4 clear;
5
6 Rax=30;
7 Rcx=30;
8 Rac=30;
9 Ray=30;
10 Rcy=30;
11
12 // Delta to star conversion of the triangle CAX in
   the circuit
13 Rx=Rax*Rcx/(Rax+Rcx+Rac);
14 Ra=Rax*Rac/(Rax+Rcx+Rac);
15 Rc=Rac*Rcx/(Rax+Rcx+Rac);
16
17 R1=Ra+Ray;// Resistance from the common to Y of the
   upper limb
18 R2=Rc+Rcy;// Resistance from the common to Y of the
   lower limb
19
20 Reff=R1*R2/(R1+R2); // Effective resistance of both
   the limbs
21
22 Rxy=Rx+Reff; // Effective resistance across X and Y
23
```

```
24 printf('The Equivalent resistance = %g ohms\n',Rxy)
```

---

**Scilab code Exa 2.21** Determine current through branch AB using loop and nodal analysis

```
1 // Determine current through branch AB using loop
   and nodal analysis
2
3 clc;
4 clear;
5
6 Is=4; // Current Source
7 //Resistances
8 Rab=2;
9 R1=4; // After point B towards the right
10 R2=1;
11
12 V=10; // Voltage source
13
14 //Using Simple Logic
15 i1=Is; // Current source connected in series with
   resistor
16 i2=10/(R1+R2);
17
18 printf('The Current through branch AB: \n')
19 printf('i) Simple Logic = %g A\n',i1)
20
21 //Using Loop Analysis
22
23 //Conversion of Current source into voltage source ,
   R tends to infinity
24
25 R=poly(0,'R');
26
27 Rmat=[R+2 0; 0 5];
```

```

28 Vmat=[(4*R)-V;V];
29 Imat=inv(Rmat)*Vmat;
30 printf ('\nii) Loop Analysis\n')
31 disp(Imat(1,1), 'The current through AB is ')
32 printf ('\nWhere R tends to infinity\n')
33
34 R=%inf;
35 i1=(4-(V/R))/(1+(Rab/R));
36 printf ('\n = %g A\n',i1)
37
38 // Using Nodal Analysis
39 // Conversion of voltage source into current source ,
40 // R then tends to zero
41 R=poly(0,'R');
42
43 // Nodal Eqaution
44 // 0.5V1-0.5V2+0V3 = 4
45 // -0.5V1+(0.75+(1/R))V2-0.25V3 = 10/R
46 // 0V1-0.25V2+1.25V3=0
47
48 Y=[0.5 -0.5 0;-0.5 (0.75+(1/R)) -0.25;0 -0.25 1.25];
        // Admittance Matrix
49 Im=[4; (10/R); 0] ; // Current Matrix
50Vm=inv(Y)*Im; // Voltage Matrix
51 V1=Vm(1,1);
52 V2=Vm(2,1);
53 V3=Vm(3,1);
54
55 DiffV=V1-V2;
56
57 printf ('\niii) Nodal Analysis:\n')
58 disp(V2,'V2:',V1,'V1:')
59 Vdiff=roots(DiffV(2)-R); // To change data type
60 disp(DiffV,'V1-V2 :')
61 In=Vdiff/Rab; // Current due to nodal analysis
62
63 printf ('\n The Current Through 2 ohm resistor = %g A

```

\n', In )

---

**Scilab code Exa 2.22** Current through 2 ohm resistor given a current source

```
1 // Current through 2 ohm resistor given a current
   source
2
3 clc;
4 clear;
5
6 Is=2; // Current Source
7
8 // Resistors connected directly to the current source
9 Rs1=0.5;
10 Rs2=0.5;
11
12 // Resistors in various branches starting from the
   top
13 R1=1;
14 R2=1;
15 R3=2;
16
17 //Conversion to voltage sources
18 V1=Rs1*Is; // Voltage across first half of the
   branch
19 V2=Rs2*Is; // Voltage across second half of the
   branch
20
21 // Voltage sources in the circuit
22 V3=1;
23 V4=2;
24
25 //Characteristic Equations
26 //2.5i1-1i2 = 2
27 // -1i1+3.5i2 = 2
```

```

28
29 R=[2.5 -1; -1 3.5]; // Resistor Vector
30 V=[(V1+V3);(V2+V4-V3)]; // Voltage Vector
31 I=inv(R)*V; // Current Vector
32 i1=I(1);
33 i2=I(2);
34
35 printf('The Current through the 2 ohm resistor = %g
A\n',i2)

```

---

**Scilab code Exa 2.23** To find voltage v and current through 3 ohm resistor using nodal analysis

```

1 //To find voltage v and current through 3 ohm
   resistor using nodal analysis
2
3 clc;
4 clear;
5
6 V=poly(0, 'V');
7
8 Va=8-V;
9 Vb=-6;
10
11 // Resistors in order from the 8V side
12 R1=1;
13 R2=2;
14 R3=3;
15 R4=4;
16
17 // Nodal Analysis
18
19 X=((8-Va)/R1)+((Vb-Va)/R3)-((Va-(4*V))/R2); //
   Characteristic equation to find V
20

```

```

21 V=roots(X);
22
23 Va=8-V;
24
25 I=(Vb-Va)/3;
26
27 printf('i) The Voltage V (across 1 ohm resistor) is
    %g V\n',V)
28
29 if(imag(sqrt(I))) // Condition to check for negative
    sign
30     printf('ii) The Current through 3 ohm resistor
        is %g A flowing from A to B\n',abs(I))
31 else
32     printf('ii) The Current through 3 ohm resistor is %g
        A flowing from B to A\n',abs(I))
33 end

```

---

**Scilab code Exa 2.24** Determine the current through 10 ohm resistor using thevenins circuit

```

1 // Determine the current through 10 ohm resistor
   using thevenins circuit
2
3 clc;
4 clear;
5
6 //Source Voltages
7 V1=10;
8 V2=2;
9
10 // Resistances of upper limb
11 R1=15;
12 R2=25;
13

```

```

14 // Resistances of lower limb
15
16 R3=30;
17 R4=20;
18
19 //For a thevenin circuit
20 i1=(V1-V2)/(R1+R2); // Current in upper limb
21 i2=V1/(R3+R4); // Current in lower limb
22
23 Vac=(i1*R2)+2;
24 Vbc=(i2*R4);
25
26 Vab=Vac-Vbc; // Thevenin Voltage
27
28 Vth=Vab;
29 Zl=10; // Load resistance
30
31 Reff1=(R1*R2/(R2+R1));
32 Reff2=(R3*R4/(R3+R4));
33
34 Zth=Reff1+Reff2;
35
36 I=Vth/(Zl+Zth); // Current through AB
37
38 printf('The current through the 10 ohm resistor = %g
          mA\n', I*1000)

```

---

# Chapter 3

## Three Phase Supply

**Scilab code Exa 3.1** To determine the parameters of a balanced 3 phase star connected to a resistive load

```
1 // To determine the parameters of a balanced 3 phase
   star connected to a resistive load
2
3 clc;
4 clear;
5
6 V=208;
7 Vph=V/sqrt(3);
8 R=35;
9
10 // Star Connected load has its line current = phase
    current
11
12 Ia=Vph/R;
13 Ib=Ia*(expm(%i*(-2*pi/3)));
14 Ic=Ia*(expm(%i*(2*pi/3)));
15
16 Pperphase= (abs(Ia)^2)*R;
17
18 Pt=3*Pperphase;
```

```

19
20 // Resistive Load , p.f is unity
21
22 pf=1;
23
24 printf('The power factor is %g \n',pf)
25 printf('The total power dissipated = %g W \n',Pt)
26 printf('The currents of the system are\n Ia = %g /-0
          A \n Ib = %g /-120 A \n Ic = %g /-120 A \n',abs
          (Ia),abs(Ib),abs(Ic))

```

---

**Scilab code Exa 3.2** To determine the parameters of a balanced 3 phase star connected to an impedance

```

1 // To determine the parameters of a balanced 3 phase
   star connected to an impedance
2
3 clc;
4 clear;
5
6 V=208;
7 Vph=V/sqrt(3);
8 Z=15+(%i*20);
9
10 // Star Connected load has its line current = phase
    current
11
12 Ia=Vph/Z;
13 Ib=Ia*(expm(%i*(-2*pi/3)));
14 Ic=Ia*(expm(%i*(2*pi/3)));
15
16 Pperphase= (abs(Ia)^2)*real(Z);
17
18 Pt=3*Pperphase;
19

```

```

20 Atheta=atand(imag(Ia)/real(Ia));
21 Btheta=atand(imag(Ib)/real(Ib));
22 Ctheta=atand(imag(Ic)/real(Ic));
23
24 pf=cosd(Atheta);
25
26 printf('The power factor is %g lagging \n',pf)
27 printf('The total power dissipated = %g W \n',Pt)
28 printf('The currents of the system are \n')
29 printf('Ia= %g /-%g A \n',abs(Ia),Atheta)
30 printf('Ib= %g /-%g A \n',abs(Ib),Btheta-180)
31 printf('Ic= %g /-%g A \n',abs(Ic),Ctheta)

```

---

**Scilab code Exa 3.3** To determine the potential of the star point and line currents

```

1 //To determine the potential of the star point and
   line currents
2
3 clc;
4 clear;
5
6 Zr=10*(expm(%i*pi/6));
7 Zy=12*(expm(%i*pi/4));
8 Zb=15*(expm(%i*2*pi/9));
9
10 V=440;
11 Vph=V/(sqrt(3));
12
13 //Phase Voltages
14 Vr=Vph*(expm(%i*0));
15 Vy=Vph*(expm(%i*-2*pi/3));
16 Vb=Vph*(expm(%i*2*pi/3));
17
18 Vs=((Vr/Zr)+(Vy/Zy)+(Vb/Zb))/((1/Zr)+(1/Zy)+(1/Zb));

```

```

19
20 tvs=atand(imag(Vs)/real(Vs)); // Phase Angle of the
   star point voltage
21
22 Ia=(Vr-Vs)/Zr;
23 iat=atand(imag(Ia)/real(Ia)); // Angle of current in
   phase R
24 Ib=(Vy-Vs)/Zy;
25 ibt=atand(imag(Ib)/real(Ib)); // Angle of current in
   phase Y
26 Ic=(Vb-Vs)/Zb;
27 ict=atand(imag(Ic)/real(Ic)); // Angle of current in
   phase B
28
29 I=Ia+Ib+Ic;
30 I=ceil(real(I)*1000)+%i*(ceil(imag(I)*1000));
31
32 printf('The potential of the star point = %g /-%g V
   \n',abs(Vs),tvs)
33 printf('The line currents are : \n')
34 printf('R phase current = %g /-%g A \n',abs(Ia),iat)
35 printf('Y phase current = %g /-%g A \n',abs(Ib),ibt
   -180)
36 printf('B phase current = %g /-%g A \n',abs(Ic),ict)

```

---

**Scilab code Exa 3.4** To determine the line currents if one inductor is short circuited

```

1 //To determine the line currents if one inductor is
   short circuited
2
3 clc;
4 clear;
5
6 V=460; // Line to Line voltage

```

```

7 pf=0.8; // Power Factor
8 P=8*(10^3); // Power Consumed by the network
9
10 Vph=V/sqrt(3);
11
12 Iph=P/(sqrt(3)*V*pf);
13
14 theta=acos(pf); // Power factor angle
15 Z=(Vph/Iph)*(exp(%i*theta));
16
17 Va=V*exp(%i*0); // Voltage of Phase A
18 Vc=V*exp(%i*-2*pi/3); // Voltage of Phase C
19
20 Ia=Va/Z; // Current in phase A
21 Ic=Vc/Z; // Current in phase C
22
23 iat=atand(imag(Ia)/real(Ia)); // Phase angle of Ia
24 ict=atand(imag(Ic)/real(Ic)); // Phase angle of Ic
25
26 tac=iat-ict; // Angle between current Ia and Ic
27
28 Ib=sqrt((abs(Ia)^2)+(abs(Ic)^2)+(2*abs(Ia)*abs(Ic)*
    cosd(tac)));
29
30 printf('The line currents are : \n')
31 printf('Phase a = %g/_%g A \n',abs(Ia),iat)
32 printf('Phase b = %g A \n',abs(Ib))
33 printf('Phase c = %g/_%g A \n',abs(Ic),ict)

```

---

**Scilab code Exa 3.5** To find line current and pf and powers of a balanced delta load

```

1 //To find line current and pf and powers of a
   balanced delta load
2

```

```

3 clc;
4 clear;
5
6 Z=8+6*i; // Load
7 V=230; // Voltage supply
8
9 iR=V/Z;
10 theta= atand(imag(iR)/real(iR));
11
12 I1= iR*sqrt(3); // Line current
13
14 Pa=sqrt(3)*V*abs(I1)*cosd(theta); // Active Power
15 Pr=sqrt(3)*V*abs(I1)*sind(theta); // Reactive Power
16
17 Pt=sqrt(3)*V*abs(I1); // Total Volt amperes
18
19 printf('The line current = %g A \n',abs(I1))
20 printf('The power factor = %g lagging \n',cosd(theta))
21 printf('The Active Power = %g kW \n',abs(Pa)/1000)
22 printf('The Reactive Power = %g kV Ar \n',abs(Pr)
23 printf('The total volt amperes = %g kVA \n',abs(Pt)
/1000)

```

---

**Scilab code Exa 3.6** To find Line currents and star connected resistors for the same power

```

1 //To find Line currents and star connected resistors
   for the same power
2
3 clc;
4 clear;
5
6 // Phase Voltages

```

```

7 Vr=400*(expm(%i*0));
8 Vy=400*(expm(%i*-2*pi/3));
9 Vb=400*(expm(%i*2*pi/3));
10
11 Zry=100; // Impedance between Phase R and Phase Y
12 Zyb=%i*100; // Impedance between Phase Y and Phase B
13 Zbr=-%i*100; // Impedance between Phase B and Phase R
14
15 Iry=Vr/Zry;
16 Iyb=Vy/Zyb;
17 Ibr=Vb/Zbr;
18
19 Ir=Iry-Ibr;
20 Iy=Iyb-Iry;
21 Ib=Ibr-Iyb;
22
23 //Phase angles of the line currents in RYB sequence
24 tr=atand(imag(Ir)/real(Ir));
25
26 if(real(Iy)==0)
27 ty=atand((imag(Iy)/abs(imag(Iy)))*%inf);
28 else
29 ty=atand(imag(Iy)/real(Iy));
30 end
31 if(real(Ib)==0)
32 tb=atand((imag(Ib)/abs(imag(Ib)))*%inf);
33 else
34 tb=atand(imag(Ib)/real(Ib));
35 end
36
37 P=(Iry^2)*Zry; // Power consumed by the circuit (
      Arm RY)
38
39 Vph=Vr/sqrt(3); // Phase voltage in a star connected
      system
40
41 R=poly([0 1], 'R', 'c');
42

```

```

43 x=(3*(Vph^2))-(P*R); // Characteristic Eqaution to
   find R
44
45 R=roots(x);
46
47 printf('a) The line currents in RYB sequence are : \
   n')
48 printf(' R line = %g/-%g A \n',abs(Ir),tr);
49 printf(' Y line = %g/-%g A \n',abs(Iy),ty);
50 // Error in text book answer
51 printf(' B line = %g/-%g A \n \n',abs(Ib),tb);
52 printf('b) The value of resistors to draw same power
   as in problem statement a) = %g ohms \n',R(1))

```

---

**Scilab code Exa 3.7** Reduction in load when one resistor is removed

```

1 //Reduction in load when one resistor is removed
2
3 clc;
4 clear;
5
6 // Assuming the variables to be eqaul to unit
   quantities
7
8 Vph=1;
9 Vl=sqrt(3)*Vph;
10 R=1;
11
12 // Star connected
13
14 Pis=3*(Vph^2)/R; // Initial Power
15
16 Pfs=(Vl^2)/(2*R); // Power when one resitor is
   removed
17

```

```

18 pers=(Pis-Pfs)*100/Pis; // Percentage decrease in
    Load
19
20 // Mesh connected
21
22 Pim=3*(Vl^2)/R; // Initial Power
23
24 Pfm=2*(Vl^2)/R; // Power when one resistor is removed
25
26 perm=(Pim-Pfm)*100/Pim; // Percentage decrease in
    Load
27
28 printf(' Vl= square root (3) * Vph \n \n')
29 printf('a) Star Connected Power = 3*(Vph^2)/R \n')
30 printf(' When one resistor is removed Power = (Vl
    ^2)/2R \n')
31 printf(' The percentage reduction in load = %g \n
    ',pers)
32
33 printf('b) Mesh Connected Power = 3*(Vl^2)/R \n')
34 printf(' When one resistor is removed , Power = 2*(
    Vl^2)/R \n ')
35 printf(' The percentage reduction in load = %g \n
    ',perm)

```

---

**Scilab code Exa 3.8** To measure power by two wattmeter method

```

1 //To measure power by two wattmeter method
2
3 clc;
4 clear;
5
6 pf=0.85 // Power Factor
7
8 Po=37.3*(10^3); // Power Output

```

```

9
10 eff=90/100; // Efficiency
11
12 V=500; // Rated Voltage
13
14 Pi=Po/eff; // Power Input
15
16 phi=acosd(pf); // Power Factor angle
17
18 printf('W1 + W2 = %g kW \n',Pi/1000)
19 printf('tan(phi) = square root (3)*(W2-W1)/(W2+W1) = %g \n',tand(phi))
20
21 x=Pi; // Let x = W1+W2
22
23 y= tand(phi)*x/(sqrt(3)); // Let y = W2-W1
24
25 printf('W1 + W2 = %g kW \n',x/1000)
26 printf('W2 - W1 = %g kW \n',y/1000)
27 printf('W2 = %g kW \n',(x+y)/(2*1000))
28 printf('W1 = %g kW \n',(x-y)/(2*1000))

```

---

**Scilab code Exa 3.9** To find power using two wattmeter method of a circuit with non reactive resistances

```

1 //To find power using two wattmeter method of a
   circuit with non reactive resistances
2
3 clc;
4 clear;
5
6 V=400; // Line Voltage
7 Vph=V/(sqrt(3)); // Magnitude of Phase Voltage
8
9 // Phase Voltage in RYB sequence

```

```

10 Vr=Vph*(expm(%i*0));
11 Vy=Vph*(expm(%i*-2*pi/3));
12 Vb=Vph*(expm(%i*2*pi/3));
13
14 // Resistances of the RYB limbs
15 Rr=10;
16 Ry=15;
17 Rb=20;
18
19 // Taking Vr as reference
20 // Millain's Theorem
21
22 Vs= ((Vr/Rr)+(Vy/Ry)+(Vb/Rb))/((1/Rr)+(1/Ry)+(1/Rb))
     ; // Star point voltage
23
24 //Line Currents in RYB sequence
25 Ir= (Vr-Vs)/Rr;
26 Iy= (Vy-Vs)/Ry;
27 Ib= (Vb-Vs)/Rb;
28
29 Vry=Vr-Vy;
30 Vby=Vb-Vy;
31
32 W1= real(Vry*conj(Ir));
33 W2= real(Vby*conj(Ib));
34
35 Wt= W1+W2; // Total Power
36
37 // Note Iy in the text book there is a error in the
     sign of the real part of Vy
38
39 printf('The line currents in RYB sequence are : \n')
40 disp(Ir,' R line :')
41 printf(' Magnitude = %g A \n',abs(Ir))
42 disp(Iy,' Y line :')
43 printf(' Magnitude = %g A\n',abs(Iy))
44 disp(Ib,' B line :')
45 printf(' Magnitude = %g A\n \n',abs(Ib))

```

```
46 printf(' Total Power = %g kW \n \n',Wt/1000)
47 printf(' W1 = %g kW\n',W1/1000)
48 printf(' W2 = %g kW\n',W2/1000)
```

---

**Scilab code Exa 3.10** Two wattmeter power dertermination for a delta system

```
1 // Two wattmeter power dertermination for a delta
   system
2
3 clc;
4 clear;
5
6 V=250; // Phase Voltage
7
8 // Phase Voltage in RYB sequence
9 Vry=V*(expm(%i*0));
10 Vyb=V*(expm(%i*-2*pi/3));
11 Vbr=V*(expm(%i*2*pi/3));
12
13 // Resistances of the RYB limbs
14 Rry=10+%i*10;
15 Ryb=20-%i*15;
16 Rbr=10+%i*20;
17
18 // Phase Currents in RYB
19
20 Iry= Vry/Rry;
21 Iyb= Vyb/Ryb;
22 Ibr= Vbr/Rbr;
23
24 // Phase Current Angles wrt to Vr
25
26 ary=atand(imag(Iry)/real(Iry));
27 ayb=atand(imag(Iyb)/real(Iyb));
```

```

28 abr=atand(imag(Ibr)/real(Ibr));
29
30 // Line Currents in RYB
31 Ir=Iry-Ibr;
32 Iy=Iyb-Iry;
33 Ib=Ibr-Iyb;
34
35 W1=real(-Vbr*conj(Ir));
36 W2=real(Vyb*conj(Iy));
37
38 Wt= W1+W2; // Total Power
39
40 printf('i)\n')
41 printf(' The Currents in each branch are : \n')
42 printf(' Branch RY = %g/%g A \n',abs(Iry),ary)
43 printf(' Branch YB = %g/%g A \n',abs(Iyb),ayb)
44 printf(' Branch BR = %g/%g A \n',abs(Ibr),abr)
45
46 printf('ii) \n')
47 printf('The line currents in RYB sequence are : \n')
48 disp(Ir,' R line :')
49 printf(' Magnitude = %g A \n',abs(Ir))
50 disp(Iy,' Y line :')
51 printf(' Magnitude = %g A\n',abs(Iy))
52 disp(Ib,' B line :')
53 printf(' Magnitude = %g A\n \n',abs(Ib))
54
55 // Precision is more, The Text book includes round
      off error
56 printf(' W1 = %g W\n',W1)
57 printf(' W2 = %g W\n',W2)

```

---

# Chapter 4

## Basic Instruments

**Scilab code Exa 4.1** Torque on the coil at a current of 1mA

```
1 //Torque on the coil at a current of 1mA
2
3 clc;
4 clear;
5
6 N=60;
7 B=50*(10^-3);
8 I=1*(10^-3);
9
10 l=3*(10^-2);
11
12 // w= 2*r; w is the width
13 w=2*(10^-2);
14
15 Td=N*B*I*l*w;
16
17 printf('The torque on the coil carrying 1mA = %g
           micro Nm \n',Td*(10^6))
```

---

**Scilab code Exa 4.2** To find the deflection produced by 200V

```
1 //To find the deflection produced by 200V
2
3 clc;
4 clear;
5
6 R=10*(10^3);
7 V=200;
8 B=80*(10^-3);
9 N=100;
10 A=9*(10^-4); // The area of the coil is the product
                 of the length and width (l.2r)
11 I=V/R;
12
13 Td=N*B*I*A;
14
15 K=30*(10^-7);
16
17 theta=Td/K;
18
19 printf('The deflection produced by 200V = %g degrees
          \n',theta)
```

---

**Scilab code Exa 4.3** Reading on ammeters when their shunts are interchanged

```
1 // Reading on ammeters when their shunts are
   interchanged
2
3 clc;
4 clear;
5
6 I=10;
7 Ra=1000;
```

```

8 Rsa=0.02;
9
10 Rb=1500;
11 Rsb=0.01;
12
13 def( 'x=cur(y,z)' , 'x=I*z/y' )
14
15 Ia1=cur(Ra,Rsa); // Initial Current in meter A
16 Ia2=cur(Ra,Rsb); // Changed Current in meter A
17
18 Ib1=cur(Rb,Rsb); // Initial Current in meter B
19 Ib2=cur(Rb,Rsa); // Changed Current in meter B
20
21 //Factor by which the current readings change in the
   two ammeters
22
23 A=Ia2/Ia1; // Ammeter A
24 B=Ib2/Ib1; // Ammeter A
25
26 printf('The initial current in ammeter A and ammeter
   B are %g A and %g A respectively. \n \n',I,I)
27
28 printf('The current in ammeter A and ammeter B when
   the shunt resistances are interchanged are %g A
   and %g A respectively. \n \n',I*A,I*B)

```

---

**Scilab code Exa 4.4** To create an instrument that measures voltages and currents upto a rated value

```

1 //To create an instrument that measures voltages and
   currents upto a rated value
2
3 clc;
4 clear;
5

```

```

6 Rm=10;
7 Im=50*(10^-3);
8 V=750;
9 I=100;
10
11 //To Calculate the required voltage a resistor
   should be added in series with the internal
   resistance
12
13 R=poly([0 1], 'R', 'c');
14
15 sr=Im*(R+Rm)-V;
16
17 R=roots(sr); //Characteristic equation to find R
18
19 // To attain the required current , a resistor should
   be added in parallel to the internal resistance
20
21 r=poly([0 1], 'r', 'c'); // Characteristic equation to
   find r
22
23 pr=Im*(r+Rm)-(I*r);
24
25 r=roots(pr);
26
27 printf('To Read 750 V a series resistance of %g ohms
   should be connected to the instrument \n',R)
28 printf('To Read 100 A a parallel resistance of %g
   milli ohms should be connected to the instrument
   \n',r*1000)

```

---

**Scilab code Exa 4.5** To determine the range and current and deflection at various conditions

```
1 //To determine the range and current and deflection
```

```

        at various conditions

2
3 clc;
4 clear;
5
6 I=25;
7 theta=90;
8
9 // Various conditions
10 ta=360; // Angle in case a
11 tb=180; // Angle in case b
12 Ic=20; // Current in case c
13
14 // theta directly proportional to the square of the
   current
15
16 Ia=sqrt(ta*(I^2)/theta);
17
18 Ib=sqrt(tb*(I^2)/theta);
19
20 tc=((Ic/I)^2)*theta;
21
22 printf('a) Full Scsle deflection (360) current = %g
      A \n',Ia)
23 printf('b) Half Scsle deflection (180) current = %g
      A \n',Ib)
24 printf('c) Deflection for a current of 20 A = %g
      degrees \n',tc)

```

---

### Scilab code Exa 4.6 Error calculation

```

1 // Error calculation
2
3 clc;
4 clear;

```

```

5
6 I=20; //Current
7 V=230; // Voltage
8 C=480; // Meter Constant
9 L=4.6*(10^3); // Load
10 t=66/3600; // Time in hour
11
12 R=40; //No of revolutions
13
14 Pc=L*t/1000; // Energy Consumed in kWhr
15
16 Pr=R/C; // Energy recorded in kWhr
17
18 err=(Pc-Pr)*100/Pc;
19
20 printf('The Error in the meter is that the disc
rotates %g percent slow \n',err)

```

---

**Scilab code Exa 4.7** Dynamometer wattmeter power calculation of the load

```

1 //Dynamometer wattmeter power calculation of the
load
2
3 clc;
4 clear;
5
6 P=250; // Power Recorded by the wattmeter
7
8 V=200; // Load voltage
9
10 R=2000; // Resistance of the highly non-inductive
pressure coil
11
12 I=V/R; // Ohm's Law
13

```

```
14 Pcoil=V*I; // Power Absorbed by the pressure coil
15
16 P1=P-Pcoil; // Power taken by the load
17
18 printf('The Power taken by the load = %g watts.\n',
P1)
```

---

### Scilab code Exa 4.8 Percentage error calculation in a wattmeter

```
1 //Percentage error calculation in a wattmeter
2
3 clc;
4 clear;
5
6 //Rated Parameters
7 I=50;
8 V=230;
9
10 R=61; // No. of revolutions
11 t=37/3600; // Time in hours
12
13 C=520; // Normal Disc Speed
14
15 Pfl=I*V;// Power at full load
16
17 Ps=Pfl*t/1000; // Power Supplied in kWhr
18
19 Pr=R/C; //Power recorded in kWhr
20
21 err=(Ps-Pr)*100/Ps;
22
23 printf('The Percentage Error = %g percent slow\n',
err)
```

---

# Chapter 5

## Transformer

**Scilab code Exa 5.1** To find flux density in the core and induced emf in the secondary winding

```
1 // To find flux density in the core and induced emf  
  in the secondary winding  
2  
3 clc;  
4 clear;  
5  
6 E1=500;  
7 A=60*(10^-4);  
8 f=50;  
9 N1=400;  
10 N2=1000;  
11  
12 // E=4.44*f*N*Bm*A Induced EMF equation  
13  
14 Bm=E1/(4.44*f*N1*A);  
15  
16 E2=4.44*f*N2*Bm*A;  
17  
18 printf('a) The peak value of the flux density in the  
core = %f tesla \n',Bm)
```

```
19 printf('b) The voltage induced in the secondary  
winding = %f V \n',E2)
```

---

**Scilab code Exa 5.2** To calculate the number of turns per limb on the high and low voltage sides

```
1 // To calculate the number of turns per limb on the  
high and low voltage sides  
2  
3 clc;  
4 clear;  
5  
6 f=50;  
7 A=400*(10^-4);  
8 Bm=1;  
9 V1=3000;  
10 V2=220;  
11  
12 l=2; // Number of limbs  
13  
14 // Neglecting the series voltage drop  
15  
16 // Induced EMF equation  
17 a=V1/(4.44*f*A*Bm);  
18  
19 b=V2*a/V1;  
20  
21 if(modulo(round(a),2)==0) // No. of turns is a whole  
    even number as it has 2 limbs  
22     N1=round(a);  
23 else  
24     N1=round(a)+1;  
25 end  
26  
27 if(modulo(round(b),2)==0) // No. of turns is a whole
```

```

        even number as it has 2 limbs
28     N2=round(b);
29 else
30     N2=round(b)+1;
31 end
32
33 printf('The number of turns in the high voltage side
            per limb = %d \n',N1/1)
34 printf('The number of turns in the low voltage side
            per limb = %d \n',N2/1)

```

---

**Scilab code Exa 5.3** To calculate resistance of primary in terms of secondary and vice versa

```

1 // To calculate resistance of primary in terms of
   secondary and vice versa
2
3 clc;
4 clear;
5
6 N1=90;
7 N2=180;
8
9 R2=0.233;
10 R1=0.067;
11
12 n=N2/N1; // Transformation ratio
13
14 R1w2=(n^2)*R1;
15 R2w1=R2/(n^2);
16
17 Rt=R1+R2w1; // Total resistance in terms of primary
18
19 printf('a) Resistance of primary in terms of the
            secondary = %f ohms \n',R1w2)

```

```
20 printf('b) Resistance of secondary in terms of the  
primary = %f ohms \n',R2w1)  
21 printf('c) Total resistance of the transformer in  
terms of the primary winding =%f ohms \n',Rt)
```

---

**Scilab code Exa 5.4** Total resistance and total copper loss at full load

```
1 // Total resistance and total copper loss at full  
load  
2  
3 clc;  
4 clear;  
5  
6 P=40*(10^3);  
7 E1=2000;  
8 E2=250;  
9  
10 n=E2/E1; // Transformation ratio  
11  
12 R1=1.15;  
13 R2=0.0155;  
14  
15 R1w2=R1*(n^2);  
16 R2w1=R2/(n^2);  
17  
18 Rt=R2+R1w2;  
19  
20 // Full load currents  
21 I1=P/E1;  
22 I2=P/E2;  
23  
24 Pc1=(I1^2)*R1; // Primary Loss  
25 Pc2=(I2^2)*R2; // Secondary Loss  
26  
27 Pc= Pc1+Pc2; // Total Copper loss at full load
```

```
28
29 printf('a) The total resistance in terms of the
   secondary winding = %f ohms \n',Rt)
30 printf('b) Total copper loss on full load = %f watts
   ',Pc)
```

---

### Scilab code Exa 5.5 Voltage regulation at a pf lagging

```
1 // Voltage regulation at 0.8 pf lagging
2
3 clc;
4 clear;
5
6 E1=1100;
7 E2=110;
8
9 P=5*(10^3);
10
11 I=P/E1; // Primary full load current
12
13 I2=P/E2;// Secondary full load current
14
15 V=33;
16
17 pf=0.8; // Power Factor lagging , so the angle is
   positive
18
19 theta=acosd(pf); // Power factor angle
20
21 Pc=85;
22
23 R=Pc/(I^2);
24
25 Z=V/I;
26
```

```

27 V1=E1;
28
29 X=sqrt((Z^2)-(R^2));
30
31 // Using equation 5.22 to determine V2
32
33 V2=poly([0 1], 'V2', 'c');
34
35 x=(V2^2)+(2*V2*I*R*pf)+(2*V2*I*X*sind(theta))+((I^2)
    *((R^2)+(X^2)))-(V1^2);
36
37 r=roots(x);
38
39 a1=sqrt(r(1));
40 a2=sqrt(r(2));
41
42 if(imag(a1))
43     V2=r(2);
44 else
45     if(imag(a2))
46         V2=r(1);
47     else
48         disp('Error')
49     end
50 end
51
52 reg=(V1-V2)/V2; // Voltage regulation
53
54 regper=reg*100; // Voltage regulation percent
55
56 disp(x, 'The characteristic equation to find V2
equated to zero is')
57
58 disp(regper, 'The percentage voltage regulation for a
load at 0.8 pf lagging is')

```

---

**Scilab code Exa 5.6** Regulation at lagging leading and unity power factors

```
1 // Regulation at lagging leading and unity power
   factors
2
3 clc;
4 clear;
5
6 ol=0.01; // Ohmic loss is 1% of the output
7
8 // Output = V*I; Ohmic loss =(I^2)*R
9
10 // (I*R)/V = 0.01
11
12 rd=0.05; // Reactance drop is 5% of the output
   voltage
13
14 // Power Factors
15 pf1=0.8; // lag
16 pf2=1; // unity
17 pf3=0.8; // lead
18
19 deff('y=angle(x)', 'y=acosd(x)'); // Function to find
   out the angle
20
21 // Angles
22 t1=angle(pf1); // Positive sign as it is lagging
23 t2=angle(pf2);
24 t3=-angle(pf3); // Minus sign as it is leading
25
26 deff('a=vr(b)', 'a=((ol*cosd(b))+(rd*sind(b)))*100');
   // Function to find out voltage regulation
27
28 printf('The voltage regulation percentages is as
```

```
    follows \n')
29 printf('a) For 0.8 p.f lag = %f percent \n',vr(t1))
30 printf('b) For unity p.f = %f percent \n',vr(t2))
31 printf('c) For 0.8 p.f lead = %f percent \n',vr(t3))
```

---

**Scilab code Exa 5.7** Calculate the circuit parameters of a transformer using OC and SC tests

```
1 // Calculate the circuit parameters of a transformer
   using OC and SC tests
2
3 clc;
4 clear;
5
6 E1=200;
7 E2=400;
8
9 n=E2/E1; // Transformation ratio
10
11 // O.C Calculations
12 V1=200;
13 Ioc=0.7;
14 Pi=70;
15
16 R0=(V1^2)/Pi;
17
18 Iw=V1/R0;
19
20 Im=sqrt((Ioc^2)-(Iw^2));
21
22 X0=V1/Im;
23
24 //S.C Calculations on HT side
25
26 Pc=80;
```

```

27 I=10;
28 V=15;
29
30 Rth= Pc/(I^2);
31 Z=V/I;
32
33 Xth=sqrt((Z^2)-(Rth^2));
34
35 // Both these value are referred to HT side , but the
   answer is required to be referred to LT side
36
37 Xtl=Xth/(n^2); // Reactance referred to LT side
38 Rtl=Rth/(n^2); // Resistance referred to LT side
39
40 printf('The Circuit parameters referred to LT side
   is as follows \n')
41
42 printf('Ro = %f ohms \n Xo = %f ohms \n Rt = %f ohms
   \n Xt = %f ohms \n',R0,X0,Rtl,Xtl)

```

---

**Scilab code Exa 5.8** To calculate terminal voltage and current and efficiency

```

1 // To calculate terminal voltage and current and
   efficiency
2
3 clc;
4 clear;
5
6 n=10; // Transformation ratio
7
8 E1=200;
9
10 R0=400;
11 X0=251*%i;

```

```

12
13 R1=0.16;
14 X1=0.7*%i;
15
16 R2=5.96; // As referred to the primary side
17 X2=4.44*%i; // As referred to the primary side
18
19 I1=E1/(R1+R2+X1+X2);
20
21 t1=atand(imag(I1)/real(I1)); // Angle for primary
   current
22
23 Iw=E1/R0;
24 Im=E1/X0;
25
26 Ip=Iw+Im+I1;
27
28 Zl=R2+X2;
29
30 V2p=I1*Zl; // Secondary terminal voltage referred to
   primary side
31
32 V2=n*V2p;
33
34 t2=atand(imag(V2)/real(V2)); // Angle for V2
35
36 Po= (abs(I1)^2)*R2; // Output power
37
38 Pc=(abs(I1)^2)*R1; // Copper Loss
39
40 Pil=(abs(Iw)^2)*R0; // Iron Loss
41
42 eff= Po*100/(Po+Pc+Pil) // Efficiency
43
44 printf('a) The secondary terminal voltage = %f /-%f
   V \n',abs(V2),t2)
45 printf('b) The primary current = %f /-%f A \n',abs(
   I1),t1)

```

```
46 printf('c) The efficiency is %f percent \n',eff)
```

---

### Scilab code Exa 5.9 Regulation at full load pf lag

```
1 // Regulation at full load p.f 0.8 lag
2
3 clc;
4 clear;
5
6 Pi=500*(10^3); // Power Input
7 Meff=97/100; // Max Efficiency
8 pf1=1;
9
10 E1=3300;
11 E2=500;
12
13 Po=Pi*pf1*3/4;
14
15 // Iron loss = Copper loss at maximum efficiency
16
17 x=poly([0 1], 'x', 'c');
18
19 Pin=Po+(2*x);
20
21 xx=(Pin*Meff)-Po;
22
23 x=roots(xx); // Iron Loss = Copper Loss
24
25 I2=Po/E2;
26
27 R=x/(I2^2);
28
29 I2fl=Pi/E2;
30
31 Rfl=E2/I2fl;
```

```

32
33 // Per unit values
34 Rpu=R*100/Rfl;
35 Zpu=10;
36 Xpu=sqrt((Zpu^2)-(Rpu^2));
37
38 pf2=0.8; // Lagging
39
40 ang=acosd(pf2); // Positive Angle as it is lagging
41
42 perreg=(Rpu*cosd(ang))+(Xpu*sind(ang));
43
44 printf('The regulation at full load , p.f 0.8 lag =
%f percent\n',perreg)

```

---

**Scilab code Exa 5.10** Calculate efficiency on unity pf at different cases

```

1 // Calculate efficiency on unity pf at different
   cases
2
3 clc;
4 clear;
5
6 Pi=25*(10^3);
7
8 E1=2000;
9 E2=200;
10
11 Pil=350;
12 Pc=400;
13
14 // Full load efficiency
15
16 nfl=Pi*100/(Pi+Pil+Pc);
17

```

```

18 // Half Load efficiency
19
20 Pihl=Pi/2; // Half Load
21 nhl=Pihl*100/(Pihl+Pil+(Pc/4));
22
23 // Load at which maximum efficiency occurs
24
25 Pimpl=sqrt(Pil/Pc)*Pi;
26 Pcm=Pc*((Pimpl/Pi)^2);
27
28 printf('a) Efficiency at full load = %f percent \n',
29      nfl)
30 printf('b) Efficiency at half load = %f percent \n',
31      nhl)
32 printf('c) Maximum Efficiency will occur at %f KVA
33      and the losses are each %d watt. \n',(Pimpl/1000),
34      Pcm)

```

---

### Scilab code Exa 5.11 Calcualte efficiencies at various loads

```

1 // Calcualte efficiencies at various loads
2
3 clc;
4 clear;
5
6 P=100*(10^3); // Power Input
7 Pc=1000; // Copper Loss
8 Pil=1000; // Iron Loss
9 pf=0.8;
10
11 deff('y=unity(x)', 'y=(P*100*x)/((P*x)+Pil+(Pc*(x^2)))
12      ') // Unit Power Factor
12 deff('y=pfactor(x)', 'y=(P*100*x*pf)/((P*pf*x)+Pil+
13      Pc*(x^2)))'') // 0.8 p.f

```

```

14 printf('a) Unity power factor efficiencies at \n \n')
      )
15 printf('i) Half of full load = %f percent \n',unity
      (1/2))
16 printf('ii) Full load = %f percent \n',unity(1))
17 printf('iii) (5/4) of full load = %f percent \n \n',
      unity(5/4))
18
19
20 printf('b) 0.8 power factor efficiencies at \n \n')
21 printf('i) Half of full load = %f percent \n',
      pfactor(1/2))
22 printf('ii) Full load = %f percent \n',pfactor(1))
23 printf('iii) (5/4) of full load = %f percent \n',
      pfactor(5/4))

```

---

**Scilab code Exa 5.12** To determine all day efficiency

```

1 // To determine all day efficiency
2
3 clc;
4 clear;
5
6 p=15*(10^3);
7 t1=12;
8 t2=6;
9 t3=6;
10
11 pf1=0.5;
12 pf2=0.8;
13 pf3=0.9;
14
15 x=poly([0 1], 'x', 'c');
16
17 nm=0.98; // Max Efficiency

```

```

18
19 y=(nm*(p+(2*x)))-p;
20
21 x=roots(y); // To find the iron loss or copper loss
   at unity p.f for maximum efficiency
22
23 Pil=x; // Iron loss
24
25 Pc=x; // Copper Loss at unity p.f for maximum
   efficiency
26
27 def('a=culoss(b,c)', 'a=b*Pc*((c/(p/1000))^2)');
28
29 Pc1=culoss(12,(2/pf1)); // Total Copper Loss for 12
   hrs - 2 kW at p.f 0.5
30 Pc2=culoss(6,(12/pf2)); // Total Copper Loss for 6
   hrs - 12 kW at p.f 0.8
31 Pc3=culoss(6,(18/pf3)); // Total Copper Loss for 6
   hrs - 18 kW at p.f 0.9
32
33 Po=((12*2)+(6*12)+(6*18))*(10^3); // Power Output
34
35 eff=Po*100/(Po+(Pc1+Pc2+Pc3)+(24*Pil));
36
37 // Note the iron loss has to be considered to
   calculate the Efficiency , Text Error
38
39 printf('The all day efficiency = %f percent \n',eff)

```

---

### Scilab code Exa 5.13 Calculating Efficiency using Sumpner test

```

1 // Calculating Efficiency using Sumpner test
2
3 clc;
4 clear;

```

```

5
6 P=200*(10^3);
7
8 W1= 4*(10^3); // Total iron loss for both the
      transformers
9 W2= 6*(10^3); // Total copper loss for both the
      transformers
10
11 n=P*100/(P+(W1/2)+(W2/2));// Efficiency
12
13 printf('The Efficiency of each transformer at full
load = %f percent \n',n)

```

---

**Scilab code Exa 5.14** To determine the ratio of weights of copper

```

1 // To determine the ratio of weights of copper
2
3 clc;
4 clear;
5
6 n=3; //transformation ratio
7
8 // Ratio of weights of copper in an ato transformer
     and a two winding transformer
9
10 roc=(1-(1/n));
11
12 printf('Ratio of weights of copper in an ato
transformer and a two winding transformer = %f \n
',roc)

```

---

**Scilab code Exa 5.15** To find voltage ratio and output

```

1 // To find voltage ratio and output
2
3 clc;
4 clear;
5
6 E1=11500;
7 E2=2300;
8
9 n1=(E1+E2)/E1; // Voltage ratio of 13.8 kV/11.5 kV
      auto transformer
10
11 Pi=100*(10^3);
12
13 P1=Pi*n1/(n1-1);
14
15 n2=(E1+E2)/E2; // Voltage ratio of 13.8 kV/2.3 kV
      auto transformer
16
17 P2=Pi*n2/(n2-1);
18
19 printf('The transformation ratio of the auto
      transformer is %g and is rated %g / %g kV, %g KVA
      \n',n1,(E1+E2)/1000,E1/1000,P1/1000)
20 printf('The transformation ratio of the auto
      transformer is %g and is rated %g / %g kV, %g KVA
      \n',n2,(E1+E2)/1000,E2/1000,P2/1000)

```

---

**Scilab code Exa 5.16** Determine primary and secondary voltages and current

```

1 // Determine primary and secondary voltages and
   current
2
3 clc;
4 clear;

```

```

5
6 R1=100;
7 R2=40;
8
9 P=2; // Power
10
11 r=sqrt(R2/R1); // n2/n1 Turns ratio
12
13 if(r<1)
14     printf(' The turns ratio is 1 : %g \n',(1/r));
15 else
16     printf('The turns ratio is %g : 1 \n',r);
17 end
18
19 V1=sqrt(P*(R1));
20 V2=sqrt(P*(R2));
21
22 I1=V1/R1;
23 I2=V2/R2;
24
25 printf('\n Voltages are as follows \n')
26 printf('The primary voltage = %g V \n',V1)
27 printf('The secondary voltage = %g V \n',V2)
28 printf('\n Currents are as follows \n')
29 printf('The primary current = %g A \n',I1)
30 printf('The secondary current = %g A \n',I2)

```

---

**Scilab code Exa 5.17** Equivalent resistance and leakage reactance wrt primary

```

1 // Equivalent resistance and leakage reactance wrt
   primary
2
3 clc;
4 clear;

```

```

5
6 P=1200;
7 V=60;
8 I1=100;
9 R1eq=P/(I1^2);
10
11 Zeq=V/I1;
12
13 X1eq=sqrt((Zeq^2)-(R1eq^2));
14
15 // Secondary short circuited there the parameters
   calculated are wrt to primary itself
16
17 printf('Equivalent Resistance of the transformer w.r
   .t primary = %g ohms \n',R1eq)
18 printf('Leakage Reactance of the transformer w.r.t
   primary = %g ohms \n',X1eq)// Text Book Error
   Please note

```

---

**Scilab code Exa 5.18** To determine Input current and voltage during SC test

```

1 // To determine Input current and voltage during SC
   test
2
3 clc;
4 clear;
5
6 Vh=6600;
7 Vl=250;
8 V=400;
9
10 a=Vh/Vl; // Turns ratio
11
12 Rh=0.21;

```

```

13 Rl=2.72*(10^-4);
14
15 Xh=1;
16 Xl=1.3*(10^-3);
17
18 Rt=Rh+Rl*(a^2); // Equivalent resistance w.r.t the
                     primary
19 Xt=Xh+Xl*(a^2); // Equivalent reactance w.r.t the
                     primary
20
21 ZHeq= sqrt((Rt^2)+(Xt^2));
22
23 Ih=V/ZHeq; // Current on high voltage side
24
25 Pi=(Ih^2)*Rt; // Power input
26
27 printf('W.R.T High Voltage side the equivalent
           resistance is %g ohms and the equivalent
           reactance is %g ohms \n',Rt,Xt)
28
29 printf('The current on the high voltage side is %g A
           \n',Ih)
30
31 printf('Power Input on the high voltage side is %g
           kW \n',Pi/1000)

```

---

**Scilab code Exa 5.19** To determine the load for max efficiency at two power factors

```

1 // To determine the load for max efficiency at two
   power factors
2
3 clc;
4 clear;
5

```

```

6 P=100*(10^3); // Power Input
7
8 E1=1000;
9 E2=10000;
10
11 Pil=1200;
12
13 I2=P/E2; // Full load current on the HV side
14
15 Isc=6; // Current for 500W copper loss in HV winding
16 Psc=500; // Copper Loss for 6A in HV winding
17
18 Pc=((I2/Isc)^2)*Psc; // Copper loss at full load.
19
20 Pmax=sqrt(Pil/Pc)*P; // Is a factor of square root
    of the ratio of Iron loss and Copper loss at full
    load.
21
22 def(x=eff(y,z)',x=(P*y*z)*100/((P*y*z)+Pil+(Pc*(z
    ^2)))')// Function to find the efficiency for a
    given power factor(y) and load(z).
23
24 printf('a) The Efficiency at various loads for unity
    power factor are as follows. \n')
25 printf('i) At 25 percent load = %f percent \n',eff
    (1,0.25))
26 printf('ii) At 50 percent load = %g percent \n',eff
    (1,0.5))
27 printf('iii) At 100 percent load = %g percent \n',
    eff(1,1))
28
29 printf('\n b) The Efficiency at various loads for
    0.8 power factor are as follows. \n')
30 printf('i) At 25 percent load = %g percent \n',eff
    (0.8,0.25))
31 printf('ii) At 50 percent load = %g percent \n',eff
    (0.8,0.5))
32 printf('iii) At 100 percent load = %g percent \n \n'

```

```

        ,eff(0.8,1))
33
34 printf('The Load at which efficiency is maximum = %g
          kVA \n',(Pmax/1000))

```

---

**Scilab code Exa 5.20** To determine the max regulation and the pf at which it occurs

```

1 //To determine the max regulation and the pf at
   which it occurs
2
3 clc;
4 clear;
5
6 Vr=2.5;
7 Vx=5;
8
9 printf('The expression for voltage regulation is y=
          %g cos(phi) + %g sin(phi) \n',Vr,Vx )
10
11 printf('Differentiating w.r.t phi and equating it to
           zero , we get the power factor angle \n')
12
13 printf('We get tan(phi)=> Vr/Vx => 5/2.5 => 2 \n \n'
           )
14
15 phi=atand(Vx/Vr); // power factor angle
16
17 y= Vr*cosd(phi)+Vx*sind(phi); // Max Volatge
   regulation
18
19 printf('The maximum regulation is %g percent \n and
           the power factor at which it occurs is %g degrees
           \n',y,phi)

```

---

**Phasor Diagrams for example 5.21**

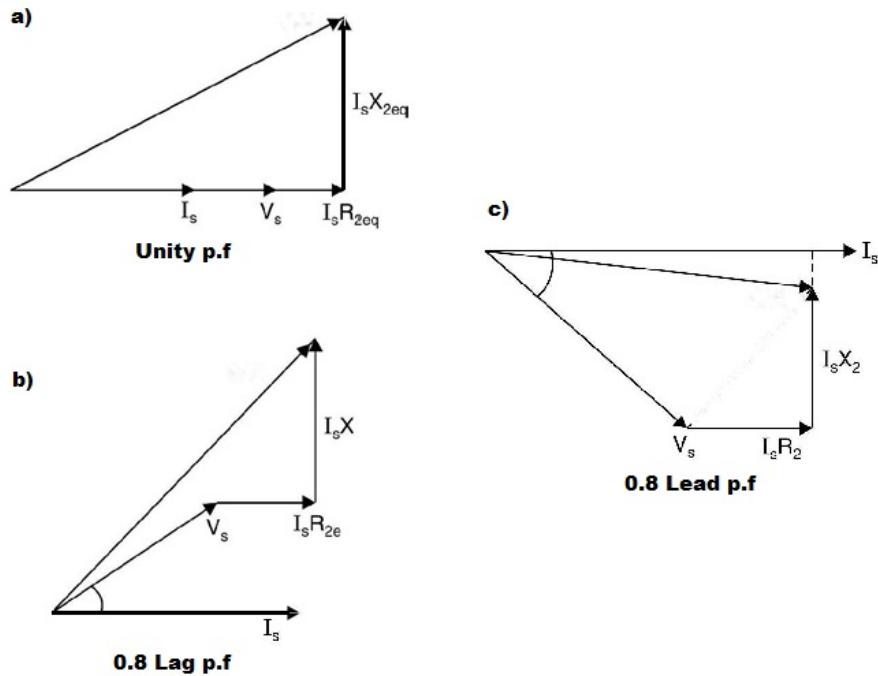


Figure 5.1: To calculate secondary terminal voltage and full load efficiency at unity pf

**Scilab code Exa 5.21** To calculate secondary terminal voltage and full load efficiency at unity pf

```

1 //To calculate secondary terminal voltage and full
   load efficiency at unity pf
2
3 clc;
```

```

4  clear;
5
6  P=4*(10^3);
7  E1=200;
8  E2=400;
9
10 // O.C Test
11 V=200;
12 Pil=70; // Iron Loss
13 Ioc=0.8;
14
15 R0=(V^2)/Pil;
16
17 Iw=V/R0;
18 Im=sqrt((Ioc^2)-(Iw^2));
19
20 X0=V/Im;
21
22 // S.C Test
23 Vsc=17.5;
24 Isc=9;
25 Psc=50;
26
27 R2eq=Psc/(Isc^2);
28
29 Z2eq=Vsc/Isc;
30
31 X2eq=sqrt((Z2eq^2)-(R2eq^2));
32
33 Is=P/E2; // Full load current
34
35 Pc=((Is/Isc)^2)*Psc;
36
37 fleff=(P*100)/(P+Pil+Pc); // Full load efficiency
38
39 printf('i) The Full load efficiency at unity power
       factor = %g percent \n \n',fleff)
40

```

```

41 // Secondary Terminal voltages cosidering full load
   secondary current as reference
42
43 Vs=poly([0 1], 'Vs', 'c');
44
45 Vz=Is*(R2eq+(X2eq*%i));
46
47 // Using the characteristic equation in polar form ,
   'Is' as reference
48 // E = V/_theta + Is/_0 *(Z/_phi)
49
50 // Function to evaluate the right side of the
   equation in complex form
51 def('a=stv(b)', 'a=Vs*(complex(cosd(b),sind(b)))+Vz',
      )
52
53 case1=stv(acosd(1));
54 case2=stv(acosd(0.8));
55 case3=stv(-acosd(0.8));
56
57 // Funtion to calculate the characteristic equation
   of Vs
58 def('x=svol(y)', 'x=(real(y)^2)+(imag(y)^2)-(E2^2)')
59
60 cs1=svol(case1);
61 cs2=svol(case2);
62 cs3=svol(case3);
63
64 // Roots of the characteristic equations
65
66 r1=roots(cs1);
67 r2=roots(cs2);
68 r3=roots(cs3);
69
70
71 // To find the positive roots
72 if(imag(sqrt(r1(1))))
73   Vs1=r1(2);

```

```

74 else
75     Vs1=r1(1);
76 end
77
78 if(imag(sqrt(r2(1))))
79     Vs2=r2(2);
80 else
81     Vs2=r2(1);
82 end
83
84 if(imag(sqrt(r3(1))))
85     Vs3=r3(2);
86 else
87     Vs3=r3(1);
88 end
89
90 printf('ii) The Secondary terminal voltages for
         various power factors are as follows \n')
91 printf('a) At Unity power factor , Vs = %g V \n',Vs1)
92 printf('b) At 0.8 power factor (Lagging) , Vs = %g V \
         \n',Vs2)
93 printf('c) At 0.8 power factor (Leading) , Vs = %g V \
         \n',Vs3)

```

---

# Chapter 6

## DC Machines

**Scilab code Exa 6.1** To Determine the useful flux per pole

```
1 //To Determine the useful flux per pole
2
3 clc;
4 clear;
5
6 E=600;
7 N=1200;
8 Z=250;
9 A=2;
10 P=6;
11
12 // EMF Equation
13
14 phi=E*A*60/(N*Z*P); // Flux developed
15
16 printf('The useful flux per pole = %g Wb \n',phi)
```

---

**Scilab code Exa 6.2** Determine the EMF generated

```
1 // Determine the EMF generated
2
3 clc;
4 clear;
5
6 phi=40*(10^-3);
7 A=8; //Lap Winding
8 P=8;
9 N=400;
10 Z=960;
11
12 E=P*N*Z*phi/(60*A); // EMF equation of a DC machine
13
14 printf('The EMF generated = %g volts \n',E)
```

---

**Scilab code Exa 6.3** Determine the EMF generated in a wave winding

```
1 // Determine the EMF generated in a wave winding
2
3 clc;
4 clear;
5
6 phi=40*(10^-3);
7 A=2; //Wave Winding
8 P=8;
9 E=400;
10 Z=960;
11
12 N=E*60*A/(phi*Z*P) // EMF equation of a DC machine
13
14 printf('The speed generated = %g rpm \n',N)
```

---

**Scilab code Exa 6.4** Ratio of speeds of a generator and motor

```

1 //Ratio of speeds of a generator and motor
2
3 clc;
4 clear;
5
6 V=250;
7 Il=80;
8 Ra=0.12;
9 Rf=100; // Field Resistance
10
11 Ish=V/Rf; // Field Current
12
13 Ia1=Il+Ish; // Machine Current generated
14 Ia2=Il-Ish; // Motor Current taken by the motor
15
16 E=V+(Ia1*Ra); // Generator Induced EMF
17
18 Eb=V-(Ia2*Ra); // Motor Operating EMF
19
20 //Speeds are directly proportional to the EMFs
21
22 Nr=E/Eb; // Ratio of speeds
23
24 printf('The ratio of Generator speed to motor speed
 = %g \n',Nr)

```

---

**Scilab code Exa 6.5 Calculate Load Current in a shunt generator**

```

1 // Calculate Load Current in a shunt generator
2
3 clc;
4 clear;
5
6 E=127;
7 V=120;

```

```

8 Ra=0.02;
9 Rf=15; // Field Resistance
10
11 Ish=V/Rf;
12
13 Ia=(E-V)/Ra;
14
15 Il=Ia-Ish;
16
17 printf('The load current = %g A \n',Il)

```

---

**Scilab code Exa 6.6** Useful Flux per pole on no load shunt motor

```

1 //Useful Flux per pole on no load shunt motor
2
3 clc;
4 clear;
5 V=250;
6 Z=2*110; // One turn is two conductors
7 Ia=13.3;
8 N=908;
9 Ra=0.2;
10 A=2; //Wave Winding
11 P=6;
12
13 Eb=V-(Ia*Ra); // Back EMF
14
15 phi=Eb*60*A/(N*Z*P);
16
17 printf('The useful flux per pole on no load of a 250
      V, 6 pole shunt motor = %g mWb \n',phi*1000)

```

---

**Scilab code Exa 6.7** To find efficiency and useful torque

```

1 //To find efficiency and useful torque
2
3 clc;
4 clear;
5
6 V=500;
7 N=600/60; // Rotation per second
8 I=18;
9 Hp=735.5; // The Value of one horse power is 735.5 W
10 Pd=10*Hp; // Power Output
11
12 Pi=V*I; // Power input
13
14 eff=Pd*100/Pi; // Efficiency
15
16 //Power ouput electrical = Power mechanical = Po= 2*
    pi*N*T
17 T=Pd/(2*pi*N);
18
19 printf('The efficiency of the shunt motor = %g
    percent \n',eff)
20 printf('Useful torque = %g Nm \n',T)

```

---

### Scilab code Exa 6.8 Speed calculation of series motor

```

1 // Speed calculation of series motor
2
3 clc;
4 clear;
5
6 N1=800; // Speed in Case 1
7 Ra=1;
8 I=15;
9 V=200;
10 Rs=5; // Series resistance

```

```

11
12 Eb1=V-(I*Ra); // Back Emf in Case 1
13 Eb2=V-(I*(Ra+Rs)); // Back Emf in case 2
14
15 //Speed directly proportional to EMF
16
17 N2=Eb2*N1/Eb1;
18
19 printf("The speed of the motor when connected in
series to a resistance of 5 ohms = %g rpm \n",N2)

```

---

**Scilab code Exa 6.9** Parameters calculated due to armature reaction

```

1 // Parameters calculated due to armature reaction
2
3 clc;
4 clear;
5
6 P=8;
7 Z=960;
8 A=2; //Wave Winding
9
10 Ia=100;
11
12 cmti=Ia*Z/(2*A*P); // Total number of magnetising
turns
13
14 def( 'y=dm( x )' , 'y=cmti*2*x/180' )// Function to find
out demagnetising ampere turns
15
16 // The demagnetising and cros magnetising ampere
turns of the three cases respectively
17
18 DM1=ceil(dm(0));
19 CM1=cmti-DM1;

```

```

20
21
22 DM2=ceil(dm(10)); // To avoid decimal error ceil is
   used
23 CM2=cmti-DM2;
24
25
26 DM3=ceil(dm(10*4)); // Mechanical degree * no of
   pair of poles = Electrical degree
27 CM3=cmti-DM3;
28
29 printf('i) Brushes along GNP. \n Demagnetising and
   cross magnetising ampere turns are %g AT/pole and
   %g AT/pole respectively \n\n',DM1,CM1)
30
31 printf('ii) Brushes are shifted by 10 electrical
   degress. \n Demagnetising and cross magnetising
   ampere turns are %g AT/pole and %g AT/pole
   respectively \n\n',DM2,CM2)
32
33 printf('iii) Brushes are shifted by 10 mechanical
   degress. \n Demagnetising and cross magnetising
   ampere turns are %g AT/pole and %g AT/pole
   respectively \n\n',DM3,CM3)

```

---

### Scilab code Exa 6.10 Number of conductors of compensating winding

```

1 //Number of conductors of compensating winding
2
3 clc;
4 clear;
5
6 P=8; // No of Poles
7 Z=960; // No of conductors
8 ep=70/100; // Effective pole pitch

```

```

9
10 Zp=Z/P; // No os conductors per pole
11
12 AZp= ep*Zp; // No of actice armature conductors
13
14 Zpc=ceil(AZp/P); // Conductors in compensating
   winding
15
16 printf('The number of conductors of compensating
   winding = %g conductor/pole \n',Zpc)

```

---

### Scilab code Exa 6.11 Swinburne test on a dc shunt motor

```

1 //Swinburne test on a dc shunt motor
2
3 clc;
4 clear;
5
6 V=500;
7 I=5;
8 Rf=250;
9 Ra=0.5;
10
11 P=V*I;
12 If=V/Rf;
13
14 Ia=I-If;
15
16 Pfc=(If^2)*Rf;// Field Copper Loss
17
18 Pac=(Ia^2)*Ra; // Armature Copper Loss
19
20 Pil=P-Pfc-Pac;// Iron loss
21
22 // Generator

```

```

23
24 Vg=500;
25 Ig=100;
26
27 Pog=Vg*Ig; // Power Output
28
29 Iag=Ig+If; //Armature current
30
31 Pgac=(Iag^2)*Ra; // Armature Copper loss
32
33 slg=0.01*Pog; //stray loss
34
35 Pgtl=Pgac+Pfc+slg+Pil; // Total losses
36
37 effg=Pog*100/(Pog+Pgtl);
38
39 // Motor
40
41Vm=500;
42 Im=100;
43
44 Pim=Vm*Im; // Power input to the motor
45
46 Iam=Ig-If; // Armature current
47
48 Pmac=(Iam^2)*Ra; // Armature Copper Loss
49
50 Pom=Pim-Pmac-Pil-Pfc; // Ouput of the motor
51 slm=0.01*Pom; // Stray loss
52
53 Pmtl=Pmac+Pil+Pfc+slm; // Total loss of the motor
54
55 effm=(Pom-slm)*100/(Pim);
56
57
58 printf('i) The Efficiency of the machine as a
      generator delivering 100A at 500V = %g percent \n
      ',effg)

```

```
59
60 printf('ii) The Efficiency of the machine as a motor
      having a line current 100A at 500V = %g percent
      \n',effm)
```

---

### Scilab code Exa 6.12 Speed of a belt driven shunt generator

```
1 //Speed of a belt driven shunt generator
2
3 clc;
4 clear;
5
6 Pg=100*(10^3); // Power output of the generator
7 Pm=10*(10^3); // Power input of the motor
8 V=220;
9 Ng=300; // Running speed of the generator
10 Ra=0.025; // Armature resistance
11 Rf=60; // Field Resistance
12 Vb=2; // Voltage drop due to brushes
13
14 Im=Pm/V; // Current taken by the motor
15 Ig=Pg/V; // Current delivered by the generator
16
17 Eg=V+(Ig*Ra)+Vb; // Induced EMF of generator
18
19 Eb=V-(Im*Ra)-Vb; // Back EMF of the motor
20
21 Nm=Eb*Ng/Eg;
22
23 printf('The Speed under motoring condition = %g rpm
      \n',Nm)
```

---

**Scilab code Exa 6.13** Voltage between feeder and bus bar in a series generator

```
1 // Voltage between feeder and bus bar in a series
   generator
2
3 clc;
4 clear;
5
6 V=50;
7 I=200;
8
9 Rf=0.3; // Feeder resistance
10
11 // Various Currents
12 I1=160;
13 I2=50;
14
15 deff( 'y=vol(x)' , 'y=(x*Rf)-(V*x/I)' ) // Function to
   calculate the voltages
16
17 Va=vol(I1);
18 Vb=vol(I2);
19
20 printf('The voltage between the far end of the
   feeder and the bus bar at a current of \n')
21 printf('a) 160A = %g V \n',Va)
22 printf('b) 50A = %g V \n',Vb)
```

---

**Scilab code Exa 6.14** Induced EMF and Armature current in a long shunt compound generator

```
1 // Induced EMF and Armature current in a long shunt
   compound generator
2
```

```

3 clc;
4 clear;
5
6 I1=50; // Load Current
7 V1=500; // Load Voltage
8 Ra=0.05; // Armature Resistance
9 Rfs=0.03; // Series Field Resistance
10 Rfp=250; // Shunt Field Resistance
11 Vb=2; // Contact drop
12
13 Ish=V1/Rfp;
14
15 Ia=I1+Ish;
16
17 E=V1+(Ia*(Ra+Rfs))+Vb; // Induced EMF
18
19 printf('The Induced EMF and Armature Current is %g V
and %g A respectively \n',E,Ia)

```

---

**Scilab code Exa 6.15** Speed at 50A considering armature reaction of a shunt motor

```

1 //Speed at 50A considering armature reaction of a
shunt motor
2
3 clc;
4 clear;
5
6 N=1000; // Speed at No load
7 I=5; // Current at no load
8 V=250;
9 Ra=0.2; // Armature Resistance
10 Rf=250; // Field Resistance
11
12 Ish=V/Rf; // Field Current

```

```

13
14 Ia=I-Ish; //Armature Current at no load
15 Eb=V-(Ia*Ra); // Back EMF at no load
16 Il=50; // Current taken when loaded
17
18 Ebl=V-(Il-Ish)*Ra; // Back EMF when loaded
19
20 Nl=Ebl*N/(0.97*Eb)
21
22 printf('The Speed at 50A considering weakening of
           the field due to armature reaction = %g rpm \n',
           ceil(Nl) )

```

---

**Scilab code Exa 6.16** Speed of shunt motor taking 50kW input

```

1 // Speed of shunt motor taking 50kW input
2
3 clc;
4 clear;
5
6 Pog=50*(10^3); // Power output of the generator
7 Ng=400; // Speed of the generator
8 Vg=250;
9 Ra=0.02;
10 Rf=50;
11
12 Pim=50*(10^3); // Power Input of motor
13Vm=250;
14
15 Vb=2; // Contact drop
16
17 // Generator
18
19 Ish=Vg/Rf; // Field Current
20 Ilg=Pog/Vg; // Load Current

```

```

21 Iag=Ish+Ilg; // Armature Current
22
23 Eg=Vg+(Iag*Ra)+Vb;
24
25 // Motor
26
27 Ilm=Pim/Vm; // Input Current
28 Ish=Vm/Rf; // Field Current
29 Iam=Ilm-Ish; // Armature Current
30
31 Eb=Vm-(Iam*Ra)-Vb; // Back EMF
32
33 Nm=Eb*Ng/Eg;
34
35 printf('The speed of shunt generator as a motor = %g
           rpm',ceil(Nm))

```

---

### Scilab code Exa 6.17 Useful torque and efficiency of a shunt motor

```

1 //Useful torque and efficiency of a shunt motor
2
3 clc;
4 clear;
5
6 Po=10.14*735; // 1 HP is 735 W, Power Developed
7 N=600/60; // Speed in rotations per sec
8 I=18;
9 V=500;
10 Pi=V*I; // Power input
11
12 eff=Po*100/Pi;
13
14 T=Po/(2*pi*N);
15
16 printf('The Efficiency and the useful torque of the

```

shunt motor are %g percent and %g Nm respectively  
\n', eff, T)

---

**Scilab code Exa 6.18** Total torque developed in a 4 pole shunt motor

```
1 //Total torque developed in a 4 pole shunt motor
2
3 clc;
4 clear;
5
6 P=4;
7 A=4; // Lap Winding
8 Z=60*20; // Slots * no of conductors in each slot
9 phi=23*(10^-3);
10 Ia=50; // Armature current
11
12 printf('The eqaution to find out torque is given by
    \n \n 2*pi*N*T = phi*Z*P*N/(60*A) * Ia \n\n')
13 T=((phi*Z*P*Ia)/(60*A))/(2*pi/60);
14
15 printf('Total torque developed = %g Nm \n',T)
```

---

**Scilab code Exa 6.19** EMF and copper losses of a Shunt Motor

```
1 //EMF and copper losses of a Shunt Motor
2
3 clc;
4 clear;
5
6 V=250;
7 I=200;
8 Ra=0.02; // Armature Resistance
9 Rf=50; // Field Resistance
```

```

10 Pil=950; // Iron and frictional losses
11
12 Ish=V/Rf; // Field Current
13 Ia=Ish+I; // Armature Current
14
15 Pac=(Ia^2)*Ra; // Armature copper loss
16 Pfc=(Ish^2)*Rf; // Field copper loss
17
18 Pc=Pac+Pfc;
19
20 E=V+(Ia*Ra);
21
22 Prime=(V*I)+Pil+Pc; // Ouput of prime mover is the
    input to the generator
23
24 eff=(V*I*100)/Prime;
25
26 printf('i) The EMF generated = %g V \n',E)
27 printf('ii) Total Copper Loss = %g watts \n',Pc)
28 printf('iii) Output of the prime mover is %g watts
    and the efficiency is %g percent \n',Prime,eff)

```

---

**Scilab code Exa 6.20** Current taken by a motor at 90 percent efficiency

```

1 //Current taken by a motor at 90 percent efficiency
2
3 clc;
4 clear;
5
6 V=500;
7 N=400/60; // Speed in rotations per sec
8 eff=90/100;
9 T=195
10
11 Pd=2*pi*N*T; // Power developed by the motor

```

```

12
13 Pi=Pd/eff; // Power input to the motor
14
15 I=Pi/V;
16
17 printf('The Current taken by the motor = %g A \n',I)

```

---

**Scilab code Exa 6.21** Rated torque calculation by resistance addition

```

1 //Rated torque calculation by resistance addition
2
3 clc;
4 clear;
5
6 V=240;
7 I=40;
8 Ra=0.3;
9 N1=1500/60; // speed in rotations per sec
10 N2=1000/60;
11
12 Pi=V*I; // Power input
13
14 Pc=(I^2)*Ra; // Copper loss
15
16 Po=Pi-Pc;
17
18 T=Po/(2*pi*N1); // Rated torque
19
20 R1=V/I; // Back EMF is zero
21
22 Rex1=R1-Ra;
23
24 //Eb directly to N(speed)
25
26 Eb1500=V-(I*Ra);

```

```

27 Eb1000=N2*Eb1500/N1;
28
29 R=poly([0 1], 'R', 'c');
30
31 x=(V-Eb1000)-(I*(R+Ra)); // Characteristic equation
   to find external resistance
32
33 Rex2=roots(x);
34
35 printf('The value of the resistance to be added to
   obtain rated torque \n')
36 printf('a) At starting = %g ohms\n',Rex1)
37 printf('b) At 1000 rpm = %g ohms\n',Rex2)

```

---

### Scilab code Exa 6.22 Efficiency at full load

```

1 // Efficiency at full load
2
3 clc;
4 clear;
5
6 V=400;
7 Inl=5; // No load current
8 Ra=0.5; // Armature Resistance
9 Rf=200; // Field Resistance
10 Ifl=40; // Full load current
11
12 Ish=V/Rf; // Field Current
13
14 Psc=(Ish^2)*Rf; // Field copper loss
15
16 Prs=(V*Inl)-Psc; // Stray losses assuming no
   armature losses
17
18 Ia=Ifl-Ish; // Armature Current

```

```
19
20 Pc=(Ia^2)*Ra; // Armature copper loss
21
22 Pi=If1*V; // Power input
23
24 Po=Pi-Psc-Prs-Pc;
25
26 eff=Po*100/Pi;
27
28 printf('The efficiency at full load = %g percent \n',
,eff)
```

---

# Chapter 7

## Three Phase Synchronous Machines

**Scilab code Exa 7.1** Power delivered to 3 phase synchronous motor

```
1 //Power delivered to 3 phase synchronous motor
2
3 clc;
4 clear;
5
6 Vl=2300;
7 I1=8.8;
8 pf=0.8 // Lead Power Factor
9 theta=acosd(pf)
10
11 P=sqrt(3)*Vl*I1; // Power delivered by the pump
12
13 I=P/(sqrt(3)*Vl*pf); // Increase in Current
14
15 Pr=sqrt(3)*Vl*I*sind(theta); // kVAr supplied
16
17 printf('The Power delivered by the pump = %g kW \n',
18 P/1000)
19 printf('The Rheostat should be decreased such that
```

```

    the ammeter reads %g A \n',I)
19 printf('The kVar supplied by the motor = %g kVAr',Pr
/1000)

```

---

**Scilab code Exa 7.2** New plant pf and percent decrease in line current

```

1 //New plant pf and percent decrease in line current
2
3 clc;
4 clear;
5
6 Pmp=5000*(10^3); // Electrical load
7 pfmp=0.8; // Lag
8
9 Pim=500*735; // One horse power is 735W
10 Effim=96/100; // Efficiency of the motor
11 pfim=0.9; // Lag
12 pfsm=0.8; // Lead
13
14 Pime=Pim/Effim; // Effective power delivered by the
induction motor
15
16 deff( 'x=com(y,z)', 'x=y+(%i*y*tand(acosd(z)))' ) //
Function to find the complex powers
17
18 //Complex Powers
19 Pcmp=com(Pmp,pfmp); // Manufacturing Plant Load
20 Pcim=com(Pime,pfim); // Induction Motor
21 Pcsm=com(Pime,-pfsm); // Synchronous Machine, Minus
Sign indicates Lead
22
23 Pr=Pcmp-Pcim+Pcsm; // Plant Requirement after
replacement
24
25 pfar=real(Pr)/abs(Pr); // New Power Factor of the

```

```

    plant
26
27 Pnp=abs(Pr);
28
29 Vl=poly([0 1], 'Vl', 'c');
30
31 Io=Pmp/(pfmp*sqrt(3)*Vl);
32 In=Pnp/(sqrt(3)*Vl); // Improved Factor Value =1;
33
34 red=(Io-In)*100/Io; // Reduction percent in
    fractions
35
36 redeq=Vl-red; // Reduction percent in decimal
    characteristic equation
37
38 redper=roots(redeq(2));
39
40 printf('The New Power Factor of the plant = %g lag \
    n', pfar)
41 printf('The Percentage decrease in line current that
    will result in improved p.f = %g percent \n',
    redper)

```

---

### Scilab code Exa 7.3 kVAr rating of a synchronous condenser

```

1 //kVAr rating of a synchronous condenser
2
3 clc;
4 clear;
5
6 P=5000*(10^3); // Power delivered to the load
7 pfo=0.8; // Original Power Factor
8 pfnew=0.9; // New Power Factor
9 Pcomo=P+%i*(P*tand(acosd(pfo))); // Original Complex
    Power

```

```

10 Pcomn=P+%i*(P*tand(acosd(pfn))); //New Complex Power
11
12 Psc=abs(imag(Pcomo-Pcomn)); // Difference in kVar;
13
14 printf('The kVar rating of the synchronous condenser
      to correct the original p.f to 0.9 = %g kVar \n',
      ,Psc/1000)

```

---

**Scilab code Exa 7.4** Calculate E per phase and Current and pf

```

1 // Calculate E per phase and Current and pf
2
3 clc;
4 clear;
5
6 V=2300;
7 delta=20;
8 Pd=255*735.5; // Power delivered converted to W from
                  HP
9 Xs=10;
10 eff=90/100; // Efficiency
11
12 P=Pd/eff;
13
14 E=poly([0 1], 'E', 'c');
15
16 x=sqrt(3)*E*V*sind(delta)-(P*Xs); // Characteristic Equation to find E
17
18 E=roots(x);
19
20 Vph=V/(sqrt(3)); // Phase Voltage
21
22 I=((Vph*expm(%i*0))-(E*expm(%i*(-%pi/9))))/(%i*Xs);
                  // Current Eqaution

```

```

23
24 [Im,phi]=polar(I); // Angle in radians and magnitude
25
26 phid=(abs(phi)/pi)*180; // Power Factor Angle in
   Degrees
27
28 pf=cosd(phid);
29
30 // High Precision Answers
31 printf('a) E per phase = %g V \n',E)
32 disp('ampères ',I,'b) I =')
33 printf('\n c) p.f = %g lead \n',pf)

```

---

### Scilab code Exa 7.5 Voltage Regulation of a 3 Phase alternator

```

1 //Voltage Regulation of a 3 Phase alternator
2
3 clc;
4 clear;
5
6 Ra=0.093;
7 Xs=8.5;
8 Z=(Ra+(%i*Xs)); // Total Impedance
9
10 P=1500*(10^3); // Power delivered at full load
11 V=6.6*(10^3); // Voltage per line
12 Vph=V/(sqrt(3)); // Voltage per phase
13
14 I1=P/(sqrt(3)*V); // Full Load Current
15
16
17 // Taking voltage as reference
18 //Power Angles
19 theta1=-acos(0.8); // Negative Sign as It is lagging
20 theta2=acos(0.8);

```

```

21
22 def('a=pot(b)', 'a=Vph+((I1*expm(%i*b))*Z)') //  

    Function to find out the output phase voltage
23
24 E1=pot(theta1);
25 E2=pot(theta2);
26
27 def('y=vg(x)', 'y=(abs(x)-Vph)*100/Vph') // Function  

    to find out the voltage regulation using the  

    formula
28
29 Vreg1=vg(E1);
30 Vreg2=vg(E2);
31
32 printf('The Voltage regulation of a 3-Phase 1500 kVA  

    , 6.6 kV alternator at \n')
33 printf('i) 0.8 lag = %g percent \n', Vreg1)
34 printf('ii) 0.8 lead = %g percent \n', Vreg2)

```

---

### Scilab code Exa 7.6 Internal Voltage drop in an alternator

```

1 // Internal Voltage drop in an alternator
2
3 clc;
4 clear;
5
6 If=10;
7 Voc=900; // Open Circuit Voltage
8
9 Isc=150; // Short Circuit Current
10
11 Zs=Voc/Isc;
12
13 I=60; // Load current
14

```

```
15 Vd=I*Zs; // Internal Voltage Drop
16
17 printf('The internal voltage drop with a load
           current of 60 A = %g V \n',Vd)
```

---

# Chapter 8

## Three Phase Induction Motors

**Scilab code Exa 8.1** Find the percentage slip and poles of the motor

```
1 //Find the percentage slip and poles of the motor
2
3 clc;
4 clear;
5
6 p=12;
7 n=500;
8 nlim=1440;
9 f=p*n/120;
10 c=1;
11
12 while(c>0) // Used to find out the poles of the
               motor nearest to the full load slip
13     P=2*c;
14     N=120*f/P;
15     g=(5/100)*N;
16     if((N-nlim)>(0.05*N))
17         c=c+1;
18     else
19         c=0;
20 end
```

```
21 end
22
23 slip=(N-nlim)*100/N;
24
25 printf('The Number of poles of the induction motor
    is %g \n',P)
26 printf('The percentage slip is %g percent \n',slip)
```

---

**Scilab code Exa 8.2** To calculate motor speed and its slip

```
1 //To calculate motor speed and its slip
2
3 clc;
4 clear;
5
6 f=50;
7 sf=3/2;
8 s=sf/f;
9
10 p=8;
11 N=120*f/8;
12
13 Nr=poly([0 1], 'Nr', 'c'); // Actual Speed Variable
14
15 x=(750*s)-(750-Nr); // Equation To find the Actual
    Speed
16
17 Nr=roots(x); // Actual Speed Constant
18
19 printf('The motor runs at a speed of %g rpm and has
    a slip of %g \n',ceil(Nr),s)
```

---

**Scilab code Exa 8.3** To Calculate Parameters of a 3 phase 4 pole induction machine

```
1 // To Calculate Parameters of a 3 phase 4 pole
   induction machine.
2
3 clc;
4 clear;
5
6 V1=200;
7 R2=0.1;
8 X2=0.9;
9 f=50;
10 p=4;
11 s=4/100;
12 a=0.67; // The Ratio of rotor to stator turns
13
14 P=((a*V1)^2)*R2*(1-s)*s/(((R2)^2)+((s*X2)^2)); // 
   Power Delivered referred to the rotor side (
   Mechanical Power)
15
16 N=120*f/p; // Rated Speed
17
18 N1=N*(1-s); // Speed at 4% slip
19
20 T4=P*60/(2*pi*N1); // Total Torque at 4% slip
21
22 sm=floor((R2/X2)*1000)/1000; // Condition for
   Maximum Torque
23
24 Pmax=((a*V1)^2)*R2*(1-sm)*sm/((R2^2)+((sm*X2)^2)); //
   Power at maximum torque
25
26 Nmax=ceil(N*(1-sm)); // Speed at Maximum Torque
27
28 Tmax=Pmax*60/(2*pi*Nmax); // Maixmum Torque
29
30 // Please Note that the answers are accurate and no
```

quantities are neglected as in the text book.

---

```

31 printf('a) Total torque at 4 percent slip = %g Nm \n
      ',T4)
32 printf('b) Total Mechanical Power at 4 percent slip
      = %g watts or %g H.P \n',P,(P/735))
33 printf('c) Maximum Torque = %g Nm \n',Tmax)
34 printf('d) Speed at maximum torque = %g rpm \n',Nmax
      )
35 printf('e) Maximum Mechanical Power = %g watt or %g
      H.P \n',Pmax,(Pmax/735))

```

---

### Scilab code Exa 8.4 Calculation of slip from losses

```

1 // Calculation of slip from losses
2
3 clc;
4 clear;
5
6 eff=0.9; // Efficiency
7 P=50*735; // Load in watts
8 x=poly([0 1], 'x', 'c'); // Rotor Copper Loss Variable
9
10 tx=(x+x+x+(x/3)); // Total loss
11
12 loss=((P+tx)*eff)-P; // Equation to calculate x
13
14 x=roots(loss); // Rotor Copper Loss Constant
15
16 s=poly([0 1], 's', 'c'); // Variable for slip
17 slip=(P*s)-(x*(1-s)); // Gives the variable equation
      of slip
18
19 s=roots(slip); // Numerical Value of slip
20
21 printf('The slip of an induction motor of 0.9

```

efficiency at 50 HP load = %g \n', s)

---

**Scilab code Exa 8.5** apping of an auto transformer to limit current in squirrel cage motor

```
1 //Tapping of an auto transformer to limit current in
   squirrel cage motor
2
3 clc;
4 clear;
5
6 V=400; // Line to line voltage
7 Vph=V/sqrt(3); // Phase voltage
8 Z=1.54; // Standstill impedance
9 Ifl=30; // Full Load Current
10 Imax=75; // Max current which can be taken by the
    line
11 s=4/100; // Full load slip
12
13 t=poly([0 1], 't', 'c'); // Variable for tapping
    percent of normal voltage
14
15 Is=t*(Vph/(100*Z)); // Starting current in the motor
16
17 Ias=(t/100)*Is; // Current on supply side of the
    auto transformer
18
19 Tap=Ias-Imax; // Equation to find t
20
21 t=roots(Tap); // Numerical Value for t
22
23 if(imag(sqrt(t(1))))
24     t=t(2);
25 else
26     t=t(1);
```

```

27 end
28
29
30 Ism=Imax*100/t; // Starting current in the motor (
    Numerical Value)
31
32 st=((Ism/Ifl)^2)*s; // Starting torque to full load
    torque ratio
33
34 printf('The tapping provided to the auto transformer
        = %g percent of Normal Voltage \n',t)
35
36 printf('The starting torque available is %g times
        the full load torque \n',st)

```

---

**Scilab code Exa 8.6** To find the total mechanical power and rotor copper loss

```

1 //To find the total mechanical power and rotor
    copper loss
2
3 clc;
4 clear;
5
6 P=60*(10^3); // Power input
7 Pstat=1*(10^3); // Stator Losses
8 Pirot=P-Pstat; // Rotor Input
9 s=3/100; // Running slip
10
11 Prc=poly([0 1], 'Prc', 'c'); // Variable for rotor
    copper loss
12 // Prc = I2^2 * R2
13
14 rloss=(Pirot*s)-(3*Prc);
15

```

```

16 Prc=roots(rloss); // Numerical Value of rotor loss
    per phase;
17
18 Pm=Pirot-(3*Prc); // Mechanical power developed
19
20 printf('The rotor loss per phase = %g W \n',Prc)
21 printf('The Mechanical Power developed = %g kW \n',
    Pm/1000)

```

---

**Scilab code Exa 8.7** To determine the starting torque and current using different starters

```

1 // To determine the starting torque and current
    using different starters
2
3 clc;
4 clear;
5
6 // Rated Parameters of the motor
7 V=400; // Delta connected
8 P=50*735.5; // Power developed
9 N=750; // Speed
10
11 Ifl=50; // Full Load current
12 Z=2.5; // Impedance per phase
13 sf=4.5/100; // Slip
14 f=50;
15
16 Tfl=P*60/(2*pi*N);
17
18 deff('y=curr(x)', 'y=(sqrt(3))*x/Z');
19
20 deff('a=stor(b)', 'a=((b/If1)^2)*sf*Tfl');
21
22 //Case 1

```

```

23 I1=curr(V);
24 T1=stor(I1);
25
26 //Case 2
27 I3=curr(70*V/100);
28 T3=stor(I3);
29
30 T2=Tf1*((1/sqrt(3))^2); // Case 2 torque
31 I2=I1;
32
33 printf('The starting torque and the starting current
           using different starters are : \n')
34
35 printf('i) D.O.L starter = %g Nm and %g A \n',T1,I1)
36 printf('ii) Star-delta starter = %g Nm and %g A \n',
         T2,I2)
37 printf('iii) An auto transformer starter with 70
           percent tapping = %g Nm and %g A \n',T3,I3)

```

---

**Scilab code Exa 8.8** To actual rotor speed and the rotor frequency at 3 percent slip

```

1 // To actual rotor speed and the rotor frequency at
   3 percent slip
2
3 clc;
4 clear;
5
6 P=2;
7 f=50;
8 V=400;
9 Vph=V/sqrt(3);
10 s=3/100;
11
12 Ns=120*f/P;

```

```

13
14 Nr=Ns*(1-s);
15
16 rf=s*f; // Rotor Frequency
17
18 printf('The Actual rotor speed = %g rpm \n',Nr)
19 printf('The rotor frequency = %g Hz \n',rf)

```

---

**Scilab code Exa 8.9** To determine the various parameters of a 3 phase 400V 6 poles Induction Motor

```

1 // To determine the various parameters of a 3 phase
   400V 6 poles Induction Motor
2
3 clc;
4 clear;
5
6 f=50;
7 p=6;
8 s=3/100;
9 V=400;
10
11 N=120*f/p; // Synchronous speed
12 Ns=0; // Speed of stator
13 rf=s*f; // Rotor Frequency
14 Nr=N*(1-s); // Rotor speed
15 Nrs=N-Ns; // Speed of Rotor field wrt stator
16 Nrr=120*rf/6; // Speed of rotor field wrt rotor
17 Nrmsm=0; // Speed of rotor field wrt stator field
18
19 printf('i) The speed of the rotor = %g rpm \n',Nr)
20 printf('ii) The frequency of rotor current = %g Hz \
n',rf)
21 printf('iii) The Speed of the rotor magnetic field w
.r.t the stator = %g rpm \n',Nrs)

```

```
22 printf('iv) The speed of the rotor magnetic field w.  
r.t the rotor = %g rpm \n',Nr)  
23 printf('v) The speed of the rotor magnetic field w.r  
.t the stator magnetic field = %g rpm \n',Nrmsm)
```

---

**Scilab code Exa 8.10** To determine parameters of an 3 phase delta connected 4 pole induction motor

```
1 //To determine parameters of an 3 phase delta  
connected 4 pole induction motor  
2  
3 clc;  
4 clear;  
5  
6 V=440;  
7 f=50;  
8 p=4;  
9 E2=150;  
10 Nr=1450;  
11  
12 Ns=120*f/p;  
13  
14 s=(Ns-Nr)/Ns;  
15  
16 rf=s*f; // Rotor frequency  
17  
18 Eir=s*E2; // Rotor induced EMF per phase  
19 gc=1;  
20  
21 // To find the GCD of both the voltages  
22 for i=E2:-1:1  
23     a=modulo(V,i);  
24     b=modulo(E2,i);  
25     if(a==0&b==0)  
         gc=gc*i;
```

```

27         break;
28     end
29 end
30
31 printf('The parameters for a motor running at 1450
    rpm are \n')
32 printf('i) The slip = %g percent \n',s)
33 printf('ii) The frequency of the rotor induced EMF =
    %g Hz \n',rf)
34 printf('iii) The rotor induced EMF per phase = %g V
    \n',Eir)
35 printf('iv) Stator to rotor turn ratio = %g : %g \n'
    ,V/gc,E2/gc)

```

---

**Scilab code Exa 8.11** Determine the shaft power of 6 pole Induction Motor

```

1 // Determine the shaft power of 6 pole Induction
   Motor
2
3 clc;
4 clear;
5
6 f=50;
7 p=6;
8 rf=120/60; // Rotor Frequency
9 T=150; // Full Load torque
10
11 s=rf/f;
12
13 Ns=120*f/p;
14
15 Nr=Ns*(1-s);
16
17 Ps=2*pi*Nr*T/60; // Shaft power

```

```
18
19 printf('The shaft power of the motor = %g kW \n',Ps
/1000)
```

---

**Scilab code Exa 8.12** Motor parameters at a load power factor

```
1 // Motor parameters at a load power factor
2
3 clc;
4 clear;
5
6 p=4;
7 f=50;
8 V=400;
9 pf=0.8;
10 Nr=1440;
11 Pm=20*(10^3); // Mechanical Power Developed
12 Ns=120*f/p;
13 s=(Ns-Nr)/Ns;
14
15 rf=s*f; // Rotor frequency
16
17 Pstat=1000; // Stator Loss
18
19 // Power input to the rotor = Mechanical Power
   Developed / (1-s)
20
21 Pirot=Pm/(1-s); // Rotor Power Input
22
23 Pi=Pirot+Pstat; // Power input to stator
24
25 I1=Pi/(sqrt(3)*V*pf); // Line Current
26
27 printf('For a 4 pole motor running at 1440 rpm and
  0.8 p.f \n')
```

```
28 printf('i) Rotor Current frequency = %g Hz \n',rf)
29 printf('ii) Total input if stator loss is 1000W = %g
      kW \n',Pi/1000)
30 printf('iii) The line current = %g A \n',I1)
```

---

**Scilab code Exa 8.13** To determine the auto transformer ratio and starting torque

```
1 // To determine the auto tranformer ratio and
   starting torque
2
3 clc;
4 clear;
5
6 V=400;
7 f=50;
8 p=4;
9 sfl=4/100;
10
11 Ria=2.5; // Ratio of starting current to full load
   current (Auto transformer)
12 Rir=4; // Ratio of starting current to full load
   current ( For the Rated Voltage)
13
14 x=sqrt(Ria/Rir);
15
16 Rt=((x*Rir)^2)*sfl; // Ratio of starting torque to
   full load torque;
17
18 printf('The auto-transformer ratio = %g \n',x)
19 printf('The starting torque at the above transformer
   ratio = %g percent of full load torque \n',100*
Rt)
```

---

**Scilab code Exa 8.14** To determine the starting torque in terms of full load torque

```
1 //To determine the starting torque in terms of full
   load torque
2
3 clc;
4 clear;
5
6 sfl=4/100;
7
8 Rir=5; // Ratio of starting current to the full load
          current at rated voltage
9
10 x=70.7/100; // Auto transformer tapping
11
12 Rsd=((Rir)^2)*sfl/3; // Ratio of the starting load
          to full load torque for a star -delta starter
13
14 Ra=((x*Rir)^2)*sfl; // Ratio of the starting load to
          full load torque for an 70.7% tapped auto
          transformer
15
16 printf('The starting torque in terms of full load
          torque by \n')
17 printf('i) Star-Delta starter = %g Tfl \n',Rsd)
18 printf('ii) An auto-tranformer starter with 70.7
          percent tapping = %g Tfl \n',Ra)
```

---

**Scilab code Exa 8.15** Stator input of 3 phase 4 pole induction motor

```
1 // Stator input of 3 phase 4 pole induction motor
```

```

2
3 clc;
4 clear;
5
6 p=4;
7 f=50;
8 Pd=4000; // Power Developed
9 Nr=1440;
10 Ps=320; // Stator loss
11
12 Ns=120*f/p;
13
14 s=(Ns-Nr)/Ns;
15
16 Pir=Pd/(1-s); // Power to the rotor
17
18 Pi=Pir+Ps; // The input to the stator
19
20 printf('The stator input of a 440V 3 phase 4 pole
           induction motor = %g W \n',ceil(Pi))

```

---

**Scilab code Exa 8.16** Motor parameters of a 6 pole motor with 40 hp mechanical power

```

1 // Motor parameters of a 6 pole motor with 40 hp
   mechanical power
2
3 clc;
4 clear;
5
6 f=50;
7 p=6;
8 Pd=40*735.5; // Mechanical Power developed
9 V=500;
10 Nr=960;

```

```

11 pf= 0.8; // Lag
12 Pm=1500; // Mechanical Loss
13
14 Ns=120*f/p;
15
16 s=(Ns-Nr)/Ns;
17 Ps=1800; // Stator Loss
18
19 Po=Pd-Pm; // Power Output
20
21 Pir=Pd/(1-s); // Power input to rotor
22
23 Prc=s*Pir; // Copper Loss of the Rotor
24
25 Pi=Pir+Ps; // Power input to the stator
26
27 eff=Po*100/Pi;
28
29 I1=Pi/(sqrt(3)*V*pf); // Line Current
30
31 printf('For a 6 pole 3 phase motor at 500V with a
         power factor of 0.8 lag \n')
32 printf('i) Rotor Copper Loss = %g W \n',Prc)
33 printf('ii) Total input to stator if the stator loss
         is 1500W = %g W \n',Pi)
34 printf('iii) The line Current = %g A \n',I1)
35 printf('iv) Efficiency = %g percent \n',eff)

```

---

**Scilab code Exa 8.17** To determine parameters of 4 pole induction motor considering circuit parameters

```

1 //To determine parameters of 4 pole induction motor
   considering circuit parameters
2
3 clc;

```

```

4 clear;
5
6 R1=0.5;
7 R2=0.35;
8 X1=1.2;
9 X2=X1;
10 Xm=25;
11 f=50;
12 p=4;
13
14 Pd=25*735.5; // Power Developed
15 Prl=800; // Rotational Losses
16 V=400;
17 Vph=V/sqrt(3);
18
19 Ns=120*f/p;
20 s=2.5/100;
21 Nr=(1-s)*Ns;
22 rf=s*f; // Rotor Frequency
23
24 Z1=R1+(%i*X1);
25 Z2=(R2/s)+(%i*X2);
26 Zm=%i*Xm;
27
28 Z2m=(Zm*Z2)/(Zm+Z2);
29
30 Zeff=Z1+Z2m; // Effective Impedance
31
32 Is= Vph/Zeff; // Stator Current
33
34 Psc= 3*(abs(Is)^2)*R1; // Copper Loss in the Stator
35 Ztheta= atand(imag(Zeff)/real(Zeff)); // Phase angle
            of impedance
36 Ctheta= atand(imag(Is)/real(Is)); // Phase angle of
            current
37
38 pf= cosd(Ctheta); // Lagging Power Factor
39 Ir=Is*(Zm/(Zm+Z2)); // Rotor Current

```

```

40
41 Prc= 3*(abs(Ir)^2)*R2; // Rotor Copper Loss
42
43 Pim= sqrt(3)*V*abs(Is)*cosd(Ctheta); // Power input
     to the motor
44 Pom= Pim-Prc-Psc-Prl; // Power Output to the motor
45
46 eff=Pom*100/Pim; // Efficiency
47
48 printf('For a rotor slip of 2.5 percent at rated
          voltage and frequency \n');
49 printf('i) The motor speed = %g rpm \n',Nr)
50 printf('ii) The stator Current = %g /-%g A \n',abs(
          Is),Ctheta)
51 printf('iii) The p.f = %g lagging \n',pf)
52 printf('iv) The efficiency = %g percent \n',eff)

```

---

**Scilab code Exa 8.18** Stator Current and pf and efficiency of a motor operating at rated slip

```

1 // Stator Current and pf and efficiency of a motor
     operating at 0.03 slip
2
3 clc;
4 clear;
5
6 V=400;
7 Vph=V/sqrt(3);
8 R1=0.2;
9 R2=0.15;
10 X1=%i*0.5;
11 X2=%i*0.3;
12
13 s=3/100;
14

```

```

15 Pt1=2000; // Total Losses
16
17 Z1=R1+X1;
18 Z2=(R2/s)+X2;
19 Zt=Z1+Z2; // Total Impedance of the circuit
20
21 Is= Vph/Zt; // Stator Current
22
23 Ctheta=atand(imag(Is)/real(Is)); // Phase angle of
   stator current
24
25 pf= cosd(Ctheta); // Power factor lagging
26
27 Pi=sqrt(3)*V*abs(Is)*cosd(Ctheta);
28
29 Po=Pi-Pt1; // Power Output
30
31 eff=Po*100/Pi;
32
33 printf('For a 3 phase, 4 pole, 400V Induction Motor
          operating at 3 percent slip \n')
34 printf('i) The Stator current = %g +/-%g A \n',abs(Is
           ),Ctheta)
35 printf('ii) The p.f = %g lagging \n',pf)
36 printf('iii) The efficiency = %g percent \n',eff)

```

---

# Chapter 10

## Power System

**Scilab code Exa 10.1** Determine the additional load which can be supplied

```
1 //Determine the additional load which can be supplied
2
3 clc;
4 clear;
5
6 printf('a) D.C two wire: \nPower transmitted by DC
    two wire = P and Voltage between the wires = V\n',
)
7 printf('Copper Loss = 2 * (P/V)^2 * R ; where R is the
    resistance of each wire\n')
8 printf('Per Unit Loss = 2 * P * R / (V^2)\n\n')
9 printf('b) 3 phase 3 wire: \nPower transmitted = P',
\n')
10 printf('I' = P / (sqrt(3) * V) for unity p.f\n')
11 printf('Copper Loss = 3 * ((P / (sqrt(3) * V))^2 * R = ((P/V)^2 * R\n')
12 printf('Per Unit Loss = P * R / (V^2)\n\n')
13 printf('Equating the per unit loss we have\n')
14 printf('2 * P * R / (V^2) = P * R / (V^2) or P = 2P\n')
```

Which proves that 100 %% aditional pwer can be supplied by 3 phase 3 wire system\n')

---

**Scilab code Exa 10.2** Pf at which the slow machine will work

```
1 //Pf at which the slow machine will work
2
3 clc;
4 clear;
5
6 pf1=0.8; //Power Factor Lag (Combined)
7 Pa=2500*(10^3); // Combined Power
8 Pr=Pa*(tand(acosd(pf1))); // Combined VAr
9 Pat=1000*(10^3); // Active power of the turbo
                     alternator unity pf so no VAr
10 Prt=0;
11 Pas=Pa-Pat; // Active power of the slow speed
                 alternator
12 Prs=Pr-Prt; // Reactive power of the slow speed
                 alternator
13
14 theta=atand(Prs/Pas); // Power Factor Angle
15
16 powfac=cosd(theta); // Power factor
17
18 printf('The Power Factor of the slow speed
           alternator is %g\n',powfac)
```

---

**Scilab code Exa 10.3** Detemine the load and pf of the other machine

```
1 //Detemine the load and pf of the other machine
2
3 clc;
```

```

4 clear;
5
6 Pa=3000*(10^3); // Lighting load
7 Pma=5000*(10^3); // Aggregate Motor load
8 pfm=0.71; // power factor of motor load
9
10 P1a=5000*(10^3); // One Machine load
11 pf1=0.8; // Power factor machine 1 (lagging)
12
13 Pta=Pa+Pma; // Total load active power requirement
14
15 // Reactive power
16
17 Pr=0; // Lighting
18 Pmr=Pma*tand(acosd(pfm)); // Motor
19 P1r=P1a*tand(acosd(pf1)); // Machine 1
20
21 P2a=Pta-P1a; // Active power by other machine
22 P2r=Pr+Pmr-P1r; // Reactive power by other machine
23
24 pf2=cosd(atand(P2r/P2a)); // Power factor of other
      machine
25
26 printf('The other machine supplies:\n')
27 printf('    A load of %g kw at a p.f of %g\n', P2a
      /1000, pf2)

```

---

**Scilab code Exa 10.4** Determine the value of a shunt capacitor

```

1 //Determine the value of a shunt capacitor
2
3 clc;
4 clear;
5
6 V=440; // Line to line voltage

```

```

7 f=50; // Frequency of operation
8 w=2*pi*f; // Angular frequency
9 Vph= V/sqrt(3); // Phase voltage
10 I=40; // Magnitude of current
11 pfi=0.7; // Lagging power factor of the current
12 ti=acosd(0.7);
13
14 // Iv=I*(expm(%i*-1*pi*ti/180));
15
16 // For pf = 0.7
17 Pa=Vph*I*pfi; // Active power
18 Pr=Vph*I*sind(ti); // Reactive power
19
20 // To gain a pf of 0.9
21 pfn=0.9;
22 Pnr=Pa*tand(acosd(pfn)); // Reactive power at pf of
    0.9
23
24 PRC=Pr-Pnr; // VArs supplied from the capacitor
25
26 C=PRC/((Vph^2)*w); // Capacitance required to meet
    the condition
27
28 printf('The value of the shunt capacitor should
    raise the pf to 0.9 = %g mF\n',C*1000)

```

---

**Scilab code Exa 10.5** Calculate the inductance of a choke to enable the lamp

```

1 // Calculate the inductance of a choke to enable the
    lamp
2
3 clc;
4 clear;
5

```

```

6 P=500; // Power Rating of a discharge lamp
7 I=4; // Current drawn by the lamp
8 w=2*pi*50; // Angular frequency
9
10 Vdl=P/I; // Supply voltage for the proper working of
    the lamp
11 V=250; // AC supply voltage
12
13 //According the Voltage triangle
14
15 Vil=sqrt((V^2)-(Vdl^2)); // Voltage drop across
    inductor
16
17 Xl=Vil/I; //Reactance
18 L=Xl/w; // Inductor
19
20 Prl=(I^2)*Xl; // Reactive power requirement of the
    coke
21
22 C=Pr1/((V^2)*w); // Capacitor supplying the
    necessary reactive power
23
24 printf('The inductance that should be connected in
    series with the lamp to make it work = %g mH\n',L
    *1000)
25 printf('The capacitor that should be connected in
    parallel to make the power factor unity = %g mF \n
    ',C*1000)

```

---

# Chapter 11

## Domestic Wiring

**Scilab code Exa 11.1** Determine the size of the conductor for power and lighting circuit

```
1 // Determine the size of the conductor for power and
   lighting circuit
2
3 clc;
4 clear;
5
6 P5=3*800; // Load wattage in 5A circuit
7 P15=2*1500; // Load wattage in 15 A circuit
8
9 Pt=P5+P15; // Total Load
10
11 // Assume a average of 0.8 pf, common for
   distribution systems
12
13 pf=0.8;
14
15 V=230; // Supply voltage
16
```

Size of conductor		2 cables d.c. or single phase a.c.		3 or 4 cables or balanced three phase		Four cables d.c. or single phase a.c.	
Nominal area in Sq. mm	No. and diameter of wire in mm.	Current rating in Amperes	Approx. length of run for one volt. (M.)	Current rating in Amps.	Approx. run for one volt drop in (Mts.)	Current rating (amps.)	Approx. run for one volt drop in Mts.
1.5	1/1.40	10	2.3	9	2.9	9	2.5
2.5	1/1.80	15	2.5	12	3.6	11	3.4
4.0	1/2.24	20	2.9	17	3.9	15	4.4
6.0	1/2.80	27	3.4	24	4.3	21	4.3
10.0	1/3.55	34	4.3	31	5.4	27	5.4
16.0	7/1.70	43	5.4	38	7.0	35	6.8
25.0	7/2.24	59	6.8	54	8.5	48	8.5
35.0	7/2.50	69	7.2	62	9.3	55	9.0
50.0	[ 7/3.50 19/1.80 ]	91	7.9	82	10.1	69	10.0
70.0	19/2.24	134	8.0	131	9.5	—	—
95.5	19/2.50	153	8.8	152	10.1	—	—

Figure 11.1: Determine the size of the conductor for power and lighting circuit

Size of conductor		2 cables d.c. or single phase a.c.		3 or 4 cables or balanced three phase		Four cables d.c. or single phase a.c.	
Nominal area in Sq. mm	No. and diameter of wire in mm.	Current rating in Amperes	Approx. length of run for one volt. (M.)	Current rating in Amps.	Approx. run for one volt drop in (Mt.)	Current rating (amps.)	Approx. run for one volt drop in Mts.
1.5	1/1.40	10	2.3	9	2.9	9	2.5
2.5	1/1.80	15	2.5	12	3.6	11	3.4
4.0	1/2.24	20	2.9	17	3.9	15	4.4
6.0	1/2.80	27	3.4	24	4.3	21	4.3
10.0	1/3.55	34	4.3	31	5.4	27	5.4
16.0	7/1.70	43	5.4	38	7.0	35	6.8
25.0	7/2.24	59	6.8	54	8.5	48	8.5
35.0	7/2.50	69	7.2	62	9.3	55	9.0
50.0	[ 7/3.50 19/1.80 ]	91	7.9	82	10.1	69	10.0
70.0	19/2.24	134	8.0	131	9.5	—	—
95.5	19/2.50	153	8.8	152	10.1	—	—

Figure 11.2: Determine the size of the conductor at 25 m distance

```

17 I=Pt/(V*pf); // Current at 230 supply
18
19 Isc=1.5*I; // Short Circuit Current
20
21 printf('The Current is %g A and the short circuit
   current is %g A\n\n',I,Isc)
22 printf('From the result sheet provided along with
   this code,\n for aluminium wire the size of the
   conductor comes out to be 25 mm^2.\nIn fact for
   43 A it is 16 mm^2 but we should always go for
   one higher size of the conductor\n and hence we
   select conductor of size 25 mm^2 or 7/2.24 mm. ')
23 printf('\n \n Refer the table in the result sheet \n
   ')

```

---

**Scilab code Exa 11.2** Determine the size of the conductor at 25 m distance

```
1 //Determine the size of the conductor at 25 m
   distance
2
3 clc;
4 clear;
5
6 V=230; // Supply Voltage
7 d=25; // Distance between mains and residence
8 I=5; // Supply current
9
10 pvd=1+((2/100)*V); // Permissible Voltage drop
11
12 // From the table given in the result sheet along
   with this code , Minimum size of wire for 10A
13
14 A=1.5*(10^-6);
15
16 dm=2.3;
17 Vd=d/dm; // Voltage drop at 10A
18
19 Vd5=Vd/2; // Voltage drop at 5A
20
21 //According to the table (Refer below) Permissible
   drop is 5.6 V
22
23 printf('The permissible voltage drop = %g V\n', pvd)
24 printf('The voltage drop at 5 A = %g V\n', Vd5)
25 printf('As the permissible drop is 5.6 volts \nand
   the conductor with 1.5 mm^2 section gives \
   nvoltage drop of 5.4 volts hence the suitable
   size is 1/1.40 mm. ')
26 printf('\n \n Refer the table in the result sheet \n')
```

Size of conductor		2 cables d.c. or single phase a.c.		3 or 4 cables or balanced three phase		Four cables d.c. or single phase a.c.	
Nominal area in Sq. mm	No. and diameter of wire in mm.	Current rating in Amperes	Approx. length of run for one volt. (M.)	Current rating in Amps.	Approx. run for one volt drop in (Mt.)	Current rating (amps.)	Approx. run for one volt drop in Mts.
1.5	1/1.40	10	2.3	9	2.9	9	2.5
2.5	1/1.80	15	2.5	12	3.6	11	3.4
4.0	1/2.24	20	2.9	17	3.9	15	4.4
6.0	1/2.80	27	3.4	24	4.3	21	4.3
10.0	1/3.55	34	4.3	31	5.4	27	5.4
16.0	7/1.70	43	5.4	38	7.0	35	6.8
25.0	7/2.24	59	6.8	54	8.5	48	8.5
35.0	7/2.50	69	7.2	62	9.3	55	9.0
50.0	[ 7/3.50 19/1.80 ]	91	7.9	82	10.1	69	10.0
70.0	19/2.24	134	8.0	131	9.5	—	—
95.5	19/2.50	153	8.8	152	10.1	—	—

Figure 11.3: Size of conductor to be used for wiring a 10 kW 400V 3 Phase induction motor

)

---

**Scilab code Exa 11.3** Size of conductor to be used for wiring a 10 kW 400V 3 Phase induction motor

```

1 // Size of conductor to be used for wiring a 10 kW
   400V 3 Phase induction motor
2
3 clc;
4 clear;
5
6 P=10*(10^3); // Power Rating

```

```

7 V=400; // Voltage Rating
8 f=50; // Frequency of operation
9
10 // Assumptions Made
11 eff=85/100; // Efficiency
12 pf=0.8 // Power Factor
13
14 I=P/(sqrt(3)*V*eff*pf); // Current flowing in the
   conductor
15
16 Is=2*I; //At the time of starting the induction
   motor may take 2 times the rated current
17
18 printf('The Rated Current = %g A\n\n',I)
19 printf(' At the time of starting the induction motor
   may take\n 2 times the rated current and hence
   starting current = %g A \n\n',Is)
20
21 printf(' From the table corresponding to 42.4 A that
   is 43 A\n the wire used is 7 /1. 7 mm or 16 mm
   ^2.\n')

```

---

# Chapter 12

## DC Circuits

**Scilab code Exa 12.1** To Compute the number of electrons

```
1 // To Compute the number of electrons .
2
3 clc;
4 clear;
5
6 I=(25)*(10^-3);
7 t=(30)*(10^-3);
8 C=I*t;
9 // 1C = 6.242*(10^18)
10 n= 6.242*(10^18);
11 e_s=C*n;
12 disp(e_s, 'The Number Of Electrons passing through
the person is' )
```

---

**Scilab code Exa 12.2** Computing the Average lighting current

```
1 // Compute Average lighting current
2 clc;
```

```
3 clear;
4
5 q=20;
6 t=(10)*(10^-3);
7
8 // Coulomb's Law
9
10 I=q/t;
11
12 disp('amperes',I,'The Average Lightning current =')
```

---

**Scilab code Exa 12.3** To Calculate the average voltage

```
1 // To Calculate the average voltage.
2 clc;
3 clear;
4
5 W=500;
6 I=40;
7 t=15*(10^-3);
8
9 V=W/(I*t);
10
11 disp('volts',V,'The Average volatage across the
      terminals of the device =')
```

---

**Scilab code Exa 12.4** Calculating resistance

```
1 // Calculating resistance.
2 clc;
3 clear;
4
```

```
5 L=2.5*(10^-2); // Length of rectangular cross-
6 section .
7 B=0.05*(10^-2); // Breadth of rectangular cross-
8 section .
9 A=L*B;
10
11 p=1.724*(10^-8);
12
13 R=p*l/A;
14
15 disp('ohms',R,'The Resistance of the copper strip =' )

```

---

**Scilab code Exa 12.5** Current Calculation using ohms law

```
1 //Current Calculation using ohm's law .
2 clc;
3 clear;
4
5 V=220;
6 R=80;
7
8 // Using Ohm's Law V=I*R
9
10 I=V/R;
11
12 disp('amperes',I,'The Load Current =')
```

---

**Scilab code Exa 12.6** Determination of conductance in a short circuit

```
1 // Determination of conductance of a short circuit
```

```
2
3 clc;
4 clear;
5
6 V=120;
7 I=500;
8
9 G=I/V;
10
11 disp('siemens',G,'The Conductance =')
```

---

### Scilab code Exa 12.7 Power Rating Calculation

```
1 // Power Rating Calculation
2
3 clc;
4 clear;
5
6 V=250;
7 I=15;
8
9 // Power Equation or Watt's Law P=V*I.
10
11 P=V*I;
12
13 disp('watts',P,'The power rating of the device =')
```

---

### Scilab code Exa 12.8 To calculate current ratings and maximum voltage of a rated resistor

```
1 //To calculate current ratings and maximum voltage
   of a rated resistor.
2
```

```

3 clc;
4 clear;
5
6 P=1;
7 R=10*(10^3);
8
9 // Using Power Equation and Ohm's Law.
10
11 V=sqrt(P*R);
12
13 I=sqrt(P/R);
14
15 disp('volts',V,'The Maximum voltage of the resistor
      =')
16
17 disp('amperes',I,'The Current rating of the resistor
      =')

```

---

**Scilab code Exa 12.9** Determine the output power of the motor

```

1 //Determine the output of the motor.
2
3 clc;
4 clear;
5
6 eff=80/100;
7
8 V=220;
9 I=8;
10
11 // Power Equation P=V*I
12
13 P=V*I; // Input Power
14
15 Pout=eff*P; // Output Power

```

```
16
17 disp('watts',Pout,'The output power of the motor =')
```

---

**Scilab code Exa 12.10** Calculation of Current and power dissipated in resistors connected in series

```
1 // Calculation of Current and power dissipated in
   resistors connected in series .
2
3 clc;
4 clear;
5
6 R1=100;
7 R2=200;
8 R3=300;
9
10 Rt=R1+R2+R3;
11
12 V=250;
13
14 //Ohm's Law V=I*R
15
16 I=V/Rt;
17
18 // Power Loss Equation P=(I ^ 2)*R
19
20 P1=(I ^ 2)*R1;
21 P2=(I ^ 2)*R2;
22 P3=(I ^ 2)*R3;
23
24 Pt=P1+P2+P3;
25
26 P=V*I;
27
28 disp('ohms',Rt,'The total resistance in the circuit')
```

```

        =')
29 disp('amperes',I,'The Current in the circuit =')
30 disp('watts',P1,'The power loss in the 100 ohms
      resistor =')
31 disp('watts',P2,'The power loss in the 200 ohms
      resistor =')
32 disp('watts',P3,'The power loss in the 300 ohms
      resistor =')
33 disp('watts',Pt,'The total power loss in the circuit
      =')
34 disp('watts',P,'The power loss in the circuit (using
      P=V*I ) =')

```

---

**Scilab code Exa 12.11** To find the value of the unknown resistance in the series of resistances in a circuit

```

1 // To find the value of the unknown resistance in the
   series of resistances in a circuit .
2
3 clc;
4 clear;
5
6 R1=20;
7
8 V=220;
9
10 P=50;
11
12 R=poly([0 1], 'R', 'c');
13 Rt=R1+R;
14
15 I=V/Rt;
16
17 A=(I^2)*R; // To get the characteristic equation to
   find R.

```

```

18 B=A-50;
19 C=B(2);
20
21 rts=roots(C); // To find the two resistances
22
23 R=round(10000.*rts)./10000; // Rounding off to four
      decimal points.
24
25 Rt=R1+R; // Total resistance
26
27 I=V./Rt; // Currents
28
29 pow=(I.^2)*(R)';
30
31 power=diag(pow);
32
33 disp(B(2), 'The Characteristic polynomial to find
      resistance R equated to zero is')
34
35 disp('ohms',R, 'The solution of the above equation
      yields two resistances')
36
37 disp('Now to check which resistance is suitable by
      finding out the power dissipated by each of them',
      )
38
39 disp('watts',power, 'The Power dissipated by both the
      resistors are')
40
41 disp('ohms',R(1), 'From comparison with the given
      value (50 watts), We find that the suitable
      resistance is')
42
43 // The higher resistance is preferred because it
      limits the amount of current, ( Please see the
      current ratings of the resistors (Heating effect)
      )

```

---

**Scilab code Exa 12.12** To Compute the resistance when operating voltage is altered

```
1 // To Compute the resistor , when operating voltage  
  is altered .  
2  
3 clc;  
4 clear;  
5  
6 V=120;  
7 P=100;  
8  
9 Rd=(V^2)/P;  
10  
11 Vr=80; // Reduced voltage  
12  
13 Ir= Vr/Rd; // Reduced current  
14  
15 Rt=V/Ir; // The Total Resistance required to  
  circulate the reduced current .  
16  
17 Re= Rt-Rd; // External resistance required .  
18  
19 disp('ohms',Re,'The external resistance required to  
  be connected in series to operate at 80V')
```

---

**Scilab code Exa 12.13** To Determine the voltage and branch currents in a circuit with resistors connected in parallel

```
1 // To Determine the voltage and branch currents in a  
  circuit with resistors connected in parallel  
2
```

```

3  clc;
4  clear;
5
6  R1=750;
7  R2=600;
8  R3=200;
9
10 C1=1/R1;
11 C2=1/R2;
12 C3=1/R3;
13
14 C= C1+C2+C3; // Total Conductance
15
16 I=1;
17
18 // 1/C is total resistance R, We use Ohm's Law to
   find the voltage applied.
19
20 V=I/C; // V=I*R
21
22 // Branch Currents
23 I1=V/R1;
24 I2=V/R2;
25 I3=V/R3;
26
27 disp('volts',V,'The applied voltage = ')
28 disp('amperes',I1,'The Current through 750 ohm
      Resistor =')
29 disp('amperes',I1,'The Current through 600 ohm
      Resistor =')
30 disp('amperes',I1,'The Current through 200 ohm
      Resistor =')
31 disp('amperes',Hence Verified.,(I1+I2+I3),'The
      Total Current through the circuit =' )

```

---

**Scilab code Exa 12.14** To determine resistances in parallel

```
1 // To determine resistances in parallel.  
2  
3 clc;  
4 clear;  
5  
6 I=25;  
7 V=200;  
8 P1=1500;  
9  
10 // Voltage remains the same in both the coils.  
11 // Power Equation and Ohm's Law is being  
    incorporated.  
12  
13 I1=P1/V;  
14  
15 R1=V/I1;  
16  
17 I2=I-I1;  
18  
19 R2= V/I2;  
20  
21 disp('ohms',R1,'The resistance of coil 1 =')  
22 disp('ohms',R2,'The resistance of coil 2 =')
```

---

**Scilab code Exa 12.15** To determine the currents in parallel branches of a network

```
1 // To determine the currents in parallel branches of  
    a network.  
2  
3 clc;  
4 clear;  
5
```

```

6 I=40;
7
8 R1=20;
9 R2=60;
10
11 // Current Divider equation I1= I*(R2/(R1+R2))
12
13 I1=I*(R2/(R1+R2));
14 I2=I*(R1/(R1+R2));
15
16 disp('A',I1,'The Current in the 20 ohm branch =')
17 disp('A',I2,'The Current in the 60 ohm branch =')

```

---

**Scilab code Exa 12.16** To determine current through each resistor in series and parallel combinational circuit

```

1 // To determine current through each resistor in
   series and parallel combinational circuit
2
3 clc;
4 clear;
5
6 R=10;
7 R1=20;
8 R2=30;
9
10 // R is the resistance in series with the parallel
    combination of R1 and R2.
11
12 V=100;
13
14 Reff=(R1*R2)/(R1+R2);
15
16 Rt=R+Reff;
17

```

```

18 I=V/Rt;
19
20 V1=I*R; // Voltage drop across 10 ohm resistor.
21
22 I1=I*(R2/(R1+R2));
23 I2=I*(R1/(R1+R2));
24
25 disp('ohms',Rt,'The total resistance of the network
      =')
26 disp('A',I,'The current through 10 ohm resistor =')
27 disp('A',I1,'The current through 20 ohm resistor =')
28 disp('A',I2,'The current through 30 ohm resistor =')

```

---

**Scilab code Exa 12.17** To calculate current in each branch of the given network

```

1 // To calculate current in each branch of the given
   network.
2
3 clc;
4 clear;
5
6
7 // Refer diagram (a) in the book
8
9 R1=6; // one of the resistance between a and b
10 R2=3; // one of the resistance between a and b
11 R3=8; // resistance between c and a
12 R4=15; // resistance in the middle branch
13 R5=4; // resistance between d and e
14
15 V=40;
16
17 Rab=(R1*R2)/(R1+R2); // Effective resistance between
   a and b

```

```

18
19 Rcb= Rab+R3; // Effective resistance of the top
   branch between c and b
20
21 Reff=(Rcb*R4)/(Rcb+R4);
22
23 Rt=Reff+R5;
24
25 I=V/Rt;
26
27 I1=I*(Rcb/(Rcb+R4));
28
29 I2=I*(R4/(Rcb+R4));
30
31 I3=I2*(R2/(R1+R2));
32
33 I4=I2*(R1/(R1+R2));
34
35 disp('amperes',I,'The current through 4 ohm resistor
      =')
36 disp('amperes',I1,'The current through 15 ohm
      resistor =')
37 disp('amperes',I2,'The current through 8 ohm
      resistor =')
38 disp('amperes',I4,'The current through 3 ohm
      resistor =')
39 disp('amperes',I3,'The current through 6 ohm
      resistor =')

```

---

**Scilab code Exa 12.18** To determine the current using loop analysis

```

1 // To determine the current using loop analysis
2
3 clc;
4 clear;

```

```

5
6 // MESH Equations
7 //6*i1 -2*i2=30
8 // -2*i1+6*i2=-40
9
10 R=[6 -2;-2 6];
11 E=[30; -40];
12
13 //The Loop Currents
14
15 I=inv(R)*E; // Matrix Method to solve for two
   unknowns in two equations.
16
17 i1=I(1);
18 i2=I(2);
19 i3=i1-i2;
20
21 disp('A',i2,'i2 =', 'A',i1,'i1 =', 'The Calculated
   Loop Currents are')
22
23 disp('The Negative sign indicates that the assumed
   direction of flow of current should be reversed.
   ')
24
25 if(i1<0);
26     i1=abs(i1);
27 end
28
29 if(i2<0);
30     i2=abs(i2);
31 end
32
33 disp('A',i1,'The Current through 4 ohm resistor on
   the 30V side =')
34 disp('A',i2,'The Current through 4 ohm resistor on
   the 40V side =')
35 disp('A',i3,'The Current through 2 ohm resistor =')

```

---

**Scilab code Exa 12.19** To calculate current in each branch using loop analysis

```
1 // To calculate current in each branch using loop
   analysis .
2
3 clc;
4 clear;
5
6 // MESH Equations for the given network .
7 //3*i1-i2+0*i3=11
8 // -i1+10*i2-2*i3=0
9 //0*i1+-2*i2+5*i3=13
10
11 //Voltage supplies are 11V and 13V
12
13 R=[3 -1 0;-1 10 -2; 0 -2 5];
14 E=[11;0;13];
15
16 // Loop Currents
17
18 I=inv(R)*E;
19
20 i1=I(1);
21 i2=I(2);
22 i3=I(3);
23
24 ia=i1-i2; // Assumed direction from Mesh 1
25 ib=i2-i3; // Assumed direction from Mesh 2
26
27 disp('A',ib,'ib (through 2 resistor between 7 ohm
   and 3 ohm resistor) =', 'A',ia,'ia (through 1 ohm
   resistor) =', 'A',i3,'i3 =', 'A',i2,'i2 =', 'A',i1,
   'i1 =', 'The Calculated Loop Currents are')
```

```

28
29 disp('The Negative sign indicates that the assumed
      direction of flow of current should be reversed'
      )
30
31 // To obtain the magnitude of direction.
32
33 if(i1<0)
34     i1=abs(i1);
35 end
36 if(i2<0)
37     i2=abs(i2);
38 end
39 if(i3<0)
40     i3=abs(i3);
41 end
42 if(ia<0)
43     ia=abs(ia);
44 end
45 if(ib<0)
46     ib=abs(ib);
47 end
48
49 disp('A',i1,'The Current through 2 ohm resistor on
      the 11V side =')
50 disp('A',i2,'The Current through 7 ohm resistor =')
51 disp('A',i3,'The Current through 3 ohm resistor on
      the 13V side =')
52 disp('A',ia,'The Current through 1 ohm resistor =')
53 disp('A',ib,'The Current through 2 ohm resistor
      between the 7 and 3 ohm resistors =')

```

---

**Scilab code Exa 12.20** To calculate current in each branch using loop analysis and point voltages in a given network

```

1 // To calculate current in each branch using loop
   analysis and point voltages in a given network.
2
3 clc;
4 clear;
5
6 // MESH Equations for the given network.
7 //  $3.95*i1 - 3.75*i2 + 0*i3 = 120$ 
8 //  $-3.75*i1 + 9.5*i2 - 5.45*i3 = 0$ 
9 //  $0*i1 - 5.45*i2 + 5.55*i3 = -110$ 
10
11 // Positive of 120V DC supply connected to 0.2 ohm
    resistor
12 // Positive of 110 DC supply connected to 0.1 ohm
    resistor
13
14 // Voltage supplies are 120V and 110V
15
16 R=[3.95 -3.75 0; -3.75 9.5 -5.45; 0 -5.45 5.55];
17 E=[120;0;-110];
18
19 R1=abs(R(2)); // Resistor carrying ia
20 R2=abs(R(8)); // Resistor carrying ib
21
22 // Loop Currents
23
24 I=inv(R)*E;
25
26 i1=I(1);
27 i2=I(2);
28 i3=I(3);
29
30 ia=i1-i2; // Assumed direction from Mesh 1
31 ib=i2-i3; // Assumed direction from Mesh 2
32
33 // Using Nodal Analysis to find V1 and V2.
34 V1=R1*ia;
35 V2=R2*ib;

```

```

36
37 disp('A',ib,'ib (through 2 resistor between 7 ohm
      and 3 ohm resistor ) =', 'A',ia,'ia (through 1 ohm
      resistor ) =', 'A',i3,'i3 =', 'A',i2,'i2 =', 'A',i1,
      i1 =', 'The Calculated Loop Currents are')
38
39 disp('The Negative sign indicates that the assumed
      direction of flow of current should be reveresed',
      )
40
41 // To obtain the magnitude of direction.
42
43 if(i1<0)
44     i1=abs(i1);
45 end
46 if(i2<0)
47     i2=abs(i2);
48 end
49 if(i3<0)
50     i3=abs(i3);
51 end
52 if(ia<0)
53     ia=abs(ia);
54 end
55 if(ib<0)
56     ib=abs(ib);
57 end
58
59 disp('A',i1,'The Current through 0.2 ohm resistor on
      the 120V side =')
60 disp('A',i2,'The Current through 0.3 ohm resistor ='
      )
61 disp('A',i3,'The Current through 0.1 ohm resistor on
      the 110V side =')
62 disp('A',ia,'The Current through 3.75 ohm resistor ='
      ')
63 disp('A',ib,'The Current through 5.45 ohm resistor ='
      ')

```

```
64
65 disp('V',V1,'The voltage V1 =')
66 disp('V',V2,'The voltage V2 =')
```

---

**Scilab code Exa 12.21** To calculate current from a battery and pd across points A and B

```
1 // To calculate current from a battery and pd across
   points A and B
2
3 clc;
4 clear;
5
6 // Resistances in the given network
7 R1=4;
8 R2=2;
9 R3=3;
10 R4=6;
11 R5=8;
12
13 // MESH Equations
14 //9*i1 -5*i2=10
15 // -5*i1 +19*i2=0
16
17 // Supply voltage 10V
18
19 R=[(R1+R2+R3) -(R2+R3); -(R2+R3) (R2+R3+R4+R5)];
20 V=[10;0];
21
22 //Loop Currents
23 I=inv(R)*V;
24
25 i1=I(1);
26 i2=I(2);
27
```

```

28 i3=i1-i2; // From Mesh 1
29
30 // Point Voltages
31 Va=i3*R3;
32 Vb=i2*R5;
33
34 disp('amperes',abs(i1), 'The current through 4 ohm
      resistor and the battery =')
35 disp('amperes',abs(i2), 'The current through 6 ohm
      and 8 ohm resistors =')
36 disp('amperes',abs(i3), 'The current through 2 ohm
      and 3 ohm resistors =')
37
38 disp('volts',abs(Va), 'The voltage at point A =')
39 disp('volts',abs(Vb), 'The voltage at point B =')
40 disp('volts',(Va-Vb), 'The voltage across Points A
      and B =')

```

---

**Scilab code Exa 12.22** Determine Current through branch AB of the given network

```

1 // Determine Current through branch AB of the given
   network
2
3 clc;
4 clear;
5
6 // MESH Equations
7 // 4*i1 -2*i2 +0*i3=10
8 // -2*i1 +6*i2 -2*i3=0
9 // 0*i1 -2*i2 +6*i3=0
10
11 // Supply Voltage is 10V (Note printing mistake)
12
13 R=[4 -2 0;-2 6 -2; 0 -2 6];

```

```

14 V=[10;0;0];
15
16 // Loop Currents
17
18 I=inv(R)*V;
19
20 i1=I(1);
21 i2=I(2);
22 i3=I(3);
23
24 disp('amperes',abs(i2), 'The current through branch
AB of the network =')

```

---

**Scilab code Exa 12.23** Determine the current in the branches of the network using nodal analysis

```

1 // Determine the current in the branches of the
   network using nodal analysis
2
3 clc;
4 clear;
5
6 // Supply voltages
7 V1=30;
8 V2=40;
9
10 // Resistances in the network
11 R1=4;
12 R2=2;
13 R3=4;
14
15 Vb=poly([0 1], 'Vb', 'c');
16
17 AD=(V1-Vb)/R1;
18 BD=(V2-Vb)/R3;

```

```

19 CD=Vb/R2;
20
21 X=AD+BD-CD;
22
23 disp('The Characteristic Equation to find Vb is')
24
25 disp(CD,'=' ,AD,'+' ,BD)
26
27 Vb=roots(X); // Stores the numerical value of Vb
28
29 i1=(V1-Vb)/R1;
30 i2=(V2-Vb)/R3;
31 i3=Vb/R2;
32
33 disp('amperes',i1,'Current through 4 ohm resistor on
      the 30V supply side =')
34 disp('amperes',i2,'Current through 4 ohm resistor on
      the 40V supply side =')
35 disp('amperes',i3,'Current through 2 ohm resistor =' )

```

---

**Scilab code Exa 12.24** To Calculate current in all branches of the network shown using nodal analysis

```

1 // To Calculate current in all branches of the
   network shown using nodal analysis
2
3 clc;
4 clear;
5
6 // Nodal Equations
7 //13*Va-4*Vb=300
8 // -Va+4*Vb=120
9
10 X=[13 -4;-1 4];

```

```

11 V=[300;120];
12
13 E=inv(X)*V;
14
15 Va=E(1);
16 Vb=E(2);
17
18 i1=(100-Va)/20;
19 i2=(Va-Vb)/15;
20 i3=(Va/10);
21 i4=(Vb/10);
22 i5=(80-Vb)/10;
23
24 disp('V',Vb,' Voltage Vb = ', 'V',Va,' Voltage Va = ')
25
26 disp('The Branch Currents as calculated are')
27 disp(i5,'i5',i4,'i4',i3,'i3',i2,'i2',i1,'i1')
28 disp(' amperes respectively')
29
30 disp('The Negative sign indicates that the assumed
      direction of flow of current must be reversed')
31
32 disp(' amperes',abs(i1), 'The Current through 20 ohm
      resistor on the 100V side =')
33 disp(' amperes',abs(i2), 'The Current through 15 ohm
      resistor =')
34 disp(' amperes',abs(i3), 'The Current through 10 ohm
      resistor (AE) =')
35 disp(' amperes',abs(i4), 'The Current through 10 ohm
      resistor (BE) =')
36 disp(' amperes',abs(i5), 'The Current through 10 ohm
      resistor on the 80V side =')

```

---

# Chapter 13

## Electromagnetic Induction

Scilab code Exa 13.1 Computing Induced EMF

```
1 // Computing Induced EMF
2 clc;
3 clear;
4
5 l=0.5;
6 v=50;
7 b=1;
8
9 // Angles
10 x=90;
11 y=30;
12 z=0;
13
14 // EMFs
15
16 e1=b*l*v*(sind(x));
17 e2=b*l*v*(sind(y));
18 e3=b*l*v*(sind(z));
19
20 disp('volts',e1,'i') The Induced EMF perpendicular
   to the field')
```

```
21 disp('volts',e2,'ii) The Induced EMF at an angle 30  
degrees to the field')  
22 disp('volts',e3,'iii)The Induced EMF parallel to the  
field')
```

---

### Scilab code Exa 13.2 Computing Instantaneous Induced EMF

```
1 // Computing InstantaneousInduced EMF  
2 clc;  
3 clear;  
4  
5 l=0.2;  
6 n=1000;  
7 b=0.5;  
8 r=l/2;  
9 t=200;  
10  
11 //Number of conductors  
12 c=2*t;  
13  
14 //Velocity Equation.  
15 v=2*(%pi)*r*1000/60;  
16  
17 // Angles  
18 x=90;  
19 y=30;  
20 z=0;  
21  
22 // EMFs  
23  
24 e1=c*b*l*v*(sind(90-x));  
25 e2=c*b*l*v*(sind(90-y));  
26 e3=c*b*l*v*(sind(90-z));  
27  
28 disp('volts',e1,'i) The Induced EMF perpendicular
```

```
    to the field ')
29 disp('volts',e2,'ii) The Induced EMF at an angle 30
    degrees to the field ')
30 disp('volts',e3,'iii)The Induced EMF parallel to the
    field ')
```

---

### Scilab code Exa 13.3 EMF Induced between wing tips

```
1 // EMF Induced between wing tips .
2 clc;
3 clear;
4
5 l=6.1;
6 vel=800;
7 v=vel*1000/3600;
8 b=(50)*(10^-6);
9 e=b*l*v;
10
11 disp('volts',e,'The EMF induced between the wing
    tips=')
```

---

### Scilab code Exa 13.4 EMF generated due to a bar magnet

```
1 // EMF generated due to a bar magnet .
2 clc;
3 clear;
4
5 b=(300)*(10^-6);
6 N=500;
7 t=(1/10);
8
9 // Faraday ' s LAW.
10
```

```
11 e=b*N/t;
12
13 disp('volts',e,'The EMF generated between the coil
      ends =')
```

---

**Scilab code Exa 13.5** EMF induced between two coils in a circular iron core

```
1 //EMF induced between two coils in a circular iron
   core
2 clc;
3 clear;
4
5 area= 5*(10^-4);
6 l=0.5;
7
8 na=200;
9 nb=500;
10
11 dI=15;
12 dt=(1/10);
13
14 mr=250;
15 mo= 4*%pi*(10^-7);
16
17 mfa=na*dI;
18
19 H=mfa/l;
20
21 B=mo*mr*H;
22
23 // Flux Linked
24
25 flux=B*area;
26
```

```
27 eb=nb*flux/dt;
28
29 disp('volts',eb,'The Induced EMF by coil B =')
```

---

**Scilab code Exa 13.6** Force on the conductor due to a uniform magentic field

```
1 // Force on the conductor due to a uniform magentic
   field
2 clc;
3 clear;
4
5 l=0.5;
6 B=0.12;
7 I=15;
8
9 F=B*I*l;
10
11 disp('N',F,'The Force on the conductor =')
```

---

**Scilab code Exa 13.7** To determine force between single phase bus bars

```
1 // To determine force between single phase bus bars
2
3 clc;
4 clear;
5
6 eload=10^7;
7 voltage=15*(10^3);
8
9 mo=4*pi*(10^-7);
10
11 l=1;
```

```

12 r=0.3;
13
14 // Normally
15
16 I=eload/voltage;
17 F=mo*I*I*l/(2*pi*r);
18
19 // Short Circuit
20
21 Isc=10*I;
22 Fsc=mo*Isc*Isc*l/(2*pi*r);
23
24 disp('N',F,'i) Force per metre under normal
    condition =')
25 disp('N',Fsc,'ii) Force per metre under short
    circuit condition =')

```

---

**Scilab code Exa 13.8** To Compute the Maximum Induced EMF

```

1 // To Compute the Maximum Induced EMF
2
3 clc;
4 clear;
5
6 T=1/50;
7 fluxmax=0.02;
8 N=100;
9
10 flux= fluxmax*(poly([1 -4/T], 't', 'c'));// Flux
    Equation under consideration.
11
12 e=N*(-1)*derivat(flux);
13
14 disp('volts',e,'The Maximum induced EMF= ')

```

---

**Scilab code Exa 13.9** Compute Inductance and EMF induced

```
1 // Compute Inductance and EMF induced
2 clc;
3 clear;
4
5 d=0.25;
6 l=%pi*d;
7 n=1000;
8 area=6.25*(10^-4);
9 I=200;
10 mo=4*%pi*(10^-7);
11
12 L=mo*area*n*n/l;
13
14 V=L*I;
15
16 disp('H',L,'The Inductance of toriod')
17 disp('volts',V,'The Induced EMF in the toriod')
```

---

**Scilab code Exa 13.10** Change in Inductance

```
1 // Change in Inductance
2 clc;
3 clear;
4
5 L=120*(10^-3);
6 N=1000;
7 mr=75;
8 Nr=200;
9 Nc=N-Nr;
10
```

```
11 // Inductance directly proportional to the product  
    of the square of turns and the relative  
    permeability  
12  
13 Lc= L*((Nc/N)^2)*75;  
14  
15 disp('H',Lc,'The New value of inductance =')
```

---

### Scilab code Exa 13.11 Computation of Current

```
1 // Compute Current  
2 clc;  
3 clear;  
4  
5 i=3;  
6 L=10;  
7 t=20*(10^-3);  
8 V=20*(10^3);  
9  
10 E=L*i*i/2;  
11  
12 P=E/t;  
13  
14 I=P/V;  
15  
16 disp('amperes',I,'The Current in the spark plug =')
```

---

### Scilab code Exa 13.12 To determine Mutual and Self Inductances

```
1 // To determine Mutual and Self Inductances  
2  
3 clc;  
4 clear;
```

```

5
6 K=0.8;
7 I1=3;
8 flux1=0.4*(10^-3);
9 E2=85;
10 t=3*(10^-3);
11 N1=300;
12
13 L1=N1*flux1/I1;
14
15 M= E2*t/I1;
16
17 L2(((M/K)^2)/L1);
18
19 flux2=K*flux1;
20
21 N2=(M*I1/flux2);
22
23 disp('H',L1,'The inductance of coil 1');
24 disp('H',L2,'The inductance of coil 2');
25 disp('H',M,'The inductance between the coils');
26 disp('Turns',N2,'The number of turns of coil 2');

```

---

**Scilab code Exa 13.13** Computation of Mutual and self inductance in coils

```

1 //Computation of Mutual and self inductances
2
3 clc;
4 clear;
5
6 n1=600;
7 i1=2.5;
8 flux1=0.4*(10^-3);
9 flux2=0.8*(10^-3);
10 n2=2000;

```

```

11 tflux=flux1+flux2;
12
13 L1=n1*tflux/i1;
14
15 K=flux2/tflux;
16
17 M=n2*flux2/i1;
18
19 L2=((M/K)^2)/L1;
20
21 disp('H',L1,'The self inductance of coil 1= ')
22 disp('H',L2,'The self inductance of coil 2= ')
23
24 disp('(Note the accuracy of the answer.)')
25 disp('H',M,'The Mutual inductance of both coils= ')
26 disp(K,'The coupling co-efficient')

```

---

**Scilab code Exa 13.14** EMF induced in coils parallel to each other

```

1 // EMF induced in coils parallel to each other
2
3 clc;
4 clear;
5
6 Nx=1000;
7 Ix=5;
8 flux1=0.05*(10^-3);
9 di=12;
10 dt=10^-2;
11 K=60/100;
12
13 Lx= Nx*flux1/Ix;
14
15 // Since two coils are identical , Both will have
   equal self inductances .

```

```

16
17 Ly=Lx;
18
19 M=K*sqrt(Lx*Ly);
20
21 Ey=M*di/dt;
22
23 disp('volts',Ey,'The EMF induced by the coil Y=')
24 disp('H',Lx,'The Self Inductance of Coil X=')
25 disp('H',Ly,'The Self Inductance of Coil X=')
26 disp('H',M,'The Mutual Inductance of Coils')

```

---

**Scilab code Exa 13.15** To Compute the maximum flux set by an coil

```

1 //To Compute the maximum flux set by an coil.
2
3 clc;
4 clear;
5
6 L1=0.5;
7 L2=1;
8 K=0.8;
9
10 N2=1500;
11
12 M=K*sqrt(L1*L2);
13 i1=20;
14
15 theta=poly(0,'t');
16
17 fact=derivat(theta); // Derivative of the time factor
    (Linear function of 't').
18
19 omega=314; // The Angular Frequency Factor
20

```

```

21 v2=M*fact*omega*i1; // Maximum Coil 2 Voltage
22
23 disp('cos 314t V',v2,'The Voltage Across Coil 2= ')
24
25 df1x=v2/N2;
26
27 Mxflux=(df1x/omega)*(1/fact);
28
29
30 disp('sin 314t Wb',Mxflux,'The flux setup by Coil 1=
')
31
32 disp('Wb',Mxflux,'The Maximum Flux Setup by Coil 1=
')

```

---

### Scilab code Exa 13.16 Compute Loss of energy

```

1 //Compute Loss of energy
2
3 clc;
4 clear;
5
6 w=10;
7 f=50; // 50 cycles in a second.
8
9 ls_vol=250;
10
11 density=7.5; // Density in gm/cm^3
12
13 d= density*(10^6)/(10^3);
14
15 vol=w/d;
16
17 ls_cycle= ls_vol*vol;
18

```

```
19 ls_sec= ls_cycle*50;
20
21 ls_hr= ls_sec*3600;
22
23 disp('joules',ls_hr,'The Loss of energy per hour of
      an iron loop')
```

---

### Scilab code Exa 13.17 Determining Hysteresis loss

```
1 // Determining Hysteresis loss
2 clc;
3 clear;
4
5 fluxmax=1.5;
6
7 x=15/(10^-2);
8 y=1;
9
10 f=50;
11
12 a=x*y; // loss for one centimetre square.
13
14 area=0.6; // in centimetre square.
15
16 hy_ls= area*a;
17
18 vol=1500*(10^-6);
19
20 hyls_cycle= vol*hy_ls;
21
22 hyls_sec= hyls_cycle*f;
23
24 disp('watts',hyls_sec,'The Hysteresis loss =')
```

---

**Scilab code Exa 13.18** Compute the Loss per Kg at a particular frequency

```
1 //Compute the Loss per Kg at a particular frequency .
2 clc;
3 clear;
4
5 hy_ls=4.9;
6 f1=50;
7 maxflux=1;
8
9 density=7.5;
10
11 d=density*(10^6)/(10^3);
12
13 hy_ls_cycle= hy_ls*d/f1;
14
15 n=hy_ls_cycle/((maxflux)^1.7);
16
17 disp(n, 'i) The value of the Co-Efficient= ')
18
19 mflux2=1.8;
20
21 f2=25;
22
23 hy_ls2=hy_ls*(f2/f1)*((1.8)^1.7);
24
25 disp('watt/kg',hy_ls2, 'ii) The Loss per kg at 25Hz
and 1.8 Wb per square metre= ')
```

---

**Scilab code Exa 13.19** Theory Based Proof relation between self mutual inductances

```

1 // Theory Based Proof relation between self mutual
   inductances
2
3 clc;
4 clear;
5
6 disp( 'L1=((N1)^2)*Mo*A/l ')
7 disp( 'L2=((N2)^2)*Mo*A/l ')
8 disp( 'R=l/(Mo*A) ')
9
10 disp( 'L1=((N1)^2)/R' )
11 disp( 'L2=((N2)^2)/R' )
12
13 disp( 'M=K*((L1*L2)^(1/2))' )
14
15 disp( '( Substituting L1 and L2 in the above equation )' )
16
17 disp( 'M=K*N1*N2/R' )
18 disp( 'Hence Proved' )

```

---