

Scilab Textbook Companion for
Basic Electronics And Linear Circuits
by N. N. Bhargava, D. C. Kulshreshtha And S.
C. Gupta¹

Created by
Mohammad Faisal Siddiqi
B.Tech (pursuing)
Electronics Engineering
Jamia Millia Islamia, New Delhi
College Teacher
Dr. Sajad A. Loan
Cross-Checked by
TechPassion

August 10, 2013

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Basic Electronics And Linear Circuits

Author: N. N. Bhargava, D. C. Kulshreshtha And S. C. Gupta

Publisher: Tata McGraw - Hill Education, New Delhi

Edition: 1

Year: 2008

ISBN: 0074519654

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 INTRODUCTION TO ELECTRONICS	8
2 CURRENT AND VOLTAGE SOURCES	10
4 SEMICONDUCTOR DIODE	14
5 TRANSISTORS	20
6 VACUUM TUBES	27
7 TRANSISTOR BIASING AND STABILIZATION OF OPERATING POINT	32
8 SMALL SIGNAL AMPLIFIERS	46
9 MULTI STAGE AMPLIFIERS	53
10 POWER AMPLIFIERS	61
11 TUNED VOLTAGE AMPLIFIERS	64
12 FEEDBACK IN AMPLIFIERS	69
13 OSCILLATORS	73
14 ELECTRONIC INSTRUMENTS	75

List of Scilab Codes

Exa 1.1	Resistor Range Calculation using Colour Band Sequence	8
Exa 1.2	Resistor Range Calculation using Colour Band Sequence	9
Exa 2.1	Equivalent Current Source Representation	10
Exa 2.2	Equivalent Voltage Source Representation	11
Exa 2.3	Current Determination using Voltage Source and Current Source Representations	11
Exa 2.4	Output Voltage Determination	12
Exa 4.1	DC Voltage and PIV Calculation	14
Exa 4.2	DC Voltage and PIV Calculation	15
Exa 4.3.a	Peak Value of Current Calculation	15
Exa 4.3.b	DC or Average Value of Current Calculation	16
Exa 4.3.c	RMS Value of Current Calculation	16
Exa 4.3.d	Ripple Factor Determination	17
Exa 4.3.e	Rectification Efficiency Calculation	17
Exa 4.4	Maximum Permissible Current Determination	18
Exa 4.5	Capacitance Determination on changing Bias Voltage	19
Exa 5.1	Collector and Base Currents Calculation	20
Exa 5.2	Dynamic Input Resistance Determination	20
Exa 5.3	Short Circuit Current Gain Determination	21
Exa 5.4.a	Common Base Short Circuit Current Gain Calculation	22
Exa 5.4.b	Common Emitter Short Circuit Current Gain Calculation	22
Exa 5.5	DC Current Gain in Common Base Configuration	23
Exa 5.6	Determination of Dynamic Output Resistance and AC and DC Current Gains	23
Exa 5.7	Q Point Determination	24
Exa 5.8	Calculation of Dynamic Drain Resistance of JFET	25
Exa 6.1	Dynamic Plate Resistance of the Diode Determination	27

Exa 6.2	Plotting of Static Plate Characteristics	29
Exa 7.1	Calculate I_c and V_{ce} for given Circuit	32
Exa 7.2	Calculate coordinates of Operating Point	33
Exa 7.3	Quiescent Operating Point Determination	34
Exa 7.4.a	Calculate value of Resistance R_b	35
Exa 7.4.b	Calculation of Collector Current I_c	36
Exa 7.5	Calculation of I_e and V_c in the Circuit	36
Exa 7.6	Calculate Minimum and Maximum Collector Currents	37
Exa 7.7	Calculate Values of the three Currents	38
Exa 7.8	Calculate Minimum and Maximum I_e and correspond- ing V_{ce}	38
Exa 7.9	Determine the new Q Points	40
Exa 7.10	Calculate the value of R_b	41
Exa 7.11	Calculate DC bias Voltages and Currents	42
Exa 7.12	Calculate R_e and V_{ce} in the Circuit	42
Exa 7.13	Calculate I_c and V_{ce} for given Circuit	43
Exa 7.14	Calculate I_c and V_{ce} for given Circuit	44
Exa 8.1	Determination of Hybrid Parameters	46
Exa 8.2.a	Calculation of Input Impedance of Amplifier	47
Exa 8.2.b	Calculation of Voltage Gain of Amplifier	47
Exa 8.2.c	Calculation of Current Gain of Amplifier	48
Exa 8.3.a	Calculation of Voltage Gain of Amplifier	48
Exa 8.3.b	Calculation of Input Impedance of Amplifier	49
Exa 8.3.c	Calculation of Q Point Parameters of Amplifier	49
Exa 8.4	Calculation of Voltage Gain of Amplifier	50
Exa 8.5	Calculation of Gain of Single Stage Amplifier	51
Exa 8.6	Calculation of Output Signal Voltage of FET Amplifier	51
Exa 9.1	Calculate overall Voltage Gain in dB	53
Exa 9.2	Calculate Voltage at the Output Terminal	53
Exa 9.3	To Plot the Frequency Response Curve	54
Exa 9.4.a	Calculate Input Impedance of Two Stage RC Coupled Amplifier	57
Exa 9.4.b	Calculate Output Impedance of Two Stage RC Coupled Amplifier	57
Exa 9.4.c	Calculate Voltage Gain of Two Stage RC Coupled Am- plifier	58
Exa 9.5	Calculate Maximum Voltage Gain and Bandwidth of Triode Amplifier	59

Exa 10.1	Calculation of Transformer Turns Ratio	61
Exa 10.2	Calculation of Effective Resistance seen at Primary . .	61
Exa 10.3.a	Calculation of 2nd 3rd and 4th Harmonic Distortions .	62
Exa 10.3.b	Percentage Increase in Power because of Distortion . .	63
Exa 11.1.a	Calculation of Resonant Frequency	64
Exa 11.1.b	Calculation of Impedance at Resonance	64
Exa 11.1.c	Calculation of Current at Resonance	65
Exa 11.1.d	Calculation of Voltage across each Component	66
Exa 11.2	Calculation of Parameters of the Resonant Circuit at Resonance	66
Exa 11.3	Calculation of Impedance Q and Bandwidth of Reso- nant Circuit	67
Exa 12.1	Calculation of Gain of Negative Feedback Amplifier . .	69
Exa 12.2	Calculation of Internal Gain and Feedback Gain	69
Exa 12.3	Calculation of change in overall Gain of Feedback Am- plifier	70
Exa 12.4	Calculation of Input Impedance of the Feedback Ampli- fier	71
Exa 12.5	Calculation of Feedback Factor and Percent change in overall Gain	71
Exa 13.1	Calculate Frequency of Oscillation of Tuned Collector Oscillator	73
Exa 13.2	Calculate Frequency of Oscillation of Phase Shift Oscil- lator	73
Exa 13.3	Calculate Frequency of Oscillation of Wein Bridge Os- cillator	74
Exa 14.1	Calculation of Series Resistance for conversion to Voltmeter	75
Exa 14.2	Calculation of Shunt Resistance	76
Exa 14.3	Designing of a Universal Shunt for making a Multi Range Milliammeter	76
Exa 14.4	Determination of Peak and RMS AC Voltage	78
Exa 14.5	Determination of Magnitude and Frequency of Voltage Fed to Y Input	78

List of Figures

6.1	Dynamic Plate Resistance of the Diode Determination	28
6.2	Plotting of Static Plate Characteristics	29
9.1	To Plot the Frequency Response Curve	55
14.1	Determination of Magnitude and Frequency of Voltage Fed to Y Input	79

Chapter 1

INTRODUCTION TO ELECTRONICS

Scilab code Exa 1.1 Resistor Range Calculation using Colour Band Sequence

```
1 //Example 1.1
2 //Program to find Range of a Resistor so as to
   satisfy manufacturer's Tolerances
3 //Colour Band Sequence: YELLOW, VIOLET, ORANGE, GOLD
4 clear all;
5 clc ;
6 close ;
7 A=4; //NUMERICAL CODE FOR BAND YELLOW
8 B=7; //NUMERICAL CODE FOR BAND VIOLET
9 C=3; //NUMERICAL CODE FOR BAND ORANGE
10 D=5; //TOLERANCE VALUE FOR BAND GOLD i.e. 5%
11 //Resistor Value Calculation
12 R=(A*10+B)*10^C;
13 //Tolerance Value Calculation
14 T=D*R/100;
15 R1=R-T;
16 R2=R+T;
17 //Displaying The Results in Command Window
```

```

18 printf("\n\n\t Resistor Value is %f kOhms ± %f
    percent.",R/1000,D);
19 printf("\n\n\t Resistor Value is %f kOhms ± %f
    kOhms.",R/1000,T/1000);
20 printf("\n\n\t Range of Values of the Resistor is %f
    kOhms & %f kOhms.",R1/1000,R2/1000);

```

Scilab code Exa 1.2 Resistor Range Calculation using Colour Band Sequence

```

1 //Example 1.2
2 //Program to find Range of a Resistor so as to
    satisfy manufacturer's Tolerances
3 //Colour Band Sequence: GRAY, BLUE, GOLD, GOLD
4 clear all;
5 clc ;
6 close ;
7 A=8; //NUMERICAL CODE FOR BAND GRAY
8 B=6; //NUMERICAL CODE FOR BAND BLUE
9 C=-1; //NUMERICAL CODE FOR BAND GOLD
10 D=5; //TOLERANCE VALUE FOR BAND GOLD i.e. 5%
11 //Resistor Value Calculation
12 R=(A*10+B)*10^C;
13 //Tolerance Value Calculation
14 T=D*R/100;
15 R1=R-T;
16 R2=R+T;
17 //Displaying The Results in Command Window
18 printf("\n\n\t Resistor Value is %f Ohms ± %f
    percent.",R,D);
19 printf("\n\n\t Resistor Value is %f Ohms ± %f Ohms.
    ",R,T);
20 printf("\n\n\t Range of Values of the Resistor is %f
    Ohms & %f Ohms.",R1,R2);

```

Chapter 2

CURRENT AND VOLTAGE SOURCES

Scilab code Exa 2.1 Equivalent Current Source Representation

```
1 //Example 2.1
2 //Program to Obtain Equivalent Current Source
  Representaion from Given Voltage Source
  Representation
3 clear all;
4 clc ;
5 close ;
6 //Voltage Source or Thevenin's Representaion (Series
  Voltage Source & Resistor)
7 Vs=2; //Volts
8 Rs=1; //Ohm
9 //Current Source or Norton's Representaion (Parallel
  Current Source & Resistor)
10 Is=Vs/Rs; //Amperes
11 //Displaying The Results in Command Window
12 printf("\n\n\t The Short Circuit Current Value is %f
  Amperes.",Is);
13 printf("\n\n\t The Source Impedence Value is %f Ohm.
  ",Rs);
```

```
14 printf("\n\n\t The Current Source & Source Impedance
    are connected in Parallel.");
```

Scilab code Exa 2.2 Equivalent Voltage Source Representation

```
1 //Example 2.2
2 //Program to Obtain Equivalent Voltage Source
  Representaion from Given Current Source
  Representation
3 clear all;
4 clc ;
5 close ;
6 //Current Source or Norton's Representaion (Parallel
  Current Source & Resistor)
7 Is=0.2; //Amperes
8 Zs=100; //Ohms
9 //Voltage Source or Thevenin's Representaion (Series
  Voltage Source & Resistor)
10 Vs=Is*Zs; //Volts
11 //Displaying The Results in Command Window
12 printf("\n\n\t The Open Circuit Voltage is %f Volts.
    ",Vs);
13 printf("\n\n\t The Source Impedence Value is %f Ohms
    .",Zs);
14 printf("\n\n\t The Voltage Source & Source Impedance
    are connected in Series.");
```

Scilab code Exa 2.3 Current Determination using Voltage Source and Current Source Representations

```
1 //Example 2.3
2 //Program to Calculate Current in a Branch by Using
  Current Source Representation
```

```

3 //Verify the Circuit's Result for its equivalence
  with Voltage Source Representation
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Is=1.5*10(-3); //Amperes
9 Zs=2*103; //Ohms
10 Z1=10*103; //Ohms
11 Z2=40*103; //Ohms
12 //Calculation for Current Source Representation
13 Z1=Z1*Z2/(Z1+Z2);
14 I2=Is*Zs/(Zs+Z1);
15 I4I=I2*Z1/(Z1+Z2); //Using Current Divider Rule
16 //Calculation for Current Source Representation
17 Vs=Is*Zs; //Open Circuit Volatge
18 I=Vs/(Zs+Z1);
19 I4V=I*Z1/(Z1+Z2); //Using Current Divider Rule
20 //Displaying The Results in Command Window
21 printf("\n\n\t The Load Current using Current Source
  Representaion is I4I = %f Amperes.",I4I);
22 printf("\n\n\t The Load Current using Voltage Source
  Representaion is I4V = %f Amperes.",I4V);
23 if I4I==I4V then
24 printf("\n\n\t Both Results are Equivalent.");
25 else
26 printf("\n\n\t Both Results are Not Equivalent.");
27 end;

```

Scilab code Exa 2.4 Output Voltage Determination

```

1 //Example 2.4
2 //Program to Obtain Output Voltage Vo from Given A.C
  . Equivalent of an Amplifier using a Transistor
3 clear all;

```

```
4 clc ;
5 close ;
6 //Given Circuit Data
7 //Input Side
8 Vs=10*10(-3); //i.e. 10 mV
9 Rs=1*103; //i.e. 1 kOhms
10 //Output Side
11 Ro1=20*103; //i.e. 20 kOhms
12 Ro2=2*103; //i.e. 2 kOhms
13 //Calculation
14 i=Vs/Rs; //Input Current
15 Io=100*i; //Output Current
16 I1=Io*Ro1/(Ro1+Ro2); //Using Current Divider Rule
17 Vo=I1*Ro2; //Output Volatge
18 //Displaying The Results in Command Window
19 printf("\\n\\t The Output Voltage Vo = %f Volts.",Vo);
```

Chapter 4

SEMICONDUCTOR DIODE

Scilab code Exa 4.1 DC Voltage and PIV Calculation

```
1 //Example 4.1
2 //Program to determine DC Voltage across the load
  and PIV of the Diode
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vrms=220; //Volts
8 n2=1; //Assumption
9 n1=12*n2; //Turns Ratio
10 //Calculation
11 Vp=sqrt(2)*Vrms; //Maximum(Peak) Primary Voltage
12 Vm=n2*Vp/n1; //Maximum Secondary Voltage
13 Vdc=Vm/%pi; //DC load Voltage
14 //Displaying The Results in Command Window
15 printf("\n\t The DC load Voltage is = %f V .",Vdc);
16 printf("\n\t The Peak Inverse Voltage(PIV) is = %f V
  .",Vm);
```

Scilab code Exa 4.2 DC Voltage and PIV Calculation

```
1 //Example 4.2
2 //Program to determine DC Voltage across the load
  and PIV of the
3 //Centre Tap Rectifier and Bridge Rectifier
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Vrms=220; //Volts
9 n2=1; //Assumption
10 n1=12*n2; //Turns Ratio
11 //Calculation
12 Vp=sqrt(2)*Vrms; //Maximum(Peak) Primary Voltage
13 Vm=n2*Vp/n1; //Maximum Secondary Voltage
14 Vdc=2*Vm/%pi; //DC load Voltage
15 //Displaying The Results in Command Window
16 printf("\n\t The DC load Voltage is = %f V .",Vdc);
17 printf("\n\t The Peak Inverse Voltage(PIV) of Bridge
  Rectifier is = %f V .",Vm);
18 printf("\n\t The Peak Inverse Voltage(PIV) of Centre
  -tap Rectifier is = %f V .",2*Vm);
```

Scilab code Exa 4.3.a Peak Value of Current Calculation

```
1 //Example 4.3(a)
2 //Program to determine the Peak Value of Current
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
```



```

10 //Calculation
11 Im=Vm/(rd+Rl); //Peak Value of Current
12 //Displaying The Results in Command Window
13 printf("\n\t The Peak Value of Current is = %f mA ."
        ,Im/10(-3));

```

Scilab code Exa 4.3.b DC or Average Value of Current Calculation

```

1 //Example 4.3(b)
2 //Program to determine the DC or Average Value of
  Current
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=1*10(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+Rl); //Peak Value of Current
12 Idc=2*Im/%pi; //DC Value of Current
13 //Displaying The Results in Command Window
14 printf("\n\t The DC or Average Value of Current is =
        %f mA ." ,Idc/10(-3));

```

Scilab code Exa 4.3.c RMS Value of Current Calculation

```

1 //Example 4.3(c)
2 //Program to determine the RMS Value of Current
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data

```

```

7 R1=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+R1); //Peak Value of Current
12 Irms=Im/sqrt(2); //RMS Value of Current
13 //Displaying The Results in Command Window
14 printf("\n\t The RMS Value of Current is = %f mA .",
        Irms/10^(-3));

```

Scilab code Exa 4.3.d Ripple Factor Determination

```

1 //Example 4.3(d)
2 //Program to determine the Ripple Factor of Centre-
   tap Full Wave Rectifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 R1=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+R1); //Peak Value of Current
12 Idc=2*Im/%pi; //DC Value of Current
13 Irms=Im/sqrt(2); //RMS Value of Current
14 r=sqrt((Irms/Idc)^2-1) //Ripple Factor
15 //Displaying The Results in Command Window
16 printf("\n\t The Ripple Factor r = %f .",r);

```

Scilab code Exa 4.3.e Rectification Efficiency Calculation

```

1 //Example 4.3(e)

```

```

2 //Program to determine the Rectification Efficiency
  of Centre-tap Full Wave Rectifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+Rl); //Peak Value of Current
12 Idc=2*Im/%pi; //DC Value of Current
13 Irms=Im/sqrt(2); //RMS Value of Current
14 Pdc=Idc^2*Rl;
15 Pac=Irms^2*(rd+Rl);
16 n=Pdc/Pac; //Rectification Efficiency
17 //Displaying The Results in Command Window
18 printf("\n\t The Rectification Efficiency n(eeta) =
  %f percent.",n*100);

```

Scilab code Exa 4.4 Maximum Permissible Current Determination

```

1 //Example 4.4
2 //Program to determine Maximum Current the Given
  Zener Diode can handle
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vz=9.1; //Volts
8 P=364*10^(-3); //Watts
9 //Calculation
10 Iz=P/Vz;
11 //Displaying The Results in Command Window
12 printf("\n\t The Maximum permissible Current is Iz(

```

```
max) = %f mA ." ,Iz/10(-3));
```

Scilab code Exa 4.5 Capacitance Determination on changing Bias Voltage

```
1 //Example 4.5
2 //Program to determine Capacitance of Varactor Diode
   if the
3 //Reverse-Bias Voltage is increased from 4V to 8V
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Ci=18*10(-12); //i.e. 18 pF
9 Vi=4; //Volts
10 Vf=8; //Volts
11 //Calculation
12 K=Ci*sqrt(Vi);
13 Cf=K/sqrt(Vf);
14 //Displaying The Results in Command Window
15 printf("\n\t The Final Value of Capacitance is C =
   %f pF ." ,Cf/10(-12));
```

Chapter 5

TRANSISTORS

Scilab code Exa 5.1 Collector and Base Currents Calculation

```
1 //Example 5.1
2 //Program to Calculate Collector and Base Currents
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 alpha=0.98; //alpha(dc)
8 Ico=1*10^(-6); //Ampere
9 Ie=1*10^(-3); //Ampere
10 //Calculation
11 Ic=alpha*Ie+Ico; //Collector Current
12 Ib=Ie-Ic; //Base Current
13 //Displaying The Results in Command Window
14 printf("\n\t The Collector Current is Ic= %f mA .",
        Ic/10^(-3));
15 printf("\n\t The Base Current is Ib= %f uA .",Ib
        /10^(-6));
```

Scilab code Exa 5.2 Dynamic Input Resistance Determination

```

1 //Example 5.2
2 //Program to Determine Dynamic Input Resistance of
   the Transistor at //the point: Ie=0.5 mA and Vcb=
   -10 V.
3 clear all;
4 clc ;
5 close ;
6 //From the Input Characteristics
7 dIe=(0.7-0.3)*10(-3); //A
8 dVeb=(0.7-0.62); //V
9 //Calculation
10 ri=dVeb/dIe; //Dynamic Input Resistance at Vcb= -10
   V
11 //Displaying The Results in Command Window
12 printf("\n\t The Dynamic Input Resistance is ri= %f
   Ohms .",ri);

```

Scilab code Exa 5.3 Short Circuit Current Gain Determination

```

1 //Example 5.3
2 //Program to Determine Short Circuit Current Gain of
   the Transistor
3 clear all;
4 clc ;
5 close ;
6 //Given Data
7 dIe=1*10(-3); //A
8 dIc=0.99*10(-3); //A
9 //Calculation
10 hfb=dIc/dIe; //Short Circuit Current Gain
11 //Displaying The Results in Command Window
12 printf("\n\t The Short Circuit Current Gain is alpha
   or hfb= %f .",hfb);

```

Scilab code Exa 5.4.a Common Base Short Circuit Current Gain Calculation

```
1 //Example 5.4(a)
2 //Program to Determine Common Base Short Circuit
   Current Gain (alpha)
3 //of the Transistor
4 clear all;
5 clc ;
6 close ;
7 //Given Data
8 dIe=1*10(-3); //A
9 dIc=0.995*10(-3); //A
10 //Calculation
11 alpha=dIc/dIe; //Common Base Short Circuit Current
   Gain
12 //Displaying The Results in Command Window
13 printf("\n\t The Common Base Short Circuit Current
   Gain is alpha= %f .",alpha);
```

Scilab code Exa 5.4.b Common Emitter Short Circuit Current Gain Calculation

```
1 //Example 5.4(b)
2 //Program to Determine Common Emitter Short Circuit
   Current Gain (beeta)
3 //of the Transistor
4 clear all;
5 clc ;
6 close ;
7 //Given Data
8 dIe=1*10(-3); //A
```

```

9 dIc=0.995*10(-3); //A
10 //Calculation
11 alpha=dIc/dIe; //Common Base Short Circuit Current
    Gain
12 beeta=alpha/(1-alpha); //Common Emitter Short
    Circuit Current Gain
13 //Displaying The Results in Command Window
14 printf("\n\t The Common Emitter Short Circuit
    Current Gain is beeta= %f .",beeta);

```

Scilab code Exa 5.5 DC Current Gain in Common Base Configuration

```

1 //Example 5.5
2 //Program to Determine DC Current Gain in Common
    Base Configuration
3 clear all;
4 clc ;
5 close ;
6 //Given Data
7 Beeta=100;
8 //Calculation
9 Alpha=Beeta/(Beeta+1); //DC Current Gain in Common
    Base Configuration
10 //Displaying The Results in Command Window
11 printf("\n\t The DC Current Gain in Common Base
    Configuration is Alpha= %f .",Alpha);

```

Scilab code Exa 5.6 Determination of Dynamic Output Resistance and AC and DC Current Gains

```

1 //Example 5.6
2 //Refer Figure 5.20 in the Textbook

```



```

3 //Program to Determine the Dynamic Output Resistance
4 //DC Current Gain & AC Current Gain from given
   output characteristics
5 clear all;
6 clc ;
7 close ;
8 //Given Data
9 Vce=10; //V
10 Ib=30*10(-6); //A
11 //Calculation from Given Output Characteristics at
   Ib = 30uA
12 dVce=(12.5-7.5); //V
13 dic=(3.7-3.5)*10(-3); //A
14 Ic=3.6*10(-3); //A
15 ro=dVce/dic; // Dynamic Output Resistance
16 Beeta_dc=Ic/Ib; // DC Current Gain
17 Beeta_ac=((4.7-3.6)*10(-3))/((40-30)*10(-6)); //AC
   Current Gain, From Graph, Bac=delta(ic)/delta(ib)
   for given Vce
18 //Displaying The Results in Command Window
19 printf("\n\t Dynamic Output Resistance ,ro = %f
   kOhms",ro/10(3));
20 printf("\n\t DC Current Gain ,Bdc = %f ",Beeta_dc);
21 printf("\n\t AC Current Gain ,Bac = %f ",Beeta_ac);

```

Scilab code Exa 5.7 Q Point Determination

```

1 //Example 5.7
2 //Refer Figure 5.27 in the Textbook
3 //Program to Determine the Q point from given
   collector characteristics
4 clear all;
5 clc ;
6 close ;

```

```

7 //Given Data
8 Vcc=12; //V
9 Rc=1*10^(3); //Ohms
10 Vbb=10.7; //V
11 Rb=200*10^(3); //Ohms
12 Vbe=0.7; //V
13 //Calculation
14 Ib=(Vbb-Vbe)/Rb;
15 //Value of Ib comes out to be 50uA. A dotted Curve
    is drawn for
16 //Ib=40uA and Ib=60uA. At the Point of Intersection:
17 Vce=6; //V
18 Ic=6*10^(-3); //A
19 //Displaying The Results in Command Window
20 printf("\n\t Q point: \n\n\t Ib = %f uA",Ib/10^(-6))
    ;
21 printf("\n\t Vce = %f V",Vce);
22 printf("\n\t Ic = %f mA",Ic/10^(-3));

```

Scilab code Exa 5.8 Calculation of Dynamic Drain Resistance of JFET

```

1 //Example 5.8
2 //Program to Calculate Dynamic Drain Resistance of
    JFET
3 clear all;
4 clc ;
5 close ;
6 //Given Data
7 u=80; // Amplification Factor
8 gm=200*10^(-6); // S, Transconductance
9 //Calculation
10 rd=u/gm; //Dynamic Drain Resistance
11 //Displaying The Results in Command Window
12 printf("\n\t The Dynamic Drain Resistance of JFET is
    rd= %f kOhms.",rd/10^(3));

```


Chapter 6

VACUUM TUBES

Scilab code Exa 6.1 Dynamic Plate Resistance of the Diode Determination

```
1 //Example 6.1
2 //Program to Plot the Characteristics and
3 //Determine Dynamic Plate Resistance
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 V=[0 0.5 1 1.5 2]; //V
9 I=[0 1.6 4 6.7 9.8]; //mA
10 //Plotting
11 plot(V,I);
12 a= gca ();
13 xlabel ('Plate Voltage (in V)');
14 ylabel ('Plate Current (in mA)');
15 title ('STATIC CHARACTERISTIC CURVE OF THE DIODE');
16 //Calculation
17 //Values from Characteristic Plot
18 dVp=0.5; //V
```

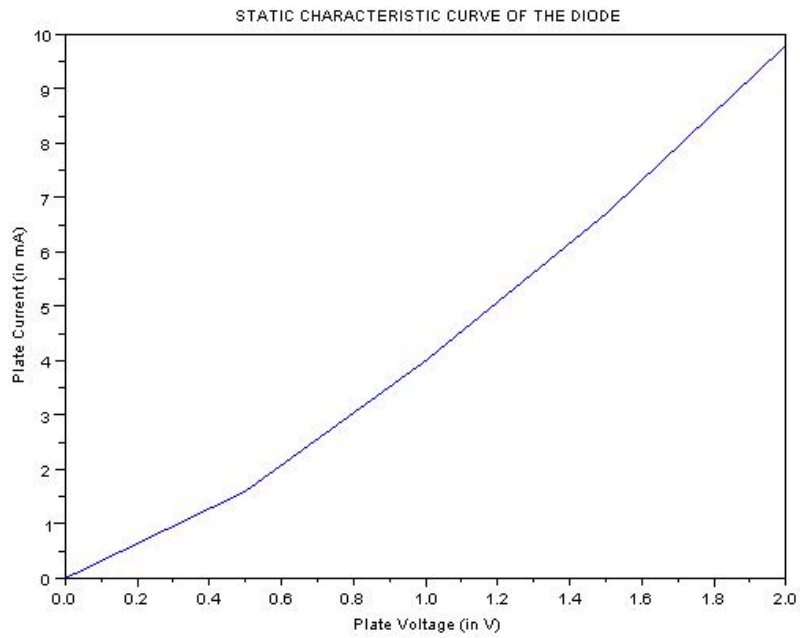


Figure 6.1: Dynamic Plate Resistance of the Diode Determination

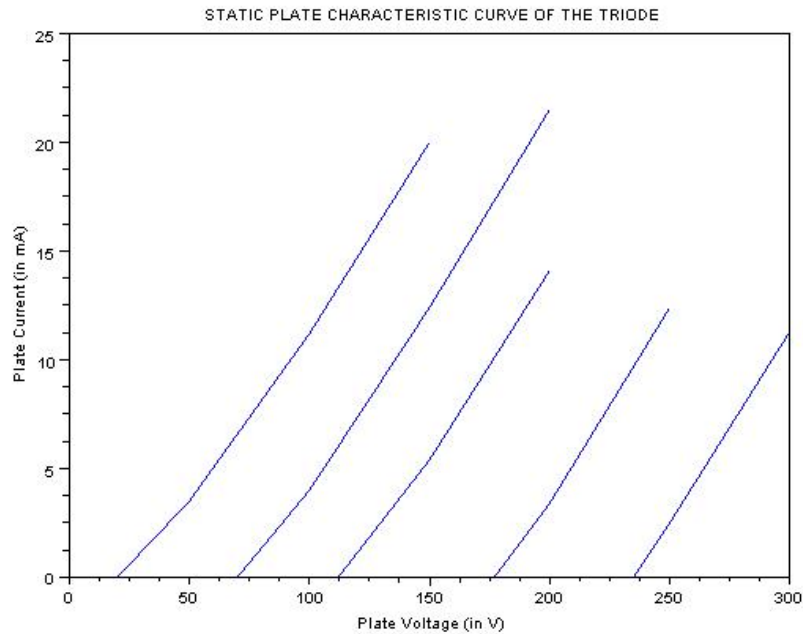


Figure 6.2: Plotting of Static Plate Characteristics

```

19 dIp=2.7*10(-3); //A
20 rp=dVp/dIp; //Dynamic Plate Resistance
21 //Displaying The Results in Command Window
22 printf("\n\t The Dynamic Plate Resistance is rp= %f
    Ohms .",rp);

```

Scilab code Exa 6.2 Plotting of Static Plate Characteristics

```

1 //Example 6.2
2 //Program to Plot the Static Plate Characteristics
  and Determine //Plate AC Resistance , Mutual

```

Conductance & Amplification Factor

```
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 //All Values Extrapolated to Touch x-axis
8 V0=[20 50 100 150]; //V
9 V1=[70 100 150 200]; //V
10 V2=[112 150 200]; //V
11 V3=[177 200 250]; //V
12 V4=[235 250 300]; //V
13 I0=[0 3.5 11.2 20]; //mA
14 I1=[0 4 12.4 21.5]; //mA
15 I2=[0 5.4 14.1]; //mA
16 I3=[0 3.4 12.4]; //mA
17 I4=[0 2.5 11.3]; //mA
18 //Plotting
19 plot(V0,I0);
20 plot(V1,I1);
21 plot(V2,I2);
22 plot(V3,I3);
23 plot(V4,I4);
24 a= gca ();
25 xlabel ('Plate Voltage (in V)');
26 ylabel ('Plate Current (in mA)');
27 title ('STATIC PLATE CHARACTERISTIC CURVE OF THE
        TRIODE');
28 //Calculation
29 //Values from Characteristic Plot
30 dip=(14.0-10.7)*10(-3); //A
31 dvp=20; //V
32 rp=dvp/dip;
33 diP=(12.4-5.3)*10(-3); //A
34 dvG=1; //V
35 gm=diP/dvG;
36 u=gm*rp;
37 ut=(192-150)/1;
38 //Displaying The Results in Command Window
```

```
39 printf("\n\t The Plate AC Resistance is rp= %f kOhms
    .",rp/10^(3));
40 printf("\n\t The Mutual Conductance is gm= %f mS .",
    gm/10^(-3));
41 printf("\n\t The Graphical Amplification Factor is u
    = %f .",u);
42 printf("\n\t The Theoretical Amplification Factor is
    ut= %f .",ut);
```

Chapter 7

TRANSISTOR BIASING AND STABILIZATION OF OPERATING POINT

Scilab code Exa 7.1 Calculate I_c and V_{ce} for given Circuit

```
1 //Example 7.1
2 //Program to Calculate
3 //(a) Collector Current
4 //(b) Collector-to-Emitter Voltage
5 clear all;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=9; //V
10 Rb=300*10^3; //Ohms
11 Rc=2*10^3; //Ohms
12 Beeta=50;
13 //Calculation
14 Ib=(Vcc)/Rb;
15 Ic=Beeta*Ib;
16 Icsat=Vcc/Rc;
17 Vce=Vcc-Ic*Rc;
```

```

18 //Displaying The Results in Command Window
19 printf("The different Parameters are \n\t Ib = %f uA
    .",Ib/10(-6));
20 if Ic < Icsat then
21     disp("Transistor is not in Saturation");
22     printf("\n\t Ic = %f mA .",Ic/10(-3));
23     printf("\n\t Vce = %f V .",Vce);
24 else
25     disp("Transistor is in Saturation");
26     printf("\n\t Ic = %f mA .",Icsat/10(-3));
27     printf("\n\t Vce = %f V .",0);
28 end

```

Scilab code Exa 7.2 Calculate coordinates of Operating Point

```

1 //Example 7.2
2 //Program to Calculate Operating Point Coordinates
  of the Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=10; //V
8 Rb=100*103; //Ohms
9 Rc=1*103; //Ohms
10 Beeta=60;
11 //Calculation
12 Ib=(Vcc)/Rb;
13 Ic=Beeta*Ib;
14 Icsat=Vcc/Rc;
15 Vce=Vcc-Ic*Rc;
16 //Displaying The Results in Command Window
17 printf("The Operating Point Coordinates of the
    Circuit are :\n\t Ib = %f uA .",Ib/10(-6));
18 if Ic < Icsat then

```

```

19     disp("Transistor is not in Saturation");
20     printf("\n\t Ic = %f mA .",Ic/10^(-3));
21     printf("\n\t Vce = %f V .",Vce);
22 else
23     disp("Transistor is in Saturation");
24     printf("\n\t Ic = %f mA .",Icsat/10^(-3));
25     printf("\n\t Vce = %f V .",0);
26 end

```

Scilab code Exa 7.3 Quiescent Operating Point Determination

```

1 //Example 7.3
2 //Program to Calculate Operating Point Coordinates
  of the Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=10; //V
8 Rb=100*10^3; //Ohms
9 Rc=1*10^3; //Ohms
10 Beeta=150;
11 //Calculation
12 Ib=(Vcc)/Rb;
13 Ic=Beeta*Ib;
14 Icsat=Vcc/Rc;
15 Vce=Vcc-Ic*Rc;
16 //Displaying The Results in Command Window
17 printf("The Operating Point Coordinates of the
  Circuit are :\n\t Ib = %f uA .",Ib/10^(-6));
18 if Ic < Icsat then
19     disp("Transistor is not in Saturation");
20     printf("\n\t Ic = %f mA .",Ic/10^(-3));
21     printf("\n\t Vce = %f V .",Vce);
22 else

```

```

23     disp("Transistor is in Saturation");
24     printf("\n\t Ic = %f mA .",Icsat/10^(-3));
25     printf("\n\t Vce = %f V .",0);
26 end

```

Scilab code Exa 7.4.a Calculate value of Resistance Rb

```

1 //Example 7.4 (a)
2 //Program to Calculate Value of Rb in the Biasing
   Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=6; //V
8 Vbe=0.3; //V
9 Icbo=2*10^(-6); //A
10 Ic=1*10^(-3); //A
11 Beeta=20;
12 //Calculation
13 //Case 1: Considering Icbo and Vbe in the
   calculations
14 Ib=(Ic-(Beeta+1)*Icbo)/Beeta;
15 Rb1=(Vcc-Vbe)/Ib;
16 //Case 2: Neglecting Icbo and Vbe in the
   calculations
17 Ib=Ic/Beeta;
18 Rb2=Vcc/Ib;
19 //Percentage Error
20 E=(Rb2-Rb1)/Rb1*100;
21 //Displaying The Results in Command Window
22 printf("\n\t The Base Resistance is , Rb = %f kOhms .
   ",Rb1/10^3);
23 printf("\n\t The Base Resistance (Neglecting Icbo
   and Vbe) is , Rb = %f kOhms .",Rb2/10^3);

```

```
24 printf("\n\t Percentage Error is = %f percent .",E);
```

Scilab code Exa 7.4.b Calculation of Collector Current I_c

```
1 //Example 7.4 (b)
2 //Program to Calculate  $R_b$  in the Biasing Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7  $I_{cbo}=10*10^{-6}$ ; //A
8  $I_b=47.9*10^{-6}$ ; //A
9 Beeta=25;
10 //Calculation
11  $I_c=Beeta*I_b+(Beeta+1)*I_{cbo}$ ;
12 //Displaying The Results in Command Window
13 printf("The Collector Current is :");
14 printf("\n\t  $I_c = %f$  mA .", $I_c/10^{-3}$ );
```

Scilab code Exa 7.5 Calculation of I_e and V_c in the Circuit

```
1 //Example 7.5
2 //Program to Calculate
3 //(a)  $I_e$ 
4 //(b)  $V_c$ 
5 clear all;
6 clc ;
7 close ;
8 //Given Circuit Data
9  $V_{cc}=10$ ; //V
10  $R_c=500$ ; //Ohms
11  $R_b=500*10^3$ ; //Ohms
12 Beeta=100;
```

```

13 // Calculation
14 Ib=Vcc/(Rb+Beeta*Rc);
15 Ic=Beeta*Ib;
16 Ie=Ic;
17 Vce=Vcc-Ic*Rc;
18 Vc=Vce;
19 // Displaying The Results in Command Window
20 printf("The Different Parameters are :");
21 printf("\n\t Ie = %f mA .",Ie/10(-3));
22 printf("\n\t Vc = %f V .",Vc);

```

Scilab code Exa 7.6 Calculate Minimum and Maximum Collector Currents

```

1 //Example 7.6
2 //Program to Calculate
3 //(a)Minimum Collector Current
4 //(b)Maximum Collector Current
5 clear all;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=20; //V
10 Rc=2*103; //Ohms
11 Rb=200*103; //Ohms
12 Beeta1=50;
13 Beeta2=200;
14 // Calculation CASE-1: Minimum Collector Current
15 Ibmin=Vcc/(Rb+Beeta1*Rc);
16 Icmin=Beeta1*Ibmin;
17 // Calculation CASE-2: Maximum Collector Current
18 Ibmax=Vcc/(Rb+Beeta2*Rc);
19 Icmax=Beeta2*Ibmax;
20 // Displaying The Results in Command Window
21 printf("\n\t The Minimum Collector Current Ic(min) =

```

```
    %f mA .",Icmin/10(-3));  
22 printf("\n\t The Maximum Collector Current Ic(max) =  
    %f mA .",Icmax/10(-3));
```

Scilab code Exa 7.7 Calculate Values of the three Currents

```
1 //Example 7.7  
2 //Program to Calculate  
3 //(a) Ib  
4 //(b) Ic  
5 //(c) Ie  
6 clear all;  
7 clc ;  
8 close ;  
9 //Given Circuit Data  
10 Vcc=10; //V  
11 Rc=2*103; //Ohms  
12 Rb=1*106; //Ohms  
13 Re=1*103; //Ohms  
14 Beeta=100;  
15 //Calculation  
16 Ib=Vcc/(Rb+(Beeta+1)*Re);  
17 Ic=Beeta*Ib;  
18 Ie=Ic+Ib;  
19 //Displaying The Results in Command Window  
20 printf("\n\t The Collector Current Ic = %f mA .",Ic  
    /10(-3));  
21 printf("\n\t The Base Current Ib = %f uA .",Ib  
    /10(-6));  
22 printf("\n\t The Emitter Current Ie = %f mA .",Ie  
    /10(-3));
```

Scilab code Exa 7.8 Calculate Minimum and Maximum I_e and corresponding V_{ce}

```
1 //Example 7.8
2 //Program to Calculate
3 //(a)Minimum Emitter Current & corresponding Vce
4 //(b)Maximum Emitter Current & corresponding Vce
5 clear all;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=6; //V
10 Vbe=0.3; //V
11 Rc=50; //Ohms
12 Rb=10*10^3; //Ohms
13 Re=100; //Ohms
14 Beeta1=50;
15 Beeta2=200;
16 //Calculation CASE-1: Minimum Emitter Current &
    corresponding Vce
17 Iemin=(Vcc-Vbe)*(Beeta1+1)/(Rb+(Beeta1+1)*Re);
18 Vcemin=Vcc-(Rc+Re)*Iemin;
19 //Calculation CASE-2: Maximum Emitter Current &
    corresponding Vce
20 Iemax=(Vcc-Vbe)*(Beeta2+1)/(Rb+(Beeta2+1)*Re);
21 Vcemax=Vcc-(Rc+Re)*Iemax;
22 //Displaying The Results in Command Window
23 printf("\n\t The Minimum Emitter Current Ie(min) =
    %f mA .",Iemin/10^(-3));
24 printf("\n\t The Corresponding Vce = %f V .",Vcemin)
    ;
25 printf("\n\t The Maximum Emitter Current Ie(max) =
    %f mA .",Iemax/10^(-3));
26 printf("\n\t The Corresponding Vce = %f V .",Vcemax)
    ;
```

Scilab code Exa 7.9 Determine the new Q Points

```
1 //Example 7.9
2 //Program to Calculate new Q points for
3 //Minimum and Maximum value of Beeta
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Vcc=6; //V
9 Vbe=0.3; //V
10 Rc=1*10^3; //Ohms
11 Rb=10*10^3; //Ohms
12 Re=100; //Ohms
13 Beeta1=50;
14 Beeta2=200;
15 //Calculation CASE-1: Minimum Emitter Current &
    corresponding Vce
16 Iemin=(Vcc-Vbe)*(Beeta1+1)/(Rb+(Beeta1+1)*Re);
17 Iemin=Iemin;
18 Vcemin=Vcc-(Rc+Re)*Iemin;
19 //Calculation CASE-2: Maximum Emitter Current &
    corresponding Vce
20 Iemax=(Vcc-Vbe)*(Beeta2+1)/(Rb+(Beeta2+1)*Re);
21 Iemax=Iemax;
22 Vcemax=Vcc-(Rc+Re)*Iemax;
23 //Displaying The Results in Command Window
24 Icsat=Vcc/(Rc+Re);
25 //Displaying The Results in Command Window
26 printf("For Beeta=50 :\n\t");
27 if Iemin < Icsat then
28     disp("Transistor is not in Saturation");
29     printf("\n\t Ic = %f mA .",Iemin/10^(-3));
30     printf("\n\t Vc = %f V .",Vcemin);
```

```

31 else
32     disp("Transistor is in Saturation");
33     printf("\n\t Ic(sat) = %f mA .",Icsat/10^(-3));
34     printf("\n\t Vc(sat) = %f V .",0);
35 end
36 printf("\nFor Beeta=200 :\n\t");
37 if Icmax < Icsat then
38     disp("Transistor is not in Saturation");
39     printf("\n\t Ic = %f mA .",Icmax/10^(-3));
40     printf("\n\t Vc = %f V .",Vce);
41 else
42     disp("Transistor is in Saturation");
43     printf("\n\t Ic(sat) = %f mA .",Icsat/10^(-3));
44     printf("\n\t Vc(sat) = %f V .",0);
45 end

```

Scilab code Exa 7.10 Calculate the value of Rb

```

1 //Example 7.10
2 //Program to Calculate Rb in the Biasing Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=9; //V
8 Vce=3; //V
9 Re=500; //Ohms
10 Ic=8*10^(-3); //A
11 Beeta=80;
12 //Calculation
13 Ib=Ic/Beeta;
14 Rb=(Vcc-(Beeta+1)*Ib*Re)/Ib;
15 //Displaying The Results in Command Window
16 printf("The Base Resistance is :");
17 printf("\n\t Rb = %f kOhms .",Rb/10^3);

```

Scilab code Exa 7.11 Calculate DC bias Voltages and Currents

```
1 //Example 7.11
2 //Program to Calculate DC Bias Voltages and Currents
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=12; //V
8 Vbe=0.3; //V
9 R1=40*10^3; //Ohms
10 R2=5*10^3; //Ohms
11 Re=1*10^3; //Ohms
12 Rc=5*10^3; //Ohms
13 Beeta=60;
14 //Calculation
15 Vb=(R2/(R1+R2))*Vcc;
16 Ve=Vb-Vbe;
17 Ie=Ve/Re;
18 Ic=Ie;
19 Vc=Vcc-Ic*Rc;
20 Vce=Vc-Ve;
21 //Displaying The Results in Command Window
22 printf("The Different Parameters are :");
23 printf("\n\t Vb = %f V .",Vb);
24 printf("\n\t Ve = %f V .",Ve);
25 printf("\n\t Ie = %f mA .",Ie/10^(-3));
26 printf("\n\t Ic = %f mA .",Ic/10^(-3));
27 printf("\n\t Vc = %f V .",Vc);
28 printf("\n\t Vce = %f V .",Vce);
```

Scilab code Exa 7.12 Calculate Re and Vce in the Circuit

```

1 //Example 7.12
2 //Program to Calculate Re and Vce of the given
   Circuit Specifications
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=15; //V
8 R1=200; //Ohms
9 R2=100; //Ohms
10 Rc=20; //Ohms
11 Ic=100*10(-3); //A
12 //Calculation
13 Ie=Ic;
14 Vb=(R2/(R1+R2))*Vcc;
15 Ve=Vb; // Neglecting Vbe
16 Re=Ve/Ie;
17 Vce=Vcc-(Rc+Re)*Ic;
18 //Displaying The Results in Command Window
19 printf("\n\t The Emitter Resistance is Re = %f Ohms
   .",Re);
20 printf("\n\t The Collector to Emitter Voltage is Vce
   = %f V.",Vce);

```

Scilab code Exa 7.13 Calculate Ic and Vce for given Circuit

```

1 //Example 7.13
2 ///Program to Calculate Ic and Vce of the given
   Circuit Specifications
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=12; //V
8 Vbe=0.3; //V

```

```

 9 R1=40*10^3; //Ohms
10 R2=5*10^3; //Ohms
11 Re=1*10^3; //Ohms
12 Rc=5*10^3; //Ohms
13 Beeta=60;
14 //Calculation
15 Vth=(R2/(R1+R2))*Vcc;
16 Rth=R1*R2/(R1+R2);
17 Ib=(Vth-Vbe)/(Rth+Beeta*Re);
18 Ic=Beeta*Ib;
19 Vce=Vcc-Ic*(Rc+Re);
20 //Displaying The Results in Command Window
21 printf("The Different Parameters are :");
22 printf("\n\t Ic = %f mA .",Ic/10^(-3));
23 printf("\n\t Vce = %f V .",Vce);

```

Scilab code Exa 7.14 Calculate Ic and Vce for given Circuit

```

1 //Example 7.14
2 //Program to Calculate
3 //(a) Ic
4 //(b) Vce
5 clear all;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=12; //V
10 Vee=15; //V
11 Rc=5*10^3; //Ohms
12 Re=10*10^3; //Ohms
13 Rb=10*10^3; //Ohms
14 Beeta=100;
15 //Calculation
16 Ie=Vee/Re;
17 Ic=Ie;

```

```
18 Vce=Vcc-Ic*Rc;
19 //Displaying The Results in Command Window
20 printf("The Parameters are :");
21 printf("\n\t Ic = %f mA .",Ic/10(-3));
22 printf("\n\t Vce = %f V .",Vce);
```

Chapter 8

SMALL SIGNAL AMPLIFIERS

Scilab code Exa 8.1 Determination of Hybrid Parameters

```
1 //Example 8.1
2 //Refer Figure 8.15 and 8.16 in the Textbook
3 //Program to find the Hybrid Parameters from the
  given Transistor Characteristics
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Ic=2*10(-3); //A
9 Vce=8.5; //V
10 //Calculation
11 //hfe=delta(ic)/delta(ib),Vce=constant
12 hfe=(2.7-1.7)*10(-3)/((20-10)*10(-6));
13 //hoe=delta(ic)/delta(Vce),ib=constant
14 hoe=(2.2-2.1)*10(-3)/(10-7);
15 //hie=delta(Vbe)/delta(ib),Vce=constant
16 hie=(0.73-0.715)/((20-10)*10(-6));
17 //hre=delta(Vbe)/delta(Vce),ib=constant
18 hre=(0.73-0.72)/(20-0);
```

```

19 //Displaying The Results in Command Window
20 printf("\n\t The Hybrid Parameters are:");
21 printf("\n\n\t hfe = %f ",hfe);
22 printf("\n\t hoe = %f uS",hoe/10(-6));
23 printf("\n\t hie = %f kOhms",hie/10(3));
24 printf("\n\t hre = %f ",hre);

```

Scilab code Exa 8.2.a Calculation of Input Impedance of Amplifier

```

1 //Example 8.2 (a)
2 //Program to find the Input Impedance of the
  Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 ri=2*10(3); //Ohms
8 Rb=150*10(3); //Ohms
9 //Calculation
10 Zin=Rb*ri/(Rb+ri);
11 //Displaying The Results in Command Window
12 printf("\n\t The Input Impedance of the Amplifier is
  Zin = %f kOhms .",Zin/10(3));

```

Scilab code Exa 8.2.b Calculation of Voltage Gain of Amplifier

```

1 //Example 8.2 (b)
2 //Program to find the Voltage Gain of the Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Beeta=100;

```



```

8 ri=2*10^3; //Ohms
9 Rac=5*10^3; //Ohms
10 //Calculation
11 Av=Beeta*Rac/ri;
12 //Displaying The Results in Command Window
13 printf("\n\t The Voltage Gain of the Amplifier is Av
    = %f with phase of 180 degrees .",Av);

```

Scilab code Exa 8.2.c Calculation of Current Gain of Amplifier

```

1 //Example 8.2 (c)
2 //Program to find the Current Gain of the Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 //Let input Current ib=2A
8 ib=2 ; //A, Assumption
9 io=100*ib ;
10 //Calculation
11 Ai=io/ib; // Current Gain
12 //Displaying The Results in Command Window
13 printf("\n\t The Current Gain of the Amplifier is Ai
    = %f .",Ai);

```

Scilab code Exa 8.3.a Calculation of Voltage Gain of Amplifier

```

1 //Example 8.3 (a)
2 //Program to find the Voltage Gain of the Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data

```

```

7  Bac=150;
8  rin=2*10^3; //Ohms
9  R1=4.7*10^3; //Ohms
10 R2=12*10^3; //Ohms
11 // Calculation
12 Rac=R1*R2/(R1+R2);
13 Av=Bac*Rac/rin;
14 //Displaying The Results in Command Window
15 printf("\n\t The Voltage Gain of the Amplifier is Av
      = %f with phase of 180 degrees .",Av);

```

Scilab code Exa 8.3.b Calculation of Input Impedance of Amplifier

```

1 //Example 8.3 (b)
2 //Program to find the Input Impedance of the
  Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 rin=2*10^3; //Ohms
8 R3=75*10^3; //Ohms
9 R4=7.5*10^3; //Ohms
10 // Calculation
11 Zin=R3*R4*rin/(R3*R4+R4*rin+rin*R3);
12 //Displaying The Results in Command Window
13 printf("\n\t The Input Impedance of the Amplifier is
      Zin = %f kOhms .",Zin/10^3);

```

Scilab code Exa 8.3.c Calculation of Q Point Parameters of Amplifier

```

1 //Example 8.3 (c)
2 //Program to find the Q Point of the Amplifier

```

```

3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=15; //V
8 R1=75*103; //Ohms
9 R2=7.5*103; //Ohms
10 Rc=4.7*103; //Ohms
11 Re=1.2*103; //Ohms
12 // Calculation
13 Vb=Vcc*R2/(R1+R2);
14 Ve=Vb;
15 Ie=Ve/Re;
16 Vce=Vcc-(Rc+Re)*Ie;
17 //Displaying The Results in Command Window
18 printf("\n\t The Different Parameters of the
    Amplifier are Ie = %f mA and Vce = %f V .", Ie
    /10(-3), Vce);

```

Scilab code Exa 8.4 Calculation of Voltage Gain of Amplifier

```

1 //Example 8.4
2 //Program to find the Voltage Gain of the Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 u=20;
8 R1=10*103; //Ohms
9 rp=10*103; //Ohms
10 // Calculation
11 A=u*R1/(rp+R1);
12 //Displaying The Results in Command Window
13 printf("\n\t The Voltage Gain of the Amplifier is A
    = %f with phase of 180 degrees .", A);

```

Scilab code Exa 8.5 Calculation of Gain of Single Stage Amplifier

```
1 //Example 8.5
2 //Program to find the Gain of the Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 gm=3000*10^(-6); //S
8 Rl=22*10^3; //Ohms
9 rp=300*10^3; //Ohms
10 //Calculation
11 //A=-(gm*Rl/(1+(Rl/rp))), For rp>>Rl we get
12 A=gm*Rl; //with Phase of 180 degrees
13 //Displaying The Results in Command Window
14 printf("\n\t The Gain of the Amplifier is A = %f
    with phase of 180 degrees .",A);
```

Scilab code Exa 8.6 Calculation of Output Signal Voltage of FET Amplifier

```
1 //Example 8.6
2 //Program to find the Output Signal Voltage of the
  Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=12*10^3; //Ohms
8 Rg=1*10^6; //Ohms
9 Rs=1*10^3; //Ohms
```

```
10 Cs=25*10^(-6); //F
11 u=20;
12 rd=100*10^3; //Ohms
13 vi=0.1; //V
14 f=1*10^3; //Hz
15 //Calculation
16 Xcs=1/(2*%pi*f*Cs);
17 //As Xcs comes out to be much smaller than Rs, Rs is
    completely bypassed
18 A=u*R1/(R1+rd);
19 vo=A*vi;
20 //Displaying The Results in Command Window
21 printf("\n\t The Output Signal Voltage of the
    Amplifier is vo = %f V .",vo);
```

Chapter 9

MULTI STAGE AMPLIFIERS

Scilab code Exa 9.1 Calculate overall Voltage Gain in dB

```
1 //Example 9.1
2 //Program to Calculate overall Voltage Gain of a
  Multistage
3 //Amplifier in dB
4 clear all;
5 clc ;
6 close ;
7 //Given Data
8 A1=30;
9 A2=50;
10 A3=80;
11 //Calculation
12 A=A1*A2*A3; //Voltage Gain
13 Adb=20*log10(A); //Voltage Gain in dB
14 //Displaying The Results in Command Window
15 printf("\n\t The overall Voltage Gain of the
  Multistage Amplifier Adb = %f dB",Adb);
```

Scilab code Exa 9.2 Calculate Voltage at the Output Terminal

```

1 //Example 9.2
2 //Program to Calculate Voltage at the Output
  Terminal of
3 //Two Stage Direct Coupled Amplifier
4 clear all;
5 clc ;
6 close ;
7 //Given Data
8 Vcc=30; //V
9 Vi=1.4; //V
10 Vbe=0.7; //V
11 B=300; //Beeta
12 R1=27*10^3; //Ohms
13 R2=680; //Ohms
14 R3=24*10^3; //Ohms
15 R4=2.4*10^3; //Ohms
16 //Calculation
17 Ve=Vi-Vbe;
18 Ie1=Vbe/R2;
19 Ic1=Ie1;
20 Vc1=Vcc-Ic1*R1;
21 Vb2=Vc1;
22 Ve2=Vb2-Vbe;
23 Ie2=Ve2/R4;
24 Ic2=Ie2;
25 Vc2=Vcc-Ic2*R3;
26 Vo=Vc2;
27 //Displaying The Results in Command Window
28 printf("\n\t The Voltage at the Output Terminal of
  Two Stage Direct Coupled Amplifier , Vo = %f V",Vo
  );

```

Scilab code Exa 9.3 To Plot the Frequency Response Curve

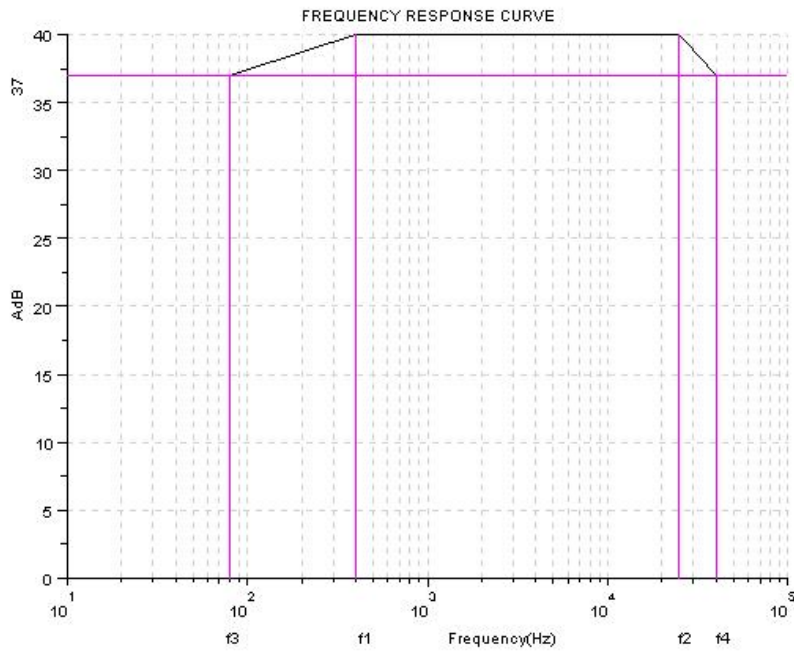


Figure 9.1: To Plot the Frequency Response Curve


```

1 //Example 9.3
2 //Program to Calculate Gain in dB at Cutoff
   Frequencies and
3 //Plot Frequency Response Curve
4 clear all;
5 clc ;
6 close ;
7 //Given Data
8 A=100;
9 f1=400;
10 f2=25*10^3;
11 f3=80;
12 f4=40*10^3;
13 //Calculation
14 Adb=20*log10(A);
15 Adbc=Adb-3; //Lower by 3dB
16 //Displaying The Results in Command Window
17 printf("\n\t The Gain at Cutoff Frequencies is , Adb
   (at Cutoff Frequencies) = %f dB",Adbc);
18 //Plotting the Frequency Response Curve
19 x = [f3 f1 f2 f4];
20 x1= [1 1 1 1];
21 y = [Adbc Adb Adb Adbc];
22 gainplot(y,x1);
23 a = gca();
24 a.y_location = 'left';
25 a.x_location = 'bottom';
26 a.x_label.text = '
   f1 f3
   Frequency (Hz) f2 f4 '
   ;
27 a.y_label.text = '
   AdB
   37 ' ;

28 a.title.text = 'FREQUENCY RESPONSE CURVE';
29 plot2d(x,y);
30 r= [37 37];
31 q = [10 100000];

```

```
32 plot2d2(q,r,6);
33 r2= [37 40 40 37];
34 q2 = [f3 f1 f2 f4];
35 plot2d3(q2,r2,6);
```

Scilab code Exa 9.4.a Calculate Input Impedance of Two Stage RC Coupled Amplifier

```
1 //Example 9.4 (a)
2 //Program to Calculate Input Impedance of the given
3 //Two Stage RC Coupled Amplifier
4 clear all;
5 clc ;
6 close ;
7 //Given Data
8 R1=5.6*10^3; //Ohms
9 R2=56*10^3; //Ohms
10 R3=1.1*10^3; //Ohms
11 //Calculation
12 Zi=R1*R2*R3/(R1*R2+R2*R3+R3*R1);
13 //Displaying The Results in Command Window
14 printf("\n\t The Input Impedance , Zi = %f kOhms ",Zi
        /10^3);
```

Scilab code Exa 9.4.b Calculate Output Impedance of Two Stage RC Coupled Amplifier

```
1 //Example 9.4 (b)
2 //Program to Calculate Output Impedance of the given
3 //Two Stage RC Coupled Amplifier
4 clear all;
5 clc ;
6 close ;
```

```

7 //Given Data
8 Ro1=3.3*10^3; //Ohms
9 Ro2=2.2*10^3; //Ohms
10 //Calculation
11 Zo=Ro1*Ro2/(Ro1+Ro2);
12 //Displaying The Results in Command Window
13 printf("\n\t The Output Impedance , Zo = %f kOhms ",
        Zo/10^3);

```

Scilab code Exa 9.4.c Calculate Voltage Gain of Two Stage RC Coupled Amplifier

```

1 //Example 9.4 (c)
2 //Program to Voltage Gain of the given Two Stage RC
  Coupled Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Data
7 Ro1=3.3*10^3; //Ohms
8 Ro2=2.2*10^3; //Ohms
9 hfe=120;
10 hie=1.1*10^3; //Ohms
11 R1=6.8*10^3; //Ohms
12 R2=56*10^3; //Ohms
13 R3=5.6*10^3; //Ohms
14 R4=1.1*10^3; //Ohms
15 //Calculation
16 Rac2=Ro1*Ro2/(Ro1+Ro2);
17 A2=-hfe*Rac2/hie;
18 Rac1=R1*R2*R3*R4/(R1*R2*R3+R2*R3*R4+R1*R3*R4+R1*R2*
  R4);
19 A1=-hfe*Rac1/hie;
20 A=A1*A2; //Overall Gain
21 //Displaying The Results in Command Window

```

```
22 printf("\n\t The Overall Gain , A = %f .",A);
```

Scilab code Exa 9.5 Calculate Maximum Voltage Gain and Bandwidth of Triode Amplifier

```
1 //Example 9.5
2 //Program to Calculate Maximum Voltage Gain &
   Bandwidth
3 clear all;
4 clc ;
5 close ;
6 //Given Data
7 Rl=10*10^3; //Ohms
8 Rg=470*10^3; //Ohms
9 Cs=100*10^(-12); //F
10 u=25;
11 rp=8*10^3; //Ohms
12 Cc=0.01*10^(-6); //F
13 //Calculation
14 gm=u/rp;
15 Req=rp*Rl*Rg/(rp*Rl+Rl*Rg+Rg*rp);
16 Avm=gm*Req;
17 Avmd=Avm^2; // Voltage Gain of Two Stages
18 Rd=(rp*Rl/(rp+Rl))+Rg;
19 f1=1/(2*pi*Cc*Rd); //Lower Cutoff Frequency
20 f1d=f1/sqrt(sqrt(2)-1); //Lower Cutoff Frequency of
   Two Stages
21 f2=1/(2*pi*Cs*Req); //Upper Cutoff Frequency
22 f2d=f2*sqrt(sqrt(2)-1); //Upper Cutoff Frequency of
   Two Stages
23 BW=f2d-f1d; //Bandwidth
24 //Displaying The Results in Command Window
25 printf("\n\t The Voltage Gain of Two Stages , Avmd =
   %f ",Avmd);
26 printf("\n\t The Bandwidth , BW = %f kHz",BW/10^3);
```


Chapter 10

POWER AMPLIFIERS

Scilab code Exa 10.1 Calculation of Transformer Turns Ratio

```
1 //Example 10.1
2 //Program to Determine the Transformer Turns Ratio
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 RL=16;// Ohms
8 RLd=10*10^3;// Ohms
9 //Calculation
10 N12=sqrt(RLd/RL);//N12=N1/N2
11 //Displaying The Results in Command Window
12 printf("\n\t The Transformer Turns Ratio is N1/N2 =
    %d:%d .",N12,1);
```

Scilab code Exa 10.2 Calculation of Effective Resistance seen at Primary

```
1 //Example 10.2
2 //Program to Determine the Effective Resistance seen
    looking into
```

```

3 //the Primary
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 R1=8; //Ohms
9 N12=15; //N12=N1/N2
10 //Calculation
11 Rld=(N12)^2*R1;
12 //Displaying The Results in Command Window
13 printf("\n\t The Effective Resistance seen looking
        into the Primary, Rld = %f kOhms .",Rld/10^3);

```

Scilab code Exa 10.3.a Calculation of 2nd 3rd and 4th Harmonic Distortions

```

1 //Example 10.3(a)
2 //Program to Determine the Second, Third & Fourth
  Harmonic Distortions
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 //io=15*sin(600*t)+1.5*sin(1200*t)+1.2*sin(1800*t)
  +0.5*sin(2400*t)
8 I1=15;
9 I2=1.5;
10 I3=1.2;
11 I4=0.5;
12 //Calculation
13 D2=(I2/I1)*100;
14 D3=(I3/I1)*100;
15 D4=(I4/I1)*100;
16 //Displaying The Results in Command Window
17 printf("\n\t The Second Harmonic Distortion is, D2 =

```

```

    %f percent .",D2);
18 printf("\n\t The Third Harmonic Distortion is , D3 =
    %f percent .",D3);
19 printf("\n\t The Fourth Harmonic Distortion is , D4 =
    %f percent .",D4);

```

Scilab code Exa 10.3.b Percentage Increase in Power because of Distortion

```

1 //Example 10.3(b)
2 //Program to Determine the Percentage Increase in
  Power because of Distortion
3 clear all;
4 clc ;
5 close ;
6 P1=poly(0,"P1");
7 //Given Circuit Data
8 //io=15*sin(600*t)+1.5*sin(1200*t)+1.2*sin(1800*t)
  +0.5*sin(2400*t)
9 I1=15;
10 I2=1.5;
11 I3=1.2;
12 I4=0.5;
13 //Calculation
14 D2=(I2/I1)*100;
15 D3=(I3/I1)*100;
16 D4=(I4/I1)*100;
17 D=sqrt(D2^2+D3^2+D4^2); //Distortion Factor
18 P=(1+(D/100)^2)*P1;
19 Pi=((P-P1)/P1)*100;
20 //Displaying The Results in Command Window
21 disp(Pi,"The Percentage Increase in Power because of
  Distortion is , Pi (in percent)= ");

```

Chapter 11

TUNED VOLTAGE AMPLIFIERS

Scilab code Exa 11.1.a Calculation of Resonant Frequency

```
1 //Example 11.1 (a)
2 //Program to Calculate Resonant Frequency of the
   given Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 C=300*10(-12); //F
8 L=220*10(-6); //H
9 R=20; //Ohms
10 //Calculation
11 fr=1/(2*%pi*sqrt(L*C));
12 //Displaying The Results in Command Window
13 printf("\n\t The Resonant Frequency , fr = %f kHz .",
   fr/103);
```

Scilab code Exa 11.1.b Calculation of Impedance at Resonance

```
1 //Example 11.1 (b)
2 //Program to Calculate Impedance at Resonance of the
   given Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 C=300*10(-12); //F
8 L=220*10(-6); //H
9 R=20; //Ohms
10 //Calculation
11 Rr=R;
12 //Displaying The Results in Command Window
13 printf("\n\t The Impedance at Resonance , Rr = %f
   Ohms .",Rr);
```

Scilab code Exa 11.1.c Calculation of Current at Resonance

```
1 //Example 11.1 (c)
2 //Program to Calculate the Current at Resonance of
   the given Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 V=10; //V
8 C=300*10(-12); //F
9 L=220*10(-6); //H
10 R=20; //Ohms
11 //Calculation
12 I=V/R;
13 //Displaying The Results in Command Window
14 printf("\n\t The Current at Resonance , I = %f A .",I
```

);

Scilab code Exa 11.1.d Calculation of Voltage across each Component

```
1 //Example 11.1 (d)
2 //Program to Calculate the Voltage across each
  Component of the given Circuit
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 V=10; //V
8 C=300*10(-12); //F
9 L=220*10(-6); //H
10 R=20; //Ohms
11 //Calculation
12 fr=1/(2*%pi*sqrt(L*C));
13 I=V/R;
14 Xl=2*%pi*fr*L;
15 Vl=I*Xl;
16 Xc=1/(2*%pi*fr*C);
17 Vc=I*Xc;
18 Vr=I*R;
19 //Displaying The Results in Command Window
20 printf("\n\t Voltage across the Inductance , Vl = %f
  V .",Vl);
21 printf("\n\t Voltage across the Capacitance , Vc = %f
  V .",Vc);
22 printf("\n\t Voltage across the Resistance , Vr = %f
  V .",Vr);
```

Scilab code Exa 11.2 Calculation of Parameters of the Resonant Circuit at Resonance

```

1 //Example 11.2
2 //Program to Calculate fr , Il , Ic , Line Current &
   Impedance of
3 //the Resonant Circuit at Resonance
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 C=100*10(-12); //F
9 L=100*10(-6); //H
10 R=10; //Ohms
11 V=100; //V
12 //Calculation
13 fr=1/(2*%pi*sqrt(L*C));
14 Xl=2*%pi*fr*L;
15 Il=V/Xl;
16 Xc=1/(2*%pi*fr*C);
17 Ic=V/Xc;
18 Zp=L/(R*C);
19 I=V/Zp;
20 //Displaying The Results in Command Window
21 printf("\n\t The Calculated Values are :");
22 printf("\n\t fr= %f kHz.",fr/103);
23 printf("\n\t Il= %f A.",Il);
24 printf("\n\t Ic= %f A.",Ic);
25 printf("\n\t Zp= %f Ohms .",Zp);
26 printf("\n\t I= %f mA.",I/10(-3));

```

Scilab code Exa 11.3 Calculation of Impedance Q and Bandwidth of Resonant Circuit

```

1 //Example 11.3
2 //Program to Calculate Impedance , Q and Bandwidth of
   the
3 //Resonant Circuit

```

```
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 C=100*10^(-12); //F
9 L=150*10^(-6); //H
10 R=15; //Ohms
11 // Calculation
12 fr=1/(2*%pi*sqrt(L*C));
13 Zp=L/(R*C);
14 Q=2*%pi*fr*L/R;
15 df=fr/Q; //Bandwidth
16 //Displaying The Results in Command Window
17 printf("\n\t The Calculated Values are :");
18 printf("\n\t Impedance , Zp= %f kOhms.",Zp/10^3);
19 printf("\n\t Quality Factor , Q= %f .",Q);
20 printf("\n\t Bandwidth , df= %f kHz .",df/10^3);
```

Chapter 12

FEEDBACK IN AMPLIFIERS

Scilab code Exa 12.1 Calculation of Gain of Negative Feedback Amplifier

```
1 //Example 12.1
2 //Program to Calculate the Gain of a Negative
   Feedback Amplifier with
3 //Given Specifications
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 A=100; //Internal Gain
9 B=1/10; //Feedback Factor
10 //Calculation
11 Af=A/(1+A*B);
12 //Displaying The Results in Command Window
13 printf("\n\t The Value of the Gain of Feedback
   Amplifier is , Af = %f .",Af);
```

Scilab code Exa 12.2 Calculation of Internal Gain and Feedback Gain

```

1 //Example 12.2
2 //Program to Calculate the A(Internal Gain) and
   Beeta(Feedback Gain) of //a Negative Feedback
   Amplifier with given Specifications
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Af=100; //Voltage Gain
8 Vin=50*10(-3); //V , Input Signal without Feedback
   Gain
9 Vi=0.6; //V , Input Signal with Feedback Gain
10 //Calculation
11 Vo=Af*Vi;
12 A=Vo/Vin;
13 B=((A/Af)-1)/A;
14 //Displaying The Results in Command Window
15 printf("\n\t The Value of the Internal Gain A is , A
   = %f .",A);
16 printf("\n\t The Value of the Feedback Gain B is , B
   = %f percent .",B*100);

```

Scilab code Exa 12.3 Calculation of change in overall Gain of Feedback Amplifier

```

1 //Example 12.3
2 //Program to Calculate the change in overall Gain of
   the Feedback //Amplifier with given Gain
   reduction
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 A=1000; //60dB, Voltage Gain
8 B=0.005; //Negative Feedback

```

```

9 dAbyA=-0.12; //dA/A = 12 %
10 //Calculation
11 dAfbyAf=1/(1+A*B)*dAbyA; //dAf/Af=1/(1+A*B)*dA/A
12 //Displaying The Results in Command Window
13 printf("\n\t The change in overall Gain of the
    Feedback Amplifier is , dAf/Af = %f which is
    equivalent to %f percent.",dAfbyAf,dAfbyAf*-100);

```

Scilab code Exa 12.4 Calculation of Input Impedance of the Feedback Amplifier

```

1 //Example 12.4
2 //Program to Calculate the Input Impedance of the
    Feedback Amplifier //with given Specifications
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Zi=1*10^3; //Ohms
8 A=1000; //Voltage Gain
9 B=0.01; //Negative Feedback
10 //Calculation
11 Zid=(1+A*B)*Zi;
12 //Displaying The Results in Command Window
13 printf("\n\t The Value of the Input Impedance of the
    Feedback Amplifier is , Zid = %f kOhms.",Zid
    /10^3);

```

Scilab code Exa 12.5 Calculation of Feedback Factor and Percent change in overall Gain

```

1 //Example 12.5

```



```

2 //Program to Calculate the value of Feedback Factor
   and Percentage //change in overall Gain of the
   Internal Amplifier
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 A=1000; //60dB, Voltage Gain
8 Zo=12000; //Ohms
9 Zod=600; //Ohms
10 dAbyA=0.1; //dA/A = 10 %
11 //Calculation
12 B=((Zo/Zod)-1)/A; //Zod=Zo/(1+A*B)
13 dAfbyAf=1/(1+A*B)*dAbyA; //dAf/Af=1/(1+A*B)*dA/A
14 //Displaying The Results in Command Window
15 printf("\n\t The Feedback Factor of the Feedback
   Amplifier is , B = %f percent .",B*100);
16 printf("\n\t The change in overall Gain of the
   Feedback Amplifier is , dAf/Af = %f percent.",
   dAfbyAf*100);

```

Chapter 13

OSCILLATORS

Scilab code Exa 13.1 Calculate Frequency of Oscillation of Tuned Collector Oscillator

```
1 //Example 13.1
2 //Program to Calculate Frequency of Oscillation of
3 //Tuned Collector Oscillator
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 L=58.6*10(-6); // H
9 C=300*10(-12); // F
10 //Calculation
11 fo=1/(2*%pi*sqrt(L*C));
12 //Displaying The Results in Command Window
13 printf("\n\t The Frequency of Oscillation of Tuned
    Collector Oscillator is fo = %f kHz .",fo/103);
```

Scilab code Exa 13.2 Calculate Frequency of Oscillation of Phase Shift Oscillator

```

1 //Example 13.2
2 //Program to Calculate Frequency of Oscillation of
3 //Vacuum Tube Phase Shift Oscillator
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 R=100*103; // Ohms
9 C=0.01*10(-6); //F
10 //Calculation
11 fo=1/(2*%pi*R*C*sqrt(6));
12 //Displaying The Results in Command Window
13 printf("\n\t The Frequency of Oscillation of Vacuum
    Tube Phase Shift Oscillator is fo = %f Hz .",fo);

```

Scilab code Exa 13.3 Calculate Frequency of Oscillation of Wein Bridge Oscillator

```

1 //Example 13.3
2 //Program to Calculate Frequency of Oscillation of
3 //Wein Bridge Oscillator
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 R1=220*103; // Ohms
9 R2=220*103; // Ohms
10 C1=250*10(-12); //F
11 C2=250*10(-12); //F
12 //Calculation
13 fo=1/(2*%pi*sqrt(R1*C1*R2*C2));
14 //Displaying The Results in Command Window
15 printf("\n\t The Frequency of Oscillation of Wein
    Bridge Oscillator is fo = %f kHz .",fo/103);

```

Chapter 14

ELECTRONIC INSTRUMENTS

Scilab code Exa 14.1 Calculation of Series Resistance for conversion to Voltmeter

```
1 //Example 14.1
2 //Program to Determine the Series Resistance to
  Convert given
3 //d' Arsonval movement into a Voltmeter with the
  specified Range
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Rm=100; //Ohms
9 Is=100*10(-6); //A
10 Vr=100; //V
11 //Calculation
12 Rtotal=Vr/Is;
13 Rs=Rtotal-Rm;
14 //Displaying The Results in Command Window
15 printf("\n\t The Series Resistance to Convert given
  dArsonval movement into a Voltmeter is , Rs = %f
```

```
kOhms ." ,Rs/10^3);
```

Scilab code Exa 14.2 Calculation of Shunt Resistance

```
1 //Example 14.2
2 //Program to Determine the Shunt Resistance required
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rm=100; //Ohms
8 CS=100*10^(-6); //A
9 Imax=10*10^(-3); //A
10 //Calculation
11 Ish=Imax-CS;
12 Rsh=Rm*CS/Ish;
13 //Displaying The Results in Command Window
14 printf("\n\t The Value of Shunt Resistance is , Rsh =
    %f Ohms ." ,Rsh);
```

Scilab code Exa 14.3 Designing of a Universal Shunt for making a Multi Range Milliammeter

```
1 //Example 14.3
2 //Program to Design the Universal Shunt for making
    Multi-Range //Milliammeter with Range 0-1 mA
    ,0-100 mA,0-500 mA,0-1 A
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 CS=100*10^(-6); //A
8 R=100; //Ohms
```

Scilab code Exa 14.4 Determination of Peak and RMS AC Voltage

```
1 //Example 14.4
2 //Program to Determine the AC Voltage
3 clear all;
4 clc ;
5 close ;
6 //Given Circuit Data
7 DS=5; //V/cm, Deflection Sensitivity
8 l=10; //cm, Trace Length
9 //Calculation
10 Vp=DS*l;
11 Vm=Vp/2;
12 V=Vm/sqrt(2);
13 //Displaying The Results in Command Window
14 printf("\n\t The Peak AC Voltage , Vm = %f V .",Vm);
15 printf("\n\t The RMS AC Voltage , V = %f V .",V);
```

Scilab code Exa 14.5 Determination of Magnitude and Frequency of Voltage Fed to Y Input

```
1 //Example 14.5
2 //Program to Determine the Magnitude and the
   Frequency of the
3 //wave Voltage fed to the Y-input
4 clear all;
5 clc ;
6 close ;
7 //Given Circuit Data
```

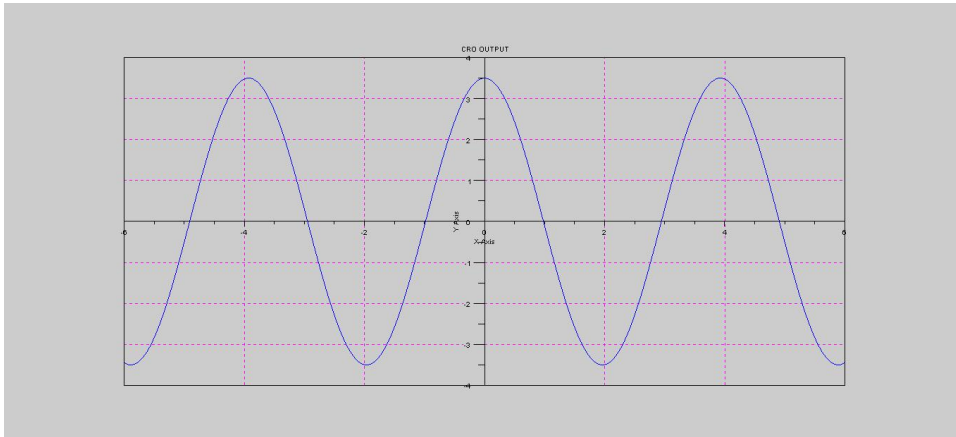


Figure 14.1: Determination of Magnitude and Frequency of Voltage Fed to Y Input

```

8 Am=3.5; //V, Amplitude
9 tb=0.1*10-3; //seconds
10 TP=4; //Time Period
11 // Calculation
12 Vm=2*Am;
13 V=Vm/sqrt(2);
14 T=TP*tb;
15 f=1/T;
16 //Displaying The Results in Command Window
17 printf("\n\t The Magnitude of Wave Voltage , V = %f V
      .",V);
18 printf("\n\t The Frequency of Wave Voltage , f = %f
      kHz .",f/103);
19 //Plot of the given Wave
20 figure
21 x=-6:0.01:6;
22 y=Am*cos(1.6*x); //Given Waveform
23 plot (x,y);
24 a= gca ();
25 a.x_location="origin";
26 a.y_location="origin";
27 xlabel ('X Axis ');

```



```
28 ylabel ('Y Axis');  
29 title ('CRO OUTPUT');  
30 xgrid (6);
```
