

Scilab Textbook Companion for  
Basic Electronics And Linear Circuits  
by N. N. Bhargava, D. C. Kulshreshtha And S.  
C. Gupta<sup>1</sup>

Created by  
Mohammad Faisal Siddiqi  
B.Tech (pursuing)  
Electronics Engineering  
Jamia Millia Islamia, New Delhi  
College Teacher  
Dr. Sajad A. Loan  
Cross-Checked by  
TechPassion

May 19, 2016

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Basic Electronics And Linear Circuits

**Author:** N. N. Bhargava, D. C. Kulshreshtha And S. C. Gupta

**Publisher:** Tata McGraw - Hill Education, New Delhi

**Edition:** 1

**Year:** 2008

**ISBN:** 0074519654

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 INTRODUCTION TO ELECTRONICS	6
2 CURRENT AND VOLTAGE SOURCES	8
4 SEMICONDUCTOR DIODE	12
5 TRANSISTORS	18
6 VACUUM TUBES	25
7 TRANSISTOR BIASING AND STABILIZATION OF OPERATING POINT	30
8 SMALL SIGNAL AMPLIFIERS	44
9 MULTI STAGE AMPLIFIERS	51
10 POWER AMPLIFIERS	59
11 TUNED VOLTAGE AMPLIFIERS	62
12 FEEDBACK IN AMPLIFIERS	67
13 OSCILLATORS	71
14 ELECTRONIC INSTRUMENTS	73

# List of Scilab Codes

Exa 1.1	Resistor Range Calculation using Colour Band Sequence	6
Exa 1.2	Resistor Range Calculation using Colour Band Sequence	7
Exa 2.1	Equivalent Current Source Representation . . . . .	8
Exa 2.2	Equivalent Voltage Source Representation . . . . .	9
Exa 2.3	Current Determination using Voltage Source and Current Source Representations . . . . .	9
Exa 2.4	Output Voltage Determination . . . . .	10
Exa 4.1	DC Voltage and PIV Calculation . . . . .	12
Exa 4.2	DC Voltage and PIV Calculation . . . . .	13
Exa 4.3.a	Peak Value of Current Calculation . . . . .	13
Exa 4.3.b	DC or Average Value of Current Calculation . . . . .	14
Exa 4.3.c	RMS Value of Current Calculation . . . . .	14
Exa 4.3.d	Ripple Factor Determination . . . . .	15
Exa 4.3.e	Rectification Efficiency Calculation . . . . .	15
Exa 4.4	Maximum Permissible Current Determination . . . . .	16
Exa 4.5	Capacitance Determination on changing Bias Voltage . . . . .	17
Exa 5.1	Collector and Base Currents Calculation . . . . .	18
Exa 5.2	Dynamic Input Resistance Determination . . . . .	18
Exa 5.3	Short Circuit Current Gain Determination . . . . .	19
Exa 5.4.a	Common Base Short Circuit Current Gain Calculation . . . . .	20
Exa 5.4.b	Common Emitter Short Circuit Current Gain Calculation . . . . .	20
Exa 5.5	DC Current Gain in Common Base Configuration . . . . .	21
Exa 5.6	Determination of Dynamic Output Resistance and AC and DC Current Gains . . . . .	21
Exa 5.7	Q Point Determination . . . . .	22
Exa 5.8	Calculation of Dynamic Drain Resistance of JFET . . . . .	23
Exa 6.1	Dynamic Plate Resistance of the Diode Determination . . . . .	25

Exa 6.2	Plotting of Static Plate Characteristics . . . . .	27
Exa 7.1	Calculate $I_c$ and $V_{ce}$ for given Circuit . . . . .	30
Exa 7.2	Calculate coordinates of Operating Point . . . . .	31
Exa 7.3	Quiescent Operating Point Determination . . . . .	32
Exa 7.4.a	Calculate value of Resistance $R_b$ . . . . .	33
Exa 7.4.b	Calculation of Collector Current $I_c$ . . . . .	34
Exa 7.5	Calculation of $I_e$ and $V_c$ in the Circuit . . . . .	34
Exa 7.6	Calculate Minimum and Maximum Collector Currents	35
Exa 7.7	Calculate Values of the three Currents . . . . .	36
Exa 7.8	Calculate Minimum and Maximum $I_e$ and correspond- ing $V_{ce}$ . . . . .	36
Exa 7.9	Determine the new Q Points . . . . .	38
Exa 7.10	Calculate the value of $R_b$ . . . . .	39
Exa 7.11	Calculate DC bias Voltages and Currents . . . . .	40
Exa 7.12	Calculate $R_e$ and $V_{ce}$ in the Circuit . . . . .	40
Exa 7.13	Calculate $I_c$ and $V_{ce}$ for given Circuit . . . . .	41
Exa 7.14	Calculate $I_c$ and $V_{ce}$ for given Circuit . . . . .	42
Exa 8.1	Determination of Hybrid Parameters . . . . .	44
Exa 8.2.a	Calculation of Input Impedance of Amplifier . . . . .	45
Exa 8.2.b	Calculation of Voltage Gain of Amplifier . . . . .	45
Exa 8.2.c	Calculation of Current Gain of Amplifier . . . . .	46
Exa 8.3.a	Calculation of Voltage Gain of Amplifier . . . . .	46
Exa 8.3.b	Calculation of Input Impedance of Amplifier . . . . .	47
Exa 8.3.c	Calculation of Q Point Parameters of Amplifier . . . . .	47
Exa 8.4	Calculation of Voltage Gain of Amplifier . . . . .	48
Exa 8.5	Calculation of Gain of Single Stage Amplifier . . . . .	49
Exa 8.6	Calculation of Output Signal Voltage of FET Amplifier	49
Exa 9.1	Calculate overall Voltage Gain in dB . . . . .	51
Exa 9.2	Calculate Voltage at the Output Terminal . . . . .	51
Exa 9.3	To Plot the Frequency Response Curve . . . . .	52
Exa 9.4.a	Calculate Input Impedance of Two Stage RC Coupled Amplifier . . . . .	55
Exa 9.4.b	Calculate Output Impedance of Two Stage RC Coupled Amplifier . . . . .	55
Exa 9.4.c	Calculate Voltage Gain of Two Stage RC Coupled Am- plifier . . . . .	56
Exa 9.5	Calculate Maximum Voltage Gain and Bandwidth of Triode Amplifier . . . . .	57

Exa 10.1	Calculation of Transformer Turns Ratio . . . . .	59
Exa 10.2	Calculation of Effective Resistance seen at Primary . .	59
Exa 10.3.a	Calculation of 2nd 3rd and 4th Harmonic Distortions .	60
Exa 10.3.b	Percentage Increase in Power because of Distortion . .	61
Exa 11.1.a	Calculation of Resonant Frequency . . . . .	62
Exa 11.1.b	Calculation of Impedance at Resonance . . . . .	62
Exa 11.1.c	Calculation of Current at Resonance . . . . .	63
Exa 11.1.d	Calculation of Voltage across each Component . . . . .	64
Exa 11.2	Calculation of Parameters of the Resonant Circuit at Resonance . . . . .	64
Exa 11.3	Calculation of Impedance Q and Bandwidth of Reso- nant Circuit . . . . .	65
Exa 12.1	Calculation of Gain of Negative Feedback Amplifier . .	67
Exa 12.2	Calculation of Internal Gain and Feedback Gain . . . .	67
Exa 12.3	Calculation of change in overall Gain of Feedback Am- plifier . . . . .	68
Exa 12.4	Calculation of Input Impedance of the Feedback Ampli- fier . . . . .	69
Exa 12.5	Calculation of Feedback Factor and Percent change in overall Gain . . . . .	69
Exa 13.1	Calculate Frequency of Oscillation of Tuned Collector Oscillator . . . . .	71
Exa 13.2	Calculate Frequency of Oscillation of Phase Shift Oscil- lator . . . . .	71
Exa 13.3	Calculate Frequency of Oscillation of Wein Bridge Os- cillator . . . . .	72
Exa 14.1	Calculation of Series Resistance for conversion to Voltmeter	73
Exa 14.2	Calculation of Shunt Resistance . . . . .	74
Exa 14.3	Designing of a Universal Shunt for making a Multi Range Milliammeter . . . . .	74
Exa 14.4	Determination of Peak and RMS AC Voltage . . . . .	76
Exa 14.5	Determination of Magnitude and Frequency of Voltage Fed to Y Input . . . . .	76

# List of Figures

6.1	Dynamic Plate Resistance of the Diode Determination . . . .	26
6.2	Plotting of Static Plate Characteristics . . . . .	27
9.1	To Plot the Frequency Response Curve . . . . .	53
14.1	Determination of Magnitude and Frequency of Voltage Fed to Y Input . . . . .	77



# Chapter 1

## INTRODUCTION TO ELECTRONICS

Scilab code Exa 1.1 Resistor Range Calculation using Colour Band Sequence

```
1 //Example 1.1
2 //Program to find Range of a Resistor so as to
   satisfy manufacturer's Tolerances
3 //Colour Band Sequence: YELLOW, VIOLET, ORANGE, GOLD
4 clear;
5 clc ;
6 close ;
7 A=4; //NUMERICAL CODE FOR BAND YELLOW
8 B=7; //NUMERICAL CODE FOR BAND VIOLET
9 C=3; //NUMERICAL CODE FOR BAND ORANGE
10 D=5; //TOLERANCE VALUE FOR BAND GOLD i.e. 5%
11 //Resistor Value Calculation
12 R=(A*10+B)*10^C;
13 //Tolerance Value Calculation
14 T=D*R/100;
15 R1=R-T;
16 R2=R+T;
17 //Displaying The Results in Command Window
```

```

18 printf("\n\n\t Resistor Value is %f kOhms ± %f
    percent.",R/1000,D);
19 printf("\n\n\t Resistor Value is %f kOhms ± %f
    kOhms.",R/1000,T/1000);
20 printf("\n\n\t Range of Values of the Resistor is %f
    kOhms & %f kOhms.",R1/1000,R2/1000);

```

---

**Scilab code Exa 1.2** Resistor Range Calculation using Colour Band Sequence

```

1 //Example 1.2
2 //Program to find Range of a Resistor so as to
    satisfy manufacturer's Tolerances
3 //Colour Band Sequence: GRAY, BLUE, GOLD, GOLD
4 clear;
5 clc ;
6 close ;
7 A=8; //NUMERICAL CODE FOR BAND GRAY
8 B=6; //NUMERICAL CODE FOR BAND BLUE
9 C=-1; //NUMERICAL CODE FOR BAND GOLD
10 D=5; //TOLERANCE VALUE FOR BAND GOLD i.e. 5%
11 //Resistor Value Calculation
12 R=(A*10+B)*10^C;
13 //Tolerance Value Calculation
14 T=D*R/100;
15 R1=R-T;
16 R2=R+T;
17 //Displaying The Results in Command Window
18 printf("\n\n\t Resistor Value is %f Ohms ± %f
    percent.",R,D);
19 printf("\n\n\t Resistor Value is %f Ohms ± %f Ohms.
    ",R,T);
20 printf("\n\n\t Range of Values of the Resistor is %f
    Ohms & %f Ohms.",R1,R2);

```

---

## Chapter 2

# CURRENT AND VOLTAGE SOURCES

Scilab code Exa 2.1 Equivalent Current Source Representation

```
1 //Example 2.1
2 //Program to Obtain Equivalent Current Source
  Representaion from Given Voltage Source
  Representation
3 clear;
4 clc ;
5 close ;
6 //Voltage Source or Thevenin's Representaion (Series
  Voltage Source & Resistor)
7 Vs=2; //Volts
8 Rs=1; //Ohm
9 //Current Source or Norton's Representaion (Parallel
  Current Source & Resistor)
10 Is=Vs/Rs; //Amperes
11 //Displaying The Results in Command Window
12 printf("\n\n\t The Short Circuit Current Value is %f
  Amperes.",Is);
13 printf("\n\n\t The Source Impedence Value is %f Ohm.
  ",Rs);
```

```
14 printf("\n\n\t The Current Source & Source Impedance
    are connected in Parallel.");
```

---

### Scilab code Exa 2.2 Equivalent Voltage Source Representation

```
1 //Example 2.2
2 //Program to Obtain Equivalent Voltage Source
  Representaion from Given Current Source
  Representation
3 clear;
4 clc ;
5 close ;
6 //Current Source or Norton's Representaion (Parallel
  Current Source & Resistor)
7 Is=0.2; //Amperes
8 Zs=100; //Ohms
9 //Voltage Source or Thevenin's Representaion (Series
  Voltage Source & Resistor)
10 Vs=Is*Zs; //Volts
11 //Displaying The Results in Command Window
12 printf("\n\n\t The Open Circuit Voltage is %f Volts.
    ",Vs);
13 printf("\n\n\t The Source Impedence Value is %f Ohms
    .",Zs);
14 printf("\n\n\t The Voltage Source & Source Impedance
    are connected in Series.");
```

---

### Scilab code Exa 2.3 Current Determination using Voltage Source and Current Source Representations

```
1 //Example 2.3
2 //Program to Calculate Current in a Branch by Using
  Current Source Representation
```

```

3 //Verify the Circuit's Result for its equivalence
  with Voltage Source Representation
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Is=1.5*10(-3); //Amperes
9 Zs=2*103; //Ohms
10 Z1=10*103; //Ohms
11 Z2=40*103; //Ohms
12 //Calculation for Current Source Representation
13 Z1=Z1*Z2/(Z1+Z2);
14 I2=Is*Zs/(Zs+Z1);
15 I4I=I2*Z1/(Z1+Z2); //Using Current Divider Rule
16 //Calculation for Current Source Representation
17 Vs=Is*Zs; //Open Circuit Volatge
18 I=Vs/(Zs+Z1);
19 I4V=I*Z1/(Z1+Z2); //Using Current Divider Rule
20 //Displaying The Results in Command Window
21 printf("\n\n\t The Load Current using Current Source
  Representaion is I4I = %f Amperes.",I4I);
22 printf("\n\n\t The Load Current using Voltage Source
  Representaion is I4V = %f Amperes.",I4V);
23 if I4I==I4V then
24 printf("\n\n\t Both Results are Equivalent.");
25 else
26 printf("\n\n\t Both Results are Not Equivalent.");
27 end;

```

---

#### Scilab code Exa 2.4 Output Voltage Determination

```

1 //Example 2.4
2 //Program to Obtain Output Voltage Vo from Given A.C
  . Equivalent of an Amplifier using a Transistor
3 clear;

```

```
4 clc ;
5 close ;
6 //Given Circuit Data
7 //Input Side
8 Vs=10*10(-3); //i.e. 10 mV
9 Rs=1*103; //i.e. 1 kOhms
10 //Output Side
11 Ro1=20*103; //i.e. 20 kOhms
12 Ro2=2*103; //i.e. 2 kOhms
13 //Calculation
14 i=Vs/Rs; //Input Current
15 Io=100*i; //Output Current
16 I1=Io*Ro1/(Ro1+Ro2); //Using Current Divider Rule
17 Vo=I1*Ro2; //Output Volatge
18 //Displaying The Results in Command Window
19 printf("\\n\\t The Output Voltage Vo = %f Volts.",Vo);
```

---

# Chapter 4

## SEMICONDUCTOR DIODE

Scilab code Exa 4.1 DC Voltage and PIV Calculation

```
1 //Example 4.1
2 //Program to determine DC Voltage across the load
  and PIV of the Diode
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vrms=220; //Volts
8 n2=1; //Assumption
9 n1=12*n2; //Turns Ratio
10 //Calculation
11 Vp=sqrt(2)*Vrms; //Maximum(Peak) Primary Voltage
12 Vm=n2*Vp/n1; //Maximum Secondary Voltage
13 Vdc=Vm/%pi; //DC load Voltage
14 //Displaying The Results in Command Window
15 printf("\n\t The DC load Voltage is = %f V .",Vdc);
16 printf("\n\t The Peak Inverse Voltage(PIV) is = %f V
  .",Vm);
```

---

### Scilab code Exa 4.2 DC Voltage and PIV Calculation

```
1 //Example 4.2
2 //Program to determine DC Voltage across the load
  and PIV of the
3 //Centre Tap Rectifier and Bridge Rectifier
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Vrms=220; //Volts
9 n2=1; //Assumption
10 n1=12*n2; //Turns Ratio
11 //Calculation
12 Vp=sqrt(2)*Vrms; //Maximum(Peak) Primary Voltage
13 Vm=n2*Vp/n1; //Maximum Secondary Voltage
14 Vdc=2*Vm/%pi; //DC load Voltage
15 //Displaying The Results in Command Window
16 printf("\n\t The DC load Voltage is = %f V .",Vdc);
17 printf("\n\t The Peak Inverse Voltage(PIV) of Bridge
  Rectifier is = %f V .",Vm);
18 printf("\n\t The Peak Inverse Voltage(PIV) of Centre
  -tap Rectifier is = %f V .",2*Vm);
```

---

### Scilab code Exa 4.3.a Peak Value of Current Calculation

```
1 //Example 4.3(a)
2 //Program to determine the Peak Value of Current
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
```



```

10 //Calculation
11 Im=Vm/(rd+Rl); //Peak Value of Current
12 //Displaying The Results in Command Window
13 printf("\n\t The Peak Value of Current is = %f mA .",
        ,Im/10(-3));

```

---

**Scilab code Exa 4.3.b** DC or Average Value of Current Calculation

```

1 //Example 4.3(b)
2 //Program to determine the DC or Average Value of
  Current
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=1*10(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+Rl); //Peak Value of Current
12 Idc=2*Im/%pi; //DC Value of Current
13 //Displaying The Results in Command Window
14 printf("\n\t The DC or Average Value of Current is =
        %f mA .", Idc/10(-3));

```

---

**Scilab code Exa 4.3.c** RMS Value of Current Calculation

```

1 //Example 4.3(c)
2 //Program to determine the RMS Value of Current
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data

```

```

7 R1=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+R1); //Peak Value of Current
12 Irms=Im/sqrt(2); //RMS Value of Current
13 //Displaying The Results in Command Window
14 printf("\n\t The RMS Value of Current is = %f mA .",
        Irms/10^(-3));

```

---

#### Scilab code Exa 4.3.d Ripple Factor Determination

```

1 //Example 4.3(d)
2 //Program to determine the Ripple Factor of Centre-
   tap Full Wave Rectifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 R1=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+R1); //Peak Value of Current
12 Idc=2*Im/%pi; //DC Value of Current
13 Irms=Im/sqrt(2); //RMS Value of Current
14 r=sqrt((Irms/Idc)^2-1) //Ripple Factor
15 //Displaying The Results in Command Window
16 printf("\n\t The Ripple Factor r = %f .",r);

```

---

#### Scilab code Exa 4.3.e Rectification Efficiency Calculation

```

1 //Example 4.3(e)

```

```

2 //Program to determine the Rectification Efficiency
   of Centre-tap Full Wave Rectifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=1*10^(3); //Ohms
8 rd=10; //Ohms
9 Vm=220; //Volts(Peak Value of Voltage)
10 //Calculation
11 Im=Vm/(rd+Rl); //Peak Value of Current
12 Idc=2*Im/%pi; //DC Value of Current
13 Irms=Im/sqrt(2); //RMS Value of Current
14 Pdc=Idc^2*Rl;
15 Pac=Irms^2*(rd+Rl);
16 n=Pdc/Pac; //Rectification Efficiency
17 //Displaying The Results in Command Window
18 printf("\n\t The Rectification Efficiency n(eeta) =
   %f percent.",n*100);

```

---

#### Scilab code Exa 4.4 Maximum Permissible Current Determination

```

1 //Example 4.4
2 //Program to determine Maximum Current the Given
   Zener Diode can handle
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vz=9.1; //Volts
8 P=364*10^(-3); //Watts
9 //Calculation
10 Iz=P/Vz;
11 //Displaying The Results in Command Window
12 printf("\n\t The Maximum permissible Current is Iz(

```

```
max) = %f mA ." ,Iz/10(-3));
```

---

**Scilab code Exa 4.5** Capacitance Determination on changing Bias Voltage

```
1 //Example 4.5
2 //Program to determine Capacitance of Varactor Diode
   if the
3 //Reverse-Bias Voltage is increased from 4V to 8V
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Ci=18*10(-12); //i.e. 18 pF
9 Vi=4; //Volts
10 Vf=8; //Volts
11 //Calculation
12 K=Ci*sqrt(Vi);
13 Cf=K/sqrt(Vf);
14 //Displaying The Results in Command Window
15 printf("\n\t The Final Value of Capacitance is C =
   %f pF ." ,Cf/10(-12));
```

---

# Chapter 5

## TRANSISTORS

Scilab code Exa 5.1 Collector and Base Currents Calculation

```
1 //Example 5.1
2 //Program to Calculate Collector and Base Currents
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 alpha=0.98; //alpha(dc)
8 Ico=1*10(-6); //Ampere
9 Ie=1*10(-3); //Ampere
10 //Calculation
11 Ic=alpha*Ie+Ico; //Collector Current
12 Ib=Ie-Ic; //Base Current
13 //Displaying The Results in Command Window
14 printf("\n\t The Collector Current is Ic= %f mA .",
        Ic/10(-3));
15 printf("\n\t The Base Current is Ib= %f uA .",Ib
        /10(-6));
```

---

Scilab code Exa 5.2 Dynamic Input Resistance Determination

```

1 //Example 5.2
2 //Program to Determine Dynamic Input Resistance of
   the Transistor at //the point: Ie=0.5 mA and Vcb=
   -10 V.
3 clear;
4 clc ;
5 close ;
6 //From the Input Characteristics
7 dIe=(0.7-0.3)*10(-3); //A
8 dVeb=(0.7-0.62); //V
9 //Calculation
10 ri=dVeb/dIe; //Dynamic Input Resistance at Vcb= -10
   V
11 //Displaying The Results in Command Window
12 printf("\n\t The Dynamic Input Resistance is ri= %f
   Ohms .",ri);

```

---

**Scilab code Exa 5.3** Short Circuit Current Gain Determination

```

1 //Example 5.3
2 //Program to Determine Short Circuit Current Gain of
   the Transistor
3 clear;
4 clc ;
5 close ;
6 //Given Data
7 dIe=1*10(-3); //A
8 dIc=0.99*10(-3); //A
9 //Calculation
10 hfb=dIc/dIe; //Short Circuit Current Gain
11 //Displaying The Results in Command Window
12 printf("\n\t The Short Circuit Current Gain is alpha
   or hfb= %f .",hfb);

```

---

**Scilab code Exa 5.4.a** Common Base Short Circuit Current Gain Calculation

```
1 //Example 5.4(a)
2 //Program to Determine Common Base Short Circuit
   Current Gain (alpha)
3 //of the Transistor
4 clear;
5 clc ;
6 close ;
7 //Given Data
8 dIe=1*10(-3); //A
9 dIc=0.995*10(-3); //A
10 //Calculation
11 alpha=dIc/dIe; //Common Base Short Circuit Current
   Gain
12 //Displaying The Results in Command Window
13 printf("\n\t The Common Base Short Circuit Current
   Gain is alpha= %f .",alpha);
```

---

**Scilab code Exa 5.4.b** Common Emitter Short Circuit Current Gain Calculation

```
1 //Example 5.4(b)
2 //Program to Determine Common Emitter Short Circuit
   Current Gain (beeta)
3 //of the Transistor
4 clear;
5 clc ;
6 close ;
7 //Given Data
8 dIe=1*10(-3); //A
```

```

9 dIc=0.995*10(-3); //A
10 //Calculation
11 alpha=dIc/dIe; //Common Base Short Circuit Current
    Gain
12 beeta=alpha/(1-alpha); //Common Emitter Short
    Circuit Current Gain
13 //Displaying The Results in Command Window
14 printf("\n\t The Common Emitter Short Circuit
    Current Gain is beeta= %f .",beeta);

```

---

**Scilab code Exa 5.5** DC Current Gain in Common Base Configuration

```

1 //Example 5.5
2 //Program to Determine DC Current Gain in Common
    Base Configuration
3 clear;
4 clc ;
5 close ;
6 //Given Data
7 Beeta=100;
8 //Calculation
9 Alpha=Beeta/(Beeta+1); //DC Current Gain in Common
    Base Configuration
10 //Displaying The Results in Command Window
11 printf("\n\t The DC Current Gain in Common Base
    Configuration is Alpha= %f .",Alpha);

```

---

**Scilab code Exa 5.6** Determination of Dynamic Output Resistance and AC and DC Current Gains

```

1 //Example 5.6
2 //Refer Figure 5.20 in the Textbook

```



```

3 //Program to Determine the Dynamic Output Resistance
4 //DC Current Gain & AC Current Gain from given
   output characteristics
5 clear;
6 clc ;
7 close ;
8 //Given Data
9 Vce=10; //V
10 Ib=30*10(-6); //A
11 //Calculation from Given Output Characteristics at
   Ib = 30uA
12 dVce=(12.5-7.5); //V
13 dic=(3.7-3.5)*10(-3); //A
14 Ic=3.6*10(-3); //A
15 ro=dVce/dic; // Dynamic Output Resistance
16 Beeta_dc=Ic/Ib; // DC Current Gain
17 Beeta_ac=((4.7-3.6)*10(-3))/((40-30)*10(-6)); //AC
   Current Gain, From Graph, Bac=delta(ic)/delta(ib)
   for given Vce
18 //Displaying The Results in Command Window
19 printf("\n\t Dynamic Output Resistance ,ro = %f
   kOhms",ro/10(3));
20 printf("\n\t DC Current Gain ,Bdc = %f ",Beeta_dc);
21 printf("\n\t AC Current Gain ,Bac = %f ",Beeta_ac);

```

---

### Scilab code Exa 5.7 Q Point Determination

```

1 //Example 5.7
2 //Refer Figure 5.27 in the Textbook
3 //Program to Determine the Q point from given
   collector characteristics
4 clear;
5 clc ;
6 close ;

```

```

7 //Given Data
8 Vcc=12; //V
9 Rc=1*10^(3); //Ohms
10 Vbb=10.7; //V
11 Rb=200*10^(3); //Ohms
12 Vbe=0.7; //V
13 //Calculation
14 Ib=(Vbb-Vbe)/Rb;
15 //Value of Ib comes out to be 50uA. A dotted Curve
    is drawn for
16 //Ib=40uA and Ib=60uA. At the Point of Intersection:
17 Vce=6; //V
18 Ic=6*10^(-3); //A
19 //Displaying The Results in Command Window
20 printf("\n\t Q point: \n\n\t Ib = %f uA",Ib/10^(-6))
    ;
21 printf("\n\t Vce = %f V",Vce);
22 printf("\n\t Ic = %f mA",Ic/10^(-3));

```

---

### Scilab code Exa 5.8 Calculation of Dynamic Drain Resistance of JFET

```

1 //Example 5.8
2 //Program to Calculate Dynamic Drain Resistance of
    JFET
3 clear;
4 clc ;
5 close ;
6 //Given Data
7 u=80; // Amplification Factor
8 gm=200*10^(-6); // S, Transconductance
9 //Calculation
10 rd=u/gm; //Dynamic Drain Resistance
11 //Displaying The Results in Command Window
12 printf("\n\t The Dynamic Drain Resistance of JFET is
    rd= %f kOhms.",rd/10^(3));

```



# Chapter 6

## VACUUM TUBES

Scilab code Exa 6.1 Dynamic Plate Resistance of the Diode Determination

```
1 //Example 6.1
2 //Program to Plot the Characteristics and
3 //Determine Dynamic Plate Resistance
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 V=[0 0.5 1 1.5 2]; //V
9 I=[0 1.6 4 6.7 9.8]; //mA
10 //Plotting
11 plot(V,I);
12 a= gca ();
13 xlabel ('Plate Voltage (in V)');
14 ylabel ('Plate Current (in mA)');
15 title ('STATIC CHARACTERISTIC CURVE OF THE DIODE');
16 //Calculation
17 //Values from Characteristic Plot
18 dVp=0.5; //V
```

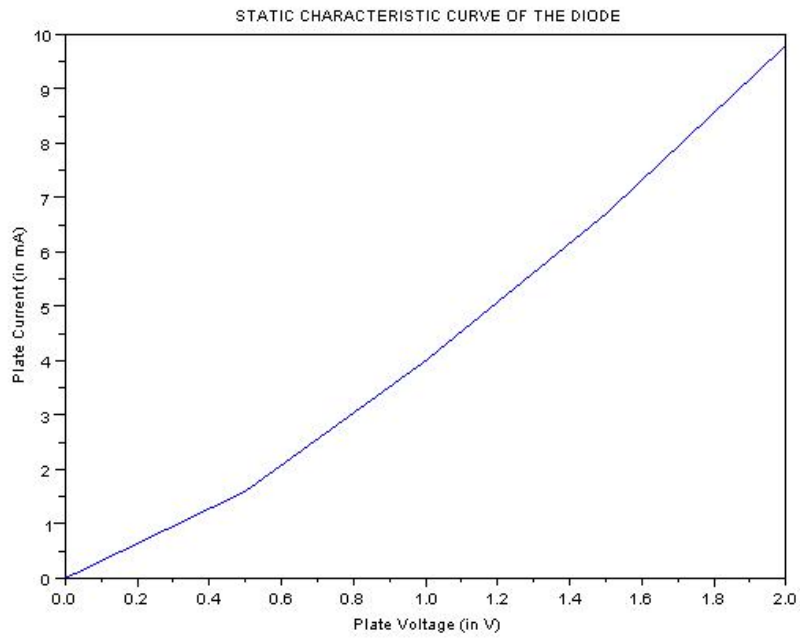


Figure 6.1: Dynamic Plate Resistance of the Diode Determination

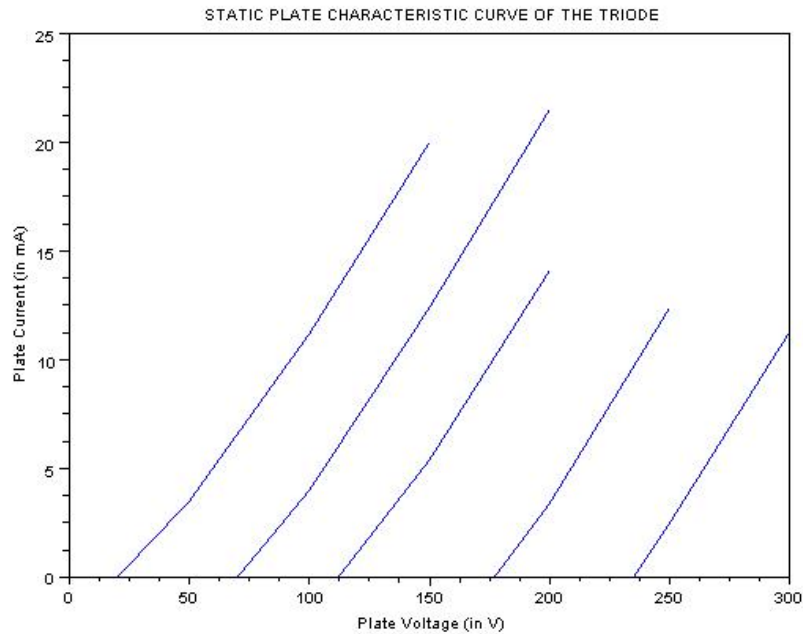


Figure 6.2: Plotting of Static Plate Characteristics

```

19 dIp=2.7*10(-3); //A
20 rp=dVp/dIp; //Dynamic Plate Resistance
21 //Displaying The Results in Command Window
22 printf("\n\t The Dynamic Plate Resistance is rp= %f
    Ohms .",rp);

```

---

**Scilab code Exa 6.2** Plotting of Static Plate Characteristics

```

1 //Example 6.2
2 //Program to Plot the Static Plate Characteristics
  and Determine //Plate AC Resistance , Mutual

```

### Conductance & Amplification Factor

```
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 //All Values Extrapolated to Touch x-axis
8 V0=[20 50 100 150]; //V
9 V1=[70 100 150 200]; //V
10 V2=[112 150 200]; //V
11 V3=[177 200 250]; //V
12 V4=[235 250 300]; //V
13 I0=[0 3.5 11.2 20]; //mA
14 I1=[0 4 12.4 21.5]; //mA
15 I2=[0 5.4 14.1]; //mA
16 I3=[0 3.4 12.4]; //mA
17 I4=[0 2.5 11.3]; //mA
18 //Plotting
19 plot(V0,I0);
20 plot(V1,I1);
21 plot(V2,I2);
22 plot(V3,I3);
23 plot(V4,I4);
24 a= gca ();
25 xlabel ('Plate Voltage (in V)');
26 ylabel ('Plate Current (in mA)');
27 title ('STATIC PLATE CHARACTERISTIC CURVE OF THE
        TRIODE');
28 //Calculation
29 //Values from Characteristic Plot
30 dip=(14.0-10.7)*10(-3); //A
31 dvp=20; //V
32 rp=dvp/dip;
33 diP=(12.4-5.3)*10(-3); //A
34 dvG=1; //V
35 gm=diP/dvG;
36 u=gm*rp;
37 ut=(192-150)/1;
38 //Displaying The Results in Command Window
```

```
39 printf("\n\t The Plate AC Resistance is rp= %f kOhms
    .",rp/10^(3));
40 printf("\n\t The Mutual Conductance is gm= %f mS .",
    gm/10^(-3));
41 printf("\n\t The Graphical Amplification Factor is u
    = %f .",u);
42 printf("\n\t The Theoretical Amplification Factor is
    ut= %f .",ut);
```

---



## Chapter 7

# TRANSISTOR BIASING AND STABILIZATION OF OPERATING POINT

Scilab code Exa 7.1 Calculate  $I_c$  and  $V_{ce}$  for given Circuit

```
1 //Example 7.1
2 //Program to Calculate
3 //(a) Collector Current
4 //(b) Collector-to-Emitter Voltage
5 clear;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=9; //V
10 Rb=300*10^3; //Ohms
11 Rc=2*10^3; //Ohms
12 Beeta=50;
13 //Calculation
14 Ib=(Vcc)/Rb;
15 Ic=Beeta*Ib;
16 Icsat=Vcc/Rc;
17 Vce=Vcc-Ic*Rc;
```

```

18 //Displaying The Results in Command Window
19 printf("The different Parameters are \n\t Ib = %f uA
      .",Ib/10(-6));
20 if Ic < Icsat then
21     disp("Transistor is not in Saturation");
22     printf("\n\t Ic = %f mA .",Ic/10(-3));
23     printf("\n\t Vce = %f V .",Vce);
24 else
25     disp("Transistor is in Saturation");
26     printf("\n\t Ic = %f mA .",Icsat/10(-3));
27     printf("\n\t Vce = %f V .",0);
28 end

```

---

### Scilab code Exa 7.2 Calculate coordinates of Operating Point

```

1 //Example 7.2
2 //Program to Calculate Operating Point Coordinates
  of the Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=10; //V
8 Rb=100*103; //Ohms
9 Rc=1*103; //Ohms
10 Beeta=60;
11 //Calculation
12 Ib=(Vcc)/Rb;
13 Ic=Beeta*Ib;
14 Icsat=Vcc/Rc;
15 Vce=Vcc-Ic*Rc;
16 //Displaying The Results in Command Window
17 printf("The Operating Point Coordinates of the
      Circuit are :\n\t Ib = %f uA .",Ib/10(-6));
18 if Ic < Icsat then

```

```

19     disp("Transistor is not in Saturation");
20     printf("\n\t Ic = %f mA .",Ic/10^(-3));
21     printf("\n\t Vce = %f V .",Vce);
22 else
23     disp("Transistor is in Saturation");
24     printf("\n\t Ic = %f mA .",Icsat/10^(-3));
25     printf("\n\t Vce = %f V .",0);
26 end

```

---

### Scilab code Exa 7.3 Quiescent Operating Point Determination

```

1 //Example 7.3
2 //Program to Calculate Operating Point Coordinates
  of the Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=10; //V
8 Rb=100*10^3; //Ohms
9 Rc=1*10^3; //Ohms
10 Beeta=150;
11 //Calculation
12 Ib=(Vcc)/Rb;
13 Ic=Beeta*Ib;
14 Icsat=Vcc/Rc;
15 Vce=Vcc-Ic*Rc;
16 //Displaying The Results in Command Window
17 printf("The Operating Point Coordinates of the
  Circuit are :\n\t Ib = %f uA .",Ib/10^(-6));
18 if Ic < Icsat then
19     disp("Transistor is not in Saturation");
20     printf("\n\t Ic = %f mA .",Ic/10^(-3));
21     printf("\n\t Vce = %f V .",Vce);
22 else

```

```

23     disp(" Transistor is in Saturation");
24     printf("\n\t Ic = %f mA .",Icsat/10^(-3));
25     printf("\n\t Vce = %f V .",0);
26 end

```

---

#### Scilab code Exa 7.4.a Calculate value of Resistance Rb

```

1 //Example 7.4 (a)
2 //Program to Calculate Value of Rb in the Biasing
  Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=6; //V
8 Vbe=0.3; //V
9 Icbo=2*10^(-6); //A
10 Ic=1*10^(-3); //A
11 Beeta=20;
12 //Calculation
13 //Case 1: Considering Icbo and Vbe in the
  calculations
14 Ib=(Ic-(Beeta+1)*Icbo)/Beeta;
15 Rb1=(Vcc-Vbe)/Ib;
16 //Case 2: Neglecting Icbo and Vbe in the
  calculations
17 Ib=Ic/Beeta;
18 Rb2=Vcc/Ib;
19 //Percentage Error
20 E=(Rb2-Rb1)/Rb1*100;
21 //Displaying The Results in Command Window
22 printf("\n\t The Base Resistance is , Rb = %f kOhms .
  ",Rb1/10^3);
23 printf("\n\t The Base Resistance (Neglecting Icbo
  and Vbe) is , Rb = %f kOhms .",Rb2/10^3);

```

```
24 printf("\n\t Percentage Error is = %f percent .",E);
```

---

#### Scilab code Exa 7.4.b Calculation of Collector Current Ic

```
1 //Example 7.4 (b)
2 //Program to Calculate Rb in the Biasing Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Icbo=10*10(-6); //A
8 Ib=47.9*10(-6); //A
9 Beeta=25;
10 //Calculation
11 Ic=Beeta*Ib+(Beeta+1)*Icbo;
12 //Displaying The Results in Command Window
13 printf("The Collector Current is :");
14 printf("\n\t Ic = %f mA .",Ic/10(-3));
```

---

#### Scilab code Exa 7.5 Calculation of Ie and Vc in the Circuit

```
1 //Example 7.5
2 //Program to Calculate
3 //(a) Ie
4 //(b) Vc
5 clear;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=10; //V
10 Rc=500; //Ohms
11 Rb=500*103; //Ohms
12 Beeta=100;
```

```

13 // Calculation
14 Ib=Vcc/(Rb+Beeta*Rc);
15 Ic=Beeta*Ib;
16 Ie=Ic;
17 Vce=Vcc-Ic*Rc;
18 Vc=Vce;
19 //Displaying The Results in Command Window
20 printf("The Different Parameters are :");
21 printf("\n\t Ie = %f mA .",Ie/10(-3));
22 printf("\n\t Vc = %f V .",Vc);

```

---

**Scilab code Exa 7.6** Calculate Minimum and Maximum Collector Currents

```

1 //Example 7.6
2 //Program to Calculate
3 //(a)Minimum Collector Current
4 //(b)Maximum Collector Current
5 clear;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=20; //V
10 Rc=2*103; //Ohms
11 Rb=200*103; //Ohms
12 Beeta1=50;
13 Beeta2=200;
14 //Calculation CASE-1: Minimum Collector Current
15 Ibmin=Vcc/(Rb+Beeta1*Rc);
16 Icmin=Beeta1*Ibmin;
17 //Calculation CASE-2: Maximum Collector Current
18 Ibmax=Vcc/(Rb+Beeta2*Rc);
19 Icmax=Beeta2*Ibmax;
20 //Displaying The Results in Command Window
21 printf("\n\t The Minimum Collector Current Ic(min) =

```

```
    %f mA .",Icmin/10(-3));  
22 printf("\n\t The Maximum Collector Current Ic(max) =  
    %f mA .",Icmax/10(-3));
```

---

### Scilab code Exa 7.7 Calculate Values of the three Currents

```
1 //Example 7.7  
2 //Program to Calculate  
3 //(a) Ib  
4 //(b) Ic  
5 //(c) Ie  
6 clear;  
7 clc ;  
8 close ;  
9 //Given Circuit Data  
10 Vcc=10; //V  
11 Rc=2*103; //Ohms  
12 Rb=1*106; //Ohms  
13 Re=1*103; //Ohms  
14 Beeta=100;  
15 //Calculation  
16 Ib=Vcc/(Rb+(Beeta+1)*Re);  
17 Ic=Beeta*Ib;  
18 Ie=Ic+Ib;  
19 //Displaying The Results in Command Window  
20 printf("\n\t The Collector Current Ic = %f mA .",Ic  
    /10(-3));  
21 printf("\n\t The Base Current Ib = %f uA .",Ib  
    /10(-6));  
22 printf("\n\t The Emitter Current Ie = %f mA .",Ie  
    /10(-3));
```

---

**Scilab code Exa 7.8** Calculate Minimum and Maximum  $I_e$  and corresponding  $V_{ce}$

```
1 //Example 7.8
2 //Program to Calculate
3 //(a)Minimum Emitter Current & corresponding Vce
4 //(b)Maximum Emitter Current & corresponding Vce
5 clear;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=6; //V
10 Vbe=0.3; //V
11 Rc=50; //Ohms
12 Rb=10*10^3; //Ohms
13 Re=100; //Ohms
14 Beeta1=50;
15 Beeta2=200;
16 //Calculation CASE-1: Minimum Emitter Current &
    corresponding Vce
17 Iemin=(Vcc-Vbe)*(Beeta1+1)/(Rb+(Beeta1+1)*Re);
18 Vcemin=Vcc-(Rc+Re)*Iemin;
19 //Calculation CASE-2: Maximum Emitter Current &
    corresponding Vce
20 Iemax=(Vcc-Vbe)*(Beeta2+1)/(Rb+(Beeta2+1)*Re);
21 Vcemax=Vcc-(Rc+Re)*Iemax;
22 //Displaying The Results in Command Window
23 printf("\n\t The Minimum Emitter Current Ie(min) =
    %f mA .",Iemin/10^(-3));
24 printf("\n\t The Corresponding Vce = %f V .",Vcemin)
    ;
25 printf("\n\t The Maximum Emitter Current Ie(max) =
    %f mA .",Iemax/10^(-3));
26 printf("\n\t The Corresponding Vce = %f V .",Vcemax)
    ;
```

---



### Scilab code Exa 7.9 Determine the new Q Points

```
1 //Example 7.9
2 //Program to Calculate new Q points for
3 //Minimum and Maximum value of Beeta
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Vcc=6; //V
9 Vbe=0.3; //V
10 Rc=1*10^3; //Ohms
11 Rb=10*10^3; //Ohms
12 Re=100; //Ohms
13 Beeta1=50;
14 Beeta2=200;
15 //Calculation CASE-1: Minimum Emitter Current &
    corresponding Vce
16 Iemin=(Vcc-Vbe)*(Beeta1+1)/(Rb+(Beeta1+1)*Re);
17 Iemin=Iemin;
18 Vcemin=Vcc-(Rc+Re)*Iemin;
19 //Calculation CASE-2: Maximum Emitter Current &
    corresponding Vce
20 Iemax=(Vcc-Vbe)*(Beeta2+1)/(Rb+(Beeta2+1)*Re);
21 Iemax=Iemax;
22 Vcemax=Vcc-(Rc+Re)*Iemax;
23 //Displaying The Results in Command Window
24 Icsat=Vcc/(Rc+Re);
25 //Displaying The Results in Command Window
26 printf("For Beeta=50 :\n\t");
27 if Iemin < Icsat then
28     disp("Transistor is not in Saturation");
29     printf("\n\t Ic = %f mA .",Iemin/10^(-3));
30     printf("\n\t Vc = %f V .",Vcemin);
```

```

31 else
32     disp("Transistor is in Saturation");
33     printf("\n\t Ic(sat) = %f mA .",Icsat/10^(-3));
34     printf("\n\t Vc(sat) = %f V .",0);
35 end
36 printf("\nFor Beeta=200 :\n\t");
37 if Icmax < Icsat then
38     disp("Transistor is not in Saturation");
39     printf("\n\t Ic = %f mA .",Icmax/10^(-3));
40     printf("\n\t Vc = %f V .",Vce);
41 else
42     disp("Transistor is in Saturation");
43     printf("\n\t Ic(sat) = %f mA .",Icsat/10^(-3));
44     printf("\n\t Vc(sat) = %f V .",0);
45 end

```

---

**Scilab code Exa 7.10** Calculate the value of Rb

```

1 //Example 7.10
2 //Program to Calculate Rb in the Biasing Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=9; //V
8 Vce=3; //V
9 Re=500; //Ohms
10 Ic=8*10^(-3); //A
11 Beeta=80;
12 //Calculation
13 Ib=Ic/Beeta;
14 Rb=(Vcc-(Beeta+1)*Ib*Re)/Ib;
15 //Displaying The Results in Command Window
16 printf("The Base Resistance is :");
17 printf("\n\t Rb = %f kOhms .",Rb/10^3);

```

---

**Scilab code Exa 7.11** Calculate DC bias Voltages and Currents

```
1 //Example 7.11
2 //Program to Calculate DC Bias Voltages and Currents
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=12; //V
8 Vbe=0.3; //V
9 R1=40*10^3; //Ohms
10 R2=5*10^3; //Ohms
11 Re=1*10^3; //Ohms
12 Rc=5*10^3; //Ohms
13 Beeta=60;
14 //Calculation
15 Vb=(R2/(R1+R2))*Vcc;
16 Ve=Vb-Vbe;
17 Ie=Ve/Re;
18 Ic=Ie;
19 Vc=Vcc-Ic*Rc;
20 Vce=Vc-Ve;
21 //Displaying The Results in Command Window
22 printf("The Different Parameters are :");
23 printf("\n\t Vb = %f V .",Vb);
24 printf("\n\t Ve = %f V .",Ve);
25 printf("\n\t Ie = %f mA .",Ie/10^(-3));
26 printf("\n\t Ic = %f mA .",Ic/10^(-3));
27 printf("\n\t Vc = %f V .",Vc);
28 printf("\n\t Vce = %f V .",Vce);
```

---

**Scilab code Exa 7.12** Calculate Re and Vce in the Circuit

```

1 //Example 7.12
2 //Program to Calculate Re and Vce of the given
   Circuit Specifications
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=15; //V
8 R1=200; //Ohms
9 R2=100; //Ohms
10 Rc=20; //Ohms
11 Ic=100*10(-3); //A
12 //Calculation
13 Ie=Ic;
14 Vb=(R2/(R1+R2))*Vcc;
15 Ve=Vb; // Neglecting Vbe
16 Re=Ve/Ie;
17 Vce=Vcc-(Rc+Re)*Ic;
18 //Displaying The Results in Command Window
19 printf("\n\t The Emitter Resistance is Re = %f Ohms
   .",Re);
20 printf("\n\t The Collector to Emitter Voltage is Vce
   = %f V.",Vce);

```

---

**Scilab code Exa 7.13** Calculate Ic and Vce for given Circuit

```

1 //Example 7.13
2 //Program to Calculate Ic and Vce of the given
   Circuit Specifications
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=12; //V
8 Vbe=0.3; //V

```

```

 9 R1=40*10^3; //Ohms
10 R2=5*10^3; //Ohms
11 Re=1*10^3; //Ohms
12 Rc=5*10^3; //Ohms
13 Beeta=60;
14 //Calculation
15 Vth=(R2/(R1+R2))*Vcc;
16 Rth=R1*R2/(R1+R2);
17 Ib=(Vth-Vbe)/(Rth+Beeta*Re);
18 Ic=Beeta*Ib;
19 Vce=Vcc-Ic*(Rc+Re);
20 //Displaying The Results in Command Window
21 printf("The Different Parameters are :");
22 printf("\n\t Ic = %f mA .",Ic/10^(-3));
23 printf("\n\t Vce = %f V .",Vce);

```

---

**Scilab code Exa 7.14** Calculate Ic and Vce for given Circuit

```

1 //Example 7.14
2 //Program to Calculate
3 //(a) Ic
4 //(b) Vce
5 clear;
6 clc ;
7 close ;
8 //Given Circuit Data
9 Vcc=12; //V
10 Vee=15; //V
11 Rc=5*10^3; //Ohms
12 Re=10*10^3; //Ohms
13 Rb=10*10^3; //Ohms
14 Beeta=100;
15 //Calculation
16 Ie=Vee/Re;
17 Ic=Ie;

```

```
18 Vce=Vcc-Ic*Rc;
19 //Displaying The Results in Command Window
20 printf("The Parameters are :");
21 printf("\n\t Ic = %f mA .",Ic/10^(-3));
22 printf("\n\t Vce = %f V .",Vce);
```

---

# Chapter 8

## SMALL SIGNAL AMPLIFIERS

Scilab code Exa 8.1 Determination of Hybrid Parameters

```
1 //Example 8.1
2 //Refer Figure 8.15 and 8.16 in the Textbook
3 //Program to find the Hybrid Parameters from the
   given Transistor Characteristics
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Ic=2*10(-3); //A
9 Vce=8.5; //V
10 //Calculation
11 //hfe=delta(ic)/delta(ib),Vce=constant
12 hfe=(2.7-1.7)*10(-3)/((20-10)*10(-6));
13 //hoe=delta(ic)/delta(Vce),ib=constant
14 hoe=(2.2-2.1)*10(-3)/(10-7);
15 //hie=delta(Vbe)/delta(ib),Vce=constant
16 hie=(0.73-0.715)/((20-10)*10(-6));
17 //hre=delta(Vbe)/delta(Vce),ib=constant
18 hre=(0.73-0.72)/(20-0);
```

```

19 //Displaying The Results in Command Window
20 printf("\n\t The Hybrid Parameters are:");
21 printf("\n\n\t hfe = %f ",hfe);
22 printf("\n\t hoe = %f uS",hoe/10(-6));
23 printf("\n\t hie = %f kOhms",hie/10(3));
24 printf("\n\t hre = %f ",hre);

```

---

**Scilab code Exa 8.2.a** Calculation of Input Impedance of Amplifier

```

1 //Example 8.2 (a)
2 //Program to find the Input Impedance of the
  Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 ri=2*10(3); //Ohms
8 Rb=150*10(3); //Ohms
9 //Calculation
10 Zin=Rb*ri/(Rb+ri);
11 //Displaying The Results in Command Window
12 printf("\n\t The Input Impedance of the Amplifier is
  Zin = %f kOhms .",Zin/10(3));

```

---

**Scilab code Exa 8.2.b** Calculation of Voltage Gain of Amplifier

```

1 //Example 8.2 (b)
2 //Program to find the Voltage Gain of the Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Beeta=100;

```



```

8 ri=2*10^3; //Ohms
9 Rac=5*10^3; //Ohms
10 //Calculation
11 Av=Beeta*Rac/ri;
12 //Displaying The Results in Command Window
13 printf("\n\t The Voltage Gain of the Amplifier is Av
    = %f with phase of 180 degrees .",Av);

```

---

**Scilab code Exa 8.2.c** Calculation of Current Gain of Amplifier

```

1 //Example 8.2 (c)
2 //Program to find the Current Gain of the Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 //Let input Current ib=2A
8 ib=2 ; //A, Assumption
9 io=100*ib ;
10 //Calculation
11 Ai=io/ib; // Current Gain
12 //Displaying The Results in Command Window
13 printf("\n\t The Current Gain of the Amplifier is Ai
    = %f .",Ai);

```

---

**Scilab code Exa 8.3.a** Calculation of Voltage Gain of Amplifier

```

1 //Example 8.3 (a)
2 //Program to find the Voltage Gain of the Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data

```

```

7 Bac=150;
8 rin=2*10^3; //Ohms
9 R1=4.7*10^3; //Ohms
10 R2=12*10^3; //Ohms
11 // Calculation
12 Rac=R1*R2/(R1+R2);
13 Av=Bac*Rac/rin;
14 //Displaying The Results in Command Window
15 printf("\n\t The Voltage Gain of the Amplifier is Av
      = %f with phase of 180 degrees .",Av);

```

---

**Scilab code Exa 8.3.b** Calculation of Input Impedance of Amplifier

```

1 //Example 8.3 (b)
2 //Program to find the Input Impedance of the
  Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 rin=2*10^3; //Ohms
8 R3=75*10^3; //Ohms
9 R4=7.5*10^3; //Ohms
10 // Calculation
11 Zin=R3*R4*rin/(R3*R4+R4*rin+rin*R3);
12 //Displaying The Results in Command Window
13 printf("\n\t The Input Impedance of the Amplifier is
      Zin = %f kOhms .",Zin/10^3);

```

---

**Scilab code Exa 8.3.c** Calculation of Q Point Parameters of Amplifier

```

1 //Example 8.3 (c)
2 //Program to find the Q Point of the Amplifier

```

```

3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Vcc=15; //V
8 R1=75*103; //Ohms
9 R2=7.5*103; //Ohms
10 Rc=4.7*103; //Ohms
11 Re=1.2*103; //Ohms
12 // Calculation
13 Vb=Vcc*R2/(R1+R2);
14 Ve=Vb;
15 Ie=Ve/Re;
16 Vce=Vcc-(Rc+Re)*Ie;
17 //Displaying The Results in Command Window
18 printf("\n\t The Different Parameters of the
    Amplifier are Ie = %f mA and Vce = %f V .", Ie
    /10(-3), Vce);

```

---

#### Scilab code Exa 8.4 Calculation of Voltage Gain of Amplifier

```

1 //Example 8.4
2 //Program to find the Voltage Gain of the Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 u=20;
8 R1=10*103; //Ohms
9 rp=10*103; //Ohms
10 // Calculation
11 A=u*R1/(rp+R1);
12 //Displaying The Results in Command Window
13 printf("\n\t The Voltage Gain of the Amplifier is A
    = %f with phase of 180 degrees .", A);

```

---

**Scilab code Exa 8.5** Calculation of Gain of Single Stage Amplifier

```
1 //Example 8.5
2 //Program to find the Gain of the Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 gm=3000*10(-6); //S
8 Rl=22*103; //Ohms
9 rp=300*103; //Ohms
10 //Calculation
11 //A=-(gm*Rl/(1+(Rl/rp))), For rp>>Rl we get
12 A=gm*Rl; //with Phase of 180 degrees
13 //Displaying The Results in Command Window
14 printf("\n\t The Gain of the Amplifier is A = %f
    with phase of 180 degrees .",A);
```

---

**Scilab code Exa 8.6** Calculation of Output Signal Voltage of FET Amplifier

```
1 //Example 8.6
2 //Program to find the Output Signal Voltage of the
  Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rl=12*103; //Ohms
8 Rg=1*106; //Ohms
9 Rs=1*103; //Ohms
```

```
10 Cs=25*10^(-6); //F
11 u=20;
12 rd=100*10^3; //Ohms
13 vi=0.1; //V
14 f=1*10^3; //Hz
15 //Calculation
16 Xcs=1/(2*%pi*f*Cs);
17 //As Xcs comes out to be much smaller than Rs, Rs is
    completely bypassed
18 A=u*Rl/(Rl+rd);
19 vo=A*vi;
20 //Displaying The Results in Command Window
21 printf("\n\t The Output Signal Voltage of the
    Amplifier is vo = %f V .",vo);
```

---

## Chapter 9

# MULTI STAGE AMPLIFIERS

**Scilab code Exa 9.1** Calculate overall Voltage Gain in dB

```
1 //Example 9.1
2 //Program to Calculate overall Voltage Gain of a
  Multistage
3 //Amplifier in dB
4 clear;
5 clc ;
6 close ;
7 //Given Data
8 A1=30;
9 A2=50;
10 A3=80;
11 //Calculation
12 A=A1*A2*A3; //Voltage Gain
13 Adb=20*log10(A); //Voltage Gain in dB
14 //Displaying The Results in Command Window
15 printf("\n\t The overall Voltage Gain of the
  Multistage Amplifier Adb = %f dB",Adb);
```

---

**Scilab code Exa 9.2** Calculate Voltage at the Output Terminal

```

1 //Example 9.2
2 //Program to Calculate Voltage at the Output
  Terminal of
3 //Two Stage Direct Coupled Amplifier
4 clear;
5 clc ;
6 close ;
7 //Given Data
8 Vcc=30; //V
9 Vi=1.4; //V
10 Vbe=0.7; //V
11 B=300; //Beeta
12 R1=27*10^3; //Ohms
13 R2=680; //Ohms
14 R3=24*10^3; //Ohms
15 R4=2.4*10^3; //Ohms
16 //Calculation
17 Ve=Vi-Vbe;
18 Ie1=Vbe/R2;
19 Ic1=Ie1;
20 Vc1=Vcc-Ic1*R1;
21 Vb2=Vc1;
22 Ve2=Vb2-Vbe;
23 Ie2=Ve2/R4;
24 Ic2=Ie2;
25 Vc2=Vcc-Ic2*R3;
26 Vo=Vc2;
27 //Displaying The Results in Command Window
28 printf("\n\t The Voltage at the Output Terminal of
  Two Stage Direct Coupled Amplifier , Vo = %f V",Vo
  );

```

---

**Scilab code Exa 9.3** To Plot the Frequency Response Curve

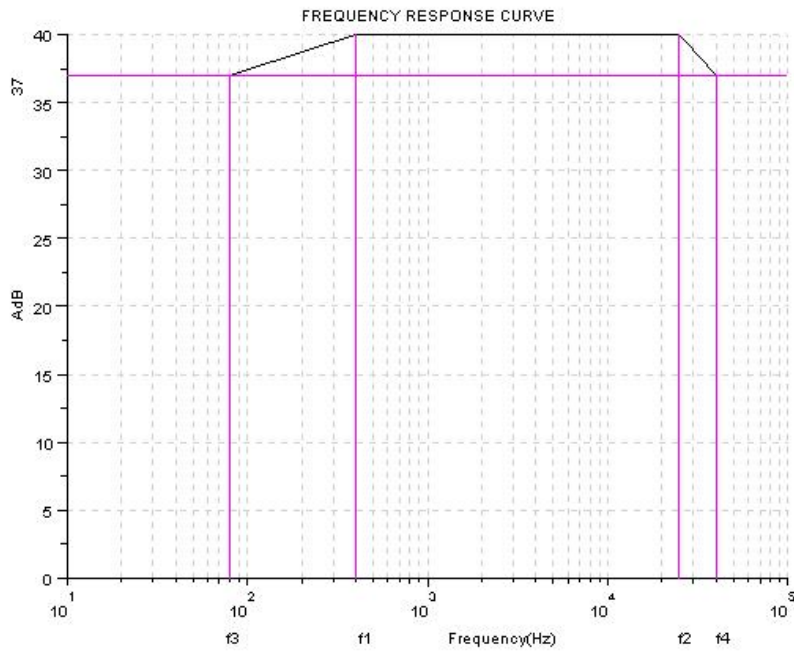


Figure 9.1: To Plot the Frequency Response Curve



```

1 //Example 9.3
2 //Program to Calculate Gain in dB at Cutoff
   Frequencies and
3 //Plot Frequency Response Curve
4 clear;
5 clc ;
6 close ;
7 //Given Data
8 A=100;
9 f1=400;
10 f2=25*10^3;
11 f3=80;
12 f4=40*10^3;
13 //Calculation
14 Adb=20*log10(A);
15 Adbc=Adb-3; //Lower by 3dB
16 //Displaying The Results in Command Window
17 printf("\n\t The Gain at Cutoff Frequencies is , Adb
   (at Cutoff Frequencies) = %f dB",Adbc);
18 //Plotting the Frequency Response Curve
19 x = [f3 f1 f2 f4];
20 x1= [1 1 1 1];
21 y = [Adbc Adb Adb Adbc];
22 gainplot(y,x1);
23 a = gca();
24 a.y_location = 'left';
25 a.x_location = 'bottom';
26 a.x_label.text = '
   f1 f3
   f2 f4 '
   Frequency (Hz)
   ;
27 a.y_label.text = '
   AdB
   37 ' ;

28 a.title.text = 'FREQUENCY RESPONSE CURVE';
29 plot2d(x,y);
30 r= [37 37];
31 q = [10 100000];

```

```
32 plot2d2(q,r,6);
33 r2= [37 40 40 37];
34 q2 = [f3 f1 f2 f4];
35 plot2d3(q2,r2,6);
```

---

**Scilab code Exa 9.4.a** Calculate Input Impedance of Two Stage RC Coupled Amplifier

```
1 //Example 9.4 (a)
2 //Program to Calculate Input Impedance of the given
3 //Two Stage RC Coupled Amplifier
4 clear;
5 clc ;
6 close ;
7 //Given Data
8 R1=5.6*10^3; //Ohms
9 R2=56*10^3; //Ohms
10 R3=1.1*10^3; //Ohms
11 //Calculation
12 Zi=R1*R2*R3/(R1*R2+R2*R3+R3*R1);
13 //Displaying The Results in Command Window
14 printf("\n\t The Input Impedance , Zi = %f kOhms ",Zi
        /10^3);
```

---

**Scilab code Exa 9.4.b** Calculate Output Impedance of Two Stage RC Coupled Amplifier

```
1 //Example 9.4 (b)
2 //Program to Calculate Output Impedance of the given
3 //Two Stage RC Coupled Amplifier
4 clear;
5 clc ;
6 close ;
```

```

7 //Given Data
8 Ro1=3.3*10^3; //Ohms
9 Ro2=2.2*10^3; //Ohms
10 //Calculation
11 Zo=Ro1*Ro2/(Ro1+Ro2);
12 //Displaying The Results in Command Window
13 printf("\n\t The Output Impedance , Zo = %f kOhms ",
        Zo/10^3);

```

---

**Scilab code Exa 9.4.c** Calculate Voltage Gain of Two Stage RC Coupled Amplifier

```

1 //Example 9.4 (c)
2 //Program to Voltage Gain of the given Two Stage RC
  Coupled Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Data
7 Ro1=3.3*10^3; //Ohms
8 Ro2=2.2*10^3; //Ohms
9 hfe=120;
10 hie=1.1*10^3; //Ohms
11 R1=6.8*10^3; //Ohms
12 R2=56*10^3; //Ohms
13 R3=5.6*10^3; //Ohms
14 R4=1.1*10^3; //Ohms
15 //Calculation
16 Rac2=Ro1*Ro2/(Ro1+Ro2);
17 A2=-hfe*Rac2/hie;
18 Rac1=R1*R2*R3*R4/(R1*R2*R3+R2*R3*R4+R1*R3*R4+R1*R2*
  R4);
19 A1=-hfe*Rac1/hie;
20 A=A1*A2; //Overall Gain
21 //Displaying The Results in Command Window

```

```
22 printf("\n\t The Overall Gain , A = %f .",A);
```

---

**Scilab code Exa 9.5** Calculate Maximum Voltage Gain and Bandwidth of Triode Amplifier

```
1 //Example 9.5
2 //Program to Calculate Maximum Voltage Gain &
   Bandwidth
3 clear;
4 clc ;
5 close ;
6 //Given Data
7 Rl=10*10^3; //Ohms
8 Rg=470*10^3; //Ohms
9 Cs=100*10^(-12); //F
10 u=25;
11 rp=8*10^3; //Ohms
12 Cc=0.01*10^(-6); //F
13 //Calculation
14 gm=u/rp;
15 Req=rp*Rl*Rg/(rp*Rl+Rl*Rg+Rg*rp);
16 Avm=gm*Req;
17 Avmd=Avm^2; // Voltage Gain of Two Stages
18 Rd=(rp*Rl/(rp+Rl))+Rg;
19 f1=1/(2*pi*Cc*Rd); //Lower Cutoff Frequency
20 f1d=f1/sqrt(sqrt(2)-1); //Lower Cutoff Frequency of
   Two Stages
21 f2=1/(2*pi*Cs*Req); //Upper Cutoff Frequency
22 f2d=f2*sqrt(sqrt(2)-1); //Upper Cutoff Frequency of
   Two Stages
23 BW=f2d-f1d; //Bandwidth
24 //Displaying The Results in Command Window
25 printf("\n\t The Voltage Gain of Two Stages , Avmd =
   %f ",Avmd);
26 printf("\n\t The Bandwidth , BW = %f kHz",BW/10^3);
```



# Chapter 10

## POWER AMPLIFIERS

Scilab code Exa 10.1 Calculation of Transformer Turns Ratio

```
1 //Example 10.1
2 //Program to Determine the Transformer Turns Ratio
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 RL=16;// Ohms
8 RLd=10*10^3;// Ohms
9 //Calculation
10 N12=sqrt(RLd/RL);//N12=N1/N2
11 //Displaying The Results in Command Window
12 printf("\n\t The Transformer Turns Ratio is N1/N2 =
    %d:%d .",N12,1);
```

---

Scilab code Exa 10.2 Calculation of Effective Resistance seen at Primary

```
1 //Example 10.2
2 //Program to Determine the Effective Resistance seen
    looking into
```

```

3 //the Primary
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 R1=8; //Ohms
9 N12=15; //N12=N1/N2
10 //Calculation
11 Rld=(N12)^2*R1;
12 //Displaying The Results in Command Window
13 printf("\n\t The Effective Resistance seen looking
        into the Primary, Rld = %f kOhms .",Rld/10^3);

```

---

**Scilab code Exa 10.3.a** Calculation of 2nd 3rd and 4th Harmonic Distortions

```

1 //Example 10.3(a)
2 //Program to Determine the Second, Third & Fourth
  Harmonic Distortions
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 //io=15*sin(600*t)+1.5*sin(1200*t)+1.2*sin(1800*t)
  +0.5*sin(2400*t)
8 I1=15;
9 I2=1.5;
10 I3=1.2;
11 I4=0.5;
12 //Calculation
13 D2=(I2/I1)*100;
14 D3=(I3/I1)*100;
15 D4=(I4/I1)*100;
16 //Displaying The Results in Command Window
17 printf("\n\t The Second Harmonic Distortion is, D2 =

```

```

    %f percent .",D2);
18 printf("\n\t The Third Harmonic Distortion is , D3 =
    %f percent .",D3);
19 printf("\n\t The Fourth Harmonic Distortion is , D4 =
    %f percent .",D4);

```

---

**Scilab code Exa 10.3.b** Percentage Increase in Power because of Distortion

```

1 //Example 10.3(b)
2 //Program to Determine the Percentage Increase in
  Power because of Distortion
3 clear;
4 clc ;
5 close ;
6 P1=poly(0,"P1");
7 //Given Circuit Data
8 //io=15*sin(600*t)+1.5*sin(1200*t)+1.2*sin(1800*t)
  +0.5*sin(2400*t)
9 I1=15;
10 I2=1.5;
11 I3=1.2;
12 I4=0.5;
13 //Calculation
14 D2=(I2/I1)*100;
15 D3=(I3/I1)*100;
16 D4=(I4/I1)*100;
17 D=sqrt(D2^2+D3^2+D4^2); //Distortion Factor
18 P=(1+(D/100)^2)*P1;
19 Pi=((P-P1)/P1)*100;
20 //Displaying The Results in Command Window
21 disp(Pi,"The Percentage Increase in Power because of
  Distortion is , Pi (in percent)= ");

```

---



# Chapter 11

## TUNED VOLTAGE AMPLIFIERS

Scilab code Exa 11.1.a Calculation of Resonant Frequency

```
1 //Example 11.1 (a)
2 //Program to Calculate Resonant Frequency of the
   given Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 C=300*10(-12); //F
8 L=220*10(-6); //H
9 R=20; //Ohms
10 //Calculation
11 fr=1/(2*%pi*sqrt(L*C));
12 //Displaying The Results in Command Window
13 printf("\n\t The Resonant Frequency , fr = %f kHz .",
   fr/103);
```

---

### Scilab code Exa 11.1.b Calculation of Impedance at Resonance

```
1 //Example 11.1 (b)
2 //Program to Calculate Impedance at Resonance of the
   given Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 C=300*10(-12); //F
8 L=220*10(-6); //H
9 R=20; //Ohms
10 //Calculation
11 Rr=R;
12 //Displaying The Results in Command Window
13 printf("\n\t The Impedance at Resonance , Rr = %f
   Ohms .",Rr);
```

---

### Scilab code Exa 11.1.c Calculation of Current at Resonance

```
1 //Example 11.1 (c)
2 //Program to Calculate the Current at Resonance of
   the given Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 V=10; //V
8 C=300*10(-12); //F
9 L=220*10(-6); //H
10 R=20; //Ohms
11 //Calculation
12 I=V/R;
13 //Displaying The Results in Command Window
14 printf("\n\t The Current at Resonance , I = %f A .",I
```

);

---

### Scilab code Exa 11.1.d Calculation of Voltage across each Component

```
1 //Example 11.1 (d)
2 //Program to Calculate the Voltage across each
  Component of the given Circuit
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 V=10; //V
8 C=300*10(-12); //F
9 L=220*10(-6); //H
10 R=20; //Ohms
11 //Calculation
12 fr=1/(2*%pi*sqrt(L*C));
13 I=V/R;
14 Xl=2*%pi*fr*L;
15 Vl=I*Xl;
16 Xc=1/(2*%pi*fr*C);
17 Vc=I*Xc;
18 Vr=I*R;
19 //Displaying The Results in Command Window
20 printf("\n\t Voltage across the Inductance , Vl = %f
  V .",Vl);
21 printf("\n\t Voltage across the Capacitance , Vc = %f
  V .",Vc);
22 printf("\n\t Voltage across the Resistance , Vr = %f
  V .",Vr);
```

---

### Scilab code Exa 11.2 Calculation of Parameters of the Resonant Circuit at Resonance

```

1 //Example 11.2
2 //Program to Calculate fr , I1 , Ic , Line Current &
   Impedance of
3 //the Resonant Circuit at Resonance
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 C=100*10(-12); //F
9 L=100*10(-6); //H
10 R=10; //Ohms
11 V=100; //V
12 //Calculation
13 fr=1/(2*%pi*sqrt(L*C));
14 Xl=2*%pi*fr*L;
15 I1=V/Xl;
16 Xc=1/(2*%pi*fr*C);
17 Ic=V/Xc;
18 Zp=L/(R*C);
19 I=V/Zp;
20 //Displaying The Results in Command Window
21 printf("\n\t The Calculated Values are :");
22 printf("\n\t fr= %f kHz.",fr/103);
23 printf("\n\t I1= %f A.",I1);
24 printf("\n\t Ic= %f A.",Ic);
25 printf("\n\t Zp= %f Ohms .",Zp);
26 printf("\n\t I= %f mA.",I/10(-3));

```

---

**Scilab code Exa 11.3** Calculation of Impedance Q and Bandwidth of Resonant Circuit

```

1 //Example 11.3
2 //Program to Calculate Impedance , Q and Bandwidth of
   the
3 //Resonant Circuit

```

```
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 C=100*10^(-12); //F
9 L=150*10^(-6); //H
10 R=15; //Ohms
11 // Calculation
12 fr=1/(2*%pi*sqrt(L*C));
13 Zp=L/(R*C);
14 Q=2*%pi*fr*L/R;
15 df=fr/Q; //Bandwidth
16 //Displaying The Results in Command Window
17 printf("\n\t The Calculated Values are :");
18 printf("\n\t Impedance , Zp= %f kOhms.",Zp/10^3);
19 printf("\n\t Quality Factor , Q= %f .",Q);
20 printf("\n\t Bandwidth , df= %f kHz .",df/10^3);
```

---

# Chapter 12

## FEEDBACK IN AMPLIFIERS

**Scilab code Exa 12.1** Calculation of Gain of Negative Feedback Amplifier

```
1 //Example 12.1
2 //Program to Calculate the Gain of a Negative
   Feedback Amplifier with
3 //Given Specifications
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 A=100; //Internal Gain
9 B=1/10; //Feedback Factor
10 //Calculation
11 Af=A/(1+A*B);
12 //Displaying The Results in Command Window
13 printf("\n\t The Value of the Gain of Feedback
   Amplifier is , Af = %f .",Af);
```

---

**Scilab code Exa 12.2** Calculation of Internal Gain and Feedback Gain

```

1 //Example 12.2
2 //Program to Calculate the A(Internal Gain) and
   Beeta(Feedback Gain) of //a Negative Feedback
   Amplifier with given Specifications
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Af=100; //Voltage Gain
8 Vin=50*10(-3); //V , Input Signal without Feedback
   Gain
9 Vi=0.6; //V , Input Signal with Feedback Gain
10 //Calculation
11 Vo=Af*Vi;
12 A=Vo/Vin;
13 B=((A/Af)-1)/A;
14 //Displaying The Results in Command Window
15 printf("\n\t The Value of the Internal Gain A is , A
   = %f .",A);
16 printf("\n\t The Value of the Feedback Gain B is , B
   = %f percent .",B*100);

```

---

**Scilab code Exa 12.3** Calculation of change in overall Gain of Feedback Amplifier

```

1 //Example 12.3
2 //Program to Calculate the change in overall Gain of
   the Feedback //Amplifier with given Gain
   reduction
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 A=1000; //60dB, Voltage Gain
8 B=0.005; //Negative Feedback

```

```

9 dAbyA=-0.12; //dA/A = 12 %
10 // Calculation
11 dAfbyAf=1/(1+A*B)*dAbyA; //dAf/Af=1/(1+A*B)*dA/A
12 //Displaying The Results in Command Window
13 printf("\n\t The change in overall Gain of the
    Feedback Amplifier is , dAf/Af = %f which is
    equivalent to %f percent.",dAfbyAf,dAfbyAf*-100);

```

---

**Scilab code Exa 12.4** Calculation of Input Impedance of the Feedback Amplifier

```

1 //Example 12.4
2 //Program to Calculate the Input Impedance of the
    Feedback Amplifier //with given Specifications
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Zi=1*10^3; //Ohms
8 A=1000; //Voltage Gain
9 B=0.01; //Negative Feedback
10 //Calculation
11 Zid=(1+A*B)*Zi;
12 //Displaying The Results in Command Window
13 printf("\n\t The Value of the Input Impedance of the
    Feedback Amplifier is , Zid = %f kOhms.",Zid
    /10^3);

```

---

**Scilab code Exa 12.5** Calculation of Feedback Factor and Percent change in overall Gain

```

1 //Example 12.5

```



```

2 //Program to Calculate the value of Feedback Factor
   and Percentage //change in overall Gain of the
   Internal Amplifier
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 A=1000; //60dB, Voltage Gain
8 Zo=12000; //Ohms
9 Zod=600; //Ohms
10 dAbyA=0.1; //dA/A = 10 %
11 //Calculation
12 B=((Zo/Zod)-1)/A; //Zod=Zo/(1+A*B)
13 dAfbyAf=1/(1+A*B)*dAbyA; //dAf/Af=1/(1+A*B)*dA/A
14 //Displaying The Results in Command Window
15 printf("\n\t The Feedback Factor of the Feedback
   Amplifier is , B = %f percent .",B*100);
16 printf("\n\t The change in overall Gain of the
   Feedback Amplifier is , dAf/Af = %f percent.",
   dAfbyAf*100);

```

---

# Chapter 13

## OSCILLATORS

**Scilab code Exa 13.1** Calculate Frequency of Oscillation of Tuned Collector Oscillator

```
1 //Example 13.1
2 //Program to Calculate Frequency of Oscillation of
3 //Tuned Collector Oscillator
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 L=58.6*10(-6); // H
9 C=300*10(-12); // F
10 //Calculation
11 fo=1/(2*%pi*sqrt(L*C));
12 //Displaying The Results in Command Window
13 printf("\n\t The Frequency of Oscillation of Tuned
    Collector Oscillator is fo = %f kHz .",fo/103);
```

---

**Scilab code Exa 13.2** Calculate Frequency of Oscillation of Phase Shift Oscillator

```

1 //Example 13.2
2 //Program to Calculate Frequency of Oscillation of
3 //Vacuum Tube Phase Shift Oscillator
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 R=100*103; // Ohms
9 C=0.01*10(-6); //F
10 //Calculation
11 fo=1/(2*%pi*R*C*sqrt(6));
12 //Displaying The Results in Command Window
13 printf("\n\t The Frequency of Oscillation of Vacuum
    Tube Phase Shift Oscillator is fo = %f Hz .",fo);

```

---

**Scilab code Exa 13.3** Calculate Frequency of Oscillation of Wein Bridge Oscillator

```

1 //Example 13.3
2 //Program to Calculate Frequency of Oscillation of
3 //Wein Bridge Oscillator
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 R1=220*103; // Ohms
9 R2=220*103; // Ohms
10 C1=250*10(-12); //F
11 C2=250*10(-12); //F
12 //Calculation
13 fo=1/(2*%pi*sqrt(R1*C1*R2*C2));
14 //Displaying The Results in Command Window
15 printf("\n\t The Frequency of Oscillation of Wein
    Bridge Oscillator is fo = %f kHz .",fo/103);

```

---

# Chapter 14

## ELECTRONIC INSTRUMENTS

Scilab code Exa 14.1 Calculation of Series Resistance for conversion to Voltmeter

```
1 //Example 14.1
2 //Program to Determine the Series Resistance to
   Convert given
3 //d' Arsonval movement into a Voltmeter with the
   specified Range
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
8 Rm=100; //Ohms
9 Is=100*10(-6); //A
10 Vr=100; //V
11 //Calculation
12 Rtotal=Vr/Is;
13 Rs=Rtotal-Rm;
14 //Displaying The Results in Command Window
15 printf("\n\t The Series Resistance to Convert given
   dArsonval movement into a Voltmeter is , Rs = %f
```

```
kOhms ." ,Rs/10^3);
```

---

#### Scilab code Exa 14.2 Calculation of Shunt Resistance

```
1 //Example 14.2
2 //Program to Determine the Shunt Resistance required
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 Rm=100; //Ohms
8 CS=100*10^(-6); //A
9 Imax=10*10^(-3); //A
10 //Calculation
11 Ish=Imax-CS;
12 Rsh=Rm*CS/Ish;
13 //Displaying The Results in Command Window
14 printf("\n\t The Value of Shunt Resistance is , Rsh =
    %f Ohms ." ,Rsh);
```

---

#### Scilab code Exa 14.3 Designing of a Universal Shunt for making a Multi Range Milliammeter

```
1 //Example 14.3
2 //Program to Design the Universal Shunt for making
    Multi-Range //Milliammeter with Range 0-1 mA
    ,0-100 mA,0-500 mA,0-1 A
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 CS=100*10^(-6); //A
8 R=100; //Ohms
```

```

9  Rm=900; //Ohms
10 // (a) Calculation
11 I_max1=1*10(-3); //A
12 Rsh=CS*R/(I_max1-CS);
13 Rm1=Rm;
14 Ish1=I_max1-CS;
15 Rsh1=Rm1*CS/Ish1;
16 // (b) Calculation
17 I_max2=10*10(-3); //A
18 Ish2=I_max2-CS;
19 R1=(R*Ish2-Rm*CS)/(Ish2-CS);
20 // (c) Calculation
21 I_max3=100*10(-3); //A
22 Ish3=I_max3-CS;
23 R2=((R-R1)*Ish3-Rm*CS)/(Ish3-CS);
24 // (d) Calculation
25 I_max4=500*10(-3); //A
26 Ish4=I_max4-CS;
27 R3=((R-R1-R2)*Ish4-Rm*CS)/(Ish4-CS);
28 // (e) Calculation
29 I_max5=1; //A
30 Ish5=I_max5-CS;
31 R4=((R-R1-R2-R3)*Ish5-Rm*CS)/(Ish5-CS);
32 R5=R-R1-R2-R3-R4;
33 // Displaying The Results in Command Window
34 printf("\n\t Shunt Resistance      , Rsh = %f
    Ohms .", Rsh);
35 printf("\n\t For Range switch at 1 mA  , Rsh1 = %f
    Ohms .", Rsh1);
36 printf("\n\t For Range switch at 10 mA , R1 = %f
    Ohms .", R1);
37 printf("\n\t For Range switch at 100 mA, R2 = %f
    Ohms .", R2);
38 printf("\n\t For Range switch at 500 mA, R3 = %f
    Ohms .", R3);
39 printf("\n\t For Range switch at 1 A    , R4 = %f
    Ohms .", R4);
40 printf("\n\t\t\t\t R5 = %f Ohms .", R5);

```

---

**Scilab code Exa 14.4** Determination of Peak and RMS AC Voltage

```
1 //Example 14.4
2 //Program to Determine the AC Voltage
3 clear;
4 clc ;
5 close ;
6 //Given Circuit Data
7 DS=5; //V/cm, Deflection Sensitivity
8 l=10; //cm, Trace Length
9 //Calculation
10 Vp=DS*l;
11 Vm=Vp/2;
12 V=Vm/sqrt(2);
13 //Displaying The Results in Command Window
14 printf("\n\t The Peak AC Voltage , Vm = %f V .",Vm);
15 printf("\n\t The RMS AC Voltage , V = %f V .",V);
```

---

**Scilab code Exa 14.5** Determination of Magnitude and Frequency of Voltage Fed to Y Input

```
1 //Example 14.5
2 //Program to Determine the Magnitude and the
   Frequency of the
3 //wave Voltage fed to the Y-input
4 clear;
5 clc ;
6 close ;
7 //Given Circuit Data
```

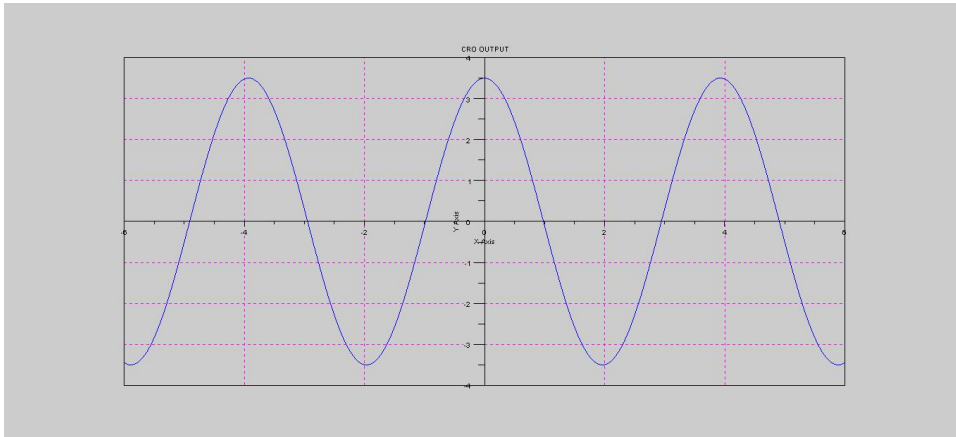


Figure 14.1: Determination of Magnitude and Frequency of Voltage Fed to Y Input

```

8 Am=3.5; //V, Amplitude
9 tb=0.1*10^(-3); //seconds
10 TP=4; //Time Period
11 // Calculation
12 Vm=2*Am;
13 V=Vm/sqrt(2);
14 T=TP*tb;
15 f=1/T;
16 //Displaying The Results in Command Window
17 printf("\n\t The Magnitude of Wave Voltage , V = %f V
      .",V);
18 printf("\n\t The Frequency of Wave Voltage , f = %f
      kHz .",f/10^3);
19 //Plot of the given Wave
20 figure
21 x=-6:0.01:6;
22 y=Am*cos(1.6*x); //Given Waveform
23 plot (x,y);
24 a= gca ();
25 a.x_location="origin";
26 a.y_location="origin";
27 xlabel ('X Axis ');

```



```
28 ylabel ('Y Axis');  
29 title ('CRO OUTPUT');  
30 xgrid (6);
```

---