

Scilab Textbook Companion for  
Electrical And Electronic Engineering  
by U. A. Bakshi And V. U. Bakshi<sup>1</sup>

Created by  
Prakhar Bangar  
B.Tech  
Electrical Engineering  
Manipal Unviversity  
College Teacher  
No Teacher  
Cross-Checked by  
Ganesh R

October 10, 2013

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electrical And Electronic Engineering

**Author:** U. A. Bakshi And V. U. Bakshi

**Publisher:** Technical Publications, Pune

**Edition:** 1

**Year:** 2009

**ISBN:** 9788184316971

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Electrical Circuits	10
2 DC Machines	35
3 Transformers	61
4 Alternators	86
5 Alternators	110
6 Instruments	126
7 Semiconductor Physics and Diode	134
8 Transistors	148
9 Cathode Ray Oscilloscope	153

# List of Scilab Codes

Exa 1.1	obtain the waveform . . . . .	10
Exa 1.2	find equivalent resistance . . . . .	11
Exa 1.3	voltage across three resistances . . . . .	12
Exa 1.4	magnitudes of total current . . . . .	12
Exa 1.5	find the values of currents . . . . .	13
Exa 1.6	find $i_1$ and $i_2$ . . . . .	14
Exa 1.7	transform voltage source to current source . . . . .	15
Exa 1.8	convert current source to voltage source . . . . .	15
Exa 1.9	convert delta to star . . . . .	16
Exa 1.10	find equivalent resistance . . . . .	16
Exa 1.11	find equivalent resistance . . . . .	16
Exa 1.12	find current . . . . .	17
Exa 1.13	find power . . . . .	18
Exa 1.14	find current . . . . .	19
Exa 1.15	node voltage . . . . .	20
Exa 1.16	instantaneous current . . . . .	21
Exa 1.17	find voltage . . . . .	22
Exa 1.18	equivalent resistance . . . . .	23
Exa 1.19	find current . . . . .	23
Exa 1.20	calculate resistance . . . . .	24
Exa 1.21	find current . . . . .	25
Exa 1.22	find voltage . . . . .	26
Exa 1.23	find current . . . . .	27
Exa 1.24	find voltage drop . . . . .	28
Exa 1.25	find inductive resistance . . . . .	28
Exa 1.26	find resistance . . . . .	29
Exa 1.27	find resistance . . . . .	29
Exa 1.28	find resistance . . . . .	30

Exa 1.29	find resistance . . . . .	30
Exa 1.30	find current . . . . .	31
Exa 1.31	obtain current . . . . .	32
Exa 1.32	calculate current . . . . .	33
Exa 2.1	generated emf . . . . .	35
Exa 2.2	generated emf and speed . . . . .	35
Exa 2.3	induced emf of generator . . . . .	36
Exa 2.4	armature resistance of generator . . . . .	37
Exa 2.5	terminal voltage at load . . . . .	37
Exa 2.6	generated voltage . . . . .	38
Exa 2.7	induced emf in motor . . . . .	39
Exa 2.8	back emf and speed of motor . . . . .	39
Exa 2.9	gross torque . . . . .	40
Exa 2.10	induced emf and armature current and stray losses and lost torque . . . . .	40
Exa 2.11	speed of motor . . . . .	41
Exa 2.12	armature current and back emf . . . . .	42
Exa 2.13	speed on full load . . . . .	42
Exa 2.14	speed of motor on new load . . . . .	43
Exa 2.15	terminal voltage . . . . .	44
Exa 2.16	full load output and efficiency of motor . . . . .	45
Exa 2.17	armature current and back emf and speed of motor . . . . .	46
Exa 2.18	extra resistance to be added . . . . .	47
Exa 2.19	efficiency of motor . . . . .	48
Exa 2.20	lap and wave wound . . . . .	49
Exa 2.21	emf generated . . . . .	50
Exa 2.22	speed of generator . . . . .	50
Exa 2.23	induced voltage . . . . .	50
Exa 2.24	commutator bars . . . . .	51
Exa 2.25	induced emf . . . . .	52
Exa 2.26	total and useful torque and flux and rotational losses and efficiency . . . . .	52
Exa 2.27	speed . . . . .	53
Exa 2.28	torque . . . . .	54
Exa 2.29	induced emf and electrical power output . . . . .	54
Exa 2.30	generated voltage and armature current . . . . .	55
Exa 2.31	induced emf and speed . . . . .	55
Exa 2.32	back emf and gross mechanical power . . . . .	56

Exa 2.33	generated emf and copper and iron losses and efficiency	56
Exa 2.34	total armature power	58
Exa 2.35	leakage coefficient	58
Exa 2.36	no load terminal voltage and area of pole	59
Exa 3.1	primary and secondary turns and area of core	61
Exa 3.2	peak value of flux in core and secondary voltage	61
Exa 3.3	iron loss and maximum value of flux in core	62
Exa 3.4	primary current	63
Exa 3.5	equivalent resistance	64
Exa 3.6	total resistance and equivalent reactance and impedance	65
Exa 3.7	regulation and secondary terminal voltage	66
Exa 3.8	total copper loss and efficiency	67
Exa 3.9	maximum efficiency	68
Exa 3.10	efficiency and unity power factor	68
Exa 3.11	copper loss and full and half load efficiency and regulation	69
Exa 3.12	voltage and power factor	71
Exa 3.13	all day efficiency	72
Exa 3.14	copper loss and efficiency	74
Exa 3.15	iron and copper loss	75
Exa 3.16	regulation	76
Exa 3.17	efficiencies	77
Exa 3.18	load impedance and maximum flux	78
Exa 3.19	number of primary and secondary turns	78
Exa 3.20	maximum efficiency	79
Exa 3.21	area of core	79
Exa 3.22	efficiency	80
Exa 3.23	turns ratio and magnetizing and working component and iron loss	81
Exa 3.24	efficiency and load	82
Exa 3.25	flux density and transformation ratio and voltage induced and	83
Exa 3.26	voltage regulation and efficiency	83
Exa 3.27	all day efficiency	84
Exa 4.1	calculate distribution factor	86
Exa 4.2	calculate coil factor	86
Exa 4.3	find induced emf	87
Exa 4.4	find poles and flux	88
Exa 4.5	calculate emf	89

Exa 4.6	calculate lagging . . . . .	90
Exa 4.7	calculate full load . . . . .	91
Exa 4.8	find current . . . . .	93
Exa 4.9	find armature conductors . . . . .	95
Exa 4.10	calculate flux . . . . .	96
Exa 4.11	find rms vlaue . . . . .	97
Exa 4.12	find induced emf . . . . .	99
Exa 4.13	find chording factor . . . . .	100
Exa 4.14	find emf . . . . .	100
Exa 4.15	find reactance . . . . .	101
Exa 4.16	find impedance . . . . .	102
Exa 4.17	find voltage regulation . . . . .	103
Exa 4.18	find regulation . . . . .	104
Exa 4.19	find regulation . . . . .	105
Exa 4.20	find voltage . . . . .	107
Exa 4.21	calculate regulation . . . . .	108
Exa 5.1	calculate full load slip . . . . .	110
Exa 5.2	calculate full load speed . . . . .	110
Exa 5.3	frequency of induced emf . . . . .	111
Exa 5.4	find full load slip . . . . .	111
Exa 5.5	calculate frequency . . . . .	112
Exa 5.6	find rotor current . . . . .	113
Exa 5.7	calculate torque developed . . . . .	114
Exa 5.8	find torque . . . . .	115
Exa 5.9	find ratio of torque . . . . .	117
Exa 5.10	find slip . . . . .	117
Exa 5.11	find shaft torque . . . . .	119
Exa 5.15	find starting torque . . . . .	121
Exa 5.18	find speed of motor . . . . .	122
Exa 5.19	find rotor input . . . . .	122
Exa 5.22	find speeds . . . . .	123
Exa 5.23	find resistance . . . . .	124
Exa 6.1	deflection . . . . .	126
Exa 6.2	theta . . . . .	126
Exa 6.3	shunt resistance . . . . .	127
Exa 6.4	current through shunt and resistance of motor . . . . .	127
Exa 6.5	multiplier resistance . . . . .	128
Exa 6.6	shunt required and multiplier required . . . . .	128



Exa 6.7	voltage induced . . . . .	129
Exa 6.8	resistance . . . . .	130
Exa 6.9	ammeter and voltmeter . . . . .	130
Exa 6.10	number of turns . . . . .	131
Exa 6.11	shunt resistance and full scale deflection . . . . .	131
Exa 7.1	forbidden gap . . . . .	134
Exa 7.2	resistivity . . . . .	134
Exa 7.3	current in the bar . . . . .	135
Exa 7.4	resistivity of intrinsic germanium . . . . .	136
Exa 7.7	comparing two values . . . . .	136
Exa 7.9	new diode current . . . . .	137
Exa 7.10	forward bias current . . . . .	138
Exa 7.11	reverse saturation current and eta for diode . . . . .	138
Exa 7.12	reverse saturation current and forward current . . . . .	139
Exa 7.14	dc output voltage . . . . .	140
Exa 7.15	dc voltage and load current . . . . .	141
Exa 7.17	power to load and regulation and efficiency and TUF of secondary . . . . .	141
Exa 7.20	ac input power . . . . .	142
Exa 7.21	percentage eta . . . . .	143
Exa 7.22	dc load current and load voltage and ripple voltage and PIV rating . . . . .	144
Exa 7.23	load voltage and ripple voltage . . . . .	145
Exa 7.25	dc output voltage . . . . .	145
Exa 7.29	forward current . . . . .	146
Exa 7.30	temperature . . . . .	147
Exa 7.31	conductivity of silicon . . . . .	147
Exa 8.1	base current . . . . .	148
Exa 8.2	alpha dc and beta dc . . . . .	148
Exa 8.3	collector current . . . . .	149
Exa 8.4	alpha dc and beta dc . . . . .	150
Exa 8.7	alpha and beta and $V_0$ and output power . . . . .	150
Exa 8.8	firing angle . . . . .	151
Exa 8.9	time for SCR remains off . . . . .	151
Exa 9.1	time for electron . . . . .	153
Exa 9.2	final velocity pf electron . . . . .	154
Exa 9.4	velocity and deflection and deflection sensitivity . . . . .	154
Exa 9.7	speed of electron and force on electron . . . . .	155

Exa 9.8	amplitude and rms value . . . . .	155
Exa 9.10	phase difference . . . . .	156
Exa 9.11	unknown frequency of vertical signal . . . . .	157
Exa 9.12	deflection sensitivity and angle of deflection and velocity of beam . . . . .	157
Exa 9.15	time for electron . . . . .	158
Exa 9.16	deflection sensitivity . . . . .	158
Exa 9.17	time taken by electron . . . . .	159
Exa 9.18	input voltage . . . . .	160
Exa 9.19	beam velocity and deflection sensitivity and deflection factor . . . . .	160

# Chapter 1

## Electrical Circuits

Scilab code Exa 1.1 obtain the waveform

```
1 //example1.1
2 clc
3 disp("From the give waveform,")
4 s=100/2
5 disp(s,"For 0<t<2, i(t) is a straight line slope=")
6 disp("Therefore i(t)=50t and di(t)/dt=50 .. 0<t<2
7 ")
8 disp("For 2<t<4, i(t)=100 and di(t)/dt=0")
9 s=(-100)/2
10 disp(s,"For 4<t<6, i(t) is a straight line slope = "
11 ")
12 disp("Therefore , i(t)= -50t and di(t)/dt= -50
13 ..4<t<6")
14 disp("Now v_l(t)=L*di(t)/dt")
15 v=(50)*10^-3
16 format(5)
17 disp(v,"V_l(t) [in volts from 0<t<2]=")
18 v=0*10^-3
19 disp(v,"V_l(t) [in volts from 2<t<4]=")
20 v=(-50)*10^-3
21 disp(v,"V_l(t) [in volts from 4<t<6]=")
```

19 `disp("The waveform is shown in the fig. 1.12(a)")`

---

### Scilab code Exa 1.2 find equivalent resistance

```
1 //example1.2
2 clc
3 disp("Identify combinations of series and parallel
   resistances.")
4 disp("The resistances 5ohm and 6ohm are in series ,
   as going to carry same current.")
5 r=5+6
6 disp(r,"So equivalent resistance is(in ohm)=")
7 disp("While the resistances 3ohm,4ohm,4ohm are in
   parallel , as voltage across them same but current
   divides.")
8 r=10/12
9 format(4)
10 disp(r,"(1/R)=(1/3)+(1/4)+(1/5)=")
11 r=12/10
12 disp(r,"Therefore , R(in ohm)=")
13 disp("Replacing these combinations redraw the fig.
   as shown in the fig. 1.28(a)")
14 disp("Now again 1.2ohm and 2ohm are in series so
   equivalent resistance is 2+1.2=3.2 ohm while 11
   ohm and 7ohm are in parallel.")
15 disp("Using formula (R1*R2)/(R1+R2)")
16 r=77/18
17 format(6)
18 disp(r,"equivalent resistance3 is (11*7)/(11+7)[in
   ohm]=")
19 disp("Replacing the respective combination redraw
   the circuit as shown in the fig 1.28(b).")
20 disp("Now 3.2 and 4.277 are in parallel")
21 r=(3.2*4.277)/(3.2+4.277)
22 format(7)
```

```

23 disp(r," Therefore , replacing them by (3.2*4.277)
      /(3.2+4.277) [in ohm]=")
24 r=1+1.8304
25 disp(r," R_ab(in ohm)=")

```

---

### Scilab code Exa 1.3 voltage across three resistances

```

1 //example1.3
2 clc
3 disp(" I=v/(R1+R2+R3) ..... series circuit")
4 i=60/60
5 disp(i," I(in amp)=")
6 v=1*10
7 disp(v," Therefore , V_r1(in V)=(I*R1)=(V*R1)/(R1+R2+
      R3)=")
8 v=1*20
9 disp(v," Therefore , V_r2(in V)=(I*R2)=(V*R2)/(R1+R2+
      R3)=")
10 v=1*30
11 disp(v," and , V_r3(in V)=(I*R3)=(V*R3)/(R1+R2+R3)=")
12 disp("Key point: It can be seen that voltage across
      any resistance of series circuit is ratio of that
      resistance to the total resistance , multiplied
      by the source voltage.")

```

---

### Scilab code Exa 1.4 magnitudes of total current

```

1 //example1.4
2 clc
3 disp("The equivalent resistance of two is ,")
4 r=(10*20)/30
5 format(5)
6 disp(r," R_eq(in ohm)=(R1*R2)/(R1+R2)=")

```

```

7 i=50/6.67
8 format(4)
9 disp(i," I_t (in amp)=V/R_eq=")
10 disp("As per the current distribution in parallel
      circuit,")
11 i=(7.5*20)/30
12 disp(" I_1 (in amp)=(I_t*R2)/(R1+R2)=")
13 i=75/30
14 disp(i," and, I_2 (in amp)=(I_t*R1)/(R1+R2)=")
15 disp("It can be verified that I_t=(I1)+(I2).")

```

---

**Scilab code Exa 1.5** find the values of currents

```

1 //example1.5
2 clc
3 disp("Application of Kirchhoffs law:")
4 disp("Step 1 and 2: Draw the circuit with all values
      which are same as the given network. Mark all
      the branch starting from +ve of any of the source
      , say +ve of 50V source.")
5 disp("Step 3: Mark all the polarities for different
      voltages across the resistances. This is combined
      with step2 shown in the network below in fig
      1.41(a).")
6 disp("Step 4: Apply KVL to different loops.")
7 disp("Loop 1: A-B-E-F-A , -15(I_1)-20(I_2)+50=0")
8 disp("Loop 2: B-C-D-E-B , -30((I_1)-(I_2))-100+20(
      I_2)=0")
9 disp("Rewriting all the equations ,taking constants
      in one side.")
10 disp("15(I_1)+20(I_2)=50 ..(1)")
11 disp("-30(I_1)+50(I_2)=100 ..(2)")
12 disp("Apply crammers rule,")
13 d=(15*50)-(-30*20)
14 format(5)

```

```

15 disp(d,"D=[15 20;-30 50]=")
16 disp(" Calculating D_v")
17 d=(50*50)-2000
18 disp(d,"D1=[50 20;100 50]=")
19 i=500/1350
20 disp(i," I_1 (in amp)=(D_1)/D=")
21 disp(" Calculating D2 ,")
22 d=1500+(30*50)
23 disp(d,"D2=[15 50;-30 100]=")
24 i=3000/1350
25 disp(i," I_2 (in amp)=D2/D=")
26 disp(" For I_1 and I_2 , as answer is positive ,
        assumed direction is correct")
27 disp(" Therefore , for I_1 answer is 0.37 amp. For I_2
        answer is 2.22amp")
28 i=0.37-2.22
29 format(5)
30 disp(i," (I_1)-(I_2) [in amp]=")
31 disp(" Negative sign indicates assumed direction is
        wrong.")
32 disp(" i.e (I_1)-(I_2)=1.85A flowing in opposite
        direction to that of the assumed direction.")

```

---

**Scilab code Exa 1.6** find  $i_1$  and  $i_2$

```

1 //example1.6
2 clc
3 disp("The current distribution using KCL is as shown
        ,")
4 disp("Key Point : KVL should not be applied to the
        loop consisting current source.")
5 disp("From branch DE,")
6 disp("(i1)=5+3(i2) ... (1)")
7 disp("Applying KVL to the loop BCDEFGB without
        current source ,")

```

```

8 disp("-1*(5+3(i2))+5(i2)=0      ... (2)")
9 disp("2(i2)=5")
10 i=5/2
11 disp(i,"i2 (in amp)=")
12 disp("from eq.(1)")
13 i=5+(3*2.5)
14 disp(i,"i1 (in amp)=")

```

---

**Scilab code Exa 1.7** transform voltage source to current source

```

1 //example1.7
2 clc
3 disp("Refer to the fig 1.45(a).")
4 i=20/5
5 disp(i,"Then current of current source is , I(in A)=V
   /R_sc=")
6 disp("with internal parallel resistance same as R_sc
   ")
7 disp("Therefore , Equivalent current is as shown in
   the fig. 1.45(b).")

```

---

**Scilab code Exa 1.8** convert current source to voltage source

```

1 //example
2 clc
3 disp("The given values are , I=50A and R_sh= 10ohm")
4 disp("For the equivalent voltage source ,")
5 v=10*50
6 disp(v,"V(in V)=(I*R_sh)=")
7 disp("R_se=R_sh=10ohm in series.")
8 disp("The equivalent voltage source is shown in the
   fig 1.46(a)")

```



```
9 disp("Note the polarities of voltage source , which  
   are such that +ve at top of arrow and -ve at  
   botttom.")
```

---

**Scilab code Exa 1.9** convert delta to star

```
1 //example1.9  
2 clc  
3 disp("Its equivalent star is as shown in the fig  
   1.57. where ,")  
4 r=50/30  
5 format(5)  
6 disp(r,"R1(in ohm)=(10*50)/(5+10+15)=")  
7 r=150/30  
8 disp(r,"R2(in ohm)=(15*10)/(5+10+15)=")  
9 r=75/(30)  
10 disp(r,"R3(in ohm)=(15*5)/(5+10+15)")
```

---

**Scilab code Exa 1.10** find equivalent resistance

```
1 //example1.10  
2 clc  
3 disp("Redrawing the circuit ,")  
4 r=(21*14)/(21+14)  
5 format(4)  
6 disp(r,"R_ab(in ohm)=(21*14)/(21+14)=")
```

---

**Scilab code Exa 1.11** find equivalent resistance

```
1 //example1.11
```

```

2  clc
3  disp("Redrawing the circuit ,")
4  disp("R1 and R2 are in series from fig. 1.59(b)")
5  r=150/25
6  disp(r,"R1(in ohm)=(15*10)/(15+10)=")
7  r=24/10
8  disp(r,"R2(in ohm)=(6*4)/(6+4)=")
9  disp("then , R_ab=R1+R2")
10 r=6+2.4
11 disp(r,"Therefore , R_ab(in ohm)=6+2.4=")

```

---

#### Scilab code Exa 1.12 find current

```

1  //example1.12
2  clc
3  disp("The various loop are shown in the fig 1.64(a)"
      )
4  disp("Apply KVL to the various loops ,")
5  disp("Loop 1,  -15(I_1) -20(I_1) +20(I_2) +100=0")
6  disp("Therefore ,  +35(I_1) -20(I_2) =100    ... (1)")
7  disp("Loop 2,  -5(I_2) -30(I_2) +30(I_3) -20(I_2) +20(I_1)=0")
8  disp("Therefore ,  20(I_1) -55(I_2) +30(I_3) =0    ... (2)"
      )
9  disp("Loop 3,  -5(I_3) -100 -30(I_3) +30(I_2) =0")
10 disp("Therefore ,  30(I_2) -35(I_3) =0    ... (3)")
11 d=35*((55*35) - (30*30)) +20*(-35*20)
12 format(6)
13 disp(d,"D1=[35  -20  0;20  -55  30;0  30  -35]=")
14 d=35*(-(100*30)) -100*(-35*20)
15 disp(d,"D2=[35  100  0;20  0  30;0  100  -35]=")
16 d=35*(-55*100) -(-20*(20*100)) +100*(30*20)
17 disp(d,"D3=[35  -20  100;20  -55  0;0  30  100]=")
18 i=(-35000)/21875
19 format(4)

```

```

20 disp(i," I_2 (in amp)=D2/D=")
21 i=(-92500)/21875
22 format(7)
23 disp(i," I_3 (in amp)=D3/D=")
24 i=(-1.6)+4.2285
25 disp(i," I_30 (in amp)=(I_2)-(I_3)=")
26 disp("As (I_2-I_3) is positive , current floes in the
        assumed direction of I_2")

```

---

### Scilab code Exa 1.13 find power

```

1 //example1.13
2 clc
3 disp("The various loop current are shown in the fig
      1.65(a). The problem consists of current sources
      hence follow supermesh steps.")
4 disp("Loops cannot be defined through current
      sources.So analyse the branches consisting of
      current sources first")
5 disp("From branch A-B we can write,")
6 disp(" I_3=2A ... (1)")
7 disp("From branch DG we can write,")
8 disp(" I_2-I_1=8A ... (2)")
9 disp("Now apply KVL to the loop without current
      source i.e.")
10 disp("loop C-D-E-H-G-F-C,")
11 disp("-(I_3)-(I_1)-3(I_3)-3(I_2)-4(I_2)+24=0")
12 disp("Therefore , 4(I_3)+7(I_2)+(I_1)=24 ... (3)")
13 disp("Using equation (1) and equation (2) in (3) we
      get,")
14 disp("8+7(I_2)+((I_2)-8)=24")
15 disp("Therefore 8(I_2)=24")
16 i=24/8
17 disp(i," I_2 (in amp)=")
18 disp("This is current through 4ohm resistor.So power

```

```

    deliverd to the 4ohm resistor is ,")
19 p=9*4
20 disp(p,"P(in W)=((I_2)^2)*4=")

```

---

### Scilab code Exa 1.14 find current

```

1 //example1.14
2 clc
3 disp("The various node voltages and currents are
    shown in the fig 1.72(a).")
4 disp("At node 1, -(I_1)-(I_2)-(I_3)=0")
5 disp("Therefore, -[(V_1-15)/1]-[V_1/1]-[(V_1-V_2)
    /0.5]=0")
6 disp("Therefore, -(V_1)+15-(V_1)-2(V_1)+2(V_2)=0")
7 disp("Therefore, 4(V_1)-2(V_2)=15 ..(1)")
8 disp("At node 2, (I_3)-(I_4)-(I_5)=0")
9 disp("Therefore, [(V_1-V_2)/0.5]-[(V_2)/2]-[((V_2)
    +20)/1]=0")
10 disp("Therefore, 2(V_1)-2(V_2)-0.5(V_2)-(V_2)+20=0"
    )
11 disp("Therefore, 2(V_1)-3.5(V_2)= -20 ...(2)")
12 disp("Multiplying equation (2) by 2 and subtracting
    from equation (1) we get,")
13 disp("5(V_2)=55")
14 v=55/5
15 disp(v,"V_2(in V)= ")
16 v=(-20+(3.5*11))/2
17 format(5)
18 disp(v,"and, V_1(in V)= ")
19 disp("Hence the various currents are,")
20 i=9.25-15
21 disp(i,"(I_1)(in A)=[(V_1)-5]/1=")
22 disp("i.e I1=5.75A upward")
23 i=9.25/1
24 disp(i,"(I_2)(in A)=(V_1)/1=")

```

```

25 i=(9.25-11)/0.5
26 disp(i,"(I_3)(in A)=[(V_1)-(V_2)]/0.5=")
27 disp("i.e I3=3.5A to left")
28 i=11/2
29 disp(i,"(I_4)(in A)=(V_2)/2=")
30 i=11-20
31 disp(i,"(I_5)(in A)=[(V_2)-20]/1=")
32 disp("i.e I5=9A upward")

```

---

### Scilab code Exa 1.15 node voltage

```

1 //example1.15
2 clc
3 disp("The various node voltage are shown in the fig
      1.73(a).")
4 disp("The various branch currents are shown.
      Applying KCL at various nodes.")
5 disp("Node 1: 9-I1-I2-I3=0 ..(1)")
6 disp("Node 1: I3-I4+4=0 ..(2)")
7 disp("Node 1: I2-4-I5=0 ..(3)")
8 disp("Key Point: Nodes V1 and V3 from supernode
      region and nodes V1 and V2 from super node region
      .")
9 disp("Super node: V1-10=V3 i.e. V1-V3=10 ..(4)")
10 disp("Super node: V1+6=V2 i.e. V1-V2=-6 ..(5)")
11 disp("From equation (2), I3=I4-4 and from equation
      (3), I2=I5+4")
12 disp("Using in equation (1), 9-I1-I5-4-I4+4=0")
13 disp("i.e I1+I4+I5=9 ..(6)")
14 disp("I1=V1/4, I4=V2/10, I5=V3/5")
15 disp("Therefore (V1/4)+(V2/10)+(V3/5)=9")
16 disp("i.e 0.25(V1)+0.1(V2)+0.2(V3)=9 ... (7)")
17 disp("Solving equations (4), (5) and (7)
      simultaneously, we get")
18 disp("0.25(V1)+0.1(V1+6)+0.2(V1-10)=9")

```

```

19 v=10.4/0.55
20 format(7)
21 disp(v,"Therefore , V1(in V)=")
22 disp("putting V1 in eq.(4) and (5), we get ")
23 v=18.909+6
24 disp(v,"V2(in V)=")
25 v=18.909-10
26 disp(v,"V3(in V)=")

```

---

#### Scilab code Exa 1.16 instantaneous current

```

1 //example1.16
2 clc
3 disp("Case 1: R=10ohm")
4 disp("V=(V_m) sin (wt)")
5 v=150*sqrt(2)
6 format(7)
7 disp("(V_m) [in V]=sqrt(2)*V_rms=")
8 i=212.13/10
9 disp(i,"(I_m) [in A]=(V_m)/R=")
10 disp("In pure resistive circuit , currents is in
      phase with the voltage.")
11 disp("Therefore , psi=phase difference= 0 degree")
12 disp("Therefore , i=(I_m) sin (wt)=(I_m) sin (2*pi*f*t)"
      )
13 disp("Therefore , i(in A) = 21.213 sin(100*pi*t)")
14 disp("The phasor diagram is shown in the fig. 1.85(a)"
      )
15 disp("Case 2: L=0.2 ohm")
16 x=2*%pi*50*0.2
17 format(6)
18 disp(x,"Inductive reactance , (X_L) [in ohm]=wL=(2*pi*
      f*L)=")
19 i=212/13/62.83
20 format(5)

```

```

21 disp(" Therefore , (I_m)[in A]=(V_m)/(X_L)=")
22 disp(" In pure inductive circuit , current lags
    voltage by 90 degree.")
23 disp(" Therefore , psi=phase difference = -90 degree
    =(pi/2)rad")
24 disp(" Therefore , i=(I_m)sin(wt-psi) i.e. i(in A)
    =3.37sin((100*pi*t)-(pi/2))")
25 disp("The phasor dig in shown in the fig 1.85(b).")
26 disp(" Case 3: C=50 micro-F")
27 c=1/(2*pi*50*50*10^-6)
28 format(6)
29 disp(c," Capacitive reactance , X_c(in ohm)=1/wC
    =1/(2*pi*f*C)=")
30 i=212.13/63.66
31 format(5)
32 disp(i," I_m(in A)=(V_m)/(X_c)=")
33 disp(" In pure capacitive circuit , current leads
    voltage by 90 degree.")
34 disp(" Therefore psi=phase difference =90 degree= (
    pi/2)radian")
35 disp(" Therefore , i=(I_m)sin(wt+psi)")
36 disp(" Therefore , i(in A)=3.33sin((100*pi*t)+(pi/2))
    ")
37 disp("The phasor dig is as shown in the fig 1.85(c).
    ")
38 disp(" All the phasor dig represent r.m.s values of
    voltage and current")

```

---

#### Scilab code Exa 1.17 find voltage

```

1 //example1.17
2 clc
3 r=10/10
4 disp(r,"R1(in ohm)=(2*5)/(2+5+3)=")
5 r=6/10

```

```

6 disp(r,"R2(in ohm)=(3*2)/(2+5+3)=")
7 r=15/10
8 disp(r,"R3(in ohm)=(5*3)/(2+5+3)=")
9 r=50/25
10 disp(r,"R1(in ohm)=(10*5)/(10+5+10)=")
11 r=100/25
12 disp(r,"R2(in ohm)=(10*10)/(10+5+10)=")
13 r=50/25
14 disp(r,"R3(in ohm)=(5*10)/(10+5+10)=")
15 disp("The circuit reduces as shown in the fig 1.86(c
    )")
16 r=0.6+4.2439+2
17 format(7)
18 disp(r,"R_ab(in ohm)=0.6+4.2439+2=")
19 disp("as , I=V/R_ab")
20 v=5*6.8439
21 format(8)
22 disp(v,"Therefore , V(in V)=I*R_ab=")

```

---

#### Scilab code Exa 1.18 equivalent resistance

```

1 //example1.18
2 clc
3 disp("Rearrange the circuit as shown below.")
4 disp("The 3.333ohm and 3.6ohm resistors are in
    series in fig 1.87(c).")
5 r=3.333+3.6
6 format(8)
7 disp(r,"Therefore , the equivalent resistance R_yz(in
    ohm)=")

```

---

#### Scilab code Exa 1.19 find current



```

1 //example1.19
2 clc
3 disp("Using the loop analysis , (fig 1.88(a) see on
      next page)")
4 disp("Applying KVL to the three loops ,")
5 disp("-(I1)-(I1)-2(I1)+2(I3)+5-2(I1)=0 i.e -6(I1)
      +2(I3)= -5 ... (1)")
6 disp("-2(I3)+2(I1)-2(I3)-5-2(I3)-(I3)+I2=0 i.e 2(
      I1)+I2-7(I3)=5 ... (2)")
7 disp("-2(I2)-(I2)+(I3)-2(I2)+5=0 i.e -5(I2)+I3=
      -5 ... (3)")
8 disp("Solving equation (1),(2)and (3)")
9 disp("so, putting equations(1) and (3) in eq (2),we
      get")
10 disp("10(I3)+25+3(I3)+15-105(I3)=75")
11 disp("Therefore , -92(I3)=35")
12 i=(-35)/92
13 format(7)
14 disp(i,"Therefore , I3(in A)=")
15 disp("Now, putting value of I3 in equations (1) and
      (2) :")
16 i=((-35/92)+5)/6
17 disp(i,"Therefore , I1(in A)=")
18 i=((-35/92)+5)/5
19 disp(i,"and, I2(in A)=")
20 disp("These are the currents in all the sources. I3
      is negative hence its direction is opposite to
      that assumed earlier.")

```

---

**Scilab code Exa 1.20** calculate resistance

```

1 //example1.20
2 clc
3 disp("The various branch currents are shown in the
      fig. 1.89. The current through branch OC is zero.

```

```

    Applying KVL to the various loops ,")
4  disp("-4(i2)-(R*i2)-2(i1)+10=0")
5  disp("i.e    2(i1)+4(i2)+(R*i2)=10    .. Loop AOBA")
6  disp("-(i1-i2)-1.5(i1-i2)-2(i1)+10=0")
7  disp("i.e    +4.5(i1)-2.5(i2)=10    .. Loop ACBA")
8  disp("-(i1-i2)-1.5(i1-i2)+(R*i2)+4(i2)=0")
9  disp("i.e    -2.5(i1)+6.5(i2)+(R*i2)=0    .. Loop
    ACBOA")
10 disp("As current through branch OC is zero , points O
    and C are equipotential. So drop across AO is
    same as drop across AC.")
11 disp("Therefore ,    4(i2)=(i1-i2)    i.e    (i1)=5(i2
    )")
12 disp("Using in loop A-C-B-A, 4.5*5*(i2)-2.5(i2)=10")
13 i=10/20
14 disp(i,"Therefore ,    i2 (in A)=")
15 i=5*0.5
16 disp(i,"and , i1 (in A)=")
17 disp("Using in loop A-O-B-A, (2*2.5)+(4*0.5)+0.5(R)
    =10")
18 r=3/0.5
19 disp(r,"Therefore ,    R(in ohm)=")
20 disp("And current through R is i2=0.5 A")

```

---

### Scilab code Exa 1.21 find current

```

1  //example1.21
2  clc
3  disp("Use nodal analysis ,")
4  disp("Applying KCL at the two nodes ,")
5  disp("21-I1-I2=0    (1)")
6  disp("I2-I3-I4=0    (2)")
7  disp("Analysing various branches ,")
8  disp("I1=(V1-0)/2, I2=(V1-V2)/3, I3=(V2-0)/3, I4
    =(V2-0)/6")

```

```

9 disp("Using in the equations (1) and (2),")
10 disp("21-(V1/2)-(V1-V2)/3 = 0")
11 disp("i.e 0.8333(V1) -0.333(V2) = 21 ... (3)")
12 disp("[ (V1-V2)/3] - (V2/3) - (V2/6)=0")
13 disp("i.e 0.3333(V1) -0.8333(V2) = 21 ... (4)")
14 disp("Solving equations (3) and (4),")
15 disp("0.8333(V1) -0.333(0.3333/0.8333)V1=21")
16 v=(-21*0.8333)/((0.333*0.3333)-(0.8333)^2)
17 format(3)
18 disp(v,"V1(in V)=")
19 v=(0.3333*30)/0.8333
20 disp(v,"V2(in V)=")
21 i=-12/6
22 disp(i,"Therefore , I(in 6ohm)=I4(in A)=")
23 disp("The current flows in downward direction in 6
ohm resistor.")
24 disp("Voltage across current soource is the voltage
across 2ohm resistance , which is node voltage V1
=30 V.")
25 p=30*21
26 format(4)
27 disp(p,"Therefore , power supplied by source P(in W)=
V1*21=30*21=")

```

---

**Scilab code Exa 1.22** find voltage

```

1 //example1.22
2 clc
3 disp("The arrangment is shown in the fig 1.92")
4 disp("P2=(I ^2)*R2")
5 disp("Therefore , 16= (2^2)*R2")
6 r=16/4
7 disp(r,"R2(in ohm)=")
8 v=4*2
9 disp(v,"V2(in ohm)=I*R2=")

```

```

10 v=2*6
11 disp("V3(in V)=I*R3=")
12 v=4+8+12
13 disp(v,"V(in V)=V1+V2+V3=")

```

---

### Scilab code Exa 1.23 find current

```

1 //example1.23
2 clc
3 disp("The branch currents are shown in the fig 1.93(
   a)")
4 disp("Applying KVL to the two loops,")
5 disp("-2(I1)-5(I2)+12=0")
6 disp("i.e 2(I1)+5(I2)=12 ..(1)")
7 disp("-4(I1-I2)-6(I1-I2)+5(I2)=0")
8 disp("i.e -10(I1)+15(I2)=0")
9 disp("Solving equation (1) and (2),")
10 disp("2(I1)+5(10/15)(I1)=12")
11 i=9/4
12 format(5)
13 disp(i,"I1(in A)=")
14 disp("put this value of I1 in eq (2),we get")
15 i=(10/15)*2.25
16 disp(i,"I2(in A)=(10/15)*2.25=")
17 disp("  Branch          Current          voltage drop
   ")
18 disp("  A-B            I1=2.25A          2(I1)=4.5V"
   )
19 disp("  B-C            I1-I2=0.75A      4(I1-I2)=3V"
   )
20 disp("  C-D            I1-I2=0.75A      6(I1-I2)=4.5
   V")
21 disp("  B-E            I2=1.5A          5(I2)=7.5V"
   )
22 disp("  F-A            I1=2.25A          12V source"

```

)

---

### Scilab code Exa 1.24 find voltage drop

```
1 //example1.24
2 clc
3 i=20/(2+1.2727)
4 format(7)
5 disp(i,"I(in A)=")
6 disp("By current division rule,")
7 i=(6.1111*2)/5.5
8 format(6)
9 disp(i,"I1(in A)=9(I*2)/(2+3.5)=")
10 v=2.222*1
11 disp(v,"V(1 ohm)=I1*1=")
12 i=(6.1111*3.5)/5.5
13 disp(i,"I2(in A)=(3.5*I)/(2 +3.5)=")
14 p=((3.888)^2)*2
15 format(7)
16 disp(p,"P(2 ohm) [in W]=(I2^2)*2=")
```

---

### Scilab code Exa 1.25 find inductive resistance

```
1 //example1.25
2 clc
3 disp("The arrangement is shown in the fig 1.97.")
4 x=110/10
5 disp(x,"X_L(in ohm)=V/I=")
6 disp("The inductive reactance is 11 ohm")
7 disp("X_L=2*pi*f*L")
8 disp("Therefore , 11=2*pi*50*L")
9 l=11/(2*%pi*50)
10 format(9)
```

```
11 disp(1,"L(in H)=")
```

---

**Scilab code Exa 1.26** find resistance

```
1 //example1.26
2 clc
3 disp("For d.c. supply frequency is 0 Hz.")
4 disp("X_C=1/(2*pi*f*C)=1/0=infinity")
5 disp("So capacitor gives infinite reactance in d.c.
    supply and acts as an open circuits.")
6 disp("In an a.c. supply of 100 Hz,")
7 x=1/(2*%pi*100*50*10^-6)
8 format(9)
9 disp(x,"X_C(in ohm)=1/(2*pi*f*C)=")
```

---

**Scilab code Exa 1.27** find resistance

```
1 //example1.27
2 clc
3 disp("The circuit can be redrawn as shown in the fig
    1.99(a)")
4 disp("fig 1.99(a,b) see on next page")
5 disp("Therefore , R_eq=[30(10+R)/(30+10+R)]=(300+30R)
    /(40+R)")
6 disp("Therefore , I=V/(R_eq) i.e 6=30/[(300+30R)
    /(40+R)]")
7 disp("6(300+30R)=50(40+R) i.e. 1800+180R
    =2000+50R")
8 r=200/130
9 format(7)
10 disp(r,"R(in ohm)=")
11 disp("By current division rule ,")
12 i=(6*11.5384)/41.5384
```

```

13 format(6)
14 disp(i," I1 (in A)=[( I_t )*(10+R)/(10+R+30)]=")
15 i=(6*30)/41.5384
16 disp(i," I2 (in A)=[( I_t )*30/(10+R+30)]=")
17 disp("Key point: Cross check I1+I2= 6 A")

```

---

### Scilab code Exa 1.28 find resistance

```

1 //example1.28
2 clc
3 disp(" Convert the delta of 2ohm, 3ohm and 5ohm to
   equivalent star as shown in the fig 1.101(a)")
4 r=15/10
5 disp(r,"R1(in ohm)=(5*3)/(5+3+2)=")
6 r=6/10
7 disp(r,"R2(in ohm)=(3*2)/(5+3+2)=")
8 r=10/10
9 disp(r,"R3(in ohm)=(5*2)/(5+3+2)=")
10 disp(" Convert the delta of 1ohm, 5.6ohm and 4ohm to
   equivalent star as shown in the fig 101(c)")
11 r=5.6/10.6
12 format(7)
13 disp(r,"R4(in ohm)=(5.6*1)/(1+5.6+4)=")
14 r=(5.6*4)/10.6
15 disp(r,"R5(in ohm)=(5.6*4)/(1+5.6+4)=")
16 r=4/10.6
17 disp(r,"R6(in ohm)=(1*4)/(1+5.6+4)=")
18 r=3.4705+0.3773
19 disp(r," Therefore , R_ab(in ohm)=3.4705+0.3773=")

```

---

### Scilab code Exa 1.29 find resistance

```

1 //example1.29

```

```

2  clc
3  disp("Convert the inner delta of 5ohm to equivalent
      star. As all the resistances of delta are same,
      all the resistances of equivalent star will be
      equal of value ")
4  r=25/15
5  disp(r,"R(in ohm)=(5*5)/(5+5+5)=")
6  disp("Convert the delta of 6.667ohm, 5ohm and 11.667
      ohm")
7  r=(6.667*11.667)/(6.667+11.667+5)
8  format(7)
9  disp(r,"R1(in ohm)=(6.667*11.667)/(6.667+11.667+5)="
      )
10 r=(6.667*5)/(6.667+11.667+5)
11 disp(r,"R2(in ohm)=(6.667*5)/(6.667+11.667+5)=")
12 r=(5*11.667)/(6.667+11.667+5)
13 format(7)
14 disp(r,"R3(in ohm)=(5*11.667)/(6.667+11.667+5)=")
15 r=5.333+2.612
16 format(7)
17 disp(r,"Therefore ,   R_ab(in ohm)=5.333+2.612=")

```

---

### Scilab code Exa 1.30 find current

```

1  //example1.30
2  clc
3  disp("Let us divide the voltage waveform into two
      sections.")
4  disp("For  $0 \leq t \leq 2$ ,  $v(t) = mt$  where,")
5  m=10/2
6  disp(m,"m=(10-0)/(2-0)=")
7  disp("Therefore ,    $i(t) = v(t)/R = 5t/40 = 0.125t$  A")
8  i=0.125*2
9  disp(i,"At  $t=2$ ,  $v(t) = 10$  V,    $i(t)$  [in A] =  $0.125*2 =$ ")
10 m=(-10)/2

```



```

11 disp(m,"For  $2 \leq t \leq 4$ ,  $v(t) = mt + c$  where  $m = (0 - 10)$ 
     $/(4 - 2) =$ ")
12 disp("Therefore ,  $v(t) = -5t + C$ ")
13 c = 5 * 4
14 disp(c,"Now at  $t = 4$ ,  $v(t) = 0$  i.e.  $0 = -5 * 4 + C$  i.e
     $C =$ ")
15 disp("Therefore ,  $v(t) = -5t + 20$ ")
16 disp("Therefore ,  $i(t) = v(t) / R = (-5t + 20) / 40 = -0.125$ 
     $t + 0.5$ ")
17 disp("At  $t = 4$ ,  $v(t) = -5 * 4 + 20 = 0$  V,  $i(t) =$ 
     $-0.125 * 4 + 0.5 = 0$  V")
18 disp("Hence the waveform of the current passing
    through the resistance is as shown in the fig
    1.105")

```

---

**Scilab code Exa 1.31** obtain current

```

1 //example1.31
2 clc
3 disp("Method 1: Kirchoffs laws")
4 disp("Now apply KVL to the two loops without current
    source as effect of the currents in various
    branches.")
5 disp("-2(I1 - 2) - I2 + 6 = 0 i.e.  $2(I1) + I2 = 10$  ..(1)"
    )
6 disp("-3(I1 - 2 - I2) - 12 + I2 = 0 i.e.  $-3(I1) + 4(I2) = 6$ 
    ..(2)")
7 disp("-3(I1) + 4(10 - 2(I1)) = 6")
8 i = 34 / 11
9 format(7)
10 disp(i,"Therefore ,  $I1$  (in A) =")
11 i = 10 - (2 * 3.0909)
12 disp(i,"and ,  $I2$  (in A) =")
13 disp("Currents through various resistances are,")
14 i = 3.0909 - 2

```

```

15 disp(i," I(2ohm) [in A]=I1-2=")
16 disp(" I(1ohm) [in A]=I2=3.8181")
17 i=3.0909-2-3.8181
18 disp(i," I(3ohm) [in A]=I1-2-I2=")
19 disp("Current through 3ohm is negative i.e. it is
        flowing in opposite direction to that assumed in
        the circuit.")
20 disp("Method II: Loop analysis")
21 disp("From the current source branch,")
22 disp(" I3= 2 A")
23 disp("Applying KVL to the other two loopos without
        current source,")
24 disp("-2(I1)+2(I3)-I1+I2+6=0    i.e.    -3(I1)+I2=
        -10    ..(1)")
25 disp("-3(I2)+3(I3)-I2-I1+I1=0    i.e.    I1-4(I2)=6
        ..(2)")
26 disp("Solving we get,")
27 disp(" I1-4(-10+3(I1))=6")
28 i=34/11
29 disp(i," I1 (in A)=")
30 i=(3.0909-6)/4
31 disp(i," and, I2 (in A)=")
32 disp("Currents through various resistances are,")
33 i=3.0909-2
34 disp(i," I(2ohm) [in A]=I1-2=")
35 i=3.0909+0.7272
36 disp(i," I(1ohm) [in A]=I1-I2=")
37 i=-0.7272-2
38 disp(i," I(3ohm) [in A]=I2-2=")
39 disp("The currents are same as obtained by the
        method 1.")

```

---

Scilab code Exa 1.32 calculate current

```
1 //example1.32
```

```

2  clc
3  disp("Use the loop analysis")
4  disp("From the current source branch,")
5  disp("I3=1 A")
6  disp("Applying KVL to the loops without current
       source we get,")
7  disp("-6(I1)-4-5(I1)+5(I2)=0    i.e.    -11(I1)+5(I2)
       )=4    ..(1)")
8  disp("-5(I2)+5(I1)-6-4(I2)-4(I3)=0    i.e.    5(I1)-9(I2)=10    (2)")
9  disp("Solving, we get:")
10 disp("-11(I1)+5((5I1-10)/9)=4")
11 disp("Therefore,    -99(I1)+25(I1)-50=36")
12 i=86/(-74)
13 format(7)
14 disp(i,"Therefore,    I1(in A)=")
15 i=((5*(-1.1621))-10)/9
16 disp(i,"and,    I2(in A)=")
17 disp("Current through 5ohm in specified direction is
       ,")
18 i=(-1.7567+1.1621)
19 disp(i,"I(5ohm)[in A]=I2-I1= -1.7567-(-1.1621)")
20 disp("As negative, current through 5ohm flows in
       opposite direction to that specified in the
       circuit.")

```

---

# Chapter 2

## DC Machines

Scilab code Exa 2.1 generated emf

```
1 //example2.1
2 clc
3 disp("P=4    Z=440    psi=0.07 Wb    and    N=900 r.p.m.
      ")
4 disp("E=(psi*P*N*Z)/(6*A)")
5 disp(" i) For lap wound,    A=P=4")
6 e=(0.07*900*440)/60
7 disp(e," Therefore ,    E(in V)=(psi*N*Z)/60=")
8 disp(" ii) For wave wound,    A=2")
9 e=(0.07*900*4*440)/120
10 disp(e," Therefore ,    E(in V)=(psi*P*N*Z)/120=")
```

---

Scilab code Exa 2.2 generated emf and speed

```
1 //example2.2
2 clc
3 disp("P=4    psi=21 mWb=21*10^-3 Wb,    N=1120 r.p.m")
4 disp(" Coils = 42 and turns/coil = 8")
```

```

5 t=42*8
6 disp(t,"Total turns = coil * turns/coil = 42*8 =")
7 z=2*336
8 disp(z,"Z= 2*total turns = 2*336 =")
9 disp("i) for lap wound, A=P")
10 e=(21*1120*672*10^-3)/60
11 format(8)
12 disp(e,"Therefore , E(in V)=(psi*N*Z)/60=")
13 disp("ii) For wave wound, A=2")
14 disp("and, E=263.424 V")
15 disp("Therefore , E=(psi*P*N*Z)/120")
16 n=263.424*120/(21*4*672*10^-3)
17 disp(n,"N(in rpm)=")

```

---

### Scilab code Exa 2.3 induced emf of generator

```

1 //example2.3
2 clc
3 disp("Consider shunt generator as shown in the fig
4 2.29")
5 disp("I_a=(I_L)+(I_sh)")
6 disp("I_sh=(V_t)/(R_sh)")
7 disp("Now, V_t=250 V")
8 disp("and, R_sh=100 ohm")
9 i=250/100
10 disp(i,"Therefore , I_sh(in A)=")
11 disp("Load power=5 kW")
12 disp("Therefore , P=(V_t)*(I_L)")
13 i=(5*10^3)/250
14 disp(i,"I_L(in A)=P/(V_t)=")
15 i=20+2.5
16 disp(i,"(I_a)[in A]=(I_L)+(I_sh)=")
17 disp("E=(V_t)+((I_a)*(R_a))[neglect V_brush]")
18 E=250+(22.5*0.22)
19 disp(E,"Therefore , E(in V)=")

```

```
19 disp("This is the induced emf to supply the given
    load.")
```

---

#### Scilab code Exa 2.4 armature resistance of generator

```
1 //example2.4
2 clc
3 disp("Consider separately excited generator as shown
    in the fig 2.30")
4 disp("Note that 250V, 10kW generator means the full
    load capacity of generator is to supply 10kW load
    at a terminal voltage V_t=250 V")
5 disp("Therefore, V_t=250V and P=10kW")
6 disp("and, P=(V_t)*(I_L)")
7 i=(10^4)/250
8 disp(i,"Therefore, I_L(in A)=")
9 disp("Therefore, I_a=I_L= 40 A ...As separately
    excited")
10 disp("Now, E=(V_t)+[(I_a)*(R_a)]+(V_brush)")
11 disp("Now there are two brushes and brush drop is 2V
    /brush")
12 v=2*2
13 disp(v,"Therefore, V_brush(in V)=")
14 disp("Therefore, E=250+40(R_a)+4")
15 disp("But, E=255 V on full load")
16 disp("255 = 250 + 40(R_a) + 4")
17 r=1/40
18 disp(r,"Therefore, R_a(in ohm)=")
```

---

#### Scilab code Exa 2.5 terminal voltage at load

```
1 //example2.5
2 clc
```

```

3 disp(" Consider the series generator as shown in fig
      2.31")
4 disp(" R_a=0.5 ohm      and      R_se=0.03 ohm")
5 disp(" V_brush=2 V")
6 disp(" N=1500 rpm")
7 disp(" Total coils are 540 with 6 turns/coil.")
8 t=540*6
9 disp(t," Therefore ,      Total turns =540*6=")
10 disp(" Total conductors Z= 2* turns")
11 z=2*3240
12 disp(z," z=2*3240=")
13 disp(" Therefore ,      E=(psi*P*N*Z)/(60*A)")
14 disp(" For lap type , A=P")
15 disp(" psi=2 mWb=2*10^-3 Wb")
16 e=(1500*6480*2*10^-3)/60
17 disp(e," Therefore ,      E(in V)=")
18 disp(" E=(V_t)+(I_a) [( R_a)+(R_sc) ]+( V_brush)      ..
      Total V_brush given")
19 disp(" Where ,      I_a=I_L=50 A")
20 disp(" 324=(V_t) +50(0.5+0.03)+2")
21 v=322-(50*(0.53))
22 disp(v," V_t (in V)=")

```

---

**Scilab code Exa 2.6** generated voltage

```

1 //example2.6
2 clc
3 disp(" Consider a short shunt generator as shown in
      the fig 2.32")
4 disp(" R_a=0.04 ohm,      R_sh=90 ohm,      R_se=0.02 ohm")
5 disp(" V_t=225 V ,      I_L=75 A")
6 disp(" I_a = I_L + I_sh")
7 disp(" Now,      E=(V_t) +[( I_a) *(R_a) ]+[( I_L) *(R_se) ]
      ")
8 disp(" and drop across armature terminals is,")

```

```

9 disp("E-[(I_a)*(R_a)]=(V_t)+[(I_t)*(R_se)]")
10 e=225+(75*0.02)
11 disp(e,"Therefore ,      E-[(I_a)*(R_a)]=")
12 disp("Therefore ,      I_sh=[E-(I_a)(R_a)]/(R_sh)=[(V_t
    )+(I_L)(R_se)]/(R_sh)")
13 i=226.5/90
14 format(7)
15 disp(i,"Therefore ,      I_sh(in A)=")
16 i=75+2.5167
17 disp(i,"Therefore ,      I_a=I_L+I_sh=")
18 disp("Therefore ,      E=V_t+[(I_a)*(I_sh)]+[(I_L)*(
    R_se)]")
19 e=225+(77.5167*0.04)+(75*0.02)
20 format(6)
21 disp(e,"E(in V)=")

```

---

#### Scilab code Exa 2.7 induced emf in motor

```

1 //example2.7
2 clc
3 disp("V=200 V, I_a=30 A, R_a=0.75 ohm are the given
    values.")
4 disp("For a motor, V=(E_b)+[(I_a)*(R_a)]")
5 disp("Therefore ,      220=(E_b)+(30*0.75)")
6 e=220-(30*0.75)
7 disp(e,"E_b(in V)=")
8 disp("This is the induced emf called back emf in a
    motor")

```

---

#### Scilab code Exa 2.8 back emf and speed of motor

```

1 //example2.8
2 clc

```



```

3 disp("P=4, A=P=4 as lap, V=230 V, Z=250")
4 disp("psi=30mWb=30*10^-3 Wb, I_a=40 A")
5 disp("From voltage equation, V=E_b+[(I_a)*(R_a)]")
6 disp("230=E_b+(40*0.6)")
7 e=230-(40*0.6)
8 disp(e,"Therefore, E_b(in V)=")
9 disp("E_b=(psi*P*N*Z)/(60*A)")
10 disp("Therefore, 206=(4*N*250*30*10^-3)/(60*4)")
11 n=(206*240)/(250*4*30*10^-3)
12 disp(n,"N(in rpm)=")

```

---

#### Scilab code Exa 2.9 gross torque

```

1 //example2.9
2 clc
3 disp("P=4, A=P=4, Z=480")
4 disp("psi=20mWb=20*10^-3 Wb, I_a=50 A")
5 t=(0.159*0.02*50*4*480)/4
6 format(7)
7 disp(t,"Now, T_a(in N-m)=0.159*(psi)*(I_a)*(P*Z)/A=")

```

---

#### Scilab code Exa 2.10 induced emf and armature current and stray losses and lost torque

```

1 //example2.10
2 clc
3 disp("P=4, A=P=4")
4 disp("Running light it is on no load.")
5 disp("Therefore, N_0=1000 rpm Z=540 and psi")
6 e=(100*540)/240

```

```

7 disp(e," Therefore , E_b0 (in V)=(psi*P*N*Z)/(60*A)=")
8 disp(" i) Induced emf, E_b0=225 V")
9 disp(" ii) From voltage equation , V=(E_b)+[(I_a)*(
      R_a)]")
10 disp("V=(E_b0)+[(I_a0)*(R_a)]")
11 disp(" 230=225+[(I_a0)*0.8]")
12 i=5/0.8
13 disp(i," I_a0 (in A)=")
14 disp(" iii) On no load ,power developed is fully the
      power required to overcome stray losses.")
15 e=225*6.25
16 format(8)
17 disp(e," Stray losses=(E_b0)*(I_a0)=")
18 t=(1406.25*60)/(2*pi*1000)
19 format(7)
20 disp(t," T_f (in N-m)=[(E_b0)*(I_a0)]/(w_0)=")

```

---

### Scilab code Exa 2.11 speed of motor

```

1 //example2.11
2 clc
3 disp("P=4, Z=200, A=2, psi=25*10^-3 Wb")
4 disp("(I_a)=(I_L)=60 A, R_a=0.15ohm, R_se=0.2
      ohm")
5 disp("V=(E_b)+(I_a*R_a)+(I_a*R_se)")
6 disp("250=E_b+60(0.15+0.2)")
7 b=250-(60*(0.15+0.2))
8 disp(b," E_b (in V)=")
9 disp("Now, E_b=(psi*P*N*Z)/(60*A)")
10 disp("Therefore , 229=(25*(10^-3)*4*N*200)/(60*2)"
      )
11 n=(229*60*2)/(800*25*10^-3)
12 disp(n," Therefore , N(in rpm)=")

```

---

**Scilab code Exa 2.12** armature current and back emf

```
1 //example2.12
2 clc
3 disp("V=250 V, I_L=20 A, R_s=0.3ohm, R_sh=200
      ohm")
4 disp("I_L=(I_a)+(I_sh)")
5 s=250/200
6 disp(s,"(I_sh) [in A]=V/(R_sh)=")
7 disp("Therefore, I_a=(I_L)-(I_sh)")
8 a=20-1.25
9 disp(a,"I_a (in A)=20-1.25=")
10 disp("Now, V=(E_b)+(I_a*R_a)")
11 disp("Therefore, E_b=V-[(I_a)*(R_a)]")
12 b=250-(18.75*0.3)
13 format(8)
14 disp(b,"E_b (in V)")
```

---

**Scilab code Exa 2.13** speed on full load

```
1 //example2.13
2 clc
3 disp("Let no load, speed be N_0=1000 rpm")
4 disp("I_L0=Line current on no load=6 A")
5 disp("I_L0=(I_a0)+(I_sh)")
6 s=220/110
7 disp(s,"(I_sh) [in A]=V/(R_sh)=")
8 a=6-2
9 disp(a,"Therefore, (I_a0) [in A]=(I_L0)-(I_sh)=")
10 disp("Therefore, Back emf on no load E_b0 can be
      determined from the voltage equation.")
11 disp("V=(E_b0)+[(I_a0)+(R_a)]")
```

```

12 disp(" Therefore ,      220=(E_b0) +(4*0.3)")
13 b=220-1.2
14 disp(b," E_b0(in V)=")
15 disp("On full load condition ,supply voltage is
      constant and hence,")
16 s=220/110
17 disp(s," (I_sh) [in A]=V/(R_sh)=")
18 disp("Now, (I_L)=(I_aFL)+(I_sh)")
19 disp(" Therefore ,      50=(I_aFL)+2")
20 f=50-2
21 disp(f," Therefore ,   (I_aFL) [in A]=")
22 disp("And,   V=(E_bFL) +[(I_aFL) *(R_a) ]")
23 disp(" Therefore ,      220=(E_bFL +(48*0.3) )")
24 b=220-(48*0.3)
25 disp(b," Therefore ,   (E_bFL) [in V]=")
26 disp("From the speed equation,")
27 disp("N directly proportional to (E_b)/psi")
28 disp("But psi is constant as I_sh is constant for
      both the load conditions")
29 disp(" Therefore ,      (N_0)/(N_FL)=(E_b0)/(E_bFL)")
30 n=(1000*205.6)/218.8
31 format(7)
32 disp(n," Therefore ,      (N_FL) [in rpm]=[(N_0) *(E_bFL)
      ]/(E_b0)=")

```

---

#### Scilab code Exa 2.14 speed of motor on new load

```

1 //example2.14
2 clc
3 disp(" For load 1, N1=800 rpm,   I1=(I_a1)=20A")
4 disp(" For load 2,   I2=(I_a2)=50 A,   R_a=0.2 ohm,
      R_se=0.3 ohm")
5 disp("From voltage equation V=(E_b1) +[(I_a1) *(R_a)
      ]+[(I_se1) *(R_se) ]")
6 disp(" but   I1=(I_a1)=(I_se1)=20 A")

```

```

7 disp(" Therefore ,      250=(E_b1) +20(0.2+0.3)")
8 b=250-10
9 disp(b," Therefore ,      E_b1(in V)=")
10 disp(" and ,      V=(E_b2) +[(I_a2)*R_a] +[(I_se2)+(R_se) ]")
11 disp(" Therefore ,      250=(E_b2) +50(0.2+0.3)")
12 b=250-25
13 disp(b," E_b2(in V)=")
14 disp("From the speed equation ,")
15 disp("N is directly proportional to (E_b)/psi")
16 disp("Now, psi proportional to (I_se) and (I_a)")
17 disp(" Therefore ,      N1/N2=[(E_b1)*(psi_2) ]/[ (E_b2)*(psi_1) ]")
18 disp(" Therefore ,      N1/N2=[(E_b1)*(I_a2) ]/[ (E_b2)*(I_a1) ]")
19 n=(800*225*20)/(240*50)
20 disp(n," Therefore ,      N2(in rpm)=[(N1)*(E_b2)*(I_a1) ]/[ (E_b1)*(I_a2) ]=")

```

---

### Scilab code Exa 2.15 terminal voltage

```

1 //example2.15
2 clc
3 disp(" Consider the generator as shown in fig 2.61")
4 disp("P=4, A=P=4, N=750 rpm, psi=30 mWb=30*10^-3, Z=720")
5 n=(4*750*720*30*10^-3)/(240)
6 disp(n,"E(in V)=(psi*P*N*Z)/(60*A)=")
7 disp("E=(V_t) +[(I_a)*(R_a) ]")
8 disp("(V_t)=(I_L)*(R_L) i.e. I_L=(V_t)/(R_L)")
9 disp("And, I_sh=(V_t)/(R_sh)")
10 disp("I_a=(I_L)+(I_sh)=[(V_t)/(R_L)] +[(V_t)/(R_sh) ]")
11 disp("Substituting in voltage equation ,")
12 disp("E=(V_t) +[(V_t)/(R_L) +(V_t)/(R_sh) ]*(R_a)")

```

```

13 disp(" Therefore ,      270=(V_t) +[(V_t)/(15)+(V_t)
      /(200)]*(0.4)")
14 disp(" 270=1.0286(V_t)")
15 v=270/1.0286
16 format(9)
17 disp(v," V_t(in V)=")

```

---

**Scilab code Exa 2.16** full load output and efficiency of motor

```

1 //example2.16
2 clc
3 disp("No load current I=2.5 A,")
4 n=440*2.5
5 disp(n,"No load input(in W)= (V*I)=")
6 s=440/550
7 disp(s," I_sh(in A)=V/R_sh=")
8 disp("In dc shunt motor,      I=(I_sh)+(I_a)")
9 a=2.5-0.8
10 disp(a," I_a(in A)=I-(I_sh)=")
11 p=1.2*(1.7)^2
12 format(6)
13 disp(p,"No load armature copper loss(in watts)= (R_a
      )*(I_a)^2=")
14 disp("Constant losses= No load input- No lpad
      armature Cu losses")
15 c=1100-3.468
16 format(9)
17 disp(c," Therefore ,      Constant losses(in Z)=")
18 disp("Now, full load line current i.e I=32 A")
19 disp("I=(I_sh)+(I_a)")
20 a=32-0.8
21 disp(a," I_a(in A)=I-(I_sh)=")
22 p=1.2*(31.2)^2
23 disp(p," Full load armature copper loss=(R_a)*(I_a)
      ^2=")

```

```

24 disp("Total losses= Full load armature Cu loss +
      Constant losses")
25 l=1168.128+1096.532
26 disp(l,"Therefore , Total losses (in W)=")
27 v=440*32
28 disp(v,"Full load motor input (in W)= V*I =")
29 v=14080-2264.66
30 disp(v,"Full load motor output (in W)= Input-Losses="
      )
31 d=(1181534)/14080
32 format(6)
33 disp(d,"% efficiency at full load= [( Full load
      Output)/(full load input)]*100=")
34 disp("Therefore ,      Efficiency of motor at full load
      = 83.91%")

```

---

**Scilab code Exa 2.17** armature current and back emf and speed of motor

```

1 //example2.17
2 clc
3 disp("R_a=0.08 ohm, E_b1=242 V")
4 disp(" i)      V=(E_b1) +[(I_a1)*(R_a)]")
5 disp("Therefore ,      250=242+[(I_a1)*0.08]")
6 a=8/0.08
7 disp(a,"I_a1 (in A)=")
8 disp(" ii)   At start ,      N=0 hence E_b=0")
9 a=250/0.08
10 disp(a,"(I_a (start)) [in A]=V/(R_a)=")
11 disp(" iii)  If (I_a2)=120 A then ,")
12 b=250-(120*0.08)
13 disp(b,"E_b2 (in V)=V-[(I_a2)*(R_a)]=")
14 disp(" iv)   Machine is running as a generator , shown
      in the fig 2.62")
15 disp("Let induced emf as generator be E_g")
16 g=250+(87*0.08)

```

```

17 format(7)
18 disp(g,"E_g(in V)=(V_t)+[(I_a)*(R_a)]=")
19 disp("In both cases as a motor or generator E is
        directly prportional to (N*psi)")
20 disp("As flux is constant, E is directly
        proportional to N")
21 disp("Therefore, (E_b/E_g)=(N_m/N_g)")
22 disp("where N_m= Speed as a motor and N_g=
        Speed as a generator")
23 disp("Therefore, (242/256.96)=(1500/N_g)")
24 n=(1500*256.96)/242
25 disp(n,"N_g(in rpm)=")

```

---

**Scilab code Exa 2.18** extra resistance to be added

```

1 //example2.18
2 clc
3 disp("V=200 V, I_a1=30 A")
4 disp("Resistance across terminals=(R_a)+(R_se)=1.5
        ohm")
5 b=200-45
6 disp(b,"Therefore, E_b1(in V)=V-[(I_a1)*(R_a-R_se
        )]=")
7 disp("N2=0.6(N1)")
8 disp("Therefore, (N1/N2)=(1/0.6)")
9 disp("Use torque equation,")
10 disp("T is directly proportional to (psi*I_a) and (
        I_a)^2")
11 disp("as ... psi is directly proportional to I_a")
12 disp("Therefore, (T1/T2)=[(I_a1)/(I_a2)]^2
        ..(1)")
13 disp("Also T is directly proportional to N^3 given,")
14 disp("(T1/T2)=(N1/N2)^3=(1/0.6)^3 ..(2)")
15 disp("Equating equation (1) and (2), (1/0.6)^3 =

```



```

    (30/I_a2)^2")
16 a=sqrt(900*(0.6^3))
17 format(8)
18 disp(a,"Therefore, I_a2 (in A)=")
19 disp("E_b2=V-[(I_a2)*(R_a+R_se+R_x)
    ]=200-13.9427(1.5+R_x) .. (3)")
20 disp("Use speed equation, N directly proportional
    to [(E_b)/psi] and [(E_b)/(I_a)] ... psi
    id directly proportional to I_a")
21 disp("Therefore, (N1/N2)=[(E_b1)/(E_b2)]*[(I_a2)
    /(I_a1)]")
22 disp("Therefore, (1/0.6)=(155/E_b2)*(13.9427/30)"
    )
23 b=155*0.139427*2
24 format(6)
25 disp(b,"E_b2 (in V)=")
26 disp("Equating equations (3) and (4),
    43.22=200-13.9427(1.5+R_x)")
27 r=[(200-43.22)/13.9427]-1.5
28 disp(r,"R_x (in ohm)=")

```

---

### Scilab code Exa 2.19 efficiency of motor

```

1 //example2.19
2 clc
3 disp("No load current = I_L0 = 4 A")
4 s=250/250
5 disp(s,"I_sh [in A]=V/(R_sh)=")
6 a=4-1
7 disp(a,"Therefore, I_a0 (in A)=(I_L0)-(I_sh)=")
8 r=0.3*(3)^2
9 disp(r,"Therefore, No. load armature copper loss(
    in W)=[(I_a0)^2*(R_a)]=")
10 o=250*4
11 disp(o,"No load input (in W) = V*I_L0 =")

```

```

12 c=1000-2.7
13 disp(c," Constant losses (in W) = No load input-No
    load armature copper loss=")
14 disp("On full load ,      I_L=60 A and I_sh=1 A")
15 j=60-1
16 disp(j," Therefore ,      I_a (in A)=(I_L)-(I_sh)=")
17 l=0.3*(59)^2
18 disp(l," Full load armature copper loss (in W)= (I_a
    ^2)*R_a=")
19 l=997.3+2041.6
20 disp(l," Total loss on full load=constant losses+ [(
    I_a)^2*(R_a) loss]=")
21 disp(" Total input on full load = V*(I_L)")
22 l=250*60
23 disp(l," Therefore ,      P_in (in W)=")
24 p=15000-2041.6
25 format(8)
26 disp(p," (P_out) [in W]=(P_in)-Total loss=")
27 n=1295840/15000
28 format(7)
29 disp(n,"% efficiency (n)=[(P_out)*100]/(P_in)=")

```

---

### Scilab code Exa 2.20 lap and wave wound

```

1 //exmaple1.20
2 clc
3 disp("P=6, Z=780, E_g=500V, N=1000 rpm")
4 disp(" a) Lap wound, A=P=6")
5 disp("(E_g)=(psi*P*N*Z)/(60*A)    i.e.    500=(psi
    *6*1000*780)/(60*6)")
6 s=(500*60*6)/(6*1000*780)
7 format(8)
8 disp(s," Therefore ,    psi (in Wb)=")
9 disp(" b) Wave wound, A=2")
10 disp("(E_g)=(psi*P*N*Z)/(60*A)    i.e.    500=(psi

```

```

        *6*1000*780)/(60*2)")
11 s=(500*60*2)/(6*1000*780)
12 disp(s," Therefore ,    psi (in Wb)=")

```

---

**Scilab code Exa 2.21** emf generated

```

1 //example2.21
2 clc
3 disp("P=6, psi=0.02 Wb, N=1000 rpm, A=P as lap wound
      ")
4 z=65*12
5 disp(z,"Z=slots*conductors/slot=")
6 g=(0.02*6*1000*780)/(60*6)
7 disp(g," E_g (in V)=(psi*P*N*Z)/(60*A)=")

```

---

**Scilab code Exa 2.22** speed of generator

```

1 //example2.22
2 clc
3 disp("P=4, A=2, psi=0.0121 Wb, Z=792, E_g=240 V")
4 disp("(E_g)=(psi*P*N*Z)/(60*A)    i.e.
      240=(0.0121*4*N*792)/(60*2)")
5 n=(480*60)/(792*4*0.0121)
6 format(9)
7 disp(n," Therefore ,          N(in rpm)=")

```

---

**Scilab code Exa 2.23** induced voltage

```

1 //example2.23
2 clc

```

```

3 disp("The generator is shown in the fig 2.64")
4 disp("The current through R_se is I_L=80 A as the
   generator is short shunt.")
5 disp("The drop across R_sh is the sum of the drop
   across R_se and V_t")
6 disp(" [( I_sh )*(R_sh)]=(V_t)+[(I_L)*(R_se)]")
7 disp(" i.e 100(I_sh)=250+(80*0.03)")
8 p=2.5+(0.8*0.03)
9 format(6)
10 disp(p,"( I_sh ) [in A]=")
11 a=80+2.524
12 format(7)
13 disp(a,"( I_a ) [in A]=(I_L)+(I_sh)=")
14 g=250+(82.524*0.05)+(80*0.03)+2
15 format(9)
16 disp(g,"E_g(in V)=(V_t)+[(I_a)*(R_a)]+[(I_L)*(R_se)
   ]+Brush drop")

```

---

#### Scilab code Exa 2.24 commutator bars

```

1 //example2.24
2 clc
3 disp("P=4, Lap hence A=P, N=1150 rpm, E_g=265 V")
4 n=56*6
5 disp(n,"Total turns=No. of coils*turns/coil=")
6 z=2*336
7 disp(z,"Therefore , Z=2*total turns=")
8 disp("E_g=(psi*P*N*Z)/(60*A) i.e 265=(psi
   *4*1150*672)/(60*A)")
9 s=(265*60*4)/(4*1150*672)
10 disp(s,"Therefore , psi(in Wb)=")
11 disp("Number of commutator bars=Number of coils=56")

```

---

### Scilab code Exa 2.25 induced emf

```
1 //example2.26
2 clc
3 disp("For a d.c. generator,")
4 disp("E_g=(psi*N*P*Z)/(60*A) i.e E_g is
      directly proportional to (psi*N) ... (P*Z)
      /(60*A) is constant")
5 disp("N1=1000 rpm, (psi_1)=0.02 Wb, (E_g1)=200 V, N2
      =1100 rpm, (psi_2)=0.019 Wb")
6 disp("[(E_g1)/(E_g2)]=[(N1*psi_1)/(N2*psi_2)] i.e
      [(200)/(E_g2)]=[(1000*0.02)/(1100*0.019)]")
7 g=(200*1100*0.019)/(1000*0.02)
8 disp(g,"Therefore, E_g2(in V)=")
```

---

### Scilab code Exa 2.26 total and useful torque and flux and rotational losses and efficiency

```
1 //example2.26
2 clc
3 disp("P=4, V=240 V, A=2 as wave, N=1000 rpm, P_out
      =11.19 kW")
4 disp("I_a=50 A, I_sh=50 A, R_a=0.1 ohm, Z=540")
5 disp("a) E_b=V-[(I_a)(R_a)]-Brush drop")
6 b=240-(50*0.1)-2
7 disp(b,"E_b(in V)=")
8 t=(233*50*60)/(2*pi*1000)
9 format(9)
10 disp(t,"Therefore, T(in Nm)=[(E_b)(I_a)]/w=[(E_b)(
      I_a)]/[(2*pi*N)/60]=")
11 t=(11190*60)/(2*pi*1000)
12 disp(t,"b) T_sh(in Nm)=useful torque=(P_out)/w=")
13 disp("c) E_b=(psi*P*N*Z)/(60*A) i.e 233=(psi
      *4*100*540)/(60*2)")
14 p=(233*60*2)/(4000*540)
```

```

15 format(6)
16 disp(p," Therefore ,      psi (in Wb)=")
17 disp(" Rotational losses= (T-T_sh)*w= (T-T_sh)*(2*pi*
      N)/60")
18 i=[(111.2493-106.8566)*(2*%pi*1000)]/60
19 format(4)
20 disp(i," Therefore , Rotational losses (in W)=")
21 p=240*51
22 format(7)
23 disp(p," P_in (in W)=V*(I_L)=V*(I_a+I_sh)=")
24 n=(11190*100)/12240
25 format(6)
26 disp(n,"% efficiency =[(P_out)*100]/(P_in)=")

```

---

#### Scilab code Exa 2.27 speed

```

1 //example2.27
2 clc
3 disp("V=250 V, N_0=1000 rpm, I_L0=5 A, R_a=0.2 ohm,
      R_sh=250 ohm")
4 i=250/250
5 disp(i," I_sh (in A)=(V/R_sh)=")
6 i=5-1
7 disp(i," Therefore , I_a0 (in A)=(I_L0)-(I_sh)=")
8 e=250-(4*0.2)
9 disp(e," E_b0 (in V)=V-[(I_a0)(R_a)]=")
10 disp("on load , I_L1=50 A, (psi_1)=(psi_0)-(3% of (
      psi_0))=0.97(psi_0)")
11 disp("I_sh remains constant as long as V and R_sh
      are constant.")
12 i=50-1
13 disp(i," I_a1 (in A)=(I_L1)-(I_sh)=")
14 e=250-(49*0.2)
15 disp(e," E_b1 (in V)=V-[(I_a1)(R_a)]=")
16 disp("N is directly proportional to (E_b/psi) ...")

```

```

Speed equation")
17 disp(" [(N_0)/N1]=[(E_b0)*(psi_1)]/[(E_b1)*(psi_0)]
    i.e. [(1000)/N1]=[(249.2)*(0.97*psi_0)]/[(240.2)
    *(psi_0)]")
18 n=(1000*240.2)/(249.2*0.97)
19 format(9)
20 disp(n," Therefore , N(in rpm)=")

```

---

### Scilab code Exa 2.28 torque

```

1 //exmaple2.28
2 clc
3 disp("P=6, A=2 as wave, Z=492, psi=30 mWb, I_a=40 A"
    )
4 disp("T=(psi*P*Z*I_a)/(2*pi*A) Nm")
5 t=(40*6*492*30*10^-3)/(2*pi*2)
6 format(9)
7 disp(t," Therefore , T(in Nm)=")
8 disp(" as 1N=(1/9.81)kg")
9 t=281.8952/9.81
10 format(8)
11 disp(t," Therefore , T(in kgm)=")

```

---

### Scilab code Exa 2.29 induced emf and electrical power output

```

1 //example2.29
2 clc
3 disp("P=4, N=1000 rpm, 80 slots , psi=6*10^-2 Wb, 8
    conductors/slot")
4 disp("A=P=4 ... Lap connected")
5 z=80*8
6 disp(z,"Z= Slots*conductors/slot=")
7 e=(4*100*640*6*10^-2)/240

```

```

8 disp(e,"E_g(in V)=(psi*P*N*Z)/(60*A)=")
9 disp("As coils are lap connected , parallel paths are
      4 and all conductors in each parallel path are
      in series , carrying a current of 50 A")
10 a=4*50
11 disp(a,"Therefore , I_a(in A)=A*current per parallel
      path=4*50=")
12 p=640*200
13 disp(p,"P(in W)=Electrical power output=[(E_g)*(I_a)
      ]=")

```

---

**Scilab code Exa 2.30** generated voltage and armature current

```

1 //exmaple2.30
2 clc
3 disp("The generator is shown in the fig. 2.66")
4 disp("I_L=50 A, V_L=500 V      ... Given")
5 i=500/250
6 disp(i,"I_sh(in A)=(V_t)/(R_sh)=")
7 a=2+50
8 disp(a,"Therefore , I_a(in A)=(I_L)+(I_sh)=2+50=")
9 disp("This is the armature current")
10 e=500+(52*0.05)+(52*0.03)+(2*1)
11 disp(e,"Therefore , E_g(in V)=(V_t)+[(I_a)*(R_a)]+[(
      I_a)*(R_se)]+Brush drop =")
12 disp("This is generated voltage.")

```

---

**Scilab code Exa 2.31** induced emf and speed

```

1 //example2.31
2 clc
3 disp("P=8, N=400 rpm, psi=40 mWb, Z=960")
4 disp("a) Lap wound, A=P=8")

```



```

5 e=(8*400*960*40*10^-3)/(60*8)
6 disp(e,"E_g (in V)=(psi*P*N*Z)/(60*A)=")
7 disp("b) Wave connected , A=2, E_g =400 V")
8 disp("Therefore , (E_g)=(psi*P*N*Z)/(60*A) i.e.
      400=[(40*10^-3)*8*N*960]/(60*2)")
9 n=(400*60*2)/(0.04*8*960)
10 disp(n,"Therefore , N(in rpm)=")

```

---

**Scilab code Exa 2.32** back emf and gross mechanical power

```

1 //example2.32
2 clc
3 disp("V=250 V, (R_a)=0.3 ohm, (I_L)=20 A, (R_sh)=200
      ohm")
4 s=250/200
5 disp(s,"I_sh (in A)=V/(R_sh)=")
6 a=20-1.25
7 disp(a,"I_a (in A)=(I_L)-(I_sh)=")
8 b=250-(18.75*0.3)
9 format(8)
10 disp(b,"E_b (in V)=V-[(I_a)(R_a)=")
11 m=244.375*18.75
12 format(10)
13 disp(m,"P_m (in W)=[(E_b)*(I_a)=")

```

---

**Scilab code Exa 2.33** generated emf and copper and iron losses and efficiency

```

1 //example2.33
2 clc
3 disp("The generator is shown in the fig 2.67")
4 s=500/200
5 disp("I_sh (in A)=(V_t)/(I_sh)=")

```

```

6 l=(25*10^3)/500
7 disp(1,"I_L (in A)=(P_L)/(V_t)=")
8 a=50+2.5
9 disp(a,"Therefore , I_a (in A)=(I_L)+(I_sh)=")
10 disp("Brush drop is 1V per brush hence total brush
      drop = 2V")
11 e=500+[52.5*(0.03+0.04)]+2
12 format(8)
13 disp(e,"a) E_g (in V)=(V_t)+[(I_a)*(R_a)]+[(I_a)*(
      R_se)]+(V_brush)=500+[52.5*(0.03+0.04)]+2=")
14 a=0.03*(52.5)^2
15 disp(a,"b) Armature copper loss (in W) = [(I_a)^2]*(
      R_a) =[(52.5)^2]*(0.03) =")
16 s=0.04*(52.5)^2
17 disp(s,"Series field copper loss (in W) =[(I_a)^2]*(
      R_se) =[(52.5)^2]*(0.04) =")
18 c=200*(2.5)^2
19 disp(c,"Shunt field copper loss (in W) =[(I_sh)^2]*(
      R_sh) =[(2.5)^2]*(200) =")
20 p=505.675*52.5
21 format(11)
22 disp(p,"P_in (in W)= (E_g)*(I_a)=")
23 disp("P_out = 25W")
24 t=26547.9375-25
25 format(10)
26 disp(t,"Therefore , Total losses (in W) = (P_in)-(
      P_out) =")
27 disp("Now total losses = Copper losses + Iron losses
      ")
28 disp("Therefore , 1547.9375 = 82.6875 + 110.25 +
      1250 + Iron losses")
29 i=1547.9375-(82.6875+110.25+1250)
30 format(4)
31 disp(i,"Therefore , Iron losses (in W)=")
32 n=(25000*100)/(26547.9375)
33 format(8)
34 disp(n,"%efficiency (n) =[(P_out)/(P_in)]*100 =")

```

---

**Scilab code Exa 2.34** total armature power

```
1 //example2.34
2 clc
3 disp(" i) As a generator")
4 disp("(P_out)=20 kW, (V_t)=250 V")
5 i=20000/250
6 disp(i," I_L (in A)=(P_out)/(V_t)=")
7 s=250/125
8 disp(s," I_sh (in A)=(V_t)/(R_sh)=")
9 a=80+2
10 disp(a," Therefore , I_a (in A)=(I_L)+(I_sh)=")
11 e=250+(82*0.1)
12 disp(e," E_g (in V)= (V_t)+[(I_a)*(R_a)]=")
13 p=258.2*82
14 format(7)
15 disp(p," P_g (in W)=(E_g)*(I_a)=")
16 disp(" ii) As a motor")
17 disp("(P_in)=20 kW, V=250 V")
18 i=(20000)/250
19 disp(i," Therefore , I_L (in A)=(P_in)/V=")
20 s=250/125
21 disp(s," I_sh (in A)=V/(R_sh)=")
22 a=80-2
23 disp(a," Therefore , I_a (in A)=(I_L)-(I_sh)=")
24 b=250-(78*0.1)
25 disp(b," Therefore , E_b (in V)=V-[(I_a)*(R_a)]=")
26 a=242.2*78
27 format(8)
28 disp(a," P_a (in W)=[(E_b)*(I_a)]=")
```

---

**Scilab code Exa 2.35** leakage coefficient

```

1 //example2.25
2 clc
3 disp("P=4, N=750 rpm, (E_g)=240 V, A=2 as wave, Z
      =792")
4 disp("(E_g)=(psi*P*N*Z)/(60*A) i.e. 240=(psi
      *4*750*792)/(60*2)")
5 p=(240*60*2)/(4*750*792)
6 format(8)
7 disp(p,"Therefore, psi(in Wb)=")
8 disp("Lamda= Leakage coefficient = (Total flux)/(
      Useful flux)")
9 l=0.0145/0.01212
10 format(6)
11 disp(l,"Therefore, lamda = 0.0145/0.01212 =")

```

---

**Scilab code Exa 2.36** no load terminal voltage and area of pole

```

1 //exmample2.26
2 clc
3 disp("(P_out)=1500 kW, (V_t)=550 V, P=10, A=P as lap
      , N=150 rpm, Z=2500, (P_cu)=25 kW, B=0.9 Wb/m^2")
4 i=(1500*1000)/550
5 format(10)
6 disp(i,"I_L(in A)=(P_out)/(V_t)=")
7 disp("As R_sh is not given, neglect I_sh hence (I_a)
      =2727.2727 A")
8 disp("a) P_cu = Armature copper loss = [(I_a)^2]*(
      R_a)")
9 disp("25*10^3 = (2727.2727)^2 * (R_a)")
10 a=25000/[(2727.2727)^2]
11 format(9)
12 disp(a,"Therefore, (R_a)[in ohm]=")
13 e=550+(2727.2727*3.3611*0.001)
14 disp(e,"Therefore, E_g(in V)=(V_t)+[(I_a)*(R_a)]=")
15 disp("This is load terminal voltage.")

```

```
16 disp("b) (E_g)=(psi*P*N*Z)/(60*A) i.e. 559.1667=(  
    psi*10*150*2500)/(60*10)")  
17 p=(559.1667*60*10)/(1500*2500)  
18 format(8)  
19 disp(p,"Therefore, psi(in Wb)=")  
20 disp("Now, B=(psi)/A i.e 0.9=(0.08946)/A")  
21 a=0.08946/0.9  
22 disp(a,"Therefore, A(in m^2)=")
```

---

# Chapter 3

## Transformers

**Scilab code Exa 3.1** primary and secondary turns and area of core

```
1 //example3.1
2 clc
3 disp("(B_m)=1 Wb/m^2, E1=240 V, E/turn=8 V, f=50 Hz"
   )
4 disp("E1=E/turn * N1           i.e.       240=8*N1")
5 disp("Therefore , N1=30")
6 disp("Therefore , N1/N2=E1/E2   i.e   30/N2=240/2400")
7 disp("N2=300")
8 disp("E1=4.44*(psi_m)*f*N1     i.e.       240=4.44*(
   psi_m)*50*30")
9 p=240/(4.44*50*30)
10 format(8)
11 disp(p,"Therefore , (psi_m)[in Wb]=")
12 a=0.03636/1
13 disp(a,"(B_m)=(psi_m)/a       i.e.       a(in m^2)=(
   psi_m)/(B_m)=")
```

---

**Scilab code Exa 3.2** peak value of flux in core and secondary voltage

```

1 //example3.2
2 clc
3 disp(" f=50 Hz, N1=480, N2=20, E1=5400 V")
4 disp(" E1=4.44*f*(psi_m)*N1      i.e.
      5400=4.44*50*(psi_m)*480")
5 p=5400/(4.44*50*480)
6 format(7)
7 disp(p," Therefore , (psi_m)[in Wb]=")
8 disp(" E1/E2=N1/N2  i.e.  E2=(N2*E1)/N1=(20*5400)/480
      ")
9 e=(20*5400)/480
10 disp(e," Therefore , E2(in V)=")

```

---

**Scilab code Exa 3.3** iron loss and maximum value of flux in core

```

1 //example3.3
2 clc
3 disp("The given values are , (I_0)=10 A, cos(psi_0)
      =0.25, V1=400 V and f=50Hz")
4 disp(" a) (I_m)=(I_0)*sin(psi_0)=Magnetising
      component")
5 p=acosd(0.25)
6 format(7)
7 disp(p," (psi_0)[in degree]=")
8 i=10*sind(75.522)
9 disp(i," I_m(in A)=,x")
10 disp("(P_i)=Iron loss = Power input on no load")
11 disp("= (W_0)= [(V1)*(I_0)*cos(psi_0)]= 400*10*0.25"
      )
12 w=4000*0.25
13 disp(w," P_i(in W)=")
14 disp(" c) On no load , E1=V1=400 V and N1=500")
15 disp(" E1=4.44*f*(psi_m)*N1")
16 disp(" Therefore , 400=4.44*50*(psi_m)*500")
17 i=400/(4.44*50*500)

```

```
18 format(9)
19 disp(i,"Therefore , (psi_m)[in Wb]=")
```

---

### Scilab code Exa 3.4 primary current

```
1 //example3.4
2 clc
3 disp("The given values are,")
4 disp("(I_0)=1 A, cos(psi_0)=0.4, I2=50 A, and cos(
      psi_2)=0.8")
5 k=200/400
6 disp(k,"K=E2/E1=")
7 k=0.5*50
8 disp(k,"Therefore , I2 ''(in A)=K*I2=")
9 disp("The angle of (I2 '') is to be decided from cos(
      psi_2)=0.8")
10 disp("Now, cos(psi_2)=0.8")
11 p=acosd(0.8)
12 format(6)
13 disp(p,"Therefore , (psi_2)[in degree]=")
14 disp("I2 '' is in antiphase with I2 which lags E2 by
      36.86 degree")
15 disp("Consider the phasor diagram shown in the fig
      3.18. The fluz (psi) is the reference")
16 disp("Now cos(psi_0)=0.4")
17 c=acosd(0.4)
18 disp(c,"Therefore , psi_0(in degree)")
19 disp("vector(I1)=vector(I2 '')+vector(I_0)")
20 disp("Resolve (I_0) and (I2 '') into two components,
      along reference (psi) and in quadrature with (psi
      ) in phase with V1.")
21 x=1*sind(66.42)
22 format(7)
23 disp(x,"x component of (I_0)=(I_0)*sin(psi_0)=")
24 x=1*cosd(66.42)
```



```

25 format(4)
26 disp(x,"y component of (I_0)=(I_0)*(psi_0)=")
27 disp("Therefore , vector(I_0)=0.9165+j(0.4) A")
28 i=25*sind(36.86)
29 format(7)
30 disp(i,"x component of I2 ''(in A)=I2 ''*sin(psi_2)=")
31 i=25*0.8
32 disp(i,"y component of I2 ''(in A)=I2 ''*cos(psi_2)=")
33 disp("Thus the two component of I1 are as shown in
      the fig 3.18(c)")
34 io=sqrt((15.9165^2)+(20.4^2))
35 disp(io,"I1(in A)=sqrt[((15.9165)^2)+(20.4)^2]=")
36 disp("This is the primary current magnitude.")
37 disp("while tan(phi_1)=15.9165/20.4")
38 t=atand(15.9165/20.4)
39 disp(t,"Therefore , (psi_1)[in degree]=")
40 disp("Hence the primary power factor is,")
41 i=cosd(37.96)
42 disp(i,"cos(psi_1)[lagging]=cos(37.96)=")
43 disp("Key point: Remember that (psi_1) is angle
      between V1 and I1 and as V1 is vertical , (psi_1)
      is measured with respect V1. So do not convert
      rectangular to polar as it goes angle with
      respect to x-axis and we want it with respect to
      y-axis.")

```

---

### Scilab code Exa 3.5 equivalent resistance

```

1 //example3.5
2 clc
3 disp("The given values are , R1=2.5 ohm, R2=0.01 ohm"
      )
4 k=400/6600
5 disp(k,"K=400/6600=")
6 disp("While finding equivalent resistance referred to

```

```

    primary, transfer R2 to primary as R2'',")
7 r=0.01/((0.0606)^2)
8 disp(r,"R2''(in ohm)=R2/K^2=")
9 r=2.5+2.7225
10 format(7)
11 disp(r,"Therefore, (R1e)[in ohm]=R1+R2''=")
12 disp("It can be observed that primary is high
    voltage hence high resistance side hence while
    transferring R2 from low voltage to R2'' on high
    voltage, its value increses.")
13 disp("To find total equivalent resistance referred
    to secondary, first calculate R1'',")
14 r=2.5*(0.0606)^2
15 format(8)
16 disp(r,"R1''(in ohm)=(K^2)*R1=(0.0606^2)*2.5=")
17 r=0.01+0.00918
18 disp(r,"(R2e)(in ohm)=R2*R1''=0.01*0.00918=")

```

---

### Scilab code Exa 3.6 total resistance and equivalent reactance and impedance

```

1 //example3.6
2 clc
3 disp("R1=1 ohm, R2=2 ohm, X1=3 ohm, X2=5 ohm")
4 k=110/220
5 disp(k,"K=V2/V1=")
6 r=1+(2/((0.5)^2))
7 disp(r,"Therefore, (R1e)[in ohm]=R1+R2''=R1+(R2/K
    ^2)=")
8 x=3+(5/((0.5)^2))
9 disp(x,"Therefore, (X1e)[in ohm]=X1+X2=X1+(X2/K^2)=
    ")
10 z=sqrt((9^2)+(23^2))
11 format(8)
12 disp(z,"Therefore, (Z1e)[in ohm]=sqrt((R1e^2)+(
    X1e^2))=")

```

```

13 r=9*(0.5^2)
14 disp(r," Therefore , (R_2e) [in ohm]=(K^2)*(R_1e)=")
15 x=(0.5^2)*23
16 disp(x," and , (X_2e) [in ohm]=(K^2)*(X_1e)=")
17 z=(0.5^2)*24.6981
18 format(7)
19 disp(z," Therefore , (Z_2e) [in ohm]=sqrt((R_2e^2)+(
      X_2e^2))=(K^2)*(Z_1e)=")

```

---

### Scilab code Exa 3.7 regulation and secondary terminal voltage

```

1 //example3.7
2 clc
3 disp("The given values are , R1=0.2 ohm, R2=0.05 ohm,
      X1=0.75 ohm, X2=0.2 ohm, cos(psi)=0.8 leading")
4 k=125/250
5 disp(k," E2/E1=")
6 i=(5*10^3)/125
7 disp(i," (I2) (F.L) [in A]=(kVA)/V2=")
8 r=0.05+((0.5^2)*0.2)
9 disp(r," R_2e(in ohm)=R2+(K^2)*R1=")
10 x=0.2+((0.5^2)*0.75)
11 format(7)
12 disp(x," X_2e(in ohm)=X2+(K^2)*X1=")
13 disp(" i) Regulation on full load , cos(psi)=0.8
      leading")
14 disp(" sin(psi)=0.6")
15 disp(" Therefore , %R=[(I2)*(R_2e)*cos(psi)-(I2)*(X_2e
      )*sin(psi)]/E2 * 100 , .. I2=I2(FL)=40 A")
16 disp(" = (40*0.1*0.8 - 40*0.3875*0.6)/125 * 100")
17 r=((40*0.1*0.8) - (40*0.3875*0.6))/1.25
18 format(5)
19 disp(r," = ")
20 disp(" ii) On full load , 0.8 p.f. leading the total
      voltage drop is ,")

```

```

21 disp(" Voltage drop (in V) = I2 (FL) [( R_2e) cos ( psi )-(
      X_2e) sin ( psi ) ]")
22 v=40*((0.1*0.8) -(0.3875*0.6))
23 format(4)
24 disp(v," = ")
25 disp(" Therefore , E2-V2= -6.1   i.e.   125-V2= -6.1")
26 v=125+6.1
27 format(6)
28 disp(v," Therefore , V2(in V)= Secondary terminal
      voltage = 125+ 6.1 =")

```

---

### Scilab code Exa 3.8 total copper loss and efficiency

```

1 //example3.8
2 clc
3 disp("The given values are , V1=200 V, V2=400 V, S=4
      kVA, (R_1e)=0.15 ohm, P1= 60 W")
4 k=4/2
5 disp(k,"K=400/200=")
6 r=(2^2)*0.15
7 disp(r," Therefore , (R_2e) [in ohm]=(K^2) (R_1e)=")
8 i=4000/400
9 disp(i," I2 (FL) [in A]=(kVA)/V2=")
10 disp("i) Total copper losses on full load,")
11 p=(10^2)*0.6
12 disp(p," (P_cu) (FL) [in W]=[I2 (FL)]^2 * (R_2e) =(10^2)
      *0.6 =")
13 disp(" ii) cos (psi)=0.9 lagging and full load")
14 disp(" Therefore , %n = [(VA rating cos (psi))/(VA
      rating cos (psi)+(P_i)+(P_cu)FL)]*100")
15 n=(4*0.9*10^5)/((4*0.9*10^3)+60+60)
16 format(6)
17 disp(n," Therefore , n(% efficiency)=(4*0.9*10^3)
      /((4*0.9*10^3)+60+60) * 100 =")
18 disp(" iii) cos (psi)=0.8 leading , half load")

```

```

19 disp("As half load , n=0.5")
20 p=(0.5^2)*60
21 disp(p,"(P_cu)(HL) [in W]=(n^2)*[(P_cu)(FL)]=(10.5^2)
    *60 =")
22 disp("Therefore , %n = [n*(VA rating cos(psi))/(n*VA
    rating cos(psi)+(P_i)+(P_cu)FL)]*100")
23 n=(4*0.5*0.8*10^5)/((4*0.8*0.5*10^3)+60+15)
24 disp(n," = ")

```

---

### Scilab code Exa 3.9 maximum efficiency

```

1 //exmaple3.9
2 clc
3 disp("(P_i)=1.2 kW, (P_cu)(FL)=1.5 kW, kVA=100")
4 n=100*sqrt(1.2/1.5)
5 format(8)
6 disp(n,"i) kVA for (n_max)=kVA*sqrt((P_i)/(P_cu))=")
7 disp("ii) For n_max, (P_cu)=(P_i)=-1.2 kW")
8 disp("Therefore , %(n_max)=[(kVA for n_max)*cos(psi)
    ]/[(kVA for n_max)*cos(psi)+2(P_i)]*100 ..
    cos(psi)=1")
9 n=(89.4427*10^5)/((89.4427*10^3)+(2*1.2*10^3))
10 format(7)
11 disp(n,"%eta_max(in percentage) = ")

```

---

### Scilab code Exa 3.10 efficiency and unity power factor

```

1 //example3.10
2 clc
3 disp("20 kVA, N_max=0.98 at 15 kVA and cos(psi)=1, (
    P_i)=350 W")
4 disp("Load at n_max=kVA*sqrt(P_i/P_cu)")
5 disp("Therefore , 15=20*sqrt(350/P_cu) i.e. ")

```

```

6 p=350/((15/20)^2)
7 format(8)
8 disp(p,"P_cu(FL) [in W]=")
9 disp("i) %n at cos(psi)=0.8 lag , full load")
10 disp("%n(FL)= [VA cos(psi) *100]/[(VA cos(psi))+
      P_cu(FL))+(P_i)]=[20*10^3*(0.8)
      *100]/[(20*10^3*(0.8))+(622.222)+(350)]")
11 n=[20000*(0.8)*100]/[(20000*(0.8))+(622.222)+(350)]
12 format(7)
13 disp(n,"= ")
14 disp("ii) %n at cos(psi)=1 , full load")
15 n=(20000*100)/(20000+622.222+350)
16 format(8)
17 disp(n,"%n(FL)=(20*10^3*1*100)/((20*10^3*1)
      +622.222+350)=")

```

---

**Scilab code Exa 3.11** copper loss and full and half load efficiency and regulation

```

1 //Example 3.11
2 clc
3 disp("From O.C. test we can write,")
4 disp("  Wo = P1 = 50 W = Iron loss")
5 disp("From S.C. test we can find the parameters of
      equivalent circuit. Now S.C. test is conducted on
      H.V. side i.e. meters are on H.V. side which is
      transformer secondary. Hence parameters from S.C.
      test results will be referred to secondary.")
6 disp("V_sc = 15 V,  I_sc = 30 A,  W_sc = 100 W")
7 r2e=10/(30^2)
8 format(6)
9 disp(r2e,"Therefore ,  R_2e (in ohm)= W_sc / (I_sc)^2
      =")
10 z1e=15/30
11 format(4)

```

```

12 disp(z1e," Z_1e(in ohm) = V_sc / I_sc =")
13 x2e=sqrt((0.5^2)-(0.111^2))
14 format(7)
15 disp(x2e," Therefore , X_2e(in ohm) = sqrt(Z_2e^2 -
    R_2e^2) =")
16 disp("(i) Copper loss on full load")
17 i2=(10^4)/250
18 format(3)
19 disp(i2," (I2)F.L (in A)= VA rating / V2 =")
20 disp("In short circuit test , I_sc = 30 A and not
    equal to full load value 40 A")
21 disp("Hence W_sc does not give copper loss on full
    load.")
22 disp(" Therefore , W_sc = P_cu at 30 A = 100 W")
23 disp("Now P_cu directly propotional to I^2")
24 disp(" Therefore , P_cu at 30 A / P_cu at 40 A =
    (30/40)^2")
25 disp(" Therefore , 100 / P_cu at 40 A = 900/1600")
26 pcu=(1600*100)/900
27 format(7)
28 disp(pcu," Therefore , P_cu at 40 A (in W)= ")
29 disp(" Therefore , (P_cu)F.L = 177.78 W")
30 disp("(ii) Full load eta , cos(phi2) = 0.8")
31 disp("%eta on full load = V2(I2)F.L.*cos(phi2)*100 /
    V2(I2)F.L.*cos(phi2)+Pi+(P_cu)F.L")
32 n=(250*40*0.8*100)/((250*40*0.8)+50+177.78)
33 format(6)
34 disp(n,"= (250*40*0.8*100)/((250*40*0.8)+50+177.78)
    = ")
35 disp(" iii) Half load eta , cos(phi_2)=0.8")
36 disp("n=0.5 as half load , (I2)[H.L.]=40/2 =20 A")
37 disp(" Therefore , %eta on full load = V2(I2)H.L.*cos(
    phi2)*100 / V2(I2)H.L.*cos(phi2)+Pi+(n^2)(P_cu)F.
    L")
38 disp("= n*(VA rating)*cos(phi2)*100 / n*(VA rating)*
    cos(phi2)+Pi+(P_cu)F.L")
39 disp("= 0.5*10*10^3*0.8*100/(0.5*10*10^3*0.8)
    +50+(0.5^2)*177.78")

```

```

40 n=(0.5*10*1000*0.8*100)/((0.5*0.8*10^4)
    +50+(100.78*(0.5^2)))
41 disp(n," = ")
42 disp("iv) Regulation at full load , cos(phi)=0.9
    leading")
43 disp("%R = (I2)F.L.*(R_2e)*cos(phi)-(I2)F.L.*(X_2e)*
    sin(phi)*100/V2")
44 r=((40*0.111*0.9)-(40*0.4875*0.4358))*100/250
45 format(7)
46 disp(r," = (40*0.111*0.9)-(40*0.4875*0.4358)*100/250
    =")

```

---

### Scilab code Exa 3.12 voltage and power factor

```

1 //example3.12
2 clc
3 disp("R1=0.9 ohm, R2=0.03 ohm, X1=5 ohm, X2=0.13 ohm
    ")
4 disp("K=N2/N1=1/6 as N1:N2 is 6:1")
5 r=0.03+(0.9*(1/6)^2)
6 format(6)
7 disp(r,"Therefore , (R_2e) [in ohm]=R2+R1''=R2+(K^2)*
    R1=0.03+(1/6)^2*0.9=")
8 x=0.13+(5*(1/6)^2)
9 format(8)
10 disp(x,"(X_2e) [in ohm]=X2+X1''=X2+(K^2)*X1
    =0.13+(5*(1/6)^2)=")
11 disp("I_sc = 200 A")
12 disp("(Z_2e)=(V_sc)/(I_sc) i.e. sqrt((R_2e^2)+(
    X_2e^2))=(V_sc)/200")
13 v=200*0.27444
14 disp(v,"V_sc(in V)=200*0.27444=")
15 v=54.8895*6
16 disp(v,"i) V1(in V)=(V_sc)/K=54.8895/(1/6)=")
17 disp("(W_sc)=(V_sc)*(I_sc)*cos(phi_sc) and (")

```



```

    W_sc)=(I_sc ^ 2)*(R_2e)")
18 disp(" Therefore , (200^2)*0.055 = 54.8895*200*cos(
    phi_sc)")
19 s=((0.055*200)/(54.8895))
20 format(4)
21 disp(s," Therefore , cos(phi_sc) [lagging]=")

```

---

### Scilab code Exa 3.13 all day efficiency

```

1 //exmample3.13
2 clc
3 disp(" Given values are , P_i=2.5 kW, (P_cu)F.L. = 3.5
    kW, 400 kVA")
4 disp(" Iron losses are constant for 24 hours. So
    energy spent due to iron lossses for 24 hours is ,
    ")
5 p=2.5*24
6 disp(p," P_i(in kWh)=2.5*24 hours=")
7 disp(" Total energy output in a day from given load
    cycle is ,")
8 e=(300*6)+(200*10)+(100*4)
9 disp(e," Energy output (in kWh)= (300*6 hours)
    +(200*10 hours)+(100*4 hours)=")
10 disp(" To calculate energy spent due to copper loass ,
    ")
11 disp(" i) Load 1 of 300 kW at cos(phi)=0.8")
12 k=300/0.8
13 disp(k," Therefore , kVA supplied = kW/cos(phi)
    =300/0.8=")
14 n=375/400
15 format(7)
16 disp(n," Therefore , n=(load kVA)/(kVA rating)
    =375/400=")
17 disp(" Copper losses are proportional to square of
    kVA ratio i.e. n^2")

```

```

18 l=3.5*(0.9375)^2
19 format(6)
20 disp(1," Therefore , Load 1 P_cu = n^2*(P_cu)F.L.
      =(0.9375)^2*3.5=")
21 e=3.076*6
22 format(7)
23 disp(e," Energy spent (in kWh)=3.076*6 hours=")
24 disp(" ii) Load 2 of 200 kW at cos(phi)=0.7")
25 k=200/0.7
26 format(9)
27 disp(k," Therefore , kVA supplied=(kW)/cos(phi)
      =200/0.7=")
28 n=285.7142/400
29 format(7)
30 disp(n," n=(Load kVA)/(kVA rating)=")
31 p=3.5*(0.7142^2)
32 disp(p," Therefore , Load 2 P_cu (in kW)= n^2*(P_cu)F.L
      .=(0.7142^2)*3.5=")
33 p=1.7857*10
34 disp(p," Therefore , Energy spent (in kWh)= 1.7857*10 =
      ")
35 disp(" iii) Load 3 of 100 kW at cos(phi)=0.9")
36 k=100/0.9
37 format(8)
38 disp(k," Therefore , kVA supplied=kW/cos(phi)=100/0.9=
      ")
39 n=111.111/400
40 format(7)
41 disp(n," Therefore , n=111.111/400=")
42 p=3.5*(0.2778^2)
43 disp(p," Therefore , Load 3 P_cu (in kW)= n^2*(P_cu)F.L
      .=(0.2778^2)*3.5=")
44 e=0.2701*4
45 disp(e," Therefore , Energy spent (in kWh)=0.2701*4=")
46 disp(" iv) No load hence negligible copper losses.")
47 t=60+18.457+17.857+1.0804
48 format(8)
49 disp(t," Therefore , Total energy spent = Energy spent

```

```

        due to [Iron losses + Total copper loss]=
        60+18.457+17.857+1.0804 = ")
50 disp("and Total output = 4200 kWh")
51 disp("Therefore , All day eta= (Total output for 24
        hours)/(Total output for 24 hours+Total energy
        spent for 24 hours)")
52 n=420000/(4200+97.3944)
53 format(6)
54 disp(n,"= 4200*100/(4200+97.3944) = ")

```

---

### Scilab code Exa 3.14 copper loss and efficiency

```

1 //example3.14
2 clc
3 disp("eta % =98% ,S= 200 kVA, cos(phi)=0.8, Iron
        loss=200 W")
4 disp("Therefore , eta % = (200*10^3 *0.8*100)
        /(200*10^3 *0.8+2000+copper loss)")
5 disp("0.98[200*10^3 *0.8+2000+copper loss]=200*10^3
        *0.8")
6 c=((200*800)/0.98) -((200*800) -2000)
7 format(9)
8 disp(c,"i)Copper loss at full load(in watt)=")
9 disp("ii)Half load copper loss(in watt) = (n^2)*
        W_cu)full load      where n=0.5 as half load")
10 x=(0.5^2)*1265.306
11 format(8)
12 disp(x,"=(0.5^2)*1265.306 =")
13 disp("Efficiency at half load = (100*10^3 *0.8*100)
        /(100*10^-3 *0.8+2000+316.326)")
14 n=(100*800*100)/((0.8*100000)+2000+316.326)
15 format(7)
16 disp(n,"eta % = ")

```

---

### Scilab code Exa 3.15 iron and copper loss

```
1 //example3.15
2 clc
3 x=250*800
4 disp(x,"a)The output power at full load(in watt)=")
5 disp("The input power at full load =(200*10^3)
    /0.98135")
6 disp("The total loss = Input-Output")
7 t=((200*10^3)/0.98135)-200000
8 format(8)
9 disp(t,"= ")
10 disp("Therefore , P_i + P_c = 3800.88          (i)")
11 disp("where      P_i= Iron loss  ,P_c = Full load
    copper loss")
12 p=125*800
13 disp(p,"The power output at half load=125*10^3 *0.8="
    ")
14 disp("The power input at half load = (100*10^3)
    /0.97751")
15 x=((100*10^3)/0.9775)
16 disp(x,"Total loss = (100*10^3)/0.9775 - 100*10^3 ="
    )
17 disp("(P_i)+ (0.5^2)*(P_c) = 2300.74")
18 disp("(P_i)+ (0.25)*(P_c) = 2300.74          (ii)")
19 disp("From equations (i) and (ii),")
20 disp("0.75*(P_i)=3800.88-2300.74")
21 p=(3800.88-2300.74)/0.75
22 disp(p,"Therefore , P_i(in watt)=")
23 z=3800.88-2000.18
24 disp(z,"P_c(in watt)=")
```

---

### Scilab code Exa 3.16 regulation

```
1 //example3.16
2 clc
3 disp("100 kVA, 1000 V/ 10000 V, P_i=1200 W, cos(phi)
      =0.8, P_cu on I2 = 6A is 500W, X_2e=10 ohm")
4 disp("For eta_max, P_cu=(P_i)=1200 W")
5 i=(100*10^3)/10000
6 disp(i,"(I_2)F.L.[in A] = VA rating/V2 = (100*10^3)
      /10000 = ")
7 disp("Therefore, P_cu on any load/(P_cu)F.L. = [I2
      load/I2 F.L]^2 ... As (P_cu) directly
      proportional I^2")
8 disp("Therefore, 500/(P_cu)F.L. = (6/10)^2")
9 p=500*(10/6)^2
10 format(8)
11 disp(p,"Therefore, (P_cu)F.L.[in W] = ")
12 k=100*sqrt(1200/1388.88)
13 disp(k,"kVA at eta_max = (kVA rating)*sqrt(P_i/(P_cu)
      F.L) = 100*sqrt(1200/1388.88) =")
14 disp("Therefore, % eta_max = (kVA for n_max cos(phi)
      *100)/(kVA for n_max cos(phi)+2P_i)")
15 n=(92951.8*0.8*100)/((92951.8*0.8)+(2*1200))
16 disp(n,"= (92951.8*0.8*100)/((92951.8*0.8)+(2*1200))
      = ")
17 i=10*sqrt(1200/1388.88)
18 format(7)
19 disp(i,"(I_2m) at eta_max [in A]= (I_2)F.L. * sqrt(
      P_i/(P_cu)F.L.) = ")
20 disp("Therefore, (P_cu) at eta_max = P_i = (I_2m)^2
      * R_2e")
21 disp("Therefore, 1200 = (9.2951^2)*R_2e")
22 r=1200/(9.2951^2)
23 disp(r,"Therefore, R_2e[in ohm] = ")
24 disp("% R = (I_2m) [R_2e cos(phi)+(X_2e) sin(phi)
      *100]/V2")
25 po=(9.2951*((13.889*0.8)+(10*10*0.6)))/100
26 format(5)
```

```
27 disp(po,"= (9.2951*((13.889*0.8)+(10*10*0.6))*100)
    /10000 = ") //answer in text book is wrong
```

---

### Scilab code Exa 3.17 efficiencies

```
1 //exmaple3.17
2 clc
3 disp("5 kVA, 2300/230 V, P_i=40 W, (P_cu)F.L. =112 W
    , cos(phi)=0.8")
4 disp("Sr.      kVA      n=Fraction of full load
        New P_cu=      %eta=n[Total VA] cos(phi)/
        n[Total VA] cos(phi)+P_i+New P_cu *100")
5 disp("No.      output      =Actual kVA/total kVA      n
        ^2 P_cu(F.L.) ")
6 disp("1      1.25      0.25
        95.51%")
7 disp("2      2.5      0.5
        96.711%")
8 disp("3      3.75      0.75
        96.668%")
9 disp("4      5      1
        96.339%")
10 disp("5      6.25      1.25
        95.877%")
11 disp("6      7.5      1.5
        95.359%")
12 disp("")
13 disp("The efficiency against kVA output curve is
        shown in the fig. 3.28")
```

---

**Scilab code Exa 3.18** load impedance and maximum flux

```
1 //example3.18
2 clc
3 disp(" 50 kVA, V1=2400 V, V2=240 V, N2=23")
4 k=1/10
5 disp("K=N2/N1=1/10=")
6 i=(50*10^3)/240
7 format(8)
8 disp(i,"(I_2)F.L. = VA/V2 = (50*10^3)/240 =")
9 r=240/208.333
10 disp(r,"R_L (in ohm)=V2/(I_2)F.L. = 240/208.333=")
11 disp("From the e.m.f equation,")
12 disp("240 = 4.44*50*phi*23")
13 p=240/(4.44*50*23)
14 format(6)
15 disp(p,"Therefore , phi_m(in Wb)=")
```

---

**Scilab code Exa 3.19** number of primary and secondary turns

```
1 //example3.19
2 clc
3 disp("E1=2300 V, E2=230 V, f=50 Hz, B_m=1.1 Wb/m^2 ,
      A=0.05 m^2")
4 disp("B_m=(phi_m)/A      i.e      1.1=(phi_m)/0.05")
5 p=1.1*0.05
6 format(6)
7 disp(p,"Therefore , (phi_m)[in Wb]=")
8 disp("E1=4.44(phi_m)*f*N1      i.e.
      2300=4.44*0.055*50*N1")
9 n=2300/(4.44*0.055*50)
```

```

10 format(7)
11 disp(n," Therefore , N1 = ")
12 disp(" E2=4.44(phi_m)*f*N2    i.e.
        230=4.44*0.055*50*N2")
13 n=230/(4.44*0.055*50)
14 disp(n," Therefore , N2 = ")

```

---

### Scilab code Exa 3.20 maximum efficiency

```

1 //example3.20
2 clc
3 disp(" 150 kVA, P_i=1.4 kW, P_cu(FL)=1.6 kW")
4 k=150*sqrt(1.4/1.6)
5 format(9)
6 disp(k," a) kVA for eta_max = kVA*sqrt(P_i/P_cu(FL))=
        ")
7 disp(" For maximum efficiency , P_cu=P_i=1.4kW and cos(
        phi)=1")
8 disp(" Therefore , %eta_max=(VA for eta_max *cos(phi))
        /(VA for eta_max*cos(phi)+2P_i *100")
9 n=(140.3121*1000*100)/(140312.1+(2*1.4*1000))
10 format(7)
11 disp(n," = (140.3121*1000*100)/(140312.1+(2*1.4*1000)
        ) = ")
12 disp(" b) At half load , n=0.5, cos(phi)=0.8")
13 disp(" Therefore , %eta_HL = (n*VA*cos(phi)*100)/(n*VA
        *cos(phi)+P_i+[n^2 *P_cu(FL)])")
14 n=(0.5*150*1000*0.8*100)/((0.5*150*1000*0.8)
        +(1.4*10^3)+(1.6*1000*0.5^2))
15 disp(n," = (0.5*150*1000*0.8*100)/((0.5*150*1000*0.8)
        +(1.4*10^3)+(1.6*1000*0.5^2)) = ")

```

---

### Scilab code Exa 3.21 area of core



```

1 //exmaple3.21
2 clc
3 disp("E1=1900 V, E2=240 V, f=50Hz, B_m=1.5 Wb/m^2,
      emf/turn = E1/N1 = E2/N2")
4 disp(" Therefore , 1.5=1900/N1=240/N2")
5 n=1900/1.5
6 format(8)
7 disp(n," Therefore , N1=")
8 n=240/1.5
9 disp(n," and , N2=")
10 disp("E1=4.44*(phi_m)*f*N1 i.e. 1900=4.44(phi_m)
      *50*1267")
11 p=1900/(4.44*50*1267)
12 format(9)
13 disp(p," Therefore , (phi_m)[in Wb]=")
14 disp("(B_m)=(phi_m)/A i.e. 1.5=(6.7567*10^-3)/A")
15 a=(6.7567*10^-3)/1.5
16 format(10)
17 disp(a," Therefore , A(in m^2)=")
18 i=10000/240
19 format(7)
20 disp(i," I2(in A)=Output VA/E2 = (10*10^3)/240 = ")

```

---

### Scilab code Exa 3.22 efficiency

```

1 //example3.22
2 clc
3 disp("%eta_FL = 96%, cos(phi)=0.8, %eta_HL =97.2%,
      cos(phi)=1")
4 disp("%eta_FL=(VA*cos(phi))/(VA*cos(phi)+P_i+P_cu(
      FL))*100 i.e. 0.96=((259*10^3)*0.8)
      /((250*10^3)*0.8+P_i+P_cu(FL))")
5 disp(" Therefore , P_i+P_cu(FL)=8333.333 ... (1)")
6 disp("%eta_HL=(n*VA*cos(phi))/(n*VA*cos(phi)+P_i+(n
      ^2)*P_cu(FL))*100 ... n=0.5 for half load")

```

```

7 disp(" Therefore , 97.2=(0.5*250*(10^3)*1)
      /(0.5*250*(10^3)*1+P_i+(0.5^2)*P_cu(FL)) *100")
8 disp(" Therefore , P_i+(0.5^2)*P_cu(FL)=3600.823
      ..(2)")
9 disp(" Solving equations (1) and (2) ,")
10 disp(" 3600.823 -(0.5^2)*P_cu(FL)+P_cu(FL)=8333.333")
11 disp(" 0.75*(P_cu)FL=8333.333 -3600.823")
12 p=(8333.333-3600.823)/0.75
13 format(9)
14 disp(p," P_cu(FL) [in W]=")
15 p=8333.333-6310.013
16 format(9)
17 disp(p," P_i(in W)=")
18 disp(" At 75% of full load , n=0.75 and cos(phi)=0.8")
19 disp(" Therefore , %eta=(n*VA*cos(phi))/(n*VA*cos(phi)
      +P_i+(n^2)*P_cu(FL)) *100")
20 disp(" =(0.75*2508(10^3)*0.8)/(0.75*250*(10^3)
      *0.8+2023.319+(0.75^2)*6310.013)) *100")
21 n=(0.75*250*(10^3)*0.8*100)/((0.75*250*(10^3)*0.8)
      +2023.319+((0.75^2)*6310.013))
22 format(8)
23 disp(n,"= ")

```

---

**Scilab code Exa 3.23** turns ratio and magnetizing and working component and iron loss

```

1 //example3.23
2 clc
3 disp(" V_0=220 V, I_0=0.5 A, W_0=30 W, R1=0.6ohm")
4 disp(" W_0=(V_0)*(I_0)*cos(phi_0) i.e. cos(
      phi_0)=30/(220*0.5)")
5 c=30/(220*0.5)
6 format(8)
7 disp(c," Therefore , cos(phi_0)=")
8 p=acosh(0.27272)

```

```

9 disp(p," i.e. (phi_0) [in degree]=")
10 k=110/220
11 disp(k," a) K=Turns ratio=Secondary voltage/Primary
    voltage=110/220=")
12 i=0.5*0.27272
13 disp(i," b) I_m (in A)=(I_0)*cos(phi_0)=0.5*0.27272=")
14 i=0.5*sind(74.1733)
15 format(6)
16 disp(i," I_c (in A)=(I_0)*sin(phi_0)=0.5*sin(74.1733)=
    ")
17 p=30-((0.5^2)*0.6)
18 disp(p," P_i (in W)=Iron loss=(W_0)-No load copper
    loss=(W_0)-(I_0^2)*R1=")

```

---

### Scilab code Exa 3.24 efficiency and load

```

1 //example3.24
2 clc
3 disp(" 50 kVA, P_i=500 W, P_cu(FL)=600 W")
4 disp(" a) cos(phi)=1, Full load")
5 n=(50*(10^3)*1*100)/((50*10^3)+500+600)
6 format(7)
7 disp(" Therefore , %eta=(VA*cos(phi))/(VA*cos(phi)+P_i
    +P_cu(FL)) *100=(50*(10^3)*1*100)/((50*10^3)
    *1+500+600)=")
8 k=50*sqrt(500/600)
9 format(8)
10 disp(k," b) kVA at eta_max= kVA*sqrt(P_i/P_cu(FL))
    =50*sqrt(500/600)=")
11 i=(50*10^3)/400
12 disp(i," I_2 (FL) [in A]=VA/V2=(50*10^3)/400=")
13 i=125*sqrt(500/600)
14 format(9)
15 disp(i," I_2m (in A)=I_2 (FL)*sqrt(P_i/P_cu(FL))=")

```

---

**Scilab code Exa 3.25** flux density and transformation ratio and voltage induced and

```

1 //example3.25
2 clc
3 disp("N1=400, N2=1000, A=60 cm^2, f=50 Hz, E1=520 V"
      )
4 disp("a) E1=4.44*(phi_m)*f*N1   i.e.   520=4.44*(
      phi_m)*50*400")
5 p=520/(4.44*50*400)
6 format(9)
7 disp(p,"Therefore, (phi_m)[in Wb]= ")
8 b=(5.8558*10^-3)/(60*10^-4)
9 format(7)
10 disp(b,"Therefore, (B_m)[in Wb/m^2]=(phi_m)/A= ")
11 k=1000/400
12 disp(k,"b) K=N2/N1=1000/400= ")
13 disp("c) N2/N1=E2/E1   i.e.   1000/400=E2/520")
14 e=(1000*520)/400
15 disp(e,"Therefore, E2(in V)=")
16 e=520/400
17 disp(e,"d) E1/turns=E1/N1=520/400=")
18 e=1300/1000
19 disp(e,"E2/turns=E2/N2=1300/1000=")

```

---

**Scilab code Exa 3.26** voltage regulation and efficiency

```

1 //example3.26
2 clc
3 disp("From O.C. test, P_i=Iron losses=75 W")
4 disp("From S.C. test, V_sc=9.5 V, I_sc=20A, W_sc=110
      W")

```

```

5 disp("The meters are on H.V. side i.e. primary hence
      ,")
6 z=9.5/20
7 format(6)
8 disp(z,"Z_1e(in ohm)=(V_sc)/(I_sc)=")
9 r=110/(20^2)
10 disp(r,"R_1e(in ohm)=(W_sc)/(I_sc)^2=")
11 x=sqrt((0.475^2)-(0.275^2))
12 format(7)
13 disp(x,"Therefore, (X_1e)[in ohm]=sqrt((Z_1e^2)-(
      R_1e^2))=")
14 i=(8*10^3)/400
15 disp(i,"I1(FL)[in A]=I_sc=VA/V1=(8*10^3)/400=")
16 disp("Therefore, (W_sc)[in W]=(P_cu)(FL)=110 W
      ... Copper losses on full load")
17 disp("For cos(phi)=0.8, sin(phi)=0.6")
18 disp("Therefore, %R = I1(FL)*100*[R_1e*cos(phi)+X_1e
      *sin(phi)]")
19 r=(20*100*((0.275*0.8)+(0.3873*0.6)))/400
20 disp(r," = 20*100*[0.275*0.8+0.3873*0.6]/400= ")
21 disp("%eta_FL= VA*cos(phi)/(VA*cos(phi)+P_i+P_cu(FL)
      )*100")
22 n=((8*10^3)*0.8*100)/((8*0.8*10^3)+75+110)
23 format(6)
24 disp(n,"= ((8*10^3)*0.8*100)/((8*0.8*10^3)+75+110)=
      ")

```

---

**Scilab code Exa 3.27** all day efficiency

```

1 //example3.27
2 clc
3 disp("Load distribution in hours is as give in the
      table.")
4 disp("P_i=Iron loss=1.6 kW, P_cu(FL)=3.02 kW")
5 disp("As iron losses are constant for 24 hours,

```

```

        energy spent due to iron losses ,")
6  p=1.6*24
7  disp(p," P_i(in kWh)=1.6*24= ")
8  e=(6*160)+(4*80)+(1*0)
9  disp(e," Energy Output(in kWh)= (6*160)+(4*80)+(1*0)
    = ")
10 disp("To calculate energy spent due to copper loss:")
11 disp("Load 1: 160 kW, cos(phi)=0.8")
12 k=160/0.8
13 disp(k," Therefore , kVA=kW/cos(phi)=160/0.8=")
14 e=3.02*6
15 disp(e," Therefore , E1(in kWh)=P_cu(FL)*hours=3.02*6=
    ")
16 disp("Load 2: 80kW, cos(phi)=1")
17 k=80/1
18 disp(k," Therefore , kVA=kW/cos(phi)=80/1=")
19 n=80/200
20 disp(n," Therefore , n=Fraction of load=(load kVA)/(
    kVA rating)=80/200=")
21 p=(0.4^2)*3.02
22 format(7)
23 disp(p," Therefore , P_cu(in kW)=(n^2)*P_cu(FL)
    =(0.4^2)*3.02=")
24 e=0.4832*4
25 disp(e," Therefore , E2(in kWh)=P_cu*hours=0.4832*4=")
26 t=38.4+18.12+1.9328
27 format(8)
28 disp(t," Total energy spent(in kWh)=P_i+E1+E2
    =38.4+18.12+1.9328= ")
29 n=(1280*100)/(1280+58.4528)
30 disp(n," Therefore , All day eta=(total energy output
    in 24 hours*100)/(total energy output for 24
    hours+total energy spent)=(1280*100)
    /(1280+58.4528)=")

```

---

# Chapter 4

## Alternators

Scilab code Exa 4.1 calculate distribution factor

```
1 //Example 4.1
2 clc
3 n=120/8
4 format(3)
5 disp(n,"n = slots/pole =")
6 m=15/3
7 disp(m,"m = slots/pole/phase = n/3 =")
8 beta=180/15
9 disp(beta,"beta(in degree) = 180/n =")
10 kd=(sind(30)/(5*sind(6)))
11 format(6)
12 disp(kd,"Therefore ,  $K_d = \frac{\sin(m \cdot \beta / 2)}{m \cdot \sin(\beta / 2)}$  =")
```

---

Scilab code Exa 4.2 calculate coil factor

```
1 //Example 4.2
2 clc
```

```

3 n=36/4
4 format(3)
5 disp(n,"n = slots/pole =")
6 beta=180/9
7 disp(beta,"beta(in degree) = 180/n =")
8 disp("Now coil is shorted by 1 slot i.e. by 20 to
      full pitch distance.")
9 disp("Therefore ,  alpha = Angle of short pitch = 20"
      )
10 kc=cosd(10)
11 format(7)
12 disp(kc,"Therefore ,  K_c = cos(alpha/2) =")

```

---

#### Scilab code Exa 4.3 find induced emf

```

1 //Example 4.3
2 clc
3 disp("Ns = 250 r.p.m,  f = 50 Hz")
4 disp("Ns = 120f / P")
5 p=(120*50)/250
6 disp(p,"Therefore ,  P = ")
7 n=216/24
8 format(3)
9 disp(n,"n = slots/pole =")
10 m=9/3
11 disp(m,"m = n/3 =")
12 beta=180/9
13 disp(beta,"beta(in degree) = 180/n =")
14 kd=(sind(30)/(3*sind(10)))
15 format(6)
16 disp(kd,"Therefore ,  K_d = sin(m*beta/2) / m*sin(
      beta/2) =")
17 disp("K_c = 1 as full pitch coils.")
18 z=216*5
19 format(8)

```



```

20 disp(z,"Total number of conductors Z = ")
21 zph=1080/3
22 disp(zph,"Therefore , Z_ph = Z/3 =")
23 tph=360/2
24 disp(tph,"Therefore , T_ph = Z_ph/2 = ...
      2 conductors constitute 1 turn")
25 eph=4.44*0.9597*30*50*180*10^-3
26 format(8)
27 disp(eph,"E_ph(in V) = 4.44*Kc*Kd*f*phi*T_ph =")
28 e1=sqrt(3)*1150.48
29 disp(e1,"E_line(in V) = sqrt(3)*E_ph = ...
      star connection")

```

---

#### Scilab code Exa 4.4 find poles and flux

```

1 //Example 4.4
2 clc
3 disp("E_line = 4000 V, f = 50 Hz, N_s = 750 r.p.m,
      m = 3, K_c = 1")
4 eph=4000/sqrt(3)
5 format(9)
6 disp(eph,"E_ph(in V) = E_line/sqrt(3) =")
7 p=(120*50)/750
8 disp("(i) N_s = 120f / P")
9 disp(p,"Therefore , P =")
10 disp("(ii) n = slots/pole = m*3 = 9")
11 b=180/9
12 disp(b,"beta = 180/n =")
13 kd=sind(30)/(3*sind(10))
14 format(7)
15 disp(kd,"Therefore , K_d = sin(m*beta/2) / m*sin(
      beta/2) =")
16 ns=9*8
17 disp(ns,"Number of slots = n * P =")
18 z=72*12

```

```

19 disp(z,"Z = Slots * conductors/slots =")
20 zp=864/3
21 disp(zp,"Therefore , Z_ph = Z/3 =")
22 tp=288/2
23 disp(tp,"Therefore , T_ph = Z_ph/2 =")
24 phi=2309.401/(4.44*0.9598*50*144)
25 format(8)
26 disp("Therefore , E_ph = 4.44*K_c*K_d*phi*f*T_ph")
27 disp(phi,"Therefore , phi(in Wb) =
    ... flux per pole")

```

---

#### Scilab code Exa 4.5 calculate emf

```

1 //Example 4.5
2 clc
3 disp("P = 100 kW, cos(phi) = 0.8 lagging")
4 disp("V_L = 11 kV, R_a = 0.4 ohm, X_s = 3 ohm")
5 disp("For three phase load, P = sqrt(3)*V_L*I_L*cos
    (phi)")
6 il=(1000*10^3)/(sqrt(3)*11*0.8*10^3)
7 format(5)
8 disp(il,"Therefore , I_L(in A) =")
9 disp("Now I_L = I_a as for star connected
    alternator I_L = I_ph")
10 disp("Therefore , I_laph = 65.6 A ... full
    load per phase armature current")
11 disp("For lagging p.f. loads,")
12 disp("(E_ph)^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*X_s)^2")
13 vp=(11*10^3)/sqrt(3)
14 format(9)
15 disp(vp,"Now V_ph = V_L / sqrt(3) =
    ... as star connected")
16 eph=(((6350.853*0.8)+(65.6*0.4))^2)+(((6350.853*0.6)
    +(65.6*3))^2)

```

```

17 p=sqrt(eph)
18 format(8)
19 disp(p," Therefore ,   E_ph(in V) = ")
20 e1=(sqrt(3)*6491.47)*10^-3
21 format(6)
22 disp(e1," Therefore ,   E_line(in kV) =")
23 regu=((6491.47-6350.853)/6350.853)*100
24 disp(regu,"and   %Regulation(in percentage) = (E_ph-
      V_ph / V_ph)*100 =")
25 disp("For lagging p.f. loads , regulation is always
      positive.")

```

---

**Scilab code Exa 4.6** calculate lagging

```

1 //Example 4.6
2 clc
3 disp("kVA = 1200,   V_L = 6600 V,   R_a = 0.25 ohm,
      X_s = 5 ohm")
4 disp("Now   kVA = sqrt(3)*V_L*I_L*10^-3")
5 il=1200/(sqrt(3)*6600*10^-3)
6 format(7)
7 disp(il," Therefore ,   I_L(in A) =")
8 disp(" Therefore ,   I_laph = 104.97 A           ... as
      star connected.")
9 disp("This is its full load current")
10 vph=6600/sqrt(3)
11 format(9)
12 disp(vph,"   V_ph(in V) = V_L/3 =")
13 disp("(i) For 0.8 lagging p.f. load")
14 disp("(E_ph)^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
      sin(phi)+I_a*X_s)^2")
15 eph=((((3810.512*0.8)+(104.97*0.25))^2)
      +(((3810.512*0.6)+(104.97*5))^2)
16 p=sqrt(eph)
17 format(8)

```

```

18 disp(p," Therefore ,  E_ph(in V) = ")
19 regu=((4166.06-3810.512)/3810.512)*100
20 format(5)
21 disp(regu," Therefore ,  %Regulation(in percentage) = (
    E_ph-V_ph / V_ph)*100 =")
22 disp("(ii) For 0.8 leading p.f. load")
23 disp("(E_ph)^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*X_s)^2")
24 eph=(((3810.512*0.8)+(104.97*0.25))^2)
    +(((3810.512*0.6)-(104.97*5))^2)
25 p=sqrt(eph)
26 format(8)
27 disp(p," Therefore ,  E_ph(in V) = ")
28 regu=((3543.47-3810.512)/3810.512)*100
29 format(5)
30 disp(regu," Therefore ,  %Regulation(in percentage) = (
    E_ph-V_ph / V_ph)*100 =")
31 disp("The regulation is negative for leading p.f.
    loads")

```

---

#### Scilab code Exa 4.7 calculate full load

```

1 //Example 4.7
2 clc
3 disp("V_L = 866 V,  kVA = 100")
4 disp(" Therefore ,  kVA = sqrt(3)*V_L*I_L*10^-3")
5 il=100/(sqrt(3)*866*10^-3)
6 format(6)
7 disp(il," Therefore ,  I_L(in A) =")
8 disp(" Therefore ,  I_aph F.L. = I_L = 66.67 A
    ... as star connected alternator")
9 disp("V_ph = Rated terminal voltage per phase = V_L
    /3")
10 vp=866/sqrt(3)
11 disp(vp," Therefore ,  V_ph(in V) =")

```

```

12 disp("For calculation of Z_s on full load, it is
    necessary to plot O.C.C. and S.C.C. to the scale"
    )
13 disp("Note : If for same value of I_f, both I_ssc
    and V_oc can be obtained from the table itself,
    graph need not be plotted. In some problems, the
    values of V_oc and I_ssc for same I_f are
    directly given, in that case too, the graph need
    not be plotted.")
14 disp("In this problem, I_ssc = 25 A for I_f = 1 A")
15 disp("But we want to calculate Z_s for I_ssc = its
    full load value which is 66.67 A. So graph is
    required to be plotted.")
16 disp("For plotting O.C.C. the lines values of open
    circuit voltage are converted to phase by
    dividing each value by sqrt(3)")
17 disp("From S.C.C.")
18 disp("For I_scc = 66.67 A, I_f = 2.4 A")
19 disp("From O.C.C.")
20 disp("For I_f = 2.4 A, (V_oc)_ph = 240 V")
21 disp("From the graph, Z_s for full load is,")
22 disp("Z_s = (V_oc)_ph / (I_scc)_ph |for same
    excitation")
23 zs=240/66.67
24 format(4)
25 disp(zs,"Therefore, Z_s(in ohm/phase) =")
26 disp("R_a = 0.15 ohm/phase")
27 xs=sqrt((3.6^2)-(0.15^2))
28 format(6)
29 disp(xs,"Therefore, X_s(in ohm/phase) = sqrt(Z_s^2
    - R_a^2) =")
30 disp("V_ph F.L = 500 V")
31 disp("cos(phi) = 0.8")
32 disp("Therefore, sin(phi) = 0.6 lagging p.f.")
33 disp("So E_ph for full load, 0.8 lagging p.f.
    condition can be calculated as,")
34 disp("(E_ph)^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*X_s)^2")

```

```

35 eph=(((500*0.8)+(66.67*0.15))^2)+(((500*0.6)
    +(66.67*3.597))^2)
36 p=sqrt(eph)
37 format(7)
38 disp(p,"Therefore , E_ph(in V) = ")
39 regu=((677.86-500)/500)*100
40 format(6)
41 disp(regu,"Therefore , %Regulation(in percentage) = (
    E_ph-V_ph / V_ph)*100 =")

```

---

#### Scilab code Exa 4.8 find current

```

1 //Example 4.8
2 clc
3 disp("V_L = 230 V, R_a between lines = 1.8 ohm")
4 disp("(V_oc)_line = 230 V, I_scc = 12.5 A for same
    I_f = 0.38 A")
5 disp("The value of open circuit e.m.f is always line
    value unless and until specifically mentioned to
    be a phase value")
6 disp("Therefore , Z_s = (V_oc)_ph / (I_scc)_ph | for
    same I_f")
7 voc=230/sqrt(3)
8 format(7)
9 disp(voc," (V_oc)_ph(in V) =")
10 zs=132.79/12.5
11 disp(zs,"Therefore , Z_s(in ohm/phase) =")
12 disp("R_a between lines = 1.8 ohm")
13 disp("For star connection , R_a between the terminals
    is 2 R_a per ph")
14 disp("Therefore , 2R_a per ph = 1.8")
15 disp("Therefore , R_a per ph = 0.9 ohm")
16 xs=sqrt((10.623^2)-(0.9^2))
17 format(7)
18 disp(xs,"Therefore , X_s(in ohm/phase) = sqrt(Z_s^2

```

```

    - R_a^2) =")
19 disp("Now regulated is asked for I_a = 10 A")
20 disp("Now : The value of Z_s is calculated for I_s
    = 12.5 A and not at I_s = 10 A. It will be
    different for I_s = 10 A. But in this problem the
    test results are not given hence it is not
    possible to sketch the graphs to determine Z_s at
    I_a = 10 A. So value of Z_s calculated is assumed
    to be same as I_a = 10 A")
21 disp("(i) For 0.8 lagging p.f.")
22 vph=230/sqrt(3)
23 format(7)
24 disp(vph,"V_ph(in V) = V_L/sqrt(3) =")
25 disp("I_a = 10 A")
26 disp("cos(phi) = 0.8      so sin(phi) = 0.6")
27 disp("(E_ph)^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*X_s)^2")
28 eph=((132.79*0.8)+(10*0.9))^2+(((132.79*0.6)
    +(10*10.585))^2)
29 p=sqrt(eph)
30 format(8)
31 disp(p,"Therefore , E_ph(in V) = ")
32 regu=((218.39-132.79)/132.79)*100
33 format(6)
34 disp(regu,"Therefore , %Regulation(in percentage) = (
    E_ph-V_ph / V_ph)*100 =")
35 disp("(ii) For 0.8 leading p.f.")
36 disp("(E_ph)^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*X_s)^2")
37 eph=((132.79*0.8)+(10*0.9))^2+(((132.79*0.6)
    -(10*10.585))^2)
38 p=sqrt(eph)
39 format(8)
40 disp(p,"Therefore , E_ph(in V) = ")
41 regu=((118.168-132.79)/132.79)*100
42 format(6)
43 disp(regu,"Therefore , %Regulation(in percentage) = (
    E_ph-V_ph / V_ph)*100 =")

```

---

**Scilab code Exa 4.9** find armature conductors

```
1 //Example 4.9
2 clc
3 disp("P = 10, N_a = 600 r.p.m, slots = 90")
4 disp("phi = 16 mWb, E_line = 11 kW")
5 f=6000/120
6 format(3)
7 disp("N_s = 120f / P")
8 disp(f,"Therefore, f(in Hz) =")
9 eph=(11*10^3)/sqrt(3)
10 format(9)
11 disp(eph,"For star connection, E_ph(in V) = E_line/
    sqrt(3) =")
12 disp("Now E_ph = 4.44*K_c*K_d*phi*f*T_ph")
13 disp("K_c = 1 as no information about short pitching
    is given")
14 n=90/10
15 disp(n,"n = slots/pole =")
16 m=9/3
17 disp(m,"m = slots/pole/phase = n/3 =")
18 beta=180/9
19 disp(beta,"beta = slot angle = 180/n =")
20 kd=sind(30)/(3*sind(10))
21 format(7)
22 disp(kd,"Therefore, K_d = sin(m*beta/2) / m*sin(
    beta/2) =")
23 disp("Therefore, 6350.853 =
    4.44*1*0.9598*16*10^-3*50*T_ph")
24 tph=6350.853/(4.44*1*0.9598*16*50*10^-3)
25 format(5)
26 disp(tph,"Therefore, T_ph =")
27 zph=2*1862
28 disp(zph,"Therefore, Z_ph = 2*T_ph =")
```



29 `disp("These are armature conductors per phase  
required to be connected in series.")`

---

**Scilab code Exa 4.10** calculate flux

```
1 //Exmaple 4.10
2 clc
3 disp("N_s = 250 r.p.m., f = 50 Hz")
4 disp("slots = 288, E_line = 6600 V")
5 disp("N_s = 120*f/P")
6 p=(120*50)/250
7 format(3)
8 disp(p,"Therefore, P =")
9 n=288/24
10 disp(n,"n = slots/pole =")
11 m=12/3
12 disp(m,"m = n/2 =")
13 beta=180/12
14 disp(beta,"beta = 180/n =")
15 kd=sind(30)/(4*sind(7.5))
16 format(7)
17 disp(kd,"Therefore, K_d = sin(m*beta/2) / m*sin(
    beta/2) =")
18 disp("Now coil is short pitched by 2 slots")
19 a1=2*15
20 disp(a1,"Therefore, alpha = angle of short pitch =
    2 * beta =")
21 kc=cosd(15)
22 disp(kc,"Therefore, K_c = cos(alpha/2) =")
23 disp("Each coil consists of 16 turns, i.e. in a slot
    each coil side consists of 16 conductors as
    shown in the fig.4.42 and in each slot there are
    2 coil sides. So each slot consists of 16 per
    coil side x 2 i.e. 32 conductors.")
24 disp("Therefore, conductors/slot = 32")
```

```

25 disp("Therefore , total conductors = slots x
      conductors/slot")
26 z=288*32
27 format(5)
28 disp(z,"Therefore , Z =")
29 zp=9216/3
30 disp(zp,"Therefore , Z_ph = conductors/phase =")
31 tp=3072/2
32 disp(tp,"Therefore , T_ph = Z_ph/2 =
      ... 2 conductors -> 1 turn")
33 ep=6600/sqrt(3)
34 format(8)
35 disp(ep,"Now E_ph(in V) = E_line / sqrt(3) =")
36 disp("E_ph = 4.44*K_c*K_d*phi*f*T_ph")
37 phi=(3810.51/(4.44*0.9659*0.9576*50*1536))*10^3
38 format(3)
39 disp(phi,"Therefore , phi(in mWb) =")

```

---

#### Scilab code Exa 4.11 find rms vlaue

```

1 //Example 4.11
2 clc
3 disp("P = 12, N_s = 600 r.p.m")
4 f=(12*600)/120
5 format(3)
6 disp(f,"Therefore , f(in Hz) = P*N_s/120 =")
7 disp("(i) Average value of e.m.f in a conductor = 2*
      f*phi")
8 rms=1.11*2*60*0.05
9 format(5)
10 disp(rms,"Therefore , r.m.s value(in V) = 1.11*2*f*
      phi =")
11 disp("(ii) Average value of e.m.f in a turn = 4*f*
      phi")
12 disp("As 2 conductors joined properly form a turn")

```

```

13 rms=1.11*4*60*0.05
14 format(6)
15 disp(rms," Therefore , r.m.s value(in V) = 1.11*4*f*
    phi =")
16 disp("(iii) Now each slot has 10 conductors and 2
    coil sides. So,")
17 c=10/2
18 disp(c,"conductors/coil side = 10/2 =")
19 disp("Such coil sides are connected to another coil
    sides to form a coil. So in a coil there are 5
    turns as shown in fig.4.43")
20 rmss=13.32*5
21 format(5)
22 disp(rmss," Therefore , R.M.S value of e.m.f in a
    coil(in V) = R.M.S value of e.m.f/turn * Number
    of turns/coil =")
23 disp("(iv) Now total conductors Z = conductors/
    slots * Number of slots")
24 z=10*180
25 disp(z," Therefore , Z =")
26 zph=1800/3
27 disp(zph," Therefore , Z_ph = Z/3 =")
28 tph=600/2
29 disp(tph," T_ph = Z_ph/2 =")
30 n=180/12
31 disp(n," And n = slots/pole =")
32 m=15/3
33 disp(m," m = n/3 =")
34 beta=180/15
35 disp(beta," beta(in degree) =")
36 kd=sind(30)/(5*sind(6))
37 format(7)
38 disp(kd," Therefore , K_d = sin(m*beta/2) / m*sin(
    beta/2) =")
39 disp("E_ph = R.M.S value per turn*T_ph*K_d*K_c")
40 ep=13.32*300*0.9566*1
41 format(8)
42 disp(ep," Therefore , E_ph(in V) =")

```

```

43 disp(" or E_ph = 4.44*K_c*K_d*phi*f*T_ph")
44 eph=4.44*0.9566*0.05*60*300
45 format(8)
46 disp(eph," Therefore , E_ph(in V) =")

```

---

**Scilab code Exa 4.12** find induced emf

```

1 //Example 4.12
2 clc
3 disp("P = 6, f = 50 Hz, n = 12 slots/pole, 4
   conductors/slot")
4 disp("For full pitch, n = 12 slots/pole")
5 ap=60/6
6 format(4)
7 disp(ap," Actual pitch of winding(in slots) = 5/6 * n
   =")
8 ws=12-10
9 disp(ws,"so winding shorted by(in slots) =")
10 disp("Therefore, alpha = short pitch angle = 2 slot
   angle = 2*beta")
11 beta=180/12
12 disp(beta,"beta(in degree) =")
13 alp=2*15
14 disp(alp,"Therefore, alpha(in degree) = 2*beta =")
15 kc=cosd(15)
16 format(7)
17 disp(kc,"Therefore, K_c = cos(alpha/2) =")
18 m=12/3
19 disp(m,"m(in slots/pole/phase) = n/3 =")
20 kd=sind(30)/(4*sind(7.5))
21 format(8)
22 disp(kd,"Therefore, K_d = sin(m*beta/2) / m*sin(
   beta/2) =")
23 ts=12*6
24 disp(ts,"Total slots = n*P =")

```

```

25 z=72*4
26 disp(z,"Therefore , Z = total conductors =")
27 zph=288/3
28 disp(zph,"Therefore , Z_ph = Z/3 =")
29 tph=96/2
30 disp(tph,"T_ph = Z_ph/2 =")
31 disp("Therefore , E_ph = 4.44*K_c*K_d*phi*f*T_ph")
32 eph=(4.44*0.9659*0.95766*1.5*50*48)*10^-3
33 format(8)
34 disp(eph,"Therefore , E_ph(in kV) =")
35 e1=sqrt(3)*14.7852
36 disp(e1,"Therefore , E_line(in kV) = sqrt(3)*E_ph =")
    )

```

---

**Scilab code Exa 4.13** find chording factor

```

1 //Example 4.13
2 clc
3 disp("The coil span of 120 degree is shown in the
    fig.4.44")
4 disp("The angle of shorts pitch is,")
5 alp=180-120
6 format(3)
7 disp(alp,"alpha(in degree) = 180 - coil span =")
8 kc=cosd(30)
9 format(6)
10 disp("The chording factor is,")
11 disp(kc,"K_c = cos(alpha/2) =")

```

---

**Scilab code Exa 4.14** find emf

```

1 //Example 4.14
2 clc

```

```

3 disp("V_ph = 200 V, 60 kVA, R_a = 0.016 ohm, X_s =
      0.07 ohm")
4 disp("VA = V_ph*I_ph      i.e. 60*10^3 = 200*I_ph
      ... Single phase")
5 disp("Therefore, I_ph = 300 A = I_a
      ... Full load current")
6 disp("(a) cos(phi) = 1, sin(phi) = 0")
7 eph=sqrt((((200+((300*0.016)))^2)+((300*0.07)^2)))
8 disp("Therefore, E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
      + (I_a*X_a)^2")
9 format(9)
10 disp(eph,"E_ph(in V) =")
11 disp("(b) cos(phi) = 0.7 lagging, sin(phi) = 0.714"
      )
12 ephi=sqrt((((200*0.7)+(300*0.016))^2)
      +(((200*0.7141)+(300*0.07))^2)))
13 disp("Therefore, E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
      + (V_ph*sin(phi)+I_a*R_a)^2")
14 format(9)
15 disp(eph,"E_ph(in V) =")

```

---

#### Scilab code Exa 4.15 find reactance

```

1 //Example 4.15
2 clc
3 disp("V_ph = 550 V, 55 kVA, R_a = 0.2 ohm")
4 disp("I_f = 10 A, I_ssc = 200 A, V_oc = 450 V")
5 za=450/200
6 format(5)
7 disp(za,"Therefore, Z_s(in ohm) = V_oc / I_ssc |
      same I_f =")
8 xs=sqrt((2.25^2)-(0.2^2))
9 format(7)
10 disp(xs,"(a) X_s(in ohm) = sqrt(Z_a^2 - R_a^2) =")
11 iph=(55*10^3)/550

```

```

12 disp("VA = V_ph*I_ph          ...As single phase")
13 disp(iph," Therefore ,  I_ph(in A) = I_a =          ...
    Full load armature current")
14 disp("(b) cos(phi) = 0.8 lagging ,  sin(phi) = 0.6")
15 ephi=sqrt((((550*0.8)+(100*0.2))^2)+(((550*0.6)
    +(100*2.2411))^2)))
16 disp(" Therefore ,  E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
    + (V_ph*sin(phi)+I_a*R_a)^2")
17 format(9)
18 disp(eph," E_ph(in V) =")
19 r=((720.1652-550)/550)*100
20 format(6)
21 disp(r," Therefore ,  %R = (E_ph-V_ph / V_ph)*100 = ")

```

---

#### Scilab code Exa 4.16 find impedance

```

1 //Example 4.16
2 clc
3 disp("V_ph = 2200 V,  f = 50 Hz,  440 kVA,  R_a = 0.5
    ohm")
4 disp("I_laph = 200 A = I_ac ,  V_oc = 1160 V,  I_f =
    40 A")
5 za=1160/200
6 format(4)
7 disp(za," (a)  Z_s(in ohm) = V_oc/I_ssc |same I_f =")
8 xs=sqrt((5.8^2)-(0.5^2))
9 format(7)
10 disp(xs," (b)  X_s(in ohm) = sqrt(Z_a^2 - R_a^2) =")
11 disp("(c)  cos(phi) = 0.707 leading ,  sin(phi) =
    0.707")
12 ephi=sqrt((((2200*0.707)+(200*0.5))^2)
    +(((2200*0.707)-(200*5.7784))^2)))
13 disp(" Therefore ,  E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
    + (V_ph*sin(phi)-I_a*R_a)^2")
14 format(10)

```

```

15 disp(ephil,"E_ph(in V) =")
16 r=((1702.9754-2200)/2200)*100
17 format(7)
18 disp(r,"Therefore, %R(in percentage) = (E_ph-V_ph /
      V_ph)*100 = ")

```

---

#### Scilab code Exa 4.17 find voltage regulation

```

1 //Example 4.17
2 clc
3 disp("Assume star connected alternator")
4 disp("R_a+R_a = V_dc/I_dc")
5 disp("2R_a = 6/10")
6 ra=0.6/2
7 format(4)
8 disp(ra,"Therefore, R_a(in ohm/ph) =")
9 disp("V_oc(line) = 420, V_L = 1100 V, 100 kVA")
10 disp("Therefore, VA = sqrt(3)*V_L*I_L")
11 il=(100*10^3)/(sqrt(3)*1100)
12 format(8)
13 disp(il,"Therefore, I_L(in A) = I_aph =")
14 disp("Therefore, Rated armature current = 52.4864 A
      = I_ssc")
15 zs=(420/sqrt(3))/52.4864
16 format(5)
17 disp(zs,"Therefore, Z_s(in ohm/ph) = V_oc(ph) /
      I_ssc(ph) =")
18 xs=sqrt((4.62^2)-(0.3^2))
19 format(7)
20 disp(xs,"Therefore, X_s(in ohm/ph) = sqrt(Z_a^2 -
      R_a^2) =")
21 disp("For cos(phi) = 0.8 lagging, sin(phi) = 0.6")
22 disp("E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*sin
      (phi)+I_a*R_a)^2")
23 vph=1100/sqrt(3)

```



```

24 format(8)
25 disp(vph,"V_ph(in V) = V_L/sqrt(3) =")
26 ephi=sqrt((((635.085*0.8)+(52.4864*0.3))^2)
      +(((635.085*0.6)+(52.4864*4.6102))^2)))
27 format(9)
28 disp(eph,"Therefore , E_ph(in V) =")
29 r=((813.9654-635.085)/635.085)*100
30 format(8)
31 disp(r,"Therefore , %R(in percentage) = (E_ph-V_ph /
      V_ph)*100 = ")

```

---

**Scilab code Exa 4.18** find regulation

```

1 //Example 4.18
2 clc
3 disp("2R_a = 2 i.e. R_a = 1 ohm/ph")
4 disp("V_L = 3.6 kVA, MVA = 1")
5 disp("Therefore , VA = sqrt(3)*V_L*I_L")
6 il=(1*10^6)/(sqrt(3)*3.6*10^3)
7 format(8)
8 disp(il,"Therefore , I_L(in A) = I_aph = ...
      Star")
9 disp("From the test results , obtain the open circuit
      and short circuit characteristics and obtain
      V_oc for full load I_sc of 160.373 A")
10 disp("From the graph , for full load short circuit
      current of 160.37 A, I_f = 53 A and corresponding
      V_oc(line) = 2250 V")
11 zs=(2250/sqrt(3))/160.37
12 format(4)
13 disp(zs,"Therefore , Z_s(in ohm/ph) = V_ocph/I_scph
      |same I_f =")
14 xs=sqrt((8.1^2)-(1^2))
15 format(6)
16 disp(xs,"Therefore , X_s(in ohm/ph) = sqrt(Z_a^2 -

```

```

    R_a^2) =")
17 vph=(3.6*10^3)/sqrt(3)
18 format(8)
19 disp(vph,"V_ph(in V) = V_L/sqrt(3) =")
20 disp("I_aplh = 160.37 A")
21 disp("(i)  cos(phi) = 0.707 lagging ,  sin(phi) =
    0.707")
22 disp("Therefore ,  E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
    + (V_ph*sin(phi)+I_a*R_a)^2")
23 ephi=sqrt((((2078.46*0.707)+(160.37*1))^2)
    +((((2078.46*0.707)+(160.37*8.038))^2)))
24 format(10)
25 disp(ephi,"Therefore ,  E_ph(in V) =")
26 r=((3204.0356-2078.46)/2078.46)*100
27 format(6)
28 disp(r,"Therefore ,  %R(in percentage) = (E_ph-V_ph /
    V_ph)*100 = ")
29 disp("(ii)  cos(phi) = 0.8 leading ,  sin(phi) = 0.6"
    )
30 disp("Therefore ,  E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
    + (V_ph*sin(phi)-I_a*R_a)^2")
31 ephi=sqrt((((2078.46*0.8)+(160.37*1))^2)
    +((((2078.46*0.6)-(160.37*8.038))^2)))
32 format(10)
33 disp(ephi,"Substituting the values ,  E_ph(in V) =")
34 r=((1823.6271-2078.46)/2078.46)*100
35 format(6)
36 disp(r,"Therefore ,  %R(in percentage) = (E_ph-V_ph /
    V_ph)*100 = ")

```

---

#### Scilab code Exa 4.19 find regulation

```

1 //Example 4.19
2 clc
3 disp("1 MVA,  V_L = 11 kV,  R_a = 0.6 ohm")

```

```

4 disp("VA = sqrt(3)*V_L*I_L")
5 il=(10^6)/(sqrt(3)*11*10^3)
6 format(7)
7 disp(il,"Therefore , I_L(in A) = I_aph(full load) =")
8 disp("Now I_f = 40 A for I_ssc = 52.486 A. To find
Z_s, plot the O.C.C and obtain V_oc for I_f = 40
A")
9 disp("From the graph , V_oc(line) = 6600 V for I_f =
40 A")
10 zs=(6000/sqrt(3))/52.486
11 format(3)
12 disp(zs,"Therefore , Z_s(in ohm) = V_ocph/I_ascph |
same I_f =")
13 xs=sqrt((66^2)-(0.6^2))
14 format(7)
15 disp(xs,"Therefore , X_s(in ohm) = sqrt(Z_s^2 - R_a
^2) =")
16 disp("(a) cos(phi) = 0.8 lagging , sin(phi) = 0.6 ,
half load")
17 ip=0.5*52.486
18 format(7)
19 disp(ip,"At half load , I_aph(in A) = 1/2 * I_aph(FL
) =")
20 vp=(11*10^3)/sqrt(3)
21 format(9)
22 disp(vp,"V_ph(in V) = V_L/sqrt(3) =")
23 disp("E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*sin
(phi)+I_a*R_a)^2")
24 ephi=sqrt((((6350.853*0.8)+(26.243*0.6))^2)
+((((6350.853*0.6)+(26.243*65.99))^2)))
25 format(10)
26 disp(efhi,"Therefore , E_ph(in V) =")
27 r=((7529.3113-6350.853)/6350.853)*100
28 format(6)
29 disp(r,"Therefore , %R(in percentage) = (E_ph-V_ph /
V_ph)*100 = ")
30 disp("(b) cos(phi) = 0.9 leading , sin(phi) =")

```

```

    0.4358, full load so Iaph = 52.486 A")
31 disp("Eph2 = (Vph*cos(phi)+Ia*Ra)2 + (Vph*sin
    (phi)-Ia*Ra)2")
32 ephi=sqrt((((6350.853*0.9)+(52.486*0.6))2)
    +(((6350.853*0.4358)-(52.486*65.99))2))
33 format(9)
34 disp(ephi,"Therefore, Eph(in V) =")
35 r=((5789.231-6350.853)/6350.853)*100
36 format(6)
37 disp(r,"Therefore, %R(in percentage) = (Eph-Vph /
    Vph)*100 = ")

```

---

**Scilab code Exa 4.20** find voltage

```

1 //Example 4.20
2 clc
3 disp("Rs = 0.6 ohm, Xs = 6 ohm, Iaph = 180 A")
4 eph=6599/sqrt(3)
5 format(10)
6 disp(eph,"Eph(in V) = Eline/sqrt(3) =")
7 disp("(a) cos(phi) = 0.9 lagging, sin(phi) = 0.4358"
    )
8 disp("Therefore, Eph2 = (Vph*cos(phi)+Ia*Ra)2
    + (Vph*sin(phi)+Ia*Ra)2")
9 disp("Therefore, (3809.9344)2 = [Vph*0.9 +
    180*0.6]2 + [Vph*0.4358 + 180*6]2")
10 disp("Therefore, 14.5156*106 = 0.81*Vph2 +
    194.4*Vph + 11664 + 0.1899*Vph2 + 941.328*Vph
    + 1166400")
11 disp("Therefore, Vph2 + 1135.728*Vph - 13337536
    = 0")
12 disp("Therefore, Vph = 3128.08, -4263.808
    ... Neglect negative value")
13 disp("Therefore, Vph = 3128.08 V
    ... Terminal voltage")

```

```

14 r=((3809.9344-3128.08)/3128.08)*100
15 format(8)
16 disp(r,"Therefore, %R(in percentage) = (E_ph-V_ph /
      V_ph)*100 = ")
17 disp("(b) cos(phi) = 0.8 leading, sin(phi) = 0.6")
18 disp("Therefore, E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2
      + (V_ph*sin(phi)+I_a*R_a)^2")
19 disp("Therefore, (3809.9344)^2 = [V_ph*0.8 +
      180*0.6]^2 + [V_ph*0.6 + 180*6]^2")
20 disp("Therefore, 14.5156*10^6 = 0.64*V_ph^2 +
      172.8*V_ph + 11664 + 0.36*V_ph^2 - 1296*V_ph +
      1166400")
21 disp("Therefore, V_ph^2 - 1123.2*V_ph - 13337536 =
      0")
22 disp("Therefore, V_ph = 4256.5872 V ...
      Neglect negative value")
23 r=((3809.9344-4256.5872)/4256.5872)*100
24 format(7)
25 disp(r,"Therefore, %R(in percentage) = (E_ph-V_ph /
      V_ph)*100 = ")

```

---

#### Scilab code Exa 4.21 calculate regulation

```

1 //Example 4.21
2 clc
3 disp("1500 kVA, V_L = 12 kV, R_a = 2 ohm, X_s =
      10 ohm")
4 vp=(12*10^3)/sqrt(3)
5 format(10)
6 disp(vp," V_ph(in V) = ... Star")
7 disp("P_L = sqrt(3)*V_L*I_L*cos(phi)")
8 disp("(a) cos(phi) = 0.8 lagging, sin(phi) = 0.6")
9 il=(1200*10^3)/(sqrt(3)*0.8*12*10^3)
10 format(7)
11 disp(il,"Therefore, I_L(in A) = I_aph = ...")

```

```

Star")
12 disp(" E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*R_a)^2")
13 ephi=sqrt((((6928.2032*0.8)+(72.168*2))^2)
    +((((6928.2032*0.6)+(72.168*10))^2)))
14 format(9)
15 disp(ephi," Therefore , E_ph(in V) =")
16 r=((7492.768-6928.2032)/6928.2032)*100
17 format(6)
18 disp(r," Therefore , %R(in percentage) = (E_ph-V_ph /
    V_ph)*100 = ")
19 disp("(b) cos(phi) = 0.707 leading , sin(phi) =
    0.707")
20 il=(1200*10^3)/(sqrt(3)*0.707*12*10^3)
21 format(6)
22 disp(il," Therefore , I_L(in A) = I_a = ...
    Star")
23 disp(" E_ph^2 = (V_ph*cos(phi)+I_a*R_a)^2 + (V_ph*
    sin(phi)+I_a*R_a)^2")
24 ephi=sqrt((((6928.2032*0.707)+(81.66*2))^2)
    +((((6928.2032*0.707)-(81.66*10))^2)))
25 format(10)
26 disp(ephi," Therefore , E_ph(in V) =")
27 r=((6502.2433-6928.2032)/6928.2032)*100
28 format(6)
29 disp(r," Therefore , %R(in percentage) = (E_ph-V_ph /
    V_ph)*100 = ")

```

---

# Chapter 5

## Alternators

Scilab code Exa 5.1 calculate full load slip

```
1 //Example 5.1
2 clc
3 disp("Given values are,")
4 disp("P = 4, f = 50 Hz, N = 1410 r.p.m")
5 ns=(120*50)/4
6 disp(ns,"N_s(in r.p.m) = 120*f / P =")
7 disp("Full load absolute slip is given by,")
8 s=((1500-1410)/1500)
9 format(5)
10 disp(s,"s = N_s-N / N_s =")
11 s=0.06*100
12 disp(s,"Therefore , %s =")
```

---

Scilab code Exa 5.2 calculate full load speed

```
1 //Example 5.2
2 clc
3 disp("Given values are,")
```

```

4 disp("P = 4, f = 50 Hz, %s = 4%")
5 disp("s = Full load absolute slip = 0.04")
6 ns=(120*50)/4
7 disp(ns,"N_s(in r.p.m) = 120*f / P =")
8 disp("s = N_s-N / N_s      where N_s = full load speed
      of motor")
9 disp("0.04 = 1500-N_s / 1500")
10 ns=1500-(1500*0.04)
11 disp(ns,"Therefore, N_s(in r.p.m) =")
12 disp("This is the full load speed of the motor")

```

---

### Scilab code Exa 5.3 frequency of induced emf

```

1 //Example 5.3. frequency of induced emf in the rotor
2 clc
3 disp("The given values are,")
4 disp("P = 4, f = 50 Hz, N = 1470 r.p.m")
5 ns=(120*50)/4
6 format(5)
7 disp(ns,"N_s(in r.p.m) = 120f/P =")
8 s=(1500-1470)/1500
9 disp(s,"s = N_s-N / N_s =")
10 f=0.02*50
11 disp(f,"Therefore, f_r(in Hz) = s*f =")

```

---

### Scilab code Exa 5.4 find full load slip

```

1 //Example 5.4
2 clc
3 disp("The given values are,")
4 disp("P = 8, f = 50 Hz, f_r = 2 Hz")
5 disp("Now      f_r = s*f")
6 s=2/50

```



```

7 format(5)
8 disp(s," Therefore , s =")
9 sp=0.04*100
10 disp(sp," Therefore , %s = ... Full load
      slip")
11 disp("The corresponding speed is given by,")
12 disp("N = N_s*(1-s) ... From s = N_s-N
      / N_s")
13 ns=(120*50)/8
14 disp(ns," where N_s(in r.p.m) = 120f/P =")
15 n=750*(1-0.04)
16 disp(n," Therefore , N(in r.p.m) = ... Full
      load speed")

```

---

**Scilab code Exa 5.5** calculate frequency

```

1 //Example 5.6
2 clc
3 disp("The given values are , K = Rotor turns/Stator
      turns = 1/2 = 0.5 and")
4 disp("P = 4, f = 50 Hz, N = 1455 r.p.m, E_line = 415
      V")
5 ns=(120*50)/4
6 format(5)
7 disp(ns," N_s(in r.p.m) = 120f/P =")
8 disp("For a given load , N = 1455 r.p.m")
9 s=(1500-1455)/1500
10 disp(s," Therefore , s = N_s-N / N_s =")
11 f=0.03*50
12 disp(f," (i) f_r(in Hz) = s*f =")
13 disp("(ii) At standstill , induction motor acts as a
      transformer so,")
14 disp("E_2ph/E_1ph = rotor turns/stator turns = K")
15 disp("But ratio of stator to rotor turns is given as
      2, i.e.")

```

```

16 disp(" N1/N2 = 2           Therefore ,  N2/N1 = 1/2 = K")
17 disp("and  E_1line = 415 V")
18 disp("The given values are always line values unless
      and until specifically stated as per phase.")
19 e1=415/sqrt(3)
20 format(6)
21 disp(e1," Therefore ,  E_1ph(in V) = E_1/sqrt(3) =
      ...As star connection E_line = sqrt
      (3)*E_ph")
22 disp(" Therefore ,  E_2ph/E_1ph = 1/2")
23 e2=239.6/2
24 disp(e2," Therefore ,  E_2ph(in V) =           ...
      Rotor induced e.m.f on standstill")
25 disp("(iii) In running condition ,")
26 er=0.03*119.8
27 disp(er," E_2r(in V) = s*E_2 =")
28 disp("The value of rotor induced e.m.f in the
      running condition is also very very small")

```

---

#### Scilab code Exa 5.6 find rotor current

```

1 //Example 5.6
2 clc
3 disp("The given values are ,")
4 disp("P = 4, f = 50 Hz, R2 = 0.2 ohm, X2 = 1 ohm")
5 disp("Now open circuit e.m.f between slip rings
      means rotor induced e.m.f on standstill. As long
      as rotor is open, there cannot be rotor current
      rotation of rotor. And between the slip rings
      means its a line value of E2, for a star
      connected rotor. The open circuit e.m.f is shown
      in fig.5.15")
6 disp(" Therefore ,  E_2line = 120 V, for star E_2line
      = sqrt(3)*E_2ph")
7 e2=120/sqrt(3)

```

```

8 format(6)
9 disp(e2," Therefore ,  $E_{2ph}$ (in V) =  $E_2/\sqrt{3}$  =")
10 ns=(120*50)/4
11 format(5)
12 disp(ns,"  $N_s$ (in r.p.m) = 120f/P =")
13 disp("(i) At start ,")
14 cp=0.2/(sqrt((0.2^2)+1))
15 format(6)
16 disp(cp,"  $\cos(\phi) = R_2/Z_2 = R_2 / \sqrt{R_2^2+X_2^2}$  =")
17 i2=69.28/(sqrt((0.2^2)+1))
18 disp(i2,"  $I_2$ (in A/phase) =  $E_2/Z_2 = E_2 / \sqrt{R_2^2+X_2^2}$  =")
19 disp("(ii) On full load , N = 1440 r.p.m")
20 s=(1500-1440)/1500
21 format(5)
22 disp(s," Therefore ,  $s = N_s - N / N_s$  =")
23 cpr=0.2/(sqrt((0.2^2)+(0.04^2)))
24 format(7)
25 disp(cpr," Therefore ,  $\cos(\phi)_{2r} = R_2/Z_{2r} = R_2 / \sqrt{R_2^2+(s*X_2)^2}$  =")
26 i2r=(0.04*69.28)/(sqrt((0.2^2)+(0.04^2)))
27 disp(i2r," Therefore ,  $I_{2r}$ (in A) =  $E_{2r}/Z_{2r} = sE_2 / \sqrt{R_2^2+(s*X_2)^2}$  =")
28 disp("It can be observed that current is drastically reduced from its value at start. In the running condition , slip controls and limits the magnitude of the motor current")

```

---

### Scilab code Exa 5.7 calculate torque developed

```

1 //Example 5.7 calculate torque developed on full
  load by the motor.
2 clc
3 disp("P = 4, f = 50 Hz, R2 = 0.1 ohm, X2 = 1 ohm, N
  = 1440 r.p.m")

```

```

4 disp("Stator turns/Rotor turns = 2/1")
5 disp("Therefore , K = E2/E1 = Rotor turns/Stator
      turns = 1/2 = 0.5")
6 ns=(120*50)/4
7 format(5)
8 disp(ns,"N_s(in r.p.m) = 120f/P =")
9 disp("E_1line = 400 V          ...Stator line
      voltage given")
10 e1=400/sqrt(3)
11 format(7)
12 disp(e1,"Therefore , E_1ph(in V) = E_1line/sqrt(3) =
      ")
13 disp("But E_2ph/E_1ph = 0.5 = K")
14 e2=230.94/2
15 disp(e2,"Therefore , E_2ph(in V) =")
16 s=(1500-1440)/1500
17 format(5)
18 disp(s,"Full load slip , s = N_s-N / N_s =")
19 ns=1500/60
20 disp("n_s(in r.p.s) = Synchronous speed in r.p.s")
21 disp(ns,"          = N_s/60 =")
22 t=(3/(2*pi*25))*((0.04*0.1*115.47^2)/((0.1^2)
      +(0.04^2)))
23 format(6)
24 disp(t,"T(in N-m) = (3 / 2*pi*ns) * (s*E2^2*R2 / R2
      ^2+(s*X2)^2) =")

```

---

#### Scilab code Exa 5.8 find torque

```

1 //Example 5.8
2 clc
3 disp("P = 4, f = 50 Hz, Stator turns/Rotor turns =
      4, R2 = 0.01 ohm, X2 = 0.1 ohm")
4 disp("E_1line = stator line voltage = 400 V")
5 e1=400/sqrt(3)

```

```

6 format(7)
7 disp(e1,"E1ph(in V) = E1line/sqrt(3) =
...star connection")
8 disp("K = E2ph/E1ph = Rotor turns/stator turns =
1/4")
9 e2=230.94/4
10 disp(e2,"Therefore , E2(in V) = 1/4 * E1ph =")
11 ns=(120*50)/4
12 format(5)
13 disp(ns,"Ns(in r.p.m) = 120f/P =")
14 disp("(i) At start , s = 1")
15 disp("Therefore , Tst = (k*E22*R2 / R22+X22)
where k = 3 / 2*pi*ns")
16 ns=1500/60
17 disp(ns,"ns(in r.p.s) = Ns/60 =")
18 k=3/(2*pi*25)
19 format(8)
20 disp(k,"Therefore , k = 3 / 2*pi*25 =")
21 t=((0.01909*0.01*57.7352)/((0.012)+(0.12)))
22 format(7)
23 disp(t,"Therefore , Tst(in N-m) =")
24 disp("(ii) Slip at which maximum torque occurs is ,")
25 sm=0.01/0.1
26 disp(sm,"sm = R2/X2 =")
27 psm=0.1*100
28 disp(psm,"%sm =")
29 disp("(iii) Speed at which maximum torque occurs is
speed corresponding to sm,")
30 n=1500*(1-0.1)
31 format(5)
32 disp(n,"N(in r.p.m) = Ns*(1-sm) =")
33 disp("(iv) The maximum torque is ,")
34 tm=(0.01909*57.7352)/(2*0.1)
35 format(7)
36 disp(tm,"Tm(in N-m) = k*E22 / 2*X2 =")
37 disp("(v) Full load slip , sf = 0.04 as %sf = 4%
")
38 t=((0.01909*0.04*0.01*57.7352)/((0.012)+(0.0042)))

```

```

    )
39 format(7)
40 disp(tf," T_f.l (in N-m) =(k*s*E2^2*R2 / R2^2+(s_f*X2
    ^2) =")

```

---

**Scilab code Exa 5.9** find ratio of torque

```

1 //Exmaple 5.9
2 clc
3 disp("Given values are,")
4 disp("P = 24, f = 50 Hz, R2 = 0.016 ohm, X2 = 0.265
    ohm, N = 247 r.p.m")
5 ns=(120*50)/24
6 format(5)
7 disp(ns," N_s (in r.p.m) = 120f/P =")
8 s=(250-247)/250
9 format(6)
10 disp(s," s_f = Full load slip = N_s-N / N_s =")
11 sm=0.016/0.265
12 format(8)
13 disp(sm," s_m = R2/X2 =")
14 tf=(2*0.06037*0.012)/((0.06037^2)+(0.012^2))
15 format(7)
16 disp(tf," (i) T_F.L/T_m = 2*s_m*s_f / s_m^2+s_f^2 =")
17 ts=(2*0.06037)/((0.06037^2)+(1^2))
18 format(7)
19 disp(ts," (ii) T_st/T_m = 2*s_m / 1+s_m^2 =")

```

---

**Scilab code Exa 5.10** find slip

```

1 //Example 5.10 slip , net o/p power, rotor copper
    loss/phase, efficiency and resistance
2 clc

```

```

3 disp("The given values are,")
4 disp("P = 4, f = 50 Hz, T_sh = 300 N-m, T_lost = 50
      N-m")
5 disp("Rotor frequency = 120 cycles/min = 120/60
      cycles/sec i.e. Hz")
6 disp("i.e. f_r = 2 Hz")
7 disp("(i) f_r = s*f")
8 s=2/50
9 format(5)
10 disp(s,"Therefore, s = f_r/f =")
11 disp("(ii) P_out = T_sh * omega = T_sh * 2*pi*N/60")
12 disp("Now N = N_s(1-s) at slip s = 0.04")
13 ns=(120*50)/4
14 format(5)
15 disp(ns,"N_s(in r.p.m) = 120f/P =")
16 n=1500*(1-0.04)
17 disp(n,"Therefore, N(in r.p.m) = N_s(1-s) =")
18 po=(300*((2*pi*1440)/60))*10^-3
19 format(8)
20 disp(po,"Therefore, P_out(in kW) =")
21 disp("Remember that T_sh is not output torque
      available to load at shaft")
22 disp("(iii) T_lost = 50 Nm in fiction")
23 f=50*((2*pi*1440)/60)
24 format(9)
25 disp(f,"Therefore, Frictional loss(in W) = T_lost *
      omega = T_lost * 2*pi*N/60 =")
26 disp("Now P_out = P_in - frictional loss")
27 pin=45.2389+7.539822
28 disp(pin,"Therefore, P_in(in kW) = P_out +
      frictional loss =")
29 disp("We know, P_2:P_c:P_m is 1:s:1-s")
30 disp("Therefore, P_c/P_m = s/1-s")
31 pc=(52.77872*10^3)*(0.04/(1-0.04))
32 format(10)
33 disp(pc,"Therefore, P_c(in W) = P_m * (s/1-s) =")
34 disp("These are total rotor copper losses")

```

```

35 rc=2199.1134/3
36 format(9)
37 disp(rc,"Therefore , Rotor copper loss per phase(in
      W) = P_c/3 =")
38 disp("(iv) Rotor efficiency = (Rotor output P_in /
      Rotor input P2)*100")
39 p2=2199.1134/0.04
40 format(12)
41 disp(p2,"Now P2(in W) = P_c/s =")
42 re=52778.72*100/54977.83
43 format(3)
44 disp(re,"Therefore , % Rotor eta(in percentage) =")
45 disp("(v) I_2r = 60 A      given per phase")
46 disp("now Rotor copper loss/ph = I_2r^2 * R2")
47 r2=733.0378/60^2
48 format(7)
49 disp(r2,"Therefore , R2(in ohm/ph) =")

```

---

#### Scilab code Exa 5.11 find shaft torque

```

1 //Example 5.11
2 clc
3 disp("P_out = 24 kW, I_L = 57 A")
4 disp("P = 8, N = 720 r.p.m, f = 50 Hz")
5 disp("I_L = 415 V, cos(phi) = 0.707")
6 ns=(120*50)/8
7 format(4)
8 disp(ns,"N_s(in r.p.m) = 120f/P =")
9 s=(750-720)/750
10 format(5)
11 disp(s,"Therefore , s = N_s-N / N_s =")
12 disp("P_m - mechanical loss = P_out")
13 pin=24000+1000
14 format(6)
15 disp(pin,"Therefore , P_in(in W) = P_out +

```



```

    mechanical loss = 24*10^3 + 1000 =")
16 disp("For rotor P2:P_c:P_m is 1:s:1-s")
17 disp("Therefore, P_c/P_m = s/1-s")
18 pc=(25000)*(0.04/(1-0.04))
19 format(8)
20 disp(pc,"Therefore, P_c(in W) = P_m * (s/1-s) =")
21 po=((24*10^3)/((2*pi*720)/60))
22 format(8)
23 disp(po,"(i) Shaft torque T_sh(in Nm) = P_out/omega
    = P_out / (2*pi*N/60) =")
24 t=((25*10^3)/((2*pi*720)/60))
25 disp(t,"(ii) Gross torque T(in Nm) = P_out/omega =
    P_out / (2*pi*N/60) =")
26 disp("(iii) Rotor copper losses = 1041.66 W")
27 disp("Now P2/P_c = 1/s")
28 p2=1041.66/0.04
29 disp(p2,"Therefore, P2(in W) = P_c/s =")
30 pin=sqrt(3)*415*57*0.707
31 format(9)
32 disp(pin,"And net input P_in(in W) = sqrt(3)*V_L*
    I_L*cos(phi) =")
33 disp("Stator current per phase = I_L = 57 A (as
    star connected)")
34 disp("R_s = Stator resistance per phase = 0.1 ohm")
35 st=3*(57^2)*0.1
36 format(6)
37 disp(st,"Therefore, Stator copper losses(in W) = 3*
    I_s^2*R_s")
38 disp("Now P_in - Stator losses = P_2")
39 s1=28966.96-26041.5
40 format(8)
41 disp(s1,"Therefore, Stator losses(in W) =")
42 disp("But Stator losses = Stator iron loss + Stator
    copper loss")
43 stp=2925.46-974.7
44 disp(stp,"Therefore, Stator iron losses(in W) =")
45 disp("(iv) Stator copper losses = 974.7 W")
46 disp("(v) Stator iron losses = 1950.76 W")

```

```

47 eta=(100*24*10^3)/28966.96
48 format(6)
49 disp(eta,"(iv) % eta(in percentage) = P_out/P_in *
      100 =")

```

---

### Scilab code Exa 5.15 find starting torque

```

1 //Example 5.15
2 clc
3 disp("P = 12, f = 50 Hz, R2 = 0.15 ohm, X2 = 0.25
      ohm, E2 = 32 V per phase given")
4 disp("Now T = (k*s*E2^2*R2 / R2^2+s*X2^2)
      where k = 3 / 2*pi*ns")
5 ns=(120*50)/12
6 format(4)
7 disp(ns,"N_s(in r.p.m) = 120f/P =")
8 ns=500/60
9 format(5)
10 disp(ns,"n_s(in r.p.s) = N_s/60 =")
11 tf=(3/(2*pi*8.33))*((0.15*32^2)/((0.15^2)+(0.25^2))
      )
12 format(7)
13 disp(tf,"(i) T_st = (k*E2^2*R2 / R2^2+X2^2) = (3/2*
      pi*ns)*(k*E2^2*R2 / R2^2+X2^2) =")
14 disp("(ii) At N = 480 r.p.m")
15 s=(500-480)/500
16 format(5)
17 disp(s,"s = N_s-N / N_s =")
18 tfi=(3/(2*pi*8.33))*((0.04*0.15*32^2)/((0.15^2)
      +((0.04*0.25)^2)))
19 format(7)
20 disp(tfi,"Therefore, T_F.L(in Nm) = (3/2*pi*ns)*(s*
      E2^2*R2 / R2^2+s*X2^2) =")
21 disp("(iii) T_m = (3/2*pi*ns)*(E2^2 / 2*X2)
      substituting s_m = R2/X2")

```

```

22 tm=(3/(2*pi*8.33))*((32^2)/(2*0.25))
23 format(8)
24 disp(tm,"Therefore , T_m(in Nm) =")
25 sm=0.15/0.25
26 format(4)
27 disp(sm,"(iv) Slip at T_m is , s_m = R2/X2 =")
28 n=500*(1-0.6)
29 format(4)
30 disp(n,"Therefore , N(in r.p.m) = N_s*(1-s_m) =")

```

---

**Scilab code Exa 5.18** find speed of motor

```

1 //Example 5.18
2 clc
3 disp("P = 8, f = 50 Hz, f_s = 1.5 Hz")
4 disp("f_s = s*f")
5 s=1.5/50
6 format(5)
7 disp(s,"Therefore , s = ... Slip")
8 ns=(120*50)/8
9 format(4)
10 disp(ns,"N_s(in r.p.m) = 120 f/P =")
11 n=750*(1-0.03)
12 format(6)
13 disp(n,"N(in r.p.m) = N_s*(1-s_m) =
... Speed of the motor")

```

---

**Scilab code Exa 5.19** find rotor input

```

1 //Example 5.19
2 clc
3 disp("P = 4, f = 50 Hz, T_sh = 159 Nm, s = 5% = 0.05
")

```

```

4 ns=(120*50)/4
5 format(5)
6 disp(ns,"N_s(in r.p.m) = 120f/P =")
7 n=1500*(1-0.05)
8 disp(n,"Therefore, N(in r.p.m) = N_s*(1-s_m) =")
9 po=159*((2*pi*1425)/60)
10 format(11)
11 disp(po,"Therefore, P_out(in W) = T_sh * omega =")
12 pm=23726.8785+500
13 disp(pm,"Therefore, P_m(in W) = P_out + Friction
and windage loss =")
14 disp("(a) P_2:P_c:P_m is 1:s:1-s")
15 p2=24226.8785/(1-0.05)
16 disp("Therefore, P_2/P_m = 1/1-s")
17 disp(p2,"Therefore, P_2(in W) = ...
Rotor input")
18 pi=25501.9774+1000
19 disp(pi,"(b) P_in(in W) = P_2 + Stator losses =
... Motor input")
20 eta=(23726.8785/26501.9774)*100
21 format(7)
22 disp(eta,"(e) %eta(in percentage) = P_out/P_in * 100
=")

```

---

**Scilab code Exa 5.22** find speeds

```

1 //Example 5.22
2 clc
3 disp("P = 6, f = 50 Hz, s_0 = 1%, s_a = 3%")
4 ns=(120*50)/6
5 format(5)
6 disp(ns,"(a) N_s(in r.p.m) = 120f/P =
... Synchronous speed")
7 n=1000*(1-0.01)
8 format(4)

```

```

9 disp(n,"(b) N_0(in r.p.m) = N_s*(1-s_0) =
      ...No load speed")
10 n=1000*(1-0.03)
11 format(6)
12 disp(n,"(c) N_ft(in r.p.m) = N_s*(1-s_a) =
      ...Full load speed")
13 disp("(d) Frequency of rotor current at standstill =
      f = 50 Hz")
14 sa=0.03*50
15 disp(sa,"(e) Frequency of rotor current at full load
      (in Hz) = s_a*f =")

```

---

#### Scilab code Exa 5.23 find resistance

```

1 //Example 5.23
2 clc
3 disp("P = 6, f = 50 Hz, I_2r = 40 A, N = 960 r.p.m")
4 ns=(120*50)/6
5 format(5)
6 disp(ns,"Therefore , N_s(in r.p.m) = 120f/P =")
7 s=40/1000
8 disp(s,"Therefore , s = N_s-N / N_s =")
9 po=50*735.5
10 format(6)
11 disp(po,"P_out(in W) = 50*H.P =          ...1
      H.P = 735.5 W")
12 pin=36775+1200+300
13 disp(pin,"P_in(in W) = P_out + Mechanical losses +
      Gear loss =")
14 disp("Now P_2:P_c:P_m is 1:s:1-s")
15 disp("Therefore , P_c/P_m = s/1-s")
16 pc=(38275*0.04)/(1-0.04)
17 format(10)
18 disp(pc,"Therefore , P_c(in W) =          ...
      Total rotor copper loss")

```

```
19 r2=1594.7916/(3*40^2)
20 format(7)
21 disp("Now P_c = 3 * I_2r^2 * R2")
22 disp(r2,"Therefore , R2(in ohm/ph) =")
```

---

# Chapter 6

## Instruments

Scilab code Exa 6.1 deflection

```
1 //exmaple6.1
2 clc
3 disp("The deflecting torque is given by,")
4 disp("(T_d)=NBAI=100*15*A*5*10^-3 Nm")
5 disp("Now A= Area = 10*8 =80 mm^2= 80*10^-6 m^2")
6 t=100*0.15*80*5*10^-9
7 disp(t," Therefore , (T_d) [in Nm]=100*0.15*80*(10^-6)
      *5*(10^-3)=")
8 disp("Now, T_d=T_c=K*(theta)")
9 disp(" Therefore , 6*10^-6 = 0.2*10^-6 *(theta)")
10 t=(6*10^-6)/(0.2*10^-6)
11 disp(t," Therefore , theta (in degree)=(6*10^-6)
      /(0.2*10^-6)= ")
```

---

Scilab code Exa 6.2 theta

```
1 //example6.2
2 clc
```

```

3 disp("The rate of change of inductance with
      deflection is,")
4 disp("dL/d(theta)=d(12+6(theta)-(theta^2))/d(theta)
      =6-2(theta) uH/radian= 6-2(theta)*10^-6 H/radians
      ")
5 disp("From the torque equation,")
6 disp("theta=(I^2)dL/(2*K*d(theta))")
7 disp("therefore , theta=(8^2)*[6-2(theta)]*10^-6
      /(2*12*10^-6)")
8 disp("Therefore , 0.375(theta)=6-2(theta)")
9 t=6/2.375
10 format(6)
11 disp(t,"Therefore , theta[in radians]= ")

```

---

#### Scilab code Exa 6.3 shunt resistance

```

1 //example6.3
2 clc
3 disp("Given values are , (R_m)=100 ohm, (I_m)=2 mA, I
      =150 mA")
4 disp("(R_sh)=[(I_m)*(R_m)]/[I-(I_m)]")
5 r=(2*100*10^-3)/((150*10^-3)-(2*10^-3))
6 format(6)
7 disp(r,"Therefore , (R_sh)[in ohm]=(2*100*10^-3)
      /((150*10^-3)-(2*10^3))=")

```

---

#### Scilab code Exa 6.4 current through shunt and resistance of motor

```

1 //example6.4
2 clc
3 disp("a) The drop across the shunt is same as drop
      across the coil.")
4 disp("Therefore , [(I_sh)*(R_sh)]=400 mV")

```



```

5 i=(400*10^-3)/0.01
6 disp(i,"Therefore , I_sh(in A)=(400*10^-3)/0.01= ")
7 disp("b) The voltage across shunt for shunted
      current of 50 A is,")
8 v=50*0.01
9 disp(v,"V_sh(in V)=[(I_sh)*(R_sh)]=50*0.01=")
10 disp("For this voltage the meter should give full
      scale deflection. In first case, the current
      through meter for full deflection was,")
11 i=(400*10^-3)/750
12 disp(i,"I_m(in A)=(400mV)/(R_m)=(400*10^-3)/750=")
13 disp("The same I_m must flow for new voltage across
      the meter of 0.5 V")
14 disp("Therefore , [(I_m)*(R_m) ' ']=0.5")
15 disp("Therefore , [(5.33*10^-4)*(R_m) ' ']=0.5")
16 r=0.5/(5.33*10^-4)
17 disp(r,"Therefore , (R_m' ')[in ohm]=")
18 disp("This is the resistance of the meter required
      for 50 A shunted current to give full scale
      defection.")

```

---

#### Scilab code Exa 6.5 multiplier resistance

```

1 //example6.5
2 clc
3 disp("Given values are , R_m=500 ohm, I_m=40 uA and V
      =10 V")
4 r=(10/(40*10^-6))-500
5 format(8)
6 disp(r,"Now, (R_s)[in ohm]=V/(I_m) - R_m =")
7 disp("This is the required multiplier resistance")

```

---

#### Scilab code Exa 6.6 shunt required and multiplier required

```

1 //example6.6
2 clc
3 disp("The meter current (I_m)=20 mA")
4 disp("Drop across meter, (V_m)=200 mV")
5 disp("Now, (V_m)=[(I_m)*(R_m)]")
6 disp("Therefore, 200 mV = (20 mA)(R_m)")
7 r=200/20
8 disp(r,"Therefore, (R_m)[in ohm]=")
9 disp("i) For using it as an ammeter, I=200 A")
10 r=(200*10^-3)/(200-(20*20^-3))
11 format(6)
12 disp(r,"R_sh(in ohm)=[(I_m)*(R_m)]/[I-(I_m)]=")
13 disp("This is the required shunt.")
14 disp("ii) For using it as a voltmeter, V=500 V")
15 disp("Therefore, (R_s)=V/(I_m) - (R_m)")
16 r=(500/(20*10^-3))-10
17 format(8)
18 disp(r,"= (500/(20*10^-3))-10 = ")
19 disp("This is the required multiplier.")

```

---

### Scilab code Exa 6.7 voltage induced

```

1 //example6.7
2 clc
3 disp("The arrangement is shown in the Fig 6.18(a)")
4 disp("The voltmeter range = 50 V")
5 r=100*50
6 disp(r,"Therefore, (R_m)[in ohm] = Voltmeter
   resistance = 100 ohm/V * 50 =")
7 disp("This appears in parallel with 55 ohm resistor
   as shown in the Fig.6.18(b)")
8 r=(55*5000)/(55+5000)
9 format(9)
10 disp(r,"Therefore, R' (in ohm)= 55||5000 =
   (55*5000)/(55+5000)= ")

```

```

11 i=80/(105+54.40158)
12 format(8)
13 disp(i," Therefore , I(in A)=80/(105+R' '=")
14 v=0.501877*54.40158
15 disp(v," Therefore , Voltage across R' '(in V)=[I*R
    '']=0.501877*54.40158=")
16 disp("The voltmeter will sense this voltage.")
17 disp(" Therefore , Voltage indicated = 27.3029 V")

```

---

#### Scilab code Exa 6.8 resistance

```

1 //example6.8
2 clc
3 disp(" I_m=15 mA, R_m=5 ohm")
4 disp(" i) I=2A")
5 r=(15*5*10^-3)/(2-(15*10^-3))
6 format(8)
7 disp(r," R_sh(in ohm)=[(I_m)*(R_m)]/[I-(I_m)]=")
8 disp(" ii) V=100 V")
9 r=(100/(15*10^-3))-5
10 format(10)
11 disp(r," R_s(in ohm)=V/I_m - R_m =")

```

---

#### Scilab code Exa 6.9 ammeter and voltmeter

```

1 //example6.9
2 clc
3 disp(" R_m=5 ohm, I_m=15 mA")
4 disp(" i) I=15A")
5 r=(15*5*10^-3)/(15-(15*10^-3))
6 format(9)
7 disp(r," R_sh(in ohm)=[(I_m)*(R_m)]/[I-(I_m)]=")
8 disp(" ii) V=15 V")

```

```

9 r=(15/(15*10^-3))-5
10 format(4)
11 disp(r,"R_s(in ohm)=V/I_m - R_m =")

```

---

**Scilab code Exa 6.10** number of turns

```

1 //example6.10
2 clc
3 disp("R_m=2000 ohm, V_m=100 V, N=10000")
4 i=100/2000
5 disp(i,"Therefore , I_m(in A)=(V_m)/(R_m)=100/2000=")
6 i=0.05*10000
7 disp(i,"Therefore , AT for full scale deflection = (
      I_m)*N=0.05*10000")
8 disp("For I=20 A, AT=I*N' ")
9 disp("Therefore , 500=20*N' ")
10 n=500/20
11 disp(n,"Therefore , N' =")

```

---

**Scilab code Exa 6.11** shunt resistance and full scale deflection

```

1 //example6.11
2 clc
3 disp("I_m=15 mA, R_m=1.5 ohm at 15 degree celcius , R
      =3.5 ohm")
4 r=1.5+3.5
5 disp(r,"Therefore , R_mT(in ohm)= Total meter
      resistance = 1.5+3.5 = ")
6 disp(" i) I=20A")
7 r=(15*5*10^-3)/(20-(15*10^-3))
8 format(10)
9 disp(r,"Therefore , R_sh(in ohm)=[(I_m)*(R_mT)]/[I-(
      I_m)]=")

```

```

10 disp(" ii ) V=250 V")
11 r=(100/(15*10^-3))-5
12 disp(r," R_s(in ohm)=V/I_m - R_mT =")
13 disp("Now at 25 degree celcius , (R_m)'' is the new
meter resistance.")
14 disp("R_m'' = R_m[1+(alpha_1)*(t2-t1)] where t1=15
degree celcius , t2=25 degree celcius")
15 a=(1/234.5)/(1+(15/234.5))
16 format(6)
17 disp(a,"(alpha_1)[in per degree celcius]=(alpha_0)
/(1+[(alpha_0)*t1])=(1/234.5)/(1+(15/234.5))=")
18 r=1.5*(1+(0.004*(25-15)))
19 format(8)
20 disp(r,"Therefore , R_m''(in ohm)
=1.5*(1+(0.004*(25-15)))=")
21 r=1.56012+3.5
22 format(8)
23 disp(r,"Therefore , R_mT''(in ohm)=1.56012+3.5=")
24 disp("Error in part(i) : The Fig. 6.19 shows two
cases.")
25 disp("Therefore , I_m1 at 15 degree celcius = (I*R_sh
)/[(R_sh+(R_mT))]=7.4999*10^-4 I")
26 disp("Therefore , I_m2 at 25 degree celcius = (I*R_sh
)/[(R_sh+(R_mT'')]=7.41092*10^-4 I")
27 i=((7.41092*10^-2)-(7.4999*10^-2))/(7.4999*10^-4)
28 format(7)
29 disp(i,"% error = [(I_m2)-(I_m1)*100]/(I_m1)=")
30 disp("Negative sign indicates that the reading is
less than the actual reading.")
31 disp("Error in part(ii) : The Fig. 6.19 shows two
cases.")
32 disp("Therefore , V_m1 = (V*R_mT)/(R_mT+R_s)=(5*V)
/(5+16661.67)=2.9999*10^-4 V")
33 disp("Therefore , V_m2 = (V*R_mT'')/(R_mT''+R_s)
=(5.06012*V)/(5.06012+16661.67)=3.03606*10^-4 V")
34 v=((3.03606*10^-2)-(2.9999*10^-2))/(2.9999*10^-4)
35 format(7)
36 disp(v,"% error = [(V_m2)-(V_m1)*100]/(V_m1)=")

```



# Chapter 7

## Semiconductor Physics and Diode

Scilab code Exa 7.1 forbidden gap

```
1 //Example 7.1
2 clc
3 disp("Forbidden gap for silicon is given by,")
4 disp("E_C = 1.21 - 3.6*10^-4 * T")
5 disp("Now T = 35+273 = 308 K")
6 ec=1.21-(308*3.6*10^-4)
7 format(6)
8 disp(ec,"Therefore , E_C(in eV) =")
9 disp("While forbidden gap for germanium is given by,")
10 disp("E_C = 0.785 - 2.23*10^-4 * T")
11 ec=0.785-(308*2.23*10^-4)
12 format(7)
13 disp(ec,"Therefore , E_C(in eV) =")
```

---

Scilab code Exa 7.2 resistivity

```

1 //Example 7.2
2 clc
3 disp("The given values are , n_i = 1.5*10^10 / cm^3")
4 disp("Therefore , n_i = 1.5*10^10/10^-6 /m^3")
5 disp("          = 1.5*10^16 /m^3")
6 disp("And u_n = 1300*10^-4 m^2/V-sec")
7 disp("u_p = 500*10^-4 m^2/V-sec")
8 disp("Now sigma_i = n_i*(u_n + u_p)*e
      ... conductivity")
9 sig=(1.5*10^16)*(1300+500)*(1.6*10^-23)
10 format(9)
11 disp(sig,"Therefore sigma_i(in per ohm-m) =")
12 rho=1/0.000432
13 format(10)
14 disp(rho,"Therefore , rho(in ohm-m) = 1/sigma_i =")
15 disp("This is the required resistivity")

```

---

### Scilab code Exa 7.3 current in the bar

```

1 //Example 7.3
2 clc
3 disp("Electron density = n_i = carrier intrinsic
      concentration")
4 disp("Therefore , n_i = 1.5*10^16 /m^3")
5 disp("For intrinsic semiconductor,")
6 disp("sigma_i = n_i*(u_n + u_p)*e")
7 disp("where e = charge on one electron = 1.6*10^-19
      C")
8 sig=(1.5*10^16)*(0.14+0.05)*(1.6*10^-19)
9 format(9)
10 disp(sig,"Therefore sigma_i(in per ohm-m) =
      Conductivity =")
11 rho=1/0.000456
12 format(9)
13 disp(rho,"Therefore , rho(in ohm-m) = Resistivity =")

```



```

    1/sigma_i =")
14 disp("      Now      R = roh*l/A")
15 disp(" Therefore ,   V/A = roh*l/A")
16 l=((9*2.5*10^-4)/(2192.982*1.2*10^-3))*10^3
17 format(6)
18 disp(1," Therefore ,   l(in mm) =")
19 disp(" This is the length of the bar")

```

---

#### Scilab code Exa 7.4 resistivity of intrinsic germanium

```

1 //Example 7.4
2 clc
3 disp(" Given values are")
4 disp("   n_i = 2.5*10^13 /cm^3")
5 disp(" Therefore ,   n_i = 2.5*10^13/10^-6 /m^3")
6 disp("                = 2.5*10^19 /m^3")
7 disp(" And   u_n = 3800*10^-4 m^2/V-sec")
8 disp("       u_p = 1800*10^-4 m^2/V-sec")
9 disp("   sigma_i = n_i*(u_n + u_p)*e")
10 sig=(2.5*10^19)*(3800+1800)*(1.6*10^-23)
11 format(5)
12 disp(sig," Therefore   sigma_i(in per ohm-m) =")
13 rho=1/2.24
14 format(7)
15 disp(rho," Therefore ,   rho_i(in ohm-cm) = 1/sigma_i =
    ")

```

---

#### Scilab code Exa 7.7 comparing two values

```

1 //Example 7.7
2 clc
3 disp(" Referring to the table 7.2 of properties of
    germanium has 4.4*10^22 atoms/cm^3")

```

```

4 disp("For 10^8 germanium atom there is 1 atom
      impurity added, as given.")
5 disp("Thus, for 4.4*10^22 germanium atoms, we have,")
6 disp("      = 4.4*10^22 / 10^8 = 4.4*10^14 atoms of
      impurity/cm^3")
7 disp("This is nothing but concentration of donor
      atoms i.e. N_D")
8 disp("Therefore, N_D = 4.4*10^14 per cm^3 =
      4.4*10^14/10^-6 = 4.4*10^20 per m^3")
9 disp("Now as donor impurity is added, n-type
      material will form,")
10 disp("Therefore, sigma_n = n_n*u_n*q = N_D*u_n*q")
11 disp("where n_n ~ N_D and u_n = 3800 cm^2/V-sec =
      3800*10^-4 m^2/V-sec")
12 sigm=4.4*3800*1.6*10^-3
13 format(7)
14 disp(sigm,"Therefore, sigma_n(in per ohm-m) =")
15 rho=(1/26.752)*10^2
16 format(5)
17 disp(rho,"Therefore, rho_n(in ohm-cm) = Resistivity
      = 1/sigma_i =")
18 disp("Comparing this with resistivity of intrinsic
      germanium it can be observed that resistivity
      reduces considerably due to addition of impurity.
      Hence conductivity of n-type material is much
      higher and hence it can carry more current as
      compared to the intrinsic semiconductors. By
      controlling amount of doping we can control the
      conductivity.")

```

---

#### Scilab code Exa 7.9 new diode current

```

1 //Example 7.9
2 clc

```

```

3 disp("The current equation of a diode is")
4 disp("I = I_0 * (e^(V/eta*VT) - 1)")
5 disp("At 300 K, VT = 26 mV = 26*10^-3 V")
6 disp(" V = 0.71 V for I = 2.5 mA and eta = 2 for
    silicon")
7 i0=(2.5*10^-3)/((%e^(0.71/(2*26*10^-3)))-1)
8 format(9)
9 disp(i0,"Therefore , I_0(in A) =")
10 disp("Now V = 0.8 V")
11 i=((2.93*10^-9)*((%e^(0.8/(2*26*10^-3)))-1))*10^3
12 format(6)
13 disp(i,"Therefore , I(in mA) =")

```

---

#### Scilab code Exa 7.10 forward bias current

```

1 //Example 7.10
2 clc
3 disp("the given values are I_0 = 3 uA, T = 27 C =
    27+273 = 300 K, eta =1")
4 disp("Now I_rated = 1 A for diode")
5 disp("and I = 1% of I_rated at 27 C")
6 disp("Therefore , I = 0.01 A")
7 vt=300*8.62*10^-5
8 format(6)
9 disp(vt,"V_T(in V) = k*T =")
10 disp("According to diode equation , I = I_0 * (e^(V/
    eta*VT) - 1)")
11 v=8.112*0.026
12 format(7)
13 disp(v,"Therefore , V(in V) =")

```

---

#### Scilab code Exa 7.11 reverse saturation current and eta for diode

```

1 //Example 7.11
2 clc
3 disp("At V1 = 0.4 V, I1 = 10 mA and at V2 = 0.42 V,
      I2 = 2*I1 = 20 mA")
4 disp("Now I = I_0 * (e^(V/eta*VT) - 1)")
5 disp("Therefore, (10*10^-3) = I_0 * (e^(0.4/(eta
      *26*10^3)) - 1) ... (1)")
6 disp("and (20*10^-3) = I_0 * (e^(0.42/(eta*26*10^3)
      ) - 1) ... (2)")
7 disp("In forward bias condition 1 << e^(VT/eta*VT),
      Therefore, Neglecting 1")
8 disp("(10*10^-3) = (I_0)*e^(15.384/eta) .. (3)")
9 disp("and, (20*10^-3) = (I_0)*e^(16.153/eta)")
10 disp("Dividing the two equations (3) and (4),")
11 disp("(1/2) = (e^(15.384/eta))/(e^(16.153/eta))")
12 disp("Therefore, (e^(16.153/eta)) = 2*(e^(15.384/eta
      ))")
13 disp("Taking natural logarithm of both sides,")
14 disp("Therefore, 16.153/eta = ln2 + 15.384/eta")
15 disp("Therefore, (1/eta)*(16.153 - 15.384) = 0.6931")
16 e=(16.153-15.384)/0.6931
17 disp(e,"Therefore, eta=")
18 disp("Hence (I_0)=9.45 nA")

```

---

**Scilab code Exa 7.12** reverse saturation current and forward current

```

1 //Example 7.12
2 clc
3 disp("I_01 = 3 nA at T1 = 27 C, T2 = 82 C")
4 dt=82-27
5 format(3)
6 disp(dt,"(i) deltaT(in degree C) = T2 - T1 =")
7 dt1=(2^(55/10))*3
8 format(8)
9 disp(dt1,"Therefore, I_02(in nA) = 2^(deltaT/10) *

```

```

    I_01 =")
10 disp("(ii) V = 0.25 V, I_02 = 135.764 nA at 82 C")
11 disp("Therefore I_f = I_0 * (e^(V/eta*VT) - 1)")
12 vt=(82+273)/11600
13 format(7)
14 disp(vt,"V_T(in V) = T/11600 =")
15 disp("eta = 2 for Si")
16 i0=((135.764*10^-9)*((%e^(0.25/(2*0.0306))))-1))*10^6
17 format(6)
18 disp(i0,"Therefore , I_f(in uA) =")

```

---

#### Scilab code Exa 7.14 dc output voltage

```

1 //Example 7.14
2 clc
3 disp("In the circuit of the fig.7.47(a), the diode
    will be forward biased during negative half cycle
    of a.c. input voltage , and d.c output voltage
    will be negative w.r.t common ground terminal , as
    shown.")
4 disp("(a) For an ideal diode , cut-in voltage V_T =
    0, R_T = 0")
5 dc=-((15/%pi)
6 format(5)
7 disp(dc,"D.C. output voltage(in V) = -Maximum value
    of a.c. input voltage / pi =")
8 disp("Negative sign indicates that voltage is
    negative w.r.t ground.")
9 disp("(b) For a silicon diode , V_T = 0.7 V, R_f is
    assumed to be zero")
10 dc1=-((15-0.7)/%pi)
11 format(5)
12 disp(dc1,"D.C. output voltage(in V) = -[Maximum
    value of a.c. voltage-V_T] / pi =")

```

---

**Scilab code Exa 7.15** dc voltage and load current

```
1 //Example 7.15
2 clc
3 disp("Given values are R_L = 1 k-ohm, V_m = 10 V
      peak")
4 disp("case(i) Ideal diode")
5 disp("Cut-in voltage V_T = 0 V, R_f = 0 ohm")
6 edc=10/%pi
7 format(5)
8 disp(edc,"Therefore , E_DC(in V) = V_m/pi =")
9 idc=3.18
10 disp(idc,"Therefore , I_DC(in mA) = E_DC/R_L =")
11 disp("case(ii) Silicon diode")
12 disp("Cut-in voltage V_T = 0.7 V")
13 edc=9.3/%pi
14 format(5)
15 disp(edc,"Therefore , E_DC(in V) = V_m-V_T / pi =")
16 idc=2.96
17 disp(idc,"Therefore , I_DC(in mA) = E_DC/R_L =")
```

---

**Scilab code Exa 7.17** power to load and regulation and efficiency and TUF of secondary

```
1 //example7.17
2 clc
3 disp("Given: E_s=30 V, R_f=2 ohm, R_s=8 ohm, R_L=1 k
      -ohm")
4 disp("E_s=E_RMS=30 V")
5 e=30*sqrt(2)
6 disp(7)
7 disp(e,"E_sm(in V)=(E_s)*sqrt(2)=")
```

```

8 i=(30*sqrt(2))/(2+1000+8)
9 format(6)
10 disp(i,"I_m(in A)=(E_sm)/(R_f+R_L+R_s)=")
11 i=(2*42)/(%pi)
12 format(6)
13 disp(i,"I_DC(in mA)=(2*I_m)/pi=")
14 p=1000*(26.74*10^-3)^2
15 disp(p,"a) Power delivered to the load = (I_DC^2)*
    R_L) = ")
16 v=(2*30*sqrt(2))/(%pi)
17 format(3)
18 disp(v,"V_DC, no load = (2*E_sm)/pi = ")
19 v=26.74*1000*10^-3
20 format(6)
21 disp(v,"V_DC, full load (in V) = (I_DC)*R_L = ")
22 r=((27-26.74))/26.74
23 format(5)
24 disp(r,"% Regulation = ((V_NL-V_FL)*100)/(V_FL)= ")
25 e=(8/(%pi)^2)*(1/(1+(10/1000)))
26 format(6)
27 disp(e,"c) Efficiency of rectification = dc output/
    ac output =")
28 t=(30*42*10^-3)/sqrt(2)
29 format(5)
30 disp(t,"d) Transformer secondary rating(in W) = (
    E_RMS)*(I_RMS) = ")
31 u=0.715/0.89
32 disp(u,"TUF = DC power output/AC rating = ")

```

---

### Scilab code Exa 7.20 ac input power

```

1 //example7.20
2 clc
3 disp("P_DC=500 W, Half wave rectifier")
4 disp("For half wave rectifier , %eta=40.6%      ...("

```

```

    Assuming maximum)")
5 disp(" Therefore , 40.6=(P_DC*100)/(P_AC)")
6 disp(" Therefore , 40.6=(500*100)/(P_AC)")
7 p=(500*100)/(40.6)
8 format(9)
9 disp(p," Therefore , P_AC(in W)=")
10 disp(" For the same load , with full wave rectifier
    the maximum rectifier efficiency is 81.2%")
11 disp(" Therefore , 81.2=(500*100)/(P_AC)")
12 p=(500*100)/81.2
13 format(10)
14 disp(p," Therefore , P_AC(in W)=")

```

---

#### Scilab code Exa 7.21 percentage eta

```

1 //example7.21
2 clc
3 disp("The given values are,")
4 disp(" R_f=0.1 ohm, I_DC=10 A, R_s= 0 ohm, E_s (RMS)
    =30 V")
5 e=30*sqrt(2)
6 format(8)
7 disp(e,"Now, (E_sm)=E_sm(RMS)*sqrt(2) =")
8 disp("(I_DC)=(2*I_m)/pi")
9 i=(%pi*10)/2
10 disp(i,"I_m (in A)=(pi*I_DC)/2=")
11 disp("Now, (I_m)=(E_m)/(2*R_f+R_s+R_L)")
12 disp(" Therefore , 15.7079 = 42.4264/(2*0.1+R_L)")
13 disp(" Therefore , R_L+0.2=2.7")
14 r=2.7-0.2
15 disp(r," Therefore , R_L (in ohm)=")
16 p=(10^2)*2.5
17 disp(p,"P_DC (in W)=(I_DC^2)*R_L=")
18 disp("P_AC = (I_RMS^2)*(2*R_f+R_s+R_L)")
19 i=15.7079/sqrt(2)

```



```

20 disp(i,"and, (I_RMS) [in A]=(I_m)/sqrt(2)=")
21 p=(11.1071^2)*(0.2+2.5)
22 disp(p,"Therefore, (P_AC) [in W]=")
23 e=(250*100)/333.092
24 disp(e,"% eta=(P_DC*100)/(P_AC)=")

```

---

**Scilab code Exa 7.22** dc load current and load voltage and ripple voltage and PIV rating

```

1 //example7.22
2 clc
3 disp("R_L =5 k-ohm=5*10^3 ohm, N1:N2 is 2:1")
4 disp("E_p = 460V RMS value")
5 disp("Therefore, (E_s)/(E_p)=N2/N1=1/2")
6 disp("Therefore, E_s = (E_p)/2 = 230 V")
7 e=230*sqrt(2)
8 format(8)
9 disp(e,"Therefore, E_sm(in V)=")
10 disp("Now, (I_DC)=(2*I_m)/pi where (I_m)=(E_sm)
      /(R_L) neglecting R_f")
11 i=(2*325.269)/(%pi*5*10^3)
12 format(8)
13 disp(i,"Therefore, (I_DC) [in A]=(2*E_sm)/(pi*R_L)=")
14 d=41.41*5
15 format(8)
16 disp(d,"DC load voltage E_DC(in V) = (I_DC)*(R_L) =
      ")
17 disp("Ripple voltage = ripple factor*(V_DC)")
18 disp("Ripple factor of bridge rectifier is 0.482")
19 r=0.482*207.072
20 format(5)
21 disp(r,"Therefore, Ripple factor = ")
22 disp("PIV rating of each diode = (E_sm) for bridge
      rectifier = 325.27 V")

```

---

**Scilab code Exa 7.23** load voltage and ripple voltage

```
1 //exmaple7.23
2 clc
3 disp("E_p(rms) = 230V, N2/N1 = 1/15, R_L=50 ohm")
4 disp("R_f = R_s = 0 ohm as ideal")
5 disp("Now, E_p(rms)/E_s(rms) = N1/N2")
6 e=230/15
7 format(7)
8 disp(e,"Therefore , E_s(rms) [in V] = N2*E_p(rms)/N1 =
      230/15 = ")
9 e=15.333*sqrt(2)
10 disp(e,"Therefore , E_sm(in V) = ")
11 i=21.684/50
12 disp(i,"Therefore , (I_m) = (E_sm)/(R_s+2*R_f+R_L)= ")
13 i=(2*0.4336)/(%pi)
14 disp(i,"I_DC(in A)=(2*I_m)/pi=")
15 e=0.276*50
16 disp(e,"Therefore , E_DC(in V)=Load voltage=(I_DC)*(
      R_L)=")
17 disp("Ripple factor = 0.482      ..For full wave
      rectifier")
18 disp("Ripple factor = (ac rms output)/(dc output)=(
      ripple voltage)/E_DC")
19 disp("Therefore , 0.482=ripple factor")
20 r=13.8*0.482
21 disp(r,"Therefore , Ripple voltage = 13.8*0.482 = ")
```

---

**Scilab code Exa 7.25** dc output voltage

```
1 //example7.25
```

```

2  clc
3  disp("For a half wave rectifier ,")
4  disp("(I_m) = (E_sm)/(R_f+R_L)")
5  disp("and, (I_DC) = (I_m)/pi = (E_sm)/pi*(R_f+R_L)")
6  disp("and, (V_DC) = (I_DC)*(R_L)")
7  disp("Therefore, (P_DC) = (V_DC)*(I_DC) = (I_DC^2)*(R_L) = ((E_sm^2)*(R_L))/((pi^2)*(R_f+R_L)^2)")
8  disp("For this power to be maximum,")
9  disp("(dP_DC)/(dR_L) = 0")
10 disp("(d/dR_L)*((E_sm^2)*(R_L))/((pi^2)*(R_f+R_L)^2) = ((E_sm^2)/(pi^2))*((R_f+R_L)^2 - R_L*2*(R_f+R_L))/((R_f+R_L)^4)")
11 disp("Therefore, (R_f+R_L)^2 - 2*R_L*(R_f+R_L) = 0")
12 disp("Therefore, (R_f^2)-(R_L^2) = 0")
13 disp("Therefore, (R_L)^2 = (R_f)^2 i.e. R_L = R_f")
14 disp("Thus the power output is maximum if R_L = R_f")

```

---

### Scilab code Exa 7.29 forward current

```

1  //example7.29
2  clc
3  disp("For silicon diode, eta=2, (I_0)=10 uA, (V_T)=26 mV")
4  disp("I = (I_0)*[e^(V/(eta*V_T))-1]")
5  i=(10*10^-6)*(%e^(0.1/(2*26*10^-3))-1)
6  format(13)
7  disp(i,"i) I(in A)=(10*10^-6)*(e^(0.1/(2*26*10^-3))-1)=")
8  i=(10*10^-6)*(%e^(0.2/(2*26*10^-3))-1)
9  disp(i,"ii) I(in A)=(10*10^-6)*(e^(0.1/(2*26*10^-3))-1)=")
10 i=(10*10^-6)*(%e^(0.3/(2*26*10^-3))-1)

```

```
11 disp(i," iii ) I(in A)=(10*10^-6)*(e^(0.1/(2*26*10^-3)
    )-1)=")
```

---

### Scilab code Exa 7.30 temperature

```
1 //example7.30
2 clc
3 disp("(I_01)=0.1 uA, (T_1)=20 degree celcius , (T_2)
    =40 degree celcius")
4 i=(0.1)*(2^(20/10))
5 disp(i," Therefore , (I_02) [in uA]=(I_01)*(2^(delta(T)
    )/10)")
```

---

### Scilab code Exa 7.31 conductivity of silicon

```
1 //example7.31
2 clc
3 disp("As the impurity is acceptor , it forms a p-type
    material.")
4 disp(" Therefore , N_A = 10^22 /m^3 = p_p")
5 disp(" Now, (p_p)*(n_p)=(n_i)^2 i.e. (10^22)*(
    n_p)=(1.4*10^16)^2")
6 n=((1.4*10^16)^2)/(10^22)
7 disp(n," Therefore , n(in /m^3)= ")
8 r=((1.96*0.145*10^10)+(0.05*10^22))*(1.6*10^-19)
9 disp(r," rho(in (ohm-m)^-1) = ((n_p*u_n)+(p_p*u_p))*e
    = ")
```

---

# Chapter 8

## Transistors

Scilab code Exa 8.1 base current

```
1 //exmaple8.1
2 clc
3 disp(" Given : I_E=12 mA, I_E= 1.02(I_c)")
4 disp(" Therefore , 1.02(I_c)=12*10^-3")
5 i=(12*10^-3)/1.02
6 format(9)
7 disp(i," I_c (in A)=")
8 disp(" I_E = I_B + I_c")
9 b=12-11.765
10 disp(b," Therefore , I_B (in mA) = I_E - I_c =
    (12-11.765)mA = ")
```

---

Scilab code Exa 8.2 alpha dc and beta dc

```
1 //example8.2
2 clc
3 disp(" a) (alpha_dc)=(beta_dc)/(1+(beta_dc))")
4 b=50/51
```

```

5 format(7)
6 disp(b,"For , (beta_dc)=50, (alpha_dc)=50/(1+50)=")
7 b=190/191
8 disp(b,"For , (beta_dc)=190, (alpha_dc)=190/(1+190)=")
9 disp("b) (beta_dc)=(alpha_dc)/(1-(alpha_dc))")
10 a=0.995/(1-0.995)
11 disp(a,"For , (alpha_dc)=0.995, (beta_dc)
    =0.995/(1-0.995)=")
12 a=0.9765/(1-0.9765)
13 format(6)
14 disp(a,"For , (alpha_dc)=0.9765, (beta_dc)
    =0.9765/(1-0.9765)=")

```

---

### Scilab code Exa 8.3 collector current

```

1 //example8.3
2 clc
3 disp("Given : I_B=20 uA, I_E=6.4 mA")
4 disp("I_E=I_B+I_C=I_B +[(I_B)*(beta_dc)]=(I_B)*(1+(
    beta_dc))")
5 b=(6.4*10^-3)/(20*20^-6)
6 disp(b,"(beta_dc)+1=(I_E)/(I_B)=")
7 b=320-1
8 disp(b,"Therefore , (beta_dc)=")
9 a=319/320
10 format(7)
11 disp(a,"(alpha_dc)=(beta_dc)/(1+(beta_dc))
    =319/(1+319)=")
12 i=319*20
13 disp(i,"I_C (in uA)=[(beta_dc)*(I_B)]=")
14 c=0.9968*6.4
15 disp(c,"Also , (I_C) [in mA]=[ (alpha_dc)*(I_E)]=")

```

---

#### Scilab code Exa 8.4 alpha dc and beta dc

```
1 //example8.4
2 clc
3 disp(" Given: I_CO=1.1 uA, I_E=21 uA")
4 disp(" I_CEO=(1+(beta_dc))*(I_CO)")
5 disp(" 1+(beta_dc)=(I_CEO).(I_CO)=(21 uA)/(1.1 uA)=19
      ")
6 b=19-1
7 disp(b," Therefore , (beta_dc)=")
8 a=18/19
9 format(6)
10 disp(a," (alpha_dc)=(beta_dc)/(1+(beta_dc))=18/(1+18)
      =")
```

---

#### Scilab code Exa 8.7 alpha and beta and V0 and output power

```
1 //example8.7
2 clc
3 disp("V_m= Peak value of input =200 V")
4 disp("V_BO=100 V with I_G=2 mA and R_L=100 ohm")
5 a=asind(1/2)
6 disp(a," i) Firing angle alpha(in degree)=sinh((V_BO)
      /(V_m))=sinh(100/200)=")
7 a=180-30
8 disp(a," ii) Conduction angle beta = 180-(alpha) =")
9 v=(200*(1+cosd(30)))/(2*%pi)
10 format(7)
11 disp(v," iii) Average output voltage (V_dc)=(V_m*(1+
      cos30))/(2*pi)=")
12 p=(59.39^2)/100
13 format(8)
```

```
14 disp(p, "(P_dc(av)) [in W]=(V_dc^2)/R_L=")
```

---

#### Scilab code Exa 8.8 firing angle

```
1 //example8.8
2 clc
3 disp("(V_dc(av))=80 V, (V_rms)=230 V")
4 disp("Note that given ac mains voltage is rms unless
      and otherwise specified to be peak")
5 v=230*sqrt(2)
6 format(8)
7 disp(v, "Therefore, V_m(in V)=sqrt(2)*(V_rms)=")
8 disp("Now, (V_dc(av))=(V_m*(1+cos(alpha)))/(2*pi)")
9 disp("Therefore, 80=(325.269*(1+cos(alpha)))/(2*pi)"
      )
10 disp("Therefore, cos(alpha)=0.5453")
11 c=acosd(0.5453)
12 format(6)
13 disp(c, "Therefore, alpha(in degree)=")
```

---

#### Scilab code Exa 8.9 time for SCR remains off

```
1 //example8.9
2 clc
3 disp("For half wave rectifier, the SCR operates as
      shown in the Fig. 8.63.")
4 disp("V_in = 325*sin(wt)=V_m*sin(wt)")
5 disp("Therefore, V_m = 325 V")
6 disp("w=100*pi rad/sec")
7 disp("V_BO=125 V")
8 a=sinh(125/325)
9 format(6)
10 disp(a, "Therefore, alpha=sinh(V_BO/V_m)=")
```



```
11 d=(22.619*%pi)/180
12 format(7)
13 disp(d," Therefore , alpha=(22.619*pi)/180 radian=")
14 t=0.3947/(100*%pi)
15 format(8)
16 disp(t," Therefore , Time of alpha(in sec)=alpha/w
    =0.3947/(100*pi)=")
17 disp("For this period SCR remains OFF in positive
    half cycle.")
18 disp("While for entire negative half cycle i.e. for
    pi radians (180 degree) it remains OFF. Thus
    corresponding time is (angle/w)")
19 a=1/100
20 disp(a," i.e. pi/(100*pi)[in sec]= ")
21 t=10+1.25
22 disp(t," Total time for which SCR is OFF(in msec) =
    10+1.25= ")
```

---

## Chapter 9

# Cathode Ray Oscilloscope

Scilab code Exa 9.1 time for electron

```
1 //example9.1
2 clc
3 disp("The arrangement is shown in the Fig. 9.2")
4 disp("Let x=0 at negative plate and x=2*10^-2 m at
   positive plate.")
5 disp("The E is constant and its magnitude is given
   by,")
6 e=10/(2*10^-2)
7 disp(e,"E(in V/m)=V/d=")
8 disp("The electron will move with constant
   acceleration as field is uniform,")
9 a=(1.6*500*10^-19)/(9.107*10^-13)
10 disp(a,"a_x(in m/sec^2)=(q*E)/m=")
11 disp("The velocity v_x is given by,")
12 disp("(v_x)=(a_x)*t+(V_ox) .. v_ox =0 as
   electron is at rest")
13 disp("and x=(1/2 *a_x *t^2)+(V_ox *t)+(x_o) ....(
   v_ox)=(x_o)=0")
14 x=(1/2)*8.7844*(10^13)*((1*10^-9)^2)
15 disp(x,"Therefore , x(in m)=(1/2)*8.7844*(10^13)
   *((1*10^-9)^2)=")
```

```

16 disp(" ii) When electron reaches to second plate , x
    =2*10^-2 m")
17 disp(" Therefore , x=(1/2)*(a_x)*t^2")
18 disp(" Therefore , 2*10^-2 = (1/2)*(8.7844*10^13)*t^2"
    )
19 disp(" Therefore , t^2 = 4.5535*10^-16")
20 t=sqrt(4.5535*10^-16)
21 format(15)
22 disp(t," Therefore , t(in sec)=")

```

---

#### Scilab code Exa 9.2 final velocity pf electron

```

1 //example9.2
2 clc
3 disp(" Initially electron is at rest and V=200 V")
4 disp(" Therefore , v(in m/sec)=sqrt(2*q*V/m)
    =(5.94*10^5)*sqrt(V)")
5 v=(5.94*10^5)*sqrt(200)
6 format(8)
7 disp(v,"= (5.94*10^5)*sqrt(200) = ")

```

---

#### Scilab code Exa 9.4 velocity and deflection and deflection sensitivity

```

1 //example9.4
2 clc
3 disp(" d=1 cm, L=33 cm, l=4.5 cm, (V_a)=300 V, (V_d)
    =50 V")
4 v=sqrt((2*1.6*300*10^-19)/(9.107*10^-31))
5 format(9)
6 disp(v," i) (v_ox [in m/s])=sqrt(2*q*(V_a)/m)=sqrt
    ((2*1.6*300*10^-19)/(9.107*10^-31))=")
7 d=((4.5*10^-2)*(33*10^-2)*50)/(2*300*10^-2)
8 format(7)

```

```

9 disp(d," ii) D(in m)=(l*L*(V_d))/(2*d*V_a)= ")
10 s=0.1237/50
11 format(9)
12 disp(s," iii) S(in m/V)=D/(V_d)= ")

```

---

### Scilab code Exa 9.7 speed of electron and force on electron

```

1 //exmaple9.7
2 clc
3 disp("phi=8 degree , l=3 cm, B=0.6 mT=0.6*10^-3 Wb/m
      ^2")
4 disp("a) phi=(l*q*B)/(m*v) where v= velocity of
      electrons")
5 disp("But phi must be in radians")
6 p=(8*%pi)/180
7 format(7)
8 disp(p," Therefore , phi=8 degree=(8*pi)/180 radians=
      ")
9 disp(" Therefore , 0.1396 = ((3*10^-2)*(1.6*10^-19)
      *(0.6*10^-3))/(9.107*10^-31 *v)")
10 v=((3*10^-2)*(1.6*10^-19)*(0.6*10^-3))
      /(0.1396*9.107*10^-31)
11 format(9)
12 disp(v," Therefore , v(in m/s)=")
13 disp("b) f_m(in N) = (B*q*v) = force on each
      electron")
14 f=(0.6*10^-3)*(1.6*10^-19)*(22.65*10^6)
15 disp(f,"= (0.6*10^-3)*(1.6*10^-19)*(22.65*10^6) = ")

```

---

### Scilab code Exa 9.8 amplitude and rms value

```

1 //example9.8
2 clc

```

```

3 disp("It can be observed that the screen is divided
      such that one part is subdivided into 5 units.")
4 disp("Therefore , 1 subdivision = 1/5 = 0.2 units")
5 disp("It can be observed that positive peak of
      signal corresponds to two full divisions and
      three subdivisions. Hence positive peak is
      2+3*0.2=2.6 units while the negative peak also
      corresponds to 2.6 units.")
6 v=2.6+2.6
7 disp(v,"Therefore , (V_pp)[in divisions]=Peak to peak
      =2.6+2.6=")
8 v=5.2*2*10^-3
9 disp(v,"Therefore , (V_pp)[in V]=Number of divisions*
      volts/divisions=")
10 a=10.4/2
11 disp(a,"Therefore , (V_m)[in mV]=Amplitude=(V_pp)/2=")
12 v=5.2/(sqrt(2))
13 format(8)
14 disp(v,"and , (V_RMS)[in mV]= (V_m)/sqrt(2)=")

```

---

#### Scilab code Exa 9.10 phase difference

```

1 //example9.10
2 clc
3 disp("It can be observed from the Lissajous figures
      that ,")
4 disp("(y_1)=8 units      and ,      (y_2)=10 units")
5 s=asind(8/10)
6 format(6)
7 disp(s,"Therefore , phi (in degree)= asind((y_1)/(y_2
      ))=asind(8/10)=")

```

---

**Scilab code Exa 9.11** unknown frequency of vertical signal

```
1 //example9.11
2 clc
3 disp("It can be observed that,")
4 disp("Number of vertical tangencies = 2")
5 disp("Number of horizontal tangencies = 5")
6 disp("Now, (f_v/f_H) = 5/2")
7 disp("Therefore, f_v = 5/2")
8 disp("f_H = 5/2 * 1 kHz")
9 f=5/2
10 disp(f,"Therefore, f_v (in kHz)=")
11 disp("This is the unknown frequency.")
```

---

**Scilab code Exa 9.12** deflection sensitivity and angle of deflection and velocity of beam

```
1 //example9.12
2 clc
3 disp("d=0.5 cm, L=20 cm, l=2 cm, (V_a)=1000 V, (V_d)
   =25 V")
4 d=((2*10^-2)*(20*10^-2)*25)/(2*0.5*1000*10^-2)
5 disp(d,"i) D(in m)=(l*L*(V_d))/(2*d*V_a)")
6 s=0.01/25
7 disp(s,"Therefore, S(in m/V)=D/(V_d)")
8 disp("ii) tan(theta)=(l*a_y)/(v_ox^2)")
9 a=((1.6*10^-19)*25)/((0.5*10^-2)*(9.107*10^-31))
10 format(9)
11 disp(a,"where, a_y(in m/s^2)=(q*v_d)/(d*m)= ")
12 v=sqrt((2*1.6*1000*10^-19)/(9.107*10^-31))
13 disp(v,"v_ox(in m/s)=sqrt((2*q*V_a)/m)")
14 t=((2*10^-2)*(8.7844*10^14))/((18.745*10^6)^2)
15 format(5)
16 disp(t,"Therefore, tan(theta)=t=((2*10^-2)
   *(8.7844*10^14))/((18.745*10^6)^2)= ")
```

```

17 a=atand(0.05)
18 format(6)
19 disp(a,"Therefore , theta(in degree)= ")
20 format(9)
21 disp(v,"iii) (v_ox)= Velocity of electrons -
      Velocity of beam =")

```

---

#### Scilab code Exa 9.15 time for electron

```

1 //example9.15
2 clc
3 disp("The arrangement is shown in the fig. 9.19")
4 disp("Negative plate is at x=0")
5 disp("Therefore , Positive plate is at x=1*10^-2 m")
6 disp("E=V/d=1000/(1*10^-2)      ...d= 1*10^-2 m")
7 e=1000/(10^-2)
8 disp(e,"Therefore , E(in V/m)=")
9 disp("As field is uniform , the electron will move
      with constant acceleration.")
10 disp("Therefore , x = (1/2)*(a_x)*(t^2)")
11 a=((1.6*10^-19)*(1*10^5))/(9.107*10^-31)
12 disp(a,"where , a_x(in m/s^2)=(q*E)/m=")
13 disp("So time for electron to reach positive plate is
      ,")
14 disp("(t^2)=(2*x)/(a_x)=(2*1*10^-2)/(1.7568*10^16)")
15 t=sqrt((2*1*10^-2)/(1.7568*10^16))
16 disp(t,"Therefore , t(in s)=")

```

---

#### Scilab code Exa 9.16 deflection sensitivity

```

1 //example9.16
2 clc
3 disp("l=2 cm, d=4 mm, L=25 cm")

```

```

4 disp("S=D/(V_d)=(l*L)/(2*d*V_a) m/V      ... Deflection
      sensitivity")
5 disp(" i) V_a=1000 V")
6 s=((2*10^-2)*(25*10^-2))/(2*4*1000*10^-3)
7 disp(s," Therefore , S(in m/V)=((2*10^-2)*(25*10^-2))
      /(2*4*1000*10^-3)= ")
8 disp(" ii) V_a=2000 V")
9 s=((2*10^-2)*(25*10^-2))/(2*4*2000*10^-3)
10 disp(s," Therefore , S(in m/V)=((2*10^-2)*(25*10^-2))
      /(2*4*2000*10^-3)= ")
11 disp(" iii) V_a=3500 V")
12 s=((2*10^-2)*(25*10^-2))/(2*4*3500*10^-3)
13 disp(s," Therefore , S(in m/V)=((2*10^-2)*(25*10^-2))
      /(2*4*13500*10^-3)= ")

```

---

#### Scilab code Exa 9.17 time taken by electron

```

1 //example9.17
2 clc
3 disp("D=5 mm, V=250V, v_ox=1*10^6 m/s")
4 e=250/(5*10^-3)
5 disp(e,"E(in V/m)=V/d=")//answer in text book is
      wrong
6 a=((1.6*10^-19)*(50*10^3))/(9.107*10^-31)
7 disp(a," a_x(in m/s^2)=(q*E)/m=")
8 disp("Now, x= (1/2)*(a_x)*(t^2)+(V_ox)*t+(x_o) but
      (x_o)=0 initially")
9 disp(" Therefore , x= (1/2)*(a_x)*(t^2)+(V_ox)*t")
10 disp("When electron reaches to anode, x=5 mm.")
11 disp(" Therefore , (5*10^-3)=(1/2)*(8.7844*10^15)*(t
      ^2)+(1*10^6)*t")
12 disp(" Therefore , t(in sec)=9.5916D-10      ...
      neglecting negative value")
13 disp("Thus time taken by electron to reach anode
      from cathode is 0.95916 ns.")

```



---

**Scilab code Exa 9.18** input voltage

```
1 //example9.18
2 clc
3 disp("l=2 cm, d=5 mm, L=30 cm, V_a=2000 V, D=3 cm")
4 disp("D=(l*L*V_d)/(2*d*V_a)")
5 disp("i.e. (3*10^-2)=((2*10^-2)*(30*10^-2)*(V_d))
        /((2*5*10^-3)*2000)")
6 v=((3*10^-2)*(2*5*10^-3)*2000)/((2*10^-2)*(30*10^-2)
   )
7 disp(v,"Therefore , V_d(in V)=")
8 disp("But it is applied through amplifier of gain
        100")
9 g=100/100
10 disp(g,"Therefore , Input voltage required = (V_d)/
        gain = 100/100 =")
```

---

**Scilab code Exa 9.19** beam velocity and deflection sensitivity and deflection factor

```
1 //example9.19
2 clc
3 disp("l=1.5 cm, d=5 mm, L=50 cm, V_a=2000 V")
4 v=sqrt((2*2000*1.6*10^-19)/(9.107*10^-31))
5 disp(v,"1. v_ox(in m/s)=Beam velocity=sqrt((2*q*V_a
        )/m)=")
6 s=((1.5*10^-2)*(50*10^-2))/((2*5*10^-3)*2000)
7 disp(s,"S(in m/V)=D/(V_d)=(l*L)/(2*d*V_a)=")
8 g=1/(3.75*10^-4)
9 disp(g,"G(in V/m)=1/S=")
```

---