

Scilab Textbook Companion for  
Basics Of Electrical Engineering  
by S. Sharma<sup>1</sup>

Created by  
Arundhati Yadava  
B.Tech  
Electrical Engineering  
School of Engineering, JRE Group of Institutions  
College Teacher  
Mr. Abrar Ahmad  
Cross-Checked by

October 26, 2016

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Basics Of Electrical Engineering

**Author:** S. Sharma

**Publisher:** I. K. International Publishing House, New Delhi

**Edition:** 2

**Year:** 2008

**ISBN:** 978-81-906942-5-4

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 DC Circuit Analysis and Network Theorems</b>	<b>5</b>
<b>2 Steady State Analysis of Single Phase AC Circuit</b>	<b>73</b>
<b>3 Three Phase AC Circuits</b>	<b>140</b>
<b>4 Measuring Instruments</b>	<b>158</b>
<b>6 Magnetic Circuits</b>	<b>169</b>
<b>7 Single Phase Transformer</b>	<b>179</b>
<b>8 Direct Current Machines</b>	<b>248</b>
<b>10 Three Phase Induction Machines</b>	<b>293</b>
<b>11 Single Phase Induction Motor</b>	<b>317</b>

# List of Scilab Codes

Exa 1.1	Independent loop equations . . . . .	5
Exa 1.2	Resistance between A and B . . . . .	6
Exa 1.3	Resistance between A and B . . . . .	7
Exa 1.4	Values of Rab Rcd and Rde . . . . .	8
Exa 1.5	Rac and Rbd . . . . .	10
Exa 1.6	Finding value of current by mesh analysis . . . . .	11
Exa 1.7	Source transformation . . . . .	12
Exa 1.8	Source transformation and mesh analysis . . . . .	14
Exa 1.9	Equivalent resistance . . . . .	15
Exa 1.10	Current through R3 using nodal analysis . . . . .	16
Exa 1.11	Current through R3 using mesh analysis . . . . .	17
Exa 1.12	Current through R3 using superposition theorem . . . . .	18
Exa 1.13	Current through R3 using Thevenin theorem . . . . .	19
Exa 1.14	Current through R3 using Norton theorem . . . . .	20
Exa 1.15	To find Vx by mesh analysis . . . . .	21
Exa 1.16	To find Vx by nodal analysis . . . . .	22
Exa 1.17	To find Vx by Superposition theorem . . . . .	23
Exa 1.18	To find Vx by Thevenin theorem . . . . .	24
Exa 1.19	To find Vx by Norton theorem . . . . .	25
Exa 1.20	To find I using Norton theorem . . . . .	27
Exa 1.21	To find I using Thevenin theorem . . . . .	28
Exa 1.22	To find I using mesh analysis . . . . .	29
Exa 1.23	To find I using nodal analysis . . . . .	30
Exa 1.24	To find I using Superposition theorem . . . . .	32
Exa 1.25	To find I using mesh analysis . . . . .	33
Exa 1.26	To find I using nodal analysis . . . . .	34
Exa 1.27	To find I using Thevenin theorem . . . . .	34
Exa 1.28	To find I using Norton theorem . . . . .	35

Exa 1.29	To find I using Superposition theorem . . . . .	36
Exa 1.30	Source transformation and mesh and nodal methods . . . . .	37
Exa 1.31	Delta to star transformation . . . . .	39
Exa 1.32	To find I through 1 ohm by mesh analysis . . . . .	40
Exa 1.33	To find I through 1 ohm R by nodal analysis . . . . .	41
Exa 1.34	To find I through 1 ohm R by Superposition theorem . . . . .	43
Exa 1.35	To find I through 1 ohm by Thevenin theorem . . . . .	45
Exa 1.36	To find I through 1 ohm R by Norton theorem . . . . .	46
Exa 1.37	To calculate Vab by Thevenin and Norton theorem . . . . .	47
Exa 1.38	Thevenin and Norton equivalent . . . . .	49
Exa 1.39	Delta to star transformation to find I . . . . .	50
Exa 1.40	Currents in different branches . . . . .	51
Exa 1.41	Current when resistance is connected across AB . . . . .	52
Exa 1.42	Thevenin and Nodal analysis . . . . .	53
Exa 1.43	Superposition theorem . . . . .	55
Exa 1.44	Determination of voltage . . . . .	56
Exa 1.45	value of resistance . . . . .	56
Exa 1.46	Resistance of metal filament lamp . . . . .	57
Exa 1.47	Copper wire and platinum silver wire . . . . .	58
Exa 1.48	Cells B1 and b2 . . . . .	59
Exa 1.49	Values of R1 and R2 . . . . .	60
Exa 1.50	Currents i1 and i2 . . . . .	62
Exa 1.51	Currents in all branches . . . . .	62
Exa 1.52	Thevenin theorem and Norton theorem . . . . .	63
Exa 1.53	Thevenin equivalent circuit . . . . .	65
Exa 1.54	Thevenin theorem . . . . .	66
Exa 1.55	Nodal analysis . . . . .	67
Exa 1.56	Delta values . . . . .	68
Exa 1.57	Superposition theorem to find I . . . . .	69
Exa 1.58	Thevenin or Norton theorem . . . . .	70
Exa 1.59	Mesh analysis . . . . .	71
Exa 2.1	Form factor of sine wave . . . . .	73
Exa 2.3	Average and rms value . . . . .	74
Exa 2.4	Vav and Vrms . . . . .	74
Exa 2.5	Fluorescent lamp . . . . .	75
Exa 2.6	Single phase motor . . . . .	76
Exa 2.7	Apparent power of 300 kVA . . . . .	77
Exa 2.8	Two element series circuit . . . . .	78

Exa 2.9	120 V 100 W lamp . . . . .	79
Exa 2.10	Current and power drawn . . . . .	80
Exa 2.11	To calculate parameters of coil and power factor . . . . .	81
Exa 2.13	Current in load in rectangular form . . . . .	82
Exa 2.14	To find frequency and current elements . . . . .	83
Exa 2.15	Choke coil takes current of 2 Amperes . . . . .	85
Exa 2.16	Two coils of 5 ohm and 10 ohm connected in parallel . . . . .	86
Exa 2.17	AC voltage applied to series RC circuit . . . . .	89
Exa 2.18	Non inductive resistance of 10 ohm . . . . .	91
Exa 2.19	Admittance in each parallel branch . . . . .	92
Exa 2.20	Resonant frequency and band width . . . . .	94
Exa 2.22	Series RLC circuit . . . . .	95
Exa 2.23	An alternating current of frequency of 50 Hertz . . . . .	97
Exa 2.24	RMS value average value and form factor . . . . .	98
Exa 2.25	50 Hz sinusoidal voltage wave shape . . . . .	99
Exa 2.26	Sinusoidal alternating current of frequency 25 Hz . . . . .	100
Exa 2.27	Impedance resistance reactance and power factor of the circuit . . . . .	101
Exa 2.28	Total impedance current drawn from the supply . . . . .	103
Exa 2.29	An alternating current of frequency of 60 Hertz . . . . .	105
Exa 2.30	An alternating current with RMS value of 20 A . . . . .	106
Exa 2.31	Significance of RMS and average values of wave . . . . .	107
Exa 2.32	Average value effective value and form factor . . . . .	108
Exa 2.33	Three coils of resistances . . . . .	109
Exa 2.34	To draw the vector diagram . . . . .	110
Exa 2.35	Total impedance and total current . . . . .	111
Exa 2.36	Total current taken from supply . . . . .	113
Exa 2.37	Current taken by each branch . . . . .	114
Exa 2.38	To solve example 27 by j method . . . . .	116
Exa 2.39	To draw the complete vector diagram . . . . .	116
Exa 2.40	Power factor and average power delivered to the circuit	118
Exa 2.41	100 V 60 W lamp . . . . .	119
Exa 2.42	Three sinusoidally alternating currents . . . . .	121
Exa 2.43	Resultant current wave made up of two components . . . . .	122
Exa 2.44	To find power consumed by the circuit . . . . .	123
Exa 2.45	Quality factor and bandwidth . . . . .	124
Exa 2.46	To find power consumed and reactive power . . . . .	125
Exa 2.47	RL series circuit . . . . .	127

Exa 2.48	Power factor of the combination . . . . .	128
Exa 2.49	kVA and kW in each branch circuit and in the main circuit . . . . .	130
Exa 2.50	Current in each branch when total current is 20 A . .	132
Exa 2.51	Admittance and impedance of the circuit . . . . .	133
Exa 2.52	Total impedance and current in each branch . . . . .	134
Exa 2.53	Total impedance and power taken . . . . .	137
Exa 2.54	Q factor at resonance . . . . .	138
Exa 3.1	Identical impedances each consisting of 15 ohm in series	140
Exa 3.2	Resistance and reactance values of each impedance . .	141
Exa 3.3	Three similar coils each of 30 ohms . . . . .	142
Exa 3.4	Line and phase current when phase sequence is positive	144
Exa 3.5	Power measurement by 2 wattmeter method . . . . .	146
Exa 3.6	3300 V synchronous alternator . . . . .	147
Exa 3.7	Three phase star connected system . . . . .	149
Exa 3.8	Balanced delta connection . . . . .	150
Exa 3.9	400 V 50 Hz three phase supply . . . . .	151
Exa 3.11	Balanced load of 20kVA . . . . .	153
Exa 3.12	Three identical impedances each having a resistance R	156
Exa 4.1	Deflecting torque exerted on a coil . . . . .	158
Exa 4.2	Current through galvanometer . . . . .	159
Exa 4.3	Resistance of wire . . . . .	159
Exa 4.4	Resistance required to read current and voltage . . .	160
Exa 4.5	Number of revolutions made by energy meter and percentage error . . . . .	161
Exa 4.6	Series resistance to measure 500 V on full scale . . .	162
Exa 4.7	Percentage error of energy meter . . . . .	163
Exa 4.8	Resistance required to read current and voltage . . .	164
Exa 4.9	Percentage error of meter . . . . .	164
Exa 4.10	Readings of two voltmeters . . . . .	165
Exa 4.11	Readings of two voltmeters with different internal resistances . . . . .	166
Exa 4.12	Total current carried by two ammeters . . . . .	167
Exa 6.1	Magnetic circuit having two air gaps . . . . .	169
Exa 6.2	Steel ring of 25 cm mean diameter . . . . .	171
Exa 6.3	Magnetic circuit with cast steel core . . . . .	173
Exa 6.4	Iron ring made of round iron rod . . . . .	174
Exa 6.5	Ring made of composite material . . . . .	176

Exa 7.1	To calculate magnetizing component of no load current	179
Exa 7.2	To calculate the primary current . . . . .	180
Exa 7.3	To find the voltage regulation . . . . .	182
Exa 7.4	10 kVA transformer . . . . .	184
Exa 7.5	Transformer with 350 primary and 1050 secondary turns	186
Exa 7.6	Primary current and power factor . . . . .	187
Exa 7.8	Efficiency of transformer . . . . .	188
Exa 7.9	Core loss current of distribution transformer . . . . .	191
Exa 7.10	Number of turns on HT and LT sides . . . . .	192
Exa 7.11	To calculate primary and full load currents . . . . .	193
Exa 7.12	Magnetising component of no load current . . . . .	194
Exa 7.13	Current taken by primary . . . . .	196
Exa 7.14	To calculate total resistance and reactance referred to primary . . . . .	197
Exa 7.15	To calculate percent regulation at full load . . . . .	199
Exa 7.16	Maximum value of percent regulation . . . . .	200
Exa 7.17	200 kVA transformer with 1000 W iron loss and 2000 W copper loss at full load . . . . .	202
Exa 7.18	To calculate all day efficiency . . . . .	203
Exa 7.19	Open circuit and short circuit test . . . . .	205
Exa 7.20	4kVA 200 400 V transformer . . . . .	207
Exa 7.21	To determine the regulation while supplying full load	209
Exa 7.22	Total equivalent resistance referred to primary and secondary . . . . .	210
Exa 7.23	33 kVA 2200 220 V 50 Hz transformer . . . . .	211
Exa 7.24	To calculate secondary terminal voltage . . . . .	214
Exa 7.25	15 kVA 2200 110 V transformer . . . . .	216
Exa 7.26	Open circuit and short circuit test . . . . .	219
Exa 7.27	Open and short circuit test . . . . .	221
Exa 7.28	Open and short circuit test . . . . .	223
Exa 7.29	200 kVA 4000 1000 V transformer . . . . .	227
Exa 7.30	Secondary terminal voltage at full load . . . . .	229
Exa 7.31	To calculate the value of maximum flux density in the core and the emf . . . . .	230
Exa 7.32	To calculate total copper loss . . . . .	231
Exa 7.33	No load and short circuit results of transformer . . . . .	233
Exa 7.34	50 kVA transformer of 5 is to 1 ratio of turns . . . . .	235
Exa 7.35	No load and short circuit results of transformer . . . . .	237

Exa 7.36	Value of load for maximum efficiency . . . . .	239
Exa 7.37	To calculate regulation at full load . . . . .	240
Exa 7.38	Total no load loss . . . . .	242
Exa 7.39	Percentage of hysteresis and copperloss . . . . .	243
Exa 7.40	To draw the phasor diagram . . . . .	245
Exa 7.41	Star connected auto transformer . . . . .	246
Exa 8.1	Generated emf . . . . .	248
Exa 8.2	Ratio of speed . . . . .	249
Exa 8.3	Armature induced emf and developed torque and efficiency . . . . .	250
Exa 8.4	Armature resistance and load current at maximum efficiency . . . . .	251
Exa 8.5	BHP of prime mover . . . . .	252
Exa 8.6	20 HP 230 V 1150 rpm shunt motor . . . . .	254
Exa 8.7	New operating speed . . . . .	255
Exa 8.8	250 V DC shunt machine . . . . .	256
Exa 8.9	Torque developed in the motor . . . . .	258
Exa 8.10	6 pole DC machine with 400 conductors . . . . .	259
Exa 8.11	Total emf generated in the armature . . . . .	261
Exa 8.12	Terminal voltage of the machine . . . . .	262
Exa 8.13	Current in each conductor and emf generated . . . . .	263
Exa 8.14	Armature resistance and load current at maximum efficiency . . . . .	264
Exa 8.15	Full load speed . . . . .	265
Exa 8.16	250 V 4 pole shunt motor . . . . .	266
Exa 8.17	200 V DC shunt motor . . . . .	267
Exa 8.18	Value of inserted resistance . . . . .	269
Exa 8.19	New speed of motor on inserting a 250 ohm resistance . . . . .	270
Exa 8.20	Reduction of main flux to raise the speed by 50 percent . . . . .	271
Exa 8.21	10 kW 6 pole DC generator . . . . .	272
Exa 8.22	Shunt wound motor running at 600 rpm from a 230 V supply . . . . .	274
Exa 8.23	Value of inserted resistance in field circuit for increasing the speed . . . . .	275
Exa 8.24	New speed of motor on inserting a 250 ohm resistance in the field circuit . . . . .	276
Exa 8.25	24 slot 2 pole DC machine . . . . .	277
Exa 8.27	Counter emf of motor and power developed in armature . . . . .	279

Exa 8.28	Voltage between far end of feeder and bus bar . . . . .	280
Exa 8.29	Speed of motor when connected in series with 5 ohm resistance . . . . .	281
Exa 8.30	Value of starting torque . . . . .	281
Exa 8.31	Value of speed when flux is increased by 20 percent . .	282
Exa 8.32	250 V series motor with 20 A current and 1000 rpm . .	283
Exa 8.33	Resistance to be added to obtain rated torque at starting and at 1000 rpm . . . . .	285
Exa 8.34	Total emf and armature current . . . . .	286
Exa 8.35	Armature current and induced emf . . . . .	287
Exa 8.36	Constant losses and full load efficiency . . . . .	288
Exa 8.37	Hysteresis and eddy current losses . . . . .	290
Exa 8.38	Speed of motor when flux per pole is increased by 10 percent . . . . .	291
Exa 10.2	6 pole wound rotor induction motor . . . . .	293
Exa 10.3	3 phase induction motor running at 1140 rpm . . . . .	296
Exa 10.4	3 phase squirrel cage motor . . . . .	298
Exa 10.5	Speed of motor . . . . .	299
Exa 10.6	Speed of 4 pole induction motor . . . . .	300
Exa 10.7	4 pole 3 phase induction motor . . . . .	301
Exa 10.8	3 phase induction motor with synchronous speed 1200 rpm . . . . .	302
Exa 10.9	150 kW 6 pole star connected induction motor . . . . .	304
Exa 10.10	6 pole 60 Hz induction motor . . . . .	305
Exa 10.11	4 pole induction motor . . . . .	306
Exa 10.12	3 phase 440 V distribution . . . . .	307
Exa 10.13	3 phase 50 Hz induction motor . . . . .	309
Exa 10.14	10 kW 400 V delta connected induction motor . . . . .	311
Exa 10.15	4 pole 3 phase SRIM . . . . .	313
Exa 10.16	3 phase induction motor . . . . .	314
Exa 11.1	Shaft torque . . . . .	317
Exa 11.2	Slip and resistance in forward and backward direction	318

# Chapter 1

## DC Circuit Analysis and Network Theorems

**Scilab code Exa 1.1** Independent loop equations

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 1  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 1");  
7  
8 //VARIABLE INITIALIZATION  
9 b=14; //number of branches  
10 n=8; //number of nodes  
11  
12 //SOLUTION  
13 m=b-n+1; //number of loop  
equations  
14 disp(sprintf("The total number of independent loop  
equations are %d",m));  
15  
16 //END
```

---

### Scilab code Exa 1.2 Resistance between A and B

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 2  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 2");  
7  
8 //VARIABLE INITIALIZATION  
9 // star values ra , rc and rd  
10 ra=2; //in Ohms  
11 rc=4; //in Ohms  
12 rd=3; //in Ohms  
13 r1=5; //in Ohms  
14 r2=4; //in Ohms  
15 r3=6; //in Ohms  
16  
17 //SOLUTION  
18 //converting star with points A, C and D into delta  
ACD  
19 r=(ra*rc)+(rc*rd)+(rd*ra); // 'r' is the  
resistance that appears in the numerator of the  
equation of star-delta conversion  
20  
21 //delta values rac , rcd and rad  
22 rac=r/rd;  
23 rcd=r/ra;  
24 rad=r/rc;  
25 req1=(r1*rad)/(r1+rad); // equivalent  
resistance between A and D  
26 req2=(r2*rcd)/(r2+rcd); // equivalent  
resistance between C and D
```

```

27 req3=req1+req2;           // series combination
    of resistors
28 req4=(req3*rac)/(req3+rac); // parallel
    combination of resistors
29 req5=req4+r3;
30 req6=(req5*7)/(req5+7);
31 disp(sprintf("The equivalent resistance between
    points A and B is %f ",req6));
32
33 //END

```

---

### Scilab code Exa 1.3 Resistance between A and B

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 3
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 r1=4.6;                      // in Ohms
10 r2=7.6;                     // in Ohms
11
12
13 // star values
14 rc=3;
15 rd=7;
16 re=5;
17
18 //SOLUTION
19 //converting star with points C, D and E to delta
    CDE
20 r=(rc*rd)+(rd*re)+(re*rc);   // 'r' is the

```

```

        resistance that appears in the numerator of the
        equation of star-delta conversion
21
22 //delta values rcd , rde and rec
23 rcd=r/re;
24 rde=r/rc;
25 rec=r/rd;
26 req1=(8*rec)/(8+rec);           // equivalent
        resistance between C and E
27 req2=(6*rde)/(6+rde);         // equivalent
        resistance between D and E
28 req3=(4*rcd)/(4+rcd);         // equivalent
        resistance between C and D
29 req4=req2+req3;
30 req5=(req1*req4)/(req1+req4); // parallel
        combination of resistors
31 req6=req5+r1;                // series combination
        of resistors
32 req7=(req6*r2)/(req6+r2);
33 disp(sprintf("The equivalent resistance between
        points A and B is %f    ",req7));
34
35 //END

```

---

### Scilab code Exa 1.4 Values of Rab Rcd and Rde

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 4
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION

```

```

9 r1=1;                                //LHS resistance in
   Ohms
10 r2=2;                                 //in Ohms
11 r3=3;                                 //in Ohms
12 r4=4;                                 //in Ohms
13 r5=5;                                 //in Ohms
14 r6=6;                                 //in Ohms
15 r7=7;                                 //in Ohms
16 r8=8;                                 //RHS resistance in
   Ohms
17
18 //SOLUTION
19
20 //To find resistance between a and b
21 req1=r1+r2;                           //series combination
   of resistors
22 req2=(req1*r3)/(req1+r3);            //parallel combination
   of resistors
23 req3=req2+(r4+r5);
24 req4=(req3*r6)/(req3+r6);
25 req5=req4+r7;
26 req6=(req5*r8)/(req5+r8);
27 disp(sprintf("The equivalent resistance between
   points a and b is %f ",req6));
28
29 //To find resistance between c and d
30 req7=r7+r8;
31 req8=(req7*r6)/(req7+r6);
32 req9=req2+r5+req8;
33 req10=(req9*r4)/(req9+r4);
34 disp(sprintf("The equivalent resistance between
   points c and d is %f ",req10));
35
36 //To find resistance between d and e
37 req11=req2+r4+r5;
38 req12=(req11*r6)/(req11+r6);
39 req13=(req12*req7)/(req12+req7);
40 disp(sprintf("The equivalent resistance between

```

```
    points d and e is %f    ",req13));  
41  
42 //END
```

---

### Scilab code Exa 1.5 Rac and Rbd

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 5  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 5");  
7  
8 //VARIABLE INITIALIZATION  
9 r1=2;                                //in Ohms  
10 r2=4;                                 //in Ohms  
11 r3=8;                                 //in Ohms  
12 r4=8;                                 //in Ohms  
13 r5=2;                                 //middle resistance in  
                                         Ohms  
14  
15 //SOLUTION  
16  
17 //To find resistance between a and c  
18 req1=r1+r2;  
19 req2=r1+r4;  
20 req3=(req1*r1)/(req1+r1);  
21 rac=(req3*req2)/(req3+req2);  
22 disp(sprintf("The equivalent resistance between  
points a and c is %f    ",rac));  
23  
24 //To find resistance between b and d  
25 //converting delta abc into star with points a, b  
                                         and c
```

```

26 //delta values
27 rab=r1;
28 rbc=r2;
29 rac=6;
30 //star values
31 r=rab+rbc+rac;           // 'r' is the resistance
                            that appears in the denominator of the equation
                            of delta-star conversion
32 ra=(rab*rbc)/r;
33 rb=(rab*rac)/r;
34 rc=(rbc*rac)/r;
35 req5=rb+rac;
36 req6=rc+8;
37 rbd=ra+((req5*req6)/(req5+req6));
38 disp(sprintf("The equivalent resistance between
points b and d is %f ",rbd));
39
40 //END

```

---

**Scilab code Exa 1.6** Finding value of current by mesh analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
THEOREMS
2 //Example 6
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 n=4;                           // number of
                                 nodes
10 b=6;                          // number of
                                 branches
11

```

```

12 //SOLUTION
13 m=b-n+1;                                // number of
   mesh equations
14 disp(sprintf("Number of mesh equations are %d",m));
15 nd=n-1;                                  //number of
   node equations
16 disp(sprintf("Number of node equations are %d",nd));
17
18 // (5/2) I1 + (-2) I2 + (-1/2) I3 = 4.....eq (1)
19 // (0) I1 + (0) I2 + (1) I3 = -2 .....eq (2)
20 // (-2) I1 + (10/3) I2 + (-1/3) I3 = 0....eq (3)
21 //using matrix method to solve the set of equations
22 A=[5/2 -2 -1/2;-2 10/3 -1/3;0 0 1];
23 b=[4;0;-2];
24 x=inv(A)*b;
25 I=x(1,:);                               //to access
   the 1st element of 3X1 matrix
26 disp(sprintf("The current from the source Vs is %d A
   ",I));
27
28 //END

```

---

### Scilab code Exa 1.7 Source transformation

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 7
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 I1=1;                                     // current source in
   Amperes

```

```

10 v1=4;                                // voltage source in
   Volts
11 v2=3;                                // voltage source in
   Volts
12 v3=6;                                // voltage source in
   Volts
13 r1=2;                                // resistance in Ohms
14 r2=2;                                // resistance in Ohms
15 r3=1;                                // resistance in Ohms
16 r4=3;                                // resistance in Ohms
17
18 //SOLUTION
19 //converting all the voltage sources into current
   sources
20 I2=v1/r1;
21 I3=v2/r3;
22 I4=v3/r4;
23 disp(sprintf("The four current sources are %d A, %d
   A, %d A and %d A",I1,I2,I3,I4));
24
25 req1=(r1*r2)/(r1+r2);                // parallel
   combination of resistors
26 req2=(r3*r4)/(r3+r4);
27 v2=(I1+I4)*req1;
28 v3=(I3-I2)*req2;
29 req=req1+req2;
30 v=v2+v3;
31 I=v/req;
32 disp("VOLTAGE EQUIVALENT CIRCUIT:");
33 disp(sprintf("    Voltage source= %f V",v));
34 disp(sprintf("    Equivalent resistance(in series)=
   %f ",req));
35 disp("CURRENT EQUIVALENT CIRCUIT:");
36 disp(sprintf("    Current source= %f A",I));
37 disp(sprintf("    Equivalent resistance(in parallel)=
   %f ",req));
38
39 //END

```

---

### Scilab code Exa 1.8 Source transformation and mesh analysis

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 8  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 8");  
7  
8 //VARIABLE INITIALIZATION  
9 I=2;                                // current source  
    in Amperes  
10 r1=1/2;                               //in Ohms  
11 r2=1/2;                               //in Ohms  
12  
13 //SOLUTION  
14 //the current source of 2A is converted into two 1V  
    sources  
15 v1=I*r1;  
16 v2=I*r2;  
17 disp(sprintf("The voltage sources after conversion  
    are %d V and %d V",v1,v2));  
18 //(5/2)I1+(-1)I2 = 0.....eq (1) // applying KVL in  
    mesh 1  
19 //(-1)I1+(7/2)I2 = 2.....eq (2) // applying KVL in  
    mesh 2  
20 //using matrix method to solve the set of equations  
21 A=[5/2 -1;-1 7/2];  
22 b=[2;2];  
23 x=inv(A)*b;  
24 x=x(2,:);  
25 disp(sprintf("The current in 2 resistor is %f A",x  
));
```

26  
27 //END

---

### Scilab code Exa 1.9 Equivalent resistance

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
  THEOREMS
2 //Example 9
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 r1=1;                                //in Ohms
10 r2=2;                                 //in Ohms
11 r3=3;                                 //in Ohms
12 r4=1;                                 //in Ohms
13
14 //SOLUTION
15
16 //delta values
17 rab=r1;                               //between points a
  and b
18 rac=r2;                               //between points a
  and c
19 rbc=r3;                               //between points b
  and c
20 //converting delta abc into star with points a, b and
  c
21 //star values ra, rb and rc
22 r=rab+rbc+rac;                      // 'r' is the
  resistance that appears in the denominator of the
  equation of delta-star conversion
23 ra=(rab*rac)/r;
```

```

24 rb=(rab*rbc)/r;
25 rc=(rbc*rac)/r;
26 req1=r1+r4;
27 req2=rb+r2;
28 req3=(req1*req2)/(req1+req2);
29 req4=ra+req3;
30 disp(sprintf("The equivalent input resistance is %f
               ",req4));
31
32 //END

```

---

### Scilab code Exa 1.10 Current through R3 using nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 10
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 v=10;                                // voltage source in
   Volts
10 I=5;                                  // current source in
    Amperes
11 r1=2;                                 // in Ohms
12 r2=2;                                 // in Ohms
13 r3=4;                                 // in Ohms
14
15 //SOLUTION
16 res=I+(v/r1);
17 v1=res/((1/r1)+(1/r2)+(1/r3));
18 I1=v1/r3;
19 disp(sprintf("By Nodal analysis , the current through

```

```
    resistor R3 is %d A",I1));  
20  
21 //END
```

---

**Scilab code Exa 1.11** Current through R3 using mesh analysis

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 11  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 11");  
7  
8 //VARIABLE INITIALIZATION  
9 I3=-5;                                // direction of  
                                         I3 is opposite to the current which flows from  
                                         the current source  
10  
11 //SOLUTION  
12  
13 // using mesh analysis , the following equations are  
obtained  
14 // (4) I1+(-2)I2 = 10..... eq (1)  
15 // (-2)I1+(6)I2 = -20..... eq (2)  
16 // solving the two equations using matrix method  
17 A=[4 -2; -2 6];  
18 b=[10; -20];  
19 x=inv(A)*b;  
20 I1=x(1,:);                            // to access 1st  
                                         element of 2X1 matrix  
21 I2=x(2,:);                            // to access 2nd  
                                         element of 2X1 matrix  
22 I=I2-I3;  
23 disp(sprintf("By mesh analysis , the current through
```

```
    resistor R3 is %d A" ,I));  
24  
25 //END
```

---

**Scilab code Exa 1.12** Current through R3 using superposition theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 12  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 12");  
7  
8 //VARIABLE INITIALIZATION  
9 v=10;                                //voltage source  
   in Volts  
10 I=5;                                  //current source  
    in Amperes  
11 r1=2;                                 //in Ohms  
12 r2=2;                                 //in Ohms  
13 r3=4;                                 //in Ohms  
14  
15 //SOLUTION  
16  
17 //deactivating current source  
18 v1=(v/r1)/((1/r1)+(1/r2)+(1/r3));  //using nodal  
   analysis  
19 I1=v1/r3;  
20  
21 //deactivating voltage source  
22 v2=I/((1/r1)+(1/r2)+(1/r3));        //using nodal  
   analysis  
23 I2=v2/r3;  
24 I_tot=I1+I2;                          //applying
```

```

25
26 Superposition Theorem (I1 and I2 are in same
27 direction)
28 disp(sprintf("By Superposition Theorem, the current
   through resistor R3 is %d A",I_tot));
29 //END

```

---

**Scilab code Exa 1.13** Current through R3 using Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 13
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 v=10;                                // voltage source in
   Volts
10 I=5;                                 // current source in
   Amperes
11 r1=2;                                // in Ohms
12 r2=2;                                // in Ohms
13 r3=4;                                // in Ohms
14
15 //SOLUTION
16 //solving by nodal analysis
17 res=I+(v/r1);                         // 'res' is used to
   make the calculation easy
18 vth=res/((1/r1)+(1/r2));              // Thevenin voltage
19 rth=(r1*r2)/(r1+r2);                  // Thevenin resistance
20 Ith=vth/(rth+r3);                    // Thevenin current
21 disp(sprintf("By Thevenin Theorem, the current

```

```
through resistor R3 is %d A",Ith));  
22  
23 //END
```

---

**Scilab code Exa 1.14** Current through R3 using Norton theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 14  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 14");  
7  
8 //VARIABLE INITIALIZATION  
9 v=10; // voltage source in  
Volts  
10 I3=-5; // current source in  
Amperes  
11 r1=2; // in Ohms  
12 r2=2; // in Ohms  
13 r3=4; // in Ohms  
14  
15 //SOLUTION  
16 //by loop analysis  
17 //(1) I1+(-1)I2 = 0..... eq (1)  
18 //(4) I1+(-2)I2 = 10..... eq (2)  
19 //solving the equations by matrix method  
20 A=[1 -1;4 -2];  
21 b=[0;10];  
22 x=inv(A)*b;  
23 I1=x(1,:); // to access 1st  
element of 2X1 matrix  
24 I2=x(2,:); // to access 2nd  
element of 2X1 matrix
```

```

25 In=I2-I3;
26 rn=(r1*r2)/(r1+r2);
27 I=(rn*In)/(rn+r3);
28 disp(sprintf("By Norton Theorem, the current through
    resistor R3 is %d A",I));
29
30 //END

```

---

**Scilab code Exa 1.15** To find Vx by mesh analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 15
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 v=7;                                // voltage source in
    Volts
10 I=7;                                 // current source in
    Amperes
11 r3=1;                                // in Ohms
12
13 //SOLUTION
14 //(1) I1+(-4)I2+(4)I3 = 7..... eq (1)
15 //(-1)I1+(6)I2+(-3)I3 = 0..... eq (2)
16 //(1)I1+(0)I2+(-1)I3 = 7..... eq (3)
17 //solving the equations by matrix method
18 A=[1 -4 4;-1 6 -3;1 0 -1];
19 b=[7;0;7];
20 x=inv(A)*b;
21 I1=x(1,:);                           //to access the 1st
    element of 3X1 matrix

```

```

22 I2=x(2,:);                                //to access the 2nd
      element of 3X1 matrix
23 I3=x(3,:);                                //to access the 3rd
      element of 3X1 matrix
24 vx=-(I3*r3);
25 disp(sprintf("By Mesh analysis , the value of Vx is
      %d V",vx));
26
27 //END

```

---

**Scilab code Exa 1.16** To find Vx by nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 16
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 16");
7
8 //VARIABLE INITIALIZATION
9 v=7;                                         // voltage source in
   Volts
10 I=7;                                         // current source in
    Amperes
11 r1=1;                                         //in Ohms
12 r2=2;                                         //in Ohms
13 r3=1;                                         //in Ohms
14 r4=2;                                         //in Ohms
15 r5=3;                                         //in Ohms
16
17 //SOLUTION
18 //(4)vb+(-1)vc = 0 ..... eq (1)
19 //(-2)vb+(11)vc = 21 ..... eq (2)
20 //solving the equations by matrix method

```

```

21 A=[4 -1;-2 11];
22 b=[0;21];
23 x=inv(A)*b;
24 vb=x(1,:); //to access the 1st
   element of 2X1 matrix
25 vc=x(2,:); //to access the 2nd
   element of 2X1 matrix
26 vx=-vc;
27 disp(sprintf("By Nodal analysis , the value of Vx is
    %d V",vx));
28
29 //END

```

---

**Scilab code Exa 1.17** To find Vx by Superposition theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 17
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 17");
7
8 //VARIABLE INITIALIZATION
9 v=7; // voltage source in
   Volts
10 I=7; // current source in
   Amperes
11 r1=1; //in Ohms
12 r2=2; //in Ohms
13 r3=1; //in Ohms
14 r4=2; //in Ohms
15 r5=3; //in Ohms
16
17 //SOLUTION

```

```

18
19 //deactivating the current source
20 res=(v/4)+(v/2);
21 vc=res/((1/4)+(1/r1)+(1/r2));
22 vx1=-vc;
23
24 //deactivating voltage source
25 //(4)va+(-1)vb = -21.....eq (1)
26 /(2)va+(-11)vb = 0.....eq (2)
27 //solving the equations by matrix method
28 A=[4 -1;2 -11];
29 b=[-21;0];
30 x=inv(A)*b;
31 va=x(1,:);                                //to access 1st
32 vb=x(2,:);                                //to access 2nd
33 vx2=-vb;
34 vx=vx1+vx2;
35 disp(sprintf("By Superposition Theorem, the value of
   Vx is %d V",vx));
36
37 //END

```

---

**Scilab code Exa 1.18** To find Vx by Thevenin theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 18
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 18");
7
8 //VARIABLE INITIALIZATION

```

```

9 v=7;                                // voltage source in
    Volts
10 I=7;                                // current source in
    Amperes
11 r1=1;                                //in Ohms
12 r2=2;                                //in Ohms
13 r3=1;                                //in Ohms
14 r4=2;                                //in Ohms
15 r5=3;                                //in Ohms
16
17 //SOLUTION
18 //solving by mesh analysis
19 I2=0;                                 //since mesh 2 is
    open
20 I1=I-I2;
21 I3=I1/6;                             //from the equation
    of mesh 3
22 vth=-(r2*I3)+v;                     //Thevenin voltage
23 r=r1+r5;                            //series combination
    of resistors
24 rth=(r*r4)/(r+r4);                  //parallel
    combination of resistors (Thevenin resistance)
25 I=vth/(rth+r3);                     //Thevenin current
26 vx=-I*r3;
27 disp(sprintf("By Thevenin Theorem , the value of Vx
    is %d V",vx));
28
29 //END

```

---

**Scilab code Exa 1.19** To find Vx by Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 19
3

```

```

4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 19");
7
8 //VARIABLE INITIALIZATION
9 v=7; // voltage source in
      Volts
10 I=7; // current source in
       Amperes
11 r1=1; //in Ohms
12 r2=2; //in Ohms
13 r3=1; //in Ohms
14 r4=2; //in Ohms
15 r5=3; //in Ohms
16
17 //SOLUTION
18 //by using mesh analysis , the following equations
   are obtained
19 // (1) I1+(-4)I2+(3)In = 7..... eq (1)
20 // (-1)I1+(6)I1+(-3)In = 0..... eq (2)
21 // (0)I1+(1)I2+(-1)In = 0..... eq (3)
22 // solving the equations by matrix method
23 A=[1 -4 3;-1 6 -3;0 1 -1];
24 b=[7;0;0];
25 x=inv(A)*b;
26 I1=x(1,:); //to access the 1st
   element of 3X1 matrix
27 I2=x(2,:); //to access the 2nd
   element of 3X1 matrix
28 IN=x(3,:); //to access the 3rd
   element of 3X1 matrix; IN is Norton current
29 r=r1+r5; //series combination
   of resistors
30 rN=(r*r4)/(r+r4); // parallel
   combination of resistors (Norton resistance)
31 I=(rN*IN)/(rN+r3);
32 vx=-I*r3;
33 disp(sprintf("By Norton Theorem , the value of Vx is

```

```
    %d V" ,vx));  
34  
35 //END
```

---

**Scilab code Exa 1.20** To find I using Norton theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 20  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 20");  
7  
8 //VARIABLE INITIALIZATION  
9 I=20;                                // current source  
    in Amperes  
10 v1=10;                                 // voltage source  
    in Volts  
11 v2=40;                                 // voltage source  
    in Volts  
12 r1=8;                                  // in Ohms  
13 r2=5;                                  // in Ohms  
14 r3=4;                                  // in Ohms  
15 r4=12;                                 // in Ohms  
16  
17 //SOLUTION  
18 req=r1+r2;  
19 rn=(req*r3)/(req+r3);  
20 //finding In by mesh analysis  
21 //(17)I2+(-4)I3 = 110.....eq (1)  
22 //(1)I2+(-1)I3 = -10.....eq (2)  
23 //solving the equations by matrix method  
24 A=[17 -4;1 -1];  
25 b=[110;-10];
```

```

26 x=inv(A)*b;
27 I2=x(1,:);                                //to access the 1
     st element of 2X1 matrix
28 I3=x(2,:);                                //to access the 2
     nd element of 2X1 matrix
29 In=I3;
30 I=(rn*In)/(rn+r4);
31 disp(sprintf("By Norton Theorem, the value of I is
   %f A",I));
32
33 //END

```

---

**Scilab code Exa 1.21** To find I using Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 21
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 21");
7
8 //VARIABLE INITIALIZATION
9 I=20;                                         // current source
   in Amperes
10 v1=10;                                         // voltage source
    in Volts
11 v2=40;                                         // voltage source
    in Volts
12 r1=8;                                          // in Ohms
13 r2=5;                                          // in Ohms
14 r3=4;                                          // in Ohms
15 r4=12;                                         // in Ohms
16
17 //SOLUTION

```

```

18
19 req=r1+r2; // series
   combination of resistors
20 rth=(req*r3)/(req+r3); // parallel
   connection of resistors (Thevenin resistance)
21
22 //by using nodal analysis , the following equations
   are obtained
23 // (13)v1+(-8)v2=750.....eq (1)
24 // (-4)v1+(9)v2=200.....eq (2)
25 // solving the equations by matrix method
26
27 A=[13 -8;-4 9];
28 b=[750;200];
29 x=inv(A)*b;
30 v1=x(1,:); //to access the 1
   st element of 2X1 matrix
31 v2=x(2,:); //to access the 2
   nd element of 2X1 matrix
32 vth=v2; //Thevenin voltage
33 I=vth/(rth+r4); //Thevenin current
34 disp(sprintf("By Thevenin Theorem , the value of I is
   %f A",I));
35
36 //END

```

---

**Scilab code Exa 1.22** To find I using mesh analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 22
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 22");

```

```

7
8 //VARIABLE INITIALIZATION
9 I1=20;                                // current source
10 v1=10;                                 // voltage source
11 v2=40;                                 // voltage source
12 r1=8;                                  // in Ohms
13 r2=5;                                  // in Ohms
14 r3=4;                                  // in Ohms
15 r4=12;                                 // in Ohms
16
17 //SOLUTION
18
19 //by using mesh analysis the following equations are
   obtained
20 // (17) I2+(-4)I3 = 110.....eq (1)
21 // (-1)I2+(4)I3 = 10.....eq (2)
22 //solving the equations by matrix method
23 A=[17 -4;-1 4];
24 b=[110;10];
25 x=inv(A)*b;
26 I2=x(1,:);                           //to access the 1
   st element of 2X1 matrix
27 I3=x(2,:);                           //to access the 2
   nd element of 2X1 matrix
28 I=I3;
29 disp(sprintf("By mesh analysis , the value of I is %f
   A",I));
30
31 //END

```

---

**Scilab code Exa 1.23** To find I using nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 23
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 23");
7
8 //VARIABLE INITIALIZATION
9 I1=20;                                // current source
   in Amperes
10 v1=10;                                 // voltage source
    in Volts
11 v2=40;                                 // voltage source
    in Volts
12 r1=8;                                  // in Ohms
13 r2=5;                                  // in Ohms
14 r3=4;                                  // in Ohms
15 r4=12;                                 // in Ohms
16
17 //SOLUTION
18 // (17) I2+(-4)I3 = 110..... eq (1)
19 // (-4)v1+(16)I3 = 40..... eq (2)
20 // solving the equations by matrix method
21 A=[17 -4;-4 16];
22 b=[110;40];
23 x=inv(A)*b;
24 I2=x(1,:);                            //to access the 1
   st element of 2X1 matrix
25 I3=x(2,:);                            //to access the 2
   nd element of 2X1 matrix
26 disp(sprintf("By Nodal analysis , the value of I is
   %f A",I3));
27
28 //END

```

---

**Scilab code Exa 1.24** To find I using Superposition theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 24  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 24");  
7  
8 //VARIABLE INITIALIZATION  
9 I=20;                                // current source  
    in Amperes  
10 v1=10;                                // voltage source  
     in Volt  
11 v2=40;                                // voltage source  
     in Volts  
12 r1=8;                                  // in Ohms  
13 r2=5;                                  // in Ohms  
14 r3=4;                                  // in Ohms  
15 r4=12;                                 // in Ohms  
16  
17 //SOLUTION  
18  
19 // activating 20A current source  
20 r=r2+((r3*r4)/(r3+r4));  
21 I1=(r*I)/(r+r1);  
22 I_20=(r3*I1)/(r3+r4);  
23  
24 // activating 10V battery source  
25 req=r1+r2;  
26 v_10=(-v1/req)/((1/req)+(1/r3)+(1/r4));  
27 I_10=v_10/r4;  
28
```

```

29 // activating 40V battery source
30 v_40=(v2/r3)/((1/req)+(1/r3)+(1/r4));
31 I_40=v_40/r4;
32 I_tot=I_20+I_10+I_40;
33 disp(sprintf("By Superposition Theorem, the value of
               I is %f A",I_tot));
34
35 //END

```

**Scilab code Exa 1.25** To find I using mesh analysis

```
    A" , I));  
21  
22 //END
```

---

**Scilab code Exa 1.26** To find I using nodal analysis

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 26  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 26");  
7  
8 //VARIABLE INITIALIZATION  
9 I1=5;                                // current source in  
                                         Ampères  
10 v2=100;                               // voltage source in  
                                         Volts  
11 r1=20;                                // in Ohms  
12 r2=10;                                // in Ohms  
13 r3=20;                                // in Ohms  
14  
15 //SOLUTION  
16 v1=(I1+(v2/r2))/((1/r1)+(1/r2));  
17 I=(v1-v2)/r2;  
18 disp(sprintf("By Nodal analysis , the value of I is  
%d A" ,I));  
19  
20 //END
```

---

**Scilab code Exa 1.27** To find I using Thevenin theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 27
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 27");
7
8 //VARIABLE INITIALIZATION
9 I1=5;                                // current source in
    Ampères
10 vb=100;                               // voltage source in
    Volts
11 r1=20;                                // in Ohms
12 r2=10;                                // in Ohms
13 r3=20;                                // in Ohms
14
15 //SOLUTION
16 va=I1*r1;                            // by applying node
    analysis at point 'a'
17 vth=va-vb;                            // Thevenin voltage
    vth=vab
18 rth=r1+((r3*0)/(r3+0));             // Thevenin resistance
19 I=vth/(rth+r2);
20 disp(sprintf("By Thevenin Theorem , the value of I is
    %d A",I));
21
22 //END

```

---

**Scilab code Exa 1.28** To find I using Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 28
3

```

```

4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 28");
7
8 //VARIABLE INITIALIZATION
9 I1=5;                                // current source in
                                         Ampères
10 va=100;                               // voltage source in
                                         Volts
11 r1=20;                                // in Ohms
12 r2=10;                                // in Ohms
13 r3=20;                                // in Ohms
14
15 //SOLUTION
16 IN=I1-(va/r1);                      // using nodal
                                         analysis at point 'a'
17 rN=r1+((r3*0)/(r3+0));
18 I=(rN*IN)/(rN+r2);
19 disp(sprintf("By Norton Theorem, the value of I is
%d A",I));
20
21 //END

```

---

**Scilab code Exa 1.29** To find I using Superposition theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
                                         THEOREMS
2 //Example 29
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 29");
7
8 //VARIABLE INITIALIZATION
9 I=5;                                // current source in

```

```

    Ampères
10 v=100;                                // voltage source in
    Volts
11 r1=20;                                 // in Ohms
12 r2=10;                                 // in Ohms
13 r3=20;                                 // in Ohms
14
15 //SOLUTION
16
17 // activating current source
18 I1=(I*r1)/(r1+r2);                  //by current divider
    law
19
20 // activating voltage source
21 I2=-(v/(r1+r2));
22
23 I_tot=I1+I2;
24 disp(sprintf("By Superposition Theorem, the value of
    I is %d A",I_tot));
25
26 //END

```

---

**Scilab code Exa 1.30** Source transformation and mesh and nodal methods

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 30
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 30");
7
8 //VARIABLE INITIALIZATION
9 I1=25;                                // current source
    in Amperes

```

```

10 I2=20;                                // current source
    in Amperes
11 v=20;                                  // voltage source
    in Volts
12 r1=4;                                   //LHS resistance
    in Ohms
13 r2=10;                                 //in Ohms
14 r3=2;                                   //in Ohms
15 r4=1;                                   //in Ohms
16 r5=10;                                 //RHS resistance
    in Ohms
17
18 //SOLUTION
19
20 //source transformation
21 v1=I1*r1;                               // current source
    I1 is converted to voltage source v1
22 v2=I2*r3;                               //current source
    I2 is converted to voltage source v2
23
24 //using mesh analysis
25 // (8)IA+(-1)IB = 30..... eq (1)
26 // (-2)IA+(3)IB = 20..... eq (2)
27 // solving the equations by matrix method
28 A=[8 -1;-2 3];
29 b=[30;20];
30 x=inv(A)*b;
31 IA=x(1,:);                            //to access the 1
    st element of 2X1 matrix
32 IB=x(2,:);                            //to access the 2
    nd element of 2X1 matrix
33 disp(sprintf("By Mesh analysis I_A= %d A and I_B= %d
    A",IA,IB));
34
35 // using nodal analysis
36 req=r1+r2;
37 res=(v1/req)+(v2/r3)+(v/r4);
38 v3=res/((1/req)+(1/r3)+(1/r4));

```

```

39 I3=(v1-v3)/req;
40 I4=(v2-v)/r3; //since here ((v2-
    v)/r3)=((v3-v)/r4) (this is only done for
    convinient calculation)
41 disp(sprintf("By Nodal analysis I_1= %d A and I_2=
    %d A",I3,I4));
42
43 //END

```

---

### Scilab code Exa 1.31 Delta to star transformation

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 // Example 31
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 31");
7
8 //VARIABLE INITIALIZATION
9 r1=6; //in Ohms
10 r2=4; //in Ohms
11 r3=4; //in Ohms
12 r4=4; //in Ohms
13 r5=6; //in Ohms
14 r6=6; //in Ohms
15 r7=6; //in Ohms
16 r8=8; //in Ohms
17 r9=4; //in Ohms
18 r10=10; //in Ohms
19 r11=10; //middle resistance
    in Ohms
20
21 //SOLUTION
22 //converting delta cde in a star

```

```

23 req1=r5+r6+r7;
24 req2=(r6*r7)/req1;
25 req3=(r5*r6)/req1;
26 req4=(r5*r7)/req1;
27
28 req5=r1+r2+r3;                                //on LHS of middle
     resistance
29 req6=r4+req2;                                //top LHS
30 req7=req4+r11;                               //equivalent middle
     resistance
31 req8=req3+r8+r9+r10;                          //top RHS
32
33 req9=(req7*req8)/(req7+req8);                //parallel
     combination of resistors
34 req10=req9+req6;                             //series combination
     of resistors
35 req11=(req5*req10)/(req5+req10);
36
37 disp(sprintf("The equivalent resistance between A
     and B is %d",req11));
38
39 //END

```

---

**Scilab code Exa 1.32** To find I through 1 ohm by mesh analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 32
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 32");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                         // current source in

```

```

    Ampères
10 v=10;                                // voltage source in
    Volts
11 r1=4;                                 //top resistance in
    Ohms
12 r1=4;                                 //right resistance
    in Ohms
13 r3=4;                                 //bottom resistance
    in Ohms
14 r4=6;                                 //left resistance in
    Ohms
15 r5=1;                                 //in Ohms
16
17 //SOLUTION
18 //without converting the current source into voltage
    source
19 // (10)I1+(-4)I2+(0)I3 = 50..... eq (1)
20 // (-4)I1+(9)I2+(-4)I3 = 0..... eq (2)
21 // (0)I1+(-4)I2+(8)I3 = 10..... eq (3)
22 //solving the equations by matrix method
23 A=[10 -4 0;-4 9 -4;0 -4 8];
24 b=[50;0;10];
25 x=inv(A)*b;
26 I2=x(2,:);                           //to access the 2nd
    element of 3X1 matrix
27 disp(sprintf("By Mesh analysis , the current through
    1 resistor is %f A",I2));
28
29 //END

```

---

**Scilab code Exa 1.33** To find I through 1 ohm R by nodal analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 33

```

```

3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 33");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // current source in
   Ampères
10 v=10;                                 // voltage source in
    Volts
11 r1=4;                                //top resistance in
   Ohms
12 r1=4;                                //right resistance
   in Ohms
13 r3=4;                                //bottom resistance
   in Ohms
14 r4=6;                                //left resistance in
   Ohms
15 r5=1;                                //in Ohms
16
17 //SOLUTION
18
19 //by applying nodal analysis at node 1, the
   following equations are obtained:
20 //(17)v1+(-12)v2=150.....eq (1)
21 //(-4)v1+(6)v2=10.....eq (2)
22 //solving the equations by matrix method
23
24 A=[17 -12;-4 6];
25 b=[150;10];
26 x=inv(A)*b;
27 v1=x(1,:);                           //to access the 1st
   element of 2X1 matrix
28 v2=x(2,:);                           //to access the 1st
   element of 2X1 matrix
29 if(v1>v2) then
30 I=(v1-v2)/r5;
31 disp(sprintf("By nodal analysis , the current through

```

```

1      resistor is %f A",I));
32 else
33 I=(v2-v1)/r5;
34 disp(sprintf("By nodal analysis , the current through
1      resistor is %f A",I));
35 end;
36
37 //END

```

---

**Scilab code Exa 1.34** To find I through 1 ohm R by Superposition theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
THEOREMS
2 //Example 34
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 34");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // current source in
                                         Ampères
10 v=10;                                 // voltage source in
                                         Volts
11 r1=4;                                 //top resistance in
                                         Ohms
12 r1=4;                                 //right resistance
                                         in Ohms
13 r3=4;                                 //bottom resistance
                                         in Ohms
14 r4=6;                                 //left resistance in
                                         Ohms
15 r5=1;                                 //in Ohms
16

```

```

17 //SOLUTION
18
19 // activating the current source
20 //((17)v1+(-12)v2=120.....eq (1)
21 //(-4)v1+(6)v2=0.....eq (2)
22 //solving the equations by matrix method
23 A=[17 -12;-4 6];
24 b=[120;0];
25 x=inv(A)*b;
26 v1=x(1,:); //to access the 1st
   element of 2X1 matrix
27 v2=x(2,:); //to access the 1st
   element of 2X1 matrix
28 if(v1>v2) then
29 I1=(v1-v2)/r5;
30 else
31 I1=(v2-v1)/r5;
32 end;
33
34 // activating the voltage source
35 //((17)v1+(-12)v2=30.....eq (1)
36 //(-4)v1+(6)v2=10.....eq (2)
37 //solving the equations by matrix method
38 A=[17 -12;-4 6];
39 b=[30;10];
40 x=inv(A)*b;
41 v3=x(1,:); //to access the 1st
   element of 2X1 matrix
42 v4=x(2,:); //to access the 1st
   element of 2X1 matrix
43 if(v3>v4) then
44 I2=(v3-v4)/r5;
45 else
46 I2=(v4-v3)/r5;
47 end;
48
49 I_tot=I1+I2;
50 disp(sprintf("By Superposition Theorem , the current

```

```
    through 1      resistor  is "%f A",I_tot));  
51  
52 //END
```

---

**Scilab code Exa 1.35** To find I through 1 ohm by Thevenin theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 35  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 35");  
7  
8 //VARIABLE INITIALIZATION  
9 I=10;                                // current source in  
    Ampères  
10 v=10;                                 // voltage source in  
    Volts  
11 r1=4;                                  //top resistance in  
    Ohms  
12 r2=4;                                  //right resistance  
    in Ohms  
13 r3=4;                                  //bottom resistance  
    in Ohms  
14 r4=6;                                  //left resistance in  
    Ohms  
15 r5=1;                                  //in Ohms  
16  
17 //SOLUTION  
18 res=I+(v/r1);                         // 'res' is used to  
    make calucations easy  
19 va=res/((1/r4)+(1/r1));                // applying nodal  
    analysis at node 1  
20 vb=(v/r2)/((1/r2)+(1/r3));            // applying nodal
```

```

        analysis at node 2
21 vth=va-vb;
22 req1=(r1*r4)/(r1+r4);
23 req2=(r2*r3)/(r2+r3);
24 rth=req1+req2;
25 Ith=vth/(rth+r5);
26 disp(sprintf("By Thevenin's Theorem, the current
      through the 1    resistor is %f A",Ith));
27
28 //END

```

---

**Scilab code Exa 1.36** To find I through 1 ohm R by Norton theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 36
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 36");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                //current source
   in Amperes
10 v=10;                                 //voltage source
    in Volts
11 r1=4;                                  //top resistance
    in Ohms
12 r2=4;                                  //right
    resistance in Ohms
13 r3=4;                                  //bottom
    resistance in Ohms
14 r4=6;                                  //left resistance
    in Ohms
15 r5=1;                                  //in Ohms

```

```

16
17 //SOLUTION
18 // (1) v1+(12/5) In = 30..... eq (1)
19 // (2) v1+(-4) In = 10..... eq (2)
20 A=[1 12/5;2 -4];
21 b=[30;10];
22 x=inv(A)*b;
23 v1=x(1,:);                                //to access the
24          1st element of 2X1 matrix
25 In=x(2,:);                                //to access the
26          2nd element of 2X1 matrix
27 req1=(r1*r4)/(r1+r4);
28 req2=(r2*r3)/(r2+r3);
29 rn=req1+req2;
30 I1=(rn*In)/(rn+r5);
31 disp(sprintf("By Norton Theorem, the current through
               1 resistor is %f A",I1));
30
31 //END

```

---

**Scilab code Exa 1.37** To calculate Vab by Thevenin and Norton theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 37
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 37");
7
8 //VARIABLE INITIALIZATION
9 v1=90;                                     //voltage source
   in Volts
10 r1=8;                                       //in Ohms
11 r2=6;                                       //in Ohms

```

```

12 r3=5; // in Ohms
13 r4=4; // in Ohms
14 r5=8; // diagonal
    resistance in Ohms
15 r6=8; // in Ohms
16
17 //SOLUTION
18
19 //solution (i): using Thevenin's Theorem
20 // (3)v1+(-2)v2 = 90 ..... eq (1) // applying nodal
    analysis at node 1
21 //(-2)v1+(4)v2 = -90 ..... eq (2) // applying nodal
    analysis at node 2
22 A=[3 -2;-2 4];
23 b=[90;-90];
24 x=inv(A)*b;
25 v1=x(1,:);
26 v2=x(2,:);
27 vth=v1;
28 req1=(r1*r5)/(r1+r5);
29 req2=req1+r4;
30 req3=(req2*r6)/(req2+r6);
31 rth=req3+r2;
32 vab1=(vth*r3)/(rth+r3);
33 disp(sprintf("By Thevenin's Theorem, the value of
    Vab is %f V",vab1));
34
35 //solution (ii): using Norton's Theorem
36 //(13)v1+(-7)v2 = 270 ..... eq (1) // applying nodal
    analysis at node 1
37 //(7)v1+(-13)v2 = 0 ..... eq (2) // applying nodal
    analysis at node 2
38 A=[13 -7;7 -13];
39 b=[270;0];
40 x=inv(A)*b;
41 v1=x(1,:);
42 v2=x(2,:);
43 req1=(r1*r5)/(r1+r5);

```

```

44 req2=req1+r4;
45 req3=(req2*r6)/(req2+r6);
46 rN=req3+r2;
47 if(v1>v2) then
48 In=(v1-v2)/r2;
49 else
50 IN=(v2-v1)/r2;
51 end;
52 vab2=(r3*IN)*(rN/(rth+r3));
53 disp(sprintf("By Norton's Theorem, the value of Vab
      is %f V",vab2));
54
55 //END

```

---

### Scilab code Exa 1.38 Thevenin and Norton equivalent

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 38
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 38");
7
8 //VARIABLE INITIALIZATION
9 I=2;                                // current source in
   Amperes
10 r1=2;                                 // in Ohms
11 r2=1;                                 // in Ohms
12 r3=1;                                 // in Ohms
13 r4=2;                                 // in Ohms
14
15 //SOLUTION
16
17 //Thevenin Equivalent circuit

```

```

18 I1=1;                                //since there is
19   equal resistance of 3 , hence , current=1A
20 vth=(I1*r2)+(-I1*r4);
21 req1=r1+r2;
22 req2=r3+r4;
23 disp("THEVENIN EQUIVALENT CIRCUIT IS-");
24 disp(sprintf("      Thevenin voltage= %d V",vth));
25 disp(sprintf("      Thevenin resistance= %f      ",rth)
26 );
27 //Norton Equivalent circuit
28 v1=I/((1/r2)+(1/r4));
29 v2=-I/((1/r3)+(1/r1));
30 req1=r1+r2;
31 req2=r3+r4;
32 rn=(req1*req2)/(req1+req2);
33 Isc=(v1/r4)+v2;
34 disp("NORTON EQUIVALENT CIRCUIT IS-");
35 disp(sprintf("      Norton current= %f A",Isc));
36 disp(sprintf("      Norton resistance= %f      ",rn));
37
38 //END

```

---

### Scilab code Exa 1.39 Delta to star transformation to find I

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
2   THEOREMS
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 39");
7
8 //VARIABLE INITIALIZATION

```

```

9 v=2;                                //in Volts
10 r=2;                               //in Ohms
11
12 //SOLUTION
13 z_star=r/3;
14 req1=(r/3)+r;
15 req2=(r/3)+r;
16 req3=(req1*req2)/(req1+req2);
17 req4=(r/3)+req3;
18 req5=(req4*r)/(req4+r);
19 I=v/req5;
20 disp(sprintf("The value of I is %d A",I));
21
22 //END

```

---

### Scilab code Exa 1.40 Currents in different branches

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 40
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 40");
7
8 //VARIABLE INITIALIZATION
9 v1=20;                                //in Volts
10 v2=10;                                 //in Volts
11 r1=5;                                  //top resistance in
   Ohms
12 r2=10;                                 //bottom resistance in
   Ohms
13 r3=5;                                  //in Ohms
14 r4=5;                                  //in Ohms
15 r5=10;                                 //in Ohms

```

```

16
17 //SOLUTION
18 // (5) I1+(10) I3+(-10) I4 = 20 ..... eq (1)
19 // (0) I1+(10) I3+(10) I4 = -50 ..... eq (2)
20 // (5) I1+(20) I3+(0) I4 = -30 ..... eq (3) (eq(1) +
    eq(2))
21 // Since the determinant of matrix A is 0, hence , the
    set of these equations cannot be solved by
    matrix method
22 //So , solving them directly ,
23
24 I3=-15/25;
25 I1=-3-(3/5);
26 I4=-5-(-3/5);
27 I=I1+3+5;
28 disp("The currents (in Amperes) flowing in different
    branches are:");
29 disp(I1);
30 disp(I3);
31 disp(I4);
32 disp(sprintf("The total current is %f A",I));
33
34 //END

```

---

**Scilab code Exa 1.41** Current when resistance is connected across AB

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
    THEOREMS
2 //Example 41
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 41");
7
8 //VARIABLE INITIALIZATION

```

```

9  vs=6;                                // in Volts
10 Is=4;                                 // in Amperes
11 r1=5;                                 // in Ohms
12 r2=2;                                 // in Ohms
13 r3=2;                                 // in Ohms
14 r=2/3;                                // in Ohms
15 r4=3;                                 // in Ohms
16 r5=1;                                 // in Ohms
17 r6=2;                                 // in Ohms
18
19 //SOLUTION
20 req1=(r2*r3)/(r2+r3);
21 req2=req1+r1;                         // resistance across
   vs
22 va=vs/req2;                           // voltage divider law
23 rth1=(req1*r1)/(req1+r1);
24 I1=Is*(r2/req2);                     // current divider law
25 vb=I1*r4;
26 rth2=(r4*r4)/(r4+r4);
27 I=(vb-va)/(rth1+r+rth2);
28 disp(sprintf("The value of the current is %d A",I));
29
30 //END

```

---

### Scilab code Exa 1.42 Thevenin and Nodal analysis

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 42
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 42");
7
8 //VARIABLE INITIALIZATION

```

```

9 v=10; //in Volts
10 I=0.5; //in Amperes
11 r1=4; //top LHS
   resistance in Ohms
12 r2=2; //top RHS
   resistance in Ohms
13 r3=2; //first
   resistance in Ohms
14 r4=2; //second
   resistance in Ohms
15
16 //SOLUTION
17
18 // using Thevenin's theorem
19 rth=(r1*r3)/(r1+r3);
20 vth=v*(r3/(r1+r3)); //Thevenin
   voltage
21 R=(40-(56*I))/(24*I); //solving for R
   directly
22 disp(sprintf("( i ) By Thevenin's Theorem , the value
   of R is %d ",R));
23
24 //v1=(10R+4)/(3R+4)..... eq(1) //using nodal
   analysis at node 1
25 //v1=1+R..... eq(2) //using nodal
   analysis at node 2
26 //the following the quadratic equation is formed
   when both the equations are compared
27 //(3)R^2+(-3)R+(0)=0
28 //solving the quadratic equation
29 a=3;
30 b=-3;
31 c=0;
32 D=(b^2)-(4*a*c); //discriminant
33 R1=(-b+sqrt(D))/(2*a);
34 R2=(-b-sqrt(D))/(2*a);
35 if(R1==1) then
36 disp(sprintf("( ii ) By Nodal analysis , the value of R

```

```

        is %d    " ,R1));
37 else
38 disp(sprintf("( ii) By Nodal analysis , the value of R
            is %d    " ,R1));
39 end;
40
41 //END

```

---

### Scilab code Exa 1.43 Superposition theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 43
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 43");
7
8 //VARIABLE INITIALIZATION
9 Is1=2;                                // first current
   source in Amperes
10 Is2=4;                                 // second current
    source in Amperes
11 v=2;                                    //in Volts
12 r1=200;                                 //in Ohms
13 r2=100;                                 //in Ohms
14 r3=4;                                   //in Ohms
15
16 //SOLUTION
17 req1=34;
18 I1=Is2*(r3/req1);
19 req2=24;
20 Iab=Is1*(req2/req1);
21 I=Ia+Iab;
22 vab=I*10;

```

```
23 disp(sprintf("By Superposition Theorem the voltage  
Vab is %f V",vab));  
24  
25 //END
```

---

### Scilab code Exa 1.44 Determination of voltage

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 44  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 44");  
7  
8 //VARIABLE INITIALIZATION  
9 I=40; //in Amperes  
10 r=5; //in Ohms  
11  
12 //SOLUTION  
13 v=I*r; //Ohm's Law  
14 disp(sprintf("The voltage required is %d V",v));  
15  
16 //END
```

---

### Scilab code Exa 1.45 value of resistance

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 45  
3  
4 clc;  
5 disp("CHAPTER 1");
```

```

6 disp("EXAMPLE 45");
7
8 //VARIABLE INITIALIZATION
9 w=5*1000;                                // power consumed by
   coil in Watts
10 v=200;                                    // applied voltage in
    Volts
11
12 //SOLUTION
13 r=(v^2)/w;                                // since w=(v^2)/r
14 disp(sprintf("Value of resistance is %d ",r));
15
16 //END

```

---

### Scilab code Exa 1.46 Resistance of metal filament lamp

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 46
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 46");
7
8 //VARIABLE INITIALIZATION
9 v=240;                                     // in Volts
10
11 //SOLUTION
12 //case1: p=60W
13 p1=60;                                       // in Watts
14 r1=(v^2)/p1;
15 disp(sprintf("Resistance of the metal filament lamp
   is %d ",r1));
16
17 //case2: p=100W

```

```

18 p2=100;                                //in Watts
19 r2=(v^2)/p2;
20
21 if(r1>r2) then
22 disp(sprintf("Resistance of %d W lamp will be
      greater",p1));
23 else
24 disp(sprintf("Resistance of %d W lamp will be
      greater",p2));
25 end;
26
27 //END

```

---

### Scilab code Exa 1.47 Copper wire and platinum silver wire

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 47
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 47");
7
8 //VARIABLE INITIALIZATION
9 lc=20;                               //length of copper
   wire in m
10 dc=0.015/100;                         //diameter of copper
   wire in m
11 rhoc=1.7;                             //specific resistance
   for copper
12 lp=15;                               //length of platinum
   silver wire in m
13 dp=0.015/100;                         //diameter of
   platinum silver wire in m
14 rhop=2.43;                            //specific resistance

```

```

        for platinum silver
15
16 //SOLUTION
17
18 //for copper wire
19 sc=(%pi/4)*(dc^2);                                // area
20 rc=rhoc*(lc/sc);
21
22 //for platinum silver
23 sp=(%pi/4)*(dp^2);                                // area
24 rp=rhop*(lp/sp);
25
26
27 if(rc>rp) then
28 disp("Copper wire has greater resistance");
29 else
30 disp("Platinum silver wire has greater resistance");
31 end;
32
33 //END

```

---

### Scilab code Exa 1.48 Cells B1 and b2

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 48
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 48");
7
8 //VARIABLE INITIALIZATION
9 v1=2.05;                                         //1st cell in
   Volts
10 v2=2.15;                                         //2nd cell in

```

```

    Volts
11 r1=0.05;                                //in Ohms
12 r2=0.04;                                //in Ohms
13 r3=1;                                   //in Ohms
14
15 //SOLUTION
16 //((r3+r1)I1+(r3)I2=v1 ..... eq (1)
17 //((r3)I1+(r3+r2)I2=v2 ..... eq (2)
18 req1=r3+r1;
19 req2=r3+r2;
20 A=[req1 r3; r3 req2];
21 b=[v1; v2];
22 x=inv(A)*b;
23 I1=x(1,:);                               //to access the
                                             1st element of 2X1 matrix
24 I2=x(2,:);                               //to access the
                                             2nd element of 2X1 matrix
25 I=I1+I2;
26 pd=I*r3;
27 disp(sprintf("Current through B1 is %f A",I1));
28 disp(sprintf("Current through B2 is %f A",I2));
29 disp(sprintf("Potential difference across AC is %f V
",pd));
30
31 //END

```

---

### Scilab code Exa 1.49 Values of R1 and R2

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 49
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 49");

```

```

7
8 //VARIABLE INITIALIZATION
9 v1=110;                                // voltage source in
   Volts
10 v2=80;                                 // voltage source in
    Volts
11 v3=50;                                 // voltage source in
    Volts
12 r=2;                                   // in Ohms
13
14 //SOLUTION
15
16 //solution (a)
17 I1=4;                                    // charging
18 I2=6;                                    // charging
19 r1=((v1-v2)-((I1+I2)*r))/I1;
20 r2=((v1-v3)-((I1+I2)*r))/I2;
21 disp(sprintf("(a) R1= %f    ",r1));
22 disp(sprintf("      R2= %f    ",r2));
23
24 //solution (b)
25 I1=2;                                     // discharging
26 I2=20;                                    // charging
27 r1=((v1-v2)-((I2-I1)*r))/(-I1);
28 r2=((v1-v3)-((I2-I1)*r))/I2;
29 disp(sprintf("(b) R1= %f    ",r1));
30 disp(sprintf("      R2= %f    ",r2));
31
32 //solution (c)
33 I1=0;
34 I2=(v1-v2)/r;
35 r2=((v1-v3)-(I2*r))/I2;
36 disp(sprintf("(c) I1=0 when R2= %d    ",r2));
37
38 //END

```

---

### Scilab code Exa 1.50 Currents i1 and i2

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 50  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 50");  
7  
8 //SOLUTION  
9 // (5) I1+(-3)I2 = 10 ..... eq (1)  
10 // (-3)I1+(34)I2 = 40 ..... eq (2)  
11 A=[5 -3;-3 34];  
12 b=[10;40];  
13 x=inv(A)*b;  
14 I1=x(1,:); //to access the 1st  
// element of 2X1 matrix  
15 I2=x(2,:); //to access the 2nd  
// element of 2X1 matrix  
16 I=I2-I1;  
17 disp(sprintf("Current i1 is %f A (loop EFAB)",I1));  
18 disp(sprintf("Current i2 is %f A (loop BCDE)",abs(I)) );  
19  
20 //END
```

---

### Scilab code Exa 1.51 Currents in all branches

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 //Example 51
```

```

3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 51");
7
8 //SOLUTION
9 // (9) I1+(-5)I2+(-3)I3 = 5 ..... eq (1)
10 //(-5)I1+(8)I2+(-1)I3 = 5 ..... eq (2)
11 //(-3)I1+(-1)I2+(6)I3 = 3 ..... eq (3)
12 A=[9 -5 -3;-5 8 -1;-3 -1 6];
13 b=[5;5;3];
14 x=inv(A)*b;
15 I1=x(1,:); //to access the 1st
   element of 3X1 matrix
16 I2=x(2,:); //to access the 2nd
   element of 3X1 matrix
17 I3=x(3,:); //to access the 3rd
   element of 3X1 matrix
18 disp(sprintf("Current i1 is %f A (loop ABGH)",I1));
19 disp(sprintf("Current i2 is %f A (loop BCDH)",I2));
20 disp(sprintf("Current i3 is %f A (loop GDEF)",I3));
21
22 //END

```

---

**Scilab code Exa 1.52** Thevenin theorem and Norton theorem

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 52
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 52");
7
8 //VARIABLE INITIALIZATION

```

```

9 v1=20;                                //LHS voltage source
   in Volts
10 v2=12;                                //RHS voltage source
    in Volts
11 r1=5;                                 //LHS resistance in
   Ohms
12 r2=2;                                 //in Ohms
13 r3=8;                                 //in Ohms
14 r4=10;                                //RHS resistance in
   Ohms
15
16 //SOLUTION
17
18 //by Thevenin's Theorem
19 rth=r3+((r1*r2)/(r1+r2));           //Thevenin
   resistance
20 v=v1*(r2/(r1+r2));                  //voltage divider
   law
21 vab=-v2+(r3*0)+(rth*0)+v;
22 It=vab/(rth+r4);                    //current obtained
   by applying Thevenin's Theorem
23 Isc=vab/rth;
24 disp(sprintf("By Thevenin's Theorem, current in the
10 resistor is %f A",It));
25
26 //verification by Norton's Theorem
27 //(7)I1+(2)I2 = 20 ..... eq (1)
28 //(2)I1+(10)I2 = 12 ..... eq (2)
29 //solving the equations using matrix method
30 A=[7 2;2 10];
31 b=[20;12];
32 x=inv(A)*b;
33 x1=x(1,:);                          //to access 1st
   element of 2X1 matrix
34 x2=x(2,:);                          //to access 2nd
   element of 2X1 matrix and Isc=-x2
35 Isc=-x2;                            //Isc is negative
   because its direction is opposite to I2

```

```

36 I=Isc*(rth/(rth+r4));           // current obtained
   by applying Norton's Theorem
37 if (It==I)
38 disp(sprintf("By Norton Theorem, current in the 10
   resistor is %f A",I));
39 disp(sprintf("Hence, answer is confirmed by Norton
   Theorem"));
40 else
41 disp(sprintf("The answer is not confirmed by Norton
   Theorem"));
42 end;
43
44 //END

```

---

### Scilab code Exa 1.53 Thevenin equivalent circuit

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 53
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 53");
7
8 //VARIABLE INITIALIZATION
9 v1=10;                      //LHS voltage source
   in Volts
10 v2=4;                       //RHS voltage source
   in Volts
11 r1=2;                        //LHS resistance in
   Ohms
12 r2=3;                        //in Ohms
13 r3=10;                       //in Ohms
14 r4=3;                        //in Ohms
15 r5=1;                        //RHS resistance in

```

Ohms

```
16
17 //SOLUTION
18 van=v1*(r2/(r1+r2));           // voltage divider
   law
19 vbn=-v2*(r4/(r5+r4));           // voltage divider
   law
20 ran=(r1*r2)/(r1+r2);
21 rbn=(r4*r5)/(r4+r5);
22 vab=(ran*0)+van-vbn+(rbn*0);    // current is zero as
   AB is open circuited when Thevenin's Theorem is
   applied
23 disp(sprintf("The Thevenin voltage is %d V",vab));
24
25 //END
```

---

**Scilab code Exa 1.54** Thevenin theorem

```
1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 54
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 54");
7
8 //VARIABLE INITIALIZATION
9 v=5;                           // voltage source in
   Volts
10 r1=1;                          //LHS resistance in
   Ohms
11 r2=5;                          //in Ohms
12 r3=1;                          //in Ohms
13 r4=1;                          //RHS resistance in
   Ohms
```

```

14 I=10; // current source in
          Ampères
15
16 //SOLUTION
17
18 req1=r1+r3+r4; //on deactivating
          the current source , current I1 flows in the
          circuit
19 I1=v/req1;
20 vab1=v-(I1*r1); // (I1*r1) is voltage
          drop across 1 resistance
21 I2=I/req1;
22 vab2=vab1+(I2*r1); // (I2*r1) is voltage
          drop across 1 resistance
23 req=r1+((r3*r4)/(r3+r4)); // 'req' is the same
          as 'Rth' mentioned in the book
24 I=vab2/(req+r2);
25 RTh=(6/5)+(3/4);
26 req2=10+2;
27 I3=9/12;
28 disp(sprintf("The value of the current is %f A",I3))
      ;
29
30 //END

```

---

### Scilab code Exa 1.55 Nodal analysis

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
          THEOREMS
2 //Example 55
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 55");
7

```

```

8 //VARIABLE INITIALIZATION
9 vcd=50;                                // voltage source in
   Volts
10 v=100;                                 // voltage source in
    Volts
11 r1=40;                                //in Ohms
12 r2=50;                                //in Ohms
13 r3=20;                                //in Ohms
14 r4=10;                                //in Ohms
15
16 //SOLUTION
17 res=(vcd/r2)-(v/r3);                  // 'res' (short for
   result) is used to make calculations easy
18 vp=res/((1/r2)+(1/r3)+(1/r4));
19 vba=vp+v;
20 disp(sprintf("The voltage between A and B is %f V",
   vba));
21
22 //END

```

---

### Scilab code Exa 1.56 Delta values

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 56
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 56");
7
8 //VARIABLE INITIALIZATION
9 r=1;                                     // this is an
   assumption
10 r1=r*1;                                  //in Ohms
11 r2=r*2;                                  //in Ohms

```

```

12 r3=r*3;                                //in Ohms
13
14 //SOLUTION
15 req=(r1*r2)+(r2*r3)+(r3*r1);      // 'req' is the
   equivalent resistance that appears in the
   numerator of the equation of star-delta
   conversion
16 ra=req/r3;
17 rb=req/r1;
18 rc=req/r2;
19 disp(sprintf("The equivalent delta values are ra=(%
   %f x r) , rb=( %f x r) and rc=( %f x r) " ,
   ra,rb,rc));
20
21 //END

```

---

### Scilab code Exa 1.57 Superposition theorem to find I

```

1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 57
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 57");
7
8 //VARIABLE INITIALIZATION
9 v=10;                                //voltage source in
   Ohms
10 r1=2;                                 //RHS resistance in
   Ohms
11 r2=2;                                //in Ohms
12 r3=4;                                //in Ohms
13 r4=4;                                //in Ohms
14 I=20;                                 //current source in

```

```

        Ampères
15
16 //SOLUTION
17
18 r=r1+r2;
19 //deactivating voltage source of 10
20 v1=-I/((1/r)+(1/r3)+(1/r4));    //from equation
21 I1=v1/r3;
22
23 //deactivating current source of 20A
24 v2=(v/r)/((1/r)+(1/r3)+(1/r4));
25 I2=v2/r3;
26
27 I_tot=I1+I2;
28 if(I_tot>0)
29 disp(sprintf("The value of I is %f A (upward)",I_tot
    ));
30 else
31 disp(sprintf("The value of I is %f A (downward)",-
    I_tot));
32
33 //END

```

---

### Scilab code Exa 1.58 Thevenin or Norton theorem

```

1 //CHAPTER 1– D.C. CIRCUIT ANALYSIS AND NETWORK
   THEOREMS
2 //Example 58
3
4 clc;
5 disp("CHAPTER 1");
6 disp("EXAMPLE 58");
7
8 //VARIABLE INITIALIZATION
9 v1=20;                                //LHS voltage source in

```

```

          Volts
10 v2=5;                                //RHS voltage source in
          Volts
11 r1=100;                               //LHS resistance in
          Ohms
12 r2=2;                                 //in Ohms
13 r3=1;                                 //in Ohms
14 r4=4;                                 //in Ohms
15 r5=1;                                 //RHS resistance in
          Ohms
16
17 //SOLUTION
18
19 // applying Thevenin's Theorem
20 //Thevenin's equivalent resistance , r_th is same as
   r_AB
21 r_th=((r3+r5)*r2)/((r3+r5)+r2);
22 v_th=(v1-v2)/2;                      //from the equation
23 I1=v_th/(r4+r_th);
24 v1=I1*r4;
25 disp(sprintf("By Thevenin Theorem , the value of V is
   %d V",v1));
26
27 // applying Norton's Theorem
28 //Norton's equivalent resistance , r_n is same as
   r_AB
29 r_n=((r3+r5)*r2)/((r3+r5)+r2);
30 I_n=(v1-v2)/r2;                      //since v_A=0
31 I2=r_n*(I_n/(r4+r_n));
32 v2=I2*r4;
33 disp(sprintf("By Norton Theorem , the value of V is
   %d V",v2));
34
35 //END

```

---

### Scilab code Exa 1.59 Mesh analysis

```
1 //CHAPTER 1- D.C. CIRCUIT ANALYSIS AND NETWORK  
THEOREMS  
2 // Example 59  
3  
4 clc;  
5 disp("CHAPTER 1");  
6 disp("EXAMPLE 59");  
7  
8 //SOLUTION  
9  
10 //I1+I2 = 20 ..... eq (1)  
11 // -I1+I2 = 10 ..... eq (2)  
12 //solving the simultaneous equations by matrix  
method  
13  
14 A=[1 1;-1 1];  
15 b=[20;10];  
16 I=inv(A)*b;  
17 I1=I(1,:); //to access 1st element of  
2X1 matrix  
18 I2=I(2,:); //to access 2nd element of  
2X1 matrix  
19 disp(sprintf("Current I1= %d A",I1));  
20 disp(sprintf("Current I2= %d A",I2));  
21  
22 //END
```

---

# Chapter 2

## Steady State Analysis of Single Phase AC Circuit

Scilab code Exa 2.1 Form factor of sine wave

```
1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
     .C. CIRCUIT
2 //Example 1
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 1");
7
8 //SOLUTION
9
10 //average value
11 v_av=(integrate('sin(x)', 'x', 0, %pi))/(2*%pi);
12
13 //rms value
14 v_rms=(integrate('sin(x)^2', 'x', 0, %pi))/(2*%pi);
15 v_rms=sqrt(v_rms);
16
17 ff=v_rms/v_av;
18 disp(sprintf("The form factor is %f", ff));
```

```
19
20 //END
```

---

### Scilab code Exa 2.3 Average and rms value

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 3
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 v_m=5;                                //peak value of
    voltage in Volts
10
11 //SOLUTION
12 v_av=(integrate('v_m*sin(x)', 'x', 0, %pi)) / (%pi);
13 v_rms=(integrate('(v_m*sin(x))^2', 'x', 0, %pi)) / (%pi);
14 v_rms=sqrt(v_rms);
15 disp(sprintf("Average value of full wave rectifier
    sine wave is %f V", v_av));
16 disp(sprintf("Effective value of full wave rectifier
    sine wave is %f V", v_rms));
17
18 //END
```

---

### Scilab code Exa 2.4 Vav and Vrms

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 4
```

```

3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 v_m=10;                                //peak value of
   voltage in Volts
10 angle=60*(%pi/180);                   //delay angle in
   radians
11
12 //SOLUTION
13 v_av=(integrate('v_m*sin(x)', 'x', angle, %pi)) / (%pi);
14 v_rms=(integrate(' (v_m*sin(x))^2 ', 'x', angle, %pi)) / (
   %pi);
15 v_rms=sqrt(v_rms);
16 disp(sprintf("Average value of full wave rectifier
   sine wave is %f V", v_av));
17 disp(sprintf("Effective value of full wave rectifier
   sine wave is %f V", v_rms));
18
19 //END

```

---

### Scilab code Exa 2.5 Fluorescent lamp

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 5
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 I1=0.75;                                // in Amperes

```

```

10 v=240; //in Volts
11 f=50; //in Hertz
12 p=80; //in Watts
13
14 //SOLUTION
15 res=p/v;
16 pf1=res/I1; //1st power factor =
    cos( 1 )
17 phi1=acos(pf1);
18 res1=tan(phi1); //result1 = tan( 1 )
19 w=2*pi*f;
20
21 //solution (a)
22 res2=0; //result2 = tan( 2 )
23 Ic1=res*(res1-res2);
24 c1=Ic1/(v*w);
25 disp(sprintf("(a) When power factor is unity , the
    value of capacitance is %f F ",c1*(10^6)));
26
27 //solution (b)
28 pf2=0.95; //given
29 phi2=acos(pf2);
30 res2=tan(phi2);
31 Ic2=res*(res1-res2);
32 c2=Ic2/(v*w);
33 disp(sprintf("(b) When power factor is 0.95(lagging)
    , the value of capacitance is %f F ",c2*(10^6)))
    ;
34
35 //END

```

---

### Scilab code Exa 2.6 Single phase motor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT

```

```

2 //Example 6
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 f=50;                                //in Hertz
10 I1=20;                                 //in Amperes
11 pf1=0.75;                             //power factor
12 v=230;                                 //in Volts
13 pf2=0.9;                               //power factor(
    lagging)
14
15 //SOLUTION
16 phi1=acos(pf1);
17 res1=tan(phi1);                      // result1 = tan( 1
    )
18 phi2=acos(pf2);
19 res2=tan(phi2);                      // result2 = tan( 2
    )
20 Ic=I1*pf1*(res1-res2);
21 w=2*pi*f;
22 c=Ic/(v*w);
23 disp(sprintf("The value of capacitance is %f F ",c
    *(10^6)));
24 Qc=v*Ic;
25 disp(sprintf("The reactive power is %f kVAR",Qc
    /(10^3)));
26 I2=I1*(pf1/pf2);
27 disp(sprintf("The new supply current is %f A",I2));
28
29 //END

```

---

**Scilab code Exa 2.7** Apparent power of 300 kVA

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 7
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 s1=300;                                // apparent power in
    kVA
10 pf1=0.65;                               // power factor(
    lagging)
11 pf2=0.85;                               // power factor(
    lagging)
12
13 //SOLUTION
14
15 // solution (a)
16 p=s1*pf1;                                // active power
17 q1=sqrt((s1^2)-(p^2));
18 disp(sprintf("(a) To bring the power factor to unity
    , the capacitor bank should have a capacity of %f
    kVAR",q1));
19
20 //solution (b)
21 s2=p/pf2;
22 q2=sqrt((s2^2)-(p^2));
23 disp(sprintf("(b) To bring the power factor to 85%
    lagging , the capacitor bank should have a
    capacity of %f kVAR",q2));
24
25 //END

```

---

**Scilab code Exa 2.8** Two element series circuit

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
. C. CIRCUIT
2 //Example 8
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 v=300/sqrt(2);                                //in Volts
10 angle_v=110;                                  //in degrees
11 I=15/sqrt(2);                                //in Amperes
12 angle_I=80;                                   //in degrees
13
14 //SOLUTION
15 Z=v/I;
16 angle_Z=angle_v-angle_I;
17 disp(sprintf("The circuit impedance is %d ",Z));
18 disp(sprintf("The phase angle is %d degrees",angle_Z
));
19 p_av=v*I*cos(angle_Z*(pi/180));   //to convert
angle_z from degrees to radians
20 disp(sprintf("The average power drawn is %f W",p_av)
);
21
22 //END

```

---

### Scilab code Exa 2.9 120 V 100 W lamp

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
. C. CIRCUIT
2 //Example 9
3
4 clc;
5 disp("CHAPTER 2");

```

```

6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 v1=120;                                // voltage of lamp in
   Volts
10 p=100;                                  //in Watts
11 v2=220;                                //supply voltage in
   Volts
12 f=50;                                   //in Hertz
13
14 //SOLUTION
15 v1=sqrt((v2^2)-(v1^2));
16 x1=(v1*v1)/p;
17 L=x1/(2*pi*f);
18 disp(sprintf("The pure inductance should have a
      value of %f H",L));
19
20 //END

```

---

### Scilab code Exa 2.10 Current and power drawn

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 10
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 v=230;                                    // in Volts
10 z1=3+(%i*4);                           //impedance in
   rectangular form in Ohms
11 z2=6+(%i*8);                           //impedance in
   rectangular form in Ohms

```

```

12
13 //SOLUTION
14 function [z,angle]=rect2pol(x,y);
15 z=sqrt((x^2)+(y^2)); //z is impedance &
16 the resultant of x and y
17 angle=atan(y/x)*(180/%pi); //to convert the
18 angle from radians to degrees
19 endfunction;
20
21 [z1,angle1]=rect2pol(3,4);
22 [z2,angle2]=rect2pol(6,8);
23
24 z=(z1*z2)/(z1+z2);
25 I=v/z;
26 angle=-angle1; //as angle1=angle2
27 p=v*I*cos(angle*%pi/180); //to convert the
28 angle from degrees to radians
29 disp(sprintf("The power drawn from the source is %f
30 kW",p/1000));
31
32 //END

```

---

**Scilab code Exa 2.11** To calculate parameters of coil and power factor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
2 .C. CIRCUIT
3 //Example 11
4
5 clc;
6 disp("CHAPTER 2");
7 disp("EXAMPLE 11");
8 //VARIABLE INITIALIZATION
9 vdc=100; //DC voltage in Volts
10 vac=100; //AC voltage in Volts

```

```

11 f=50;                                //in Hertz
12 I1=10;                               //in Amperes
13 I2=5;                                //in Amperes
14
15 //SOLUTION
16 r=vdc/I1;
17 z=vac/I2;
18 xl=sqrt((z^2)-(r^2));
19 L=xl/(2*pi*f);
20 pf=r/z;
21 disp(sprintf("The inductance of the coil is %f H",L))
   );
22 disp(sprintf("The power factor of the coil is %f ("
   lagging)",pf));
23
24 //END

```

---

**Scilab code Exa 2.13** Current in load in rectangular form

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
   .C. CIRCUIT
2 //Example 13
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 z=1+(%i*1);                           //load impedance
   in rectangular form in Ohms
10 v=20*sqrt(2);                         //amplitude of
   rms value of voltage in Volts
11
12 //SOLUTION
13 function [zp,angle]=rect2pol(x,y); //function '

```

```

rect2pol()' converts impedance in rectangular
form to polar form
14 zp=sqrt((x^2)+(y^2)); //z= (x) + j(y)=
(1)+ j(1); 'zp' is in polar form
15 angle=atan(y/x)*(180/%pi); //to convert the
angle from radians to degrees
16 endfunction;
17
18 //solution (i)
19 [zp,angle]=rect2pol(1,1); //since x=1 and y
=1
20 v=v/sqrt(2);
21 angle_v=100; //v=(20/sqrt(2))*sin(t+100)
22 I=v/zp; //RMS value of
current
23 angle_I=angle_v-angle;
24 Im=I*sqrt(2);
25 disp(sprintf("(i) The current in load is i = %d sin(
t +%d) A",Im,angle_I));
26
27 //solution (ii)
28 p=(v/sqrt(2))*(I*sqrt(2))*cos(angle*(%pi/180));
29 disp(sprintf("(ii) The real power is %f W",p));
30
31 //solution (iii)
32 pa=(v/sqrt(2))*(I*sqrt(2));
33 disp(sprintf("(ii) The apparent power is %f VAR",pa));
34
35 //END

```

---

**Scilab code Exa 2.14** To find frequency and current elements

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 14
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 14");
7
8 //VARIABLE INITIALIZATION
9 v=100;                                // amplitude of rms
    value of voltage in Volts
10 I=20;                                  // amplitude of rms
    value of current in Amperes
11
12 //SOLUTION
13
14 //solution(i)
15 w=314;                                 // angular frequency
    in radian/sec
16 f=w/(2*pi);                           // as w=2*(pi)*f
17 f=ceil(f);
18 disp(sprintf("(i) The frequency is %d Hz",f));
19
20 //solution (ii)
21 E=v/sqrt(2);                          // in degrees
22 angle_E=-45;
23 I=I/sqrt(2);                          // in degrees
24 angle_I=-90;
25 z=E/I;
26 angle=angle_E-angle_I;
27 disp(sprintf("(ii) The impedance is %d , %d
    degrees",z,angle));
28
29 function [x,y]=pol2rect(mag,angle1);
30 x=mag*cos(angle1*(pi/180));        //to convert the
    angle from degrees to radian
31 y=mag*sin(angle1*(pi/180));
32 endfunction;

```

```

33 [r,x]=pol2rect(z,angle);
34 L=x/(2*pi*f);
35 disp(sprintf(" The inductance is %f H",L));
36
37 //END

```

---

**Scilab code Exa 2.15** Choke coil takes current of 2 Amperes

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 15
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 I=2;                                //in Amperes
10 angle_I=60;                          //in degrees
11 v1=200;                             //in Volts
12 f1=50;                              //in Hertz
13 v2=100;                             //in Volts
14 f2=25;                              //in Hertz
15
16 //SOLUTION
17
18 //solution (i): when supply is 200V and frequency is
     50 Hz
19 z1=v1/I;
20 disp(sprintf("(i) When the supply is 200V and
     frequency is 50 Hz:"));
21 disp(sprintf("The impedance is %d , %d degrees",z1
     ,angle_I));
22 function [x,y]=pol2rect(mag,angle); //function '
     pol2rect()' converts impedance in polar form to

```

```

    rectangular form
23 x=mag*cos(angle*(%pi/180));           //to convert
      the angle from degrees to radians
24 y=mag*sin(angle*(%pi/180));
25 endfunction;
26 [r,x1]=pol2rect(z1,angle_I);
27 disp(sprintf("The resistance is %d ",r));
28 L=x1/(2*pi*f1);
29 disp(sprintf("The inductance is %f H",L));
30
31 //solution (ii): when supply is 100V and frequency
      is 25 Hz
32 x2=2*pi*f2*L;
33 z2=sqrt((r^2)+(x2^2));
34 angle=atan(x2/r);
35 I1=v2/z2;
36 p=v2*I1*cos(-angle);
37 disp(sprintf("(ii) When supply is 100V and frequency
      is 25 Hz:"));
38 disp(sprintf("The power consumed is %f W",p));
39
40 //Answer may be slightly different due to precision
      of floating point numbers
41
42 //END

```

---

**Scilab code Exa 2.16** Two coils of 5 ohm and 10 ohm connected in parallel

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
      .C. CIRCUIT
2 //Example 16
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 16");

```

```

7
8 //VARIABLE INITIALIZATION
9 r1=5;                                     //in Ohms
10 r2=10;                                     //in Ohms
11 L1=0.04;                                    //in Henry
12 L2=0.05;                                    //in Henry
13 v=200;                                      //in Volts
14 f=50;                                       //in Hertz
15
16 //SOLUTION
17
18 //solution (i)
19 x11=L1*(2*pi*f);
20 x12=L2*(2*pi*f);
21 z1=r1+(%i*x11);
22 z2=r2+(%i*x12);
23 function [z,angle]=rect2pol(x,y);           //function '
    rect2pol() ' converts impedance in rectangular
    form to polar form
24 z=sqrt((x^2)+(y^2));                      //z=(x) + j(y)
    where 'x' represents resistance and 'y'
    represents inductive reactance
25 angle=atan(y/x)*(180/%pi);                //to convert
    the angle from radians to degrees
26 endfunction;
27 [z1,angle1]=rect2pol(r1,x11);
28 [z2,angle2]=rect2pol(r2,x12);
29 Y1=1/z1;                                     //admittance
30 Y2=1/z2;
31 function [x,y]=pol2rect(mag,angle);         //function '
    pol2rect() ' converts admittance in polar form to
    rectangular form
32 x=mag*cos(angle*(%pi/180));               //to convert
    the angle from degrees to radians
33 y=mag*sin(angle*(%pi/180));
34 endfunction;
35 [G1,B1]=pol2rect(Y1,angle1);
36 [G2,B2]=pol2rect(Y2,angle2);

```



**Scilab code Exa 2.17** AC voltage applied to series RC circuit

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 17
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 17");
7
8 //VARIABLE INITIALIZATION
9 e=141.4; // amplitude of
    e(t) in Volts
10 E=141.4/sqrt(2); //RMS value of
    e(t) in Volts
11 angle_E=0; // in degrees
12 //i(t)=(14.14<0)+(7.07<120)
13 i1=14.14; // in Amperes
14 angle_i1=0; // in degrees
15 i2=7.07; // in Amperes
16 angle_i2=120; // in degrees
17
18 //SOLUTION

```

```

19 function [x,y]=pol2rect(mag,angle); //function
    pol2rect() converts current in polar form to
    rectangular form
20 x=mag*cos(angle*(%pi/180));           //to convert
    the angle from degrees to radians
21 y=mag*sin(angle*(%pi/180));
22 endfunction;
23 //the given current i(t) is composed of two currents
    i1(t) and i2(t)
24 //i1(t) and i2(t) are not mentioned in the book but
    are considered for the sake of convenience
25 [i1_x,i1_y]=pol2rect(i1,angle_i1); //i1(t)= 14.14
    sin(120t)
26 [i2_x,i2_y]=pol2rect(i2,angle_i2); //i2(t)=7.07
    cos(120t+30)
27 i=(i1_x+i2_x)+(%i*(i1_y+i2_y));
28 function [mag,angle]=rect2pol(x,y); //function
    rect2pol() converts current in rectangular form
    to polar form
29 mag=sqrt((x^2)+(y^2));
30 angle=atan(y/x)*(180/%pi);           //to convert
    the angle from radians to degrees
31 endfunction;
32 [I,angle_I]=rect2pol((i1_x+i2_x),(i1_y+i2_y));
33 I=I/sqrt(2);
34
35 //solution (i)
36 z=E/I;
37 angle_z=angle_E-angle_I;
38 [r,xc]=pol2rect(z,angle_z);
39 f=50;
40 c=1/(2*%pi*f*(-xc));
41 disp(sprintf("(i) The value of resistance is %f ", r));
42 disp(sprintf("The value of capacitance is %f F ", c*10^6));
43
44 //solution (ii)

```

```

45 pf=cos(angle_z*(%pi/180));
46 disp(sprintf("( ii ) The power factor is %f ",pf));
47
48 //solution ( iii )
49 p=E*I*pf;
50 disp(sprintf("( iii ) The power absorbed by the source
      is %f W",p));
51
52 //END

```

---

**Scilab code Exa 2.18** Non inductive resistance of 10 ohm

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
     .C. CIRCUIT
2 //Example 18
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 18");
7
8 //VARIABLE INITIALIZATION
9 r=10;                                //in Ohms
10 v=200;                               //in Volts
11 f=50;                                 //in Hertz
12 I=10;                                 //in Amperes
13 rc=2;                                 //resistance of
     coil in Ohms
14
15 //SOLUTION
16
17 //solution ( i )
18 z=v/I;
19 xl=sqrt((z^2)-((r+rc)^2));
20 L=xl/(2*%pi*f);
21 disp(sprintf("( i ) The inductance of the coil is %f H

```

```

" ,L));
22
23 //solution ( ii )
24 pf=(r+rc)/z;
25 disp(sprintf("( ii ) The power factor is %f",pf));
26
27 //solution ( iii )
28 v1=I*(rc+(%i*x1));
29 function [mag,angle]=rect2pol(x,y); //function
    rect2pol() converts voltage in rectangular form
    to polar form
30 mag=sqrt((x^2)+(y^2));
31 angle=atan(y/x)*(180/%pi); //to convert the
    angle from radians to degrees
32 endfunction;
33 [v1,angle_v1]=rect2pol(real(v1),imag(v1));
34 disp(sprintf("( iii ) The voltage across the coil is
    %f V, %f degrees",v1,angle_v1));
35
36 //END

```

---

**Scilab code Exa 2.19** Admittance in each parallel branch

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 19
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 19");
7
8 //VARIABLE INITIALIZATION
9 z1=4+(%i*3); //impedance in
    rectangular form in Ohms
10 z2=6-(%i*8); //impedance in

```

```

    rectangular form in Ohms
11 z3=1.6+(%i*7.2);                                //impedance in
    rectangular form in Ohms
12 v=100                                              //in volts
13 //SOLUTION
14
15 //SOLUTION ( i )
16
17 //Y1 and Y2 are admittances of each parallel branch
18 Y1=1/z1;
19 Y2=1/z2;
20 disp("SOLUTION ( i )");
21 disp(sprintf("Admittance parallel branch 1 is %3f
%3fj S", real(Y1), imag(Y1)));
22 disp(sprintf("Admittance parallel branch 2 is %3f+
%3fj S", real(Y2), imag(Y2)));
23 disp(" ");
24
25 //SOLUTION ( ii )
26
27 z=z3+(z2*z1)/(z1+z2)                                //series and
    parallel combination of impedances
28 disp("SOLUTION ( ii )");
29 disp(sprintf("Total circuit impedance is %3f %3fj S"
, real(z), imag(z)));
30 //solution given in the book is wrong as j
    (7.2+0.798) cannot be equal to j11.598
31
32 //SOLUTION ( iii )
33
34 I=V/Z;
35 function [Z,angle]=rect2pol(x,y); //function '
    rect2pol()' converts impedance in rectangular
    form to polar form
36 Z0=sqrt((x^2)+(y^2));                                //z is impedance &
    the resultant of x and y
37 angle=atan(y/x)*(180/%pi);                          //to convert the
    angle from radians to degrees

```

```

38 endfunction;
39 [Z, angle]=rect2pol(real(I), imag(I));
40 //disp(sprintf("%f, %f",z,angle));
41 //disp(sprintf("%f, %f",real(i), imag(i)));
42 pf=cos(angle*%pi/180);
43 disp("SOLUTION (iii)");
44 disp(sprintf("The power factor is %f",pf));
45
46 //SOLUTION (iv)
47
48 P=v*real(i)*pf; //power supplied
    by source is either (VI cos ) or (I^2 . R)
49 disp("SOLUTION (iv)");
50 disp(sprintf("The power supplied by source is %f
    watt",P));
51 //END

```

---

### Scilab code Exa 2.20 Resonant frequency and band width

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 20 // read it as example 19 in the book on
    page 2.72
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 20");
7
8 //VARIABLE INITIALIZATION
9 L=0.5 //in Henry
10 C=5 //in mf, multiply by
    10^-6 to convert to f
11 R=25 //in ohms
12 //SOLUTION
13

```

```

14 //solution (i)
15 //Resonance frequency f = (1/2) sqrt ((1/LC)-R^2/L
16 ^2)
17 fr=(1/(2*pi))*sqrt((1/(L*C*10^-6))-(R^2)/(L^2));
18 disp("SOLUTION ( i )");
19 disp(sprintf("For parallel circuit , Resonant frquency
20 is %3f Hz", fr));
21 disp(" ");
22 //solution ( ii )
23 //Total circuit impedance at resonance is Z=L/RC
24 z=L/(R*C*10^-6);
25 disp("SOLUTION ( ii )");
26 disp(sprintf("Total impedance at resonance is %3f
27 k ", z/1000));
28 //
29 //solution ( iii )
30 //Bandwidth (f2-f1)=R/(2. .L)
31 bw=R/(2*pi*L);
32 disp("SOLUTION ( iii )");
33 disp(sprintf("Bandwidth is %3f Hz", bw));
34 //
35 //solution ( iv )
36 //Quality factor Q=1/R. sqrt (L/C)
37 Q=(1/R)*sqrt(L/(C*10^-6));
38 disp("SOLUTION ( iv )");
39 disp(sprintf("Quality Factor is %3f", Q));
40 //solution in the book is wrong as there is a total
41 //mistake in imaginary part 7.2+0.798=11.598
42 //
43 //END

```

---

### Scilab code Exa 2.22 Series RLC circuit

```
1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
```

```

.C. CIRCUIT
2 //Example 22 (mentioned as 'example 21' in the book)
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 22");
7
8 //VARIABLE INITIALIZATION
9 L=0.1                                //in Henry
10 C=8*10^-6                             //in Farad
11 R=10                                  //in Ohms
12 //SOLUTION
13
14 //solution (i)
15 fr=1/(2*pi*sqrt(L*C));                //resonant frequency
16 disp("SOLUTION (i)");
17 disp(sprintf("For series circuit , resonant frquency
           is %3f Hz", fr));
18 disp(" ");
19
20 //solution (ii)
21 w=2*pi*fr;
22 Q=w*L/R;
23 disp("SOLUTION (ii)");
24 disp(sprintf("The Q-factor at resonance is %3f k ", Q));
25
26 //solution (iii)
27 bw=R/(2*pi*L);
28 f1=fr+bw/2;
29 disp("SOLUTION (iii)");
30 disp(sprintf("Half power frequencies are %3f Hz and
           %3f Hz", f1, fr));
31
32 //END

```

---

**Scilab code Exa 2.23** An alternating current of frequency of 50 Hertz

```
1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
   .C. CIRCUIT
2 //Example 22 (mentioned as 'example 22' in the book)
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 23");
7
8 //VARIABLE INITIALIZATION
9 A=100                         //amplitude in
                                 Amperes
10 f=50                           //frequency in Hz
11 t1=1/600                        //time in seconds
                                 after wave becomes zero again
12 a1=86.6                         //amplitude in
                                 Amperes at some time 't' after start
13
14 //SOLUTION
15
16 //solution (a)
17 //Amplitude at 1/600 second after it becomes zero
18 w=f*2*pi;                      //angular speed
19 hp=1/(2*f);                   //half period , the
                                 point where sine becomes zero again after origin
20 t=hp+t1;
21 a2=A*sin(w*t);
22 disp("SOLUTION (a)");
23 disp(sprintf("Amplitude after 1/600 sec is %3f A",
               a2));
24 disp(" ");
25 //solution (b)
26 //since A=A0.sinwt , t=asin(A/A0)/w
```

```

27 t2=(asin(a1/A))/w;
28 disp("SOLUTION (b)");
29 disp(sprintf("The time at which amp would be %f is
    %3f sec", a1, t2));
30
31 //END

```

---

### Scilab code Exa 2.24 RMS value average value and form factor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 22 // read it as example 23 in the book on
   page 2.77
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 24");
7
8 //VARIABLE INITIALIZATION
9 V=200                                // Amplitude in Volts
10 w=314                                  // angular spped
11 R=20                                    // in ohms
12 //SOLUTION
13
14 //solution
15 //comparing with standard equation
16 Im=V/R;                                 // in Amps
17 rms=Im/2;
18 Iav=Im/%pi;                            // average current
19 ff=rms/Iav;
20 disp("SOLUTION");
21 disp(sprintf("RMS value of current is %3f A", rms))
   ;
22 disp(sprintf("Average value of current is %3f A",
   Iav));

```

```

23 disp(sprintf("Form Factor of current is %3f A", ff)
   );
24 disp("");
25
26 //END

```

---

### Scilab code Exa 2.25 50 Hz sinusoidal voltage wave shape

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 25 // read it as example 24 in the book on
 page 2.78
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 25");
7
8 //VARIABLE INITIALIZATION
9 V=350                                //Amplitude in Volts
10 f=50                                  //frequency in Hz
11 t1=0.005                               //sec after wave
   becomes zero again
12 t2=0.008                               //sec after waves
   passes through 0 in -ve direction
13 //SOLUTION
14 //e=Esinwt
15 //solution (a)
16 //RAmplitude at 1/600 second after it becomes zero
17 w=f*2*pi;                             //angular speed
18 v1=V*sin(w*t1);
19 disp("SOLUTION (a)");
20 disp(sprintf("Voltage after %f sec is %3f A", t1, v1
   ));
21 disp("");
22 //solution (b)

```

```

23 // since wave will pass in -ve direction after half
   period
24 hp=1/(2*f);                                // half period , the
   point where sine becomes zero again after origin
25 t=hp+t2;
26 v2=V*sin(w*t);
27 disp("SOLUTION (b)");
28 disp(sprintf("The voltage would be %f V %3f sec",
   v2,t));
29 //
30 //END

```

---

**Scilab code Exa 2.26** Sinusoidal alternating current of frequency 25 Hz

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 26 // read it as example 25 in the book on
   page 2.79
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 26");
7
8 //VARIABLE INITIALIZATION
9 A=100                                         // Amplitude in Amps
10 f=25                                           // frquency in Hz
11 a1=20                                         // svalue in Amps to
   be achieved in certain time
12 a2=100                                         //in Amps
13
14 //SOLUTION
15 //i=Isinwt
16 //solution (a)
17 //RAmplitude at 1/600 second after it becomes zero
18 w=f*2*pi;                                     //angular speed

```

```

19 t1=(asin(a1/A))/w;
20 disp("SOLUTION (a)");
21 disp(sprintf("The time to reach value %f A is %3f
sec", a1,t1));
22 disp("");
23 //solution (b)
24 //since wave will pass in -ve direction after half
period
25 t2=(asin(a2/A))/w;
26 disp("SOLUTION (a)");
27 disp(sprintf("The time to reach value %f A is %3f
sec", a2,t2));
28 disp("");
29 //
30 //END

```

---

**Scilab code Exa 2.27** Impedance resistance reactance and power factor of the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 27 // read it as example 26 in the book on
page 2.79
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 27");
7
8 //VARIABLE INITIALIZATION
9 V=250;                                //Amplitude in
                                         Volts
10 w=314;                                 //angular spped
11 pv=-10;                               //phase angle in
                                         degrees
12 I=10;                                  //Amplitude in Amps

```

```

13 pi=50                                // phase angle in
   degrees
14
15 //SOLUTION
16 //v=Vsin(wt+pv)
17 //i=Isin(wt+pi)
18 //solution
19 //representing V in polar format as V=V0/sqrt(2) <
   , we get
20 v1=V/sqrt(2);
21 i1=I/sqrt(2);
22 //converting polar to rect
23 function [x,y]=pol2rect(mag,angle);
24 x=mag*cos(angle*pi/180);           // angle convert in
   radians
25 y=mag*sin(angle*pi/180);
26 endfunction;
27 [x,y]=pol2rect(v1,pv);
28 V=x+y*i;
29 [x,y]=pol2rect(i1,pi);
30 I=x+y*i;
31 Z=V/I;
32 //convert back into angles in deg
33 function [mag,angle]=rect2pol(x,y);
34 mag=sqrt((x^2)+(y^2));           //z is impedance &
   the resultant of x and y
35 angle=atan(y/x)*(180/pi);        //to convert the
   angle from radians to degrees
36 endfunction;
37 [mag,angle]=rect2pol(real(Z),imag(Z));
38 disp("SOLUTION (a)");
39 disp(sprintf("The impedance is %f < %3f Deg", mag
   ,angle));
40 //disp("");
41 //power factor=cos(angle)
42 pf=cos(-1*angle*pi/180);         //convert to radians
   and change sign
43 disp(sprintf("The power factor is %f", pf));

```

```

44 //Z=R-jXc by comparing real and imag paarts we get
45 disp(sprintf("The resistance is %f and Reactance
    is %3f ", real(Z), imag(Z)));
46 disp("");
47 //
48 //END

```

---

**Scilab code Exa 2.28** Total impedance current drawn from the supply

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 28 // read it as example 27 in the book on
    page 2.80
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 28");
7
8 //VARIABLE INITIALIZATION
9 z1=2+(%i*3);                                //impedance in
    rectangular form in Ohms
10 z2=1-(%i*5);                               //impedance in
    rectangular form in Ohms
11 z3=4+(%i*2);                                //impedance in
    rectangular form in Ohms
12 v=10;                                         //in volts
13 //SOLUTION
14
15 //solution (a)
16 //Total impedance
17 //Total circuit impedance Z=(Z1 || Z2)+Z3
18 z=z1+(z2*z3)/(z2+z3);
19 disp("SOLUTION ( i )");
20 disp(sprintf("Total circuit impedance is %3f %3fj S"
    , real(z), imag(z)));

```

```

21 //Total supply current I=V/Z
22 //solution (b)
23 i=v/z;
24 function [mag ,angle]=rect2pol(x,y);
25 mag=sqrt((x^2)+(y^2));           //z is impedance &
26 the resultant of x and y
26 angle=atan(y/x)*(180/%pi);      //to convert the
27 angle from radians to degrees
27 endfunction;
28 [mag , angle]=rect2pol(real(i), imag(i));
29 disp("SOLUTION (b)");
30 disp(sprintf("Total current is %f<%f Amp",mag ,angle));
31 //solution (c)
32 //Vbc=I . Zbc where Zbc=(z2*z3)/(z2+z3)
33 Vbc=i*((z2*z3)/(z2+z3));
34 [mag1 , angle1]=rect2pol(real(Vbc) , imag(Vbc));
35 disp("SOLUTION (c)");
36 disp(sprintf("The voltage across the || circuit is
37 %f<%f",mag1 , angle1));
37 disp(sprintf("The voltage Vbc lags circuit by %f Deg
38 ",angle-angle1));
38 //solution (d)
39 //i2=Vbc/z2 , i3=Vbc/z3
40 i2=Vbc/z2;
41 i3=Vbc/z3;
42 [mag2 , angle2]=rect2pol(real(i2) , imag(i2));
43 [mag3 , angle3]=rect2pol(real(i3) , imag(i3));
44 disp(sprintf("The current across fist branch of ||
45 circuit is %f<%f",mag2 , angle2));
45 disp(sprintf("The current across second branch of ||
46 circuit is %f<%f",mag3 , angle3));
46 //solution (e)
47 pf=cos(-1*angle*%pi/180);
48 disp("SOLUTION (e)");
49 disp(sprintf("The power factor is %f",pf));
50 //solution (iv)
51 //Apparent power s=VI, True Power , tp I^2R, Reactive

```

```

    Power , rp=I^2X or VISSin( angle )
52 s=v*mag;
53 tp=mag*mag*real(z);
54 rp=v*mag*sin(-1*angle*%pi/180);
55 disp("SOLUTION ( f )");
56 disp(sprintf("The Apparent power is %f VA, True
      power is %f W , Reactive power is %f vars",s,tp,
      rp));
57 disp(" ");
58 //END

```

---

**Scilab code Exa 2.29** An alternating current of frequency of 60 Hertz

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 29 // read it as example 28 in the book on
   page 2.83
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 29");
7
8 //VARIABLE INITIALIZATION
9 I=120;                                // Amplitude in Amps
10 f=60;                                  //Hz
11 t1=1/360;                             //in sec time to
   find amplitude
12 i2=96;                                 //in Amps ,2 to
   find time taken to reach this
13 //SOLUTION
14 //i=Isin(wt)
15 //solution (a)
16 w=2*pi*f;
17 i=I*sin(w*t1);
18 disp("SOLUTION ( a )");

```

```

19 disp(sprintf("The amplitude at time %f sec is %f Amp
           ", t1,i));
20 //solution (b)
21 t2=(asin(i2/I))/w;
22 disp("SOLUTION (b)");
23 disp(sprintf("The time taken to reach %f Amp is %f
           Sec", i2,t2));
24 disp("");
25 //
26 //END

```

---

**Scilab code Exa 2.30** An alternating current with RMS value of 20 A

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 30 // read it as example 29 in the book on
     page 2.83
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 30");
7
8 //VARIABLE INITIALIZATION
9 f=50;                                //Hz
10 rms=20;                               //in Amp
11 t1=0.0025;                            //in sec time to
     find amplitude
12 t2=0.0125;                            //in sec , to
     find amp after passing through +ve maximum
13 i3=14.14;                             //in Amps, to
     find time when will it occur after passing
     through +ve maxima
14 //SOLUTION
15 //i=Isin(wt)
16 //solution (a)

```

```

17 w=2*pi*f;
18 Im=rms*sqrt(2);
19 disp(sprintf("The equation would be i=%f. sin (%f. t)"
    , Im,w));
20 t0=(asin(1)/w);                                //time to reach
    maxima in +ve direction
21 i=Im*sin(w*t1);
22 disp("SOLUTION (a)");
23 disp(sprintf("The amplitude at time %f sec is %f Amp"
    , t1,i));
24 //solution (b)
25 tx=t0+t2;
26 i2=Im*sin(w*tx);
27 disp("SOLUTION (b)");
28 disp(sprintf("The amplitude at time %f sec is %f Amp"
    , t2,i2));
29 //solution (c)
30 ty=(asin(i3/Im))/w;
31 t3=t0-ty;                                     //since ty is
    the time starting from 0, the origin needs to be
    shifted to maxima
32 disp("SOLUTION (c)");
33 disp(sprintf("The amplitude of %f Amp would be
    reached in %f Sec", i3,t3));
34 disp("");
35 //
36 //END

```

---

**Scilab code Exa 2.31** Significance of RMS and average values of wave

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
    .C. CIRCUIT
2 //Example 31 // read it as example 30 in the book on
    page 2.84
3

```

```

4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 31");
7
8 //VARIABLE INITIALIZATION
9 //function of the waveform is deduced to be y=10+10.
10 t/T
11 //SOLUTION
12 //Yav=(1/T).Integral(ydt) from 0 to T
13 //say
14 T=1; // 1 sec
15 Yav=(1/T)*integrate('(10+10*t/T)', 't', 0, 1);
16 disp(sprintf("The average value of waveform is %f", Yav));
17 //RMS value Yrms=(1/T).Integral(y^2.dt) from 0 to T
18 Yms=(1/T)*integrate('(10+10*t/T)^2', 't', 0, 1);
19 disp(sprintf("The RMS value of waveform is %f", sqrt(Yms)));
20 disp("");
21 //
22 //END

```

---

**Scilab code Exa 2.32** Average value effective value and form factor

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 32 // read it as example 31 in the book on
 page 2.85
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 32");
7
8 //VARIABLE INITIALIZATION
9 //function of the waveform is deduced to be i=Im.

```

```

        sin
10 //SOLUTION
11 //Iav=(1/2. ).Integral( y d ) from 0 to , and
   to 2. is zero , interval is 2.
12 //
13 //say
14 Im=1;                                // in Amp
15 Iav=(1/(2*pi))*integrate( '(Im*sin(th))' , 'th' , 0 ,
   %pi);
16 //disp(sprintf("The average value of waveform is %f
   " , Iav));
17 //RMS mean square value (1/ ).Integral(y^2. d )
   from 0 to
18 Ims=(1/(2*pi))*integrate( '(Im*sin(th))^2' , 'th' , 0 ,
   %pi);
19 //disp(sprintf("The RMS value of waveform is %f",
   sqrt(Ims)));
20 ff=sqrt(Ims)/Iav;
21 disp(sprintf("The form factor of waveform is %f" ,ff))
   );
22 disp("");
23 //
24 //END

```

---

### Scilab code Exa 2.33 Three coils of resistances

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 33 // read it as example 32 in the book on
   page 2.86
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 33");
7

```

```

8 //VARIABLE INITIALIZATION
9 r1=20;                                //in
10 r2=30;                                 //
11 r3=40;                                 //
12 l1=0.5;                                //in Henry
13 l2=0.3;                                 //
14 l3=0.2;                                //
15 V=230;                                  // volts
16 f=50;                                   //Hz
17 //coils connected in series
18 //
19 //SOLUTION
20 R=r1+r2+r3;
21 L=l1+l2+l3;
22 XL=2*pi*f*L;
23 //impedence Z=sqrt(R^2 +XL^2)
24 Z=sqrt(R^2 +XL^2);
25 I=V/Z;
26 pf=R/Z;
27 pc=V*I*pf;
28 disp(sprintf("The total current is %f Amp", I));
29 disp(sprintf("The Power Factor is %f lagging", pf))
;
30 disp(sprintf("The Power consumed in the circuit is
    %f W", pc));
31 disp("");
32 //
33 //END

```

---

**Scilab code Exa 2.34** To draw the vector diagram

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
     .C. CIRCUIT
2 //Example 34 // read it as example 33 in the book on
     page 2.87

```

```

3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 34");
7
8 //VARIABLE INITIALIZATION
9 r=100; //in
10 c=40*10^(-6); //
11 V=400; // volts
12 f=50; //Hz
13 //
14 //SOLUTION
15 XC=1/(2*pi*f*c);
16 //impedence Z=sqrt(R^2 +XL^2)
17 Z=sqrt(r^2 +XC^2);
18 I=V/Z;
19 pf=r/Z;
20 pc=V*I*pf;
21 disp(sprintf("The total current is %f Amp", I));
22 disp(sprintf("The Power Factor is %f leading", pf))
;
23 disp(sprintf("The Power consumed in the circuit is
%f W", pc));
24 disp("");
25 //
26 //END

```

---

**Scilab code Exa 2.35** Total impedance and total current

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 35 // read it as example 34 in the book on
page 2.88
3
4 clc;

```

```

5 disp("CHAPTER 2");
6 disp("EXAMPLE 35");
7
8 //VARIABLE INITIALIZATION
9 R=100;                                //in
10 L=0.2;                                 //in Henry
11 C=20*10^(-6);                         //farads
12 V=240;                                // volts
13 f=50;                                  //Hz
14 //
15 //SOLUTION
16 //Solution (a)
17 XL=2*pi*f*L;
18 XC=1/(2*pi*f*C);
19 //impedence Z=sqrt(R^2 +XL^2)
20 X=XL-XC;
21 Z=sqrt(R^2 +X^2);
22 disp("SOLUTION (a)");
23 disp(sprintf("The total impedance is %f ", Z));
24 I=V/Z;
25 disp("SOLUTION (b)");
26 disp(sprintf("The total current is %f Amp", I));
27 Vr=I*R;
28 Vi=I*XL;
29 Vc=I*XC;
30 disp("SOLUTION (c)");
31 disp(sprintf("The voltage across resistance is %f V"
    ,Vr));
32 disp(sprintf("The voltage across inductance is %f V"
    ,Vi));
33 disp(sprintf("The voltage across capacitance is %f V"
    ,Vc));
34 pf=R/Z;
35 pc=V*I*pf;
36 disp("SOLUTION (d)");
37 disp(sprintf("The Power Factor is %f leading", pf))
    ;
38 disp("SOLUTION (e)");

```

```

39 disp(sprintf("The Power consumed in the circuit is
    %f W",pc));
40 //XL=XC
41 f0=1/(2*pi*sqrt(L*C));
42 disp("SOLUTION ( f )");
43 disp(sprintf("Resonance will occur at %f Hz",f0));
44 disp("");
45 //
46 //END

```

---

**Scilab code Exa 2.36** Total current taken from supply

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
    .C. CIRCUIT
2 //Example 36 // read it as example 35 in the book on
    page 2.90
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 36");
7
8 //VARIABLE INITIALIZATION
9 R1=10;                                //in
10 XL=15;                                 //in
11 R2=12;                                 //
12 C=20;                                  //capacitative
    reactance in
13 V=230;                                 // volts
14 f=50;                                   //Hz
15 //
16 //SOLUTION
17 //Solution (a)
18 //conductance g, susceptance b
19 Z12=(R1^2 +XL^2);                     // squared impedance
    Z^2 for branch 1

```

```

20 Z22=(R1^2 +C^2); // squared impedance
21 Z^2 for branch 2
22 g1=R1/Z12;
23 g2=R2/Z22;
24 b1=-XL/Z12;
25 b2=C/Z22;
26 g=g1+g2;
27 b=b1+b2;
28 Y=sqrt(g^2+b^2);
29 I=V*Y;
30 disp("SOLUTION (a)");
31 disp(sprintf("The total current is %f Amp", I));
32 pf=g/Y;
33 disp("SOLUTION (b)");
34 disp(sprintf("The power factor is %f", pf));
35 disp("");
36 //
37 //END

```

---

### Scilab code Exa 2.37 Current taken by each branch

```

1 //CHAPTER 2- STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 // Example 37 // read it as example 36 in the book on
page 2.93
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 37");
7
8 //VARIABLE INITIALIZATION
9 R1=20; // // in ohms
10 XL=15; // assumed
11 R2=0;

```

```

12 C=50;                                // in ohms
   capacitative reactance
13 V=200;
14 f=60;                                 // Hz
15 //
16 //SOLUTION
17 //Solution (a)
18 //conductance g, susceptance b
19 Z1=sqrt(R1^2 +XL^2);                  // squared
   impedance Z^2 for branch 1
20 Z2=sqrt(R2^2 +C^2);                  // squared
   impedance Z^2 for branch 2
21 i1=V/Z1;
22 i2=V/Z2;
23 disp("SOLUTION (a)");
24 disp(sprintf("The current in Branch 1 is %f Amp", i1));
25 disp(sprintf("The current in Branch 2 is %f Amp", i2));
26 phi1=atan(XL/R1);
27 phi2=%pi/2;                           // atan(C/R2);
   //R2=0, output is infinity
28 Icos=i1*cos(phi1)+i2*cos(phi2);     // phi in
   radians
29 Isin=-i1*sin(phi1)+i2*sin(phi2);    // phi in
   radians
30 I=sqrt(Icos^2+Isin^2);
31 //
32 disp("SOLUTION (b)");
33 disp(sprintf("The total current is %f Amp", I));
34 //
35 pf=Icos/I;
36 disp("SOLUTION (c)");
37 disp(sprintf("The power factor is %f ", pf));
38 disp(" ");
39 //
40 //END

```

---

**Scilab code Exa 2.38** To solve example 27 by j method

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 38 // read it as example 37 in the book on
page 2.93
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 38");
7
8 //VARIABLE INITIALIZATION
9 z1=10+15*j;
10 z2=12-20*j;
11 V=230;
12 //invZ=1/z1+1/z2 ;
13 Z=z1*z2/(z1+z2);
14 magZ=sqrt(real(Z)^2+imag(Z)^2);
15 I=V/magZ;
16 pf=real(Z)/magZ;
17 disp("SOLUTION (a)");
18 disp(sprintf("The current is %f Amp", I));
19 //
20 disp("SOLUTION (b)");
21 disp(sprintf("The Power factor is %f", pf));
22 disp(" ");
23 //
24 //END
```

---

**Scilab code Exa 2.39** To draw the complete vector diagram

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 39 // read it as example 38 in the book on
    page 2.94
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 39");
7
8 //VARIABLE INITIALIZATION
9 z1=2.5+1.5*i;
10 z2=4+3*i;
11 z3=3-4*i;
12 V=200;
13 f=50;
14 E=V+0*i;                                // representing
    as a vector
15 //invZ=1/z1+1/z2;
16 Z23=z2*z3/(z2+z3);
17 Z=z1+Z23;
18 I=E/Z;
19 magI=sqrt(real(I)^2+imag(I)^2);        //total current
20 phi=atan(-imag(I)/real(I));              //total phase
21 //
22 //Voltages across the branches
23 e12=I*z1;                               //voltage across
    series branch
24 mage12=sqrt(real(e12)^2+imag(e12)^2);
25 phi12=atan(imag(e12)/real(e12));
26 //
27 e23=E-e12;                             //voltage across
    parallel branch
28 mage23=sqrt(real(e23)^2+imag(e23)^2);
29 phi23=atan(-imag(e23)/real(e23));
30 //
31 //current in branch 1 upper
32 i1=e23/z2;
33 magi1=sqrt(real(i1)^2+imag(i1)^2);

```

```

34 phii1=atan(-imag(i1)/real(i1));
35 //
36 //current in branch 2 lower
37 i2=e23/z3;
38 magi2=sqrt(real(i2)^2+imag(i2)^2);
39 phii2=atan(imag(i2)/real(i2));
40 disp("SOLUTION (b)");
41 disp(sprintf("The current in Upper branch is %f
Amp",magI1));
42 disp(sprintf("The current in Lower branch is %f
Amp",magI2));
43 disp(sprintf("The Total current is %f Amp",magI));
44 ;
45 //
46 pf=cos(phi); //%
47 disp("SOLUTION (c)");
48 disp(sprintf("The Power factor is %f", pf));
49 //
50 disp("SOLUTION (d)");
51 disp(sprintf("The voltage across series branch is
%f V", mage12));
52 disp(sprintf("The voltage across parallel branch is
%f V", mage23));
53 //
54 tp=V*magI*pf;
55 disp("SOLUTION (e)");
56 disp(sprintf("The total power absorbed in circuit
is %f W", tp));
57 //
58 //END

```

---

**Scilab code Exa 2.40** Power factor and average power delivered to the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 40 // read it as example 39 in the book on
page 2.98
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 40");
7
8 //VARIABLE INITIALIZATION
9 V=100; // max amplitude
10 w=314; //angular speed
11 phiV=5; //phase angle
12 in degrees
13 I=5; //max current
14 amplitude
15 phiI=-40; //phase angle in
current in deg
16
17 //SOLUTION
18 phi=phiI-phiV;
19 pf=cos(phi*pi/180); //convert to
radians
20 p=(V/sqrt(2))*(I/sqrt(2))*pf;
21 //disp(sprintf("The Power factor is %f lagging", pf));
22 disp(sprintf("The Power delivered is %f W", p));
23 disp("");
24 //
25 //END

```

---

**Scilab code Exa 2.41 100 V 60 W lamp**

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 41 // read it as example 40 in the book on
    page 2.99
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 41");
7
8 //VARIABLE INITIALIZATION
9 lampV=100;                                //Volts
10 lampW=60;                                 //watts
11 V=250;
12 f=50;
13 //
14 //SOLUTION
15 lampI=lampW/lampV;
16 lampR=lampW/lampI^2;                      //W=I ^ 2.R
17 //
18 disp("SOLUTION (a)");
19 disp(sprintf("The resistance of the lamp is t is %f
    Ohms", lampR));
20 //
21 //in purely resistive / non inductive circuit ,V=IR
    applies , and R=lampR+R
22 R=V/lampI-lampR;
23 disp(sprintf("The value value of resistor to be
    placed in series with the lamp is %f Ohms", R));
24 //
25 //in case of inductance
26 //XL=2*pi*f*L;
27 //V=Z.I where Z^2=R^2+XL^2
28 //L=sqrt((V^2/I^2-R^2)/2*pi*f)
29 L=sqrt((V/lampI)^2-lampR^2)/(2*pi*f);
30 disp(sprintf("The inductive resistance to be placed
    is %f H", L));
31 disp("");
32 //

```

33 //END

---

**Scilab code Exa 2.42** Three sinusoidaly alternating currents

```
1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
 .C. CIRCUIT
2 //Example 42 // read it as example 41 in the book on
 page 2.100
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 42");
7
8 //VARIABLE INITIALIZATION
9 I=10;                                // max
   amplitude of wave in Amp
10 rms1=5;
11 rms2=7.5;
12 rms3=10;
13 phi1=30;
14 phi2=-60;
15 phi3=45;
16 f=50;                                 //Hz
17 w=2*pi*f;
18 //
19 //SOLUTION
20 av1=rms1/1.11;
21 av2=rms2/1.11;
22 av3=rms3/1.11;
23 disp("SOLUTION ( i )");
24 disp(sprintf("The average value of 1st current is
 %f Amp", av1));
25 disp(sprintf("The average value of 2nd current is
 %f Amp", av2));
26 disp(sprintf("The average value of 3rd current is
```

```

        %f Amp" , av3));
27 //
28 disp("SOLUTION ( i i )");
29 disp(sprintf("The instantaneous value of 1st
    current is %f sin(%f*t+%f) Amp" , rms1*sqrt(2) , w ,
    phi1));
30 disp(sprintf("The instantaneous value of 2nd
    current is %f sin(%f*t%f) Amp" , rms2*sqrt(2) , w ,
    phi2));
31 disp(sprintf("The instantaneous value of 3rd
    current is %f sin(%f*t+%f) Amp" , rms3*sqrt(2) , w ,
    phi3));
32 //
33 //instantaneous values of current at t=100msec=0.1
    sec
34 t=0.1;
35 i1=(rms1*sqrt(2))*(sin(w*t+phi1*pi/180));
36 i2=(rms2*sqrt(2))*(sin(w*t+phi2*pi/180));
37 i3=(rms3*sqrt(2))*(sin(w*t+phi3*pi/180));
38 disp("SOLUTION ( iv )");
39 disp(sprintf("The instantaneous value of 1st
    current is %f Amp at %f Sec" , i1 , t));
40 disp(sprintf("The instantaneous value of 2nd
    current is %f Amp at %f Sec" , i2 , t));
41 disp(sprintf("The instantaneous value of 3rd
    current is %f Amp at %f Sec" , i3 , t));
42 disp(" ");
43 //
44 //END
```

---

**Scilab code Exa 2.43** Resultant current wave made up of two components

```

1 //CHAPTER 2– STEADY–STATE ANALYSIS OF SINGLE–PHASE A
    .C. CIRCUIT
2 //Example 43 // read it as example 42 in the book on
```

page 2.102

```

3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 43");
7
8 //VARIABLE INITIALIZATION
9 I=5;                                // max amplitude
   of wave in Amp
10 f=50;                                 //Hz
11 //wave for is to be obtained by adding the two waves
12 //i=5+5.sin(wt)=5+5.sin(theta)
13 //
14 //SOLUTION
15 Iav=(1/(2*pi))*integrate('5+5*sin(theta)', 'theta', 0, 2*
   %pi);
16 ImS=(1/(2*pi))*integrate('(5+5*sin(theta))^2', 'theta',
   0, 2*pi);
17 //
18 disp(sprintf("The average value of resultant
   current is %f Amp", Iav));
19 disp(sprintf("The RMS value of resultant current is
   %f Amp", sqrt(ImS)));
20 disp("");
21 //
22 //END

```

---

**Scilab code Exa 2.44** To find power consumed by the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 44
3
4 clc;
5 disp("CHAPTER 2");

```

```

6 disp("EXAMPLE 44");
7
8 //VARIABLE INITIALIZATION
9 r=20; // in Ohms
10
11 //SOLUTION
12 p0=(4^2)*r;
13 p1=((5/sqrt(2))^2)*r;
14 p2=((3/sqrt(2))^2)*r;
15 p=p0+p1+p2;
16 I=sqrt(p/r);
17 disp(sprintf("The power consumed by the resistor is
    %d W",p));
18 disp(sprintf("The effective value of current is %f A
    ",I));
19
20 //END

```

---

### Scilab code Exa 2.45 Quality factor and bandwidth

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 45
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 45");
7
8 //VARIABLE INITIALIZATION
9 L=1.405; //in Henry
10 r=40; //in Ohms
11 c=20/(10^6); //in Farad
12 v=100; //in Volts
13
14 //SOLUTION

```

```

15 f0=1/(2*pi*sqrt(L*c));
16 disp(sprintf("The frequency at which the circuit
    resonates is %d Hz",f0));
17
18 I0=v/r;
19 disp(sprintf("The current drawn from the supply is
    %f A",I0));
20
21 x10=2*pi*f0*L;
22 z0=sqrt((r^2)+(x10^2));
23 v10=I0*z0;
24 disp(sprintf("The voltage across the coil is %f V",
    v10));
25
26 xc0=1/(2*pi*f0*c);
27 disp(sprintf("The capacitative reactance is %f      ",
    xc0));
28
29 Q0=(2*pi*f0*L)/r;
30 disp(sprintf("The quality factor is %f", Q0));
31
32 bw=r/L;
33 disp(sprintf("The bandwidth is %f Hz", bw));
34
35 //END

```

---

**Scilab code Exa 2.46** To find power consumed and reactive power

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
    .C. CIRCUIT
2 //Example 46
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 46");

```

```

7
8 //VARIABLE INITIALIZATION
9 I=120-(%i*(50));                                //in Amperes
10 v=8+(%i*(2));                                  //in Volts
11
12 //SOLUTION
13
14 //function to convert from rectangular form to polar
   form
15 function [mag,angle]=rect2pol(x,y);
16 mag=sqrt((x^2)+(y^2));
17 angle=atan(y/x)*(180/%pi);          //to convert the
   angle from radians to degrees
18 endfunction;
19 [v,angle_v]=rect2pol(real(v),imag(v));
20 [I,angle_I]=rect2pol(real(I),imag(I));
21
22 //solution (i)
23 z=v/I;
24 angle_z=angle_v-angle_I;
25 disp(sprintf("(i) The impedance is %f , %f degrees
   ",z,angle_z));
26
27 //solution (ii)
28 phi=angle_z;
29 pf=cos(phi* (%pi/180));
30 disp(sprintf("(ii) The power factor is %f (lagging)"
   ,pf));
31
32 //solution (iii)
33 s=v*I;
34 angle_s=angle_v-angle_I;
35 //function to convert from polar form to rectangular
   form
36 function [x,y]=pol2rect(mag,angle);
37 x=mag*cos(angle* (%pi/180));    //to convert the angle
   from degrees to radians
38 y=mag*sin(angle* (%pi/180));

```

```

39 endfunction;
40 [p,q]=pol2rect(s,angle_s);
41 disp(sprintf("(iii) The power consumed is %f W",p));
42 disp(sprintf("          The reactive power is %f VAR",q)
    );
43
44 //END

```

---

### Scilab code Exa 2.47 RL series circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
 .C. CIRCUIT
2 //Example 47
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 47");
7
8 //VARIABLE INITIALIZATION
9 r=10;                                // in Ohms
10 xl=8.66;                             // in Ohms
11 I=5-(%i*10);                          // in Amperes
12
13 //SOLUTION
14 z=r+(%i*(xl));
15 // function to convert from rectangular form to polar
   form
16 function [mag,angle]=rect2pol(x,y);
17 mag=sqrt((x^2)+(y^2));
18 angle=atan(y/x)*(180/%pi);           //to convert the
   angle from radians to degrees
19 endfunction;
20 [z,angle_z]=rect2pol(real(z),imag(z));
21 [I,angle_I]=rect2pol(real(I),imag(I));
22

```

```

23 //solution (i)
24 v=I*z;
25 angle_v=angle_I+angle_z;
26 disp(sprintf("(i) The applied voltage is %f V, %f
degrees",v,angle_v));
27
28 //solution (ii)
29 phi=angle_I-angle_v;
30 pf=cos(phi*(%pi/180));
31 disp(sprintf("(ii) The power factor is %f (lagging)"
,pf));
32
33 //solution (iii)
34 s=v*I;
35 angle_s=angle_v-angle_I;
36 //function to convert from polar form to rectangular
form
37 function [x,y]=pol2rect(mag,angle);
38 x=mag*cos(angle*(%pi/180)); //to convert the angle
from degrees to radians
39 y=mag*sin(angle*(%pi/180));
40 endfunction;
41 [p,q]=pol2rect(s,angle_s);
42 disp(sprintf("(iii) The active power is %f W",p));
43 disp(sprintf("The reactive power is %f VAR",q));
44
45 //END

```

---

### Scilab code Exa 2.48 Power factor of the combination

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
.C. CIRCUIT
2 //Example 48
3

```

```

4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 48");
7
8 //VARIABLE INITIALIZATION
9 pf1=0.8;                                //power factor of 1st
    circuit
10 pf2=0.6;                                //power factor of 2nd
    circuit
11 z=1;                                     //this is an
    assumption
12
13 //SOLUTION
14 angle1=acos(pf1)*(180/%pi);           //in degrees
15 angle2=acos(pf2)*(180/%pi);           //in degrees
16 //function to convert from polar form to rectangular
    form
17 function [x,y]=pol2rect(mag,angle);
18 x=mag*cos(angle*(%pi/180));          //to convert the
    angle from degrees to radians
19 y=mag*sin(angle*(%pi/180));
20 endfunction;
21 [z1_x,z1_y]=pol2rect(z,angle1);
22 [z2_x,z2_y]=pol2rect(z,angle2);
23 nr=angle1+angle2;                      //numerator
24 z_x=z1_x+z2_x;
25 z_y=z1_y+z2_y;
26
27 //function to convert from rectangular form to polar
    form
28 function [z,angle]=rect2pol(x,y);
29 I=sqrt((x^2)+(y^2));
30 angle=atan(y/x)*(180/%pi);           //to convert the
    angle from radians to degrees
31 endfunction;
32 [z,angle]=rect2pol(z_x,z_y);
33 angle_z=nr-angle;
34 pf=cos(angle_z*(%pi/180));

```

```

35 disp(sprintf("The power factor of the combination is
36 %f",pf));
37 //END

```

---

**Scilab code Exa 2.49** kVA and kW in each branch circuit and in the main circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
2 .C. CIRCUIT
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 49");
7
8 //VARIABLE INITIALIZATION
9 v=200;                                //in Volts
10 angle_v=30;                            //in degrees
11 I1=20;                                 //in Amperes
12 angle_I1=60;                            //in degrees
13 I2=40;                                 //in Amperes
14 angle_I2=-30;                           //in degrees
15
16 //SOLUTION
17 //function to convert from polar form to rectangular
18 //form
19 function [x,y]=pol2rect(mag,angle);
20 x=mag*cos(angle*(%pi/180));           //to convert the
21 //angle from degrees to radians
22 y=mag*sin(angle*(%pi/180));
23 endfunction;
24 [v_x,v_y]=pol2rect(v,angle_v);
25 [I1_x,I1_y]=pol2rect(I1,angle_I1);
26 [I2_x,I2_y]=pol2rect(I2,angle_I2);

```

```

25 s1=v*I1;
26 angle_s1=-angle_v+angle_I1;
27 disp(sprintf("The apparent power in 1st branch is %d
kVA",s1/1000));
28 [s1_x,s1_y]=pol2rect(s1,angle_s1);
29 disp(sprintf("The true power in 1st branch is %f kW"
,s1_x/1000));
30
31 disp("");
32
33 s2=v*I2;
34 angle_s2=angle_v-angle_I2;
35 disp(sprintf("The apparent power in 2nd branch is %d
kVA",s2/1000));
36 [s2_x,s2_y]=pol2rect(s2,angle_s2);
37 disp(sprintf("The true power in 2nd branch is %d kW"
,s2_x/1000));
38 I=(I1_x+I2_x)+(%i*(I1_y+I2_y)); disp(I);
39
40 //function to convert from rectangular form to polar
form
41 function [I,angle]=rect2pol(x,y);
42 I=sqrt((x^2)+(y^2));
43 angle=atan(y/x)*(180/%pi); //to convert the
angle from radians to degrees
44 endfunction;
45 [I,angle]=rect2pol(real(I),imag(I));
46 disp(I);
47 s=v*I;
48 angle_s=angle_v-angle;
49 disp(sprintf("The apparent power in the main circuit
is %f kVA",s/1000));
50 [p,q]=pol2rect(s,angle_s);
51 disp(sprintf("The true power in the main circuit is
%f kW",p/1000));
52
53 //END

```

---

**Scilab code Exa 2.50** Current in each branch when total current is 20 A

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 50
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 50");
7
8 //VARIABLE INITIALIZATION
9 z1=6+(%i*5);                                //impedance in Ohms
10 z2=8-(%i*6);                               //impedance in Ohms
11 z3=8+(%i*10);                             //impedance in Ohms
12 I=20;                                         //in Amperes
13
14 //SOLUTION
15 Y1=1/z1;
16 Y2=1/z2;
17 Y3=1/z3;
18 Y=Y1+Y2+Y3;
19 //function to convert from rectangular form to polar
   form
20 function [Y,angle]=rect2pol(x,y);
21 Y=sqrt((x^2)+(y^2));
22 angle=atan(y/x)*(180/%pi);           //to convert the
   angle from radians to degrees
23 endfunction;
24 [Y_tot,angle]=rect2pol(real(Y),imag(Y));
25 v=I/Y_tot;
26 angle_v=-angle;
27 [z1,angle1]=rect2pol(real(z1),imag(z1));
28 [z2,angle2]=rect2pol(real(z2),imag(z2));
29 [z3,angle3]=rect2pol(real(z3),imag(z3));
```

```

30 I1=v/z1;
31 angle_I1=angle_v-angle1;
32 I2=v/z2;
33 angle_I2=angle_v-angle2;
34 I3=v/z3;
35 angle_I3=angle_v-angle3;
36 disp("The current in each branch in polar form is-")
    ;
37 disp(sprintf("%f A, %f degrees",I1,angle_I1));
38 disp(sprintf("%f A, %f degrees",I2,angle_I2));
39 disp(sprintf("%f A, %f degrees",I3,angle_I3));
40
41 //END

```

---

### Scilab code Exa 2.51 Admittance and impedance of the circuit

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 51
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 51");
7
8 //VARIABLE INITIALIZATION
9 Y1=0.4+(%i*0.6);           // admittance of 1st
     branch in Siemens
10 Y2=0.1+(%i*0.4);          // admittance of 2nd
     branch in Siemens
11 Y3=0.06+(%i*0.23);        // admittance of 3rd
     branch in Siemens
12
13 //SOLUTION
14 Y=Y1+Y2+Y3;
15 //function to convert from rectangular form to polar

```

```

        form
16 function [Y,angle]=rect2pol(x,y);
17 Y=sqrt((x^2)+(y^2));
18 angle=atan(y/x)*(180/%pi);      //to convert the
        angle from radians to degrees
19 endfunction;
20 [Y1,angle]=rect2pol(real(Y),imag(Y));
21 disp(sprintf("The total admittance of the circuit is
        %f S, %f degrees",Y1,angle));
22 z=1/Y1;
23 disp(sprintf("The impedance of the circuit is %f ,
        %f degrees",z,-angle));
24
25 //END

```

---

**Scilab code Exa 2.52** Total impedance and current in each branch

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
     .C. CIRCUIT
2 //Example 52
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 52");
7
8 //VARIABLE INITIALIZATION
9 r1=7;                                //in Ohms
10 L1=0.015;                             //in Henry
11 r2=12;                                //in Ohms
12 c2=180*(10^(-6));                   //in Farad
13 r3=5;                                 //in Ohms
14 L3=0.01;                              //in Henry
15 v=230;                                //in Volts
16 f=50;                                 //in Hertz
17

```

```

18 //SOLUTION
19
20 // solution (a)
21 x11=2*%pi*f*L1;
22 xc2=1/(2*%pi*f*c2);
23 x13=2*%pi*f*L3;
24 Z1=r1+x11*%i; //complex
   representations
25 Z2=r2-xc2*%i;
26 Z3=r3+x13*%i;
27 //function to convert from rectangular form to polar
   form
28 function [z,angle]=rect2pol(r,x);
29 z=sqrt((r^2)+(x^2));
30 angle=atan(x/r)*(180/%pi); //to convert the angle
   from radians to degrees
31 endfunction;
32 [z1,angle1]=rect2pol(r1,x11);
33 [z2,angle2]=rect2pol(r2,xc2);
34 [z3,angle3]=rect2pol(r3,x13);
35 //to obtain rectangular form of (Z1+Z2)
36 req1=r1+r2;
37 xeq1=x11-xc2;
38 //to obtain polar form of (Z1+Z2)
39 [zeq1,angle_eq1]=rect2pol(req1,-xeq1);
40 zp=(z1*z2)/(zeq1);
41 angle_p=(angle1-angle2)+angle_eq1;
42 //function to convert from polar form to rectangular
   form
43 function [r,x]=pol2rect(z,angle);
44 r=z*cos(angle*(%pi/180)); //to convert the angle
   from degrees to radians
45 x=z*sin(angle*(%pi/180));
46 endfunction;
47 [rp,xp]=pol2rect(zp,angle_p);
48 [req,xeq]=pol2rect(z3,angle3);
49 r_tot=req+rp;
50 x_tot=xeq+xp;

```

```

51 [z_tot,angle_tot]=rect2pol(r_tot,x_tot);
52 Z=r_tot+x_tot*j; //complex
      representation
53 disp(sprintf("(a) The total impedance is %f , %f
      degrees",z_tot,angle_tot));
54
55 //solution (b)
56 I=v/Z; //complex division
57 angle_I=-angle_tot;
58 [I_x,I_y]=pol2rect(I,angle_I);
59 disp(sprintf("(b) The total current is (%f-j%f) A",
      real(I),imag(I)));
60
61 //solution (c)
62 //Voltage drop across Z3
63 Vab=I*Z3;
64 disp(sprintf("      The Voltage between AB is (%f-j%f)
      A",real(Vab),imag(Vab)));
65 //since we know that V=Vab+Vbc
66 Vbc=v-Vab;
67 disp(sprintf("      The Voltage between BC is (%f-j%f)
      A",real(Vbc),imag(Vbc)));
68 I1=Vbc/Z1; //Branch 1 current
69 I2=Vbc/Z2; //branch 2 current
70 //I3=I, main branch current
71 [mag1,angle1]=rect2pol(real(I1),imag(I1));
72 [mag2,angle2]=rect2pol(real(I2),imag(I2));
73 disp(sprintf("(c) Current in branch 1 is %f A, %f
      degrees",mag1,angle1));
74 disp(sprintf("      The current in branch 1 is (%f-
      j%f) A",real(I1),imag(I1)));
75 disp(sprintf("      The current in branch 2 is %f A,
      %f degrees",mag2,angle2));
76 disp(sprintf("      The current in branch 2 is (%f-
      j%f) A",real(I2),imag(I2)));
77 //END

```

---

**Scilab code Exa 2.53** Total impedance and power taken

```
1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 53 Read Example 52 of the Text Book
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 53");
7
8 //VARIABLE INITIALIZATION
9 v=230;                                //in Volts
10 angle_v=30;                            //in degrees
11 I1=20;                                 //in Amperes
12 angle_I1=60;                            //in degrees
13 I2=40;                                 //in Amperes
14 angle_I2=-30;                           //in degrees
15
16 //SOLUTION
17 //function to convert from polar form to rectangular
   form
18 function [x,y]=pol2rect(mag,angle);
19 x=mag*cos(angle*(%pi/180));           //to convert the
   angle from degrees to radians
20 y=mag*sin(angle*(%pi/180));
21 endfunction;
22 [x1,y1]=pol2rect(I1,angle_I1);
23 [x2,y2]=pol2rect(I2,angle_I2);
24 X=x1+x2;
25 Y=y1+y2;
26
27 //function to convert from rectangular form to polar
   form
28 function [I,angle]=rect2pol(x,y);
```

```

29 I=sqrt((x^2)+(y^2));
30 angle=atan(y/x)*(180/%pi); //to convert the
   angle from radians to degrees
31 endfunction;
32 [I,angle]=rect2pol(X,Y);
33
34 //solution (i)
35 z=v/I;
36 angle_z=angle_v-angle;
37 disp(sprintf("(i) The total impedance of the circuit
   is %f , %f degrees",z,angle_z));
38
39 //solution (ii)
40 //disp(sprintf("The value of I is %f and angle is %f
   ",I, angle_z));
41 pf=cos(angle_z*(%pi/180));
42 p=v*I*pf;
43 disp(sprintf("(ii) The power taken is %f W",p));
44 //END

```

---

### Scilab code Exa 2.54 Q factor at resonance

```

1 //CHAPTER 2– STEADY-STATE ANALYSIS OF SINGLE-PHASE A
   .C. CIRCUIT
2 //Example 54 Read example 53 of the Book
3
4 clc;
5 disp("CHAPTER 2");
6 disp("EXAMPLE 54");
7
8 //VARIABLE INITIALIZATION
9 C=2.5/(10^6); //capacitance in
   Farads
10 R=15; //in Ohms
11 L=260/1000; //in Henry

```

```

12
13 //SOLUTION
14
15 //solution ( i )
16 f_r=(1/(2*pi))*sqrt((1/(L*C)-(R^2/L^2)));
17 f_r=round(f_r);                                //to round off the
18 disp(sprintf("( i ) The resonant frequency is %d Hz" ,
19 f_r));
20 //solution ( ii )
21 q_factor=(2*pi*f_r*L)/R;
22 disp(sprintf("( ii ) The Q-factor of the circuit is %f
23 " ,q_factor));
24 //solution ( iii )
25 Z_r=L/(C*R);
26 disp(sprintf("( iii ) The dynamic impedance of the
27 circuit is %f " ,Z_r));
28 //END

```

---

# Chapter 3

## Three Phase AC Circuits

**Scilab code Exa 3.1** Identical impedances each consisting of 15 ohm in series

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 1
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 v_l=400;                                // line voltage in
   Volts
10 r=15;                                    // resistance in
    Ohms
11 xc=10;                                   // capacitive
    reactance in Ohms
12
13 //SOLUTION
14
15 //solution (i)
16 v_ph=v_l/sqrt(3);                      // phase voltage=(
   line voltage)/sqrt(3) for star connection
```

```

17 disp(sprintf("( i ) The phase voltage is %f V",v_ph));
18
19 //solution ( ii )
20 z_ph=sqrt((r^2)+(xc^2));
21 I_l=v_ph/z_ph; //phase current =
    line current for star connection
22 disp(sprintf("( ii ) The line current is %f A",I_l));
23
24 //solution ( iii )
25 disp(sprintf("( iii ) The phase current is %f A",I_l))
    ;
26
27 //solution ( iv )
28 pow_fact=r/z_ph;
29 disp(sprintf("( iv ) The power factor of the circuit
    is %f (leading)",pow_fact));
30
31 //solution ( v )
32 p=sqrt(3)*v_l*I_l*pow_fact;
33 disp(sprintf("( v ) The total power absorbed is %f W",
    p));
34
35 //solution ( vi )
36 va=sqrt(3)*v_l*I_l;
37 disp(sprintf("( vi ) The apparent power is %f VA",va))
    ;
38 var=sqrt((va^2)-(p^2));
39 disp(sprintf("The reactive power is %f VAR",var));
40
41 //Answers ( v ) and ( vi ) are different due to
    precision of floating point numbers
42
43 //END

```

---

**Scilab code Exa 3.2** Resistance and reactance values of each impedance

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 2
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 v_l=400;                                //line voltage in
                                              Volts
10 I_l=30;                                  //line current in
                                              Amperes
11 p=12*1000;                               //power absorbed
                                              in Watts
12
13 //SOLUTION
14 v_ph=v_l/sqrt(3);                      //phase voltage =
                                              (line voltage)/sqrt(3)
15 z_ph=v_ph/I_l;                          //phase current =
                                              line current for star connection
16 pow_fact=p/(sqrt(3)*v_l*I_l);        //three-phase
                                              power = sqrt(3)*v_l*I_l*pow_fact
17 r_ph=z_ph*pow_fact;                    //from impedance
                                              triangle
18 disp(sprintf("The resistance of each impedance is %f
                                              ",r_ph));
19 x_ph=sqrt((z_ph^2)-(r_ph^2));
20 disp(sprintf("The reactance of each impedance is %f
                                              ",x_ph));
21
22 //END

```

---

**Scilab code Exa 3.3** Three similar coils each of 30 ohms

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
```

```

2 //Example 3
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 r_ph=30;                                // resistance of coils
10    in Ohms
11 l=0.07;                                  // inductance of coils
12    in Henry
13 v_l=400;                                  //line voltage in Volts
14 f=50;                                     //frequency in Hertz
15
16 //SOLUTION
17
18 //solution (a)
19 x_ph=2*(%pi)*f*l;                      //inductive reactance
20 z_ph=sqrt((r_ph^2)+(x_ph^2));
21 I_ph=v_l/z_ph;                          //phase voltage = line
22    voltage for delta connection
23 disp(sprintf("(a) The phase current is %f A",I_ph));
24
25 //solution (b)
26 I_l=sqrt(3)*I_ph;                      //phase current = (line
27    current)/sqrt(3) for delta connection
28 disp(sprintf("(b) The line current is %f A",I_l));
29
30 //solution (c)
31 pow_fact=r_ph/z_ph;
32 disp(sprintf("(c) The power factor is %f (lagging)",pow_fact));
33
34 //solution (d)
35 p=sqrt(3)*v_l*I_l*pow_fact;
36 disp(sprintf("(d) The power absorbed is %f W",p));
37
38 //Answer is different due to precision of floating

```

```
    point numbers  
35  
36 //END
```

---

**Scilab code Exa 3.4** Line and phase current when phase sequence is positive

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS  
2 //Example 4  
3  
4 clc;  
5 disp("CHAPTER 3");  
6 disp("EXAMPLE 4");  
7  
8 //VARIABLE INITIALIZATION  
9 v_l=866;                                //line voltage  
    in Volts  
10 z_delta=177-(%i*246);                  //impedance of  
    delta connected load in Ohms  
11 z_wire=1+(%i*2);                      //impedance of  
    each wire of the line in Ohms  
12  
13 //SOLUTION  
14 v_ph=v_l/sqrt(3);                     //phase  
    current = (line current)/sqrt(3) for star  
    connection  
15 z_star=z_delta/3;  
16 z=z_wire + z_star;                    //I_na in  
17 I=v_ph/z;                            rectangular form  
18 //I_na, I_nb and I_nc are same in magnitude and are  
    the line currents for delta connection or vice-  
    versa  
19 //function is not used to convert quantities in  
    rectangular form to polar form
```

```

20 // I_na
21 I_na=sqrt((real(I))^2+(imag(I))^2); // I_na from
    rectangular to polar form
22 a=atan(imag(I)/real(I)); // angle in
    radians
23 a=a*(180/%pi); // radians to
    degrees
24 // I_nb
25 I_na=sqrt((real(I))^2+(imag(I))^2);
26 b=a-120; // lags by 120
    degrees
27 // I_nc
28 I_na=sqrt((real(I))^2+(imag(I))^2);
29 c=a-240; // lags by
    another 120 degrees ie., 240 degrees
30 disp(sprintf("The line currents are %f A (%f degrees
    ), %f A (%f degrees) and %f A (%f degrees)",I_na,
    a,I_na,b,I_na,c));
31
32
33 // line current lags phase current by 30 degrees ,
    hence (-30)
34 //I_AB
35 I_AB=I_na/sqrt(3);
36 a1=a-(-30);
37 //I_BC
38 I_BC=I_na/sqrt(3);
39 b1=b-(-30);
40 //I_AC
41 I_AC=I_na/sqrt(3);
42 c1=c-(-30);
43 disp(sprintf("The phase currents are %f A (%f
    degrees), %f A (%f degrees) and %f A (%f degrees)
    ",I_AB,a1,I_BC,b1,I_AC,c1));
44
45 //converting z_delta from polar form to rectangular
    form
46 z=sqrt((real(z_delta))^2+(imag(z_delta))^2);

```

```

47 angle=atan(imag(z_delta)/real(z_delta));
48 angle=angle*(180/%pi);
49
50 //line voltages for load or phase voltages for the
   delta load-
51 //v_AB
52 v_AB=I_AB*z;
53 a2=a1+angle;
54 //v_B
55 v_BC=I_BC*z;
56 b2=b1+angle;
57 //v_AC
58 v_AC=I_AC*z;
59 c2=c1+angle;
60 disp(sprintf("The phase voltages for the delta load
      are %f A (%f degrees), %f A (%f degrees) and %f
      A (%f degrees)",v_AB,a2,v_BC,b2,v_AC,c2));
61
62 p_AB=(I_AB^2)*real(z_delta);
63 p_load=3*p_AB;
64 disp(sprintf("The power absorbed by the load is %f W
      ",p_load));
65 p_l=3*(I_na^2)*real(z_wire);
66 disp(sprintf("The power dissipated by the line is %f
      W",p_l));
67 p=p_load+p_l;
68 disp(sprintf("The total power supplied by 3-
      source is %f W",p));
69
70 //Answers may be slightly different due to precision
   of floating point numbers
71
72 //END

```

---

**Scilab code Exa 3.5** Power measurement by 2 wattmeter method

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 5
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 w1=5000;                                // reading of 1st
   wattmeter in Watts
10 w2=-1000;                                // reading of 2nd
    wattmeter in Watts
11
12 //SOLUTION
13
14 //solution (a)
15 p1=w1+w2;
16 disp(sprintf("(a) The total power is %d W",p1));
17
18 //solution (b)
19 p2=w1-w2;
20 phi=atan((sqrt(3)*p2)/p1);      //this equation comes
   from two-wattmeter method
21 pow_fact=cos(phi);
22 disp(sprintf("(b) The power factor of the load is %f",
   , pow_fact));
23
24 //END

```

---

### Scilab code Exa 3.6 3300 V synchronous alternator

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 6
3
4 clc;

```

```

5 disp("CHAPTER 3");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 v_l=3300;                                //line voltage in
   Volts
10 p_out=1500*735.5;                      //output power in
   Watts (1 metric horsepower= 735.498W)
11 eff=0.85;
12 pow_fact=0.81;
13
14 //SOLUTION
15
16 // solution (a)
17 p_in=p_out/eff;
18 disp(sprintf("(a) The motor input is %f kW",p_in
   /1000));
19
20 // solution (b)
21 I=p_in/(sqrt(3)*v_l*pow_fact); //phase current = line
   current for star connection
22 disp(sprintf("(b) The line and phase current of the
   alternator is %f A",I));
23
24 // solution (c)
25 I_l=I;
26 I_ph=I_l/sqrt(3);                      //phase current = (
   line current)/sqrt(3) for delta connection
27 disp(sprintf("(c) The line current of the motor is
   %f A",I_l));
28 disp(sprintf("The phase current of the motor is %f A
   ",I_ph));
29
30 //Answers may be different due to precision of
   floating point numbers
31
32 //END

```

---

### Scilab code Exa 3.7 Three phase star connected system

```
1 //CHAPTER 3– THREE-PHASE A.C. CIRCUITS
2 //Example 7
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 v_ph=200;                                //phase voltage
   in Volts
10 r1=5;                                     //in Ohms
11 r2=8;                                     //in Ohms
12 r3=10;                                    //in Ohms
13
14 //SOLUTION
15 I1=v_ph/r1;
16 I2=v_ph/r2;
17 I3=v_ph/r3;
18 disp(sprintf("The current in the three phases are %d
   A, %d A and %d A",I1,I2,I3));
19
20 I_x=0+I2*(sqrt(3)/2)-I3*(sqrt(3)/2); //x-component
   of the three currents =>I_x = I1*cos(90) + I2*cos
   (30) + I3*cos(30)
21 I_y=I1-(I2*0.5)-(I3*0.5);              //y-component
   of the three currents =>I_y = I1*sin(90) + I2*sin
   (30) + I3*sin(30)
22 I=sqrt((I_x^2)+(I_y^2));
23 disp(sprintf("The neutral current is %f A",I));
24
25 p1=v_ph*I1;                            //power
   consumed in 1st phase
```

```

26 p2=v_ph*I2;                                // power
      consumed in 2nd phase
27 p3=v_ph*I3;                                // power
      consumed in 3rd phase
28 disp(sprintf("The power consumed in the three phases
      are %d W, %d W and %d W",p1,p2,p3));
29
30 p=p1+p2+p3;
31 disp(sprintf("The total power is %d W",p));
32
33 //END

```

---

### Scilab code Exa 3.8 Balanced delta connection

```

1 //CHAPTER 3– THREE-PHASE A.C. CIRCUITS
2 //Example 8
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 v_ph=230;                                     //in Volts
      and in polar form
10 z=8+(%i*6);                                  //in Ohms
      and in rectangular form
11
12 //SOLUTION
13 //converting z from rectangular form to polar form
14 z_mag=sqrt(real(z)^2+imag(z)^2);
15 phi=atan(imag(z)/real(z));                   // atan()
      gives output in radians
16
17 I_ph=v_ph/z_mag;
18 I_l=sqrt(3)*I_ph;

```

```

19 disp(sprintf("The line current is %f A", I_1));
20
21 pow_fact=cos(phi);
22 disp(sprintf("The power factor is %f", pow_fact));
23
24 p=sqrt(3)*v_ph*I_1*pow_fact; //phase volt=
    line volt in delta connection(v_l=v_ph)
25 disp(sprintf("The power is %f W", p));
26
27 var=sqrt(3)*v_ph*I_1*sin(phi);
28 var=var/1000; //from VAR to
    kVAR
29 disp(sprintf("The reactive power is %f kVAR", var));
30
31 va=sqrt(3)*v_ph*I_1;
32 va=va/1000; //from VA to
    kVA
33 disp(sprintf("The total volt amperes is %f kVA", va))
    ;
34
35 //END

```

---

### Scilab code Exa 3.9 400 V 50 Hz three phase supply

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 9
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 v_ab=400; //in Volts
10 v_bc=400; //in Volts
11 v_ac=400; //in Volts

```

```

12 z_ab=100; //in Ohms
13 z_bc=100; //in Ohms
14 z_ac=100; //in Ohms
15
16 //solution (a)
17
18 //function to convert from polar to rectangular form
19 function [x,y]=pol2rect(mag,angle);
20 x=mag*cos(angle);
21 y=mag*sin(angle);
22 endfunction;
23
24 I_AB=v_ab/z_ab;
25 mag1=abs(real(I_AB));
26 ang1=0; //I_AB is represented as
           mag1 ang1
27 I_BC=v_bc/z_bc;
28 ang2=-210*(%pi/180); //I_BC is represented
           as mag1 ang2
29 I_AC=v_ac/z_ac;
30 ang3=210*(%pi/180); //I_AC is represented
           as mag1 ang3
31 [x1,y1]=pol2rect(I_AB,ang1);
32 [x2,y2]=pol2rect(I_BC,ang2);
33 [x3,y3]=pol2rect(I_AC,ang3);
34 //let us consider values X1, Y1, X2, Y2, X3 and Y3
           for the ease of calculation (these are not
           mentioned in the book)
35 X1=x1-x3;
36 Y1=y1-y3;
37 X2=x2-x1;
38 Y2=y2-y1;
39 X3=x3-x2;
40 Y3=y3-y2;
41 I_A=X1+(%i*Y1);
42 I_B=X2+(%i*Y2);
43 I_C=X3+(%i*Y3);
44

```

```

45 //function to convert from rectangular to polar form
46 function [z,angle]=rect2pol(x,y);
47 z=sqrt((x^2)+(y^2)); //z is impedance &
    the resultant of x and y
48 if(x==0 & y>0) then angle=90; //in case atan=
49 elseif(x==0 & y<0) then angle=-90 //in case atan=-
50 else
51 angle=atan(y/x)*(180/%pi); //to convert the
    angle from radians to degrees
52 end;
53 endfunction;
54
55 [mag4 ,ang4]=rect2pol(X1 ,Y1 );
56 [mag5 ,ang5]=rect2pol(X2 ,Y2 );
57 [mag6 ,ang6]=rect2pol(X3 ,Y3 );
58 disp(sprintf("(a) The line current I_A is %f %f A"
    ,mag4 ,ang4));
59 disp(sprintf("The line current I_B is %f %f A",
    mag5 ,(180+ang5)));
60 disp(sprintf("The line current I_C is %f %f A",
    mag6 ,ang6));
61
62 //solution (b)
63 //since power is consumed only by 100 resistance
    in the arm AB
64 r1=100;
65 p1=(I_AB^2)*r1;
66 p2=160000;
67 r2=p2/p1;
68 disp(sprintf("(b) The star connected balanced
    resistance is %d ",r2));
69
70 //END

```

---

### Scilab code Exa 3.11 Balanced load of 20kVA

```
1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 11
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 11");
7
8 //SOLUTION
9 function power_sum=p1(phi);
10 power_sum=20*cos(phi); //power_sum=
    p1+p2=20*cos(phi) and in KiloWatts
11 endfunction;
12 function power_diff=p2(phi);
13 power_diff=(20*sin(phi))/sqrt(3); //power_diff=
    p1-p2=(20*sin(phi))/sqrt(3) and in KiloWatts
14 endfunction;
15
16 //solution (a): when phi=0
17 power_sum=20*cos(0); //eq(i)
18 power_diff=(20*sin(0))/sqrt(3); //eq(ii)
19 //solving eq(i) and eq(ii) to get values of p1 and
    p2
20 A=[1 1;1 -1];
21 b=[power_sum;power_diff];
22 x=inv(A)*b;
23 x1=x(1,:); //to access
    the 1st row of 2X1 matrix
24 x2=x(2,:); //to access
    the 2nd row of 2X1 matrix
25 disp("Solution (a)");
26 disp(sprintf("P1 + P2 = %d kW",power_sum));
27 disp(sprintf("P1 - P2 = %d kW",power_diff));
28 disp(sprintf("The two wattmeter readings are %d kW
    and %d kW",x1,x2));
29
30 //solution (b): when phi=30 or %pi/6 (lagging)
```

```

31 power_sum=20*cos(%pi/6);
32 power_diff=(20*sin(%pi/6))/sqrt(3);
33 A=[1 1;1 -1];
34 b=[power_sum;power_diff];
35 x=inv(A)*b;
36 x1=x(1,:);
37 x2=x(2,:);
38 disp("Solution (b)");
39 disp(sprintf("P1 + P2 = %f kW",power_sum));
40 disp(sprintf("P1 - P2 = %f kW",power_diff));
41 disp(sprintf("The two wattmeter readings are %f kW
        and %f kW",x1,x2));
42
43 //solution (c): when phi=60 or %pi/3
44 power_sum=20*cos(%pi/3);
45 power_diff=(20*sin(-(pi/3)))/sqrt(3); //leading
46 A=[1 1;1 -1];
47 b=[power_sum;power_diff];
48 x=inv(A)*b;
49 x1=x(1,:);
50 x2=x(2,:);
51 disp("Solution (c)");
52 disp(sprintf("P1 + P2 = %f kW",power_sum));
53 disp(sprintf("P1 - P2 = %f kW",power_diff));
54 disp(sprintf("The two wattmeter readings are %f kW
        and %f kW",x1,x2));
55
56 //solution (d): when phi=90 or %pi/2
57 power_sum=20*cos(%pi/2);
58 power_diff=(20*sin(%pi/2))/sqrt(3); //leading
59 A=[1 1;1 -1];
60 b=[power_sum;power_diff];
61 x=inv(A)*b;
62 x1=x(1,:);
63 x2=x(2,:);
64 disp("Solution (d)");
65 disp(sprintf("P1 + P2 = %f kW",power_sum));
66 disp(sprintf("P1 - P2 = %f kW",power_diff));

```

```

67 disp(sprintf("The two wattmeter readings are %f kW
    and %f kW",x1,x2));
68
69 //END

```

---

**Scilab code Exa 3.12** Three identical impedances each having a resistance R

```

1 //CHAPTER 3- THREE-PHASE A.C. CIRCUITS
2 //Example 12
3
4 clc;
5 disp("CHAPTER 3");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 v_1=400;                                //in Volts
10 f=50;                                    //in Hertz
11 w1=2000;                                 //in Watts
12 w2=800;                                  //in Watts
13
14 //SOLUTION
15 //solution (a)
16 p1=w1+w2;
17 p2=w1-w2;
18 phi=atan(sqrt(3)*p2)/p1;      //this equation comes
                                from two-wattmeter method
19 pow_fact=cos(phi);
20 disp(sprintf("(a) The power factor of the circuit is
    %f (leading)",pow_fact));
21
22 //solution (b)
23 I_1=p1/(sqrt(3)*v_1*pow_fact);
24 disp(sprintf("(b) The line current is %f A",I_1));
25

```

```
26 //solution (c)
27 v_ph=v_l/sqrt(3);
28 z_ph=v_ph/I_l; //phase current = line
                  current for delta connection
29 r_ph=z_ph*pow_fact;
30 disp(sprintf("(c) The resistance of each phase is %f
                 ",r_ph));
31 xc=sqrt((z_ph^2)-(r_ph^2));
32 c=1/(2*pi*f*xc);
33 disp(sprintf("The capacitance of each phase is %E F"
                 ,c));
34
35 //END
```

---

# Chapter 4

## Measuring Instruments

**Scilab code Exa 4.1** Deflecting torque exerted on a coil

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 1
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 N=10;           //number of turns
10 I=5;           //in amperes
11 B=500;          //flux density in Wb/m^2
12 ar=15/10000;    //area in m^2
13
14 //SOLUTION
15 T_d=N*B*I*ar;
16 disp(sprintf("The deflecting torque exerted on the
   coil is %f N-m",T_d));
17
18 //END
```

---

### Scilab code Exa 4.2 Current through galvanometer

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 2
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 G=10;           //galvanometer resistance in Ohms
10 S=1;           //shunt resistance in Ohms
11 r=12;          //total resistance in Ohms
12 emf=2;         //emf of cell in Volts
13
14 //SOLUTION
15 I=emf/r;       //current in the circuit
16 I_g=(S*I)/(S+G);
17 disp(sprintf("The current through the galvanometer
18           is %f A",I_g));
19 //END
```

---

### Scilab code Exa 4.3 Resistance of wire

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 3
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 3");
7
```

```

8 //VARIABLE INITIALIZATION
9 I=1;                      //in Amperes (I=1 is an
   assumption)
10 I_g=I/100;                //in Amperes
11 G=2970;                  //in Ohms
12
13 //SOLUTION
14 S=(G*I_g)/(I-I_g); //since I_g=(S*I)/(S+G);
15
16 disp(sprintf("The wire should have a resistance of
   %f    ",S));
17
18 //END

```

---

**Scilab code Exa 4.4** Resistance required to read current and voltage

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 4
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 r_A=10;                      //in Ohms
10 I_A=15/1000;                 //from mA to A
11 I=100;                       //in A
12 V=500;                       //in Volts
13
14 //SOLUTION
15
16 //solution (a)
17 R_sh=r_A/((I/I_A)-1); //((I/I_A) is the
   multiplying factor of the shunt
18

```

```

19 disp(sprintf("The required shunt resistance is %f
",R_sh));
20
21 //solutuion (b)
22 r=V/I_A;                                // total resistance
23 R_se=r-r_A;
24 disp(sprintf("The required resistance to be added in
series is %f ",R_se));
25
26 //END

```

---

**Scilab code Exa 4.5** Number of revolutions made by energy meter and percentage error

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 5
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 m_c=100;                                // meter constant in rev/
kWh
10 I=20;                                    //load current in Amperes
11 v=230;                                    //supply voltage in Volts
12 pow_fact=0.8;
13 rev_act=360;                            //actual number of
revolutions
14
15 //SOLUTION
16 E=(v*I*pow_fact)/1000;                  // 'E' is energy consumed
in one hour in kWh
17 rev=m_c*E;                             //number of revolutions

```

```

        for true energy
18 disp(sprintf("The number of revolutions made by the
    meter is %f",rev));
19 err=(rev_act-rev)/rev;      //error
20 err=err*100;              //percentage error
21 disp(sprintf("The percentage error is %f %%",err));
22 if(err<0) then
23 disp("The negative sign indicates that the meter
    will run slow");
24 end
25
26 //END

```

---

**Scilab code Exa 4.6** Series resistance to measure 500 V on full scale

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 6
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 I_m=20/1000;           //full scale deflection in
    Ampères
10 v_m=50/1000;          //applied potential difference
    in Volts
11 v=500;                //in Volts
12
13 //SOLUTION
14 r_m=v_m/I_m;          //resistance of moving-coil
    instrument
15 r_s=(v/I_m)-r_m;
16 disp(sprintf("The series resistance to measure 500 V
    on full scale is %f    ",r_s));

```

```
17
18 //END
```

---

### Scilab code Exa 4.7 Percentage error of energy meter

```
1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 7
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 m_c=100;           //meter constant in rev/kwh
10 I=20;             //in Amperes
11 v=210;            //in Volts
12 pow_fact=0.8;     //leading
13 rev_act=350;      //actual revolution
14
15 //SOLUTION
16 E=(v*I*pow_fact)/1000; //from Wh to kWh
17 rev_true=m_c*E;
18 disp(sprintf("The number of revolutions made by the
   meter is %f",rev_true));
19 err=(rev_act-rev_true)/rev_true;
20 err=err*100;        //percentage error
21 disp(sprintf("The percentage error is %f %%",err));
22 if(err<0) then
23   disp("The negative sign indicates that the meter
   will run slow");
24 end
25
26 //END
```

---

**Scilab code Exa 4.8** Resistance required to read current and voltage

```
1 //CHAPTER 4- MEASURING INSTRUMENTS
2 //Example 8
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 I_m=15/1000;           //from mA to A
10 r_m=5;                //in Ohms
11 I=2;                  //in Amperes
12 v=30;                 //in Volts
13
14 //SOLUTION
15 R_sh=(I_m*r_m)/I;    //I_m=I*(R_sh/(R_sh+r_m)) if
   R_sh<<5 , then I_m=I*(R_sh/r_m) neglecting R_sh
   in the denominator
16 disp(sprintf("In order to read upto 2A, a shunt of
   %f has to be connected in parallel",R_sh));
17
18 R_se=(v-(I_m*r_m))/I_m;
19 disp(sprintf("In order to read upto 30V, a
   resistance of %f has to be connected in series
   ",R_se));
20
21 //END
```

---

**Scilab code Exa 4.9** Percentage error of meter

```
1 //CHAPTER 4- MEASURING INSTRUMENTS
```

```

2 //Example 9
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 I=50;                                //in Amperes
10 v=230;                                 //in Volts
11 rev=61;                                //revolutions
12 t=37/3600;                            //from seconds to hours
13 m_c=500;                               //meter constant in rev/
    kwh
14 pow_fact=1;                           //since load is purely
    resistive
15
16 //SOLUTION
17 E1=(v*I*t*pow_fact)/1000; //energy consumed in 37
    seconds in kWh
18 E2=rev/m_c;                          //energy consumption
    registered by meter
19 err=(E2-E1)/E1;
20 err=err*100;                         //percentage error
21 disp(sprintf("The percentage error is %f %%",err));
22 if(err<0) then
23 disp("The negative sign indicates that the meter
    will run slow");
24 end
25
26 //END

```

---

**Scilab code Exa 4.10** Readings of two voltmeters

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 10

```

```

3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 r1=2; //in Ohms (r1=2 is an
       assumption)
10 r2=2; //in Ohms (since r1=r2)
11 v=100; //in Volts
12
13 //SOLUTION
14 v1=(v*r1)/(r1+r2); //voltage divider law
15 v2=(v*r2)/(r1+r2); //voltage divider law
16 disp(sprintf("Reading of the 1st voltmeter is %d V",
      v1));
17 disp(sprintf("Reading of the 2nd voltmeter is %d V",
      v2));
18
19 //END

```

---

**Scilab code Exa 4.11** Readings of two voltmeters with different internal resistances

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 11
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 r1=30000; //in Ohms
10 r2=20000; //in Ohms
11 v=600; //in Volts

```

```

12
13 //SOLUTION
14 v1=(r1*v)/(r1+r2);      //voltage divider law
15 v2=(r2*v)/(r1+r2);      //voltage divider law
16 disp(sprintf("Reading of the 1st voltmeter is %d V",
   v1));
17 disp(sprintf("Reading of the 2nd voltmeter is %d V",
   v2));
18
19 //END

```

---

### Scilab code Exa 4.12 Total current carried by two ammeters

```

1 //CHAPTER 4– MEASURING INSTRUMENTS
2 //Example 12
3
4 clc;
5 disp("CHAPTER 4");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 I1=1;                      //full scale current in 1st
                               ammeter in mA
10 I2=10;                     //full scale current in 2nd
                               ammeter in mA
11 r1=100;                    //internal resistance of 1st
                               ammeter in Ohms
12 r2=25;                     //internal resistance of 2nd
                               ammeter in Ohms
13
14 //SOLUTION
15 R1=r2/(r1+r2);           //resistance for 1st ammeter
16 R2=r1/(r1+r2);           //resistance for 2nd ammeter
17 I=I1/R1;                  //by current divider law I1=(I*
                               r2)/(r1+r2) =>I1=I*R1 =>I=I1/R1

```

```
18 A2=I*R2;           //A2=reading of second ammeter
19 disp(sprintf("The total current that the two
    ammeters can carry is %d mA",I));
20
21 //END
```

---

# Chapter 6

## Magnetic Circuits

**Scilab code Exa 6.1** Magnetic circuit having two air gaps

```
1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 1
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 lA=17/100;           //length of A in meters (lA is
                      calculated in the solution in the book; here it
                      is initialised directly for the sake of
                      convinience)
10 l=3/100;             //in meters
11 lg=2/1000;           //width of air-gap in meters
12 N=1000;              //number of turns
13 AB=10/100;            //in meters
14 BC=20/100;            //in meters
15 CD=10/100;            //in meters
16 I=1;                  //exciting current in Amperes
17 murA=1000;            //relative permeability of part A
18 murB=1200;            //relative permeability of part B
```

```

19 mu0=4*%pi*10^(-7); // absolute permeability in Henry/
    meters
20
21 //SOLUTION
22
23 //solution ( i )
24 ar=l*l; //area of cross-section
25 rA=lA/(mu0*murA*ar);
26 disp(sprintf("( i) Reluctance of part A is %E AT/Wb" ,
    rA));
27 lB=(AB-(1/2))+(BC-1)+(CD-(1/2));
28 rB=lB/(mu0*murB*ar);
29 disp(sprintf("Reluctance of part B is %E AT/Wb" ,rB))
    ;
30
31 //solution ( ii )
32 lg=2*lg;
33 murg=1;
34 rg=lg/(mu0*murg*ar);
35 disp(sprintf("( ii) Reluctance of the two air gaps is
    %E AT/Wb" ,rg));
36
37 //solution ( iii )
38 rT=rA+rB+rg;
39 disp(sprintf("( iii) Total reluctance is %E AT/Wb" ,rT
    ));
40
41 //solution ( iv )
42 mmf=N*I;
43 disp(sprintf("( iv) MMF is %d AT" ,mmf));
44
45 //solution ( v )
46 totFlux=mmf/rT;
47 disp(sprintf("( v) Total flux is %E Wb" ,totFlux));
48
49
50 //solution ( vi )
51 b=totFlux/ar;

```

```

52 disp(sprintf("( vi) Flux density is %f Wb/m^2" ,b));
53
54 //Answers of (v) and (vi) do not match due to
55 // calculation mistake in the book
56 //END

```

---

### Scilab code Exa 6.2 Steel ring of 25 cm mean diameter

```

1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 2
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 dr=25/100;                                //diameter of steel
10 ds=3/100;                                  //diameter of
11 lg=1.5/1000;                               //length of air-gap
12 N=700;                                     //number of turns
13 mu0=4*pi*10^(-7);                         //absolute
14 I=2;                                       //in Amperes
15
16 //SOLUTION
17
18 //solution ( i )
19 mmf=N*I;
20 disp(sprintf("( i) MMF is %d AT" , mmf));
21
22 //solution ( ii )

```

```

23 netMMF=(mmf-(0.35*mmf));           //mmf taken by iron
   path is 35% of total mmf
24 b=(mu0*netMMF)/lg;                 // phi=b*area , r=lg
   /(mu0*area) & mmf=phi*r => mmf=(b*lg)/mu0 => b=(
   mmf*mu0)/lg
25 disp(sprintf("( ii ) The flux density of the air gap
   is %E Wb/m^2" , b));
26
27 //solution ( iii )
28 ar=%pi*((ds/2)^2);                // area of cross-
   section of circular section
29 phi=ar*b;
30 disp(sprintf("( iii ) The magnetic flux is %E Wb" ,phi))
   );
31
32 //solution ( iv )
33 rt=mmf/phi;
34 disp(sprintf("( iv ) The total reluctance is %E AT/wb"
   ,rt));
35
36 //solution ( v )
37 rg=lg/(mu0*ar);                  // reluctance of air
   gap
38 rs=rt-rg;                        // reluctance of
   steel
39 lr=%pi*dr;                      // circumference of
   ring
40 mur=lr/(mu0*rs*ar);
41 disp(sprintf("( v ) The relative permeability of the
   steel ring is %E" ,mur));
42
43 //solution ( vi )
44 disp(sprintf("( vi ) Reluctance of steel is %E AT/Wb" ,
   rs));
45
46 //END

```

---

### Scilab code Exa 6.3 Magnetic circuit with cast steel core

```
1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 3
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 lg1=0.025/100;                                //length of 1st air-
   gap in m
10 a1=(1*1)/10000;                               //in m^2
11 lg2=0.02/100;                                 //length of 2nd air-
   gap in m
12 a2=(1*1)/10000;                               //in m^2
13 lg3=0.02/100;                                 //length of 3rd air-
   gap in m
14 a3=(2*1)/10000;                               //in m^2
15 phi=0.75/1000;                                //flux in Wb
16 lc1=0.5;                                     //length through outer
   limb in m
17 lc2=0.5;                                     //length through outer
   limb in m
18 lc3=0.2;                                     //length through
   central limb in m
19 mu0=4*pi*10^(-7);                            //absolute
   permeability in Henry/m
20
21 //SOLUTION
22
23 //solution (a): when mur=infinity i.e., no mmf drops
   in any member of the core
24 rg1=lg1/(mu0*a1);                            //reluctance of 1st
```

```

        air-gap
25 rg2=lg2/(mu0*a2);           // reluctance of 2nd
        air-gap
26 rg3=lg3/(mu0*a3);           // reluctance of 3rd
        air-gap
27 rgeq=(rg1*rg2)/(rg1+rg2);   // parallel combination
        of resistors
28 mmf1=phi*(rg1+rg3);
29 mmf1=round(mmf1);           // to round off the
        value
30 disp(sprintf("(a) MMF of the exciting coil when
        permeability is infinity is %d AT",mmf1));
31
32 // solution (b): when mur=5000 i.e., reluctance of
        magnetic core must be considered
33 mur=5000;
34 rc1=lc1/(mu0*mur*a1);       // reluctance of first
        path in the core
35 rc2=lc2/(mu0*mur*a2);       // reluctance of second
        path in the core
36 rc3=lc3/(mu0*mur*a3);       // reluctance of third
        path in the core
37 r1=rg1+rc1;
38 r2=rg2+rc2;
39 r3=rg3+rc3;
40 req=(r1*r2)/(r1+r2);
41 totr=req+r3;                // total resistance
42 mmf2=phi*totr;
43 mmf2=round(mmf2);
44 disp(sprintf("(b) MMF of the exciting coil when
        permeability is 5000 is %d AT",mmf2));
45
46 //END

```

---

**Scilab code Exa 6.4** Iron ring made of round iron rod

```

1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 4
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 di=10;                                //diameter of iron
10 dr=1.5;                               //diameter of iron
11 mui=900;                             //relative permeability of rod
12 mu0=4*pi*10^(-7);                   //absolute permeability in Henry/m
13 lg=5/10;                            //length of air-gap
14 N=400;                               //number of turns
15 I=3.4;                               //current through
16                                         the winding in Amperes
17 //SOLUTION
18 li=(di*pi)-lg;                      //length of iron
19 area=((dr^2)*pi)/4;                  //area of iron cross
20                                         -section
21 //solution (a)
22 mmf=(4*pi*N*I)/10;                 //in gilberts , since
23                                         1 AT=(4*pi)/10
24 mmf=round(mmf);                     //to round off the
25                                         value
26 disp(sprintf("(a) MMF is %d Gilberts",mmf));
27
28 //solution (b)
29 //tot reluctance = iron reluctance + air gap
30                                         reluctance(mur=1 for air)

```

```

28 totR=(li/(area*mu0*mui))+(lg/(area*mu0*1));
29 disp(sprintf("(b) The total reluctance is %E
    Gilberts/Maxwell",totR));
30
31 //solution (c)
32 phi=mmf/totR;
33 disp(sprintf("(c) The flux in the circuit is %f
    Maxwell",phi));
34
35 //solution (d)
36 b=phi/area;
37 disp(sprintf("(d) The flux density in the circuit is
    %f Gauss",b));
38
39 //Answers of (b), (c) & (d) are different because
    absolute permeability is not included in (b)
40
41 //END

```

---

### Scilab code Exa 6.5 Ring made of composite material

```

1 //CHAPTER 6– MAGNETIC CIRCUITS
2 //Example 5
3
4 clc;
5 disp("CHAPTER 6");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 li=100/100;                                //length of iron part
    in m
10 ls=200/100;                                //length of steel
    part in m
11 lg=1/100;                                   //length of air gap
    in m

```

```

12 ai=20/10000; //cross-sectional
    area of iron in m^2
13 as=10/10000; //cross-sectional
    area of steel in m^2
14 ag=20/10000; //cross-sectional
    area of air-gap in m^2
15 muRi=300; //relative
    permeability of iron
16 muRs=900; //relative
    permeability of steel
17 muRg=1; //relative
    permeability of air
18 N=170; //number of turns
19 phi=9000*10^(-8); //flux in Wb (1 line
    = 10^(-8) Wb)
20 lkg=1.2; //leakage coefficient
21 mu0=4*pi*10^(-7); //absolute
    permeability in Henry/m
22
23 //SOLUTION
24 rg=lg/(mu0*muRg*ag);
25 mg=rg*phi;
26 mg=round(mg); //to round off the
    value
27 disp(sprintf("MMF of the air gap is %d AT",mg));
28
29 ri=li/(mu0*muRi*ai); //reluctance of iron
    paths
30 mi=lkg*ri*phi; //MMF for iron path
31 mi=round(mi);
32 disp(sprintf("MMF of iron is %d AT",mi));
33
34 rs=ls/(mu0*muRs*as); //reluctance of steel
    paths
35 ms=lkg*rs*phi; //MMF for steel path
36 ms=round(ms);
37 disp(sprintf("MMF of cast steel is %d AT",ms));
38

```

```
39 totMMF=mg+mi+ms;
40 I=totMMF/N;
41 disp(sprintf("Current through the coil is %f A",I));
42
43 //END
```

---

# Chapter 7

## Single Phase Transformer

**Scilab code Exa 7.1** To calculate magnetizing component of no load current

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 1
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 I_0=10;                                //no load current in
                                         Ampères
10 pf=0.25;                                //power factor
11 v1=400;                                  //in Volts
12 f=50;                                    //in Hertz
13
14 //SOLUTION
15
16 //solution (a)
17 //magnetizing component
18 //Iphi=I0.sin theta
19 theta=acos(pf);                         //taking value of
```

```

        theta from the given power factor
20 I_phi=I_0*sin(theta);
21 disp(sprintf("(a) The magnetizing component of no
      load current is %.2f A",I_phi));
22
23 //solution (b)
24 //iron loss
25 //Pc=V1.Ic
26 //Ic=I0.cos theta & also Ic=I0.pf as pf=cos theta
27 p_c=v1*I_0*pf;
28 disp(sprintf("(b) The iron loss is %d W",p_c));
29
30 //solution (c)
31 N1=500;                                // number of turns in
      primary given
32 phi_m=v1/(sqrt(2)*pi*f*N1);
33 disp(sprintf("(c) The maximum value of flux in the
      core is %.2f mWb",phi_m*1000));
34
35 //END

```

---

**Scilab code Exa 7.2** To calculate the primary current

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 2
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 2");
7 //
8 //400/200V transformer
9 //VARIABLE INITIALIZATION
10 v1=400;                               //primary voltage in
      Volts
11 v2=200;                               //secondary voltage

```

```

        in Volts
12 I0=1;                                //in Amperes
13 pf1=0.4;                               //power factor in
   degrees on no load
14 I2=50;                                 //secondary current
   in Amperes
15 pf2=0.8;                               //secondary supplies
   lagging power factor in degrees
16
17 //SOLUTION
18 //primary current is given by
19 //I1=I0+I2
20 //function to convert from polar to rectangular form
21 function [x,y]=pol2rect(mag,angle1);
22 x=mag*cos(angle1);
23 y=mag*sin(angle1);
24 endfunction;
25 //
26 phi_0=acos(pf1);                      // cosine inverse of
   the power factor which is given
27 phi=acos(pf2);                        // cosine inverse of
   the power factor which is given
28 I2_dash=(v2*I2)/v1;                   //v1.i1=v2.i2
29 //I0=1 < phi_0 in polar format
30 [x0,y0]=pol2rect(I0,-phi_0);
31 [x2_dash,y2_dash]=pol2rect(I2_dash,-phi);
32 I1_x=x0+x2_dash;                     //x-component of I1
33 I1_y=y0+y2_dash;                     //y-component of I1
34 disp(sprintf("The primary current in reactangular
   form is (%.3f-j%.2f) A",I1_x,-I1_y));
35 //
36 //function to convert from rectangular form to polar
   form
37 function [I,angle]=rect2pol(x,y);
38 I=sqrt((x^2)+(y^2));
39 angle=atan(y/x)*(180/pi);           //to convert the
   angle from radians to degrees
40 endfunction;

```

```

41 [I,angle]=rect2pol(I1_x,I1_y);           // converting
   current from rectangular to polar form
42 disp(sprintf("The primary current in polar form is (
   %.3f <% .2f ) A",I,angle));
43 //END

```

---

**Scilab code Exa 7.3** To find the voltage regulation

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 3
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 3");
7 //
8 //2300/230 V 50 Hz transformer
9 //VARIABLE INITIALIZATION
10 v1=2300;                                //primary
    voltage in Volts
11 v2=230;                                  //secondary
    voltage in Volts
12 f=50;
13 R1=0.286;
14 X1=0.73;
15 R_dash_2=0.319;
16 X_dash_2=0.73;
17 Rc=250;
18 Xphi=1250;
19 Z1=0.387+0.29*i;
20 //
21 //SOLUTION
22 Z_e1=(R1+R_dash_2)+(X1+X_dash_2)*%i;
23 Z_dash_1=(v1/v2)^2*Z1;
24 //
25 I_dash_1=v1/(Z_dash_1+Z_e1);

```

```

26 // [mag, angle]=rect2pol( real(I_dash_1) ,imag( I_dash_1 )
27 // );
28 //disp( sprintf(" The current is %f <%f A" ,mag, angle
29 //));
30 //impedance of shunt branch
31 Zm=Rc*(Xphi*%i)/(Rc+Xphi*%i);
32 // [mag, angle]=rect2pol( real(Zm) ,imag(Zm) );
33 //disp( sprintf(" The Zm is %f <%f A" ,mag, angle));
34 I0=v1/Zm;
35 // [mag, angle]=rect2pol( real(I0) ,imag( I0 ) );
36 //disp( sprintf(" The I0 is %f <%f A" ,mag, angle));
37 //
38 //primary current
39 I1=I0+I_dash_1;
40 function [mag, angle]=rect2pol(x,y);
41 mag=sqrt((x^2)+(y^2)); //z is impedance &
42 // the resultant of x and y
43 angle=atan(y/x)*(180/%pi); //to convert the
44 // angle from radians to degrees
45 endfunction;
46 [mag, angle]=rect2pol(real(I1), imag(I1));
47 theta1=angle;
48 disp("SOLUTION ( i )");
49 disp(sprintf("The primay current in rectangulr form
50 is %.3 f -j%.2 f A" ,real(I1),-imag(I1)));
51 disp(sprintf("The primay current in polar form is %
52 .3 f <%2 f A" ,mag, angle));
53 //
54 //input power
55 Pin=v1*I1; //=I1 .cos(
56 //theta1)
57 //disp( sprintf(" The input power is %.3 f kW" ,Pin
58 // /1000));
59 //output power
60 V_dash_2=I_dash_1*Z_dash_1;
61 [mag, angle]=rect2pol(real(V_dash_2), imag(V_dash_2));
62 theta2=angle;
63 //disp( sprintf(" The V_dash_2 is %.2 f <%2 f A" ,mag,

```

```

        angle));
56 // 
57 Pout= V_dash_2*I_dash_1;           // I_dash_1 .
      cos(theta1)
58 // disp(sprintf("The output power is %.3f kW", real(
      Pout)/1000));
59 // Efficiency
60 disp("SOLUTION (ii)");
61 disp(sprintf("The Efficiency is %.2f kW", Pout*100/
      Pin)); // text Book answer is 78.75%
62 // Losses
63 Pc=v1*I0;                         // core loss
64 loss=Pin-Pout;
65 Pcu=loss-Pc;                      // copper
      loss
66 disp(sprintf("The core loss is %.2f kW",Pc/1000));
      //text book answer is 0.8 kW
67 disp(sprintf("The copper loss is %.2f kW",Pcu/1000)
      ); //text book answer is 1..38 kW
68 //efficiency
69 //eff=Pout*100/Pin;
70 //disp(sprintf("The percent efficiency is %f W", eff
      ));
71 disp("");
72 // The answers from V_dash_2 calculation onward do
      not match with the book on page 7.21 and 7.22
73 //END

```

---

### Scilab code Exa 7.4 10 kVA transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 4
3
4 clc;
5 disp("CHAPTER 7");

```

```

6 disp("EXAMPLE 4");
7
8 //10kVA Transformer with 50 turns on primary and 10
9 //turns on secondary
10 //connected to 440 V 50Hz supply
11 //VARIABLE INITIALIZATION
12 va=10*1000; //apparent power ,
13 //converting kVA to VA
12 N1=50; //number of turns on
13 //primary side
13 N2=10; //number of turns on
14 //secondary side
14 v1=440; //primary voltage in
15 //Volts
15 f=50; //in Hertz
16
17 //SOLUTION
18
19 //solution (a)
20 //K=N2/N1=V2/V1
21 v2=v1*(N2/N1);
22 disp(sprintf("(a) The secondary voltage on no load
is %d V",v2));
23
24 //solution (b)
25 //Current on Full load
26 //primary side I1=VA/V1
27 //secondary side I2=VA/V2
28 I1=va/v1;
29 disp(sprintf("(b) The full load primary current is %
.4f A",I1));
30 I2=va/v2;
31 disp(sprintf("The full load secondary current is %.4
f A",I2));
32
33 //solution (c)
34 //As per EMF equation
35 //E2=sqrt(2).pi.f.phimax.N2

```

```

36 phi_m=v2/(sqrt(2)*pi*f*N2);
37 disp(sprintf("(c) The maximum value of the flux is %
38 .3 f mWb",phi_m*1000));
39 //END

```

---

**Scilab code Exa 7.5** Transformer with 350 primary and 1050 secondary turns

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 5
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 5");
7
8 //single phase transformer
9 //350 primary and 1050 secondary turns
10 //VARIABLE INITIALIZATION
11 N1=350;                                //number of turns on
     primary side
12 N2=1050;                                //number of turns on
     secondary side
13 v1=400;                                 //primary voltage in
     Volts
14 f=50;                                    //in Hertz
15 ar=50/10000;                            //cross-sectional area
     of core in m^2
16
17 //SOLUTION
18
19 //solution (i)
20 //emf1=sqrt(2).pi.f.Phimax.N1
21 //Phimax=Bm.Area, Bm=flux density
22 //Bm=e1/sqrt(2).pi.A.f.N1

```

```

23 Bm=v1/(sqrt(2)*%pi*ar*f*N1);
24 disp(sprintf("(i) The maximum flux density is %.4f
Wb/m^2" ,Bm));
25
26 //solution (ii)
27 //e2/e1=n2/n1=K
28 K=N2/N1;
29 e2=K*v1;
30 disp(sprintf("(ii) The induced emf in the secondary
winding is %d V" ,e2));
31
32 //END

```

---

### Scilab code Exa 7.6 Primary current and power factor

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 6
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 6");
7
8 //2200/20V 50Hz single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=2200;                                //primary voltage
     in Volts
11 v2=220;                                  //secondary
     voltage in Volts
12 I=0.6;                                    //exciting
     current in Amperes
13 p_c=361;                                  //core loss in
     Watts
14 I2=60;                                    //load current in
     Amperes
15 pf=0.8;                                  //power factor

```

```

16
17 //SOLUTION
18
19 //solution (a)
20 //core loss components
21 I1=p_c/v1;                                //vertical
22 component of I0
22 I_phi=sqrt((I^2)-(I1^2));                //horizontal
23 component of I0
23 disp(sprintf("(a) The core loss component is %.3f A"
24 ,I1));
24 disp(sprintf("And the magnetising component is %.3f
25 A" ,I_phi));
25
26 //solution (b)
27 //I1.N1=I2.N2
28 I1_dash=(v2/v1)*I2;
29 theta=acos(pf);
30 I1_x=I1_dash*sin(theta)+I_phi;           //horizontal
31 component of I0
31 I1_y=I1_dash*pf+I1;                     //vertical
31 component of I0
32 I1_res=sqrt((I1_x^2)+(I1_y^2));         //primary current
33 pf_p=I1_y/I1_res;                      //primary power
33 factor
34 disp(sprintf("(b) The primary current is %.3f A",
34 I1_res));
35 disp(sprintf("And the power factor is %.3f A" ,pf_p))
35 ;
36
37 //END

```

---

### Scilab code Exa 7.8 Efficiency of transformer

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
```

```

2 //Example 8
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 8");
7
8 //23 kVA 2300/230 V 60 Hz step down transformer
9
10 //VARIABLE INITIALIZATION
11 va=23000;                                //apparent power
12 v1=2300;                                   //primary voltage in
                                              Volts
13 v2=230;                                    //secondary voltage
                                              in Volts
14 r1=4;                                       //primary resistance
                                              in Ohms
15 r2=0.04;                                     //secondary
                                              resistance in Ohms
16 X1=12;                                      //leakage reactance
                                              primary in Ohms
17 X2=0.12;                                     //leake reactance in
                                              secondary in Ohms
18 pf=0.866;                                    //power factor(
                                              leading)
19
20 //SOLUTION
21 //assume voltage across load be 230 V
22 //V'1=I2 .( Re2+jXe2 )+V2
23 //Re2=R'1+R2
24 //R'1=R1 .( N2/N1 ) ^2
25 //Xe2=X'1+X2
26 //X'1=X1 .( N2/N1 ) ^2
27 //Ze2=Re2+j . Xe2
28 r1_dash=r1*((v2/v1)^2);
29 r_e2=r1_dash+r2;
30 X1_dash=X1*((v2/v1)^2);
31 X_e2=X1_dash+X2;
32 //

```

```

33 // disp(sprintf("The value of Re2 %f and Xe2 %f",r_e2
34 ,X_e2));
35 I2=0.75*(va/v2); //since transformer
36 // operates at 75% of its rated load
37 //function [x,y]=pol2rect(mag,angle);
38 x=mag*cos(angle*(%pi/180)); //to convert the
39 // angle from degrees to radians
40 y=mag*sin(angle*(%pi/180));
41 endfunction;
42 [x,y]=pol2rect(I2,-30);
43 I_dash_2=x+y*i;
44 // disp(sprintf("The value %f %f",real(I_dash_2),imag
45 // (I_dash_2)));
46 // Z_e2=r_e2+X_e2*i; //in rect
47 // coordinates
48 // disp(sprintf("The value %f %f",real(Z_e2),imag(
49 // Z_e2)));
50 // V_dash_1=v2+I_dash_2*Z_e2;
51 // disp(sprintf("The value %f %f",real(V_dash_1),imag
52 // (V_dash_1)));
53 //function [mag,angle]=rect2pol(x,y);
54 mag=sqrt((x^2)+(y^2)); //z is impedance &
55 // the resultant of x and y
56 angle=atan(y/x)*(180/%pi); //to convert the
57 // angle from radians to degrees
58 endfunction;
59 // [magV1,angleV1]=rect2pol(real(V_dash_1),imag(
60 // V_dash_1));
61 // disp(sprintf("The value %f <%f",magV1,angleV1));
62 // //Pin=V'1.I2.cos theta1
63 // Pout=V2.I2.cos theta2
64 Pin=magV1*I2*cos((30+angleV1)*%pi/180);

```

```

61 Pout=v2*I2*cos(30*pi/180);
62 eff=Pout*100/Pin;
63 //
64 disp(sprintf("The efficiency of the transformer is %
.2f",eff));
65 disp("");
66 //
67 //END

```

---

### Scilab code Exa 7.9 Core loss current of distribution transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 9
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 9");
7
8 //11000/400 V distribution transformer
9 //VARIABLE INITIALIZATION
10 v1=11000;                                //primary voltage in
                                              Volts
11 v2=400;                                    //secondary voltage
                                              in Volts
12 Io=1;                                      //primary current in
                                              Amp
13 pf=0.24;                                   //power factor
                                              lagging
14
15 //SOLUTION
16 //core loss current
17 //Ic=Io.cos phi
18 //Ic=Io.pf
19 Ic=Io*pf;
20 disp("SOLUTION (a)");

```

```

21 disp(sprintf("The value of core loss current is %.2f
Amp",Ic));
22 //
23 //magnetizing current
24 Iphi=sqrt(Io^2-Ic^2)
25 Iphi=sqrt(Io^2-Ic^2);
26 disp("SOLUTION (b)");
27 disp(sprintf("The value of magnetizing current is %.3
f Amp",Iphi));
28 //
29 //Iron Loss
30 //Iron loss=primary voltage X core loss current
31 IronLoss=v1*Ic;
32 disp("SOLUTION (c)");
33 disp(sprintf("The iron loss is %.0f W",IronLoss));
34 disp("");
35 //
36 //END

```

---

### Scilab code Exa 7.10 Number of turns on HT and LT sides

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 10
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 10");
7
8 //6600/220 V single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=6600;                                //primary voltage in
                                             Volts
11 v2=220;                                   //secondary voltage
                                             in Volts
12 coreA=0.05;                               //core section m^2

```

```

13 fluxD=1.2; //flux density in w/m^2
14 f=50; //Hz
15
16 //SOLUTION
17 //E1=sqrt(2).pi.f.N1. m
18 //flux density = Phimax/core area
19 phiM=coreA*fluxD;
20 N1=v1/(4.44*f*phiM); //4.44=sqrt(2).pi
21 N1=round(N1);
22 //
23 //N2=N1.E2/E1
24 N2=N1*(v2/v1);
25 N2=round(N2);
26 disp(sprintf("The no. of turns on HT side is %d",N1));
27 disp(sprintf("The no. of turns on LT side is %d",N2));
28 disp("");
29 //
30 //END

```

---

**Scilab code Exa 7.11** To calculate primary and full load currents

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 11
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 11");
7
8 //2200/220 V 44 kVA transformer with 50 turns in the
9 //secondary
10 //VARIABLE INITIALIZATION
11 va=44000; //

```

```

11 v1=2200; //primary voltage in
             Volts
12 v2=220; //secondary voltage
             in Volts
13 N2=50; //turns in secondary
            coil
14
15 //SOLUTION
16 // N1/N2=V1/V2
17 N1=N2*(v1/v2);
18 disp("SOLUTION (a)");
19 disp(sprintf("The no. of turns on HT side is %f",N1));
20 //
21 //since losses are negligible , input=output , V1.I1=
            V2.I2
22 I1=va/v1;
23 I2=va/v2;
24 disp("SOLUTION (b)");
25 disp(sprintf("The primary full load current is %.0 f
            Amp",I1));
26 disp(sprintf("The secondary full load current is %.0
            f Amp",I2));
27 disp(" ");
28 //
29 //END

```

---

**Scilab code Exa 7.12** Magnetising component of no load current

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 12
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 12");

```

```

7
8 //no load cuurent of transformer ia 10A at pf of
9 // 0.25 lagging when connected to 400V, 50 Hz supply
10 //VARIABLE INITIALIZATION
11 v1=400; //primary voltage in
12 Volts
13 f=50; //Hz
14 Io=10; //in Amp no load
15 current
16 pf =0.25; //lagging
17 N1=500; //given
18
19 //SOLUTION
20 //magnetizing component of no load current
21 // N1/N2=V1/V2
22 //Iphi=Io.sin phi0
23 //pf=cos phi0
24 phi0=acos(pf);
25 Iphi=Io*sin(phi0);
26 disp("SOLUTION (a)");
27 disp(sprintf("The magnetic component of no load
28 current is %f Amp",Iphi));
29 //
30 //iron loss
31 //Pi=ironloss=power input on no load
32 //Pi=Wo=V1.Io.cos phi0
33 ironLoss=v1*Io*pf;
34 disp("SOLUTION (b)");
35 disp(sprintf("The iron loss on no load is %.0f W",
36 ironLoss));
37 //
38 //maximum flux in the core
39 //E1=sqrt(2).pi.f.N1. m
40 //E1=V1
41 phiM=v1/(4.44*f*N1);
42 disp("SOLUTION (c)");
43 disp(sprintf("The value of flux in the core is %5.4f
44 mWb",phiM*1000));

```

```
39 disp(" ");
40 //
41 //END
```

---

**Scilab code Exa 7.13** Current taken by primary

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 13
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 13");
7 //230/115 V single phase transformer
8 //VARIABLE INITIALIZATION
9 v1=230;                                //primary voltage
   in Volts
10 v2=115;
11 f=50;                                    //Hz
12 Io=2;                                     //in Amp no load
   current
13 pf0 =0.28;                               //lagging
14 I2=20;                                    //
15 pf2=0.8;                                 //lagging
16
17 //SOLUTION
18 //
19 //given power factors in primary and secondary
20 // I1.N1=I2.N2
21 phi0=acos(pf0);
22 phi2=acos(pf2);
23 //let Ix and Iy be the components of I0 and I'1
   along X and Y axes
24 //then
25 //Ix=Io.sin phi0 + I'2.sin phi2
26 //
```

```

27 //Ix=Io.cos phi0 + I'2.cos phi2
28 I_dash_2=I2*v2/v1;
29 Ix=Io*sin(phi0)+I_dash_2*sin(phi2);
30 Iy=Io*cos(phi0)+I_dash_2*cos(phi2);
31 I1=sqrt(Ix^2+Iy^2);
32 disp(sprintf("The current taken by primary is %.1f
   Amp",I1));
33 disp("");
34 //
35 //END

```

---

**Scilab code Exa 7.14** To calculate total resistance and reactance referred to primary

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 14
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 14");
7
8 //1100/110 V 22 kVA single phase transformer
9 //VARIABLE INITIALIZATION
10 va=22000;                                // apparent power
11 v1=1100;                                   //primary voltage in
   Volts
12 v2=110;                                    //secondary voltage
   in Volts
13 R1=2;                                      //in Ohms
14 R2=0.02;                                     //in Ohms
15 X1=5;                                       //in Ohms
16 X2=0.045;                                    //in Ohms
17
18 //SOLUTION
19 //N1/N2=v1/v2;

```

```

20
21 R_dash_2=R2*((v1/v2)^2);
22 X_dash_2=X2*((v1/v2)^2);
23 disp("SOLUTION (a)");
24 disp(sprintf("The equivalent resistance of secondary
    referred to primary is %.1f ",R_dash_2));
25 disp(sprintf("The equivalent reactance of secondary
    referred to primary is %.1f ",X_dash_2));
26 //
27 R_e1=R_dash_2+R1;
28 X_e1=X_dash_2+X1;
29 disp("SOLUTION (b)");
30 disp(sprintf("The total resistance referred to
    primary is %.1f ",R_e1));
31 disp(sprintf("The total reactance referred to
    primary is %.1f ",X_e1));
32 //
33 R_dash_1=R1*((v2/v1)^2);
34 X_dash_1=X1*((v2/v1)^2);
35 disp("SOLUTION (c)");
36 disp(sprintf("The equivalent resistance of secondary
    referred to secondary is %.2f ",R_dash_1));
37 disp(sprintf("The equivalent reactance of secondary
    referred to secondary is %.2f ",X_dash_1));
38 //
39 R_e2=R_dash_1+R2;
40 X_e2=X_dash_1+X2;
41 disp("SOLUTION (d)");
42 disp(sprintf("The total resistance referred to
    secondary is %.3f ",R_e2));
43 disp(sprintf("The total reactance referred to
    secondary is %.3f ",X_e2));
44 //
45 I1=va/v1;
46 I2=va/v2;
47 copperLoss=R1*I1^2+R2*I2^2;
48 disp("SOLUTION (e)");
49 disp(sprintf("The total copper loss is %4.0f W",

```

```
        copperLoss));
50 disp("");
51 //
52 //END
```

---

**Scilab code Exa 7.15** To calculate percent regulation at full load

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 15
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 15");
7 //20kVA single phase transformer
8 //VARIABLE INITIALIZATION
9 va=20000;                                // apparent power
10 v1=2000;                                   // primary voltage
11 v2=200;                                    // secondary voltage
12 R1=2.5;                                     // in Ohms
13 R2=0.04;                                    // in Ohms
14 X1=8;                                       // in Ohms
15 X2=0.07;                                    // in Ohms
16 pf2=0.8;
17
18 //SOLUTION
19 //N1b/N2=v1/v2;
20 I2=va/v2;
21 phi2=acos(pf2);
22 //
23 R_dash_1=R1*((v2/v1)^2);
24 X_dash_1=X1*((v2/v1)^2);
25 //
26 R_e2=R_dash_1+R2;
```

```

27 X_e2=X_dash_1+X2;
28 // disp( sprintf("The total resistance referred to
      secondary is %f    ",R_e2));
29 // disp( sprintf("The total reactance referred to
      secondary is %f    ",X_e2));
30 //
31 //R=ercosphi2+vx.sinphi2
32 //E2=V2+I2 .R
33 V2=v2-(I2*R_e2*pf2+I2*X_e2*sin(phi2));
34 %reg=(v2-V2)*100/v2;
35 disp(sprintf("The secondary terminal voltage is %.2f
      V" ,V2));
36 disp(sprintf("The percent regulation at full load is
      %.2 f" ,%reg));
37 disp("");
38 //
39 //END

```

---

**Scilab code Exa 7.16** Maximum value of percent regulation

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 16
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 16");
7
8 //Values from the previous example.
9 //VARIABLE INITIALIZATION
10 va=20000;                                //apparent power
11 v1=2000;                                   //primary voltage
     in Volts
12 v2=200;                                    //secondary voltage
     in Volts
13 R1=2.5;                                    //in Ohms

```

```

14 R2=0.04; // in Ohms
15 X1=8; // in Ohms
16 X2=0.07; // in Ohms
17 pf2=0.8;
18
19 //SOLUTION
20 //N1/N2=v1/v2;
21 I2=va/v2;
22 phi2=acos(pf2);
23
24 //
25 R_dash_1=R1*((v2/v1)^2);
26 X_dash_1=X1*((v2/v1)^2);
27 //
28 R_e2=R_dash_1+R2;
29 X_e2=X_dash_1+X2;
30 // disp(sprintf("The total resistance referred to
secondary is %f ",R_e2));
31 // disp(sprintf("The total reactance referred to
secondary is %f ",X_e2));
32 //
33 //power factor angle at which regulation is zero is
given by tan.phi2=Re2/Xe2
34 phi2=atan(-R_e2/X_e2);
35 disp(sprintf("The PF at which the regulation is zero
is %.3f",cos(phi2)));
36 //
37 //power factor angle at which regulation is maximum
is given by tan.phi2=Xe2/Re2
38 phi2=atan(X_e2/R_e2);
39 disp(sprintf("The PF at which the regulation is
maximum is %.3f",cos(phi2)));
40 //R=ercosphi2+vx.sinphi2
41 //E2=V2+I2.R
42
43 V2=v2-(I2*R_e2*cos(phi2)+I2*X_e2*sin(phi2));
44 %reg=(v2-V2)*100/v2;
45 disp(sprintf("The maximum value of percent

```

```

        regulation is %.2f ",%reg));
46 disp("");
47 //
48 //END
```

---

**Scilab code Exa 7.17** 200 kVA transformer with 1000 W iron loss and 2000 W copper loss at full load

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 17
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 17");
7
8 //200kVA single phase transformer
9 //VARIABLE INITIALIZATION
10 va=200000;                                //
11 ironLoss=1000;                             // Watts
12 cuLoss=2000;                             // Watts
13 pf=0.8;
14 //
15 //SOLUTION
16 //
17 Pout=va*pf;                               // Full load output
18 loss=ironLoss+cuLoss;
19 Pin=Pout+loss;                            // INPUT=OUTPUT+LOSS
20 eff=Pout*100/Pin;
21 disp("SOLUTION (a)");
22 disp(sprintf("The percent efficiency at full load is
    %.2f",eff));
23 //
24 //at half load
25 Pout=va*pf/2;                           // ironloss is
```

```

        independent of output
27 Pin=Pout+loss;
28 eff=Pout*100/Pin;
29 disp("SOLUTION (b)");
30 disp(sprintf("The percent efficiency at full load is
    %.2f",eff));
31 //
32 //fraction x of copperloss=ironloss for maximum
    efficiency
33 //x^2.cuLoss=ironLoss
34 x=sqrt(ironLoss/cuLoss);
35 Pout=x*va*pf;
36 loss=ironLoss+cuLoss*x^2;
37 Pin=Pout+loss;
38 eff=Pout*100/Pin;
39 disp("SOLUTION (c)");
40 disp(sprintf("The percent efficiency at %f load is %
    .2f ",x,eff));
41
42 disp("");
43 //
44 //END

```

---

**Scilab code Exa 7.18** To calculate all day efficiency

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 18
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 18");
7
8 //400kVA distribution transformer variously loaded
    during day
9 //VARIABLE INITIALIZATION

```

```

10 va=400000; //  

11 ironLoss=1500; // Watts  

12 cuLoss=4000; //Watts  

13 //during the day frommidnight to midnight is as  

   below:  

14 h1=6; // first 6 hours from  

      midnight to 6 hrs  

15 load1=0;  

16 pf1=0;  

17 h2=6; // next 6 hours from  

      6 am to noon  

18 load2=100000; //kVA converted to  

      VA  

19 pf2=0.8;  

20 h3=5; // next from noon to  

      5 pm  

21 load3=400000;  

22 pf3=0.8;  

23 h4=3; // next from 5 pm to  

      8 pm  

24 load4=300000;  

25 pf4=0.7;  

26 h5=4; // next from 8 pm to  

      midnight  

27 load5=200000;  

28 pf5=0.85;  

29 //  

30 //SOLUTION  

31 //  

32 //energy loss at any load=(VA output/VA rated)^2 .  

   Full load cuLoss  

33 loss1=h1*load1;  

34 loss2=h2*(load2/va)^2*cuLoss;  

35 loss3=h3*(load3/va)^2*cuLoss;  

36 loss4=h4*(load4/va)^2*cuLoss;  

37 loss5=h5*(load5/va)^2*cuLoss;  

38 //loss in 24 hours  

39 loss24=loss1+loss2+loss3+loss4+loss5;

```

```

40 // disp(sprintf("The all day loss is %f ",loss24));
41 Pout=h1*load1*pf1+h2*load2*pf2+h3*load3*pf3+h4*load4
   *pf4+h5*load5*pf5;
42 // disp(sprintf("The all day energy output is %f ",
   Pout));
43 Pin=Pout+ironLoss*24+loss24;
44 eff=Pout*100/Pin;
45 disp(sprintf("The all day percent efficiency is %.2f
   ",eff));
46 disp("");
47 //
48 //END

```

---

### Scilab code Exa 7.19 Open circuit and short circuit test

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 19
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 19");
7
8 //Open circuit and short circuit test on 10 kVA
   transformer 500/250 V 50 Hz single phase
   transformer
9 //VARIABLE INITIALIZATION
10 va=10000;                                //apparent power
11 v1=500;                                    //primary
   voltage in Volts
12 v2=250;                                    //secondary
   voltage in Volts
13 f=50;
14 //open circuit parameters
15 Voc=500;
16 Io=2;

```

```

17 Wi=100; // watts HT side
18 Woc=Wi; //just another
19 nomenclature
20 //short circuit test
21 Vsc=25;
22 Isc=20;
23 Wc=90; // watts HT side
24 pf=0.8;
25 //SOLUTION
26 //open circuit
27 phi0=acos(Woc/(v1*Io));
28 Ic=Io*cos(phi0);
29 Iphi=Io*sin(phi0);
30 Rc=v1/Ic;
31 X=v1/Iphi;
32 disp("SOLUTION (a)");
33 disp(sprintf("The value of Ic is %.2f Amp",Ic));
34 disp(sprintf("The value of I is %.2f Amp",Iphi));
35 disp(sprintf("The value of Rc is %.0f Ohm",Rc));
36 disp(sprintf("The value of X is %.0 f ",X));
37 //
38 //short circuit
39 phisc=acos(Wc/(Vsc*Isc));
40 pf1=cos(phisc);
41 R_e1=Vsc*pf1/Isc;
42 Z_e1=Vsc/Isc;
43 X_e1=sqrt(Z_e1^2-R_e1^2);
44 disp(sprintf("The value of Power factor is %.3f",pf1));
45 disp(sprintf("The value of Re1 is %.3f Ohm",R_e1));
46 disp(sprintf("The value of Ze1 is %.3f Ohm",Z_e1));
47 disp(sprintf("The value of Xe1 is %.3 f ",X_e1));
48 //
49 //Regulation and efficiency
50 //% Regulation
51 I1=va/v1;
52 phi=acos(pf);

```

```

53 //R=ercosphi2+vx.sinphi2
54 //E2=V2+I2 .R
55 %reg=(Isc*R_e1*pf+Isc*X_e1*sin(phi))*100/v1;
56 disp("SOLUTION (c(i))");
57 disp(sprintf("The percent regulation at full load is
      %.2f",%reg));
58 //
59 // Efficiency
60 // full load output at pf=0.8
61 Pout=va*pf;
62 ironLoss=Wi;
63 cuLoss=Wc;
64 loss=ironLoss+cuLoss;
65 Pin=Pout+loss;
66 eff=Pout*100/Pin;
67 disp("SOLUTION (c(ii))");
68 disp(sprintf("The percent efficiency at full load is
      %.2f",eff));
69 disp(" ");
70 //
71 //END

```

---

### Scilab code Exa 7.20 4kVA 200 400 V transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 20
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 20");
7
8 //4 kVA 200/400 V 50 hz single phase transformer
9 //VARIABLE INITIALIZATION
10 va=4000;                                //apparent power
11 v1=200;                                    //primary

```

```

        voltage in Volts
12 v2=400;                                //secondary
        voltage in Volts
13 f=50;
14 R_e1=0.15;
15 Pi=60;                                  //core losses
        iron core
16 pf1=0.9;                                //power factor
        of primary
17 pf2=0.8;                                //power factor
        of secondary
18
19 //SOLUTION
20 //Copper loss on full load
21 R_e2=(v2/v1)^2*R_e1;
22 I1=va/v1;
23 I2=va/v2;
24 Pcu=I2^2*R_e2;                          //cu losses
25 disp("SOLUTION ( i )");
26 disp(sprintf("The value of Copper Losses at full
load is %.0f W",Pcu));
27 //
28 //efficiency
29 Pout=va*pf1;
30 Pin=Pout+Pi+Pcu;
31 eff=Pout*100/Pin;
32 disp("SOLUTION ( ii )");
33 disp(sprintf("The percent efficiency at full load %f
PF is %.2f",pf1,eff));
34 //
35 //
36 //efficiency at half load
37 Pout=va*pf2/2;
38 Pin=Pout+Pi+Pcu*(1/2)^2;
39 eff=Pout*100/Pin;
40 disp("SOLUTION ( ii )");
41 disp(sprintf("The percent efficiency at half load %f
PF is %.2f",pf2,eff));

```

```
42
43 disp(" ");
44 //
45 //END
```

---

**Scilab code Exa 7.21** To determine the regulation while supplying full load

```
1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 21
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 21");
7
8 //250/125 V 5kVA single phase transformer
9 //VARIABLE INITIALIZATION
10 va=5000;                                //apparent power
11 v1=250;                                   //primary
12 v2=125;                                   //secondary
13 R1=0.2;                                    //resistance of
14          primary
15 X1=0.75;                                  //leakage
16          reactance of primary
17 R2=0.05;                                   //resistance of
18          secondary
19 X2=0.2;                                    //leakage
20          reactance of secondary
21 pf=0.8;                                    //power factor (
22          leading)
23
24 //SOLUTION
25 R_e2=(v2/v1)^2*R1+R2;
```

```

21 X_e2=(v2/v1)^2*X1+X2;
22 I1=va/v1;
23 I2=va/v2;
24 //
25 //at full load leading
26 phi=acos(pf);
27 %reg=(I2*R_e2*pf-I2*X_e2*sin(phi))*100/v2;
28 disp("SOLUTION ( i )");
29 disp(sprintf("The percent regulation at full load is
    %.2f",%reg));
30 //
31 //R=(E2-V2).100/E2
32 V2=v2-%reg*v2/100;
33 disp("SOLUTION ( ii )");
34 disp(sprintf("The secondary terminal voltage at full
    load is %.2f V",V2));
35 disp("");
36 //
37 //END

```

---

**Scilab code Exa 7.22** Total equivalent resistance referred to primary and secondary

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 22
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 22");
7
8 //6600/400 V single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=6600;                                //primary
     voltage in Volts
11 v2=400;                                   //secondary

```

```

        voltage in Volts
12 R1=2.5;                                //primary
    resistance
13 R2=0.01;                                //secondary
    resistance
14
15 //SOLUTION
16 //while finding equivalent resistance referrd to
    primary
17 //transfer R2 resistance to R'2
18 R_dash_2=R2*(v1/v2)^2;
19 R_e1=R1+R_dash_2;
20 //
21 //to find total equivalent resistance referred to
    secondary
22 //first calculate R'1
23 R_dash_1=R1*(v2/v1)^2;
24 R_e2=R2+R_dash_1;
25 //
26 disp(sprintf("The total equivalent resistance
    referred to primary is %.6f ",R_e1));
27 disp(sprintf("The total equivalent resistance
    referred to secondary is %.6f ",R_e2));
28 disp("");
29 //
30 //END

```

---

### Scilab code Exa 7.23 33 kVA 2200 220 V 50 Hz transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 23
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 23");

```

```

7
8 //33kVA 2200/220 V 50Hz single phase transformer
9 //VARIABLE INITIALIZATION
10 va=33000;
11 v1=2200;                                // primary
   voltage in Volts
12 v2=220;                                 // secondary
   voltage in Volts
13 f=50;                                    // frequency in
   Hz
14 R1=2.4;                                  // primary
   winding (High Voltage side) resistance
15 X1=6;                                    // primary
   winding (High Voltage side) leakage reactance
16 R2=0.03;                                 // secondary
   winding (Low Voltage side) resistance
17 X2=0.07;                                // secondary
   winding (Low Voltage side) leakage reactance
18
19 //SOLUTION
20 //
21 //Primary resistance and leakage reactance referred
   to secondary
22 //R'1 & X'1
23 //Secondary resistance and leakage reactance
   referred to primary
24 //R'2 & X'2
25 //Equivalent resistance & leakage reactance referred
   to primary
26 //Re1 & Xe1
27 //Equivalent resistance & leakage reactance referred
   to secondary
28 //Re2 & Xe2
29 //
30 R_dash_2=R2*(v1/v2)^2;
31 R_e1=R1+R_dash_2;
32 X_dash_2=X2*(v1/v2)^2;
33 X_e1=X1+X_dash_2;

```

```

34 // 
35 R_dash_1=R1*(v2/v1)^2;
36 R_e2=R2+R_dash_1;
37 X_dash_1=X1*(v2/v1)^2;
38 X_e2=X2+X_dash_1;
39
40 disp("SOLUTION (a)");
41 disp(sprintf("The primary resistance referred to
secondary %.2f ",R_dash_1));
42 disp(sprintf("The primary leakage reactance referred
to secondary %.2f ",X_dash_1));
43 //
44 disp("SOLUTION (b)");
45 disp(sprintf("The secondary resistance referred to
secondary %.2f ",R_dash_2));
46 disp(sprintf("The secondary leakage reactance
referred to secondary %.2f ",X_dash_2));
47 //
48 disp("SOLUTION (C(i))");
49 disp(sprintf("The equivalent resistance referred to
primary %.2f ",R_e1));
50 disp(sprintf("The equivalent leakage reactance
referred to primary %.2f ",X_e1));
51 //
52 disp("SOLUTION (C(ii))");
53 disp(sprintf("The equivalent resistance referred to
secondaryy %.2f ",R_e2));
54 disp(sprintf("The equivalent leakage reactance
referred to secondary %.2f ",X_e2));
55 //
56 //Ohmic load
57 I1=va/v1;                      // primary full load
      current
58 I2=va/v2;                      // secondary full load
      current
59 oLoss=I2^2*R_e2;                //ohmic loss
60 disp("SOLUTION (d)");
61 disp(sprintf("The ohmic loss at full load %.0f W",

```

```

        oLoss));
62 // 
63 //Voltage to be applied on the HV side
64 //to obtain short circuit currnet of 160 A in L.V
       side winding
65 Z_e1=sqrt(R_e1^2+X_e1^2);           //
       equivalent leakage impedance
66 //voltage to be applied on HV side is equivalent
       leakage reactance x primary current
67 //relationship between current and voltage in
       transformer
68 //I1/I2=V2/V1
69 //Given V2=220 V, V1=2200 V, I2=160 Amp
70 //Therefore , I1=I2 .(V2/V1)
71 I1=160*(v2/v1);
72 V=I1*Z_e1;                         //160*(v2/v1)*Z_e1;
73 //Power Input
74 P=(I1)^2*R_e1                      //P=I ^ 2.R
75 disp("SOLUTION ( e )");
76 disp(sprintf("The voltage to be applied on HV side
       is %.2f V",v));
77 disp(sprintf("The power input is %.1f W",P));
78 disp(" ");
79 //
80 //END

```

---

**Scilab code Exa 7.24** To calculate secondary terminal voltage

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 24
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 24");
7

```

```

8 //10kVA 2500/250 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=10000;
11 v1=2500;                                // primary
   voltage in Volts
12 v2=250;                                 // secondary
   voltage in Volts
13 R1=4.8;                                 // primary HV
   side winding resistance
14 X1=11.2;                               // primary HV
   side winding leakage reactance
15 R2=0.048;                               // secondary LV
   side winding resistance
16 X2=0.112;                               // secondary LV
   side winding leakage reactaance
17
18 //SOLUTION
19 //
20 //Primary resistance and leakage reactance referred
   to secondary
21 //R'1 & X'1
22 //Secondary resistance and leakage reactance
   referred to primary
23 //R'2 & X'2
24 //Equivalent resistance & leakage reactance referred
   to primary
25 //Re1 & Xe1
26 //Equivalent resistance & leakage reactance referred
   to secondary
27 //Re2 & Xe2
28 //
29 R_dash_2=R2*(v1/v2)^2;
30 R_e1=R1+R_dash_2;
31 X_dash_2=X2*(v1/v2)^2;
32 X_e1=X1+X_dash_2;
33 //
34 R_dash_1=R1*(v2/v1)^2;
35 R_e2=R2+R_dash_1;

```

```

36 X_dash_1=X1*(v2/v1)^2;
37 X_e2=X2+X_dash_1;
38 //leakage impedance
39 //The transformer leakage impedance=z0=Re2+j.Xe2
40 //Therefore:
41 z0=R_e2+X_e2*%i;
42 //Further Given
43 //the LV winding side is connected to load impedance
   of 5+j.3.5 Ohm
44 //The power factor 0.8 lagging on LV side
45 //applied load is
46 Zl=5+3.5*%i;
47 //total impedance in series
48 //The leakage impedance and load impedance are in
   series , therefore , total impedance is sum of the
   two
49 //
50 Z=z0+Zl;
51 magZ=sqrt(real(Z)^2+imag(Z)^2);
52 magZl=sqrt(real(Zl)^2+imag(Zl)^2);
53 //V2=I2.Zl
54 I2=v2/magZ;
55 V2=I2*magZl
56 disp("SOLUTION ( a )");
57 disp(sprintf("The secondary terminal voltage is %.0f
   V" ,V2));
58 //
59 //part (b) and (c) of the problem cannot be solved
   mathematically alone.
60 disp(" ");
61 //
62 //END

```

---

**Scilab code Exa 7.25 15 kVA 2200 110 V transformer**

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 25
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 25");
7
8 //15kVA 2200/110 V transformer
9 //VARIABLE INITIALIZATION
10 va=25000;                                //power rating
11 v1=2200;                                   //primary
12 v2=110;                                    //secondary
13 f=50;
14 R1=1.75;
15 X1=2.6;
16 R2=0.0045;
17 X2=0.0075;
18
19 //SOLUTION
20 //
21 //Primary resistance and leakage reactance referred
22 //to secondary
23 //R'1 & X'1
24 //Secondary resistance and leakage reactance
25 //referred to primary
26 //R'2 & X'2
27 //Equivalent resistance & leakage reactance referred
28 //to primary
29 //Re1 & Xe1
30 //Equivalent resistance & leakage reactance referred
31 //to secondary
32 //Re2 & Xe2
33 //
34 R_dash_2=R2*(v1/v2)^2;
35 R_e1=R1+R_dash_2;
36 X_dash_2=X2*(v1/v2)^2;

```

```

33 X_e1=X1+X_dash_2;
34 //
35 R_dash_1=R1*(v2/v1)^2;
36 R_e2=R2+R_dash_1;
37 X_dash_1=X1*(v2/v1)^2;
38 X_e2=X2+X_dash_1;
39 //
40 Z_e1=R_e1+X_e1*%i;
41 Z_e2=R_e2+X_e2*%i;
42 magZ_e1=sqrt(real(Z_e1)^2+imag(Z_e1)^2);
43 magZ_e2=sqrt(real(Z_e2)^2+imag(Z_e2)^2);
44 //
45 //
46 disp("SOLUTION (a)");
47 disp(sprintf("The equivalent resistance referred to
primary %.2f ",R_e1));
48 disp("SOLUTION (b)");
49 disp(sprintf("The equivalent resistance referred to
secondary %.5f ",R_e2));
50 disp("SOLUTION (c)");
51 disp(sprintf("The equivalent leakage reactance
referred to primary %.1f ",X_e1));
52 disp("SOLUTION (d)");
53 disp(sprintf("The equivalent leakage reactance
referred to secondary %.3f ",X_e2));
54 disp("SOLUTION (e)");
55 disp(sprintf("The equivalent impedance referred to
primary %.5f ",magZ_e1));
56 disp("SOLUTION (f)");
57 disp(sprintf("The equivalent impedance referred to
secondary %.5f ",magZ_e2));
58 //
59 //primary and secondary full load current and
//voltage relationship with power rating
60 I1=va/v1; //primary current
61 I2=va/v2; //secondary current
62 cuLoss=I2^2*R_e2; //copper loss or also as I1
^2.R1 + I2^2.R2

```

```

63 disp("SOLUTION (d)");
64 disp(sprintf("The copper loss at full load %f W",
65 cuLoss));
66 //
67 //END

```

---

### Scilab code Exa 7.26 Open circuit and short circuit test

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 26
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 26");
7
8 //open circuit & short circuit test
9 //10 kVA 500/250 V 50 Hz single phase
10 //VARIABLE INITIALIZATION
11 va=10000;                                //apparent power
12 v1=500;                                    //primary
13 voltage in Volts
14 v2=250;                                    //secondary
15 voltage in Volts
16 f=50;                                       // frequency
17
18 //open circuit parameters
19 Voc=500;
20 Io=2;                                         // watts HT side
21 Wi=100;                                      // just to keep
22 Woc=Wi;
23 symbology
24
25 //short circuit test
26 Vsc=25;
27 Isc=20;
28 Wc=90;                                       // watts HT side

```

```

24 //
25 pf=0.8;
26 //SOLUTION
27 //open circuit
28 phi0=acos(Woc/(v1*Io));
29 Ic=Io*cos(phi0);
30 Iphi=Io*sin(phi0);
31 Rc=v1/Ic;
32 X=v1/Iphi;
33 disp("SOLUTION (a)");
34 disp(sprintf("The value of Ic is %.2f Amp",Ic));
35 disp(sprintf("The value of Iphi is %.2f Amp",Iphi));
36 disp(sprintf("The value of Rc is %.2f Ohm",Rc));
37 disp(sprintf("The value of X is %.2f ",X));
38 //
39 //short circuit
40 phisc=acos(Wc/(Vsc*Isc));
41 pf1=cos(phisc);
42 R_e1=Vsc*pf1/Isc;
43 Z_e1=Vsc/Isc;
44 X_e1=sqrt(Z_e1^2-R_e1^2);
45 disp(sprintf("The value of Power factor is %f",pf1))
;
46 disp(sprintf("The value of Rel is %f Ohm",R_e1));
47 disp(sprintf("The value of Ze1 is %f Ohm",Z_e1));
48 disp(sprintf("The value of Xe1 is %f ",X_e1));
49 //
50 I1=va/v1;
51 phi=acos(pf);
52 //R=er.cos phi2+vx.sin phi2
53 //E2=V2+I2.R
54 %reg=(Isc*R_e1*pf+Isc*X_e1*sin(phi))*100/v1;
55 disp("SOLUTION (c(i))");
56 disp(sprintf("The percent regulation at full load is
%.2f",%reg));
57 //
58 //full load output at pf=0.8
59 Pout=va*pf; // Output Power

```

```

60 ironLoss=Wi;
61 cuLoss=Wc;
62 loss=ironLoss+cuLoss;
63 Pin=Pout+loss;           // Input Power
64 eff=Pout*100/Pin;       // efficiency
65 disp("SOLUTION (c(i))");
66 disp(sprintf("The percent efficiency at full load is
    %.2f",eff));
67 disp("");
68 //
69 //END

```

---

### Scilab code Exa 7.27 Open and short circuit test

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 27
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 27");
7
8 //200kVA 1100/400 V delta star distribution
   transformer
9 //three phase
10 //VARIABLE INITIALIZATION
11 va=200000;           // apparent
   power
12 v1=11000;             // primary
   voltage in Volts
13 v2=400;               // secondary
   voltage in Volts
14 f=50;                 // frequency
15 //open circuit test parameters
16 V3=400;
17 I3=9;

```

```

18 W3=1500;                                //load in watts
    HT side
19 //short circuit test parameters
20 Vsc=350;
21 Isc=20;
22 Wc=2100;                                //load in watts
    HT side
23 //
24 pf=0.8;
25 //SOLUTION
26 Voc=V3/sqrt(3);                         //per phase
    applied voltage in open circuit
27 Io=9;                                    //per phase
    exciting current.= I3
28 Wi=W3/3;                                 // per phase
    core loss in watts HT side
29 Pc=Wi;                                   //core losses
30 //power factor Pc=V1.Io.cos phi0 //v1=Voc
31 //open circuit test performed on LV side
32 phi0=acos(Wi/(Voc*Io));                 //core loss
33 Ic=Io*cos(phi0);                        current
34 Iphi=Io*sin(phi0);                      //magnetising
    current
35 Rc=Voc/Ic;                             //Core loss
    resistance
36 X=Voc/Iphi;                            //
37 disp("SOLUTION (a)");                  // 
38 disp(sprintf("The value of Ic is %.0f Amp",Ic));
39 disp(sprintf("The value of I is %.2f Amp",Iphi));
40 disp(sprintf("The value of Rc is %.2f Ohm",Rc));
41 disp(sprintf("The value of X is %.2f ",X));
42 //
43 //core loss resistance referred to hv side
44 Rch=Rc*(v1/Voc)^2;
45 XphiH=X*(v1/Voc)^2;
46 disp(sprintf("The value of Rch is %.2f k ",Rch
    /1000));

```

```

47 disp(sprintf("The value of X_h is %.2f K ",XphiH
    /1000));
48 //short circuit
49 //This test performed on HV side
50 //first find rated current
51 Isc=va/(3*v1);
52 Psc=Wc/3;                                //ohmic loss per
    phase
53 phisc=acos(Wc/(Vsc*Isc));
54 pf1=cos(phisc);
55 R_e1=Psc/Isc^2;
56 Z_e1=Vsc/Isc;
57 X_e1=sqrt(Z_e1^2-R_e1^2);
58 disp(sprintf("The value of ohmic loss per phase is %
    .0f W",Psc));
59 disp(sprintf("The value of Re1 is %.2f Ohm",R_e1));
60 disp(sprintf("The value of Ze1 is %.2f Ohm",Z_e1));
61 disp(sprintf("The value of Xe1 is %.2 f ",X_e1));
62 //
63 //efficiency at half load
64 pf=1;                                     //unity
    power factor
65 Pout=(va/3)*(1/2)*pf;
66 //core losses=Pc
67 //cuLosses ohmic loss =Psc
68 Pin=Pout+Pc+(1/2)^2*Psc;
69 eff=Pout*100/Pin;
70 disp(sprintf("The efficiency at half load is %.2f" ,
    eff));
71
72 disp("");
73 //
74 //END

```

---

**Scilab code Exa 7.28** Open and short circuit test

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 28
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 28");
7
8 //10 kVA 2500/250 V single phase transformer
9 //open circuit and short circuit tests
10 //VARIABLE INITIALIZATION
11 va=10000;                                // apparent
12 v1=2500;                                  // primary
13 v2=250;                                   // secondary
14 f=50;
15 //open circuit parameters
16 Voc=250;
17 Io=0.8;
18 Wi=50;                                    // watts HT
19 side
20 //short circuit test
21 Vsc=60;
22 Isc=3;
23 Wc=45;                                    // watts HT side
24 //
25 //loads
26 pf=0.8;
27 //SOLUTION
28 //Open circuit test conducted on lv because 250 V
29 //during this test is equal to rated voltage on lv
30 //side.
31 I1=va/v1;                                // full rated
32 current on hv side
33 Psc0=Wc*(I1/Isc)^2;                      //ohmic loss/
34 cu loss at full load rated current
35 Pc=Wi;                                    // core losses

```

```

31 // 1/4 load
32 Psc=(1/4)^2*Psc0;
33 Pout=va*pf*(1/4);
34 Pin=Pout+Pc+Psc;
35 eff=Pout*100/Pin;
36 disp("SOLUTION (a)");
37 disp(sprintf("The efficiency at 1/4 load is %.2f",
    eff));
38 //
39 // 1/2 load
40 Psc=(1/2)^2*Psc0;
41 Pout=va*pf*(1/2);
42 Pin=Pout+Pc+Psc;
43 eff=Pout*100/Pin;
44 disp(sprintf("The efficiency at 1/2 load is %.2f",
    eff));
45 //
46 // full load
47 Psc=(1/1)^2*Psc0;
48 Pout=va*pf*(1/1);
49 Pin=Pout+Pc+Psc;
50 eff=Pout*100/Pin;
51 disp(sprintf("The efficiency at full load is %.2f",
    eff));
52 //
53 // 1 1/4 = 5/4 load
54 Psc=(5/4)^2*Psc0;
55 Pout=va*pf*(5/4);
56 Pin=Pout+Pc+Psc;
57 eff=Pout*100/Pin;
58 disp(sprintf("The efficiency at 1 1/4 or 5/4 load is
    %.2f",eff));
59 //
60 //maximum efficiency at x, but then ohmic loss=core
   loss
61 x=sqrt(Pc/Psc0);
62 Pout=va*x*pf;
63 Pin=Pout+Pc+Pc; //Ohmic

```

```

    losses = core losses at max efficiency
64 eff=Pout*100/Pin;
65 disp("SOLUTION (b)");
66 disp(sprintf("The maximum efficiency is %.2f",eff))
;
67 //
68 //short circuit test performed on lv side
69 phisc=acos(Wc/(Vsc*Isc));
70 pf1=cos(phisc);
71 R_e1=Vsc*pf1/Isc;
72 Z_e1=Vsc/Isc;
73 X_e1=sqrt(Z_e1^2-R_e1^2);
74 disp("SOLUTION (c)");
75 disp(sprintf("The value of Re1 is %.2f Ohm",R_e1));
76 disp(sprintf("The value of Ze1 is %.2f Ohm",Z_e1));
77 disp(sprintf("The value of Xe1 is %.2f ",X_e1));
78 //
79 //ee, ex;
80 er=I1*R_e1/v1;
81 ex=I1*X_e1/v1;
82 disp(sprintf("The value of Er is %.3f pu",er));
83 disp(sprintf("The value of Ex is %.3f",ex));
84 //
85 phi=acos(pf);
86 //R=ercosphi2+vx.sinphi2
87 //E2=V2+I2.R
88 %reg=(I1*R_e1*pf+I1*X_e1*sin(phi))*100/v1; //same as
     using er and ex
89 disp(sprintf("The percent regulation at full load
      lagging is %.2f",%reg));
90 %reg1=(I1*R_e1*pf-I1*X_e1*sin(phi))*100/v1; //same
     as using er and ex
91 disp(sprintf("The percent regulation at full load
      leading is %.2f",%reg1));
92 V21=(1-%reg/100)*v2;
93 V22=(1-%reg1/100)*v2;
94 disp(sprintf("The secondary terminal voltage at full
      load lagging is %.2f",V21));

```

```

95 disp(sprintf("The secondary terminal voltage at full
    load leading is %.2f",V22));
96 disp("");
97 //
98 //END

```

---

### Scilab code Exa 7.29 200 kVA 4000 1000 V transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 29
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 29");
7
8 //20kVA 4000/1000 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=200000;                                // apparent
    power
11 v1=4000;                                    // primary
    voltage in Volts
12 v2=1000;                                    // secondary
    voltage in Volts
13 f=50;                                       // frequency
    in Hz
14 //loads
15 pf=1;                                       // power
    factor is unity
16 eff=0.97;                                   // at full
    load and at 60% of full load
17 nlpf=0.5;                                   //no load pf
18 lpf=0.8;                                    //lagging pf
19 reg=0.05;                                   //
    %regulation at 0.8 pf
20 //

```

```

21 //SOLUTION
22 loss=(1-eff)*va/eff;                                //=Pc+Pcu
23 losses
24 //simultaneous equation to be solved
25 //eq 1: Pc+Pcu=loss;
26 //fractipon of copper/ ohmic losses
27 f=(0.6)^2;                                         // 60% of
28 full load
29 //the 2nd equation is Pc+f*Pcu=loss
30 //now the matrix
31 M=[1,1,1,f];
32 A=[loss,loss*0.6];
33 Mi=inv(M);
34 Ans=A*inv(M);
35 Pc=Ans(1,1);
36 Pcu=Ans(1,2);
37 //disp(sprintf("The Pc is %f",Pc));
38 //disp(sprintf("The Pcu is %f",Pcu));
39 //LV side
40 R_e2=Pcu/va;
41 //from %reg find X_e2
42 phi=acos(lpf);
43 X_e2=(reg-R_e2*cos(phi))/sin(phi);
44 //in oms units
45 R_e2=R_e2*v2^2/va;                                // in ohms
46 X_e2=X_e2*v2^2/va;                                // in ohms
47 disp(sprintf("The Re2 is %.3f      ",R_e2));
48 disp(sprintf("The Xe2 is %.3f      ",X_e2));
49 //
50 Rc=v2^2/Pc;
51 Ie2=Pc/(v2*0.25);
52 Ic=Pc/v2;
53 Iphi=sqrt(Ie2^2-Ic^2);
54 Xphi=v2/Iphi;
55 disp(sprintf("The Rc is %.2f      ",Rc));
56 disp(sprintf("The Ie2 is %.3f A",Ie2));
57 disp(sprintf("The Ic is %.3f A",Ic));
58 disp(sprintf("The Iphi is %.4f A",Iphi));

```

```

57 disp(sprintf("The Xphi is %.2f ",Xphi));
58 disp("");
59 //
60 //END

```

---

**Scilab code Exa 7.30** Secondary terminal voltage at full load

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 30
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 30");
7
8 //6600/440 V single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=6600;                                //primary
     voltage in Volts
11 v2=440;                                  //secondary
     voltage in Volts
12 e_r=0.02;                                 //equivalent
     resistance
13 e_x=0.05;                                 //equivalent
     reactance
14 pf=0.8;                                   //power
     factor
15 //
16 //SOLUTION
17 //worked out differently a bit from the text book in
     terms of the steps
18 phi=acos(pf);                            //phase
     angle
19 reg=e_r*cos(phi)+e_x*sin(phi);           //voltage
     regulation
20 V2=v2*(1-reg);                          //secondary

```

```

        terminal voltage
21 disp(sprintf("The secondary terminal voltage is %.2f
    V",V2));
22 disp("");
23 //
24 //END

```

---

**Scilab code Exa 7.31** To calculate the value of maximum flux density in the core and the emf

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 31
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 31");
7
8 //single phase transformer having 400 primary and
9 // 1000 secondary turns
10 //VARIABLE INITIALIZATION
11 N1=400;
12 N2=1000;
13 coreA=60;                                //net core
14 v1=500;                                    //primary
15 //                                            voltage in Volts
16 f=50;                                       //frequency
17 //
18 //SOLUTION
19 //v1=E1=4.44. m .N1. f  Volts
20 phiM=v1/(4.44*N1*f);
21 //flux density Bm= m / area
22 Bm=phiM/coreA;                            //lines per
23 cm

```

```

22 // voltage per turn
23 vpt=v1/N1;
24 v2=N2*vpt;
25 //
26 disp(sprintf("The maximum flux density is %.3fx10^-5
    Wb per cm^2",Bm*10^5)); //text book answer is 9383
    lines per cm^2
27 disp(sprintf("The secondary voltage is %.0f V",v2));
28 disp("");
29 //
30 //END

```

---

**Scilab code Exa 7.32** To calculate total copper loss

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 32
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 32");
7
8 //50 kVA 4400/220 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=50000;
11 v1=4400;                                //primary
    voltage in Volts
12 v2=220;                                  //secondary
    voltage in Volts
13 f=50;
14 R1=3.45;
15 X1=5.2;
16 R2=0.0009;
17 X2=0.015;
18
19 //SOLUTION

```

```

20 //
21 //Primary resistance and leakage reactance referred
22 //to secondary
23 //Secondary resistance and leakage reactance
24 //referred to primary
25 //Equivalent resistance & leakage reactance referred
26 //to primary
27 //Re1 & Xe1
28 //Equivalent resistance & leakage reactance referred
29 //to secondary
30 //Re2 & Xe2
31 //
32 R_dash_2=R2*(v1/v2)^2;
33 R_e1=R1+R_dash_2;
34 X_dash_2=X2*(v1/v2)^2;
35 X_e1=X1+X_dash_2;
36 //
37 R_dash_1=R1*(v2/v1)^2;
38 R_e2=R2+R_dash_1;
39 X_dash_1=X1*(v2/v1)^2;
40 X_e2=X2+X_dash_1;
41 //
42 Z_e1=R_e1+X_e1*%i;
43 Z_e2=R_e2+X_e2*%i;
44 magZ_e1=sqrt(real(Z_e1)^2+imag(Z_e1)^2);
45 magZ_e2=sqrt(real(Z_e2)^2+imag(Z_e2)^2);
46 //
47 disp("SOLUTION ( i )");
48 disp(sprintf("The equivalent resistance referred to
49 primary %.4f ",R_e1)); //text book answer is
50 7.05 ohm
51 disp("SOLUTION ( ii )");
52 disp(sprintf("The equivalent resistance referred to
53 secondary %.4f ",R_e2));
54 disp("SOLUTION ( iii )");
55 disp(sprintf("The equivalent leakage reactance

```

```

        referred to primary %.4f    ",X_e1));
51 disp(sprintf("The equivalent leakage reactance
        referred to secondary %.4f    ",X_e2));
52 disp("SOLUTION (iv)");
53 disp(sprintf("The equivalent impedance referred to
        primary %.4f    ",magZ_e1)); // text book answer
        is 13.23 ohm
54 disp(sprintf("The equivalent impedance referred to
        secondary %.4f    ",magZ_e2)); //text book answer
        is 0.0331 ohm
55 //
56 I1=va/v1;
57 I2=va/v2;
58 Pcu=I2^2*R_e2;
59 disp("SOLUTION (d)");
60 disp(sprintf("The copper loss at full load %.0f W",
        Pcu));
61 disp(" ");
62 //The answers in the book on page 7.77 are wrong for
        all but Xe1 and Xe2 values.
63 //END

```

---

**Scilab code Exa 7.33** No load and short circuit results of transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 33
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 33");
7
8 // 5kVA 400/200 V 50 Hz single phase transformer
9 //open circuit and short circuit tests
10 //VARIABLE INITIALIZATION
11 va=5000;                                // apparent

```

```

    power
12 v1=400;                                //primary
      voltage in Volts
13 v2=200;                                //secondary
      voltage in Volts
14 f=50;
15 //no load parameters
16 Voc=400;
17 Io=1;
18 Woc=50;                                 // watts HT side
19 //short circuit test
20 Vsc=12;
21 Isc=10;
22 Wc=40;                                 // watts HT side
23 //
24 pf=0.8;
25 //SOLUTION
26 //no load condition
27 phi0=acos(Woc/(v1*Io));
28 Ic=Io*cos(phi0);
29 Iphi=Io*sin(phi0);
30 Rc=v1/Ic;
31 X=v1/Iphi;
32 disp("SOLUTION ( i )");
33 disp(sprintf("The value of Ic is %f Amp",Ic));
34 disp(sprintf("The value of I   is %f Amp",Iphi));
35 //disp(sprintf("The value of Rc is %f Ohm",Rc));
36 //disp(sprintf("The value of X is %f ",X));
37 //
38 //short circuit
39 phisc=acos(Wc/(Vsc*Isc));
40 pf1=cos(phisc);
41 R_e1=Vsc*pf1/Isc;
42 Z_e1=Vsc/Isc;
43 X_e1=sqrt(Z_e1^2-R_e1^2);
44 disp(sprintf("The value of Re1 is %.2 f Ohm",R_e1));
45 disp(sprintf("The value of Ze1 is %.2 f Ohm",Z_e1));
46 disp(sprintf("The value of Xe1 is %.2 f   ",X_e1));

```

```

47 //
48 I1=va/v1;
49 phi=acos(pf);
50 //R=ercosphi2+vx.sinphi2
51 //E2=V2+I2.R
52 %reg=(I1*R_e1*pf+I1*X_e1*sin(phi))*100/v1;
53 disp("SOLUTION (c(i))");
54 disp(sprintf("The percent regulation at full load is
55 %.3f",%reg));
55 //
56 //full load output at pf=0.8
57 Pout=va*pf; //output power
58 ironLoss=Woc;
59 cuLoss=Wc;
60 loss=ironLoss+cuLoss;
61 Pin=Pout+loss; // input power
62 eff=Pout*100/Pin;
63 disp("SOLUTION (c(ii))");
64 disp(sprintf("The percent efficiency at full load is
65 %.2f",eff)); // not calculated in the text book
65 disp("");
66 //
67 //END

```

---

**Scilab code Exa 7.34** 50 kVA transformer of 5 is to 1 ratio of turns

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 35
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 35");
7
8 //single phase 50 hz, 200kVA, 11kVA/230 V
9 //open circuit and short circuit tests

```

```

10 //VARIABLE INITIALIZATION
11 va=200000;                                // apparent
12 power
13 v1=11000;                                 // primary
14 voltage in Volts
15 v2=230;                                    // secondary
16 voltage in Volts
17 Woc=1600;                                  // watts also
18 equals core losses
19 Wc=2600;                                   // watts , also
20 equals cu losses
21 f=50;                                       // hours
22 //no load parameters
23 //day cycle given
24 h1=8;                                       // load in
25 load1=160000;                             // watts
26 pf1=0.8;                                  // power
27 factor
28 h2=6;
29 load2=100000;
30 pf2=1;
31 h3=10;
32 load3=0;
33 pf3=0;
34 //SOLUTION
35 //24 hr energy output
36 Pout=load1*h1*pf1+load2*h2*pf2+load3*h3*pf3;
37 Pc24=Woc*24;                               // 24 hours
38 Pc loss
39 //cu loss= hours.(kva output/kva rated)^2.Full load
40 Cu loss
41 Pcu24=h1*(load1/va)^2*Wc+h2*(load2/va)^2*Wc+h3*(
42 load3/va)^2*Wc;
43 Pin=Pout+Pc24+Pcu24;
44 eff=Pout*100/Pin;
45 //disp(sprintf("The value Pout is %f",Pout));
46 //disp(sprintf("The value Pc is %f",Pc24));

```

```
38 //disp(sprintf(" The value Pcu is %f",Pcu24));
39 disp(sprintf("The percent efficiency at full load is
               %.2f",eff));
40 disp("");
41 //
42 //END
```

### Scilab code Exa 7.35 No load and short circuit results of transformer

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 36
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 36");
7
8 // 100kVA 50 Hz 440/11000 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=100000; // apparent power
11 v1=440; //primary voltage in Volts
12 v2=11000; //secondary voltage in Volts
13 f=50; // efficiency
14 //loads
15 pf=1; //power factor at half load current
16 eff1=0.985; // at full load at 0.8 pf
17 eff2=0.99; //at half full load at unity pf
18 pf1=0.8; // power factor at full load current

```

```

19 pf2=1; //  

20 //  

21 //SOLUTION  

22 loss1=(1-eff1)*va*pf1/eff1; //=Pc  

+Pcu losses  

23 loss2=(1-eff2)*va*(1/2)*pf2/eff2; //=Pc+Pcu losses  

24 //simultaneous equation to be solved  

25 //eq 1: Pc+Pcu=loss;  

26 //fractipon of copper/ ohmic losses  

27 f=(1/2)^2; // 60% of  

full load  

28 //the 2nd equation is Pc+f*Pcu=loss  

29 //now the matrix  

30 M=[1,1;1,f]; //Pc+Pcu=  

loss1; Pc+(1/2)^2*Pcu=loss2: 1,1,; 1,f  

31 A=[loss1,loss2];  

32 Mi=inv(M);  

33 Ans=A*inv(M);  

34 Pc=Ans(1,1);  

35 Pcu=Ans(1,2);  

36 disp(sprintf("The Pc is %.1f W",Pc));  

37 disp(sprintf("The Pcu is %.1f W",Pcu));  

38 //  

39 //maximumefficiency at farction x times the full  

load; and then f.Pcu=Pc  

40 x=sqrt(Pc/Pcu);  

41 disp(sprintf("The maximum efficiency would occur at  

a load of %.0f kVA",x*va/1000));  

42 I1=va/v1;  

43 I1maxEff=I1*x;  

44 disp(sprintf("The current at maximum efficeincy is %  

.0f A",I1maxEff));  

45 disp("");  

46 //  

47 //END

```

---

**Scilab code Exa 7.36** Value of load for maximum efficiency

```
1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 36
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 36");
7
8 //100kVA 50 Hz 440/1100 V single phase transformer
9 //VARIABLE INITIALIZATION
10 va=100000;                                // apparent
11 v1=440;                                     // primary
12 voltage in Volts
12 v2=11000;                                   // secondary
12 voltage in Volts
13 f=50;                                       // frequency
14 //loads
15 pf=1;                                        // power
15 factor unity
16 eff1=0.985;                                 // at full
16 load at 0.8 pf
17 eff2=0.99;                                  // at half
17 full load at unity pf
18 pf1=0.8;                                    // power
18 factor
19 pf2=1;                                       // power
19 factor
20 //
21 //SOLUTION
22 loss1=(1-eff1)*va*pf1/eff1;                //=Pc
22 +Pcu losses
23 loss2=(1-eff2)*va*(1/2)*pf2/eff2;
```

```

                                //=Pc+Pcu losses
24 //simultaneous equation to be solved
25 //eq 1: Pc+Pcu=loss ;
26 //fractipon of copper/ ohmic losses
27 f=(1/2)^2;                                     // 60% of
      full load
28 //the 2nd equation is Pc+f*Pcu=loss
29 //now the matrix
30 M=[1 ,1;1 ,f];                               //Pc+Pcu=
      loss1;  Pc+(1/2)^2*Pcu=loss2 : 1 ,1 ,; 1 ,f
31 A=[loss1,loss2];
32 Mi=inv(M);
33 Ans=A*inv(M);
34 Pc=Ans(1,1);
35 Pcu=Ans(1,2);
36 disp(sprintf("The Pc is %.1f W",Pc));
37 disp(sprintf("The Pcu is %.1f W",Pcu));
38 //
39 //maximumefficiency at farction x times the full
      load; and then f.Pcu=Pc
40 x=sqrt(Pc/Pcu);
41 disp(sprintf("The maximum efficiency would occur at
      a load of %.0f kVA",x*va/1000));
42 I1=va/v1;
43 I1maxEff=I1*x;
44 disp(sprintf("The current at maximum efficeincy is %
      .0f A",I1maxEff));
45 disp("");
46 //
47 //END

```

---

**Scilab code Exa 7.37** To calculate regulation at full load

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 37

```

```

3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 37");
7
8 //500 kVA 3300/500 V 50 hz single phase transformer
9 //VARIABLE INITIALIZATION
10 va=500000; // apparent power
11 v1=3300; // primary voltage in Volts
12 v2=500; // secondary voltage in Volts
13 f=50;
14 //loads
15 pf=1; //power factor unity
16 eff=0.97; // at 3/4 full load at unity pf
17 pf2=0.8; //power factor
18 //
19 //SOLUTION
20 I1=va/v1;
21 loss=(1-eff)*va*(3/4)*pf/eff; //=Pc+Pcu
    losses at 3/4 load
22 //since the eff value is maximum, Pcu=Pc; therefore ,
    2*Pc=loss
23 Pc=loss/2;
24 //(3/4)^2*Pcu=Pc;
25 f=(3/4)^2; //3/4 load
26 //Pcu=Pc/f
27 Pcu=Pc/f;
28 //disp(sprintf("The Pc is %f W",Pc));
29 //disp(sprintf("The Pcu is %f W",Pcu));
30 //
31 R_e1=Pcu/I1^2;

```

```

32 disp(sprintf("The value of Re1 is %.3f W",R_e1));
33 //10% impedance
34 Z_e1=v1*0.1/I1;
35 X_e1=sqrt(Z_e1^2-R_e1^2);
36 phi=acos(0.8);
37 %reg=(I1*R_e1*cos(phi)+I1*X_e1*sin(phi))*100/v1;
38 disp(sprintf("The percent regulation at full load
0.8 pf is %.2f W",%reg));
39 disp("");
40 //
41 //END

```

---

### Scilab code Exa 7.38 Total no load loss

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 38
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 38");
7
8 //220/115 V 25 Hz single phase transformer
9 //VARIABLE INITIALIZATION
10 v1=220; // primary
    voltage in Volts
11 v2=115; // secondary voltage in Volts
12 f1=25; // frequency rating of the transformer in Hz
13 f2=50; // frequency of the connected load
14 //loads
15 V=440 // i
    Volts
16 We1=100; // in

```

```

Watts at 220 V, eddy losses
17 Pc1=2*We1; //  

    Total iron losses which equals We+Wh due to eddy  

    and hysteresis
18 Wh1=Pc1-We1;
19 //
20 //SOLUTION
21 //since we know that We=kh.f.B1.6 and Wh=Ke.Kf2.f  

    ^2.B2
22 //since all being constant except frequency , we may  

    take We2/We1=f22/f12
23 //and Wh2/Wh1=f2/f1
24 //flux density in both cases is same as in second  

    case voltage and frequency both are doubled
25 //find values for We2 and Wh2, whence Pc2=We2+Wh2
26 We2=f22*We1/f12;
27 Wh2=f2*Wh1/f1;
28 Pc2=We2+Wh2;
29 disp(sprintf("The total no load losses at 400 V is %  

    .0 f W",Pc2));
30 disp("");
31 //
32 //END

```

---

### Scilab code Exa 7.39 Percentage of hysteresis and copperloss

```

1 //CHAPTER 7- SINGLE PHASE TRANSFORMER
2 //Example 39
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 39");
7
8 //220/440 v 50 Hz transformer
9 //VARIABLE INITIALIZATION

```

```

10 v1=220;
    //primary voltage in Volts
11 v2=440;
    //secondary voltage in Volts
12 f1=50;
    //rated frequency in Hz
13
14 //loads
15 V=110;
16 f2=25;
    //frequency of the applied load
17 //say, else computation may not be possible using
    computer
18 Pout1=100;
    //in
    watt, just assumed for computational purposes
    for the 220V supply
19 We1=0.01*Pout1;
    //in
    Watts at 220 V, eddy losses which are 1% of the
    output at 220V
20 Wh1=0.01*Pout1;
    //in
    Watts at 220 V, hysteresis losses which are 1% of
    the output at 220V
21 //Pc1=We1+Wh1;
    // Total
    iron losses which equals We+Wh due to eddy and
    hysteresis
22 Pcu1=0.01*Pout1;
    //copper
    losses
23 //
24 //SOLUTION
25 //since on connecting to half the power ie 110V, the
    output would get halved
26 Pout2=Pout1/2;
27 xPcu=xPcu1/Pout2;

```

```

28 disp(sprintf("The copper losses at 110 V would be %  

    .0 f percent of the output",xPcu*100));  

29 //now coming to frequency dependant losses ie eddy  

    and hysteresis  

30 //since we know that We=kh.f.B^1.6 and Wh=Ke.Kf^2.f  

    ^2.B^2  

31 //since all being constant except frequency , we may  

    take We2/We1=f2^2/f1^2  

32 //and Wh2/Wh1=f2/f1  

33 //find values for We2 and Wh2, whence Pc2=We2+Wh2  

34 We2=f2^2*We1/f1^2;  

35 Wh2=f2*Wh1/f1;  

36 xWe=We2/Pout2;  

37 xWh=Wh2/Pout2;  

38 disp(sprintf("The eddy losses at 110 V would be %.2f  

    percent of the output",xWe*100));  

39 disp(sprintf("The hysteresis losses at 110 V would  

    be %.2f percent of the output",xWh*100));  

40 disp(" " );  

41 //  

42 //END

```

---

**Scilab code Exa 7.40** To draw the phasor diagram

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER  

2 //Example 40  

3  

4 clc;  

5 disp("CHAPTER 7");  

6 disp("EXAMPLE 40");  

7  

8 //Given  

9 //transformer on no load has a core loss 50W, draws  

    a current of 2 A (RMS) and induced emf 220 V(RMS)  

10 //VARIABLE INITIALIZATION

```

```

11 loss=50; //core loss in Watts
12 I0=2; //no load current in
          Amperes
13 v0=220; //induced emf in
          Volts
14
15 //SOLUTION
16 pf=loss/(v0*I0); //core loss component
17 I_c=I0*pf; //magnetizing
18 I_phi=I0*sin(acos(pf)); //magnetizing
          component
19 disp(sprintf("The magnetizing component , I_c= %.4f A
           ,",I_phi));
20 disp(sprintf("The core loss component , I_c = %.4f A,
           ",I_c));
21
22 //END

```

---

### Scilab code Exa 7.41 Star connected auto transformer

```

1 //CHAPTER 7– SINGLE PHASE TRANSFORMER
2 //Example 41
3
4 clc;
5 disp("CHAPTER 7");
6 disp("EXAMPLE 41");
7
8 //3-phase 550/440 V star connected transformer
     supplies a load of 400kW
9 //VARIABLE INITIALIZATION
10 v1=550; //primary voltage in
          Volts
11 v2=440; //secondary voltage
          in Volts
12 p=400*1000; //load in Watts

```

```

13 pf=0.8; //power factor (lagging)
14
15 //SOLUTION
16
17 //solution (a)
18 I2=p/(sqrt(3)*v2*pf); //current on secondary side
19 I1=I2*(v2/v1); //since I1:I2=N2:N1
20 I=I2-I1; //in sections Oa, Ob and Oc
21 disp(sprintf("(a) The current flowing in sections Oa, Ob and Oc is %.0f A",I));
22 disp(sprintf("The current flowing in sections aA, bB and cC is %.0f A",I1));
23
24 //solution (b)
25 //power transferred by transformer action = Pin.(1-k)
26 p_o=p*(1-(v2/v1)); //k=v2/v1
27 disp(sprintf("(b) The power transferred by transformer action %.0f kW",p_o/1000));
28
29 //solution (c)
30 p_d=p-p_o;
31 disp(sprintf("(c) The power conducted directly %d kW",p_d/1000));
32
33 //END

```

---

# Chapter 8

## Direct Current Machines

Scilab code Exa 8.1 Generated emf

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 1
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;           //terminal voltage in Volts
10 I_l=500;          //load current in Amperes
11 r_a=0.04;         //armature resistance in Ohms
12 r_f=50;          //shunt field resistance in Ohms
13
14 //SOLUTION
15 I_f=v_t/r_f;
16 I_a=I_l+I_f;
17 E_a=v_t+(I_a*r_a); //E_a=emf of generator
18 disp(sprintf("The generated emf is %f V",E_a));
19
20 //END
```

---

### Scilab code Exa 8.2 Ratio of speed

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 2
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALZATION
9 v_t=230;           //terminal voltage in Volts
10 r_a=0.5;          //armature resistance in Ohms
11 r_f=115;          //shunt field resistance in Ohms
12 I_l=40;           //line current in Amperes
13
14 //SOLUTION
15
16 //for generator
17 I_f=v_t/r_f;
18 I_a=I_l+I_f;
19 E_a=v_t+(I_a*r_a); //here E_a=emf of generator
20
21 //for motor
22 I_f=v_t/r_f;
23 I_a=I_l-I_f;
24 E_b=v_t-(I_a*r_a); //here E_b=emf of motor
25
26 ratio=E_a/E_b;     //E_a:E_b=(k_a*flux*N_g):(k_a*
27   flux*N_m) =>E_a:E_b=N_g:N_m (as flux is constant)
28 disp(sprintf("The ratio of speed as a generator to
29   the speed as a motor i.e. N_g:N_m is %f",ratio));
30
31 //END
```

---

**Scilab code Exa 8.3** Armature induced emf and developed torque and efficiency

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 3
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 p_o=10*1000;                                // output of generator in
                                                Watts
10 v_t=250;                                     // terminal voltage in
                                                Volts
11 N=1000;                                      // speed in rpm
12 r_a=0.15;                                     // armature resistance in
                                                Ohms
13 I_f=1.64;                                     // field current in
                                                Amperes
14 rot_loss=540;                                  // rotational loss in
                                                Watts
15
16 //SOLUTION
17
18 //solution (i)
19 I_l=p_o/v_t;
20 I_a=I_l+I_f;
21 E_a=v_t+(I_a*r_a);
22 disp(sprintf("(i) The armature induced emf is %f V", E_a));
23
24 //solution (ii)
25 w=(2*pi*N)/60;                               // in radian/sec
```

```

26 T_e=(E_a*I_a)/w;
27 disp(sprintf("( ii) The torque developed is %f N-m" ,
T_e));
28
29 //solution ( iii)
30 arm_loss=(I_a^2)*r_a;           //armature loss
31 fld_loss=v_t*I_f;             //field loss
32 tot_loss=rot_loss+arm_loss+fld_loss;
33 p_i=p_o+tot_loss;
34 eff=(p_o/p_i)*100;
35 disp(sprintf("( iii) The efficiency is %f %%" ,eff));
36
37 //END

```

---

**Scilab code Exa 8.4** Armature resistance and load current at maximum efficiency

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 4
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 v_t=240;                      //in Volts
10 I_l=200;                      //full load current in
                                Ampères
11 r_f=60;                       //shunt field resisatnce
                                in Ohms
12 eff=90;                        //percentage full load
                                efficiency
13 s_loss=800;                   //stray(iron + friction)
                                loss in Watts
14

```

```

15 //SOLUTION
16
17 //solution (a)
18 p_o=v_t*I_l;           //output
19 eff=eff/100;
20 p_i=p_o/eff;
21 tot_loss=p_i-p_o;      //since input=output+loss
22 I_f=v_t/r_f;
23 I_a=I_l+I_f;
24 cu_loss=(I_f^2)*r_f;   //copper loss
25 c_loss=cu_loss+s_loss; //constant loss
26 arm_loss=tot_loss-c_loss; //armature loss ((I_a^2)*
    r_a)
27 r_a=arm_loss/(I_a^2);
28 disp(sprintf("(a) The armature resistance is %f ", r_a));
29
30 //solution (b)
31 //for maximum efficiency , armature loss = constant
    loss =>(I_a^2)*r_a=c_loss
32 I_a=sqrt(c_loss/r_a);
33 disp(sprintf("(b) The load current corresponding to
    maximum efficiency is %f A", I_a));
34
35 //END

```

---

### Scilab code Exa 8.5 BHP of prime mover

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 5
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 5");
7

```

```

8 //VARIABLE INITIALIZATION
9 v_t=200;                                //in Volts
10 I_l=50;                                 //in Amperes
11 r_a=0.1;                               //armature resistance in
   Ohms
12 r_f=100;                               //field resistance in Ohms
13 s_loss=500;                            //core and iron loss in
   Watts
14
15 //SOLUTION
16
17 //solution (a)
18 I_f=v_t/r_f;                          //I_sh is same as I_f and
   r_sh is same as r_f
19 I_a=I_f+I_l;
20 E_a=v_t+(I_a*r_a);
21 disp(sprintf("(a) The induced emf is %f V",E_a));
22
23 //solution (b)
24 arm_loss=(I_a^2)*r_a;                //armature copper loss
25 sh_loss=(I_f^2)*r_f;                 //shunt field copper loss
26 tot_loss=arm_loss+sh_loss+s_loss;
27 p_o=v_t*I_l;                        //output power
28 p_i=p_o+tot_loss;                  //input power
29 bhp=p_i/735.5;                     //1 metric horsepower=
   735.498W
30 disp(sprintf("(b) The Break Horse Power(B.H.P.) of
   the prime mover is %f H.P.( metric)",bhp));
31
32 //solution (c)
33 c_eff=(p_o/p_i)*100;
34 p_EE=E_a*I_a;                      //electrical power
35 m_eff=(p_EE/p_i)*100;
36 e_eff=(p_o/p_EE)*100;
37 disp(sprintf("(c) The commercial efficiency is %f %
   , the mechanical efficiency is %f %% and the
   electrical efficiency is %f %%",c_eff,m_eff,e_eff
));

```

38  
39 //END

---

Scilab code Exa 8.6 20 HP 230 V 1150 rpm shunt motor

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 6
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 p_o=20*746;           //output power from H.P. to Watts
(1 H.P.=745.699 or 746 W)
10 v_t=230;              //in Volts
11 N=1150;               //speed in rpm
12 P=4;                  //number of poles
13 Z=882;                //number of armature conductors
14 r_a=0.188;             //armature resistance in Ohms
15 I_a=73;                //armature current in Amperes
16 I_f=1.6;               //field current in Amperes
17
18 //SOLUTION
19
20 //solution (i)
21 E_b=v_t-(I_a*r_a);
22 w=(2*pi*N)/60;        //in radian/sec
23 T_e=(E_b*I_a)/w;
24 disp(sprintf("(i) The electromagnetic torque is %f N
-m", T_e));
25
26 //solution (ii)
27 A=P;                  //since it is lap winding, so A=P
and A=number of parallel paths
```

```

28 phi=(E_b*60*A)/(P*N*Z);
29 disp(sprintf("( ii) The flux per pole is %f Wb",phi))
;
30
31 //solution ( iii)
32 p_rotor=E_b*I_a; //power developed on rotor
33 p_rot=p_rotor-p_o; //p_shaft=p_out
34 disp(sprintf("( iii) The rotational power is %f W",
p_rot));
35
36 //solution ( iv)
37 tot_loss=p_rot+((I_a^2)*r_a)+(v_t*I_f);
38 p_i=p_o+tot_loss;
39 eff=(p_o/p_i)*100;
40 disp(sprintf("( iv) The efficiency is %f %%",eff));
41
42 //solution ( v)
43 T=p_o/w;
44 disp(sprintf("( v) The shaft torque is %f N-m",T));
45
46 //The answers are slightly different due to the
precision of floating point numbers
47
48 //END

```

---

### Scilab code Exa 8.7 New operating speed

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 7
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION

```

```

9 p_o=20*746;                                //output power from H.P
   . to Watts (1 H.P.=745.699 or 746 W)
10 v_t=230;                                    //in Volts
11 N1=1150;                                    //speed in rpm
12 P=4;                                         //number of poles
13 Z=882;                                       //number of armature
   conductors
14 r_a=0.188;                                  //armature resistance
   in Ohms
15 I_a1=73;                                     //armature current in
   Amperes
16 I_f=1.6;                                     //field current in
   Amperes
17 ratio=0.8;                                   //phi2 : phi1 = 0.8 ( here
   phi=flux )
18
19 //SOLUTION
20
21 E_b1=v_t-(I_a1*r_a);
22 I_a2=I_a1/ratio;                            // ( phi2 * I_a2 ) = ( phi1 *
   I_a1 )
23 E_b2=v_t-(I_a2*r_a);
24 N2=(E_b2/E_b1)*(1/ratio)*N1; //N2:N1=(E_b2/E_b1)*(
   phi1/phi2)
25 N2=round(N2);                               //to round off the
   value of N2 ( before rounding off N2=1414.695516
   rpm )
26 disp(sprintf("The new operating speed is %d rpm",N2)
   );
27
28 //The answer is slightly different due to the
   precision of floating point numbers
29
30 //END

```

---

### Scilab code Exa 8.8 250 V DC shunt machine

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 8
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 r_a=0.1;                                 //armature resistance
    in Ohms
11 r_f=125;                                //field resistance in
    Ohms
12 p_o=20*1000;                            //output power in Watts
13 N_g=1000;                               //speed as generator in
    rpm
14
15 //SOLUTION
16
17 //machine as a generator
18 I_l=p_o/v_t;
19 I_f=v_t/r_f;                            //I_f is same as I_sh
20 I_ag=I_l+I_f;
21 E_a=v_t+(I_ag*r_a);                  //induced emf = E_a =
    E_g
22
23 //machine as a motor
24 I_l=p_o/v_t;
25 I_f=v_t/r_f;
26 I_am=I_l-I_f;
27 E_b=v_t-(I_am*r_a);                  //back emf = E_b = E_m
28
29 //solution (a)
30 N_m=(N_g*E_b)/E_a;
31 N_m=round(N_m);                      //to round off the value
    of N_m
```

```

32 disp(sprintf("(a) The speed of the same machine as a
            motor is %d rpm",N_m));
33
34 //solution (b)
35
36 // (i)
37 p1=(E_a*I_ag)/1000;           //to express the answer
            in kW
38 disp(sprintf("(b) (i) The internal power developed
            as generator is %f kW",p1));
39
40 // (ii)
41 p2=(E_b*I_am)/1000;
42 disp(sprintf("(b) (ii) The internal power developed
            as motor is %f kW",p2));
43
44 //END

```

---

### Scilab code Exa 8.9 Torque developed in the motor

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 9
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 v_t=230;                             //in Volts
11 I_l=52;                              //in Amperes
12 Z=600;                               //tottal number of
            conductors
13 r_f=115;                            //in Ohms
14 d=30/100;                           //airgap diameter from cm

```

```

          to m
15 l=20/100;           //effective length of pole
16 B=4100/10000;       //flux density from Gauss
          to Wb/m^2

17
18 //SOLUTION
19 I_f=v_t/r_f;        //I_f is same as I_sh
20 I_a=I_l-I_f;
21 ar=(%pi*d*l)/P;    //area of pole
22 phi=ar*B;           //phi = flux
23 A=P;
24 T=(phi*Z*I_a)/(2*%pi*A);
25 disp(sprintf("The torque developed in the motor is
               %f N-m",T));
26
27 //The answer is different as 'A' has not been
      included in the denominator(in the book)
28
29 //END

```

---

**Scilab code Exa 8.10** 6 pole DC machine with 400 conductors

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 10
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 P=6;                  //number of poles
10 I=80;                 //current per conductor in
                           Amperes
11 Z=400;                //tottal number of
                           conductors

```

```

12 phi=0.020; //flux per pole in Wb
13 N=1800; //in rpm
14
15 //SOLUTION
16
17 //soluion (a): for wave connected
18 disp(" (a) For Wave connected");
19
20 // (i)
21 A=2; //A=number of parallel
      paths
22 I_a=I*A;
23 disp(sprintf(" (i) The total current is %f A",I_a));
24
25 // (ii)
26 E_a=(phi*Z*N*P)/(60*A);
27 disp(sprintf(" (ii) The emf is %f V",E_a));
28
29 // (iii)
30 p=E_a*I_a;
31 disp(sprintf(" (iii) The power developed in armature
      is %f kW",p/1000));
32 w=(2*pi*N)/60;
33 T_e=p/w;
34 disp(sprintf("The electromagnetic torque is %f N-m",
      T_e));
35
36
37 //soluion (b): for lap connected
38 disp(" (b) For Lap connected");
39
40 // (i)
41 A=P;
42 I_a=I*A;
43 disp(sprintf(" (i) The total current is %f A",I_a));
44
45 // (ii)
46 E_a=(phi*Z*N*P)/(60*A);

```

```

47 disp(sprintf("( ii ) The emf is %f V",E_a));
48 // ( ii )
49 p=E_a*I_a;
50 disp(sprintf("( iii ) The power developed in armature
      is %f kW",p/1000));
51 w=(2*pi*N)/60;
52 T_e=p/w;
53 disp(sprintf("The electromagnetic torque is %f N-m",
      T_e));
54
55 //END

```

---

**Scilab code Exa 8.11** Total emf generated in the armature

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 11
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 p_o=20*1000;           //output in W
10 v_t=250;               //in Volts
11 r_a=0.05;              //armature resistance in
                           Ohms
12 r_se=0.025;            //series resistance in
                           Ohms
13 r_sh=100;               //shunt resistance in Ohms
14
15 //SOLUTION
16 I_t=p_o/v_t;
17 v_se=I_t*r_se;          //for series winding
18 v_sh=v_t+v_se;          //for shunt winding

```

```

19 I_sh=v_sh/r_sh;
20 I_a=I_sh+I_t;
21 E_a=v_t+(I_a*r_a)+v_se;
22 disp(sprintf("The total emf generated is %f V",E_a))
;
23
24 //END

```

---

### Scilab code Exa 8.12 Terminal voltage of the machine

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 12
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 N=750;                               //in rpm
11 r_a=0.4;                             //in Ohms
12 r_f=200;                            //in Ohms
13 Z=720;
14 phi=2.895*(10^6)*(10^(-8));      //in Wb (1 line=10^(-8)
   Wb)
15 r_l=10;                             //load resistance in
   Ohms
16 A=2;                                //for wave winding
17
18 //SOLUTION
19 E_a=(phi*Z*N*P)/(60*A);
20 disp(sprintf("The induced emf is %f V",E_a));
21 // E_a=v+(I_a*r_a) but I_a=I_l+I_f and I_l=v/r_l ,
   I_f=v/r_f =>I_a=(v/r_l) + (v/r_f)
22 // =>E_a=v+(((v/r_l) + (v/r_f))*r_a)

```

```

23 // taking v common, the following equation is
24 // obtained
25 v=E_a/(1+(r_a/r_f)+(r_a/r_l));
26 disp(sprintf("The terminal voltage of the machine is
27 %f V",v));
28 //The answer is slightly different due to the
29 //precision of floating point numbers
30 //END

```

---

**Scilab code Exa 8.13** Current in each conductor and emf generated

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 13
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 13");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 v_t=220;                             //in Volts
11 I_l=42;                               //load current in
12 //Amperes
13 r_a=0.1;                            //in Ohms
14 r_f=110;                             //in Ohms
15 drop=1;                              //contact drop per brush
16
17 //solution (i)
18 A=P;                                  //for lap winding
19 I_f=v_t/r_f;                         //I_f is same as I_sh
20 I_a=I_l+I_f;
21 I_c=I_a/A;                           //conductor current

```

```

22 disp(sprintf("The current in each conductor of the
               armature is %d A",I_c));
23
24 //solution ( ii )
25 v_a=I_a*r_a;                      //armature voltage drop
26 v_b=2*drop;                       //brush drop
27 emf=v_t+v_a+v_b;
28 disp(sprintf("The total emf generated is %f V",emf))
   ;
29
30 //END

```

---

**Scilab code Exa 8.14** Armature resistance and load current at maximum efficiency

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 14
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 14");
7
8 //VARIABLE INITIALIZATION
9 v_t=220;                           //in Volts
10 I_l=196;                            //in Amperes
11 s_loss=720;                          //stray loss in Watts
12 r_f=55;                             //shunt field resistance
   in Ohms
13 eff=88/100;                         //efficiency
14
15 //SOLUTION
16 p_o=v_t*I_l;
17 p_i=p_o/eff;                        //electrical input
18 tot_loss=p_i-p_o;
19 I_f=v_t/r_f;

```

```

20 I_a=I_l+I_f;
21 cu_loss=v_t*I_f;           //shunt field copper
    loss
22 c_loss=cu_loss+s_loss;     //constant loss
23 arm_loss=tot_loss-c_loss;  //armature copper loss
24 r_a=arm_loss/(I_a^2);
25 disp(sprintf("The armature resistance is %f ",r_a))
    );
26
27 //for maximum efficiency , armature loss = constant
    loss =>(I_a^2)*r_a=c_loss
28 I_a=sqrt(c_loss/r_a);
29 disp(sprintf("The load current corresponding to
    maximum efficiency is %f A",I_a));
30
31 //END

```

---

### Scilab code Exa 8.15 Full load speed

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 15
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 v_t=230;                      //in Volts
10 I_a1=3.33;                     //in Amperes
11 N1=1000;                       //in rpm
12 r_a=0.3;                       //armature resistance in
    Ohms
13 r_f=160;                       // field resistance in
    Ohms
14 I_l=40;                        //in Amperes

```

```

15 phi1=1;                                // in Wb ( phi1 is an
   assumption)
16 phi2=(1-(4/100));                     // in Wb ( phi2=0.96 of
   phi1)
17
18 //SOLUTION
19
20 //At no load
21 E_a1=v_t-(I_a1*r_a);
22 I_f=v_t/r_f;
23
24 //At full load
25 I_a2=I_l-I_f;
26 E_a2=v_t-(I_a2*r_a);
27 N2=(E_a2/E_a1)*(phi1/phi2)*N1;
28 N2=round(N2);                         //to round off the value
29 disp(sprintf("The full load speed is %d rpm",N2));
30
31 //END

```

---

### Scilab code Exa 8.16 250 V 4 pole shunt motor

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 16
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 16");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 P=4;                                    //number of poles
11 Z=500;                                  //number of conductors
12 r_a=0.25;                               //in Ohms
13 r_f=125;                               //in Ohms

```

```

14 phi=0.02; //in Wb
15 I_l=14; //in Amperes
16 A=2;
17 rot_loss=300; //rotational loss in
    Watts
18
19 //SOLUTION
20
21 //solution (i)
22 I_f=v_t/r_f;
23 I_a=I_l-I_f;
24 E_a=v_t-(I_a*r_a);
25 N=(E_a*A*60)/(phi*Z*P);
26 N=round(N); //to round off the value
    of N
27 disp(sprintf("(i) The speed is %d rpm",N));
28 p_e=E_a*I_a;
29 w=(2*pi*N)/60;
30 T1=p_e/w;
31 disp(sprintf("The internal torque developed is %f N-
    m",T1));
32
33 //solution (ii)
34 p_o=p_e-rot_loss;
35 disp(sprintf("(ii) The shaft power is %f W",p_o));
36 T2=p_o/w;
37 disp(sprintf("The shaft torque is %f N-m",T2));
38 p_i=v_t*I_l;
39 eff=(p_o/p_i)*100;
40 disp(sprintf("The efficiency is %f %%",eff));
41
42 //END

```

---

**Scilab code Exa 8.17 200 V DC shunt motor**

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 17
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 17");
7
8 //VARIABLE INITIALIZATION
9 v_t=200; //in Volts
10 I_l=22; //in Amperes
11 N1=1000; //in rpm
12 r_a=0.1; //in Ohms
13 r_f=100; //in Ohms
14 N2=800; //in rpm
15
16 //SOLUTION
17
18 //solution ( i )
19 I_f=v_t/r_f;
20 I_a1=I_l-I_f;
21 E_a1=v_t-(I_a1*r_a);
22 //on rearranging the equation  $E_a2:E_a1=N2:N1$ , where
    $E_a2=v_t-I_a1*(r_a+r_s)$  and  $E_a1=v_t-(I_a1*r_a)$ ,
   we get ,
23 r_s1=((v_t - ((N2*E_a1)/N1))/I_a1)-r_a;
24 disp(sprintf("( i ) When the load torque is
   independent of speed , the additional resistance
   is %f ",r_s1));
25
26 //solution ( ii )
27 I_a2=(N2/N1)*I_a1;
28 //on rearranging the equation  $E_a2:E_a1=N2:N1$ , where
    $E_a2=v_t-I_a2*(r_a+r_s)$  and  $E_a1=v_t-(I_a1*r_a)$ ,
   we get ,
29 r_s2=((v_t - ((N2*E_a1)/N1))/I_a2)-r_a;
30 disp(sprintf("( ii ) When the load torque is
   proportional to speed , the additional resistance
   is %f ",r_s2));

```

```

31
32 //solution (iii)
33 I_a2=(N2^2/N1^2)*I_a1;
34 //on rearranging the equation E_a2:E_a1=N2:N1, where
    E_a2=v_t-I_a2*(r_a+r_s) and E_a1=v_t-(I_a1*r_a),
    we get ,
35 r_s3=((v_t - ((N2*E_a1)/N1))/I_a2)-r_a;
36 disp(sprintf("(iii)When the load torque varies as
    the square of speed , the additional resistance is
    %f ",r_s3));
37
38 //solution (iv)
39 I_a2=(N2^3/N1^3)*I_a1;
40 //on rearranging the equation E_a2:E_a1=N2:N1, where
    E_a2=v_t-I_a2*(r_a+r_s) and E_a1=v_t-(I_a1*r_a),
    we get ,
41 r_s4=((v_t - ((N2*E_a1)/N1))/I_a2)-r_a;
42 disp(sprintf("(iv)When the load torque varies as the
    cube of speed , the additional resistance is %f
    ",r_s4));
43
44 //END

```

---

### Scilab code Exa 8.18 Value of inserted resistance

```

1 //CHAPTER 8– DIRECT CURRENT MACHINES
2 //Example 18
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 18");
7
8 //VARIABLE INITIALIZATION
9 v_t=460;                                //in Volts
10 p_o=10*736;                             //in Watts (1 metric H.

```

```

P=735.5 W)
11 ratio=85/100; // as given in the
      question
12 eff=84/100;
13 I_f=1.1; //in Amperes
14 r_a=0.2; //in Ohms
15
16 //SOLUTION
17 p_i=p_o/eff;
18 I_l=p_i/v_t;
19 I_a=I_l-I_f;
20 E1=v_t-(I_a*r_a);
21 E2=E1*ratio; //E2:E1=N2:N1=ratio
22 v=v_t-E2; //voltage drop across
      r_a and r_s (r_s is the series resistance to be
      inserted)
23 r_s=(v/I_a)-r_a;
24 disp(sprintf("The resistance required is %f ",r_s));
25
26 //The answer is different because ratio equals
      85/100 and not 75/100
27
28 //END

```

---

**Scilab code Exa 8.19** New speed of motor on inserting a 250 ohm resistance

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 19
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 19");
7

```

```

8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 r_a=0.5;                                 //in Ohms
11 r_f=250;                                 //in Ohms
12 N1=600;                                  //in rpm
13 I=21;                                    //in Amperes
14 r_s=250;                                 //in Ohms
15
16 //SOLUTION
17 I_f1=v_t/r_f;
18 I_f2=v_t/(r_f+r_s);
19 I_a1=I-I_f1;
20 // T is directly proportional to ( *I_a)
21 // I_f is directly proportional to
22 // => I_f1*I_a1=I_f2*I_a2, therefore ,
23 I_a2=(I_f1*I_a1)/I_f2;
24 E_b1=v_t-(I_a1*r_a);
25 E_b2=v_t-(I_a2*r_a);
26 // E_b is directly proportional to ( *N)
27 // ( *N) is directly proportional to ( I_f*N)
28 // =>E_b1:E_b2=(I_f1:I_f2)*(N1:N2)
29 N2=(I_f1/I_f2)*(E_b2/E_b1)*N1;
30 N2=round(N2);                           //to round off the value
31 disp(sprintf("The new speed of the motor is %d rpm",
N2));
32
33 //END

```

---

**Scilab code Exa 8.20** Reduction of main flux to raise the speed by 50 percent

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 20
3
4 clc;

```

```

5 disp("CHAPTER 8");
6 disp("EXAMPLE 20");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 I_a1=20;                                 //in Amperes
11 N1=1000;                                //in rpm
12 r_a=0.5;                                 //in Ohms
13 drop=1;                                  //brush contact drop in
   Volts
14 ratio=1.5;                               //N2:N1=1.5
15 phi1=1;                                  //it is an assumption
16
17 //SOLUTION
18 E_1=v_t-(I_a1*r_a)-(2*drop);
19 //solving the quadratic equation directly ,
20 a=1;
21 b=-496;
22 c=14280;
23 D=b^2-(4*a*c);
24 x1=(-b+sqrt(D))/(2*a);
25 x2=(-b-sqrt(D))/(2*a);
26 if(x1<40)
27 I_a2=x1;
28 else if(x2<40)
29 I_a2=x2;
30 end;
31 phi2=(I_a1/I_a2)*phi1;
32 phi=(1-phi2)*100;
33 disp(sprintf("The flux to be reduced is %f %% of the
   main flux",phi));
34
35 //END

```

---

**Scilab code Exa 8.21** 10 kW 6 pole DC generator

```

1 //CHAPTER 8– DIRECT CURRENT MACHINES
2 //Example 21
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 21");
7
8 //VARIABLE INITIALIZATION
9 p_o=10*1000; //in Watts
10 P=6; //number of poles
11 E_g=200; //in Volts
12 N=1500; //in rpm
13 A=P; //since the armature
14 is lap connected
15 B=0.9; //flux density in
16 Tesla
17 l=0.25; //length of armature
18 in m
19 dia=0.2; //diameter of armature
20 in m
21
22 //SOLUTION
23
24 //solution (a)
25 area=2*pi*(dia/2)*l;
26 phi=B*area;
27 disp(sprintf("(a) The flux per pole is %f Wb",phi));
28
29 //solution (b)
30 Z=(60*E_g)/(phi*N);
31 disp(sprintf("(b) The total number of active
32 conductors is %d",Z));
33
34 //solution (c)
35 I_a=50;
36 p=E_g*I_a;
37 w=(2*pi*N)/60;
38 T=p/w;

```

```

34 disp(sprintf("(c) The torque developed when armature
               current is 50 A is %f N-m",T));
35
36 //END

```

---

**Scilab code Exa 8.22** Shunt wound motor running at 600 rpm from a 230 V supply

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 22
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 22");
7
8 //VARIABLE INITIALIZATION
9 N1=600;                                //in rpm
10 v=230;                                  //in Volts
11 I_11=50;                                 //line current in
                                             Ampères
12 r_a=0.4;                                //armature resistance
                                             in Ohms
13 r_f=104.5;                               //field resistance in
                                             Ohms
14 drop=2;                                  //brush drop in Volts
15
16 //SOLUTION
17
18 //solution (i)
19 I_12=5;
20 I_a1=I_11-(v/r_f);
21 E_b1=v-(I_a1*r_a)-drop;
22 I_a2=I_12-(v/r_f);
23 E_b2=v-(I_a2*r_a)-drop;
24 N2=(E_b2/E_b1)*N1;

```

```

25 N2=round(N2);
26 disp(sprintf("( i) The speed at no load is %d rpm",N2
));
27
28 //solution ( ii)
29 I_12=50;
30 N2=500;
31 E_b2=(N2/N1)*E_b1;
32 dif=v-drop; // difference
33 I_a2=I_12-(v/r_f);
34 r_se=((dif-E_b2)/I_a2)-r_a;
35 disp(sprintf("( ii) The additional resistance is %f
",r_se));
36
37 //solution ( iii) // it is an assumption
38 phi1=1;
39 I_a3=30;
40 N2=750;
41 E_b3=v-(I_a3*r_a)-drop;
42 phi2=(E_b3/E_b1)*(N1/N2)*phi1;
43 red=((1-phi2)*100*phi1)/phi1;
44 disp(sprintf("( iii) The percentage reduction of flux
per pole is %f %%",red));
45
46 //END

```

---

**Scilab code Exa 8.23** Value of inserted resistance in field circuit for increasing the speed

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 23
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 23");

```

```

7
8 //VARIABLE INITIALIZATION
9 v=230;                                //in Volts
10 r_a=0.4;                               //in Ohms
11 r_f1=115;                             //in Ohms
12 I_a=20;                                //in Amperes
13 N1=800;                                //in rpm
14 N2=1000;                             //in rpm
15
16 //SOLUTION
17 I_f1=v/r_f;
18 E_b1=v-(I_a*r_a);
19 //rearranging the equation , we get ,
20 r_f2=((E_b1*N2)/((v*N1)-(N1*I_a*r_a)))*r_f1;
21 r_f2_dash=r_f2-r_f1;
22 disp(sprintf("The external resistance is %f ", r_f2_dash));
23
24 //The answer is slightly different due to the
   precision of floating point numbers
25
26 //END

```

---

**Scilab code Exa 8.24** New speed of motor on inserting a 250 ohm resistance in the field circuit

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 24
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 24");
7
8 //This example is same as example 19
9

```

```

10 //VARIABLE INITIALIZATION
11 v=250;                                //in Volts
12 r_a=0.5;                               //in Ohms
13 r_f=250;                               //in Ohms
14 N1=600;                                //in rpm
15 I_l=21;                                 //in Amperes
16 r=250;                                  //in Ohms
17
18 //SOLUTION
19 I_f1=v/r_f;
20 I_a1=I_l-I_f1;
21 I_a2=2*I_a1;
22 E_b1=v-(I_a1*r_a);
23 E_b2=v-(I_a2*r_a);
24 ratio=(r+r_f)/r_f;
25 N2=(ratio*N1*E_b2)/E_b1;
26 N2=round(N2);
27 disp(sprintf("The new speed is %d rpm",N2));
28
29 //END

```

---

### Scilab code Exa 8.25 24 slot 2 pole DC machine

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 25
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 25");
7
8
9 //VARIABLE INITIALIZATION
10 slot=24;                                //number of slots
11 P=2;                                     //number of poles
12 N=18;                                    //number of turns per

```

```

    coil
13 B=1;                                //in Webers
14 l=20/100;                           //effective length in
   meters
15 rad=10/100;                          //radius in meters
16 w=183.2;                            //angular velocity in
   rad/s

17
18 //SOLUTION
19 A=2;
20 Z=slot*P*N;                         //total number of
   conductors
21 ar1=(2*%pi*rad*l)/P;
22 ar2=ar1*0.8;                          //since the magnetic
   poles 80% of the armature periphery
23 phi=B*ar2;                           //effective flux per
   pole

24
25 //solution (a)
26 E_a=(P*Z*phi*w)/(2*%pi*A);
27 disp(sprintf("(a) The induced emf is %f V",E_a));
28
29 //solution (b)
30 coil=slot/P;                         //number of coils in
   each path
31 E_coil=E_a/coil;
32 disp(sprintf("(b) The induced emf per coil is %f V",
   E_coil));

33
34 //solution (c)
35 E_turn=E_coil/N;
36 disp(sprintf("(c) The induced emf per turn is %f V",
   E_turn));

37
38 //solution (d)
39 E_cond=E_turn/A;
40 disp(sprintf("(d) The induced emf per conductor is
   %f V",E_cond));

```

```

41
42 //The answers are slightly different due to the
   precision of floating point numbers
43
44 //END

```

---

**Scilab code Exa 8.27** Counter emf of motor and power developed in armature

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 27
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 27");
7
8
9 //VARIABLE INITIALIZATION
10 v_t=200;                      //in volts
11 r_a=0.06;                      //in Ohms
12 r_se=0.04;                     //in Ohms
13 p_i=20*1000;                  //in Watts
14
15 //SOLUTION
16
17 //solution (a)
18 I_a=p_i/v_t;
19 E_b=v_t-I_a*(r_a+r_se);
20 disp(sprintf("(a) The counter emf of the motor is %d
   V",E_b));
21
22 //solution (b)
23 p_a=E_b*I_a;
24 p_a=p_a/1000;                  //from W to kW
25 disp(sprintf("(b) The power developed in the

```

```
    armature is %d kW" ,p_a));  
26  
27 //END
```

---

**Scilab code Exa 8.28** Voltage between far end of feeder and bus bar

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES  
2 //Example 28  
3  
4 clc;  
5 disp("CHAPTER 8");  
6 disp("EXAMPLE 28");  
7  
8 //VARIABLE INITIALIZATION  
9 E_a=120;                      //in Volts  
10 r_se=0.03;                     //in Ohms  
11 r_a=0.02;                      //in Ohms  
12 v1=240;                        //in Volts  
13 r=0.25;                         //in Ohms  
14 I=300;                          //in Amperes  
15  
16 //SOLUTION  
17 v=I*(r_se+r_a+r);  
18 disp(sprintf("The voltage drop across the three  
             resistances is %d V",v));  
19 v_t=v1+E_a-v;  
20 disp(sprintf("The voltage between far end and the  
             bus bar is %d V",v_t));  
21 disp(sprintf("The net increase of %d V may be beyond  
             the desired limit",v_t-v1));  
22 disp("Hence, a field diverter resistance may be  
             necessary to regulate the far-end terminal  
             voltage");  
23  
24 //END
```

---

**Scilab code Exa 8.29** Speed of motor when connected in series with 5 ohm resistance

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 29
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 29");
7
8 //VARIABLE INITIALIZATION
9 r_a=1;                                //in Ohms
10 N1=800;                                 //in rpm
11 v_t=200;                                //in Volts
12 I_a=15;                                 //in Amperes
13 r_s=5;                                  //series resistance in
                                           Ohms
14
15 //SOLUTION
16 E_b1=v_t-(I_a*r_a);
17 E_b2=v_t-I_a*(r_a+r_s);
18 N2=(E_b2/E_b1)*N1;
19 N2=round(N2);                          //to round off the value
20 disp(sprintf("The speed attained after connecting
               the series resistance is %d rpm",N2));
21
22 //END
```

---

**Scilab code Exa 8.30** Value of starting torque

```
1 //CHAPTER 8- DIRECT CURRENT MACHINES
```

```

2 //Example 30
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 30");
7
8 //VARIABLE INITIALIZATION
9 p=5*735.5;                                //in Watts (1 metric H.P
   .=735.5 W)
10 N=1000;                                     //in rpm
11 I=30;                                       //in Amperes
12 I_s=45;                                     //starting current in
   Amperes
13
14 //SOLUTION
15 T=(p*60)/(2*pi*1000);
16 T_s=(T*(I_s^2))/(I^2);
17 disp(sprintf("The starting torque is %f N-m",T_s));
18
19 //The answer is slightly different due to precision
   of floating point numbers
20
21 //END

```

---

**Scilab code Exa 8.31** Value of speed when flux is increased by 20 percent

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 31
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 31");
7
8 //VARIABLE INITIALIZATION
9 r_a=0.1;                                      //combined resistance of

```

```

        armature & field resistance in Ohms
10 v_t=230;                                //in Volts
11 I_a1=100;                                //in Amperes
12 N1=1000;                                 //in rpm
13 I_a2=200;                                //in Amperes
14 ratio=1.2;                               //ratio of 2 : 1 =1.2
15
16 //SOLUTION
17 E_b1=v_t-(I_a1*r_a);                    // numerator of LHS
    according to the book
18 E_b2=v_t-(I_a2*r_a);                    // denominator of LHS
    according to the book
19 N2=(E_b2/E_b1)*(1/ratio)*N1;
20 N2=round(N2);                           //to round off the value
21 disp(sprintf("The new speed of the armature is %d
    rpm",N2));
22
23 //END

```

---

**Scilab code Exa 8.32** 250 V series motor with 20 A current and 1000 rpm

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 32
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 32");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 I=20;                                    //in Amperes
11 N1=1000;                                 //in rpm
12 P=4;                                     //number of poles
13 r_p=0.05;                                //resistance of field
    coil on each pole in Ohms

```

```

14 r_a=0.2;                                //in Ohms
15
16 //SOLUTION
17
18 r_se=P*r_p;
19 r_m=r_a+r_se;                         //resistance of motor
20 E_b1=v_t-(I*r_m);
21 T1=I^2;
22
23 //solution (a)
24 //solving the quadratic equation directly ,
25 r=10;                                    //in Ohms
26 a=1.02;
27 b=-25;
28 c=-400;
29 D=b^2-(4*a*c);
30 x1=(-b+sqrt(D))/(2*a);
31 x2=(-b-sqrt(D))/(2*a);
32 //to extract the positive root out of the two
33 if (x1>0 & x2<0)
34 I1=x1;
35 else (x1<0 & x2>0)
36 I1=x2;
37 end;
38 I_a=((10.2*I1)-v_t)/r;
39 E_b2=v_t-(I_a*r_a);
40 N2=((E_b2/E_b1)*I*N1)/I1;
41 N2=round(N2);                          //to round off the value
42 disp(sprintf("(a) The speed with 10 resistance in
parallel with the armature is %d rpm",N2));
43
44 //solution (b)
45 //solving the quadratic equation directly ,
46 a=5/7;
47 b=0;
48 c=-400;
49 D=b^2-(4*a*c);
50 y1=(-b+sqrt(D))/(2*a);

```

```

51 y2=(-b-sqrt(D))/(2*a);
52 //to extract the positive root out of the two
53 if (y1>0 & y2<0)
54 I2=y1;
55 else (y1<0 & y2>0)
56 I2=y2;
57 end;
58 E_b3=v_t-(I2*r_a);
59 N3=((E_b3/E_b1)*I*N1)/(I2*a);
60 N3=round(N3); //to round off the value
61 disp(sprintf("(b) The speed with 0.5 resistance
       in parallel with series field is %d rpm",N3));
62
63 //The answers are slightly different due to the
   precision of floating point numbers
64
65 //END

```

---

**Scilab code Exa 8.33** Resistance to be added to obtain rated torque at starting and at 1000 rpm

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 33
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 33");
7
8 //VARIABLE INITIALIZATION
9 v_t=230; //in Volts
10 N1=1500; //in rpm
11 I_a1=20; //in Amperes
12 r_a=0.3; //armature resistance
           in Ohms
13 r_se=0.2; //series field

```

```

    resistance in Ohms
14
15 //SOLUTION
16
17 // solution (a)
18 E_b=0;                                //at starting
19 nr1=v_t-I_a1*(r_a+r_se);             //value of numerator
20 r_ext=nr1/I_a1;
21 disp(sprintf("(a) At starting, the resistance that
      must be added is %f    ",r_ext));
22
23 //solution (b)
24 I_a2=I_a1;
25 N2=1000;
26 ratio=N2/N1;
27 nr2=v_t-I_a2*(r_a+r_se);
28 r_ext=((ratio*nr1)-nr2)/(-I_a2);
29 disp(sprintf("(b) At 1000 rpm, the resistance that
      must be added is %f    ",r_ext));
30
31 //END

```

---

### Scilab code Exa 8.34 Total emf and armature current

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 34
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 34");
7
8 //VARIABLE INITIALIZATION
9 r_a=0.06;                                //armature resistance
      in Ohms
10 r_se=0.04;                               //series resistance in

```

```

    Ohms
11 r_sh=25;                                //shunt resistance in
    Ohms
12 v_t=110;                                 //in Volts
13 I_l=100;                                 //in Amperes
14
15 //SOLUTION
16
17 //solution (a)
18 I_sh=v_t/r_sh;
19 I_a=I_sh+I_l;
20 E_g=v_t+I_a*(r_a+r_se);
21 disp("(a) When the machine is connected as long
        shunt compound generator-");
22 disp(sprintf("The armature current is %f A and the
        total emf is %f V",I_a,E_g));
23
24 //solution (b)
25 I_sh=(v_t/r_sh)+(I_l*r_se/r_sh);
26 I_a=I_sh+I_l;
27 E_g=v_t+(I_a*r_a)+(I_l*r_se);
28 disp("(b) When the machine is connected as short
        shunt compound generator-");
29 disp(sprintf("The armature current is %f A and the
        total emf is %f V",I_a,E_g));
30
31 //END

```

---

### Scilab code Exa 8.35 Armature current and induced emf

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 35
3
4 clc;
5 disp("CHAPTER 8");

```

```

6 disp("EXAMPLE 35");
7
8 //VARIABLE INITIALIZATION
9 r_a=0.06;                                //armature resistance
   in Ohms
10 r_se=0.04;                                //series resistance in
   Ohms
11 r_sh=25;                                   //shunt resistance in
   Ohms
12 v_t=110;                                    //in Volts
13 I_l=100;                                    //in Amperes
14
15 //SOLUTION
16
17 //solution (a)
18 I_sh=v_t/r_sh;
19 I_a=I_l-I_sh;
20 E_g=v_t-I_a*(r_a+r_se);
21 disp("(a) When the machine is connected as long
   shunt compound generator-");
22 disp(sprintf("The armature current is %f A and the
   total emf is %f V",I_a,E_g));
23
24 //solution (b)
25 I_sh=(v_t/r_sh)-(I_l*r_se/r_sh);
26 I_a=I_l-I_sh;
27 E_g=v_t-(I_a*r_a)-(I_l*r_se);
28 disp("(b) When the machine is connected as short
   shunt compound generator-");
29 disp(sprintf("The armature current is %f A and the
   total emf is %f V",I_a,E_g));
30
31 //END

```

---

**Scilab code Exa 8.36** Constant losses and full load efficiency

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 36
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 36");
7
8 //VARIABLE INITIALIZATION
9 v_t=250;                                //in Volts
10 I_l=150;                                 //in Amperes
11 loss1=1200;                             //core loss at full load
12          in Watts
13 loss2=800;                               //mechanical loss in
14          Watts
15 r_b=0.08;                               //brush resistance in
16          Ohms
17 r_sh=62.5;                             //shunt field resistance
18          in Ohms
19 r_se=0.03;                             //series field
20          resistance in Ohms
21 r_ip=0.02;                             //interpole resistance
22          in Ohms
23
24 //SOLUTION
25
26 //solution (a)
27 p_o=v_t*I_l;
28 I_sh=v_t/r_sh;
29 I_a=I_l+I_sh;
30 r_tot=r_b+r_se+r_ip;
31 arm_loss=(I_a^2)*r_tot;                //armature circuit
32          copper loss
33 cu_loss=v_t*I_sh;                      //shunt field copper
34          loss
35 c_loss=cu_loss+loss1+loss2;            //constant loss
36 disp(sprintf("(a) The constant loss is %f W",c_loss));
37
38
39

```

```

30 //solution (b)
31 tot_loss=arm_loss+c_loss;      //total loss
32 p_i=p_o+tot_loss;
33 eff=(p_o/p_i)*100;
34 disp(sprintf("(b) The full load efficiency is %f %%"
35 ,eff));
36 //END

```

---

### Scilab code Exa 8.37 Hysteresis and eddy current losses

```

1 //CHAPTER 8- DIRECT CURRENT MACHINES
2 //Example 37
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 37");
7
8 //VARIABLE INITIALIZATION
9 p_o=50*1000;                      //in Watts
10 v_t=250;                          //in Volts
11 loss1=5000;                       //total core loss in
12 Watts
12 loss2=2000;                       //total core loss in
13 Watts (when speed is reduced to half)
13 speed=125/100;
14
15 //SOLUTION
16
17 //solution (a)
18
19 //W_h=A*N, where W_h=hysteresis loss , A=constant and
20 N=speed
20 //W_e=B*(N^2) , where W_e=eddy current loss , B=
21 constant and N=speed

```

```

21 //W_h+(W_e^2)=loss1 =>W_h+W_e=5000
22 // (W_h/2)+(W_e/4)=loss2 =>(0.5*W_h)+(0.25*W_e)=2000
    (when speed reduces to half)
23 //So, we get two equations
24 //W_h+W_e = 5 0 0 0 ..... eq( i )
25 // (0.5*W_h)+(0.25*W_e) = 2 0 0 0 ..... eq( ii )
26 //solving the equations by matrix method
27 A=[1 1;0.5 0.25];
28 b=[5000;2000];
29 x=inv(A)*b;
30 W_h1=x(1,:);           // to access the 1st row
    of 2X1 matrix
31 W_e1=x(2,:);           // to access the 2nd row
    of 2X1 matrix
32 disp("Solution (a)");
33 disp(sprintf("The hysteresis loss at full speed is
    %d W",W_h1));
34 disp(sprintf("The eddy current loss at full speed is
    %d W",W_e1));
35
36 //solution (b)
37 W_h2=speed*W_h1;
38 W_e2=(speed^2)*W_e1;
39 disp("Solution (b)");
40 disp(sprintf("The hysteresis loss at 125% of the
    full speed is %d W",W_h2));
41 disp(sprintf("The eddy current loss at 125% of the
    full speed is %d W",W_e2));
42
43 //END

```

---

**Scilab code Exa 8.38** Speed of motor when flux per pole is increased by 10 percent

1 //CHAPTER 8– DIRECT CURRENT MACHINES

```

2 //Example 38
3
4 clc;
5 disp("CHAPTER 8");
6 disp("EXAMPLE 38");
7
8 //VARIABLE INITIALIZATION
9 v_t=215;                                //in Volts
10 r_a=0.4;                                 //in Ohms
11 p=5*1000;                               //in Watts
12 N_g=1000;                                //speed as generator in
                                             rpm
13 ratio=1.1;                               //according to the
                                             solution ,   _b :   _a =1.1
14
15 //SOLUTION
16
17 //As generator
18 I_ag=p/v_t;
19 E_a=v_t+(I_ag*r_a);
20
21 //As motor
22 I_am=p/v_t;
23 E_b=v_t-(I_am*r_a);
24 N_m=(1/ratio)*N_g*(E_b/E_a);
25 N_m=round(N_m);                         //to round off the
                                             value
26 disp(sprintf("The speed of the machine as motor is
                 %d rpm",N_m));
27
28 //END

```

---

# Chapter 10

## Three Phase Induction Machines

Scilab code Exa 10.2 6 pole wound rotor induction motor

```
1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 2
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 P=6;                                //number of poles
10 f1=60;                               //stator frequency in
                                         Hertz
11 N_r1=1140;                           //in rpm
12
13 //SOLUTION
14 N_s=(120*f1)/P;                     //synchronous speed
15 s1=(N_s-N_r1)/N_s;                  //slip at full load
16
17 //solution (a)
18 N_r2=0;                             //rotor speed at
```

```

        standstill is zero
19 s2=(N_s-N_r2)/N_s;
20 disp(sprintf("(a) At standstill , the slip is %f %%",
    s2*100));
21 if(s2>1)
22 disp("Since the slip is greater than 100%, the motor
    operates as brake");
23 end;
24 if(s2<0)
25 disp("Since the slip is negative , the motor operates
    as generator");
26 end;
27 f2=s2*f1;
28 disp(sprintf("And the frequency of rotor current is
    %d Hz",f2));
29 if(f2<0)
30 disp("Since frequency is negative , phase sequence of
    voltage induced in rotor winding is reversed");
31 end;
32
33 //solution (b)
34 N_r3=500;
35 s3=(N_s-N_r3)/N_s;
36 disp(sprintf("(b) At %d rpm , the slip is %f %%",N_r3
    ,s3*100));
37 if(s3>1)
38 disp("Since the slip is greater than 100%, the motor
    operates as brake");
39 end;
40 if(s3<0)
41 disp("Since the slip is negative , the motor operates
    as generator");
42 end;
43 f3=s3*f1;
44 disp(sprintf("And the frequency is %d Hz",f3));
45 if(f3<0)
46 disp("Since frequency is negative , phase sequence of
    voltage induced in rotor winding is reversed");

```

```

47 end;
48
49 //solution (c)
50 N_r4=500;
51 s4=(N_s+N_r4)/N_s; //as motor runs in
    opposite direction
52 disp(sprintf("(c) At %d rpm, the slip is %f %%",N_r4
    ,s4*100));
53 if(s4>1)
54 disp("Since the slip is greater than 100%, the motor
    operates as brake");
55 end;
56 if(s4<0)
57 disp("Since the slip is negative, the motor operates
    as generator");
58 end;
59 f4=s4*f1;
60 disp(sprintf("And the frequency is %d Hz",f4));
61 if(f4<0)
62 disp("Since frequency is negative, phase sequence of
    voltage induced in rotor winding is reversed");
63 end;
64
65 //solution (d)
66 N_r5=2000;
67 s5=(N_s-N_r5)/N_s;
68 disp(sprintf("(d) At %d rpm, the slip is %f %%",N_r5
    ,s5*100));
69 if(s5>1)
70 disp("Since the slip is greater than 100%, the motor
    operates as brake");
71 end;
72 if(s5<0)
73 disp("Since the slip is negative, the motor operates
    as generator");
74 end;
75 f5=s5*f1;
76 disp(sprintf("And the frequency is %d Hz",f5));

```

```

77 if(f5<0)
78 disp("Since frequency is negative , phase sequence of
      voltage induced in rotor winding is reversed");
79 end;
80
81 //END

```

---

**Scilab code Exa 10.3** 3 phase induction motor running at 1140 rpm

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 3
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 3");
7
8 //VARIABLE INITIALIZATION
9 N_r=1140;                                // full load speed
     in rpm
10 f=60;                                     // frequency in Hz
11
12 //SOLUTION
13
14 //solution (i)
15 P=(120*f)/N_r;
16 P=round(P);                               //since the number
     of poles cannot be a fraction
17 disp(sprintf("( i ) The number of poles is %d",P));
18
19 //solution (ii)
20 N_s=(120*f)/P;
21 s=(N_s-N_r)/N_s;
22 disp(sprintf("( ii ) The slip at full load is %d %%",s
     *100));
23

```

```

24 //solution (iii)
25 f_r=s*f;
26 disp(sprintf("(iii) The frequency of the rotor
    voltge is %d Hz",f_r));
27
28 //solution (iv)
29 N1=(120*f_r)/P;                                //speed of rotor
    field w.r.t stator
30 N1=round(N1);
31 disp(sprintf("(iv) The speed of rotor field w.r.t
    rotor is %d rpm",N1));
32
33 //solution (v)
34 N2=N_r+N1;                                     //speed of stator
    field w.r.t stator field
35 N3=N_s-N2;                                     //speed of rotor
    field w.r.t stator field
36 disp(sprintf("(v) The speed of rotor field w.r.t
    stator field is %d rpm",N3));
37 disp("Hence, the rotor field is stationary w.r.t
    stator field");
38
39 //solution (vi)
40 ratio=10/100;                                  //since it is
    specified that slip is 10%
41 N_r=N_s*(1-ratio);
42 N_r=round(N_r);
43 disp(sprintf("(vi) The speed of rotor at 10% slip
    is %d rpm",N_r));
44 s1=(N_s-N_r)/N_s;
45 fr=s1*f;
46 disp(sprintf(" The rotor frequency at this speed is
    %f Hz",fr));
47
48 //solution (vii)
49 v=230;
50 ratio1=1/0.5;                                  //stator to rotor
    turns ratio

```

```

51 E_rotor=v*(1/ratio1);
52 E_rotor_dash=ratio*E_rotor;
53 disp(sprintf("(vii) The rotor induced emf is %f V" ,
54 E_rotor_dash));
55 //END

```

---

### Scilab code Exa 10.4 3 phase squirrel cage motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 4
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 4");
7
8 //VARIABLE INITIALIZATION
9 r2=0.2;                                // in Ohms
10 X2=2;                                   // in Ohms
11
12 //SOLUTION
13 s_m=r2/X2;
14
15 //solution (a)
16 s=1;
17 ratio1=2/((s/s_m)+(s_m/s));           // ratio of T_starting
                                             and T_max
18 ratio2=2*ratio1;                      // ratio of T_starting
                                             and T_full-load (T_max=2*T_full-load)
19 disp(sprintf("(a) If the motor is started by direct-
on-line starter , the ratio of starting torque to
full load torque is %f",ratio2));
20
21 //solution (b)
22 ratio3=(1/3)*ratio2;                  // In star-delta

```

```

        starter , T_starting=(1/3)*T_starting_of_DOL
23 disp(sprintf("(b) If the motor is started by star-
    delta starter , the ratio of starting torque to
    full load torque is %f",ratio3));
24
25 //solution (c)
26 ratio4=0.7*2*ratio2;           //due to 70% tapping
27 disp(sprintf("(c) If the motor is started by auto-
    transformer , the ratio of starting torque to full
    load torque is %f",ratio4));
28
29 //END

```

---

### Scilab code Exa 10.5 Speed of motor

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 5
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 5");
7
8 //VARIABLE INITIALIZATION
9 P1=12;                                //number of poles
    of alternator
10 N_s1=500;                             //synchronous speed
    of 12-pole alternator in rpm
11 P2=8;                                  //number of poles
    of motor
12 s=0.03;                               //slip of the motor
    in p.u.
13
14 //SOLUTION
15 f=(N_s1*P1)/120;                      //synchronous speed
16 N_s2=(120*f)/P2;

```

```

        of 8-pole alternator in rpm
17 N_r=N_s2*(1-s);
18 N_r=round(N_r);                                //to round off the
                                                 value
19 disp(sprintf("The speed of the motor is %d rpm",N_r))
 );
20
21 //END

```

---

### Scilab code Exa 10.6 Speed of 4 pole induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 6
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 6");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                         //number of poles
10 f_r=2;                                       //rotor frequency in
                                                 Hertz
11 f_s=50;                                      //stator frequency in
                                                 Hertz
12 E=400;                                       //line voltage in Volts
13 ratio=1/0.5;                                 //stator to rotor turn
                                                 ratio
14
15 //SOLUTION
16 s=f_r/f_s;
17 N_s=(120*f_s)/P;                            //synchronous speed
18 N_r=N_s*(1-s);                            //rotor speed
19 N_r=round(N_r);
20 disp(sprintf("The speed of the motor is %d rpm",N_r))
 );

```

```

21 E_s=E/sqrt(3); //phase voltage=(line
                  voltage)/sqrt(3) for star connection
22 E_r=E_s*(1/ratio);
23 E_r_dash=s*E_r;
24 disp(sprintf("The rotor induced emf above 2 Hz is %f
                  V per phase",E_r_dash)); //Answer given in the
                  book is wrong
25
26 //END

```

---

### Scilab code Exa 10.7 4 pole 3 phase induction motor

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 7
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 7");
7
8 //VARIABLE INITIALIZATION
9 P=4; //number of poles
10 f=50; //frequency in Hz
11 r2=0.1; //rotor resistance in
            Ohms
12 X2=2; //standstill
            reactance in Ohms
13 E1=100; //induced emf between
            slip ring in Volts
14 N_r=1460; //full load speed in
            rpm
15
16 //SOLUTION
17
18 //solution (i)
19 N_s=(120*f)/P;

```

```

20 s_f1=(N_s-N_r)/N_s;
21 disp(sprintf("( i) The slip at full load is %f %%",
22 s_m=r2/X2;
23 disp(sprintf("The slip at which maximum torque
24 occurs is %f %%",s_m*100));
25 //solution ( ii)
26 E2=E1/sqrt(3); //phase voltage=(line
27 disp(sprintf("( ii) The emf induced in rotor is %f V
28 per phase",E2));
29 //solution ( iii)
30 X2_dash=s_f1*X2;
31 disp(sprintf("( iii) The rotor reactance per phase is
32 %f ",X2_dash));
33 //solution ( iv)
34 z=sqrt((r2^2)+(X2_dash)^2);
35 I2=(s_f1*E2)/z;
36 disp(sprintf("( iv) The rotor current is %f A",I2));
37 //solution ( v)
38 pow_fact_r=r2/z;
39 disp(sprintf("( v) The rotor power factor is %f (
40 lagging)",pow_fact_r));
41
42 //END

```

---

**Scilab code Exa 10.8** 3 phase induction motor with synchronous speed  
1200 rpm

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 8

```

```

3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 8");
7
8 //VARIABLE INITIALIZATION
9 N_s=1200; //synchronous speed in
            rpm
10 p_in=80; //input power in kW
11 loss=5; //copper and iron
            losses in kW
12 f_loss=2; //friction and windage
            loss in kW
13 N=1152; //rotor speed in rpm
14
15 //SOLUTION
16
17 //solution (a)
18 p_rotor=p_in-loss;
19 disp(sprintf("(a) The active power transmitted to
rotor is %d kW",p_rotor));
20
21 //solution (b)
22 s=(N_s-N)/N_s;
23 cu_loss=s*p_rotor;
24 disp(sprintf("(b) The rotor copper loss is %d kW",
cu_loss));
25
26 //solution (c)
27 p_m=(1-s)*p_rotor; //since P2:Pcu:Pm=1:s
            :(1-s)
28 disp(sprintf("(c) The mechanical power developed is
%d kW",p_m));
29
30 //solution (d)
31 p_shaft=p_m-f_loss; //output power
32 disp(sprintf("(d) The mechanical power developed to
load is %d kW",p_shaft));

```

```

33
34 //solution (e)
35 eff=p_shaft/p_in;
36 disp(sprintf("(e) The efficiency of the motor is %f
37 %%", eff*100));
38 //END

```

---

### Scilab code Exa 10.9 150 kW 6 pole star connected induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 9
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 9");
7
8 //VARIABLE INITIALIZATION
9 p=150*1000;                                //in Watts
10 v=3000;                                     //in Volts
11 f=50;                                       //in Hertz
12 P=6;                                         //number of poles
13 ratio=3.6;                                   //ratio of stator
14                                                 turn to rotor turn
14 r2=0.1;                                      //rotor resistance
14                                         in Ohms
15 L=3.61/1000;                                 //leakage
15                                         inductance per phase in Henry
16
17 //SOLUTION
18
19 //solution (a)
20 X2=2*pi*f*L;
21 E1=v/sqrt(3);
22 E2=E1*(1/ratio);

```

```

23 z1=sqrt((r2^2)+(X2^2));
24 I2=E2/z1;                                // rotor current
25 I_s=I2/ratio;                            // stator current
26 N_s=(120*f)/P;
27 w=(2*pi*N_s)/60;
28 T_s1=(3*E2^2*r2)/(w*z1^2);
29 disp(sprintf("(a) The starting current is %f A and
    torque is %f N-m",I_s,T_s1));
30
31 //solution (b)
32 I_s1=30;
33 I_r=ratio*I_s1;
34 r=sqrt(((E2/I_r)^2)-(X2^2));
35 r_ext=r-r2;
36 z2=sqrt((r_ext^2)+(X2^2));
37 T_s2=(3*E2^2*r)/(w*z2^2);
38 disp(sprintf("(b) The external resistance is %f
    and torque is %f N-m",r_ext,T_s2));
39
40 //There answers are different due to precision of
    floating point numbers
41
42 //END

```

---

### Scilab code Exa 10.10 6 pole 60 Hz induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 10
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 10");
7
8 //VARIABLE INITIALIZATION
9 P=6;                                //number of poles

```

```

10 f=60;                                //in Hertz
11 p=48;                                 //stator input in
   Watts
12 N_r=1140;                            //in rpm
13 cu_loss=1.4;                          //stator copper loss
   in Watts
14 cr_loss=1.6;                          //stator core loss
   in Watts
15 me_loss=1;                            //rotor mechanical
   loss in Watts
16
17 //SOLUTION
18 N_s=(120*f)/P;
19 s=(N_s-N_r)/N_s;
20 p_g=p-(cu_loss+cr_loss);             //rotor input
21 p_m=p_g*(1-s);                      //output mechanical
   power
22 p_sh=p_m-me_loss;                   //shaft power
23 eff=p_sh/p;
24 disp(sprintf("The motor efficiency is %f %%", eff
   *100));
25
26 //END

```

---

### Scilab code Exa 10.11 4 pole induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 11
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 11");
7
8 //VARIABLE INITIALIZATION
9 P1=4;                                //number of poles

```

```

10 s=5/100;                                // slip
11 f=60;                                     // frequency of
    synchronous generator in Hertz
12
13 //SOLUTION
14
15 //solution (a)
16 N_s=(120*f)/P1;                          // synchronous speed of
    generator in rpm with four poles
17 N_r=N_s*(1-s);                           // rotor or motor speed
    in rpm
18 N_r=round(N_r);                         //to round off the
    value
19 disp(sprintf("(a) The speed of the motor is %d rpm", N_r));
20
21 //solution (b)
22 P2=6;
23 N_s=(120*f)/P2;                          // synchronous speed of
    generator in rpm with six poles
24 disp(sprintf("(b) The speed of the generator is %d
    rpm", N_s));
25
26 //END

```

---

### Scilab code Exa 10.12 3 phase 440 V distribution

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 12
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 12");
7
8 //VARIABLE INITIALIZATION

```

```

9 v=440;                                //line voltage in
   Volts
10 I=1200;                               //line current in
   Amperes
11 eff=0.85;                            //full load
   efficiency
12 pow_fact=0.8;                         //full load power
   factor
13
14 //SOLUTION
15
16 //solution (a)
17 I_f11=I/5;                           //starting current
   at rated voltage is 5 times the rated full-load
   current
18 p1=sqrt(3)*v*I_f11*pow_fact*eff;
19 disp(sprintf("(a) The maximum permissible kW rating
   when the motor when it starts at full voltage is
   %f kW",p1/1000));
20
21 //solution (b)
22 x=0.8;                                //voltage is
   stepped down to 80%
23 I_f12=I/((x^2)*5);
24 p2=sqrt(3)*v*I_f12*pow_fact*eff;
25 disp(sprintf("(b) The maximum permissible kW rating
   when the motor is used with an auto-transformer
   is %f kW",p2/1000));
26
27 //solution (c)
28 I_f13=I/((0.578^2)*5);               //since a star-
   delta is equivalent to an auto-transformer
   starter with 57.8% tapping
29 p3=sqrt(3)*v*I_f13*pow_fact*eff;
30 disp(sprintf("(c) The maximum permissible kW rating
   when the motor is used with star-delta starter is
   %f kW",p3/1000));
31

```

```
32 //The answers are slightly different due to  
    precision of floating point numbers  
33  
34 //END
```

---

### Scilab code Exa 10.13 3 phase 50 Hz induction motor

```
1 //CHAPTER 10— THREE-PHASE INDUCTION MACHINES  
2 //Example 13  
3  
4 clc;  
5 disp("CHAPTER 10");  
6 disp("EXAMPLE 13");  
7  
8 //VARIABLE INITIALIZATION  
9 f=50;                                //frequency in Hertz  
10 N_r=1440;                             //full-load rotor  
    speed in rpm  
11  
12 //SOLUTION  
13  
14 //solution (a)  
15 function N=speed(pole);           //function 'speed()' ,  
    calculates the synchronous speed in rpm  
16 N=(120*f)/pole;  
17 endfunction;  
18  
19 pole=2;  
20 N=speed(pole);  
21 if(N>N_r & N<2000)  
22 P=pole;  
23 N_s1=N;  
24 disp(sprintf("(a) The number of poles is %d",P));  
25 end;  
26 pole=4;
```

```

27 N=speed(pole);
28 if(N>N_r & N<2000)
29 P=pole;
30 N_s1=N;
31 disp(sprintf("(a) The number of poles is %d",P));
32 end;
33 pole=6;
34 N=speed(pole);
35 if(N>N_r & N<2000)
36 P=pole;
37 N_s1=N;
38 disp(sprintf("(a) The number of poles is %d",P));
39 end;
40
41 //solution (b)
42 s=(N_s1-N_r)/N_s1;
43 f_r=s*f;
44 disp(sprintf("(b) The slip is %f %% and rotor
frequency is %d Hz",s*100,f_r));
45
46 //solution (c)
47 w1=(2*pi*N_s1)/60;
48 disp(sprintf("(c(i)) The speed of stator field w.r.t
.stator structure is %f rad/s",w1)); //Answer
given in the book is wrong
49 N_s2=N_s1-N_r;
50 w2=(2*pi*N_s2)/60;
51 disp(sprintf("(c(ii)) The speed of stator field w.r.
t. rotor structure is %f rad/s",w2));
52
53 //solution (d)
54 factor=(2*pi)/60; //converting rpm to
radian/second
55 N_r1=(120*f_r)/P;
56 disp(sprintf("(d(i)) The speed of rotor field w.r.t.
rotor structure is %f rad/s",N_r1*factor));
57 N_r2=N_r+N_r1;
58 disp(sprintf("(d(ii)) The speed of rotor field w.r.t

```

```

        . stator structure is %f rad/s”,N_r2*factor));
59 N_r3=N_s1-N_r2;
60 disp(sprintf("(d(iii)) The speed of rotor field w.r.
t. stator structure is %d rad/s”,N_r3));
61
62 //END

```

---

### Scilab code Exa 10.14 10 kW 400 V delta connected induction motor

```

1 //CHAPTER 10– THREE-PHASE INDUCTION MACHINES
2 //Example 14
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 14");
7
8 //VARIABLE INITIALIZATION
9 p=10*1000;                                //in Watts
10 I_nl=8;                                     //no load line
     current in Amperes
11 p_ni=660;                                    //input power at no
     load in Watts
12 I_f1=18;                                     //full load current
     in Amperes
13 p_fi=11.20*1000;                            //input power at
     full load in Watts
14 r=1.2;                                       //stator resistance
     per phase in Ohms
15 loss=420;                                     //friction and
     winding loss in Watts
16
17 //SOLUTION
18
19 //solution (a)
20 I1=I_nl/sqrt(3);                            //phase current=(

```

```

    line current)/sqrt(3) for delta connection
21 i_sq_r1=(I1^2)*r*3;                                //stator ((I^2)*R)
    loss at no load; since resistance is given in per
    phase, 3 needs to be multiplied for 3-phase
22 s_loss=(p_ni-loss)-(i_sq_r1);
23 disp(sprintf("(a) The stator core loss is %f W" ,
    s_loss));
24
25 //solution (b)
26 I2=I_f1/sqrt(3);
27 i_sq_r2=(I2^2)*r*3;
28 p_g=p_fi-s_loss-i_sq_r2;                          //air-gap power at
    full load
29 r_loss=p_g-p;
30 disp(sprintf("(b) The total rotor loss at full load
    is %f W" ,r_loss));
31
32 //solution (c)
33 o_loss=r_loss-loss;
34 disp(sprintf("(c) The total rotor ohmic loss at full
    load is %f W" ,o_loss));
35
36 //solution (d)
37 s_f1=o_loss/p_g;                                  //full load slip
38 N_s=1500;
39 N_r=N_s*(1-s_f1);
40 disp(sprintf("(d) The full load speed is %f rpm" ,N_r
    ));
41
42 //solution (e)
43 w=(2*pi*N_s)/60;
44 T_e=p_g/w;
45 disp(sprintf("(e) The internal torque is %f N-m" ,T_e
    ));
46 T_sh=p/(w*(1-s));
47 disp(sprintf("      The shaft torque is %f N-m" ,T_sh))
    ;
48 eff=p/p_fi;

```

```

49 disp(sprintf("      The motor efficiency is %f %%",eff
   *100));
50
51 //The answers may be slightly different due to
   precision of floating point numbers
52
53 //END

```

---

### Scilab code Exa 10.15 4 pole 3 phase SRIM

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 15
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 15");
7
8 //VARIABLE INITIALIZATION
9 P=4;                                //number of poles
10 f_s=50;                             //in Hertz
11 f_l=20;                            //in Hertz
12
13 //SOLUTION
14
15 // solution (a)
16 N1=(120*f_s)/P;                     //speed of rotor
   field w.r.t. stator structure
17 N2=(120*f_l)/P;                     //speed of rotor
   field w.r.t. rotor structure
18 N_r1=N1-N2;
19 N_r2=N1+N2;
20 disp("(a) The prime mover should drive the
   rotor at two speeds-");
21 disp(sprintf("At %d rpm in the direction of stator
   field",N_r1));

```

```

22 disp(sprintf("At %d rpm against the direction of
    stator field",N_r2));
23
24 //solution (b)
25 s1=(N1-N_r1)/N1;
26 s2=(N1-N_r2)/N1;
27 ratio=s1/s2;                                // all other
    parameters in the expressions of the two voltages
    are equal
28 disp(sprintf("(b) The ratio of the two voltages at
    the two speeds is %d",ratio));
29
30 //solution (c)
31 disp("(c) The poles sequence of -3    rotor voltage
    do not remain the same");
32
33 //END

```

---

### Scilab code Exa 10.16 3 phase induction motor

```

1 //CHAPTER 10- THREE-PHASE INDUCTION MACHINES
2 //Example 16
3
4 clc;
5 disp("CHAPTER 10");
6 disp("EXAMPLE 16");
7
8 //VARIABLE INITIALIZATION
9 ratio1=1.5;                                // ratio of starting
    torque (T_est) and full load torque (T_efl)
10 ratio2=2.5;                                // ratio of maximum
    torque (T_em) and T_efl
11
12 //SOLUTION
13

```

```

14 // solution (a) (taking the ratio of T_est and T_em)
15 s=1; //at starting slip is
      equal to 1
16
17 //directly solving the quadratic equation (a,b and c
      are the coefficients of the quadratic equation)
18 a=1;
19 b=-3.333;
20 c=1;
21 D=(b)^2-(4*a*c); //discriminant
22 sm1=(-b+sqrt(D))/(2*a);
23 sm2=(-b-sqrt(D))/(2*a);
24 if(sm1<=0 & sm2<=0) then
25 disp("The value of the slip at maximum torque (
      maximum slip) is not valid");
26 else if(sm1>0 & sm1<1)
27 disp(sprintf("The slip at maximum torque (maximum
      slip) is %f",sm1)); //slip is a unitless
      quantity
28 else if(sm2>0 & sm2<1)
29 disp(sprintf("The slip at maximum torque (maximum
      slip) is %f",sm2));
30 end;
31
32 //solution (b) (taking the ratio of T_efl and T_em)
33 //directly solving the quadratic equation
34 a=1;
35 b=-1.665;
36 c=0.111;
37 D=(b)^2-(4*a*c);
38 ans1=(-b+sqrt(D))/(2*a);
39 ans2=(-b-sqrt(D))/(2*a);
40 if(ans1>0 & ans1<1)
41 disp(sprintf("The full load slip is %f",ans1));
42 sfl=ans1;
43 else if(ans2>0 & ans2<1)
44 disp(sprintf("The full load slip is %f",ans2));
45 sfl=ans2;

```

```
46 end;
47
48 //solution (c)
49 I=sqrt(ratio1/sf1);
50 disp(sprintf("The rotor current at the starting in
      terms of full load current is %f A",I));
51
52 //END
```

---

# Chapter 11

## Single Phase Induction Motor

Scilab code Exa 11.1 Shaft torque

```
1 //CHAPTER 11- SINGLE PHASE INDUCTION MOTOR
2 //Examle 1
3
4 clc;
5 disp("CHAPTER 11");
6 disp("EXAMPLE 1");
7
8 //VARIABLE INITIALIZATION
9 P=6;                                //number of poles
10 f=50;                               //frequency in Hz
11 p_fd=160;                            //gross power absorbed by
   forward field in Watts
12 p_bd=20;                            //gross power absorbed by
   backward field in Watts
13 N_r=950;                            //rotor speed in rpm
14 loss=75;                             //no load frictional loss
   in Watts
15
16 //SOLUTION
17 P_g=p_fd-p_bd;                      //air-gap power in Watts
18 N_s=(120*f)/P;                      //synchronous speed in rpm
```

```

19 S=(N_s-N_r)/N_s;           // slip
20 P_m=P_g*(1-S);           // mechanical power
   developed in Watts
21 P_o=P_m-loss;            // output or shaft power in
   Watts
22 w=(2*pi*N_r)/60;
23 T=P_o/w;                 // shaft torque in Newton-
   meters
24 disp(sprintf("The shaft torque is %f N-m",T));
25
26 //END

```

---

**Scilab code Exa 11.2** Slip and resistance in forward and backward direction

```

1 //CHAPTER 11- SINGLE PHASE INDUCTION MOTOR
2 //Example 2
3
4 clc;
5 disp("CHAPTER 11");
6 disp("EXAMPLE 2");
7
8 //VARIABLE INITIALIZATION
9 P=4;                      //number of poles
10 f=60;                     //frequency in Hz
11 N_r=1710;                  //rotor speed in rpm
12 r2=12.5;                  //rotor resistance at standstill
   in Ohms
13
14 //SOLUTION
15
16 N_s=(120*f)/P;           //synchronous speed in rpm
17
18 //solution (a)
19 disp("Solution (a)");

```

```

20 S_f=(N_s-N_r)/N_s;
21 disp(sprintf("The per unit slip in the direction of
    rotation is %f pu",S_f));
22 r_f=0.5*(r2/S_f);
23 disp(sprintf("The effective forward rotor resistance
    is %f      ",r_f));
24
25 //solution (b)
26 disp("Solution (b)");
27 S_b=(N_s+N_r)/N_s;
28 disp(sprintf("The per unit slip in the opposite
    direction is %f pu",S_b));
29 r_b=0.5*(r2/S_b);
30 disp(sprintf("The effective backward rotor
    resistance is %f      ",r_b));
31
32 //END

```

---