

Scilab Textbook Companion for
Electrical And Electronic Principles And
Technology
by J. Bird¹

Created by
Sufiyan Siddique
BE (pursuing)
Electronics Engineering
Mumbai University
College Teacher
Prof Chaya Ravindra
Cross-Checked by
Lavitha Pereira

May 26, 2016

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electrical And Electronic Principles And Technology

Author: J. Bird

Publisher: Elsevier, U.K.

Edition: 3

Year: 2007

ISBN: 9780750685566

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Units associated with basic electrical quantities	6
2 An introduction to electric circuits	10
3 Resistance variation	19
4 Batteries and alternative sources of energy	25
5 Series and parallel networks	28
6 Capacitors and capacitance	38
7 Magnetic circuits	48
8 Electromagnetism	56
9 Electromagnetic induction	59
10 Electrical measuring instruments and measurements	69
12 Transistors	82
13 DC circuit theory	84
14 Alternating voltages and currents	105
15 Single phase series AC circuits	112

16 Single phase parallel AC circuits	131
17 Filter networks	141
18 DC transients	146
19 Operational amplifiers	161
20 Three phase systems	166
21 Transformers	176
22 DC machines	192
23 Three phase induction motors	206

List of Scilab Codes

Exa 1.1	Example 1	6
Exa 1.2	Example 2	6
Exa 1.3	Example 3	7
Exa 1.4	Example 4	7
Exa 1.5	Example 5	7
Exa 1.6	Example 6	8
Exa 1.7	Example 7	8
Exa 1.8	Example 8	9
Exa 2.1	Example 1	10
Exa 2.2	Example 2	10
Exa 2.3	Example 3	11
Exa 2.4	Example 4	11
Exa 2.5	Example 5	11
Exa 2.6	Example 6	12
Exa 2.7	Example 7	12
Exa 2.8	Example 8	13
Exa 2.9	Example 9	13
Exa 2.10	Example 10	14
Exa 2.11	Example 11	14
Exa 2.12	Example 12	14
Exa 2.13	Example 13	15
Exa 2.14	Example 14	15
Exa 2.15	Example 15	16
Exa 2.16	Example 16	16
Exa 2.18	Example 18	16
Exa 2.19	Example 19	17
Exa 2.20	Example 20	18
Exa 3.1	Example 1	19

Exa 3.2	Example 2	20
Exa 3.3	Example 3	20
Exa 3.4	Example 4	21
Exa 3.5	Example 5	21
Exa 3.6	Example 6	21
Exa 3.7	Example 7	22
Exa 3.8	Example 8	22
Exa 3.9	Example 9	23
Exa 3.10	Example 10	23
Exa 3.11	Example 11	23
Exa 3.12	Example 12	24
Exa 3.13	Example 13	24
Exa 4.1	Example 1	25
Exa 4.2	Example 2	26
Exa 4.3	Example 3	26
Exa 4.4	Example 4	27
Exa 5.1	Example 1	28
Exa 5.2	Example 2	29
Exa 5.3	Example 3	29
Exa 5.4	Example 4	30
Exa 5.5	Example 5	30
Exa 5.6	Example 6	31
Exa 5.7	Example 7	32
Exa 5.8	Example 8	32
Exa 5.10	Example 10	33
Exa 5.11	Example 11	33
Exa 5.12	Example 12	34
Exa 5.13	Example 13	35
Exa 5.14	Example 14	35
Exa 5.15	Example 15	36
Exa 5.16	Example 16	37
Exa 6.1	Example 1	38
Exa 6.2	Example 2	38
Exa 6.3	Example 3	39
Exa 6.4	Example 4	39
Exa 6.5	Example 5	40
Exa 6.6	Example 6	40
Exa 6.7	Example 7	41

Exa 6.8	Example 8	41
Exa 6.9	Example 9	42
Exa 6.10	Example 10	42
Exa 6.11	Example 11	43
Exa 6.12	Example 12	43
Exa 6.13	Example 13	44
Exa 6.15	Example 15	45
Exa 6.16	Example 16	46
Exa 6.17	Example 17	46
Exa 6.18	Example 18	47
Exa 7.1	Example 1	48
Exa 7.2	Example 2	48
Exa 7.3	Example 3	49
Exa 7.4	Example 4	49
Exa 7.5	Example 5	49
Exa 7.6	Example 6	50
Exa 7.7	Example 7	51
Exa 7.8	Example 8	51
Exa 7.10	Example 10	52
Exa 7.11	Example 11	52
Exa 7.12	Example 12	53
Exa 7.13	Example 13	54
Exa 7.15	Example 15	55
Exa 8.2	Example 2	56
Exa 8.3	Example 3	56
Exa 8.4	Example 4	57
Exa 8.6	Example 6	58
Exa 8.7	Example 7	58
Exa 9.1	Example 1	59
Exa 9.2	Example 2	59
Exa 9.3	Example 3	60
Exa 9.4	Example 4	61
Exa 9.6	Example 6	61
Exa 9.7	Example 7	62
Exa 9.8	Example 8	62
Exa 9.9	Example 9	63
Exa 9.10	Example 10	63
Exa 9.11	Example 11	63

Exa 9.12	Example 12	64
Exa 9.13	Example 13	64
Exa 9.14	Example 14	64
Exa 9.15	Example 15	65
Exa 9.16	Example 16	65
Exa 9.17	Example 17	66
Exa 9.18	Example 18	67
Exa 9.19	Example 19	67
Exa 9.20	Example 20	67
Exa 9.21	Example 21	68
Exa 10.1	Example 1	69
Exa 10.2	Example 2	69
Exa 10.3	Example 3	70
Exa 10.4	Example 4	71
Exa 10.5	Example 5	72
Exa 10.6	Example 6	72
Exa 10.7	Example 7	73
Exa 10.8	Example 8	73
Exa 10.9	Example 9	74
Exa 10.10	Example 10	74
Exa 10.12	Example 12	75
Exa 10.13	Example 13	76
Exa 10.14	Example 14	76
Exa 10.15	Example 15	77
Exa 10.16	Example 16	77
Exa 10.17	Example 17	77
Exa 10.18	Example 18	78
Exa 10.19	Example 19	78
Exa 10.20	Example 20	78
Exa 10.21	Example 21	79
Exa 10.22	Example 22	79
Exa 10.23	Example 23	80
Exa 10.24	Example 24	80
Exa 12.2	Example 2	82
Exa 12.6	Example 6	82
Exa 12.9	Example 9	83
Exa 13.1	Example 1	84
Exa 13.2	Example 2	85

Exa 13.3	Example 3	85
Exa 13.4	Example 4	86
Exa 13.5	Example 5	87
Exa 13.6	Example 6	88
Exa 13.7	Example 7	90
Exa 13.8	Example 8	91
Exa 13.9	Example 9	91
Exa 13.10	Example 10	92
Exa 13.13	Example 13	93
Exa 13.14	Example 14	94
Exa 13.15	Example 15	95
Exa 13.16	Example 16	96
Exa 13.17	Example 17	96
Exa 13.19	Example 19	97
Exa 13.20	Example 20	98
Exa 13.21	Example 21	99
Exa 13.22	Example 22	102
Exa 13.23	Example 23	102
Exa 13.24	Example 24	103
Exa 14.1	Example 1	105
Exa 14.2	Example 2	105
Exa 14.3	Example 3	106
Exa 14.4	Example 4	106
Exa 14.6	Example 6	107
Exa 14.7	Example 7	108
Exa 14.8	Example 8	108
Exa 14.9	Example 9	108
Exa 14.10	Example 10	109
Exa 14.11	Example 11	110
Exa 14.12	Example 12	110
Exa 15.1	Example 1	112
Exa 15.2	Example 2	112
Exa 15.3	Example 3	113
Exa 15.4	Example 4	114
Exa 15.5	Example 5	114
Exa 15.6	Example 6	114
Exa 15.7	Example 7	115
Exa 15.8	Example 8	115

Exa 15.9	Example 9	116
Exa 15.10	Example 10	117
Exa 15.11	Example 11	117
Exa 15.12	Example 12	118
Exa 15.13	Example 13	119
Exa 15.14	Example 14	119
Exa 15.15	Example 15	120
Exa 15.16	Example 16	121
Exa 15.17	Example 17	122
Exa 15.18	Example 18	123
Exa 15.19	Example 19	124
Exa 15.20	Example 20	125
Exa 15.21	Example 21	125
Exa 15.22	Example 22	126
Exa 15.23	Example 23	126
Exa 15.24	Example 24	127
Exa 15.25	Example 25	127
Exa 15.26	Example 26	128
Exa 15.27	Example 27	128
Exa 15.28	Example 28	128
Exa 15.29	Example 29	129
Exa 15.30	Example 30	130
Exa 16.1	Example 1	131
Exa 16.2	Example 2	132
Exa 16.3	Example 3	133
Exa 16.4	Example 4	133
Exa 16.5	Example 5	134
Exa 16.6	Example 6	135
Exa 16.7	Example 7	136
Exa 16.8	Example 8	137
Exa 16.9	Example 9	138
Exa 16.10	Example 10	138
Exa 16.11	Example 11	139
Exa 16.13	Example 13	139
Exa 17.1	Example 1	141
Exa 17.2	Example 2	141
Exa 17.3	Example 3	142
Exa 17.4	Example 4	142

Exa 17.5	Example 5	143
Exa 17.6	Example 6	144
Exa 17.7	Example 7	144
Exa 18.1	Example 1	146
Exa 18.2	Example 2	148
Exa 18.3	Example 3	149
Exa 18.4	Example 4	150
Exa 18.5	Example 5	151
Exa 18.6	Example 6	152
Exa 18.7	Example 7	153
Exa 18.8	Example 8	154
Exa 18.9	Example 9	155
Exa 18.10	Example 10	156
Exa 18.11	Example 11	157
Exa 18.12	Example 12	158
Exa 18.13	Example 13	159
Exa 19.1	Example 1	161
Exa 19.2	Example 2	161
Exa 19.3	Example 3	162
Exa 19.4	Example 4	162
Exa 19.5	Example 5	162
Exa 19.6	Example 6	163
Exa 19.7	Example 7	163
Exa 19.8	Example 8	164
Exa 19.10	Example 10	164
Exa 19.11	Example 11	165
Exa 20.1	Example 1	166
Exa 20.2	Example 2	166
Exa 20.4	Example 4	167
Exa 20.5	Example 5	168
Exa 20.6	Example 6	168
Exa 20.7	Example 7	169
Exa 20.8	Example 8	169
Exa 20.9	Example 9	170
Exa 20.11	Example 11	170
Exa 20.13	Example 13	171
Exa 20.14	Example 14	172
Exa 20.15	Example 15	172

Exa 20.16	Example 16	173
Exa 20.17	Example 17	173
Exa 20.18	Example 18	174
Exa 21.1	Example 1	176
Exa 21.2	Example 2	176
Exa 21.3	Example 3	177
Exa 21.4	Example 4	177
Exa 21.5	Example 5	177
Exa 21.6	Example 6	178
Exa 21.7	Example 7	178
Exa 21.9	Example 9	179
Exa 21.10	Example 10	179
Exa 21.11	Example 11	180
Exa 21.12	Example 12	180
Exa 21.13	Example 13	181
Exa 21.14	Example 14	182
Exa 21.15	Example 15	183
Exa 21.16	Example 16	183
Exa 21.17	Example 17	183
Exa 21.18	Example 18	184
Exa 21.19	Example 19	184
Exa 21.20	Example 20	186
Exa 21.21	Example 21	186
Exa 21.22	Example 22	186
Exa 21.23	Example 23	187
Exa 21.24	Example 24	187
Exa 21.25	Example 25	188
Exa 21.26	Example 26	188
Exa 21.27	Example 27	189
Exa 21.28	Example 28	190
Exa 21.29	Example 29	190
Exa 22.1	Example 1	192
Exa 22.2	Example 2	192
Exa 22.3	Example 3	193
Exa 22.4	Example 4	193
Exa 22.6	Example 6	194
Exa 22.7	Example 7	194
Exa 22.8	Example 8	194

Exa 22.9	Example 9	195
Exa 22.10	Example 10	196
Exa 22.11	Example 11	196
Exa 22.12	Example 12	197
Exa 22.13	Example 13	197
Exa 22.14	Example 14	198
Exa 22.15	Example 15	198
Exa 22.16	Example 16	198
Exa 22.17	Example 17	199
Exa 22.18	Example 18	200
Exa 22.19	Example 19	200
Exa 22.20	Example 20	200
Exa 22.21	Example 21	201
Exa 22.23	Example 23	201
Exa 22.24	Example 24	202
Exa 22.25	Example 25	202
Exa 22.26	Example 26	203
Exa 22.27	Example 27	203
Exa 22.28	Example 28	204
Exa 22.29	Example 29	204
Exa 22.30	Example 30	205
Exa 23.1	Example 1	206
Exa 23.2	Example 2	206
Exa 23.3	Example 3	207
Exa 23.4	Example 4	207
Exa 23.5	Example 5	207
Exa 23.6	Example 6	208
Exa 23.7	Example 7	208
Exa 23.8	Example 8	209
Exa 23.9	Example 9	210
Exa 23.10	Example 10	210
Exa 23.11	Example 11	212
Exa 23.12	Example 12	213
Exa 23.13	Example 13	213

List of Figures

13.1 Example 22	101
18.1 Example 1	147
18.2 Example 2	148
18.3 Example 8	154
18.4 Example 11	157

Chapter 1

Units associated with basic electrical quantities

Scilab code Exa 1.1 Example 1

```
1 //Chapter 1, Problem 1
2 clc;
3 I=5; //current
4 T=2*60; //time taken to flow current
5 Q=I*T; //calculating quantity of
   electricity
6 printf("Quantity of electricity Q = %f C \n\n",Q);
```

Scilab code Exa 1.2 Example 2

```
1 //Chapter 1, Problem 2
2 clc;
3 M=5; //mass in kilogram
4 A=2; //acceleration in m/
   s2.
5 F=M*A; //calculating the
   force needed
```



```
6 printf("Force = %f N \n\n",F);           //
   displaying the result with unit
```

Scilab code Exa 1.3 Example 3

```
1 //Chapter 1, Problem 3
2 clc;
3 M=0.2;           //mass in Kg
4 g=9.81          // acceleration due to gravity
5 F=M*g;         //calculating the force
6 //Force acting downwards = weight
7 printf("Force acting downwards = %f N",F);
```

Scilab code Exa 1.4 Example 4

```
1 //Chapter 1, Problem 4
2 clc;
3 F=200;          //force in Newton
4 D=20;           //distance in metre
5 T=25;           //time in seconds
6 W=F*D;         //calculating work done in kJ
7 printf("Work done = %f kJ\n\n\n",W)
8 P=W/T;         //calculating Power in watt
9 printf("Average power utilized = %f W\n\n\n",P);
```

Scilab code Exa 1.5 Example 5

```
1 //Chapter 1, Problem 5
2 clc;
3 M=1000;         //mass in kg
```

```

4 H=10; //height in metre
5 T=20; //time in seconds
6 g=9.81; //acceleration due to
    gravity
7 F=M*g; //calculating force from
    newtons law of motion
8 W=F*H; //calculating work
9 printf("(a) Work done = %f kJ\n\n\n",W/1000);
10 P=W/T;
11 printf("(b) Power developed = %f kW",P/1000);

```

Scilab code Exa 1.6 Example 6

```

1 //Chapter 1, Problem 6
2 clc;
3 R1=10; //Resistance of R1 in ohms
4 R2=5; //Resistance of R2 in
    kilohms
5 R3=100*10^-3; //Resistance of R3 in ohms
6 G1=1/R1; //calculating conductance
7 G2=1/R2;
8 G3=1/R3;
9 printf("Conductance of a conductor of resistance 10
    ohms = %f S \n\n\n",G1);
10 printf("Conductance of a conductor of resistance 5 k
    .ohms = %f mS \n\n\n",G2);
11 printf("Conductance of a conductor of resistance 100
    miliohms = %f S \n\n\n",G3);

```

Scilab code Exa 1.7 Example 7

```

1 //Chapter 1, Problem 7
2 clc;

```

```

3 V=5; //source emf
4 I=3; //current in ampere
5 T=10*60; //time in seconds
6 E=V*I*T; //calculating energy
7 printf("Energy provided = %f kJ",E/1000);

```

Scilab code Exa 1.8 Example 8

```

1 //Chapter 1, Problem 8
2 clc;
3 E=1.8*10^6; //energy consumes by
   electric heater
4 T=30*60; //time in seconds
5 V=250; //supply voltage
6 P=E/T; //calculating power
   rating of the heater
7 printf("Power rating of heater = %f kW \n\n\n",P
   /1000);
8 I=P/V; //calculating
   current taken from the supply
9 printf("Current taken from supply = %f A \n\n\n",I);

```

Chapter 2

An introduction to electric circuits

Scilab code Exa 2.1 Example 1

```
1 //Chapter 2, Problem 1
2 clc;
3 Q=0.24; //Charge in coulombs
4 T=15*10^-3; //Time converted
   in seconds
5 I=Q/T; //Calculating
   current
6 printf("Current flows = %f A",I);
```

Scilab code Exa 2.2 Example 2

```
1 //Chapter 2, Problem 2
2 clc;
3 I=10; //Current flows
4 T=4*60; //Time converted in
   seconds
```

```

5 Q=I*T;                                // Calculating
   charge
6 printf("Electricity transfered = %f C",Q); //
   Displaying the result in coulombs

```

Scilab code Exa 2.3 Example 3

```

1 //Chapter 2, Problem 3
2 clc;
3 V=20;                                // Potential difference
4 I=0.8;                                // Current in ampere
5 R=V/I;                                // Calculating resistance using
   Ohm's law
6 printf("Resistance = %d ohms",R);

```

Scilab code Exa 2.4 Example 4

```

1 //Chapter 2, Problem 4
2 clc;
3 R=2*10^3;                             // Resistance in ohms
4 I=10*10^-3;                           // Current in ampere
5 V=R*I;                                 // Calculating
   voltage
6 printf("Potential difference = %d V",V);

```

Scilab code Exa 2.5 Example 5

```

1 //Chapter 2, Problem 5
2 clc;
3 V=12;                                 // voltage

```

```

4 I=50*10-3; //current
5 R=V/I; //calculating resistance
    using Ohms law
6 printf("Resistance of coil = %d ohms",R);

```

Scilab code Exa 2.6 Example 6

```

1 //Chapter 2, Problem 6
2 clc;
3 V1=100; //Battery voltage
4 I1=5*10-3; //Current of 5mA;
5 V2=25; //Voltage is now reduced
    to 25V
6 R=V1/I1; //Calculating resistance
    due to V1 using Ohms law
7 I2=V2/R; //Calculating current
    due to V2 using Ohms law
8 printf("Resistance of resistor = %d k.ohms\n\n\n",R
    /1000);
9 printf("Current when voltage is reduced to 25V = %f
    mA",I2*1000);

```

Scilab code Exa 2.7 Example 7

```

1 //Chapter 2, Problem 7
2 clc;
3 V=120; //Supply voltage
4 I1=50*10-3; //Current of 50mA
5 I2=200*10-6; //Current of 200uA
6 R1=V/I1; //Calculating
    resistance due to I1 using Ohms law
7 R2=V/I2; //Calculating
    resistance due to I1 using Ohms law

```

```

8 printf(" Resistance of coil draws 50mA current = %f
      ohms\n\n\n",R1);
9 printf(" Resistance of coil draws 100uA current = %f
      ohms\n\n\n",R2);

```

Scilab code Exa 2.8 Example 8

```

1 //Chapter 2, Problem 8, Figure 2.8
2 clc;
3 V1=20; //Voltage of resistor A
4 I1=20*10^-3; //Current of resistor A
5 V2=16; //Voltage of resistor B
6 I2=5*10^-3; //Current of resistor B
7 R1=V1/I1; //Calculating resistance
      of resistor A using Ohms law
8 R2=V2/I2; //Calculating resistance
      of resistor B using Ohms law
9 printf(" Resistance of resistor A = %d k.ohms\n\n\n",
      R1/1000);
10 printf(" Resistance of resistor B = %f k.ohms\n\n\n",
      R2/1000);

```

Scilab code Exa 2.9 Example 9

```

1 //Chapter 2, Problem 9
2 clc;
3 P=100; //power in watt
4 V=250; //voltage
5 I=P/V; //calculating current
6 R=V/I; //calculating resistance using
      Ohms law
7 printf(" (a) Current = %f A\n\n\n",I);
8 printf(" (b) Resistance = %d ohms",R);

```

Scilab code Exa 2.10 Example 10

```
1 //Chapter 2, Problem 10
2 clc;
3 I=4e-3;           //current in ampere
4 R=5e3;           //resistance
5 P=I^2*R;        //calculating power
6 printf("Power = %f W",P);
```

Scilab code Exa 2.11 Example 11

```
1 //Chapter 2, Problem 11
2 clc;
3 V=240;           //voltage
4 R=30;           //resistance
5 I=V/R;          //calculating current using Ohms
    law
6 P=I*V;          //calculating power
7 printf("Current = %d A\n\n",I);
8 printf("Power = %f kW",P/1000);
```

Scilab code Exa 2.12 Example 12

```
1 //Chapter 2, Problem 12
2 clc;
3 I=5;           //Current in ampere
4 R=100;        //Resistance in ohms
5 V=I*R;        //Calculating voltage using
    Ohms law
```



```

6 P=V*I;                               //Calculating power in
    watt
7 printf("Potential difference across winding = %d V\n
    \n\n",V);
8 printf("Power dissipated by coil = %d W",P);

```

Scilab code Exa 2.13 Example 13

```

1 //Chapter 2, Problem 13
2 clc;
3 V=240;                                //voltage
4 R=960;                                //resistance
5 I=V/R;                                //calculating current using Ohms
    law
6 P=V*I;                                //calculating power
7 printf("Power rating P = %d W",P);

```

Scilab code Exa 2.14 Example 14

```

1 //Chapter 2, Problem 14
2 clc;
3 V=12;                                  //voltage
4 R=40;                                  //resistance
5 t=2*60;                                //time period
6 I=V/R;                                  //calculating current using Ohms
    law
7 P=V*I;                                  //calculating power
8 E=P*t;                                  //calculating energy
9 printf("Current flowing in load = %f A\n\n",I);
10 printf("Power consumed = %f W\n\n",P);
11 printf("Energy dissipated = %f J",E);

```

Scilab code Exa 2.15 Example 15

```
1 //Chapter 2, Problem 15
2 clc;
3 V=15;           //e.m.f
4 I=2;           //current
5 t=6*60;        //time period
6 E=V*t*I;       //calculating energy
7 printf("Energy = %f kJ",E/1000);
```

Scilab code Exa 2.16 Example 16

```
1 //Chapter 2, Problem 16
2 clc;
3 V=240;         //supply voltage
4 I=13;         //current
5 t=30;         //time in hours
6 P=V*I;        //power
7 E=P*t;        //energy
8 printf("Energy used per week = %.1f kWh\n\n",E/1000)
;
9 printf("hence weekly cost of electricity = %.2f
euro", (E*12.5/1000)/100);
```

Scilab code Exa 2.18 Example 18

```
1 //Chapter 2, Problem 18
2 clc;
3 I=10;          //Curent in ampere
```

```

4 R=20; //Resistance in ohm
5 T=6; //Time in hours
6 unit=13; //Unit of cost of
    electricity
7 P=I^2*R; //Calculating power
    dissipated by electric fire
8 E=P*T; //Calculating Energy used
9 cost=E*unit; //Calculating cost of
    energy
10 cost=cost/100000;
11
12 printf("Power dissipated by element = %f kW\n\n",P
    /1000);
13 printf("Energy used in 6 hours = %f kWh\n\n",E
    /1000);
14 printf("Cost of energy = %fp",cost);

```

Scilab code Exa 2.19 Example 19

```

1 //Chapter 2, Problem 19
2 clc;
3 P1=3000; //power in watts
4 P2=150; //power in watts
5 t1=20; //time in hours
6 t2=30; //time in hours
7 n1=2; //no of fires
8 n2=6; //no of light
9 m=14; //cost per unit
10 E1=P1*t1;
11 w1=n1*E1;
12 E2=P2*t2;
13 w2=n2*E2;
14 T=w1+w2;
15 c=m*(T/1000);
16 printf("\nIf the cost of electricity is 14 p per

```

```

    unit\n")
17 printf("\n the weekly cost of electricity to the
    business = %f p",c);
18 printf("\n\t\t\t\t\t= %.2f euro",c/100);

```

Scilab code Exa 2.20 Example 20

```

1 //Chapter 2, Problem 20,
2 clc;
3 V=240; //Supply voltage
4 P1=1000; //Power rating
    of Electric toaster
5 P2=3000; //Power rating
    of Electric fire
6 //Calculating fuse current for electric toaster
7 I1=P1/V;
8 //Calculating fuse current for electric fire
9 I2=P2/V;
10 I1=I1+1;
11 I2=I2+1;
12 printf("(i) Current in fuse for Electric toaster =
    %d A\n\n\n",I1);
13 printf("(ii) Current in fuse for Electric fire = %d
    A\n\n\n",I2);

```

Chapter 3

Resistance variation

Scilab code Exa 3.1 Example 1

```
1 //Chapter 3, Problem 1
2 clc;
3 R=600; //Resistance of wire
4 L=5; //Length of wire in metre
5 L1=8; //Length of the same wire in
        metre
6 R2=420; //Resistance of the same
        wire
7 K=R/L; //Calculating
        proportionality constant
8 R1=K*L1; //Calculating resistance of
        an 8m length of same wire
9 L2=R2/K; //Calculating length of same
        wire when resistance is 420ohm
10 printf("The resistance of an 8m length wire= %f ohm\
        n\n\n",R1);
11 printf("Length of the same wire when the resistance
        is 420 ohm = %fm",L2);
```

Scilab code Exa 3.2 Example 2

```
1 //Chapter 3, Problem 2
2 clc;
3 A=2; //Cross-sectional area in
      milimetre square
4 R=300; //Resistance of wire
5 A1=5; //Cross-sectional area of
      same wire
6 R2=750; //Resistance of same wire
7 K=R*A; //Calculating
      proportionality constant
8 R1=K/A1; //Calculating resistance with
      cross-sectional area 5mm2
9 A2=K/R2; //Calculating cross-sectional
      area with resistance 750ohm
10 printf("(a) Resistance of wire = %f ohm\n\n",R1);
11 printf("(b) Cross-sectional area of a wire = %f mm^2
      ",A2);
```

Scilab code Exa 3.3 Example 3

```
1 //Chapter 3, Problem 3
2 clc;
3 R=0.16; //resistance of wire
4 l=8; //length of wire
5 a=3; //area of cross-section
6 //If the cross-sectional area is reduced to 1/3 of
      its original area then the length must be tripled
      to 3 8 ,
7 l1=3*l;
8 a1=a/3;
9 k=R*a/l; //calculating
      coefficient of proportionality
10 R1=k*(l1/a1); //calculating new
```

```
    resistance with reduced area of cross-section
11 printf("Resistance of wire = %f ohm",R1);
```

Scilab code Exa 3.4 Example 4

```
1 //Chapter 3, Problem 4
2 clc;
3 L=2000;           //length of wire
4 A=100*10^-6;     //area of cross section of
    wire
5 p=0.03*10^-6;   //resistivity
6 R=(p*L)/A;      //calculating resistance
7 printf("Resistance of wire = %f ohm",R);
```

Scilab code Exa 3.5 Example 5

```
1 //Chapter 3, Problem 5
2 clc;
3 l=40;           //length of wire
4 R=0.25;         //resistance of wire
5 p=0.02*10^-6;  //resistivity
6 a=p*l/R;       //calculating cross-
    sectional area of wire
7 printf("Cross-sectional area of wire = %f mm^2",a
    *10^6);
```

Scilab code Exa 3.6 Example 6

```
1 //Chapter 3, Problem 6
2 clc;
```

```

3 R=150;           //resistance of wire
4 l=1500;         //length of wire
5 a=0.17;         //area of cross-section
6 p=R*a/l;       //calculating resistivity
7 printf("Resistivity of the wire = %f micro-ohm metre
        ",p);

```

Scilab code Exa 3.7 Example 7

```

1 //Chapter 3, Problem 7
2 clc;
3 L=1200;         //Length of copper cable
        in meter
4 D=12*10^-3;    //Diameter of cable in
        meter
5 p=1.7*10^-8;   //Resistivity of cable
        in ohm.meter
6 r=D/2;         //Calculating radius
7 A=%pi*r^2;     //Calculating area
8 R=(p*L)/A;     //Calculating resistance
9 printf("Resistance of wire = %f ohm",R);

```

Scilab code Exa 3.8 Example 8

```

1 //Chapter 3, Problem 8
2 clc;
3 R0=100;         //resistance at 0 C
4 T=70;           //tempreture in C
5 a=0.0043;       //temperature
        coefficient of resistance at 0 C
6 Rt=R0*(1+(a*T)); //calculating resistance
        at 70 C
7 printf("Resistance at 70 C = %f ohm",Rt);

```

Scilab code Exa 3.9 Example 9

```
1 //Chapter 3, Problem 9
2 clc;
3 Rt=27;           //resistance at 35 C
4 a0=0.0038;      //temperature coefficient of
   resistance at 0 C
5 T=35;          //temperture
6 R0=Rt/(1+(a0*T)); //calculating resistance at 0
   C
7 printf("Resistance at 0 deg = %f ohm",R0);
```

Scilab code Exa 3.10 Example 10

```
1 //Chapter 3, Problem 10
2 clc;
3 R0=1000;        //resistance at 0 C
4 T=80;          //temperture in C
5 a=-0.0005;     //temperature
   coefficient of resistance at 0 C
6 Rt=R0*(1+(a*T)); //calculating resistance
   at 80 C
7 printf("Resistance at 80 C = %f ohm",Rt);
```

Scilab code Exa 3.11 Example 11

```
1 //Chapter 3, Problem 11
2 clc;
3 R0=10;          //resistance at 20 C
```

```

4 T=20; //temperture in C
5 T1=100; //temperture rises
6 a=0.004; //temperature coefficient
    of resistance at 0 C
7 Rt=R0*(1+(a*(T1-T))); //calculating
    resistance at 100 C
8 printf("Resistance at 100 C = %f ohm",Rt);

```

Scilab code Exa 3.12 Example 12

```

1 //Chapter 3, Problem 12
2 clc
3 t=18 //temperture in celsius
4 R1=200 //resistance in ohm
5 Rt=240 //resistance in ohm
6 tc=0.0039 //temperture coefficient of
    resistance
7 t1=((Rt-R1)/(R1*tc))+t
8 printf("Temperture = %.2f degree celsius",t1)

```

Scilab code Exa 3.13 Example 13

```

1 //Chapter 3, Problem 13
2 clc
3 t1=20 //temperture in celsius
4 t2=90 //temperture in celsius
5 R20=200 //resistance in ohm
6 a0=0.004 //coefficient of
    resistance
7 R90=(R20*(1+(a0*t2)))/(1+(a0*t1))
8 printf("Resistance of wire = %.2f ohm",R90)

```

Chapter 4

Batteries and alternative sources of energy

Scilab code Exa 4.1 Example 1

```
1 //Chapter 4, Problem 1
2 clc;
3 //There is eight cell with same emf and internal
  resistance
4 r=0.2;
5 emf=2.2;
6 //When connected in series
7 Temf=8*emf;
8 Tr=8*r;
9 //When connected in parallel
10 Tr1=(1/8)*r;
11 printf("Total emf in series = %f V\n\n\n",Temf);
12 printf("Total internal resistance in series = %f ohm
  \n\n\n",Tr);
13 printf("Total emf in parallel = %f V\n\n\n",emf);
14 printf("Total internal resistance in parallel = %f
  ohm\n\n\n",Tr1);
```

Scilab code Exa 4.2 Example 2

```
1 //Chapter 4, Problem 2
2 clc;
3 r=0.02; //Internal
   resistance in ohm
4 emf=2.0; //e.m.f
5 I1=5; // Current in
   ampere
6 I2=50;
7 V1=emf-(I1*r); //Calculating
   Voltage
8 V2=emf-(I2*r);
9 printf("Terminal p.d when 5A current = %f V\n\n",
   V1);
10 printf("Terminal p.d when 50A current = %f V\n\n",
   V2);
```

Scilab code Exa 4.3 Example 3

```
1 //Chapter 4, Problem 3
2 clc;
3 emf=25; //e.m.f
4 V=24; //Voltage
5 I=10; //Current in ampere
6 r=(emf-V)/I; //Calculating
   internal resistance in ohm
7 printf("Internal resistance of the battery = %f ohm"
   ,r);
```

Scilab code Exa 4.4 Example 4

```
1 //Chapter 4, Problem 4
2 clc;
3 emf=1.5;
4 r=0.2; //Internal resistance of
        1 cell
5 R=58; //Resistance of load in
        ohm
6 E=10*emf; //Total battery e.m.f
7 rt=10*r; //Total internal
        resistance in ohm
8 Rt=R+rt; //Total resistance in
        ohm
9 I=E/Rt; //Current flowing in the
        circuit
10 V=E-(I*rt); //P.d. at battery
        terminals
11 printf("Current flowing in the circuit = %f A\n\n",
        I);
12 printf("P.d. at battery terminals = %f V",V);
```

Chapter 5

Series and parallel networks

Scilab code Exa 5.1 Example 1

```
1 //Chapter 5, Problem 1, Figure 5.2
2 clc;
3 V1=5;

    //assigning the value to parameters
4 V2=2;
5 V3=6;
6 I=4;
7 V=V1+V2+V3;

    Calculating the Battery voltage //
8 printf(" Battery Voltage = %f V\n\n",V);
    // Displaying the value
9 R=V/I;

    Calculating the total resistance //
10 printf(" Total circuit resistance = %f ohm\n\n",R);
11 R1=V1/I;

    Calculating the invidual resistance //
12 R2=V2/I;
```

```
13 R3=V3/I;
14 printf(" Resistance R1 = %f ohm\n\n",R1);
15 printf(" Resistance R2 = %f ohm\n\n",R2);
16 printf(" Resistance R3 = %f ohm\n\n",R3);
```

Scilab code Exa 5.2 Example 2

```
1 // Problem 2, Figure 5.3
2 clc;
3 R=100; //Assigning the
        values to variable
4 V=25;
5 V1=10;
6 V2=4;
7 V3=V-V1-V2; //Calculating the
        voltage across Resistor R3
8 printf(" Potential difference across R3 = %f V\n\n\n",
        ,V3);
9 I=V/R; //Calculating the
        current
10 printf(" Current flowing through each resistor = %f A
        \n\n\n",I);
11 R2=V2/I; //Calculating the
        resistance of R2
12 printf(" Resistance R2 = %f ohm\n\n\n",R2);
```

Scilab code Exa 5.3 Example 3

```
1 //Chapter 5, Problem 3, Figure 5.4
2 clc;
3 R1=4;
4 R2=9;
5 R3=11;
```

```

6 V=12;
7 R=R1+R2+R3;                               //Calculating total
      resistance R
8 I=V/R;
9 printf("Current flowing through circuit = %f A\n\n\n",I);
10 V1=I*R2;
11 printf("Potential difference across R2 = %f V\n\n\n",
      V1);
12 P=(I^2)*R3;                               //
      Calculating power dissipated in the 11 ohm
      resistor
13 printf("Power dissipated in R3 = %f W\n\n\n",P);

```

Scilab code Exa 5.4 Example 4

```

1 //Chapter 5, Problem 4, Figure 5.6
2 clc;
3 V=(6/(6+4))*50;                             //
      Calculating the voltage by voltage divider rule
4 printf("Voltage = %f V\n\n\n",V);

```

Scilab code Exa 5.5 Example 5

```

1 //Chapter 5, Problem 5, Figure 5.8
2 clc;
3 V=24;
4 I=3;
5 R1=2;
6 T=50;
7 R=V/I;

      //Calculating total resistance

```



```

8 R2=R-R1;

   //Calculating the value of unknown resistance
9 printf("Value of unknown resistance = %f ohm\n\n\n",
   R2);
10 V1=I*R1;

   //Calculating the voltage across 2 ohm resistor
11 printf("Potential difference across 2 ohm resistor =
   %f V\n\n\n",V1);
12 E=(V*I)*T;
13 printf("Energy used = %f Wh",E);

```

Scilab code Exa 5.6 Example 6

```

1 //Chapter 5, Problem 6, Figure 5.13
2 clc;
3 //Potential difference across R1 is the same as the
   supply voltage V
4 R1=5;
5 R3=20;
6 I=11;
7 I1=8;
8 //Hence supply voltage is
9 V=R1*I1;
10 I3=V/R3;
11 //Reading on ammeter,
12 printf("Reading on ammeter = %f A\n\n\n",I3);
13 I2=I-I1-I3;
14 R2=V/I2;
15 //Current flowing through R2
16 printf("Resistance R2 = %f ohm\n\n\n",R2);

```

Scilab code Exa 5.7 Example 7

```
1 //Chapter 5, Problem 7, Figure 5.14
2 clc;
3 R1=3;
4 R2=6;
5 V=12;
6 //The total circuit resistance R is given by,
7 R=(R2*R1)/(R1+R2);
8 printf("Total circuit resistance = %f ohm\n\n\n",R);
9 //Current in the 3 ohm resistor is given by,
10 I1=V/R1;
11 printf("Current in the 3 ohm resistor = %f A\n\n\n",
    I1);
```

Scilab code Exa 5.8 Example 8

```
1 //Chapter 5, Problem 8, Figure 5.15
2 clc;
3 //Resistors R1, R2, R3 in ohm
4 R1=10;
5 R2=20;
6 R3=60;
7 //Current through R2 in ampere
8 I2=3;
9 //Calculating voltage and current
10 V=I2*R2;
11 I1=V/R1;
12 I3=V/R3;
13 I=I1+I2+I3;
14 printf("(a) Supply voltage = %f V\n\n\n",V);
15 printf("(b) Current I = %f A",I)
```

Scilab code Exa 5.10 Example 10

```
1 //Chapter 5, Problem 10, Figure 5.20
2 clc;
3 R1=1;
4 R2=2.2;
5 R3=3;
6 R4=6;
7 R5=18;
8 R6=4;
9 //R3, R4 and R5 are connected in parallel, their
   equivalent resistance R7 is
10 Z=(1/R3)+(1/R4)+(1/R5);
11 R7=1/Z;
12 //circuit is now equivalent to four resistors in
   series
13 R=R1+R2+R7+R6;
14 printf("Equivalent circuit resistance = %f ohm",R);
```

Scilab code Exa 5.11 Example 11

```
1 //Chapter 5, Problem 11, Figure 5.21
2 clc;
3 R1=10;
4 R2=20;
5 R3=30;
6 V=240;
7 //Resistor connected in series
8 Rs=R1+R2+R3;
9 Is=V/Rs;
10 //Resistor connected in parallel
11 Z=(1/R1)+(1/R2)+(1/R3);
12 Rp=1/Z;
13 Ip=V/Rp;
14 printf("Supply current when resistor in series = %f
```

```

    A\n\n\n",Is);
15 printf("Supply current when resistor in parallel =
    %f A\n\n\n",Ip);

```

Scilab code Exa 5.12 Example 12

```

1 //Chapter 5, Problem 12, Figure 5.24
2 clc;
3 R1=2.5;
4 R2=6;
5 R3=2;
6 R4=4;
7 V=200;
8 //Calculating equivalent resistance Rx of R2 and R3
   in parallel
9 Rx=(R2*R3)/(R2+R3);
10 //Calculating equivalent resistance RT of R1, Rx and
    R4 in series
11 Rt=R1+R4+Rx;
12 //Supply current
13 I=V/Rt;
14 //Calculating current through each resistor
15 I2=(R3/(R2+R3))*I;
16 I3=(R2/(R2+R3))*I;
17 //Calculating p.d across each resistor
18 V1=I*R1;
19 Vx=I*Rx;
20 V4=I*R4;
21 disp(" (a) ")
22 printf("Supply current = %f A\n\n\n",I);
23 disp(" (b) ")
24 printf("Current through R1 and R4 = %f A\n\n\n",I);
25 printf("Current through R2 = %f A\n\n\n",I2);
26 printf("Current through R3 = %f A\n\n\n",I3);
27 disp(" (c) ")

```

```

28 printf("p.d. across R1 = %f V\n\n",V1);
29 printf("p.d. across R2 and R3 = %f V\n\n",Vx);
30 printf("p.d. across R4 = %f V\n\n",V4);

```

Scilab code Exa 5.13 Example 13

```

1 //Chapter 5, Problem 13, Figure 5.26
2 clc;
3 R1=15; //in ohms
4 R2=10; //in ohms
5 R3=38; //in ohms
6 V=250; //in volts
7 Pt=2500; //in watts
8 I=Pt/V; //current in amperes
9 Rt=V/I;
10 r=(R1*R2)/(R1+R2); //equivalent resistance
    of R1 and R2
11 V1=I*r;
12 V2=V-V1;
13 i=V2/R3;
14 rx=V2/i;
15 I1=(R2/(R1+R2))*I;
16 I2=(R1/(R1+R2))*I;
17 printf("\n(a) Value of resistor Rx = %d ohm\n\n",rx)
18 printf("\n(b) Current flowing in each of the four
    resistors \n I1 = %d A\n I2 = %d A\n I3 = I4 = %d
    A",I1,I2,i);

```

Scilab code Exa 5.14 Example 14

```

1 //Chapter 5, Problem 14, Figure 5.27
2 clc;
3 //Resistance R1 R2 R3 R4 R5

```

```

4 R1=2;
5 R2=9;
6 R3=1.4;
7 R4=2;
8 R5=8;
9 V=17;
10 R45=(R4*R5)/(R4+R5);
11 R34=R3+R45;
12 R23=(R2*R34)/(R2+R34);
13 R=R1+R23;
14 //the circuit is gradually reduced in stages as
    shown in Fig. 5.28(a) (d).
15 I=V/R;
16 I1=(R2/(R2+R34))*I;
17 Ix=(R1/(R1+R5))*I1;
18 printf("From Fig. 5.27, \n\n");
19 printf("Current Ix = %f A", Ix);

```

Scilab code Exa 5.15 Example 15

```

1 //Chapter 5, Problem 15
2 clc;
3 r1=1000 //in ohms
4 r2=4000 //in ohms
5 r3=5000 //in ohms
6 r4=1500 //in ohms
7 V=24 //in volts
8 rt=((((r1+r2)*r3)/(r1+r2+r3))+r4 //equivalent
    resistance of r1,r2,r3
9 it=V/rt; //total circuit
    current
10 i1=(r3/(r1+r2+r3))*it; //current across
    top branch
11 v=i1*r2; //volt drop
    across r2

```

```

12 i2=((r1+r2)/(r1+r2+r3))*it;           //current across
    r3
13 p=it^2*r4;                           //power in wats
14 printf("(a) volt drop across 4 k resistor = %d V\n\n",v)
15 printf("(b) Current through the 5 k resistor = %d mA\n\n",i1*10e2)
16 printf("(c) Power in the 1.5 k resistor = %d mW\n\n",p*10e2)

```

Scilab code Exa 5.16 Example 16

```

1 //Chapter 5, Problem 16
2 clc;
3 R=150;                               //Combined resistance
4 R1=3*R;                               //Calculating individual
    resistance
5 printf("The resistance of one lamp = %f ohm",R1);

```

Chapter 6

Capacitors and capacitance

Scilab code Exa 6.1 Example 1

```
1 //Chapter 6, Problem 1
2 clc;
3 C=4*10^-6; //Capacitance in farad
4 Q=5*10^-3; //Charge in coulomb
5 C1=50*10^-12; //Capacitance in farad
6 V1=2000; //Voltage
7 V=Q/C;
8 Q1=C*V;
9 disp("(a)")
10 printf("Potential difference V = %f V\n\n\n",V);
11 disp("(b)")
12 printf("Charge Q = %f C",Q1);
```

Scilab code Exa 6.2 Example 2

```
1 //Chapter 6, Problem 2
2 clc;
3 I=4; //Current in ampere
```



```

4 t=3*10^-3; //time in seconds
5 C=20*10^-6; //Capacitance in farad
6 Q=I*t; //Calculating Charge
7 V=Q/C; //Calculating voltage
8 printf("p.d. between the plates = %f V",V);

```

Scilab code Exa 6.3 Example 3

```

1 //Chapter 6,Problem 3
2 clc;
3 C=5*10^-6; //Charge in coulomb
4 I=2*10^-3; //Current in ampere
5 V=800; //Voltage
6 Q=C*V; //Calculating charge
7 t=Q/I; //Calculating time of
   current 2mA to discharge
8 printf("The capacitor can provide an average
   discharge current of 2mA = %f sec",t);

```

Scilab code Exa 6.4 Example 4

```

1 //Chapter 6, Problem 4
2 clc;
3 l=20*10^-2;
4 b=40*10^-2;
5 Q=0.2*10^-6; //Charge
6 V=0.25*10^3; //Voltage
7 d=5*10^-3; //Distance between
   plates
8 A=l*b; //Calculating area of
   restangular plated
9 D=Q/A; //Calculating electric
   flux density

```

```

10 E=V/d;                                //Calculating electric
    field strength
11 printf(" Electric fulx density D = %f C/m2 \n\n\n",D)
    ;
12 printf(" Electric field strength E = %f V/m",E);

```

Scilab code Exa 6.5 Example 5

```

1 //Chapter 6, Problem 5
2 clc;
3 D=2*10^-6;                             //Flux density
4 e0=8.85*10^-12;                         //permittivity of
    free space
5 er=5;                                   //relative
    permittivity
6 E=D/(e0*er);                           //Calculating
    voltage gradient
7 disp(" Since D/E = 0 r , hence voltage gradient ,");
8 printf("\n\n\n Voltage gradient = %f V/m",E);

```

Scilab code Exa 6.6 Example 6

```

1 //Chapter 6, Problem 6
2 clc;
3 V=200;                                  //Voltage across plates
4 d=0.8*10^-3;                            //Distance between plates
5 E=V/d;                                  //Calculating electric field
    density
6 e=8.85*10^-12;
7 er=2.3;
8 D1=E*e;                                 //Calculating electric
    flux density for air

```

```

9 D2=E*e*er; //Calculating electric
flux density for polythene
10 printf("Electric field strength = %f kV/m\n\n",E
/1000);
11 disp("(a)");
12 printf("Electric flux density = %f C /m2\n\n",D1
*10^6);
13 disp("(b)");
14 printf("Electric flux density = %f C /m2",D2*10^6);

```

Scilab code Exa 6.7 Example 7

```

1 //Chapter 6, Problem 7
2 clc;
3 Q=1.2*10^-6; //Charge
4 A=4*10^-4; //Area of plates
5 d=0.1*10^-3; //Distance between
plates
6 e0=8.85*10^-12;
7 er=100;
8 C=(e0*er*A)/d; //Calculating
capacitance
9 V=Q/C; //Calculating
potential difference
10 disp("(a)");
11 printf("Capacitance = %f pF\n\n\n",C*10^12);
12 disp("(b)");
13 printf("p.d. between the plates = %f V",V);

```

Scilab code Exa 6.8 Example 8

```

1 //Chapter 6, Problem 8
2 clc

```

```

3 A=800e-4 //area of paper
4 C=4425e-12 //capacitance in pF
5 e0=8.85e-12 //permittivity of free
    space
6 er=2.5 //dielectric
7 d=(e0*er*A)/C //thickness of paper
8 printf("The thickness of the paper = %.1f mm",d
    *10^3)

```

Scilab code Exa 6.9 Example 9

```

1 //Chapter 6, Problem 9
2 clc;
3 n=19; //No of interleaved
    plates
4 n=n-1;
5 A=(75*10^-3)*(75*10^-3); //Calculating
    area of plates
6 er=5;
7 e0=8.85*10^-12;
8 d=0.2*10^-3; //Distance between
    plates
9 C=(e0*er*A*n)/d; //Calculating
    capacitance of the capacitor
10 printf("Capacitance of capacitor = %f nF",C*10^9);

```

Scilab code Exa 6.10 Example 10

```

1 //Chapter 6, Problem 10
2 clc;
3 C1=6*10^-6; //Capacitance of
    capacitor1

```

```

4 C2=4*10^-6; //Capacitance of
   capacitor2
5 C3=C1+C2; //Calculating
   equivalent capacitance in parallel
6 C4=(C1*C2)/(C1+C2); //Calculating
   equivalent capacitance in series
7 disp("(a)");
8 printf("In parallel , equivalent capacitance = %f uF"
   ,C3*10^6);
9 disp("(b)")
10 ;printf("In series , equivalent capacitance = %f uF" ,
   C4*10^6);

```

Scilab code Exa 6.11 Example 11

```

1 //Chapter 6, Problem 11
2 clc;
3 C=12*10^-6; //Equivalent capacitance
4 C1=30*10^-6; //Capacitance of
   capacitor1
5 C2=(C*C1)/(C1-C); //Calculating
   capacitance of capacitor2
6 printf("Unknown capacitance = %f uF" ,C2*10^6);

```

Scilab code Exa 6.12 Example 12

```

1 //Chapter 6, Problem 12
2 clc;
3 C1=1*10^-6; //Capacitance
4 C2=3*10^-6;
5 C3=5*10^-6;
6 C4=6*10^-6;

```

```

7 V=100; //Voltage across
    capacitor
8 C=C1+C2+C3+C4; //Calculating
    equivalent capacitance in series
9 Q=C*V; //Calculating total
    charge
10 Q1=C1*V; //Calculating charge
    on each capacitor
11 Q2=C2*V;
12 Q3=C3*V;
13 Q4=C4*V;
14 disp(" (a) ");
15 printf(" Equivalent capacitance C for parallel = %f
    uF\n\n\n",C*10^6);
16 disp(" (b) ");
17 printf(" Total charge = %f mC\n\n",Q*1000);
18 disp(" (2) ");
19 disp(" Charge on each capacitor");
20 printf(" Charge on capacitor1 = %f mC\n",Q1*1000);
21 printf(" Charge on capacitor2 = %f mC\n",Q2*1000);
22 printf(" Charge on capacitor3 = %f mC\n",Q3*1000);
23 printf(" Charge on capacitor4 = %f mC\n",Q4*1000);

```

Scilab code Exa 6.13 Example 13

```

1 //Chapter 6, Problem 13, Figure 6.8
2 clc;
3 C1=3*10^-6; //Capacitance on
    each capacitor
4 C2=6*10^-6;
5 C3=12*10^-6;
6 V=350; //Total voltage
    across capacitors
7 C=(1/C1)+(1/C2)+(1/C3); //Calculating
    equivalent capacitance

```

```

8 C=1/C;
9 Q=C*V;
10 V1=Q/C1; //Calculating voltage
    across each capacitor
11 V2=Q/C2;
12 V3=Q/C3;
13 disp(" (a)");
14 printf("Equivalent circuit capacitance = %f uF\n\n\n",
    C*10^6);
15 disp(" (b)");
16 printf("Charge on each capacitor = %f uF\n\n",Q
    *10^6);
17 disp(" (c)");
18 printf("Voltage across 3uF capacitor = %f V\n",V1);
19 printf("Voltage across 6uF capacitor = %f V\n",V2);
20 printf("Voltage across 12uF capacitor = %f V\n",V3);

```

Scilab code Exa 6.15 Example 15

```

1 //Chapter 6, Problem 15
2 clc;
3 V=1.25*10^3; //Voltage across
    terminals
4 C=0.2*10^-6; //Capacitance of
    capacitor
5 E=50*10^6; //Dielectric
    strength
6 e0=8.85*10^-12;
7 er=6;
8 d=(V/E); //
    Calculating distance between plates
9 A=(C*d)/(e0*er); //
    Calculating area of plates
10 disp(" (a)");
11 printf("Thickness of the mica needed = %f mm\n\n",d

```

```

    *10^3);
12 disp(" (b)");
13 printf("Area of a plate = %f cm2",A*10^4);

```

Scilab code Exa 6.16 Example 16

```

1 //Chapter 6, Problem 16
2 clc;
3 C=3*10^-6; //Capacitance
4 V=400; //Voltage across
    capacitor
5 t=10*10^-6; //Time in sec
6 W=(1/2)*C*V^2; //Calculating energy
    stored
7 P=W/t; //Calculating power
8 disp(" (a)");
9 printf("Energy stored in a 3 F capacitor = %f J\n\
    n",W);
10 disp(" (b)");
11 printf("Average power = %f kW",P/1000);

```

Scilab code Exa 6.17 Example 17

```

1 //Chapter 6, Problem 17
2 clc;
3 C=12*10^-6; //Capacitance
4 W=4; //Energy stored
5 V=sqrt((2*W)/C); //Calculating voltage to
    which the capacitor must be charged
6 printf("Potential difference = %f V",V);

```

Scilab code Exa 6.18 Example 18

```
1 //Chapter 6, Problem 18
2 clc;
3 Q=10*10^-3;           //Charge
4 W=1.2;               //Energy stored
5 V=(2*W)/Q;          //Calculating voltage
6 C=Q/V;              //Calculating capacitance
7 disp(" (a)");
8 printf(" Voltage = %f V\n\n",V);
9 disp(" (b)");
10 printf(" Capacitance = %f uF",C*10^6);
```

Chapter 7

Magnetic circuits

Scilab code Exa 7.1 Example 1

```
1 //Chapter 7, Problem 1
2 clc;
3 phi=150*10^-6;           //Flux
4 A=200*100*10^-6;       //Cross sectional area
5 B=phi/A;                //Calculating flux
                          //density
6 printf("Flux density = %f T",B);
```

Scilab code Exa 7.2 Example 2

```
1 //Chapter 1, Problem 2
2 clc;
3 phi=353*10^-3;          //Flux
4 B=1.8;                  //Flux density
5 A=phi/B;                //Area of pole face
6 r=sqrt(A/%pi);         //Radius
7 printf("The radius of the pole face = %f mm",r*1000)
  ;
```

Scilab code Exa 7.3 Example 3

```
1 //Chapter 7, Problem 3
2 clc;
3 H=8000; //Magnetic field
   strength
4 d=30*10^-2; //Diameter of
   coil
5 l=%pi*d; //Length
6 N=750; //No of turns
7 I=(H*l)/N; //Calculating
   current in the coil
8 printf("Current in the coil = %f A",I);
```

Scilab code Exa 7.4 Example 4

```
1 //Chapter 7, Problem 4
2 clc;
3 B=1.2; //Magnetic flux
   density
4 H=1250; //Magnetic field
   strength
5 uo=4*pi*10^-7; //permeability of
   free space
6 ur=B/(uo*H); //Calculating
   relative permeability
7 printf("Relative permeability = %f",ur);
```

Scilab code Exa 7.5 Example 5

```

1 //Chapter 7, Problem 5
2 clc;
3 B=0.25; //Magnetic flux
   density
4 u0=4*%pi*10^-7; //permeability of
   free space
5 l=12*10^-3; //Length
6 H=B/u0; //Calculating
   magnetic field strength
7 mmf=H*l; //Calculating
   magnetomotive force
8 printf("Magnetic field strength = %d A/m\n\n\n",H);
9 printf("m.m.f = %d A",mmf);

```

Scilab code Exa 7.6 Example 6

```

1 //Chapter 7, Problem 6
2 clc;
3 N=300; //No of turns
4 I=5; //Current in the coil
5 l=40*10^-2; //Length
6 A=4*10^-4; //Area of cross-
   sectional
7 H=(N*I)/l; //Calculating magnetic
   field strength
8 u0=4*%pi*10^-7; //permeability of free
   space
9 B=u0*H; //Flux density
10 phi=B*A; //Fux
11 disp("(a)");
12 printf("Magnetic field strength = %d A/m\n\n\n",H);
13 disp("(b)");
14 printf("Flux density = %f mT\n\n\n",B*1000);
15 disp("(c)");
16 printf("Flux = %f Wb",phi*10^6);

```

Scilab code Exa 7.7 Example 7

```
1 //Chapter 7, Problem 7
2 clc;
3 d=10*10-2; //Diameter
4 N=2000; //No of
   turns
5 I=0.25; //Current
   in the coil
6 B=0.4; //Magnetic
   flux density
7 u0=4*%pi*10-7; //
   permeability of free space
8 l=%pi*d; //
   Calculating length of coil
9 H=(N*I)/l; //
   Calculating magnetic field strength
10 ur=B/(u0*H); //
   Calculating relative permeability
11 disp("(a)");
12 printf("Magnetic field strength = %f A/m\n\n",H);
13 disp("(b)");
14 printf("Relative permeability = %d",ur);
```

Scilab code Exa 7.8 Example 8

```
1 //Chapter 7, Problem 8
2 clc;
3 A=10*10-4; //cross-sectional area
4 l=0.2; //mean circumference
   in meter
```

```

5 phi=0.3*10^-3;           //flux
6 B=phi/A;                 //flux density
7 H=1000;
8 mmf=H*l;                 //magnetomotive
    force
9 disp("From the magnetisation curve for cast iron on
    page74,")
10 printf("m.m.f = %f A",mmf);

```

Scilab code Exa 7.10 Example 10

```

1 //Chapter 7, Problem 10
2 clc;
3 l=150*10^-3;             //length
4 u0=4*pi*10^-7;          //
    permeability of free space
5 ur=4000;                 //relative
    permeability
6 A=1800*10^-6;           //cross-
    sectional area
7 S=1/(u0*ur*A);         //
    Calculating reluctance
8 u=u0*ur;                //
    Calculating absolute permeability
9 printf("Reluctance = %f H^-1\n\n",S);
10 printf("Absolute permeability = %f H/m",u*1000);

```

Scilab code Exa 7.11 Example 11

```

1 //Chapter 7, Problem 11
2 clc;
3 r=50*10^-3;             //radius

```

```

4 A=400*10^-6; //cross-sectional area
5 I=0.5; //current in the coil
6 u0=4*pi*10^-7; //permeability of free space
7 phi=0.1*10^-3; //flux
8 ur=200; //relative permeability
9 l=2*pi*r;
10 S=1/(u0*ur*A); //Calculating reluctance
11 N=(S*phi)/I; //Calculating no of turns
12 printf("Reluctance = %f /H\n\n",S);
13 printf("Number of turns = %d turns",N);

```

Scilab code Exa 7.12 Example 12

```

1 //Chapter 7, Problem 12
2 clc;
3 l1=6*10^-2; //length 1
4 A1=1*10^-4; //area 1
5 l2=2*10^-2; //length 2
6 A2=0.5*10^-4; //area 2
7 N=200; //no of turns
8 I=0.4; //current in the coil
9 u0=4*pi*10^-7; //permeability of free space
10 ur=750; //relative permeability
11 S1=l1/(u0*ur*A1); //calculating reluctance for 6 cm long path
12 S2=l2/(u0*ur*A2); //calculating

```

```

    reluctance for 2 cm long path
13 S=S1+S2;                               //calculating total
    reluctance
14 phi=(N*I)/S;                            //calculating flux
15 B=phi/A2;                               //calculating flux
    density in 2cm path
16 printf("Flux density in 2cm path = %f T",B);

```

Scilab code Exa 7.13 Example 13

```

1 //Chapter 7, Problem 13
2 clc;
3 l1=40*10^-2;;                            //length of iron
    path
4 l2=2*10^-3;                              //radial air gap
5 u0=4*pi*10^-7;
6 phi=0.7*10^-3;                           //flux
7 A=5*10^-4;                               //cross-
    sectional area
8 H1=1650;                                  //from B H
    curve for silicon iron
9 //Calculation for the silicon iron:
10 B=phi/A;
11 mmf1=H1*l1;
12 //Calculation for the air gap:
13 H2=B/u0;
14 mmf2=H2*l2;
15 mmf=mmf1+mmf2;
16 disp("From the B H curve for silicon iron on page
    74, when B=1.4T, H =1650A/m.");
17 printf("Hence m.m.f for the iron path = %d A\n\n\n",
    mmf1);
18 disp("The flux density will be the same in the air
    gap as in the iron,");
19 printf("Hence m.m.f for the air gap = %d A\n\n\n",

```



```

mmf2);
20 printf("Total m.m.f to produce a flux of 0.6mWb = %d
    A\n\n\n",mmf);

```

Scilab code Exa 7.15 Example 15

```

1 //Chapter 7, Problem 15, Figure 7.6
2 clc;
3 u0=4*pi*10^-7;
4 ur=1;
5 B=0.80; //flux density
6 H=750; //field intensity from B
    -H curve
7 l1=25*10^-2; //length of cast steel
    core
8 l2=1*10^-3; //air gap
9 A=2*10^-4; //cross-sectional area
10 N=5000; //no of turns
11 //for cast steel core
12 S1=(l1*H)/(B*A);
13 //For the air gap:
14 S2=l2/(u0*ur*A);
15 //Total reluctance
16 S=S1+S2;
17 phi=B*A;
18 I=(S*phi)/N;
19 printf("Current in the coil to produce a flux
    density of 0.80T = %f A",I);

```

Chapter 8

Electromagnetism

Scilab code Exa 8.2 Example 2

```
1 //Chapter 8, Problem 2
2 clc;
3 B=0.9; //flux density
4 I=20; //current
5 l=30*10^-2; //length of the conductor
6 //Calculating force when conductor is at right angle
7 F=B*I*l;
8 //Calculating force when conductor is inclined at 30
   to the field
9 F1=B*I*l*sin(%pi/6);
10 printf("Force when conductor is at right angle = %f
   N\n\n",F);
11 printf("Force when conductor is inclined at 30 to
   the field = %f N",F1);
```

Scilab code Exa 8.3 Example 3

```
1 //Chapter 8, Problem 3
```

```

2  clc;
3  F=1.92;
4  l=400*10^-3;
5  B=1.2;
6  I=F/(B*l);
7  printf("Current = %f A\n\n",I);
8  printf("If the current flows downwards, the
    direction of its");
9  printf(" magnetic field due to the current alone
    will be clockwise when viewed from above.\n");
10 printf("The lines of flux will reinforce (i.e.
    strengthen) the main magnetic field at");
11 printf("the back of the conductor and will be in
    opposition in the front (i.e. weaken the field).\n");
12 disp("Hence the force on the conductor will be from
    back to front (i.e. toward the viewer).");

```

Scilab code Exa 8.4 Example 4

```

1  //Chapter 8, Problem 4
2  clc;
3  l=350*10^-3;           //length of
    conductor
4  I=10;                 //current
5  r=0.06;              //radius of pole
6  phi=0.5*10^-3;      //flux
7  A=%pi*r^2;          //area of pole
8  B=phi/A;            //calculating
    flux density
9  F=B*I*l;            //calculating
    force
10 printf("Force = %f N",F);

```

Scilab code Exa 8.6 Example 6

```
1 //Chapter 8, Problem 6
2 clc;
3 B=0.8;
4 l=30*10^-3;
5 I=50*10^-3;
6 F=B*I*l;
7 F1=300*F;
8 printf("For a single-turn coil, force on each coil
   side\n");
9 printf("Force = %f N\n\n",F);
10 printf("When there are 300 turns on the coil there
   are effectively 300 parallel conductors each
   carrying a current of 50 mA.\n");
11 printf("Thus the total force produced by the current
   is 300 times that for a single-turn coil. Hence
   force on coil side,\n");
12 printf("Force = %f N",F1);
```

Scilab code Exa 8.7 Example 7

```
1 //Chapter 8, Problem 7
2 clc;
3 Q=1.6*10^-19; //charge in coulombs
4 v=3*10^7; //velocity of charge
5 B=18.5*10^-6; //flux density
6 F=Q*v*B; //Calculating force
7 printf("Force = %f x10^ 17 N",F*10^17);
```

Chapter 9

Electromagnetic induction

Scilab code Exa 9.1 Example 1

```
1 //Chapter 9, Problem 1
2 clc;
3 B=1.25; //flux density
4 v=4; //conductor velocity
5 l=300*10^-3; //conductor length
6 R=20; //resistance
7 E=B*l*v; //calculating emf
8 I=E/R; //calculating current
   from ohms law
9 disp("(a)");
10 disp("If the ends of the conductor are open
   circuited , no current will flow.");
11 disp("(b)");
12 disp("If its ends are connected to a load of 20ohm
   resistance , then");
13 printf("Current = %f A",I);
```

Scilab code Exa 9.2 Example 2

```

1 //Chapter 9, Problem 2
2 clc;
3 E=9; //emf
4 B=0.6; //flux density
5 l=75*10-3; //length of conductor
6 //since the conductor, the field and the direction
  of motion are mutually perpendicular
7 //calculating velocity
8 v=E/(B*l);
9 printf("Velocity = %f m/s",v);

```

Scilab code Exa 9.3 Example 3

```

1 //Chapter 9, Problem 3
2 clc;
3 v=15; //velocity of conductor
4 l=0.02; //length of conductor
5 A=2*2*10-4; //area of conductor
6 phi=5*10-6; //flux
7 Q1=%pi/2; //converting 90 degree
  into radian
8 Q2=%pi/3; //converting 60 degree
  into radian
9 Q3=%pi/6; //converting 30 degree
  into radian
10 B=phi/A; //calculating flux
  density
11 E90=B*l*v*sin(Q1); //calculating emf
12 E60=B*l*v*sin(Q2);
13 E30=B*l*v*sin(Q3);
14 disp("(a)");
15 printf("E.M.F at 90 =%f V\n\n",E90*1000);
16 disp("(b)");
17 printf("E.M.F at 60 =%f V\n\n",E60*1000);
18 disp("(c)");

```

```
19 printf("E.M.F at 30      =%f V\n\n",E30*1000);
```

Scilab code Exa 9.4 Example 4

```
1 //Chapter 9, Problem 4
2 clc;
3 B=40*10^-6;           //flux density
4 l=36;                 //length of
   conductor
5 v=(400*1000)/(60*60); //velocity of
   conductor
6 E=B*l*v;             //calculating emf
7 printf("E.M.F = %f V",E);
```

Scilab code Exa 9.6 Example 6

```
1 //Chapter 9, Problem 6
2 clc;
3 B=1.4;               //flux density
4 l=12*10^-2;         //length
5 N=80;               //no of turns
6 n=1200/60;         //rotation in
   sec
7 E1=90;              //emf
8 r=(8*10^-2)/2;
9 Q90=%pi/2;
10 //calculating velocity
11 v=2*%pi*n*r;
12 //calculating maximum emf
13 E=2*N*B*v*l*sin(Q90);
14 //calculating velocity with emf 90V
15 v=E1/(2*N*B*l*sin(Q90));
16 //calculating speed of coil
```

```

17 w=v/r;
18 w1=(w*60)/(2*%pi);
19 disp(" (a)");
20 printf("Maximum emf induced = %f V",E);
21 disp(" (b)");
22 printf("Speed of coil in rev/min = %d rev/min",w1);

```

Scilab code Exa 9.7 Example 7

```

1 //Chapter 9, Problem 7
2 clc;
3 N=200; //no of turns
4 dphi=25*10^-3; //change in flux
5 dt=50*10^-3; //change in time
6 E=-N*(dphi/dt); //calculating
   induced emf
7 printf("Induced emf E = %d V",E);

```

Scilab code Exa 9.8 Example 8

```

1 //Chapter 9, Problem 8
2 clc;
3 N=150;
4 //Since the flux reverses, the flux changes from+400
   Wb to 400 Wb,
5 // a total change of flux of 800 Wb.
6 dphi=800*10^-6; //change in flux
7 dt=40*10^-3; //change in time
8 E=-N*(dphi/dt); //calculating
   induced emf
9 printf("Induced emf = %f V",E);

```

Scilab code Exa 9.9 Example 9

```
1 //Chapter 9, Problem 9
2 clc;
3 L=12; //inductance
4 dI=4; //change in current
5 dt=1; //change in time
6 E=-L*(dI/dt); //calculating
   induced emf
7 printf("Induced emf E = %d V",E);
```

Scilab code Exa 9.10 Example 10

```
1 //Chapter 9, Problem 10
2 clc;
3 E=1.5*10^3; //emf
4 dI=4; //change in flux
5 dt=8*10^-3; //change in time
6 D=dI/dt;
7 L=E/D;
8 printf("Inductance L = %d H",L);
```

Scilab code Exa 9.11 Example 11

```
1 //Chapter 9, Problem 11
2 clc;
3 L=150*10^-3;
4 E=40;
5 //since the current is reversed, dI =6 ( 6 )=12A
```

```

6 dI=12;
7 //calculating change in time dt
8 dt=(L*dI)/E;
9 printf("Change in time dt = %f sec",dt);

```

Scilab code Exa 9.12 Example 12

```

1 //Chapter 9, Problem 12
2 clc;
3 L=8; //inductance
4 I=3; //current in coil
5 W=(1/2)*L*I^2; //calculating energy
   stored in inductor
6 printf("Energy stored = %d joules",W)

```

Scilab code Exa 9.13 Example 13

```

1 //Chapter 9, Problem 13
2 clc;
3 N=800; //no of turns
4 phi=5*10^-3; //flux
5 I=4; //current in
   coil
6 L=(N*phi)/I; //calculating
   inductance
7 printf("Inductance of coil = %f H",L);

```

Scilab code Exa 9.14 Example 14

```

1 //Chapter 9, Problem 14

```

```

2  clc;
3  N=1500;           //no of turns
4  phi=25*10^-3;    //flux
5  I=3;             //current in
   coil
6  dI=3-0;         //change in
   current
7  dt=150*10^-3;    //change in time
8  L=(N*phi)/I;     //calculating
   inductance
9  W=(1/2)*L*I^2;   //calculating
   energy stored
10 E=-L*(dI/dt);    //calculating
   induced emf
11 disp("(a)");
12 printf("Inductance = %f H\n\n",L);
13 disp("(b)");
14 printf("Energy stored = %f J\n\n",W);
15 disp("(c)");
16 printf("Induced e.m.f = %d V",E);

```

Scilab code Exa 9.15 Example 15

```

1  //Chapter 9, Problem 15
2  clc;
3  L=0.60;          //inductance
4  I=1.5;           //current in coil
5  phi=90*10^-6;   //flux
6  N=(L*I)/phi;    //calculating no of
   turns
7  printf("No of turns = %d turns",N);

```

Scilab code Exa 9.16 Example 16

```

1 //Chapter 9, Problem 16
2 clc
3 N=750 //no of turns
4 L=3 //inductance in
   henry
5 I=2 //current in ampere
6 t=20e-3 //time in milisec
7 phi=(L*I)/N
8 E=-(N*phi)/t
9 printf("Flux linking the coil = %d mWb\n\n",phi
   *1000)
10 printf("Induced emf = %d V",E)

```

Scilab code Exa 9.17 Example 17

```

1 //Chapter 9, Problem 17, Figure 9.10
2 clc;
3 N=800; //no of turns
4 I=0.5; //current in coil
5 l=%pi*120*10^-3; //length of coil
6 u0=4*%pi*10^-7; //permeability of free
   space
7 ur=3000; //relative permeability
8 dI=0.5-0; //change in current
9 dt=80*10^-3; //change in time
10 A=400*10^-6; //cross sectional area
11 S=1/(u0*ur*A); //calculating reluctance
12 L=N^2/S; //calculating inductance
13 E=-L*(dI/dt); //calculating induced
   emf
14 printf("Self inductance L = %f H\n\n\n",L);
15 printf("Induced emf E = %d V",E);

```

Scilab code Exa 9.18 Example 18

```
1 //Chapter 9, Problem 18
2 clc;
3 D=200; //rate of change of
    current w.r.t time
4 E=1.5; //induced emf
5 M=E/D; //mutual inductance
6 printf("Mutual inductance M = %f H",M);
```

Scilab code Exa 9.19 Example 19

```
1 //Chapter 9, Problem 19
2 clc;
3 E=0.72; //induced emf
4 M=0.018; //mutual inductance
5 D=E/M; //calculating rate of
    change of current
6 printf("Rate of change of current = %d A/s", D);
```

Scilab code Exa 9.20 Example 20

```
1 //Chapter 9, Problem 20
2 clc;
3 M=0.2;
4 dI=10^-4;
5 dt=10*10^-3;
6 N=500;
7 E=-M*(dI/dt);
8 dphi=(E*dt)/N;
9 printf("Induced emf = %d V\n\n",E);
10 printf("Change of flux = %f mWb",dphi*1000);
```

Scilab code Exa 9.21 Example 21

```
1 //Chapter 9, Problem 21, Figure 9.11
2 clc;
3 dI=6-1;
4 dt=200*10-3;
5 E=15;
6 Np=1000;
7 Ns=480;
8 M=E/(dI/dt);
9 S=(Np*Ns)/M;
10 Lp=Np2/S;
11 printf("Mutual Inductance = %f H\n\n",M);
12 printf("Reluctance = %d A/Wb\n\n",S);
13 printf("Primary self-inductance Lp = %f H",Lp);
```

Chapter 10

Electrical measuring instruments and measurements

Scilab code Exa 10.1 Example 1

```
1 //Chapter 10, Problem 1, figure 10.5
2 clc;
3 Ia=40*10-3; //maximum permissible
   current
4 I=50; //total circuit current
5 ra=25; //resistance of
   instrument
6 Is=I-Ia; //current flowing in
   shunt
7 V=Ia*ra; //voltage
8 Rs=V/Is; //resistance in shunt
9 printf("Shunt resistance Rs = %f miliohm\n\n",Rs
   *1000);
10 printf("A resistance of value 20.02 miliohm needs to
   be connected in parallel with the instrument.")
```

Scilab code Exa 10.2 Example 2

```
1 //Chapter 10, Problem 2, figure 10.6
2 clc;
3 I=0.008; //total circuit
   current
4 ra=10; //resistance of
   instrument
5 V=100; //total p.d
6 Va=I*ra; //calculating voltage
   across moving coil instrument
7 Rm=(V-(I*ra))/I; //calculating value of
   multiplier
8 printf("Multiplier Rm = %f K.ohm\n\n\n",Rm/1000);
9 printf("A resistance of value 12.49 k ohm needs to
   be connected in series with the instrument.");
```

Scilab code Exa 10.3 Example 3

```
1 //Chapter 10, Problem 3, figure 10.9
2 clc;
3 S=10000; //voltmeter sensitivity
4 V=100; //total voltage
5 fsd=200; //full scale deflection
6 R1=250; //load 1
7 R2=2e6; //load 2
8 Rv=S*fsd; //resistance of voltmeter ,
9 Iv=V/Rv; //current flowing in
   voltmeter
10 P=V*Iv; //calculating power
   dissipated by voltmeter
11 Ir1=V/R1; //calculating current in
   load 1
12 Ir2=V/R2; //calculating current in
   load 2
```



```

13 P1=V*Ir1; //calculating Power
    dissipated in load 1
14 P2=V*Ir2; //calculating Power
    dissipated in load 2
15 printf("Power dissipated by voltmeter = %f mW\n\n\n",
    P*1000);
16 printf("(a) Power dissipated in load 250 ohm = %f W\
    \n\n\n",P1);
17 printf("(b) Power dissipated in load 2 M.ohm = %f mW\
    \n\n\n",P2*1000);

```

Scilab code Exa 10.4 Example 4

```

1 //Chapter 10, Problem 4, figure 10.10
2 clc;
3 R=500; //load resistance
4 V=10; //supply voltage
5 ra=50; //ammeter resistance
6 Ie=V/R; //calculating expected current
7 Ia=V/(R+ra); //calculating actual current
8 P=Ia2*ra; //calculating power dissipated
    in the ammeter
9 P1=Ia2*R; //calculating power dissipated
    in load resistor
10 printf("(a) Expected ammeter reading = %f mA\n\n\n",
    Ie*1000);
11 printf("(b) Actual ammeter reading = %f mA\n\n\n",Ia
    *1000);
12 printf("(c) Power dissipated in the ammeter = %f mW\
    \n\n\n",P*1000);
13 printf("(d) Power dissipated in the load resistor =
    %f mW\n\n\n",P1*1000);

```

Scilab code Exa 10.5 Example 5

```
1 //Chapter 10, Problem 5, figure 10.11, figure 10.12
2 clc;
3 V=100; //f.s.d of voltmeter
4 S=1600; //sensitivity
5 R1=40e3; //resistor 1
6 R2=60e3; //resistor 2
7 V1=(R1/(R1+R2))*V; //voltage between A and B
8 R=R*S; //resistance of voltmeter
9 R3=((R1*R)/(R1+R)); //equivalent resistance of
   parallel network
10 V2=(R3/(R2+R3))*V; //voltage indicated by
   voltmeter
11 printf("(a) Value of voltage V1 with the voltmeter
   not connected = %f V\n\n",V1);
12 printf("(b) Voltage between A and B = %f V\n\n",V2
   );
```

Scilab code Exa 10.6 Example 6

```
1 //Chapter 10, Problem 6, figure 10.13
2 clc;
3 I=20; //current flows through a
   load
4 R=2; //load
5 r=0.01; //wattmeter coil resistance
6 P=I^2*R; //power dissipated in the
   load
7 Rt=R+r; //total resistance
8 P1=I^2*Rt; //wattmeter reading
9 printf("(a) Power dissipated in the load = %f W\n\n\
   n",P);
10 printf("(b) Wattmeter reading = %f W",P1);
```

Scilab code Exa 10.7 Example 7

```
1 //Chapter 10, Problem 7, figure 10.17
2 clc;
3 tc = 100e-6;           // in s/cm
4 Vc = 20;              // in V/cm
5 w = 5.2;              // in cm ( width of one
   complete cycle )
6 h = 3.6;              // in cm ( peak-to-peak
   height of the display )
7
8 //calculation:
9 T = w*tc
10 f = 1/T
11 ptpv = h*Vc
12
13 printf("\\n (a)The periodic time , T = %.2f ms\\n", T
   *10^3)
14 printf("\\n (b)Frequency , f = %.2f kHz\\n",f/1000)
15 printf("\\n (c)The peak-to-peak voltage = %.0f V\\n",
   ptpv)
```

Scilab code Exa 10.8 Example 8

```
1 //Chapter 10, Problem 8, figure 10.18
2 clc;
3 tc = 50e-3;           // in s/cm
4 Vc = 0.2;             // in V/cm
5 w = 3.5;              // in cm ( width of one
   complete cycle )
6 h = 3.4;              // in cm ( peak-to-peak
   height of the display )
```

```

7 // calculation :
8 T = w*tc
9 f = 1/T
10 ptpv = h*Vc
11 printf("\n\n (a)The periodic time , T = %.2 f ms" ,T
      *10^3)
12 printf("\n\n (b)Frequency , f = %.2 f Hz" ,f)
13 printf("\n\n (c)The peak-to-peak voltage = %.2 f V" ,
      ptpv)

```

Scilab code Exa 10.9 Example 9

```

1 //Chapter 10, Problem 9, figure 10.19
2 clc;
3 tc = 500e-6;           // in s/cm
4 Vc = 5;               // in V/cm
5 w = 4;                // in cm ( width of one
      complete cycle )
6 h = 5;                // in cm ( peak-to-peak
      height of the display )
7 // calculation :
8 T = w*tc
9 f = 1/T
10 ptpv = h*Vc
11 Amp = ptpv/2
12 Vrms = Amp/(2^0.5)
13 printf("\n\n (a)Frequency , f = %.0 f Hz" ,f)
14 printf("\n\n (b)the peak-to-peak voltage = %.0 f V" ,
      ptpv)
15 printf("\n\n (c)Amplitude = %.1 f V" ,Amp)
16 printf("\n\n (d)r.m.s voltage = %.2 f V" ,Vrms)

```

Scilab code Exa 10.10 Example 10

```

1 //Chapter 10, Problem 10, figure 10.20
2 clc;
3 tc = 100E-6;           // in s/cm
4 Vc = 2;                // in V/cm
5 w = 5;                 // in cm ( width of one
    complete cycle for both waveform )
6 h1 = 2;                // in cm ( peak-to-peak
    height of the display )
7 h2 = 2.5;              // in cm ( peak-to-peak
    height of the display )
8
9 //calculation:
10 T = w*tc
11 f = 1/T
12 ptpv1 = h1*Vc
13 Vrms1 = ptpv1/(2^0.5)
14 ptpv2 = h2*Vc
15 Vrms2 = ptpv2/(2^0.5)
16 phi = 0.5*360/w
17
18 printf("\\n\\n (a)Frequency , f = %f kHz",f/1000)
19 printf("\\n\\n (b1)r.m.s voltage of 1st waveform = %.2
    f V",Vrms1)
20 printf("\\n\\n (b2)r.m.s voltage of 2nd waveform = %.2
    f V",Vrms2)
21 printf("\\n\\n (c)Phase difference = %.0 f ",phi)

```

Scilab code Exa 10.12 Example 12

```

1 //Chapter 10, Problem 12, figure 10.30
2 clc;
3 rP1 = 3;               // ratio of two powers
4 rP2 = 20;              // ratio of two powers
5 rP3 = 400;             // ratio of two powers
6 rP4 = 1/20;            // ratio of two powers

```

```

7 // calculation :
8 X1 = 10*log10(3)
9 X2 = 10*log10(20)
10 X3 = 10*log10(400)
11 X4 = 10*log10(1/20)
12
13 printf("\n\n (a) decibel power ratio for power ratio
      3 = %.2f dB ", X1)
14 printf("\n\n (b) decibel power ratio for power ratio
      20 = %.1f dB ", X2)
15 printf("\n\n (c) decibel power ratio for power ratio
      400 = %.1f dB ", X3)
16 printf("\n\n (d) decibel power ratio for power ratio
      1/20 = %.1f dB ", X4)

```

Scilab code Exa 10.13 Example 13

```

1 //Chapter 10, Problem 13
2 clc;
3 I2=20; //current in amperes
4 I1=5; //current in amperes
5 d=20*log10(I2/I1); //in decibel
6 printf("decibel current ratio = %d dB",d);

```

Scilab code Exa 10.14 Example 14

```

1 //Chapter 10, Problem 14
2 clc;
3 P1=100; //input power
4 P2=6; //ouput power
5 d=10*log10(P2/P1); //decibel power ratio
6 printf("decibel power loss = %f dB",d);

```

Scilab code Exa 10.15 Example 15

```
1 //Chapter 10, Problem 15
2 clc;
3 d=14; //amplifier gain
4 P1=8e-3; //input power
5 P2=10^(14/10)*P1; //calculating output
   power using logarithm
6 printf("Output power = %f mW",P2*1000);
```

Scilab code Exa 10.16 Example 16

```
1 //Chapter 10, Problem 16
2 clc;
3 g1=12; //gain of stage 1
4 g2=15; //gain of stage 2
5 g3=-8; //gain of stage 3
6 P=g1+g2+g3; //Power ratio
7 P1=10^(P/10); //calculating overall power gain
8 printf("Overall power gain (P2/P1) = %f ",P1);
```

Scilab code Exa 10.17 Example 17

```
1 //Chapter 10, Problem 17
2 clc;
3 V2=4; //output voltage
4 V=27; //voltage gain in decibels
5 V1=V2/(10^(V/20)); //calculating input voltage
   using logarithm
6 printf("Input voltage = %f V",V1);
```

Scilab code Exa 10.18 Example 18

```
1 //Chapter 10, Problem 18
2 clc;
3 BC=100; //resistance between point B
   and C
4 DA=400; //resistance between point D
   and A
5 CD=10; //resistance between point C
   and D
6 Rx=BC*DA/CD; //calculating unknown
   resistance using balance equation
7 printf("unknown resistance = %f K ohms",Rx/1000);
```

Scilab code Exa 10.19 Example 19

```
1 //Chapter 10, Problem 19
2 clc;
3 E1=1.0186; //emf of standard cell
4 I1=400e-3; //balance length when using
   standard cell
5 I2=650e-3; //balance length when using
   dry cell
6 E2=E1*(I2/I1); //calculating emf of dry
   cell
7 printf("e.m.f of dry cell = %f V",E2);
```

Scilab code Exa 10.20 Example 20


```

1 //Chapter 10, Problem 20, figure 10.35
2 clc;
3 //resistance of coil
4 R1=400;
5 R2=400;
6 R3=5000;
7 //value of capacitance
8 C=7.5e-6;
9 //calculating the value of inductance
10 L=R1*R2*C;
11 //calculating the value unknown resistance
12 r=(R1*R2)/R3;
13 printf(" Inductance = %f H\n\n\n",L);
14 printf(" Resistance = %d ohm",r);

```

Scilab code Exa 10.21 Example 21

```

1 //Chapter 10, Problem 20, figure 10.35
2 clc;
3 fr=400e3; //resonant frequency
4 Qf=100; //Q factor
5 C=400e-12; //capacitance
6 L=((2*%pi*fr)^2*C)^-1; //calculating inductance
7 R=2*%pi*fr*L/Qf; //calculating resistance
8 printf(" (a) Inductance = %f mH\n\n\n",L*1000);
9 printf(" (b) Resistance of inductor = %f ohm",R);

```

Scilab code Exa 10.22 Example 22

```

1 //Chapter 10, Problem 22
2 clc
3 I=2.5e-3 //current in amperes
4 R=5000 //resistance in ohm

```

```

5 e1=0.4 //error tolerance
6 e2=0.5 //error tolerance
7 V=I*R
8 emax=e1+e2
9 V1=(emax/100)*V
10 printf("V = %.1f V\n accuracy = %.2f V\n",V,V1)

```

Scilab code Exa 10.23 Example 23

```

1 //Chapter 10, Problem 23
2 clc
3 V=36.5 //voltage
4 V1=50 //max voltage of
    voltameter
5 I1=10 //max current of
    ammeter
6 I=6.25 //current in amperes
7 ev=2
8 R=V/I
9 ev1=(2/100)*V1
10 ev2=ev1*100/V
11 ei1=(ev/100)*I1
12 ei2=ei1*100/I
13 eiv=ev2+ei2
14 r=eiv*R/100
15 printf("Maximum relative error = %.2f percent or %.2
    f ohm\n\n",eiv,r)
16 printf("Resistance = %.2f ohm",R)

```

Scilab code Exa 10.24 Example 24

```

1 //Chapter 10, Problem 24
2 clc

```

```

3 R2=100 //resistance in ohm
4 R3=432.5 //resistance in ohm
5 R1=1000 //resistance in ohm
6 e1=1 //error of R1 in
    percent
7 e2=0.5 //error of R2 in
    percent
8 e3=0.2 //error of R3 in
    percent
9 Rx=R2*R3/R1
10 et=e1+e2+e3
11 et1=et*Rx/100
12 printf("Unknown resistance = %.2f ohm \n\n",Rx)
13 printf("Maximum relative error = %.1f percent\n",et)
14 printf("Maximum relative erroe in ohm = %.2f ohm",
    et1)

```

Chapter 12

Transistors

Scilab code Exa 12.2 Example 2

```
1 //Chapter 12, Problem 2
2 clc;
3 Ic=100*10^-3;           //emitter current
4 Ie=102*10^-3;         //collector current
5 Ib=Ie-Ic;              //calculating base
                        current
6 printf("Value of base current Ib = %d mA",Ib*1000);
```

Scilab code Exa 12.6 Example 6

```
1 //Chapter 12, Problem 6
2 clc;
3 hFE=125;                //common-emitter current
                        gain
4 Ic=50*10^-3;           //collector current
5 Ib=Ic/hFE;            //calculating base
                        current
6 printf("Base current Ib = %d microampere",Ib*10^6);
```

Scilab code Exa 12.9 Example 9

```
1 //Chapter 12, Problem 9
2 clc;
3 Id=100*10-3; //operating
   drain current
4 dVgs=-0.1; //change in gate
   -source voltage
5 gfs=0.25;
6 dId=dVgs*gfs; //calculating
   change in drain current
7 Id1=Id+dId; //new value of
   drain current
8 disp("(a)");
9 printf("Change in drain current = %d mA\n\n",dId
   *1000);
10 disp("(b)");
11 printf("New value of drain current = %d mA",Id1
   *1000);
```

Chapter 13

DC circuit theory

Scilab code Exa 13.1 Example 1

```
1 //Chapter 13, Problem 1, Figure 13.3,
2 clc;
3 //branch currents in figure 13.3 (a)
4 I1=50-20;
5 I2=20+15;
6 I3=I1-120;
7 I4=15-I3;
8 I5=120-40;
9 disp("(a) from Fig. 13.3(a).");
10 disp("For junction B:");
11 printf("I1 = %d A",I1);
12 disp("For junction C:");
13 printf("I2 = %d A",I2);
14 disp("For junction D:");
15 printf("I3 = %d A",I3);
16 disp("For junction E:");
17 printf("I4 = %d A",I4);
18 disp("For junction F:");
19 printf("I5 = %d A\n\n\n",I5);
20 disp("(b) from Fig. 13.3(b).");
21 printf("Applying Kirchhoff s voltage law and
```

```

        moving clockwise around the loop,\n");
22 printf("starting at point A, we get,\n");
23 //from figure 13.3(b)
24 I=2;
25 E=I*(2+2.5+1.5+1)-(3+6-4);
26 printf("emf E = %d V",E);

```

Scilab code Exa 13.2 Example 2

```

1 //Chapter 13, Problem 2, Figure 13.4
2 clc;
3 A=[6 4;4 5];
4 B=[4;2];
5 X=A\B;
6 I1=X(1,1); //I1 and I2 is a branch
   current
7 I2=X(2,1);
8 disp("From figure 13.5");
9 disp("Using Kirchhoff s current law and labeling
   the current directions on the circuit");
10 disp("Divide the circuit into two loops and apply
   Kirchhoff s voltage law to each.");
11 printf("we get \n 6I1 + 4I2 = 4 \n 4I1 + 5I2 =2\n\n"
   );
12 printf(" By solving both equations , we get \n");
13 printf(" I1 = %.3 f A\n",I1);
14 printf(" I2 = %.3 f A\n",I2);
15 printf(" I1+I2 = %.3 f A",I1+I2);

```

Scilab code Exa 13.3 Example 3

```

1 //Chapter 13, Problem 3, Figure 13.7
2 clc;

```

```

3 A=[0.5 2;-5 7];
4 B=[16;12];
5 X=A\B;
6 I1=X(1,1); //I1 and I2 is a branch
   current
7 I2=X(2,1);
8 disp("From figure 13.8");
9 disp("The network is divided into two loops");
10 printf("Applying Kirchhoff s voltage law to both
   loops gives,");
11 printf("16 = 0.5I1 + 2I2 \n12 = 5I1 + 7I2\n\n\n");
   ;
12 printf("Solving these equation we get,\n");
13 printf("I1 = %.2f A\n",I1);
14 printf("I2 = %.2f A\n",I2);
15 printf("Current flowing in R3 = %.2f A",I1-I2);

```

Scilab code Exa 13.4 Example 4

```

1 //Chapter 13, Problem 4, Figure 13.9
2 clc;
3 I=8; //total current
4 A=[13 -11;16 32];
5 B=[54;112];
6 X=A\B;
7 I1=X(1,1) //I1 and I2 is a branch
   current
8 I2=X(2,1);
9 disp("from figure 13.10");
10 printf("Applying Kirchhoff s voltage law to loop 1
   and 2, we get");
11 printf("13I1 11I2 = 54\n 16I1 + 32I2 = 112\n\n\n");
   );
12 printf("Solving the above simultaneous equations, we
   get\n");

```



```

13 printf(" I1 = %d A\n",I1);
14 printf(" I2 = %d A\n",I2);
15 printf(" I-I1 = %d A\n",I-I1);
16 printf(" I1-I2 = %d A\n",I1-I2);
17 printf(" I-I1+I2 = %d A\n\n\n",I-I1+I2);
18 printf(" Therefore ,\n");
19 printf(" Current flowing in the 2ohm resistor = %f A\n",I1);
20 printf(" Current flowing in the 14ohm resistor = %f A\n",I-I1);
21 printf(" Current flowing in the 32ohm resistor = %f A\n",I2);
22 printf(" Current flowing in the 11ohm resistor = %f A\n",I1-I2);
23 printf(" Current flowing in the 3ohm resistor = %f A\n",I-I1+I2);

```

Scilab code Exa 13.5 Example 5

```

1 //Chapter 13, Problem 5, figure 13.16
2 clc;
3 E1=4; //e.m.f source 1
4 E2=2; //e.m.f source 2
5 R=4 //resistor
6 r1=2; //internal resistance 1
7 r2=1; //internal resistance 2
8 Rr2=(R*r2)/(R+r2); //equivalent resistance
9 //calculating I2, I3, I4, I5, I6 by using current
  division formula
10 I1=E1/(r1+Rr2);
11 I2=(r2/(R+r2))*I1;
12 I3=(R/(R+r2))*I1;
13 Rr1=(R*r1)/(R+r1);
14 I4=E2/(Rr1+r2);
15 I5=(r1/(R+r1))*I4;

```

```

16 I6=(R/(R+r1))*I4;
17 printf("Redraw the original circuit with sourceE2
    removed, being replaced by r2 only, as shown in
    Fig. 13.17(a)\n\n");
18 printf("From the equivalent circuit of Fig. 13.17(a)
    and (b),\n");
19 printf(" I1 = %.3f A\n",I1);
20 printf(" I2 = %.3f A\n",I2);
21 printf(" I3 = %.3f A\n\n",I3);
22 printf("Redraw the original circuit with sourceE1
    removed, being replaced by r1 only, as shown in
    Fig. 13.18(a)\n\n");
23 printf("From the equivalent circuit of Fig. 13.18(a)
    and (b)\n")
24 printf(" I4 = %.3f A\n",I4);
25 printf(" I5 = %.3f A\n",I5);
26 printf(" I6 = %.3f A\n\n",I6);
27 printf("Superimpose Fig. 13.18(a) on to Fig. 13.17(a)
    ) as shown in Fig. 13.19\n\n");
28 printf("Resultant current flowing through source 1 =
    %.3f A (discharging)\n",I1-I6);
29 printf("Resultant current flowing through source 2 =
    %.3f A (charging)\n",I4-I3);
30 printf("Resultant current flowing through resistor R
    = %.4f A\n\n",I2+I5);
31 printf("The resultant currents with their directions
    are shown in Fig. 13.20");

```

Scilab code Exa 13.6 Example 6

```

1 //Chapter 13, Problem 6, figure 13.21
2 clc;
3 E1=8; //e.m.f source 1
4 E2=3; //e.m.f source 2
5 R=18 //resistor

```

```

6  r1=3;                               //internal resistance 1
7  r2=2;                               //internal resistance 2
8  Rr2=(R*r2)/(R+r2);                 //equivalent resistance
9  //calculating I2, I3, I4, I5, I6 by using current
    division formula
10 I1=E1/(r1+Rr2);
11 I3=(r2/(R+r2))*I1;
12 I2=(R/(R+r2))*I1;
13 Rr1=(R*r1)/(R+r1);
14 I4=E2/(Rr1+r2);
15 I6=(r1/(R+r1))*I4;
16 I5=(R/(R+r1))*I4;
17 I36=I3-I6;
18 V=I36*R;
19 printf("Redraw the original circuit with source E2
    removed, being replaced by r2 only, as shown in
    Fig. 13.22(a)\n\n");
20 printf("From the equivalent circuit of Fig. 13.22(a)
    and (b),\n");
21 printf(" I1 = %.3f A\n", I1);
22 printf(" I2 = %.3f A\n", I2);
23 printf(" I3 = %.3f A\n\n", I3);
24 printf("Redraw the original circuit with source E1
    removed, being replaced by r1 only, as shown in
    Fig. 13.23(a)\n\n");
25 printf("From the equivalent circuit of Fig. 13.23(a)
    and (b)\n");
26 printf(" I4 = %.3f A\n", I4);
27 printf(" I5 = %.3f A\n", I5);
28 printf(" I6 = %.3f A\n\n", I6);
29 printf("Superimpose Fig. 13.23(a) on to Fig. 13.22(a)
    ) as shown in Fig. 13.24\n\n");
30 printf("Resultant current flowing through 18 ohm
    resistor = %.3f A\n", I36);
31 printf("P.d. across the 18ohm resistor = %.3f V\n", V
    );
32 printf("Resultant current flowing in the 8V battery
    = %.3f A (discharging)\n", I1+I5);

```

```

33 printf("Resultant current flowing in the 3V battery
    = %.3f A(charging)\n\n",I2+I4);
34 printf("The resultant currents with their directions
    are shown in Fig. 13.24");

```

Scilab code Exa 13.7 Example 7

```

1 //Chapter 13, Problem 7, figure 13.37
2 clc;
3 E1=10; //e.m.f source 1
4 R1=2; //resistor 1
5 R3=5; //resistor 2
6 R2=8; //resistor 3
7 R=10; //resistor 4
8 I1=E1/(R1+R2);
9 V2=I1*R2;
10 r=R3+((R1*R2)/(R1+R2));
11 I=V2/(R+r);
12 printf("(i) The 10 resistance is removed from the
    circuit as shown in Fig. 13.38(a)\n\n");
13 printf("(ii) There is no current flowing in the 5
    resistor and current I1 is given by\n");
14 printf("I1 = %.3f A\n",I1);
15 printf("P.d across R2 is given by\n E = %.3f V\n\n",
    V2);
16 printf("(iii) Removing the source of e.m.f. gives
    the circuit of Fig. 13.38(b) Resistance,\n");
17 printf("r = %.3f ohm\n\n",r);
18 printf("(iv) The equivalent Th venin s circuit is
    shown in Fig. 13.38(c)");
19 printf("Hence the current flowing in the 10 resistor
    of Fig. 13.37 is \n");
20 printf("I = %.3f A",I);

```

Scilab code Exa 13.8 Example 8

```
1 //Chapter 13, Problem 8, figure 13.39
2 clc;
3 E1=12; //e.m.f source
4 R1=1; //resistance in ohm
5 R3=4; //resistance in ohm
6 R2=5; //resistance in ohm
7 R=0.8; //resistance in ohm
8 I1=E1/(R1+R2+R3); //current in amperes
9 V1=R3*I1;
10 Req=R1+R2; //equivalent
    resistance
11 r=(R3*Req)/(R3+Req); //
    equivalent resistance
12 I=V1/(r+R);
13 printf("(i) The 0.8ohm resistor is removed from the
    circuit as shown in Fig. 13.40(a).\n\n");
14 printf("(ii) Current I1 = %f A \n P.d. across 4ohm
    resistor = %f V\n\n",I1,V1);
15 printf("(iii) Removing the source of e.m.f. gives
    the circuit shown in Fig. 13.40(b). The equivalent
    circuit of Fig. 13.40(b) is shown in Fig. 13.40(c
    ), from which, resistance\n");
16 printf("r = %f ohm \n\n",r);
17 printf("(iv) The equivalent Thevenin's circuit is
    shown in Fig. 13.40(d), from which, current\n");
18 printf("Current in the 0.8ohm resistor I = %f A",I);
```

Scilab code Exa 13.9 Example 9

```
1 //Chapter 13, Problem 9, figure 13.41
```

```

2  clc;
3  E1=4;           //e.m.f source 1
4  E2=2;           //e.m.f source 2
5  r1=2;           //resistance in ohm
6  r2=1;           //resistance in ohm
7  R=4;            //resistance in ohm
8  I1=(E1-E2)/(r1+r2); //current in amperes
9  E=E1-(I1*r1);
10 r=(r1*r2)/(r1+r2);
11 I=E/(r+R);
12 P=I^2*R;       //power dissipated
    in watt
13 printf("(i) The 4ohm resistor is removed from the
    circuit as shown in Fig. 13.42(a)\n\n");
14 printf("(ii) Current I1 = %f A \n P.d across AB = %f
    V\n\n",I1,E);
15 printf("(iii) Removing the sources of e.m.f. gives
    the circuit shown in Fig. 13.42(b), from which,
    resistance\n r = %f ohm\n\n",r);
16 printf("(iv) The equivalent Th venin s circuit is
    shown in Fig. 13.42(c), from which, current,\n I
    = %f A\n\n",I);
17 printf("Power dissipated in the 4 resistor , \nP = %f
    W",P);

```

Scilab code Exa 13.10 Example 10

```

1  //Chapter 13, Problem 10, figure 13.43
2  clc;
3  E1=4;           //e.m.f source 1
4  E2=12;          //e.m.f source 1
5  r1=0.5;         //resistance in ohm
6  r2=2;           //resistance in ohm
7  R3=5;           //resistance in ohm
8  I1=(E1-(-E2))/(r1+r2); //current in ampere

```

```

 9 E=E1-(I1*r1);           //p.d in volts
10 r=(r1*r2)/(r1+r2);     //resistance in ohm
11 I=E/(r+R3);
12 V=I*R3;
13 Ia=(E1-V)/r1;
14 Ib=(E2+V)/r2;
15 printf("(i) The 5ohm resistance is removed from the
    circuit as shown in Fig. 13.44(a)\n\n");
16 printf("(ii) Current I1 = %f A \n P.d across AB = %f
    V\n\n",I1,E);
17 printf("(iii) Removing the sources of e.m.f. gives
    the circuit shown in Fig. 13.44(b), from which,
    resistance\n r = %f ohm\n\n",r);
18 printf("(iv) The equivalent Th venin s circuit is
    shown in Fig. 13.44(c), from which, current,\n I
    = %f A\n\n",I);
19 printf("From Section 13.4(iii), Hence current \n Ia
    = %f A\n",Ia);
20 printf("From Fig. 13.44(d), Hence current \n Ib = %f
    A",Ib);

```

Scilab code Exa 13.13 Example 13

```

1 //Chapter 13, Problem 13, figure 13.54
2 clc;
3 E=10;           //e.m.f source 1
4 R1=2;           //resistance in ohm
5 R2=8;           //resistance in ohm
6 R3=5;           //resistance in ohm
7 R4=10;         //resistance in ohm
8 Isc=E/R1;      //short-circuit
    current in ampere
9 r=(R1*R2)/(R1+R2);
10 I=(r/(r+R3+R4))*Isc;
11 printf("(i) The branch containing the 10 resistance

```

```

    is short-circuited as shown in Fig. 13.55(a)\n\n"
);
12 printf("(ii) Fig. 13.55(b) is equivalent to Fig.
    13.55(a).\n Isc = %f A\n\n",Isc);
13 printf("(iii) If the 10V source of e.m.f. is removed
    from Fig. 13.55(a) the resistance looking -
    in at a break made between A and B is given by
    :\n");
14 printf("r = %f ohm\n\n",r);
15 printf("(iv) From the Norton equivalent network
    shown in Fig. 13.55(c) the current in the 10
    resistance, by current division, is given by:\n")
;
16 printf("I = %f A",I);

```

Scilab code Exa 13.14 Example 14

```

1 //Chapter 13, Problem 14, figure 13.56
2 clc;
3 E1=4; //e.m.f source 1
4 E2=2; //e.m.f source 2
5 R1=2; //resistance in ohm
6 R2=1; //resistance in ohm
7 R3=4; //resistance in ohm
8 I1=E1/R1; //current in ampere
9 I2=E2/R2; //current in ampere
10 Isc=I1+I2; //short-circuit current
11 r=(R1*R2)/(R1+R2);
12 I=(r/(r+R3))*Isc;
13 printf("(i) The 4ohm branch is short-circuited as
    shown in Fig. 13.57(a)");
14 printf("(ii) From Fig. 13.57(a),\n Isc = %f A\n\n",
    Isc);
15 printf("(iii) If the sources of e.m.f. are removed
    the resistance looking-in at a break made

```



```

    between A and B is given by:\n");
16 printf("r = %f ohm\n\n",r);
17 printf("(iv) From the Norton equivalent network
    shown in Fig. 13.56(b) the current in the 4ohm
    resistance is given by:\n");
18 printf("I = %f A",I);

```

Scilab code Exa 13.15 Example 15

```

1 //Chapter 13, Problem 15, figure 13.58
2 clc;
3 E1=4; //e.m.f source 1
4 E2=12; //e.m.f source 2
5 R1=0.5; //resistance in ohm
6 R2=2; //resistance in ohm
7 R3=5; //resistance in ohm
8 I1=E1/R1; //current in ampere
9 I2=E2/R2; //current in ampere
10 Isc=I1-I2; //short-circuit current
11 r=(R1*R2)/(R1+R2);
12 I=(r/(r+R3))*Isc;
13 printf("(i) The 5ohm branch is short-circuited as
    shown in Fig. 13.59(a)\n\n");
14 printf("(ii) From Fig. 13.59(a),\n Isc = %f A\n\n",
    Isc);
15 printf("(iii) If each source of e.m.f. is removed
    the resistance looking-in at a break made
    between A and B is given by:\n");
16 printf("r = %f ohm\n\n",r);
17 printf("(iv) From the Norton equivalent network
    shown in Fig. 13.59(b) the current in the 5
    resistance is given by:\n");
18 printf("I = %f A",I);

```

Scilab code Exa 13.16 Example 16

```
1 //Chapter 13, Problem 16, figure 13.60
2 clc;
3 E1=24; //e.m.f source 1
4 R1=3; //resistance in ohm
5 R2=1.66; //resistance in ohm
6 R3=10; //resistance in ohm
7 R4=5; //resistance in ohm
8 R5=20; //resistance in ohm
9 Isc=E1/R4; //short-circuit current
10 r=(R3*R4)/(R4+R3);
11 I=(r/(r+R2+R1))*Isc;
12 printf("(i) The branch containing the 3ohm
    resistance is shortcircuited as shown in Fig.
    13.61(a)\n\n");
13 printf("(ii) From the equivalent circuit shown in Fig
    . 13.61(b), \nIsc = %f A\n\n",Isc);
14 printf("(iii) If the 24V source of e.m.f. is removed
    the resistance looking -in at a break made
    between A and B is obtained from Fig. 13.61(c) and
    its equivalent circuit shown in Fig. 13.61(d)
    and is given by:\n");
15 printf("r = %f ohm\n\n",r);
16 printf("(iv) From the Norton equivalent network
    shown in Fig. 13.61(e) the current in the 3ohm
    resistance is given by: \n");
17 printf("I = %.1f A\n\n",I);
```

Scilab code Exa 13.17 Example 17

```
1 //Chapter 13, Problem 17, Figure 13.62
```

```

2  clc;
3  I1=15                                //current source
   in ampere
4  R1=6;                                //resistance in ohm
5  R2=4;                                //resistance in
   ohm
6  R3=2;                                //resistance in
   ohm
7  R4=8;                                //resistance in
   ohm
8  R5=7;                                //resistance in
   ohm
9  Isc=(R1/(R1+R2))*I1;                 //short-circuit
   current
10 R12=R1+R2;
11 R45=R4+R5;
12 r=(R12*R45)/(R12+R45);
13 I=(R1/(R1+R3))*Isc;
14 printf("(i) The 2ohm resistance branch is short-
   circuited as shown in Fig. 13.63(a)\n\n");
15 printf("(ii) Fig. 13.63(b) is equivalent to Fig.
   13.63(a).\n");
16 printf("Hence Isc = %f A\n\n",Isc);
17 printf("(iii) If the 15A current source is replaced
   by an opencircuit then from Fig. 13.63(c),");
18 printf("the resistance looking-in at a break
   made between A and B is given by (6+4)ohm in
   parallel with (8+7)ohm, i.e.\n r = %f ohm\n\n",r)
   ;
19 printf("(iv) From the Norton equivalent network
   shown in Fig. 13.63(d) the current in the 2ohm
   resistance is given by: \n");
20 printf("I = %f A",I);

```

Scilab code Exa 13.19 Example 19

```

1 //Chapter 13, Problem 19, figure 13.70
2 clc;
3 Isc=4; //short-circuit current
4 r=3; //resistance in ohm
5 E=Isc*r; //open-circuit voltage
6 printf("The open-circuit voltage E across terminals
   AB in Fig. 13.70 is given by:\n E = %d V\n\n",E);
7 printf("Hence the equivalent Th venin circuit is as
   shown in Fig. 13.71");

```

Scilab code Exa 13.20 Example 20

```

1 //Chapter 13, Problem 20, figure 13.72
2 clc;
3 E1=12; //e.m.f source 1
4 E2=24; //e.m.f source 2
5 r1=3; //resistance in
   ohm
6 r2=2; //resistance in
   ohm
7 R=1.8; //resistance in
   ohm
8 Isc1=E1/r1; //short-circuit
   current
9 Isc2=E2/r2; //short-
   circuit current
10 Isc=Isc1+Isc2; //short-
   circuit current
11 r=(r1*r2)/(r1+r2);
12 E=Isc*r;
13 I=(E/(r+R));
14 printf("For the branch containing the 12V source ,
   converting to a Norton equivalent circuit gives \
   nIsc1 = %d A\n",Isc1);
15 printf("For the branch containing the 24V source ,

```

```

    converting to a Norton equivalent circuit gives \
    nIsc2 = %d A\n\n",Isc2);
16 printf("Thus Fig. 13.73(a) shows a network
    equivalent to Fig. 13.72");
17 printf("From Fig. 13.73(a) the total short-circuit
    current and the total resistance is given by\n");
18 printf("Isc = %f A\n r = %f ohm\n Thus Fig. 13.73(a)
    simplifies to Fig. 13.73(b).",Isc,r);
19 printf("The open-circuit voltage across AB of Fig.
    13.73(b),\n E = %f V\n",E);
20 printf("Hence the Th venin equivalent circuit is as
    shown in Fig. 13.73(c).");
21 printf("When the 1.8 resistance is connected
    between terminals A and B of Fig. 13.73(c) the
    current I flowing is given by\n I = %f A",I);

```

Scilab code Exa 13.21 Example 21

```

1 //Chapter 13, Problem 21, figure 13.74
2 clc;
3 E1=10; //e.m.f source 1
4 r1=2000; //resistance in
    ohm
5 E2=6; //e.m.f source 2
6 r2=3000; //resistance in
    ohm
7 I1=1*10^-3; //current in
    ampere
8 R1=600; //resistance
    in ohm
9 R2=200; //resistance in
    ohm
10 Isc1=E1/r1; //short-circuit
    current
11 Isc2=E2/r2; //short-circuit

```

```

    current
12 Isc=Isc1+Isc2; //short-
    circuit current
13 R=(r1*r2)/(r1+r2);
14 Vcd=Isc*R;
15 Vef=I1*R1;
16 E=Vcd-Vef;
17 r=(R+R1);
18 I=E/(r+R2);
19 printf("For the branches containing the 10V
    source and 6V source, converting to a Norton
    equivalent network respectively gives\n");
20 printf("Isc1 = %f mA\nIsc2 = %f mA\n\n",Isc1*1000,
    Isc2*1000);
21 printf("Thus the network of Fig. 13.74 converts to
    Fig. 13.75(a).\n\n");
22 printf("Combining the 5mA and 2mA current sources
    gives the equivalent network of Fig. 13.75(b)\n")
    ;
23 printf("where the short-circuit current for the
    original two branches considered is 7mA and the
    resistance is \n = %f ohm\n\n",R);
24 printf("The open-circuit voltage across CD is \n =
    %f V\n",Vcd);
25 printf("The open-circuit voltage across EF is\n = %f
    V\n\n Thus Fig. 13.75(b) converts to Fig. 13.75(
    c).",Vef);
26 printf("Combining the two Th venin circuits gives\n
    E = %f V\n r = %f ohm",E,r);
27 printf("\n\nHence the current I flowing in a 200 ohm
    resistance connected between A and B is given by
    \n");
28 printf(" I = %f mA",I*1000);

```

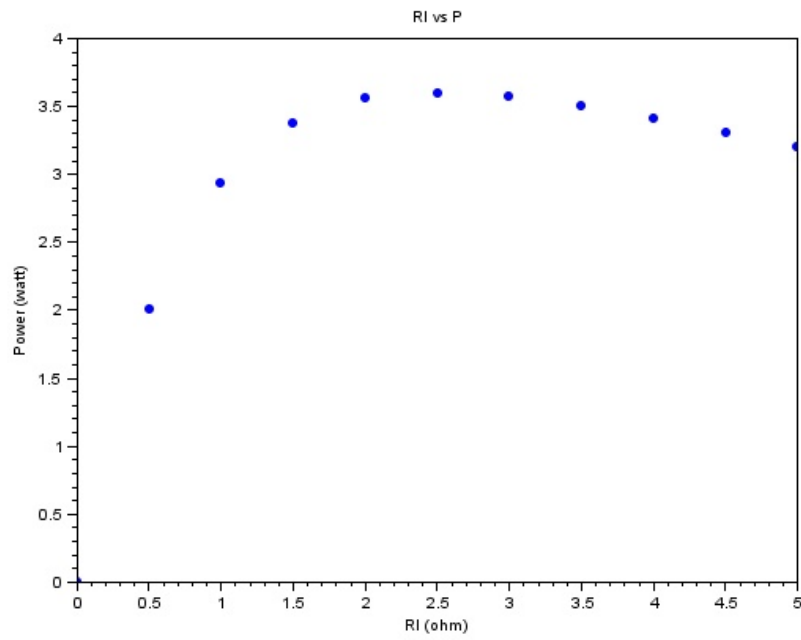


Figure 13.1: Example 22

Scilab code Exa 13.22 Example 22

```
1 //Chapter 13, Problem 22, figure 13.82
2 clc;
3 E=6; //in volt
4 r=2.5; //in ohm
5
6 //defining a function
7 function a = myfunction ( c,d,e)
8 b = c/(d+e);
9 a=b^2*e;
10 endfunction
11
12
13 for Rl=0:0.5:5
14     P=myfunction(E,r,Rl)
15     x=linspace(0,7,12);
16 y=linspace(0,5,12);
17 plot(Rl,P,".");
18 xtitle("Rl vs P", "Rl (ohm)", "Power (watt)");
19 end
20
21 printf("A graph of RL against P is shown\n");
22 printf("i.e. maximum power occurs when RL = R, which
    is what the maximum power transfer theorem
    states.");
```

Scilab code Exa 13.23 Example 23

```
1 //Chapter 13, Problem 23, figure 13.83
2 clc;
3 E=30; //e.m.f source
4 r=1.5; //resistance in ohm
5 Rl=r;
6 I=E/(r+Rl); //current in
```



```

    ampere
7 P=I^2*R1; //power in watt
8 printf("The circuit diagram is shown in Fig. 13.84.\n\n");
9 printf("From the maximum power transfer theorem, for\n\n");
    maximum power dissipation , RL =r\n\n");
10 printf("maximum power dissipated = %f W",P);

```

Scilab code Exa 13.24 Example 24

```

1 //Chapter 13, Problem 24, figure 13.85
2 clc;
3 R1=3; //resistance
    in ohm
4 R2=12; //
    resistance in ohm
5 E=15; //e.m.f
    source
6 E1=(R2/(R1+R2))*E; //p.d in
    volts
7 r=(R1*R2)/(R1+R2); //
    resistance in ohm
8 Rl=r
9 I=E1/(r+R1); //
    current in amperes
10 P=I^2*R1; //power
    in watt
11 printf("(i) Resistance RL is removed from the\n\n");
    circuit as shown in Fig. 13.86(a)\n\n");
12 printf("ii) The p.d. across AB is the same as the p.\n\n");
    d. across the 12 resistor. Hence\n\n");
13 printf("E = %d V\n\n",E1);
14 printf("(iii) Removing the source of e.m.f. gives\n\n");
    the circuit of Fig. 13.86(b), from which,\n\n");
    resistance ,\n\n");

```

```
15 printf("r = %f ohm\n\n",r);
16 printf("(iv) The equivalent Th venin s circuit
    supplying terminalsAB is shown in Fig. 13.86(c),
    from which,\n");
17 printf("For maximum power, RL =r\n");
18 printf("Power, P, dissipated in load RL, = %d W",P);
```

Chapter 14

Alternating voltages and currents

Scilab code Exa 14.1 Example 1

```
1 //Chapter 14, Problem 1
2 clc;
3 f1=50; //frequency in hertz
4 f2=20*10^3; //frequency in hertz
5 T1=1/f1; //time period in sec
6 T2=1/f2; //time period in sec
7 printf("(a) Periodic time T = %f sec\n\n",T1);
8 printf("(b) Periodic time T = %f sec",T2);
```

Scilab code Exa 14.2 Example 2

```
1 //Chapter 14, Problem 2
2 clc;
3 t1=4*10**-3; //time period in sec
4 t2=4*10**-6; //time period in sec
5 f1=1/t1; //frequency in hertz
```

```

6 f2=1/t2;                                     //frequency in hertz
7 printf("(a) Frequency F = %f Hz\n\n",f1);
8 printf("(b) Frequency F = %f KHz",f2/1000);

```

Scilab code Exa 14.3 Example 3

```

1 //Chapter 14, Problem 3
2 clc;
3 c=5;                                         //no of sycle
4 t=8*10**-3;                                 //time period in sec
5 T=t/c;
6 F=1/T;                                       //frequency in hertz
7 printf("Frequency F = %f Hz\n\n",F);

```

Scilab code Exa 14.4 Example 4

```

1 //Chapter 14, Problem 4, Figure 14.5
2 clc;
3 funcprot(0)
4 deff(' [freq]=function1(time)', 'freq=1/time')
5 deff(' [ave]=function2(base, area)', 'ave=area/base')
6 deff(' [rms]=function3(a1, a2, a3, a4)', 'rms=sqrt((a1^2+
    a2^2+a3^2+a4^2)/4)')
7 deff(' [form]=function4(rms, ave)', 'form=rms/ave')
8 deff(' [peak]=function5(max, rms)', 'peak=max/rms')
9
10 //from triangular waveform (Fig. 14.5(a))
11 t=20e-3;
12 b=t/2;
13 h=200;
14 v1=25;
15 v2=75;
16 v3=125;

```

```

17 v4=175;
18 f=function1(t);
19 a=(1/2)*b*h;
20 av=function2(b,a);
21 r=function3(v1,v2,v3,v4);
22 fr=function4(r,av);
23 p=function5(h,r);
24 disp("Triangular waveform")
25 printf("(i) Frequency = %d Hz \n\n",f);
26 printf("(ii) Average value of waveform = %d V\n\n",
    av);
27 printf("(iii) R.m.s value = %f V \n\n",r);
28 printf("(iv) Form factor = %f \n\n",fr);
29 printf("(v) peak factor = %f \n\n\n\n",p);
30
31 //from rectangular waveform (Fig. 14.5(b))
32 t1=16e-3;
33 b1=t1/2
34 i1=10;
35 f1=function1(t1);
36 a1=i1*b1;
37 av1=function2(b1,a1);
38 r1=function3(i1,i1,i1,i1);
39 fr1=function4(r1,av1);
40 p1=function5(i1,r1);
41 disp("Rectangular waveform")
42 printf("(i) Frequency = %f Hz \n\n",f1);
43 printf("(ii) Average value of waveform = %d A\n\n",
    av1);
44 printf("(iii) R.m.s value = %d A \n\n",r1);
45 printf("(iv) Form factor = %d \n\n",fr1);
46 printf("(v) peak factor = %d \n\n",p1);

```

Scilab code Exa 14.6 Example 6

```

1 //Chapter 14, Problem 6
2 clc;
3 I=20; //peak value current
4 Irms=0.707*I; //rms value
5 printf("r.m.s. value of a sinusoidal current = %f A"
, Irms);

```

Scilab code Exa 14.7 Example 7

```

1 //Chapter 14, Problem 7
2 clc;
3 Vrms=240; //rms voltage
4 Vp=Vrms/0.707; //peak voltage
5 Vav=0.637*Vp; //average value of
voltage
6 printf("Peak voltage = %f V\n\n", Vp);
7 printf("Mean value = %f V", Vav);

```

Scilab code Exa 14.8 Example 8

```

1 //Chapter 14, Problem 8
2 clc;
3 Vav=150; //average value of
voltage
4 Vp=Vav/0.637; //peak voltage
5 Vrms=0.707*Vp; //rms voltage
6 printf("Maximum value = %f V\n\n", Vp);
7 printf("r.m.s value = %f V", Vrms);

```

Scilab code Exa 14.9 Example 9

```

1 //Chapter 14, Problem 9
2 clc;
3 //from eqn  $v=282.8(\sin 314 t)$ 
4 Vm=282.8; //peak voltage
5 w=314;
6 t=4e-3;
7 Vrms=0.707*Vm;
8 f=w/(2*%pi);
9 v=282.8*sin(314*t);
10 printf("(a) Comparing Comparing  $v=282.8 \sin 314 t$ 
    with this general expression gives the peak
    voltage as 282.8V\n");
11 printf("v = %f V\n\n",Vrms);
12 printf("(b) Angular velocity w = 314 rad/s,
    therefore\n");
13 printf("f = %f Hz\n\n",f);
14 printf("(c) When t = 4ms\n");
15 printf("v = %f V",v);

```

Scilab code Exa 14.10 Example 10

```

1 //Chapter 14, Problem 10
2 clc;
3 Vm=75; //peak voltage
4 w=200*%pi;
5 phi=0.25;
6 Vpp=2*Vm; //peak to peak
    voltage
7 Vrms=0.707*Vm; //rms voltage
8 T=(2*%pi)/w; //time period
9 f=1/T; //frequency
10 angle=phi*(180/%pi);
11 printf("Comparing  $v=75 \sin((200*\pi*t) - 0.25)$  with
    the general expression, we get\n");
12 printf("(a) Amplitude or peak value = %d V\n\n",Vm);

```

```

13 printf("(b) Peak-to-peak value = %d V\n\n",Vpp);
14 printf("(c) The r.m.s. value = %d V\n\n",Vrms);
15 printf("(d) The periodic time = %f sec\n\n",T);
16 printf("(e) Frequency f = %d Hz\n\n",f);
17 printf("(d) Phase angle = %f deg",angle);

```

Scilab code Exa 14.11 Example 11

```

1 //Chapter 14, Problem 11
2 clc;
3 T=0.01; //time period
4 Vm=40; //peak voltage
5 w=(2*pi)/T;
6 v=-20;
7 phi=asin(v/Vm);
8 printf("instantaneous voltage can be expressed as\n
    v=40*sin((200*pi*t)+phi)");
9 printf("When time t=0, v=-20\n");
10 printf("phi = %d",phi);

```

Scilab code Exa 14.12 Example 12

```

1 //Chapter 14, Problem 12
2 clc;
3 Imax = 120; //current in amperes
4 w = 100*pi; // in rad/sec
5 phi = 0.36; // in rad
6 t1 = 0; // in secs
7 t2 = 0.008; // in secs
8 i = 60; // in amperes
9
10 //calculation:
11 //for a sine wave

```



```

12 f = w/(2*%pi)
13 T = 1/f
14 phid = phi*180/%pi
15 i0 = Imax*sin((w*t1) + phi)
16 i8 = Imax*sin((w*t2)+phi)
17 ti = (asin(i/Imax) - phi)/w
18 tm1 = (asin(Imax/Imax) - phi)/w
19
20 printf("\n (a) Peak value = %.0f A, Periodic time T =
      %.2f sec, Frequency, f = %.0f Hz Phase angle = %
      .1f \n\n", Imax, T, f, phid)
21 printf("\n (b) When t = 0, i = %.1f A\n\n", i0)
22 printf("\n (c) When t = 8 ms = %.1f A\n\n", i8)
23 printf("\n (d) When i is 60 A, then time t = %.2E s\n
      \n", ti)
24 printf("\n (e) When the current is a maximum, time, t
      = %.2E s\n\n", tm1)

```

Chapter 15

Single phase series AC circuits

Scilab code Exa 15.1 Example 1

```
1 //Chapter 15, Problem 1
2 clc;
3 f1=50; //frequency in hertz
4 L1=0.32; //inductance
5 x1=124; //reactance
6 f2=5000; //frequency in hertz
7 X1=2*%pi*f1*L1; //inductive
   reactance
8 L=x1/(2*%pi*f2); //inductance
9 printf("(a) Inductive reactance ,\n Xl = %.1 f ohm\n\n",X1);
10 printf("(d) Inductance ,\n L = %.3 f mH\n\n",L*1000);
```

Scilab code Exa 15.2 Example 2

```
1 //Chapter 15, Problem 2
2 clc;
3 f1=50; //frequency in hertz
```

```

4 L1=40e-3; //inductance
5 V=240; //voltage
6 V2=100; //voltage
7 f2=1000; //frequency in hertz
8 Xl=2*pi*f1*L1; //inductive
   reactance
9 Xl2=2*pi*f2*L1; //inductive
   reactance
10 I=V/Xl; //current
11 I2=V2/Xl2; //current
12 printf("(a) Inductive reactance , Xl = .2%f ohm \
   nCurrent I = %.2f A\n\n",Xl,I);
13 printf("(b) Inductive reactance , Xl = %.1f ohm \
   nCurrent I = %.3f A\n\n",Xl2,I2);

```

Scilab code Exa 15.3 Example 3

```

1 //Chapter 15, Problem 3
2 clc;
3 f=50; //frequency in hertz
4 f2=20e3; //frequency in hertz
5 C=10e-6; //capacitance in
   farad
6 Xc=1/(2*pi*f*C); //capacitive
   reactance
7 Xc2=1/(2*pi*f2*C); //capacitive
   reactance
8 printf("(a) Capacitive reactance Xc = %.1f ohm\n\n",
   Xc);
9 printf("(b) Capacitive reactance Xc = %.3f ohm\n\n",
   Xc2);
10 printf("Hence as the frequency is increased from 50
   Hz to 20 kHz, XC decreases from %.1f to %.3f (see
   Fig. 15.5)",Xc,Xc2);

```

Scilab code Exa 15.4 Example 4

```
1 //Chapter 15, Problem 4
2 clc;
3 f=50; //frequency in hertz
4 Xc=40; //capacitive reactance
5 C=1/(2*%pi*f*Xc); //capacitance in farad
6 printf("Capacitance C = %.2f uF",C*10^6);
```

Scilab code Exa 15.5 Example 5

```
1 //Chapter 15, Problem 5
2 clc;
3 f=50; //frequency in hertz
4 V=240; //voltage
5 C=23e-6; //capacitance
6 Xc=1/(2*%pi*f*C) //capacitive reactance
7 I=V/Xc; //current
8 printf("Current I = %.2f A",I)
```

Scilab code Exa 15.6 Example 6

```
1 //Chapter 15, Problem 6
2 clc;
3 Vr=12; //p.d. across the
    resistance
4 Vl=5; //p.d. across the
    inductance
5 //From the voltage triangle of Fig. 15.6,
```

```

6 V=sqrt(Vr^2+Vl^2);
7 phi=atan(Vl/Vr);
8 printf("Supply voltage V = %d V\n\n",V);
9 printf("Circuit phase angle = %.2f deg (lagging)",
    phi*(180/%pi));

```

Scilab code Exa 15.7 Example 7

```

1 //Chapter 15, Problem 7
2 clc;
3 R=4; //coil resistance
4 L=9.55e-3; //inductance
5 f=50 //frequency in hertz
6 V=240; //supply voltage
7 Xl=2*%pi*f*L; //inductive reactance,
8 Z=sqrt(R^2+Xl^2); //impedance
9 I=V/Z; //current
10 phi=atan(Xl/R);
11 printf("(a) Inductive reactance Xl = %d ohm\n\n",Xl)
    ;
12 printf("(b) Impedance Z = %d ohm\n\n",Z);
13 printf("(c) Current I = %f A\n\n",I);
14 printf("The circuit and phasor diagrams and the
    voltage and impedance triangles are as shown in
    Fig. 15.6\n");
15 printf("phi = %f lagging",phi*(180/%pi));

```

Scilab code Exa 15.8 Example 8

```

1 //Chapter 16, Problem 8
2 clc;
3 L=0.20; //inductance
4 R=60; //resistance

```

```

5 C=20e-6; //capacitance
6 V=20; //supply voltage
7 fr=(2*%pi)^-1*sqrt((1/(L*C))-(R^2/L^2));
8 Xl=2*%pi*fr*L; //inductive reactance
9 Rd=L/(R*C);
10 Ir=V/Rd;
11 Q=Xl/R;
12 printf("(a) Resonant frequency of the circuit = %f
    Hz\n\n",fr);
13 printf("(b) Dynamic resistance Rd = %f ohm\n\n",Rd);
14 printf("(c) Current at resonance Ir = %f A\n\n",Ir);
15 printf("(d) Q factor of circuit = %f",Q);

```

Scilab code Exa 15.9 Example 9

```

1 //Chapter 15, Problem 9
2 clc;
3 L=318.3e-3; //inductance
4 R=200; //resistance
5 V=240; //supply voltage
6 f=50; //frequency in hertz
7 Xl=2*%pi*f*L; //inductive reactance,
8 Z=sqrt(R^2+Xl^2); //impedance
9 I=V/Z;
10 Vl=I*Xl;
11 Vr=I*R;
12 phi=atan(Xl/R);
13 printf("(a) Inductive reactance = %f ohm\n\n",Xl);
14 printf("(b) Impedance Z = %.1f ohm\n\n",Z);
15 printf("(c) Current I = %.3f A\n\n",I);
16 printf("(d) The p.d. across the coil = %1f V\n\n",Vl
    );
17 printf(" The p.d. across the resistor = %.1f V\n
    \n",Vr);
18 printf("(e) From the impedance triangle, angle = %f

```

```
deg (lagging)\n\n",phi*(180/%pi));
```

Scilab code Exa 15.10 Example 10

```
1 //Chapter 15, Problem 10
2 clc;
3 //from eqn v=200 (sin 500t)
4 Vm=200;
5 w=500;
6 V=0.707*200;
7 L=200e-3; //inductance
8 R=100; //resistance
9 Xl=w*L; //inductive reactance
10 Z=sqrt(R^2+Xl^2); //impedance
11 I=V/Z;
12 Vl=I*Xl;
13 Vr=I*R;
14 phi=atan(Xl/R);
15 printf("(a) Inductive reactance = %d ohm\n\n",Xl);
16 printf("(b) Impedance Z = %.1 f ohm\n\n",Z);
17 printf("(c) Current I = %f A\n\n",I);
18 printf("(d) The p.d. across the coil = %f V\n\n",Vl)
    ;
19 printf(" The p.d. across the resistor = %f V\n\n
    ",Vr);
20 printf("(e) Phase angle between voltage and current
    is given by,\n angle = %d deg\n\n",phi*(180/%pi))
    ;
```

Scilab code Exa 15.11 Example 11

```
1 //Chapter 15, Problem 11
2 clc;
```

```

3 L=1.273e-3;           //inductance
4 Vr=6;                //pd across resistor
5 R=30;                //resistor
6 f=5e3;               //frequency in hertz
7 I=Vr/R;              //current
8 Xl=2*%pi*f*L;        //inductive reactance
9 Z=sqrt(R^2+Xl^2);    //impedance
10 V=I*Z;               //supply voltage
11 Vl=I*Xl;            //voltage across inductor
12 printf("From circuit in Fig. 15.7(a)\n\n");
13 printf("Supply voltage V = %f V\n\n",V);
14 printf("Voltage across the 1.273mH inductance Vl =
    %f V\n\n",Vl);
15 printf("The phasor diagram is shown in Fig. 15.7(b)"
    );

```

Scilab code Exa 15.12 Example 12

```

1 //Chapter 15, Problem 12
2 clc;
3 L=159.2e-3;          //inductance in henry
4 Rc=20;               //resistance in ohm
5 R1=60;               //resistance in ohm
6 f=50;                //frequency in hertz
7 V=240;               //supply voltage
8 R=Rc+R1;
9 Xl=2*%pi*f*L;        //inductive reactance
10 Z=sqrt(R^2+Xl^2);   //impedance
11 I=V/Z;
12 phi=atan(Xl/R);
13 Vr=I*R1;
14 Zcoil=sqrt(Rc^2+Xl^2);
15 Vcoil=I*Zcoil;
16 Vl=I*Xl;
17 Vrcoil=I*Rc;

```



```

18 printf("(a) Circuit impedance , Z = %.2 f ohm\n\n",Z);
19 printf("(b) Circuit current , I = %.3 f A\n\n",I);
20 printf("(c) Circuit phase angle , phi = %d deg
    Lagging\n\n",phi*(180/%pi));
21 printf("From Fig. 15.8(a):\n\n");
22 printf("p.d. across the 60ohm resistor , Vr = %.1 f V\
n\n",Vr);
23 printf("p.d. across the coil , Vcoil = %.1 f V\n\n",
    Vcoil);
24 printf("The 240V supply voltage is the phasor sum of
    VCOIL and VR as shown in the phasor diagram in
    Fig. 15.9");
25 printf("From circuit in Fig. 15.8(a)\n\n");

```

Scilab code Exa 15.13 Example 13

```

1 //Chapter 15, Problem 13
2 clc;
3 R=25; //resistance in ohm
4 C=45e-6; //capacitance in farad
5 V=240; //supply voltage
6 f=50; //supply frequency
7 Xc=1/(2*%pi*f*C); //capacitive reactance
8 Z=sqrt(R^2+Xc^2); //impedance
9 I=V/Z; //current
10 a=atan(Xc/R);
11 printf("(a) Impedance , Z = %.2 f ohm\n\n",Z);
12 printf("(b) Current , I = %.2 f A\n\n",I);
13 printf("Phase angle between the supply voltage and
    current , = %.2 f deg (leading)\n\n",a*(180/%pi));

```

Scilab code Exa 15.14 Example 14

```

1 //Chapter 15, Problem 14
2 clc;
3 I=3;
4 Z=50; //impedance
5 R=40; //resistance in
        ohm
6 f=60; //supply
        frequency
7 Xc=sqrt(Z^2-R^2); //capacitive
        reactance
8 C=1/(2*%pi*f*Xc); //capacitance in
        farad
9 V=I*Z; //voltage
10 a=atan(Xc/R);
11 Vr=I*R;
12 Vc=I*Xc;
13 printf("(a) Capacitance , C = %.2f uF\n\n",C*10^6);
14 printf("(b) Supply voltage V = %d V\n\n",V);
15 printf("(c) Phase angle between the supply voltage
        and current , = %.2f deg (leading)\n\n",a*(180/%pi
        ));
16 printf("(d) p.d. across resistor , Vr = %d V\n\n",Vr)
        ;
17 printf("p.d. across the capacitor , Vc = %d V\n\n",Vc
        );
18 printf("The phasor diagram is shown in Fig. 15.11,
        where the supply voltage V is the phasor sum of
        VR and VC.");

```

Scilab code Exa 15.15 Example 15

```

1 //Chapter 15, Problem 15, Fig 15.13
2 clc;
3 R=5; //resistance in
        ohm

```

```

4 L=120e-3; //inductance in
    henry
5 C=100e-6; //capacitance in
    farad
6 V=300; //supply voltage
7 f=50; //supply
    frequency
8 Xl=2*%pi*f*L; //inductive
    reactance
9 Xc=1/(2*%pi*f*C); //capacitive
    reactance
10 X=Xl-Xc;
11 Z=sqrt(R^2+X^2); //impedance
12 I=V/Z; //current
13 phi=atan(X/R);
14 Zcoil=sqrt(R^2+Xl^2); //impedance of
    coil
15 Vcoil=I*Zcoil; //voltage
    across coil
16 phi2=atan(Xl/R);
17 Vc=I*Xc; //voltage
    across capacitor
18 printf("(a) Current , I = %f A\n\n",I);
19 printf("(b) Phase angle = %f deg (leading)\n\n",phi
    *(180/%pi));
20 printf("(c) Phase angle of coil = %f deg (lagging)\n
    \n",phi2*(180/%pi));
21 printf("(d) Voltage across capacitor , Vc = %f V\n\n"
    ,Vc);
22 printf("The phasor diagram is shown in Fig. 15.14.
    The supply voltage V is the phasor sum of VCOIL
    and VC.");

```

Scilab code Exa 15.16 Example 16

```

1 //Chapter 15, Problem 16, Fig 15.16
2 clc;
3 V=40; //supply voltage
4 f=20e3; //supply
    frequency
5 R1=8; //resistance in
    ohm
6 L=130e-6; //inductance in
    henry
7 R2=5; //resistance in
    ohm
8 R3=10;
9 C=0.25e-6; //capacitance
    in farad
10 Re=R1+R2+R3; //eqv
    resistance
11 Xl=2*%pi*f*L; //inductive
    reactance
12 Xc=1/(2*%pi*f*C); //capacitive
    reactance
13 X=Xc-Xl;
14 Z=sqrt(Re^2+X^2); //impedance
15 I=V/Z; //current
16 phi=atan(X/Re);
17 Z2=sqrt(R2^2+Xl^2);
18 Z3=sqrt(R3^2+Xc^2);
19 V1=I*R1;
20 V2=I*Z2;
21 V3=I*Z3;
22 printf("(a) Current , I = %.3f A\n\n",I);
23 printf("Phase angle = %.2f deg (leading)\n\n",phi
    *(180/%pi));
24 printf("V1 = %.2f V\n\nV2 = %.2fV\n\nV3 = %.2fV",V1,
    V2,V3)

```

Scilab code Exa 15.17 Example 17

```
1 //Chapter 15, Problem 17, Fig 15.17
2 clc;
3 R1=4; //resistance in
   ohm
4 R2=8; //resistance in
   ohm
5 I=5; //current in
   ampere
6 f=5000; //supply
   frequency
7 L=0.286e-3; //inductance
   in henry
8 C=1.273e-6; //capacitance
   in farad
9 Xl=2*%pi*f*L; //inductive
   reactance
10 Z1=sqrt(R1^2+Xl^2);
11 V1=I*Z1;
12 phi=atan(Xl/R1);
13 Xc=1/(2*%pi*f*C); //capacitive
   reactance
14 Z2=sqrt(R2^2+Xc^2);
15 V2=I*Z2;
16 phi2=atan(Xc/R2);
17 printf("Phase angle 1, phi = %.2f deg (lagging)\n\n"
   ,phi*(180/%pi));
18 printf("Phase angle 2, phi2 = %.2f deg (leading)\n\n"
   ",phi2*(180/%pi));
19 printf("The phasor diagram is shown in Fig. 15.18");
```

Scilab code Exa 15.18 Example 18

```
1 //Chapter 15, Problem 18
```

```

2  clc;
3  R=10;           //resistance in
    ohm
4  L=125e-3;      //inductance in
    henry
5  C=60e-6;      //capacitance in
    farad
6  V=120;        //supply voltage
7  fr=1/(2*%pi*sqrt(L*C)); //resonant
    frequency
8  I=V/R;
9  printf("Frequency F at which resonance occur = %.2 f
    Hz\n\n",fr);
10 printf("Current I flowing at the resonant frequency
    = %d A",I);

```

Scilab code Exa 15.19 Example 19

```

1  //Chapter 15, Problem 19
2  clc;
3  I=100e-6;
4  V=2e-3;       //supply
    voltage
5  f=200e3;     //frequency
6  L=50e-6;     //inductance
    in henry
7  R=V/I;       //
    resistance in ohm
8  C=1/((2*%pi*f)^2*L); //
    capacitance in farad
9  printf("(a) Circuit resistance , R = %d ohm\n\n",R);
10 printf("(b) Circuit capacitance , C = %.1 f nF\n\n",C
    *10^9);

```

Scilab code Exa 15.20 Example 20

```
1 //Chapter 15, Problem 20
2 clc;
3 L=80e-3; //inductance in
   henry
4 C=0.25e-6; //capacitance
   in farad
5 R=12.5; //resistance in
   ohm
6 V=100; //supply voltage
7 fr=1/(2*%pi*sqrt(L*C)); //resonant
   frequency
8 I=V/R;
9 Vl=I*2*%pi*fr*L;
10 Vc=I*1/(2*%pi*fr*C);
11 Vm=Vl/V;
12 printf("(a) Resonant frequency = %.1f Hz\n\n",fr);
13 printf("(b) Current at resonance = %d A\n\n",I);
14 printf(" Q-factor of the circuit = %.3f",Vm);
```

Scilab code Exa 15.21 Example 21

```
1 //Chapter 15, Problem 21
2 clc;
3 R=2; //resistance in ohm
4 L=60e-3; //inductance in
   henry
5 C=30e-6; //capacitance in
   farad
6 Q=(1/R)*sqrt(L/C); //Q factor
7 printf("Q factor = %f ",Q);
```

Scilab code Exa 15.22 Example 22

```
1 //Chapter 15, Problem 22
2 clc;
3 R=10; //resistance in
   ohm
4 L=100e-3; //inductance in
   henry
5 C=2e-6; //capacitance in
   farad
6 V=50; //voltage
7 fr=1/(2*%pi*sqrt(L*C)); //resonant
   frequency
8 I=V/R; //current
9 Vl=I*2*%pi*fr*L; //voltage across
   coil at resonance
10 Vc=I*1/(2*%pi*fr*C); //voltage across
   capacitance at resonance
11 Vm=Vl/V;
12 printf("(a) Resonant frequency = %.1f Hz\n\n",fr);
13 printf("(b) Current at resonance = %d A\n\n",I);
14 printf("(c) Voltages across the coil and the
   capacitor at resonance\n Vl = %d V\nVc = %d V\n\n
   ",Vl,Vc);
15 printf("(d)Q-factor of the circuit = %.2f",Vm);
```

Scilab code Exa 15.23 Example 23

```
1 //Chapter 15, Problem 23
2 clc;
3 R=10; //resistance in
   ohm
```



```

4 L=20e-3; //inductance in
    henry
5 f=5000; //resonant
    frequency
6 w=2*%pi*f;
7 Qr=(w*L)/R; //Q-factor at
    resonance
8 B=f/Qr; //bandwidth
9 printf("Bandwidth of the filter = %.2f Hz",B);

```

Scilab code Exa 15.24 Example 24

```

1 //Chapter 15, Problem 24
2 clc;
3 //from eqn  $i=250 \sin t$ 
4 Im=0.250;
5 R=5000; //resistance in ohm
6 I=Im*0.707; //rms current
7 P=R*I^2; //power
8 printf("Power dissipated in the resistor = %.1f W",P
    );

```

Scilab code Exa 15.25 Example 25

```

1 //Chapter 15, Problem 25
2 clc;
3 L=75e-3; //inductance in
    henry
4 R=60; //resistance in ohm
5 V=110; //voltage
6 f=60; //frequency
7 Xl=2*%pi*f*L; //inductive
    reactance

```

```

8 Z=sqrt(R^2+Xl^2);           //impedance
9 I=V/Z;                     //current
10 P=I^2*R;                  //power
11 printf("Power dissipated = %d W",P);

```

Scilab code Exa 15.26 Example 26

```

1 //Chapter 15, Problem 26
2 clc;
3 V=150;                     //voltage
4 f=50;                      //frequency
5 S=300;                     //apparent power
6 I=S/V;                    //current
7 Xl=V/I;                   //inductive reactance
8 L=(Xl/(2*pi*f));         //inductance in henry
9 printf("Inductance L = %.3 f H",L);

```

Scilab code Exa 15.27 Example 27

```

1 //Chapter 15, Problem 27
2 clc;
3 pf=0.8;                    //power factor
4 phi=acos(0.8);
5 VI=200e3;                 //power
6 P=VI*pf;
7 Q=VI*sin(phi);           //reactive power
8 printf("Power output P = %d kW\n\n",P/1000);
9 printf("Reactive power Q = %d Kvar",Q/1000);

```

Scilab code Exa 15.28 Example 28

```

1 //Chapter 15, Problem 28
2 clc;
3 P=90*103; //power
4 pf=0.5; //power factor
5 S=P/pf; //apparent power
6 phi=acos(pf);
7 Q=S*sin(phi); //reactive power
8 printf("Reactive power = %.1f Kvar",Q/1000);

```

Scilab code Exa 15.29 Example 29

```

1 //Chapter 15, Problem 29
2 clc;
3 V=120; //voltage
4 f=50; //frequency in
   hertz
5 P=400; //power in watt
6 I=8; //current in
   ampere
7 R=P/I2; //resistance in
   ohm
8 Z=V/I; //impedance
9 Xl=sqrt(Z2-R2); //inductive
   reactance
10 pf=P/(V*I); //power factor
11 phi=acos(pf);
12 printf("(a) Resistance R = %.2f ohm\n\n",R);
13 printf("(b) Impedance Z = %d ohm\n\n",Z);
14 printf("(c) Reactance = %.2f ohm\n\n",Xl);
15 printf("(d) Power factor = %.4f\n\n",pf);
16 printf("(e) Phase angle = %.2f deg (lagging)\n\n",
   phi*(180/%pi));

```

Scilab code Exa 15.30 Example 30

```
1 //Chapter 15, Problem 30
2 clc;
3 V=100; //voltage
4 f=60; //frequency in
    hertz
5 P=100; //power in watt
6 pf=0.5; //power factor
7 I=P/(pf*V); //current in ampere
8 R=P/I^2; //resistance in
    ohm
9 Z=V/I; //impedance
10 Xc=sqrt(Z^2-R^2); //capacitive
    reactance
11 C=1/(2*%pi*f*Xc); //capacitance
12 phi=acos(pf);
13 printf("(a) Current I = %d A\n\n",I);
14 printf("(b) Phase angle = %d deg (leading)\n\n",phi
    *(180/%pi));
15 printf("(c) Resistance R = %d ohm\n\n",R);
16 printf("(d) Impedance Z = %d\n\n",Z);
17 printf("(e) Capacitance C = %.2f uF\n\n",C*10^6);
```

Chapter 16

Single phase parallel AC circuits

Scilab code Exa 16.1 Example 1

```
1 //Chapter 16, Problem 1
2 clc;
3 V=60; //voltage
4 R=20; //resistance in ohm
5 f=1000; //frequency in hertz
6 L=2.387e-3; //inductance in
   henry
7 Ir=V/R; //current flowing in
   the resistor
8 Xl=2*%pi*f*L; //inductive
   reactance
9 Il=V/Xl; //current flowing in
   the inductance
10 I=sqrt(Ir^2+Il^2); //supply current
   from phasor diagram fig 16.1
11 phi=atan(Il/Ir);
12 Z=V/I; //impedance
13 P=V*I*cos(phi); //power consumed
14 printf("(a) Current flowing in the resistor = %d A\
```

```

    n\tCurrent flowing in the inductance = %d A\n\n",
    Ir,Il);
15 printf("(b) Supply current = %d A\n\n",I);
16 printf("(c) Circuit phase angle = %.2f deg (lagging)
    \n\n",phi*(180/%pi));
17 printf("(d) Circuit impedance = %.1f ohm\n\n",Z);
18 printf("(e) Power consumed = %d W",P);

```

Scilab code Exa 16.2 Example 2

```

1 //Chapter 16, Problem 2
2 clc;
3 V=240; //voltage
4 R=80; //resistance in ohm
5 f=50; //frequency in hertz
6 C=30e-6; //capacitance in farad
7 Ir=V/R; //current flowing in
    the resistor
8 Xc=1/(2*%pi*f*C); //capacitive
    reactance
9 Ic=V/Xc; //current flowing in
    the capacitor
10 I=sqrt(Ir^2+Ic^2); //supply current
11 phi=atan(Ic/Ir);
12 Z=V/I; //impedance
13 P=V*I*cos(phi); //power consumed
14 S=V*I; //apparent power
,
15 printf("(a) Current flowing in the resistor = %d A\
    n\tCurrent flowing in the capacitor = %.3f A\n\n"
    ,Ir,Ic);
16 printf("(b) Supply current = %.3f A\n\n",I);
17 printf("(c) Circuit phase angle = %.2f deg (leading)
    \n\n",phi*(180/%pi));
18 printf("(d) Circuit impedance = %.2f ohm\n\n",Z);

```

```
19 printf("(e) Power consumed = %d W\n\n",P);
20 printf("(f) Apparent power = %.1f VA",S);
```

Scilab code Exa 16.3 Example 3

```
1 //Chapter 16, Problem 3, Fig. 16.3
2 clc;
3 V=120; //voltage
4 f=200; //frequency in
    hertz
5 I=2; //supply current
6 pf=0.6; //power factor
7 phi=acos(pf);
8 Ir=I*pf; //current flowing in
    the resistor
9 Ic=I*sin(phi); //current
    flowing in the capacitor
10 R=V/Ir; //resistance in
    ohm
11 C=Ic/(2*pi*f*V); //capacitance in
    faradd
12 printf("Capacitance of capacitor = %f uF\n\n",C
    *10^6);
13 printf("Resistance of resistor = %f ohm\n\n",R);
```

Scilab code Exa 16.4 Example 4

```
1 //Chapter 16, Problem 4
2 clc;
3 L=120e-3; //inductance in henry
4 C=25e-6; //capacitance in farad
5 V=100; //voltage
6 f=50; //frequency in hertz
```

```

7 Xl=2*%pi*f*L;           //inductive
   reactance
8 Xc=1/(2*%pi*f*C);      //capacitive
   reactance
9 Il=V/Xl;               //current flowing in
   the inductance
10 Ic=V/Xc;              //current flowing in
   the capacitor
11 I=Il-Ic;
12 Z=V/I;
13 P=V*I*cos(90*%pi/180);
14 printf("(a) Branch current ,\n Il = %.3f A\nIc = %.3f
   A\n\n",Il,Ic);
15 printf("(b) Supply current = %.3f A\nCurrent lags
   the supply voltage V by 90deg from Fig 16.4(i)",I
   );
16 printf("(c) Circuit impedance Z = %.3f ohm\n\n",Z);
17 printf("(d) Power consumed P = %d W",P);

```

Scilab code Exa 16.5 Example 5

```

1 //Chapter 16, Problem 5
2 clc;
3 L=120e-3;              //inductance in henry
4 C=25e-6;              //capacitance in farad
5 V=100;                //voltage
6 f=150;                //frequency in hertz
7 Xl=2*%pi*f*L;        //inductive
   reactance
8 Xc=1/(2*%pi*f*C);    //capacitive
   reactance
9 Il=V/Xl;             //current flowing in
   the inductor
10 Ic=V/Xc;            //current flowing in
   the capacitor

```



```

11 I=Ic-I1;
12 Z=V/I;
13 P=V*I*cos(90*%pi/180);
14 printf("(a) Branch current,\n I1 = %.3f A\nIc = %.3f
      A\n\n",I1,Ic);
15 printf("(b) Supply current = %.3f A\nCurrent lags
      the supply voltage V by 90deg from Fig 16.4(i)",I
      );
16 printf("(c) Circuit impedance Z = %.3f ohm\n\n",Z);
17 printf("(d) Power consumed P = %d W",P);

```

Scilab code Exa 16.6 Example 6

```

1 //Chapter 16, Problem 6, Fig.16.6
2 clc;
3 L=159.2e-3; //inductance in henry
4 R=40; //resistance in ohm
5 C=30e-6; //capacitance in
      farad
6 V=240; //voltage
7 f=50; //frequency
8 Xl=2*%pi*f*L; //inductive
      reactance
9 Z1=sqrt(R^2+Xl^2);
10 Ilr=V/Z1;
11 phi1=atan(Xl/R);
12 Xc=1/(2*%pi*f*C); //capacitive
      reactance
13 Ic=V/Xc;
14 Ih=Ilr*cos(51.34*%pi/180);
15 a=-Ilr*sin(51.34*%pi/180);
16 b=Ic*sin(90*%pi/180);
17 Iv=a+b;
18 I=sqrt(Ih^2+(Iv)^2);
19 phi2=atan(-Iv/Ih);

```

```

20 Z=V/I;                                     //impedance
21 P=V*I*cos(phi2);
22 S=V*I;                                     //apparent power
23 Q=V*I*sin(phi2);                           //reactive power
24 printf("(a) Current in coil = %f A\n Phase angle =
    %f deg (lagging)\n\n",Ilr,phi1*180/%pi);
25 printf("(b) Current in capacitor , Ic = %f A\n A
    leading the supply voltage by 90deg\n\n",Ic);
26 printf("(c) Supply current I = %f A\n phase angle =
    %f deg (lagging)\n\n",I,phi2*180/%pi);
27 printf("(d) Circuit impedance Z = %f ohm\n\n",Z);
28 printf("(e) Power consumed P = %f W\n\n",P);

```

Scilab code Exa 16.7 Example 7

```

1 //Chapter 16, Problem 7, Fig.16.8
2 clc;
3 L=0.12;                                     //inductance in henry
4 R=3000;                                     //resistance in ohm
5 C=0.02e-6;                                 //capacitance in
    farad
6 V=40;                                       //voltage
7 f=5000;                                    //frequency
8 Xl=2*%pi*f*L;                              //inductive reactance
9 Z1=sqrt(R^2+Xl^2);
10 Ilr=V/Z1;
11 phi1=atan(Xl/R);
12 Xc=1/(2*%pi*f*C);                          //capacitive
    reactance
13 Ic=V/Xc;
14 Ih=Ilr*cos(51.34*%pi/180);
15 a=-Ilr*sin(51.34*%pi/180);
16 b=Ic*sin(90*%pi/180);
17 Iv=a+b;
18 I=sqrt(Ih^2+(Iv)^2);

```

```

19 phi2=atan(-Iv/Ih);
20 Z=V/I; //impedance
21 P=V*I*cos(phi2);
22 S=V*I; //apparent power
23 Q=V*I*sin(phi2); //reactive power
24 printf("(a) Current in coil = %.3f mA\n Phase angle
    = %.3f deg (lagging)\n\n",Ilr*1000,phi1*180/%pi);
25 printf("(b) Current in capacitor, Ic = %.3f mA\n A
    leading the supply voltage by 90deg\n\n",Ic*1000)
    ;
26 printf("(c) Supply current I = %.3f mA\n phase angle
    = %.3f deg \n\n",I*1000,-phi2*180/%pi);
27 printf("(d) Circuit impedance Z = %.3f Kohm\n\n",Z
    /1000);
28 printf("(e) Power consumed P = %.3f mW\n\n",P*1000);

```

Scilab code Exa 16.8 Example 8

```

1 //Chapter 16, Problem 8
2 clc;
3 L=150e-3; //inductance in henry
4 C=40e-6; //capacitance in farad
5 V=50; //voltage
6 fr=(2*%pi)^-1*sqrt(1/(L*C)); //resonant frequency
7 Xc=1/(2*%pi*fr*C); //capacitive
    reactance
8 Icir=V/Xc; //current
    circulating in L and C at resonance
9 printf("(a) Resonant frequency of the circuit = %.3f
    Hz\n\n",fr);
10 printf("(b) Current circulating in the capacitor and
    inductance at resonance = %.3f A",Icir);

```

Scilab code Exa 16.9 Example 9

```
1 //Chapter 16, Problem 9
2 clc;
3 L=0.20; //inductance in henry
4 R=60; //resistance in ohm
5 C=20e-6; //capacitance in farad
6 V=20; //voltage
7 fr=(2*%pi)^-1*sqrt((1/(L*C))-(R^2/L^2));
8 Xl=2*%pi*fr*L; //inductive reactance
9 Rd=L/(R*C); //dynamic resistance
10 Ir=V/Rd; //current at
    resonance
11 Q=Xl/R; //circuit Q-factor
    at resonance
12 printf("(a) Resonant frequency of the circuit = %.2f
    Hz\n\n",fr);
13 printf("(b) Dynamic resistance Rd = %.2f ohm\n\n",Rd
    );
14 printf("(c) Current at resonance Ir = %.2f A\n\n",Ir
    );
15 printf("(d) Q factor of circuit = %.2f",Q);
```

Scilab code Exa 16.10 Example 10

```
1 //Chapter 16, Problem 10
2 clc;
3 L=100e-3; //inductance in henry
4 R=800; //resistance in ohm
5 f=5000; //frequency
6 V=12; //voltage
7 w=2*%pi*f;
8 C=(L*(w^2+(R^2/L^2)))^-1; //capacitance in
    farad
9 Xl=2*%pi*f*L; //inductive reactance
```

```

10 Rd=L/(R*C); //dynamic resistance
11 Ir=V/Rd; //current at
    resonance
12 Q=Xl/R; //circuit Q-factor
    at resonance
13 printf("(a) capacitance of the capacitor , = %f uF\n\n",C*10^6);
14 printf("(b) Dynamic resistance Rd = %.2f k.ohm\n\n",
    Rd/1000);
15 printf("(c) supply current Ir = %.3f mA\n\n",Ir
    *1000);
16 printf("(d) Q factor of circuit = %.2f",Q);

```

Scilab code Exa 16.11 Example 11

```

1 //Chapter 16, Problem 11, Fig 16.13(a)
2 clc;
3 f = 50; // in ohm
4 V = 240; // in Volts
5 pf = 0.6 // power factor
6 Im = 50; // in amperes
7
8 //calculation:
9 phi = acos(pf)
10 phid = phi*180/%pi
11 Ic = Im*sin(phi)
12 I = Im*cos(phi)
13 printf("\n\n (a)The capacitor current Ic must be %.0
    f A for the power factor to be unity. ",Ic)
14 printf("\n\n (b)Supply current I = %.0f A ",I)

```

Scilab code Exa 16.13 Example 13

```

1 //Chapter 16, Problem 13
2 clc;
3 eff = 0.8; // efficiency
4 f = 50; // in ohm
5 Pout = 4800; // in Watt
6 pf1 = 0.625 // power factor
7 pf2 = 0.95 // power factor
8 V = 240; // in Volts
9 //calculation:
10 Pin = Pout/eff
11 Im = Pin/(V*pf1)
12 phi1 = acos(pf1)
13 phi1d = phi1*180/%pi
14 //When a capacitor C is connected in parallel with
    the motor a current Ic flows which leads V by 90
    .
15 phi2 = acos(pf2)
16 phi2d = phi2*180/%pi
17 Imh = Im*cos(phi1)
18 //Ih = I*cos(phi2)
19 Ih = Imh
20 I = Ih/cos(phi2)
21 Imv = Im*sin(phi1)
22 Iv = I*sin(phi2)
23 Ic = Imv - Iv
24 C = Ic/(2*%pi*f*V)
25 kvar = V*Ic/1000
26 printf("\\n\\n (a)Current taken by the motor, Im = %.0
    f A",Im)
27 printf("\\n\\n (b)Supply current after p.f. correction
    , I = %.2f A ",I)
28 printf("\\n\\n (c)Magnitude of the capacitor current
    Ic = %.0f A",Ic)
29 printf("\\n\\n (d)Capacitance , C = %.0f F ",(C/1E-6)
    )
30 printf("\\n\\n (d)kvar rating of the capacitor = %.2f
    kvar ",kvar)

```

Chapter 17

Filter networks

Scilab code Exa 17.1 Example 1

```
1 //Chapter 17, Problem 1, Figure 17.8
2 clc;
3 L=200*10^-3; //inductance in henry
4 C=0.2*10^-6; //capacitance in farad
5 fc=1/(%pi*sqrt(L*C)); //cut-off frequency
6 R0=sqrt(L/C); //nominal impedance
7
8 disp("Comparing Fig. 17.8 with the low-pass section
9 of Fig. 17.7(a),");
9 printf("Inductance L = %f H\n\n",L);
10 printf("Capacitance C = %f uF\n\n",C*10^6);
11 printf("Cut off frequency fc = %f KHz\n\n",fc/1000 )
12 ;
12 printf("Nominal impedance R0 = %f Kohm\n\n",R0/1000)
13 ;
```

Scilab code Exa 17.2 Example 2

```

1 //Chapter 17, Problem 2, Figure 17.9
2 clc;
3 C=2*200*10^-12;           //capacitance in
   farad
4 L=0.4;                   //inductance in
   henry
5 fc=1/(%pi*sqrt(L*C));    //cut-off frequency
6 R0=sqrt(L/C);           //nominal impedance
7 disp("Comparing Fig. 17.9 with the low-pass section
   of Fig. 17.7(a),");
8 printf("Inductance L = %f H\n\n",L);
9 printf("Capacitance C = %f pF\n\n",C*10^12);
10 printf("Cut off frequency fc = %.2f KHz\n\n",fc/1000
   );
11 printf("Nominal impedance R0 = %.2f Kohm\n\n",R0
   /1000);

```

Scilab code Exa 17.3 Example 3

```

1 //Chapter 17, Problem 3
2 clc;
3 R0=600;                   //nominal impedance
4 fc=5*10^6;               //cut-off frequency
5 C=1/(%pi*R0*fc);        //capacitance in farad
6 L=R0/(%pi*fc);          //inductance in henry
7 printf("Inductance L = %d uH\n\n",L*10^6);
8 printf("Capacitance C = %d pF\n\n",C*10^12);
9 printf("A low-pass T-section filter is shown in Fig.
   17.10(a),\n\n");
10 printf("A low-pass pi-section filter is shown in Fig.
   17.10(b),\n\n");

```

Scilab code Exa 17.4 Example 4


```

1 //Chapter 17, Problem 4, Figure 17.17
2 clc;
3 C=(0.2*10^-6)/2;           //capacitance in
   farad
4 L=100*10^-3;             //inductance in
   henry
5 fc=1/(4*pi*sqrt(L*C));   //cut-off frequency
6 R0=sqrt(L/C);           //nominal
   impedance
7 disp("Comparing Fig. 17.17 with the low-pass section
   of Fig. 17.16(a),");
8 printf("Inductance L = %f H\n\n",L);
9 printf("Capacitance C = %f uF\n\n",C*10^6);
10 printf("Cut off frequency fc = %.1f Hz\n\n",fc );
11 printf("Nominal impedance R0 = %d Kohm\n\n",R0/1000)
   ;

```

Scilab code Exa 17.5 Example 5

```

1 //Chapter 17, Problem 5, Figure 17.18
2 clc;
3 L=(200*10^-6)/2;         //inductance in
   henry
4 C=4000*10^-12;          //capacitance in
   farad
5 fc=1/(4*pi*sqrt(L*C));   //cut-off frequency
6 R0=sqrt(L/C);           //nominal impedance
7 disp("Comparing Fig. 17.18 with the low-pass section
   of Fig. 17.16(b),");
8 printf("Inductance L = %f H\n\n",L);
9 printf("Capacitance C = %f uF\n\n",C*10^6);
10 printf("Cut off frequency fc = %d KHz\n\n",fc/1000 )
   ;
11 printf("Nominal impedance R0 = %d ohm\n\n",R0);

```

Scilab code Exa 17.6 Example 6

```
1 //Chapter 17, Problem 6
2 clc;
3 fc=25*10^3; //cut-off
   frequency
4 R0=600; //nominal
   impedance
5 C=1/(4*pi*R0*fc); //capacitance
   in farad
6 L=R0/(4*pi*fc); //inductance
   in henry
7 printf("Inductance L = %f mH\n\n",L*10^3);
8 printf("Capacitance C = %f pF\n\n",C*10^12);
9 printf("A high-pass T-section filter is shown in Fig.
   17.19(a),\n\n");
10 printf("A high-pass pi-section filter is shown in Fig
   . 17.19(b),\n\n");
```

Scilab code Exa 17.7 Example 7

```
1 //Chapter 17, Problem 7
2 clc;
3 R0=600; //nominal
   impedance
4 fcl=15000; //cut-off
   frequency of low pass
5 fch=10000; //cut-off
   frequency of high pass
6 C1=1/(pi*R0*fcl); //capacitance
   in farad
```

```

7 L1=R0/(%pi*fcl); //inductance
  in henry
8 C2=1/(4*%pi*R0*fch); //capacitance
  in farad
9 L2=R0/(4*%pi*fch); //inductance
  in henry
10 disp("Thus, from Fig. 17.7(a), the series arm
    inductances are each L/2");
11 printf("the series arm inductances L/2 = %f mH\n", (
    L1/2)*10^3);
12 printf("and the shunt arm capacitance = %f nF\n\n",
    C1*10^9);
13 disp("Thus, from Fig. 17.16(a), the series arm
    capacitances are each 2C");
14 printf("the series arm capacitances 2C = %f nF\n", 2*
    C2*10^9);
15 printf("and the shunt arm inductance = %f mH\n\n", L2
    *10^3);
16 disp("The composite, band-pass filter is shown in
    Fig. 17.24.");

```

Chapter 18

DC transients

Scilab code Exa 18.1 Example 1

```
1 //Chapter 18, Problem 1
2 clc;
3 v=120; //dc supply
4 c=15e-6; //capacitance in farad
5 r=47e3; //resistance in ohms
6 tau=r*c; //time constant
7 t1=tau;
8 vcta= v*(1-%e^(-1*t1/tau));
9 vct = v/2;
10 t = 0:0.1:10
11 vc = v*(1-%e^(-1*t/tau));
12 plot(t,vc)
13 xtitle("capacitor voltage/time characteristic", "t",
        "Vc")
14 t = -1*tau*log(1 - vct/v);
15
16 printf("\n (a)The capacitor voltage at a time equal
        to one time constant = %.2f V",vcta)
17 printf("\n (b)The time for the capacitor voltage to
```

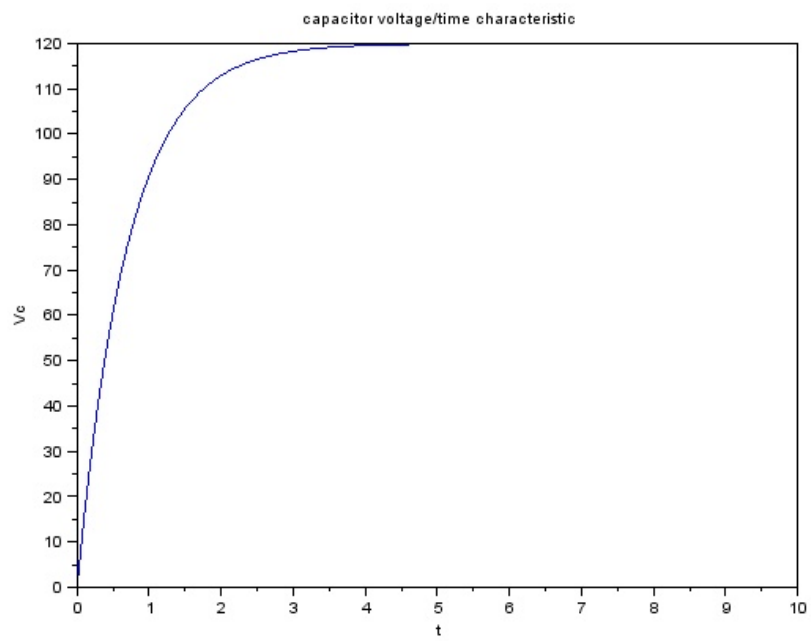


Figure 18.1: Example 1

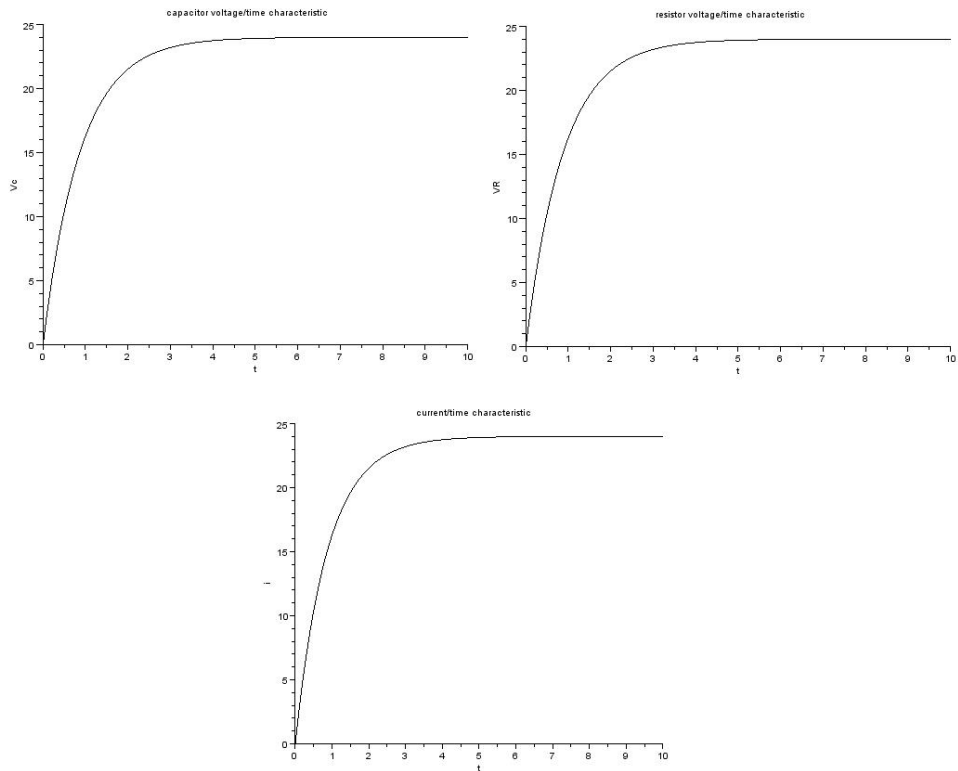


Figure 18.2: Example 2

reach one half of its steady state value = $\%.1 f$
 sec", t)

Scilab code Exa 18.2 Example 2

```

1 //Chapter 18, Problem 2
2 clc;
3 //initializing the variables:
4 c = 4E-6; //capacitance in

```

```

        farad
5  r = 220000;           //resistance in ohm
6  V = 24;             //supply voltage
7  t1 = 1.5;
8
9  //calculation:
10 taw = r*c
11 t = 0:0.1:10
12 Vc = V*(1-%e^(-1*t/taw));
13 plot2d(t,Vc)
14 xtitle("capacitor voltage/time characteristic", "t",
        "Vc")
15 xset('window',1)
16 VR = V*(1-%e^(-1*t/taw));
17 plot2d(t,VR)
18 xtitle("resistor voltage/time characteristic", "t",
        "VR")
19 xset('window',2)
20 I = V/r
21 i = I*%e^(-1*t/taw)
22 plot2d(t,i)
23 xtitle("current/time characteristic", "t", "i")
24 Vct1 = V*%e^(-1*t1/taw)
25 VRt1 = V*%e^(-1*t1/taw)
26 it1 = I*%e^(-1*t1/taw)
27
28 printf("\n The value of capacitor voltage is %.2f V
        ,\n\n resistor voltage is %.2f V,\n\n current is
        %.1E A at one and a half seconds after discharge
        has started.",Vct1, VRt1,it1)

```

Scilab code Exa 18.3 Example 3

```

1 //Chapter 18, Problem 3
2 clc;

```

```

3 //initializing the variables:
4 C = 20E-6;           //capacitance in
   farads
5 R = 50000;          //resistance in ohms
6 V = 20;             //supply voltage
7 t1 = 1;             // in secs
8 t2 = 2;             // in secs
9 VRt = 15;          // in volts
10
11 //calculation:
12 tau = R*C
13 I = V/R
14 Vct1 = V*(1-%e^(-1*t2/tau))
15 t3 = -1*tau*log(VRt/V)
16 it1 = I*%e^(-1*t1/tau)
17
18
19 printf("\n (a) Initial value of the current flowing =
   %.4f mA\n\n",I*10^3)
20 printf("\n (b) Time constant of the circuit = %.0f
   sec\n\n",tau)
21 printf("\n (c) The value of the current one second
   after connection = %.3f mA\n\n",(it1/1E-3))
22 printf("\n (d) The value of the capacitor voltage two
   seconds after connection = %.2f V\n\n",Vct1)
23 printf("\n (e) The time after connection when the
   resistor voltage is 15 V = %.3f sec\n\n",t3)

```

Scilab code Exa 18.4 Example 4

```

1 //Chapter 18, Problem 4
2 clc;
3 t=12e-3;
   //time constant
4 v=10; //

```



```

    supply voltage
5  t1=7e-3; //
    time period of capacitor
6  C=0.5e-6; //
    capacitance
7  R=t/C; //
    calculating resistance
8  vc=v*(1-exp(-t1/t)); //
    calculating capacitor voltage
9  printf("(a) Resistor = %d K.ohm\n\n",R/1000);
10 printf("(b) Capacitor voltage = %f V",vc);

```

Scilab code Exa 18.5 Example 5

```

1 //Chapter 18, Problem 5
2 clc;
3 //Initializing the variables
4 C=10*10^-6; //capacitance in farad
5 R=25*10^3; //resistance in ohm
6 V=100; //voltage dc supply
7 t1=0.5; //time in seconds
8 t2=0.1; //time in seconds
9 vc1=45; //capacitor voltage
10 Vm=V;
11
12 //Calculation
13 tau=C*R; //time
    constant
14 Im=V/R; //maximum
    current
15 vc=Vm*(1-exp(-t1/tau)); //voltage
    across the capacitor
16 i=Im*exp(-tau/tau); //current
    flowing after one time constant
17 vr=V*exp(-t2/tau); //voltage

```

```

        across the resistor
18  t3=-((log(1-(vc1/Vm))/log(exp(1))))*tau; //time in
        seconds
19  vt=V/tau; //initial
        rate of voltage rise
20
21
22  printf("\n(a) Time constant = %f sec\n",tau);
23  printf("\n(b) Maximum current = %f mA\n",Im*10^3);
24  printf("\n(c) Voltage across the capacitor after 0.5
        s = %f V\n",vc);
25  printf("\n(d) Current flowing after one time
        constant = %f mA\n",i*10^3);
26  printf("\n(e) Voltage across the resistor after 0.1
        s = %f V\n",vr);
27  printf("\n(f) Time for the capacitor voltage to
        reach 45V = %f s\n",t3);
28  printf("\n(g) Initial rate of voltage rise = %f V\n"
        ,vt);

```

Scilab code Exa 18.6 Example 6

```

1  //Chapter 18, Problem 6
2  clc;
3
4  //initializing the variables:
5  R = 50000; //resistance in ohms
6  V = 100; //supply voltage
7  Vc1 = 20; // in volts
8  tau = 0.8; // in secs
9  t1 = 0.5; // in secs
10 t2 = 1; // in secs
11
12 //calculation:
13 C = tau/R

```

```

14 t = -1*tou*log(Vc1/V)
15 I = V/R
16 it1 = I*%e^(-1*t1/tou)
17 Vc = V*%e^(-1*t2/tou)
18
19
20 printf("\n (a)The value of the capacitor = %f uF\n\n
      ",C*10^6)
21 printf("\n (b)The time for the capacitor voltage to
      fall to 20 V = %.2f sec\n\n",t)
22 printf("\n (c)The current flowing when the capacitor
      has been discharging for 0.5 s = %f mA\n\n",it1
      *10^3)
23 printf("\n (d)The voltage drop across the resistor
      when the capacitor has been discharging for one
      second = %.1f V\n\n",Vc)

```

Scilab code Exa 18.7 Example 7

```

1 //Chapter 18, Problem 7
2 clc;
3
4 //initializing the variables:
5 C = 0.1E-6;           //capacitance in farads
6 R = 4000;             //resistance in ohms
7 V = 200;              //supply voltage
8 Vc1 = 2;              // in volts
9
10 //calculation:
11 tau = R*C
12 I = V/R
13 t = -1*tau*log(Vc1/V)
14
15 printf("\n (a) Initial discharge current = %.2f A\n\n
      ",I)

```

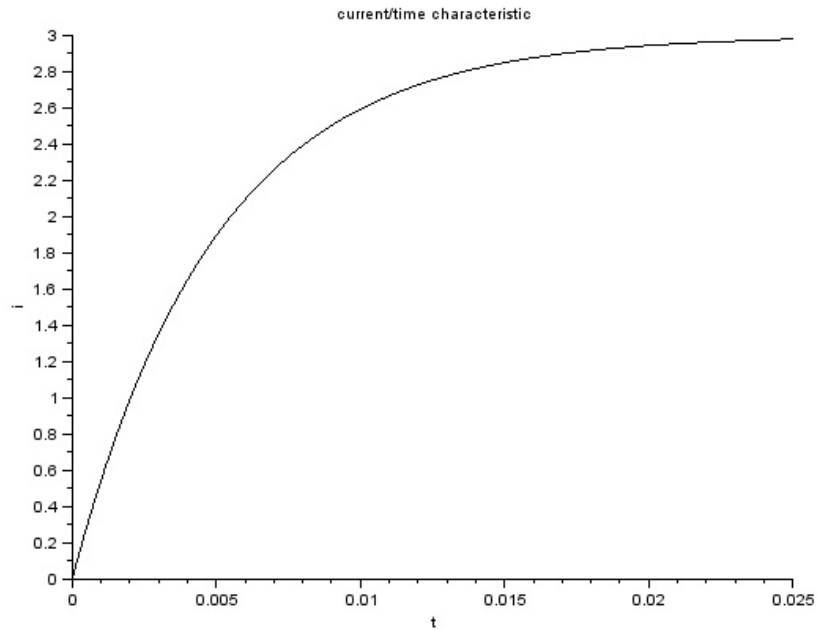


Figure 18.3: Example 8

```

16 printf("\n (b)Time constant tou = %.4f sec\n\n",tau)
17 printf("\n (c)Minimum time required for the voltage
    across the capacitor to fall to less than 2 V = %
    .3f sec",t)

```

Scilab code Exa 18.8 Example 8

```

1 //Chapter 18, Problem 8
2 clc;
3 //initializing the variables:
4 L = 0.1; //inductance in henry

```

```

5 R = 20; //resistance in ohms
6 V = 60; //supply voltage
7 i2 = 1.5; // in amperes
8
9 //calculation:
10 tau = L/R
11 t1 = 2*tau
12 t = 0:0.0001:0.025
13 I = V/R
14 i = I*(1 - %e^(-1*t/tau))
15 plot2d(t,i)
16 xtitle("current/time characteristic", "t", "i")
17 i1 = I*(1 - %e^(-1*t1/tau))
18 t2 = -1*tau*log(1 - i2/I)
19
20
21 printf("\n (a)The value of current flowing at a time
    equal to two time constants = %.3f A\n\n",i1)
22 printf("\n (b)The time for the current to grow to
    1.5 A = %.7f sec\n\n",t2)

```

Scilab code Exa 18.9 Example 9

```

1 //Chapter 18, Problem 9
2 clc;
3 //initializing the variables:
4 L = 0.04; //inductance in henry
5 R = 10; //resistance in ohms
6 V = 120; //supply voltage
7
8
9 //calculation:
10 tau = L/R
11 t1 = tau
12 I = V/R

```

```

13 i1 = I*(1 - %e^(-1*t1/taw))
14 i2 = 0.01*I
15 t2 = -1*taw*log(i2/I)
16
17 printf("(a)The final value of current = %.0f A\n\n",
    I);
18 printf("(b)Time constant of the circuit = %.3f sec\n
    \n",taw);
19 printf("(c)Value of current after a time equal to
    the time constant = %.2f A\n\n",i1);
20 printf("(d)The expected time for the current to rise
    to within 0.01 times of its final value = %.2f
    sec\n\n",t2);

```

Scilab code Exa 18.10 Example 10

```

1 //Chapter 18, Problem 10
2 clc;
3
4 //initializing the variables:
5 L = 3; //inductance in henry
6 R = 15; //resistance in ohms
7 V = 120; //supply voltage
8 t1 = 0.1; // in secs
9 t3 = 0.3; // in secs
10
11 //calculation:
12 taw= L/R
13 I = V/R
14 i2 = 0.85*I
15 VL = V*%e^(-1*t1/taw)
16 t2 = -1*taw*log(1 - (i2/I))
17 i3 = I*(1 - %e^(-1*t3/taw))
18
19 printf("(a)Steady state value of current = %.0f A\n\n",

```

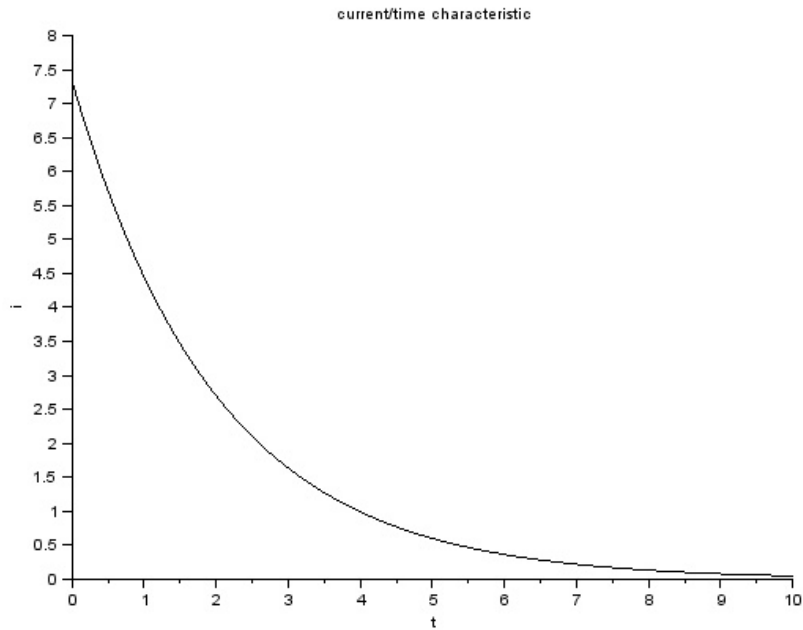


Figure 18.4: Example 11

```

n", I)
20 printf("(b) Time constant of the circuit = %.3f sec\n
    \n", tau)
21 printf("(c) Value of the induced e.m.f. after 0.1 s =
    %.2f V\n\n", VL)
22 printf("(d) Time for the current to rise to 0.85
    times of its final values = %.3f sec\n\n", t2)
23 printf("(e) Value of the current after 0.3 s = %.3f A
    \n\n", i3)

```

Scilab code Exa 18.11 Example 11

```

1 //Chapter 18, Problem 11
2 clc;
3
4 //initializing the variables:
5 R = 15; //resistance in ohms
6 V = 110; //supply voltage
7 tau = 2; //time constant
8 t1 = 3; // in secs
9 i2 = 5; // in amperes
10
11 //calculation:
12 L = tau*R
13 t = 0:0.1:10
14 I = V/R
15 i = I*(%e^(-1*t/tau))
16 plot2d(t,i)
17 xtitle("current/time characteristic", "t", "i")
18 i1 = I*(%e^(-1*t1/tau))
19 t2 = -1*tau*log((i2/I))
20
21
22 printf("\\n Inductance is %.0f H\\n\\n",L)
23 printf("\\n (a)The current flowing in the winding 3 s
    after being shorted-out = %.2f A\\n\\n",i1)
24 printf("\\n (b)The time for the current to decay to 5
    A = %.3f sec\\n\\n",t2)

```

Scilab code Exa 18.12 Example 12

```

1 //Chapter 18, Problem 12
2 clc;
3 //initializing the variables:
4 L = 6; //inductance in henry
5 r = 10; //resistance in ohms
6 V = 120; //supply voltage

```



```

7 tau = 0.3;           //time constant
8 t1 = 1;             // in secs
9
10 //calculation:
11 R = (L/tau) - r
12 Rt = R + r
13 I = V/Rt
14 i2 = 0.1*I
15 i1 = I*(%e^(-1*t1/tau))
16 t2 = -1*tau*log((i2/I))
17
18 printf("\n (a) Resistance of the coil = %.0f ohm\n\n",
        R)
19 printf("\n (b) Current flowing in the circuit one
        second after the shorting link has been placed =
        %.3f A\n\n",i1)
20 printf("\n (c) The time for the current to decay to
        0.1 times of initial value = %.3f sec\n\n",t2)

```

Scilab code Exa 18.13 Example 13

```

1 //Chapter 18, Problem 13
2 clc;
3 //initializing the variables:
4 L = 0.2;           //inductance in henry
5 R = 1000;         //resistance in ohms
6 V = 24;           //supply voltage
7
8 //calculation:
9 tau = L/R
10 t1 = 1*tau // in secs
11 t2 = 2*tau // in secs
12 t3 = 3*tau // in secs
13 I = V/R
14 i1 = I*(1 - %e^(-1*t1/tau))

```

```

15 VL = V*(%e^(-1*t2/tau))
16 VR = V*(1 - %e^(-1*t3/tau))
17
18 printf("\n Time constant of the circuit is %.4f sec ,
        and the steady-state value of the current is %
        .3f A",tau, I)
19 printf("\n (a) Current flowing in the circuit at a
        time equal to one time constant = %.5f A\n\n",i1)
20 printf("\n (b) Voltage drop across the inductor at a
        time equal to two time constants = %.3f V\n\n",
        VL)
21 printf("\n (c)The voltage drop across the resistor
        after a time equal to three time constants = %.2f
        V\n\n",VR)

```

Chapter 19

Operational amplifiers

Scilab code Exa 19.1 Example 1

```
1 //Chapter 19, Problem 1
2 clc;
3 A0=120; //voltage gain
4 V1=2.35; //input voltage
5 V2=2.45; //input voltage
6 V0=A0*(V2-V1); //output voltage
7 printf("Output voltage = %d V",V0);
```

Scilab code Exa 19.2 Example 2

```
1 //Chapter 19, Problem 2
2 clc;
3 cmrr=90; //CMRR
4 Ad=150e3; //differential gain
5 Ac=Ad/10^(cmrr/20); //common mode gain
6 printf("Common mode gain = %.2 f",Ac);
```

Scilab code Exa 19.3 Example 3

```
1 //Chapter 19, Problem 3
2 clc;
3 Av=120; //open-loop voltage gain
4 Vi=3; //input voltage
5 Vo=24*10^-3; //output voltage
6 Ac=Vo/Vi; //common mode gain
7 cmrr=20*log10(Av/Ac); //CMRR
8 printf("CMRR = %.2f dB", cmrr);
```

Scilab code Exa 19.4 Example 4

```
1 //Chapter 19, Problem 4
2 clc;
3 Ri=1000; //input resistance
4 Rf=2000; //feedback resistance
5 Vi1=0.4; //input voltage 1
6 Vi2=-1.2; //input voltage 2
7 V01=(-Rf/Ri)*Vi1; //output voltage 1
8 V02=(-Rf/Ri)*Vi2; //output voltage 2
9 printf("(a) When Vi = 0.4V,\n V0 = %.1f V\n\n", V01);
10 printf("(b) When Vi = -1.2V,\n V0 = %.1f V\n\n", V02)
; 
```

Scilab code Exa 19.5 Example 5

```
1 //Chapter 19, Problem 5, Fig.19.6
2 clc;
3 Ib=100e-9; //input bias current
4 Ri=10e3; //input resistance
5 Rf=1e6; //feedback resistance
6 A=-Rf/Ri; //voltage gain
```

```

7 Vos=Ib*((Ri*Rf)/(Ri+Rf)); //output offset voltage
8 printf("(a) Voltage gain = %f \n\n",A);
9 printf("(b) Output offset voltage due to the input
    bias current = %.2f mV\n\n",Vos*1000);
10 printf("(c) The effect of input bias current can be
    minimised by ensuring that both inputs see
    the same driving resistance.\n");
11 printf("This means that a resistance of value of 9.9
    k (from part (b)) should be placed between the
    non-inverting (+) terminal and earth in Fig. 19.6
    ");

```

Scilab code Exa 19.6 Example 6

```

1 //Chapter 19, Problem 6, Fig.19.6
2 clc;
3 Av=40; //voltage gain
4 B=5000; //bandwidth
5 Ri=10000; //input resistance
6 A=10^(Av/20); //voltage gain in
    decibels
7 Rf=A*Ri; //feedback
    resistance
8 f=A*B; //frequency
9 printf("Gain = %d\n\nFeedback Resistor Rf = %d
    Megaohm\n\nFrequency = %d Khz",A,Rf/10^6,f/1000);

```

Scilab code Exa 19.7 Example 7

```

1 //Chapter 19, Problem 7
2 clc;
3 R1=4.7e3; //resistance 1
4 R2=10e3; //resistance 2

```

```

5 Vi=-0.4; //input voltage
6 Av=1+(R2/R1); //voltage gain
7 V0=Av*Vi; //output voltage
8 printf("(a) Voltage gain = %.2f \n\n",Av);
9 printf("(b) Output voltage = %.2f V\n\n",V0);

```

Scilab code Exa 19.8 Example 8

```

1 //Chapter 19, Problem 8, Fig.19.12
2 clc;
3 R1=10e3; //
   resistance 1
4 R2=20e3; //resistance
   2
5 R3=30e3; //resistance
   3
6 V1=0.5; //input
   voltage 1
7 V2=0.8; //input
   voltage 2
8 V3=1.2; //input
   voltage 3
9 Rf=50e3; //
   feedback resistance
10 V0=-Rf*((V1/R1)+(V2/R2)+(V3/R3)); //output
   voltage
11 printf("Output voltage = %f V",V0);

```

Scilab code Exa 19.10 Example 10

```

1 //Chapter 19, Problem 10
2 clc;
3 R=200e3; //resistance

```

```

4 Vi=-0.75; //input voltage
5 C=2.5e-6; //capacitance
6 Vo = (-1/(C*R))*integrate(' -0.75', 't', 0, 0.1)
//output voltage
7 printf("\n Output voltage is %.2f V",Vo)

```

Scilab code Exa 19.11 Example 11

```

1 //Chapter 19, Problem 11
2 clc;
3 R1=10e3; //resistance 1
4 R2=10e3; //resistance 2
5 R3=100e3; //resistance 3
6 Rf=100e3; //feedback resistance
7 V1=5e-3; //input voltage 1
8 V2=5e-3; //input voltage 2
9 V3=50e-3; //input voltage 3
10 V4=25e-3; //input voltage 4
11 V5=25e-3; //input voltage 5
12 V6=50e-3; //input voltage 6
13 V01=(-Rf/R1)*V1; //output
//output voltage 1
14 V02=(R3/(R2+R3))*(1+(Rf/R1))*V2; //output
//output voltage 2
15 V03=(V3-V4)*(-Rf/R1); //output
//output voltage 3
16 V04=(V6-V5)*(R3/(R2+R3))*(1+(Rf/R1)); //output
//output voltage 4
17 printf("(a) V0 = %d mV\n\n",V01*1000);
18 printf("(b) V0 = %d mV\n\n",V02*1000);
19 printf("(c) V0 = %d mV\n\n",V03*1000);
20 printf("(d) V0 = %d mV\n\n",V04*1000);

```

Chapter 20

Three phase systems

Scilab code Exa 20.1 Example 1

```
1 //Chapter 20, Problem 1
2 clc;
3 Rp=30; //resistance in ohm
4 Vl=415; //3-phase supply
5 Vp=Vl/sqrt(3); //phase voltage
6 Ip=Vp/Rp; //phase current
7 printf("(a) System phase voltage = %.1f V\n or 240 V
   , correct to 3 significant figures\n\n",Vp);
8 printf("(b) Phase current = %.2f A\n\n",Ip);
9 printf("(c) For a star connection, Ip =IL hence the
   line current,\n Line current = %.2f A\n\n",Ip);
```

Scilab code Exa 20.2 Example 2

```
1 //Chapter 20, Problem 2
2 clc;
3 R=30; //resistance of coil
4 f=50; //supply frequency
```



```

5 L=127.3e-3; //inductance of coil
6 Ip=5.08; //line current
7 Xl=2*%pi*f*L; //inductive
   reactance
8 Zp=sqrt(R^2+Xl^2); //impedance of each
   phase
9 Vp=Ip*Zp; //phase voltage
10 Vl=sqrt(3)*Vp; //line voltage
11 printf("Line voltage = %.2f V",Vl);

```

Scilab code Exa 20.4 Example 4

```

1 //Chapter 20, Problem 4, Fig.20.7
2 clc;
3 Vl=415; //3-phase supply
4 Pr=24000; //resistance in
   ohm
5 Py=18000; //resistance in
   ohm
6 Pb=12000; //resistance in
   ohm
7 Vp=Vl/sqrt(3); //phase voltage
8 Ir=Pr/Vp; //current in
   each line
9 Iy=Py/Vp;
10 Ib=Pb/Vp;
11
12 //calculating current in the neutral conductor
13 Irh=cos(90*%pi/180);
14 Iyh=cos(330*%pi/180);
15 Ibh=cos(210*%pi/180);
16 Irv=sin(90*%pi/180);
17 Iyv=sin(330*%pi/180);
18 Ibv=sin(210*%pi/180);
19 Ih=(Ir*Irh)+(Iy*Iyh)+(Ib*Ibh);

```

```

20 Iv=(Ir*Irv)+(Iy*Iyv)+(Ib*Ibv);
21 In=sqrt(Ih^2+Iv^2);
22
23 printf("(a) Ir = %d A\n\nIy = %d A\n\nIb = %d A\n\n"
, Ir, Iy, Ib);
24 printf("(b) The three line currents are shown in the
phasor diagram of Fig. 20.8.\n");
25 printf("Since each load is resistive the currents
are in phase with the phase voltages and are
hence mutually displaced by 120 .");
26 printf("\nIn = %f A\n", In);

```

Scilab code Exa 20.5 Example 5

```

1 //Chapter 20, Problem 5
2 clc;
3 Zp=50; //phase
impedance
4 Vp=440; //3 phase supply
5 Ip=Vp/Zp; //phase current
6 I1=sqrt(3)*Ip; //line current
7 printf("(a) Phase current = %.1f A\n\n", Ip);
8 printf("(b) For a delta connection I1 = %.2f A", I1);

```

Scilab code Exa 20.6 Example 6

```

1 //Chapter 20, Problem 6
2 clc;
3 I1=15; //line current
4 V1=415; //3 phase supply
5 f=50; //supply frequency
6 Ip=I1/sqrt(3); //phase current

```

```

7 Xc=Vl/Ip; //capacitive
   reactance
8 C=1/(2*pi*f*Xc); //capacitance
9 printf("Capacitance = %.3f uF",C*10^6);

```

Scilab code Exa 20.7 Example 7

```

1 //Chapter 20, Problem 7
2 clc;
3 R=3; //resistance of coil
4 Xl=4; //inductive reactance
5 Vl=415; //3 phase supply
6 Vp1=415; //line voltage
7 Vp=Vl/sqrt(3); //phase voltage for star
   connection
8 Zp=sqrt(R^2+Xl^2); //impedance per phase
9 Ip=Vp/Zp; //phase current
10 Ip1=Vp1/Zp; //phase voltage
11 Il1=Ip1*sqrt(3); //line current
12 printf("(i) For star connection\n (a) Line
   voltage = %d V\n Phase voltage = %f V\n\n",Vl,
   Vp);
13 printf(" (b) Line current = %d V\n Phase
   current = %f V\n\n\n",Ip,Ip);
14 printf("(ii) For delta connection\n (a) Line
   voltage = %d V\n Phase voltage = %d V\n\n",Vp1
   ,Vp1);
15 printf(" (b) Line current = %f V\n Phase
   current = %f V\n",Il1,Ip1);

```

Scilab code Exa 20.8 Example 8

```

1 //Chapter 20, Problem 8

```

```

2  clc;
3  Rp=12;           //resistance
4  Vl=415;         //3 phase supply
5  Vp=Vl/sqrt(3);  //phase voltage
6  Ip=Vp/Rp;      //phase current
7  Il=Ip;
8  pf=1;          //power factor
9  P=sqrt(3)*Vl*Il*pf; //power dissipated
10 printf("Total power dissipated = %.2f kW",P/1000);

```

Scilab code Exa 20.9 Example 9

```

1  //Chapter 20, Problem 9
2  clc;
3  P=5000;         //power
4  Vl=400;         //line voltage
5  Il=8.6;         //line current
6  pf=P/(sqrt(3)*Vl*Il); //power factor
7  printf("Power factor = %.3f ",pf);

```

Scilab code Exa 20.11 Example 11

```

1  //Chapter 20, Problem 11
2  clc;
3  Po = 12750;     // in Watts
4  pf = 0.77;     // power factor
5  eff = 0.85;
6  VL = 415;      // in Volts
7
8  //calculation:
9  //eff = power_out/power_in
10 Pi = Po/eff

```

```

11 //Power  $P = VL*IL*(3^{0.5})*\cos(\phi)$  or  $P = 3*I_p*I_p*$ 
     $R_p$ )
12  $IL = Pi/(VL*(3^{0.5})*pf)$  // line current
13
14 //For a delta connection:
15 // $IL = I_p*(3^{0.5})$ 
16  $I_p = IL/(3^{0.5})$ 
17
18 printf("\\n\\n (a)Power input = %d W",Pi)
19 printf("\\n\\n (b)Line current = %.2 f A",IL)
20 printf("\\n\\n (c)Phase current = %.2 f A",Ip)

```

Scilab code Exa 20.13 Example 13

```

1 //Chapter 20, Problem 13
2 clc;
3  $Vl=400$ ; //supply voltage
4  $Rp=30$ ; //resistance
5  $Xl=40$ ; //inductive
    reactance
6  $Zp=sqrt(Rp^2+Xl^2)$ ; //phase impedance
7  $Ip=Vl/Zp$ ; //phase current
8  $I1=sqrt(3)*Ip$ ; //line current
9  $pf=Rp/Zp$ ; //power factor
10  $P=sqrt(3)*Vl*I1*pf$ ; //power dissipated
11  $S=sqrt(3)*Vl*I1$ ; //alternator output
    KVA
12 printf("(a) Current is supplied by alternator = %.3 f
    A\\n\\n",I1);
13 printf("(b) Output power = %.2 f kW\\n",P/1000);
14 printf(" Alternator ouput KVA = %.2 f KVA",S/1000)
    ;

```

Scilab code Exa 20.14 Example 14

```
1 //Chapter 20, Problem 14
2 clc;
3 f=50; //supply frequency
4 Rp=30; //resistance
5 C=80e-6; //capacitance
6 V1=400; //3 phase supply
7 Xc=1/(2*%pi*f*C); //capacitive
   reactance
8 Zp=sqrt(Rp^2+Xc^2); //phase impedance,
9 pf=Rp/Zp; //power factor
10 phi=acos(pf); //phase angle
11 Ip=V1/Zp; //phase current
12 I1=sqrt(3)*Ip; //line current
13 P=sqrt(3)*V1*I1*cos(phi); //power dissipated
14 S=sqrt(3)*V1*I1; //total KVA
15 printf("(a) Phase current = %.3f A\n\n",Ip);
16 printf("(b) Line current = %.2f A\n\n",I1);
17 printf("(c) Total power dissipated = %.3f kW\n\n",P
   /1000);
18 printf("(d) Total kVA = %.3f kVA\n\n",S/1000);
19 printf("The phasor diagram for the load is shown in
   Fig. 20.18");
```

Scilab code Exa 20.15 Example 15

```
1 //Chapter 20, Problem 15
2 clc;
3 P1=8; //power 1 in watt
4 P2=4; //power 2 in watt
5 P=P1+P2; //total input power
6 phi=atan(sqrt(3)*((P1-P2)/(P1+P2)));
7 pf=cos(phi); //load power factor
8 printf("(a) Total input power = %d kW\n\n",P);
```

```
9 printf("(b) Power factor = %.3f ",pf);
```

Scilab code Exa 20.16 Example 16

```
1 //Chapter 20, Problem 16
2 clc
3 P=12e3 //total power
4 pf=0.6 //power factor
5 ang=acos(pf)
6 ta=tan(ang)
7 P12=P*ta/3^(1/2)
8
9 //solving two equation by matrix method
10 A=[1 1;1 -1]
11 B=[12000;P12]
12 x=linsolve(A,-B)
13 printf("wattmeter 1 read = %.2f kW\n\n",x(1)/1000)
14 printf("wattmeter 2 read = %.2f kW\n\n",x(2)/1000)
```

Scilab code Exa 20.17 Example 17

```
1 //Chapter 20, Problem 17
2 clc;
3 P1=10; //power 1 in watt
4 P2=-3; //power 2 in watt
5 P=P1+P2; //total input power
6 phi=atan(sqrt(3)*((P1-P2)/(P1+P2)));
7 pf=cos(phi); //load power factor
8 disp("Since the reversing switch on the wattmeter
had to be operated the 3kW reading is taken as
3 kW");
9 printf("(a) Total input power = %f kW\n\n",P);
10 printf("(b) Power factor = %f ",pf);
```

Scilab code Exa 20.18 Example 18

```
1 //Chapter 20, Problem 18
2 clc;
3 R = 8; //resistance
4 XL = 8; //inductive reactance
5 VL = 415; //supply voltage
6
7 //calculation:
8 //For a star connection:
9 //IL = Ip
10 //VL = Vp*(3^0.5)
11 VLs = VL
12 Vps = VLs/(3^0.5)
13 //Impedance per phase,
14 Zp = (R*R + XL*XL)^0.5
15 Ips = Vps/Zp
16 ILs = Ips
17 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
18 pf = R/Zp
19 Ps = VLs*ILs*(3^0.5)*pf
20 //If wattmeter readings are P1 and P2 then P1 + P2 =
    Pst
21 Pst = Ps
22 // Pid = Pi1 - Pi2
23 phi = acos(pf)
24 Psd = Pst*tan(phi)/(3^0.5)
25 //Hence wattmeter 1 reads
26 Ps1 = (Psd + Pst)/2
27 //wattmeter 2 reads
28 Ps2 = Pst - Ps1
29
30 //For a delta connection:
```



```

31 //VL = Vp
32 //IL = Ip*(3^0.5)
33 VLd = VL
34 Vpd = VLd
35 Ipd = Vpd/Zp
36 ILd = Ipd*(3^0.5)
37 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
38 Pd = VLd*ILd*(3^0.5)*pf
39 //If wattmeter readings are P1 and P2 then P1 + P2 =
    Pdt
40 Pdt = Pd
41 // Pid = Pi1 - Pi2
42 Pdd = Pdt*tan(phi)/(3^0.5)
43 //Hence wattmeter 1 reads
44 Pd1 = (Pdd + Pdt)/2
45 //wattmeter 2 reads
46 Pd2 = Pdt - Pd1
47
48
49 printf("\n\n (a)When the coils are star-connected
    the wattmeter readings are %.3f kW and %.3f kW",
    Ps1/1000,Ps2/1000)
50 printf("\n\n (b)When the coils are delta-connected
    the wattmeter readings are are %.3f kW and %.3f
    kW",Pd1/1000,Pd2/1000)

```

Chapter 21

Transformers

Scilab code Exa 21.1 Example 1

```
1 //Chapter 21, Problem 1
2 clc;
3 n1=500;           //primary turns
4 n2=3000;         //secondary turns
5 v1=240;          //primary voltage
6 v2=(v1*n2)/n1;  //secondary voltage
7 printf("Secondary voltage = %f V",v2);
```

Scilab code Exa 21.2 Example 2

```
1 //Chapter 21, Problem 2
2 clc;
3 N=2/7;           //turns ratio
4 v1=240;          //primary voltage
5 v2=v1/N;         //secondary voltage
6 printf("Output voltage = %f V",v2);
```

Scilab code Exa 21.3 Example 3

```
1 //Chapter 21, Problem 3
2 clc;
3 N=8/1;           //turns ratio
4 i1=3;           //primary current
5 v1=240;         //primary voltage
6 v2=v1/N;       //secondary voltage
7 i2=N*i1;       //secondary current
8 printf("Secondary voltage = %f V\n\nSecondary
   current = %f A",v2,i2);
```

Scilab code Exa 21.4 Example 4

```
1 //Chapter 21, Problem 4
2 clc;
3 v1=240;         //primary voltage
4 v2=12;         //secondary voltage
5 P=150;         //power
6 N=v1/v2;       //turns ratio
7 i2=P/v2;       //secondary current
8 i1=i2/N;       //primary current
9 printf("Transformer turns ratio = %f\n\n",N);
10 printf("Current = %f A",i1);
```

Scilab code Exa 21.5 Example 5

```
1 //Chapter 21, Problem 5
2 clc;
3 v2=120;         //secondary voltage
4 r2=12;         //resistance in ohm
5 i1=4;         //primary current
6 i2=v2/r2;     //secondary current
```

```

7 v1=v2*(i2/i1); //primary voltage
8 printf("Primary voltage = %f V",v1);

```

Scilab code Exa 21.6 Example 6

```

1 //Chapter 21, Problem 6
2 clc;
3 N=10; //turns ratio
4 v1=2.5e3; //primary
   voltage
5 P=5000; //power
6 v2=v1/N; //secondary
   voltage
7 i2=P/v2; //secondary
   current
8 Rl=v2/i2; //resistance in
   ohm
9 i1=i2/N; //primary
   current
10 printf("(a) Full-load secondary current = %d A\n\n",
   i2);
11 printf("(b) Minimum value of load resistance = %.1f
   ohms\n\n",Rl);
12 printf("(c) Primary current = %d A\n\n",i1);

```

Scilab code Exa 21.7 Example 7

```

1 //Chapter 21, Problem 7
2 clc;
3 v1=2400; //
   primary voltage
4 v2=400; //
   secondary voltage

```

```

5 i0=0.5; //no
  load current
6 P1=400; //power
7 phi=acos(v2/(v1*i0)); //phase
8 im=i0*sin(phi); //
  magnetising component
9 ic=i0*cos(phi); //core
  loss component
10 printf("Magnetising loss component = %.3f A\n\n",im)
  ;
11 printf("Core loss component = %.3f A",ic);

```

Scilab code Exa 21.9 Example 9

```

1 //Chapter 21, Problem 9
2 clc;
3 v1=4000; //primary voltage
4 v2=200; //secondary voltage
5 f=50; //frequency
6 n2=100; //secondary turns
7 R=100e3; //resistance in ohm
8 E=v2;
9 i1=R/v1; //primary current
10 i2=R/v2; //secondary current
11 n1=(v1/v2)*n2; //primary turns
12 phim=E/(4.44*f*n2); //flux max
13 printf("(a) Primary current = %f A\n\nSecondary
  currenr = %f A\n\n\n",i1,i2);
14 printf("(b) Primary turns = %f\n\n\n",n1);
15 printf("(c) maximum value of the flux = %f mWb",phim
  *1000);

```

Scilab code Exa 21.10 Example 10

```

1 //Chapter 21, Problem 10
2 clc;
3 f=50; //frequency
4 n1=25; //primary turns
5 n2=300; //secondary turns
6 A=300e-4; //cross-sectional area
   of the core
7 v1=250; //primary voltage
8 phim=v1/(4.44*f*n1); //flux
9 Bm=phim/A; //maximum flux density
10 v2=v1*(n2/n1); //secondary voltage
11 printf("(a) Maximum flux density= %.2 f T\n\n",Bm);
12 printf("(b) Secondary winding voltage = %d V",v2);

```

Scilab code Exa 21.11 Example 11

```

1 //Chapter 21, Problem 11
2 clc;
3 f=50; //frequency
4 v1=500; //primary voltage
5 v2=100; //secondary voltage
6 B=1.5; //maximum core flux
   density
7 A=50e-4; //effective core
   cross-sectional area
8 phim=B*A; //maximum flux
9 n1=v1/(4.44*f*phim); //primary turns
10 n2=v2/(4.44*f*phim); //secondary turns
11 printf("Primary turns = %d turns\n\n",n1);
12 printf("Seconadry turns = %d turns\n\n",n2);

```

Scilab code Exa 21.12 Example 12

```

1 //Chapter 21, Problem 12
2 clc;
3 v1=4500; //primary voltage
4 v2=225; //secondary voltage
5 f=50; //frequency
6 en=15; //e.m.f. per turn
7 B=1.4; //maximum core flux
   density
8 n1=v1/en; //primary turns
9 n2=v2/en; //secondary turns
10 phim=v1/(4.44*f*n1); //maximum flux
11 A=phim/B; //effective core
   cross-sectional area
12 printf("(a) Primary turns = %f\n\nSecondary turns =
   %f\n\n",n1,n2);
13 printf("(b) cross-sectional area of the core = %f m2
   ",A);

```

Scilab code Exa 21.13 Example 13

```

1 //Chapter 21, Problem 13, Figure 21.5
2 clc
3 n1=2000 //no of turns on
   primary
4 n2=800 //no of turns on
   secondary
5 i2=100 //secondary current
   in amperes
6 i1=44 //current in amperes
   from phasor diagram
7 i0=5 //no load current
8 i3=40 //current from phaor
   diagram
9 pf0=0.2 //power factor
10 a1=37

```

```

11 pf2=0.85
12 i1=i2*n2/n1
13 a2=acosd(pf2)
14 a0=acosd(pf0)
15 Icos=(i0*pf0)+(i3*pf2)
16 Isin=(i0*sin(a0*pi/180))+(i3*sin(a2*pi/180))
17 I1=sqrt(Isin^2+Icos^2)
18 ta=atand(Isin/Icos)
19 pf=cos(ta*pi/180)
20 printf("I1 = %.3f A\n\n Power factor = %.3f degree\n\n", I1, pf)

```

Scilab code Exa 21.14 Example 14

```

1 //Chapter 21, Problem 14
2 clc;
3 n1=600; //primary turns
4 n2=150; //secondary
   turns
5 r1=0.25; //primary
   resistance
6 r2=0.01; //secondary
   resistance
7 x1=1; //leakage
   reactance
8 x2=0.04;
9 re=r1+r2*(n1/n2)^2; //equivalent
   resistance
10 xe=x1+x2*(n1/n2)^2; //equivalent
   reactance
11 ze=sqrt(re^2+xe^2); //equivalent
   impedance
12 phie=acos(re/ze); //phase angle of
   the impedance
13 printf("(a) Equivalent resistance = %.2f ohms\n\n",

```



```

    re);
14 printf("(b) Equivalent reactance = %.2f ohms\n\n",xe
    );
15 printf("(c) Equivalent impedance = %.2f ohms\n\n",ze
    );
16 printf("(d) Phase angle of the impedance = %.2f deg"
    ,phie*180/%pi);

```

Scilab code Exa 21.15 Example 15

```

1 //Chapter 21, Problem 15
2 clc;
3 e1=200; //primary voltage
4 e2=400; //secondary voltage
5 v2=387.6; //secondary terminal
    voltage
6 reg=((e2-v2)/e2)*100; //regulation
7 printf("Regulation = %.1f percent",reg);

```

Scilab code Exa 21.16 Example 16

```

1 //Chapter 21, Problem 16
2 clc;
3 reg=2.5; //regulation
4 e2=240; //secondary voltage
5 v2=240-((reg*e2)/100); //secondary terminal
    voltage
6 printf("Load voltage = %d V",v2);

```

Scilab code Exa 21.17 Example 17

```

1 //Chapter 21, Problem 17
2 clc;
3 vi=200e3; //rated transformer
4 pf=0.85; //power factor
5 lcu=1.5e3; //copper loss
6 lfe=1e3; //iron loss
7 po=vi*pf; //full-load output power
8 lt=lcu+lfe; //total losses
9 pi=po+lt; //input power
10 Ef=(1-(lt/pi)); //efficiency
11 printf("Transformer efficiency at full load = %f
    percent",Ef*100);

```

Scilab code Exa 21.18 Example 18

```

1 //Chapter 21, Problem 18
2 clc;
3 vi=200e3; //rated transformer
4 pf=0.85; //power factor
5 lcu=(1/2)^2*1.5e3; //copper loss
6 lfe=1e3; //iron loss
7 p0=(1/2)*vi*pf; //full-load output
    power
8 lt=lcu+lfe; //total losses
9 pi=p0+lt; //input power
10 Ef=(1-(lt/pi)); //efficiency
11 printf("Transformer efficiency at half load = %.3f
    percent",Ef*100);

```

Scilab code Exa 21.19 Example 19

```

1 //Chapter 21, Problem 19
2 clc

```

```

3 k=400000 //
  transformer rating
4 v1=5000 //primary
  current
5 v2=320 //secondary
  current
6 r1=0.5 //resistance
  in ohm
7 r2=0.001 //resistance
  in ohm
8 lfe=2500 //iron loss
9 pf=0.85 //power
  factor
10 i1=k/v1 //primary
  current
11 i2=k/v2 //secondary
  current
12 lcu=(i1^2*r1)+(i2^2*r2) //total
  copper loss
13 lt=lcu+lfe //total loss
14 pt=k*pf //total
  output power
15 pi=pt+lt //input
  power
16 n=(1-(lt/pi))*100 //efficiency
17 lc=lcu*(1/2)^2 //total
  copper loss at half load
18 lh=lc+lfe //total loss
  at half loss
19 ph0=(1/2)*pt //output
  power at half load
20 phi=(ph0+lh) //input
  power at half load
21 n1=(1-(lh/phi))*100 //efficiency
22 printf("(a) Efficiency on full load = %.3f percent\n
  \n",n)
23 printf("(b) Efficiency at half load = %.3f percent\n
  \n",n1)

```

Scilab code Exa 21.20 Example 20

```
1 //Chapter 21, Problem 20
2 clc
3 c=4e3 //coper loss
4 p=500e3 //transformer rating
5 r=2.5e3 //iron loss
6 pf=0.75 //power factor
7 x=sqrt(r/c)
8 eff=x*p
9 los=2*r
10 po=eff*pf
11 pi=po-los
12 n=(1-(los/pi))*100
13 printf("(a) The Output KVA at maximum efficiency = %
    .2f kVA\n\n",eff/1000)
14 printf("(b) Maximum efficiency = %.2f percent",n)
```

Scilab code Exa 21.21 Example 21

```
1 //Chapter 21, Problem 21
2 clc;
3 N=4/1; //turns ratio
4 Rl=100; //load resistance
5 R1=N^2*Rl; //equivalent input
    resistance
6 printf("Equivalent input resistance = %d ohms",R1);
```

Scilab code Exa 21.22 Example 22

```

1 //Chapter 21, Problem 22
2 clc;
3 R1=112; //equivalent input
   resistance
4 Rl=7; //load resistance
5 N=sqrt(R1/Rl); //turns ratio
6 printf("Optimum turns ratio = %d : 1 ",N);

```

Scilab code Exa 21.23 Example 23

```

1 //Chapter 21, Problem 23
2 clc;
3 R1=150; //equivalent
   input resistance
4 N=5; //turns ratio
5 Rl=R1/(N^2); //load
   resistance
6 printf("Optimum value of load resistance = %d ohm",
   Rl);

```

Scilab code Exa 21.24 Example 24

```

1 //Chapter 21, Problem 24
2 clc;
3 v1=220; //primary
   voltage
4 v2=1760; //secondary
   voltage
5 R=2; //cable
   resistance
6 Rl=1.28e3; //load across
   secondary winding
7 N=v1/v2; //turns ratio

```

```

8 R1=N^2*R1; //equivalent
   input resistance
9 Rin=R+R1; //total input
   resistance ,
10 I1=v1/Rin; //primary
   current
11 I2=I1*N; //secondary
   current
12 P=I2^2*R1; //power
   dissipated
13 printf("(a) Primary current = %d A\n\n",I1);
14 printf("(b) Power dissipated in load resistor = %d W
   ",P);

```

Scilab code Exa 21.25 Example 25

```

1 //Chapter 21, Problem 25
2 clc;
3 V=24; //ac source
4 R1=15e3; //input resistance
5 N=25/1; //turns ratio
6 Rin=15e3; //internal resistance
7 Rl=R1*(1/N)^2; //load resistance
8 Rt=Rin+R1; //total input resistance
9 I1=V/Rt; //primary current
10 I2=I1*N; //secondary current
11 P=I2^2*R1; //power dissipated
12 printf("(a) Load resistance = %d ohms\n\n",R1);
13 printf("(b) Power dissipated in the load = %.1f mW",
   P*1000);

```

Scilab code Exa 21.26 Example 26

```

1 //Chapter 21, Problem 26
2 clc;
3 V1=320; //primary voltage
4 V2=250; //secondary voltage
5 Rg=20e3; //rating
6 I1=Rg/V1; //primary current
7 I2=Rg/V2; //secondary current
8 I=I2-I1; //current in common part
   of the winding
9 printf("Primary current = %.1f A\n\nSecondary
   current = %d A\n\n",I1,I2);
10 printf("Hence current in common part of the winding
   = %.1f A",I);

```

Scilab code Exa 21.27 Example 27

```

1 //Chapter 21, Problem 27
2 clc;
3 v1=200; //primary voltage of
   transformer 1
4 v2=150; //secondary voltage
   of transformer 1
5 v3=500; //primary voltage of
   transformer 2
6 v4=100; //secondary voltage
   of transformer 2
7 x=v2/v1;
8 V=(1-x)*100;
9 y=v4/v3;
10 W=(1-y)*100;
11 printf("(a) 200V:150V transformer,\n Volume of
   copper = %d percent\n",V);
12 disp("Hence the saving is 75%");
13 printf("\n\n(b) 500V:100V transformer,\n Volume of
   copper = %d percent\n",W);

```

```
14 disp("Hence the saving is 20%.");
```

Scilab code Exa 21.28 Example 28

```
1 //Chapter 21, Problem 28
2 clc;
3 n1=500; //primary turns
4 n2=50; //secondary
   turns
5 v1=2.4e3; //supply voltage
6 Vp=v1/sqrt(3); //primary phase
   voltage
7 Vp2=Vp*(n2/n1); //secondary
   phase voltage
8 Vp3=v1*(n2/n1); //secondary
   phase voltage 2
9 V1=sqrt(3)*Vp3; //secondary line
   voltage
10 printf("(a) For star connection\n")
11 printf("Secondary line voltage = %.2f V\n\n",Vp2);
12 printf("(b) For delta connection\n");
13 printf("Secondary line voltage = %.2f V",V1);
```

Scilab code Exa 21.29 Example 29

```
1 //Chapter 21, Problem 29
2 clc;
3 N1=1; //primary turns
4 N2=60; //secondary turns
5 I1=300; //primary current
6 Ra=0.15; //ammeter resistance
7 R2=0.25; //secondary winding
   resistance
```



```

8 I2=I1*(N1/N2); //secondary current
9 V2=I2*Ra; //secondary voltage
10 Rt=Ra+R2; //total resistance
    of secondary circuit
11 e2=I2*Rt; //induced e.m.f. in
    secondary
12 l=e2*I2; //load on secondary
13 printf("(a) Reading on the ammeter = %d A\n\n",I2);
14 printf("(b) P.d. across the ammeter = %.2f V\n\n",V2
    );
15 printf("(c) Total load (in VA) on the secondary = %d
    VA",l);

```

Chapter 22

DC machines

Scilab code Exa 22.1 Example 1

```
1 //Chapter 22, Problem 1
2 clc;
3 Z=600; //no of armature conductors
4 c=2;
5 p=8/2; //no of pairs of poles
6 n=625/60; //armature speed
7 phi=20e-3; //flux
8 E=(2*p*phi*n*Z)/c; //e.m.f
9 printf("emf = %f V",E);
```

Scilab code Exa 22.2 Example 2

```
1 //Chapter 22, Problem 2
2 clc;
3 E=240; //e.m.f
4 Z=50*16; //no of armature
   conductors
5 phi=30e-3; //flux
```

```

6 p=4/2; //no of pairs of
    poles
7 c=2*p;
8 n=(E*c)/(2*p*phi*Z); //armature speed
9 printf("Speed = %d rev/s",n);

```

Scilab code Exa 22.3 Example 3

```

1 //Chapter 22, Problem 3
2 clc;
3 p=8/2; //no of pairs of
    poles
4 c=2*p;
5 phi=0.03; //flux
6 n=500/60; //armature speed
7 Z=1200; //no of armature
    conductors
8 E=(2*p*phi*n*Z)/c; //e.m.f
9 printf("emf = %f V",E);

```

Scilab code Exa 22.4 Example 4

```

1 //Chapter 22, Problem 4
2 clc;
3 p=8/2; //no of pairs of
    poles
4 c=2;
5 phi=0.03; //flux
6 n=500/60; //armature speed
7 Z=1200; //no of armature
    conductors
8 E=(2*p*phi*n*Z)/c; //e.m.f
9 printf("emf = %f V",E);

```

Scilab code Exa 22.6 Example 6

```
1 //Chapter 22, Problem 6
2 clc;
3 E1=200; //generated e.m.f 1
4 n1=30; //armature speed 1
5 E2=250; //generated e.m.f 2
6 n2=20; //armature speed 2
7 phi1=1; //flux 1
8 phi2=(phi1*n1*E2)/(n2*E1); //flux 2
9 printf("Increase in the flux per pole = %f percent",
    phi2*100);
```

Scilab code Exa 22.7 Example 7

```
1 //Chapter 22, Problem 7
2 clc;
3 E=200; //generated e.m.f
4 ia=30; //armature current
5 Ra=0.30; //armature
    resistance
6 V=E-(ia*Ra); //terminal voltage
7 printf("Terminal voltage = %f V",V);
```

Scilab code Exa 22.8 Example 8

```
1 //Chapter 22, Problem 8
2 clc;
```

```

3 ia=8; //armature
  current
4 Ra=1; //armature
  resistance
5 Rl=60; //loadd
  resistance
6 V=ia*Rl; //terminal
  voltage
7 E=V+(ia*Ra); //generated e.m.
  f
8 printf("(a) Terminal voltage = %f V\n\n",V);
9 printf("(b) Generated emf = %f V\n\n",E);

```

Scilab code Exa 22.9 Example 9

```

1 //Chapter 22, Problem 9
2 clc;
3 E1=150; //generated e.m.f 1
4 phi1=0.10; //flux 1
5 phi2=0.1; //flux 2
6 N1=20; //armature speed 1
7 N2=25; //armature speed 2
8 N3=24; //armature speed 3
9 N4=20 //armature speed 4
10 phi3=0.08; //flux 3
11 phi4=0.07; //flux 4
12 E2=(E1*phi1*N2)/(phi2*N1); //
  generated e.m.f 2
13 E3=(E1*phi3*N4)/(phi2*N1); //
  generated e.m.f 3
14 E4=(E1*phi4*N3)/(phi2*N1); //
  generated e.m.f 4
15 printf("(a) emf = %.1 f V\n\n\n",E2);
16 printf("(b) emf = %d V\n\n\n",E3);
17 printf("(c) emf = %d V\n\n\n",E4);

```

Scilab code Exa 22.10 Example 10

```
1 //Chapter 22, Problem 10
2 clc;
3 P=20e3; //power by shunt generator
4 V=200; //voltage
5 R=100e-3; //cable resistance
6 Rf=50; //field winding resistance
7 Ra=40e-3; //armature resistance
8 I=P/V; //load current
9 Vc=I*R; //voltage drop in cable
10 Vt=Vc+V; //terminal voltage
11 If=Vt/Rf; //field current
12 Ia=I+If; //armature current
13 E=Vt+(Ia*Ra); //generated e.m.f
14 printf("(a) Terminal voltage = %d V \n\n",Vt);
15 printf("(b) Generated e.m.f. E = %.2f V",E);
```

Scilab code Exa 22.11 Example 11

```
1 //Chapter 22, Problem 11
2 clc;
3 I=80; //current
4 Rse=0.02; //series resistance
5 Ra=0.04; //armature resistance
6 Rf=40; //field resistance
7 V=200; //supply voltage
8 Vse=I*Rse; //volt drop in series
   winding
9 V1=V+Vse; //P.d. across the field
   winding
```

```

10 If=V1/Rf;           //field current
11 Ia=I+If;           //armature current
12 E=V1+(Ia*Ra);      //generated e.m.f
13 printf("Generated e.m.f., E = %d V",E);

```

Scilab code Exa 22.12 Example 12

```

1 //Chapter 22, Problem 12
2 clc;
3 R=0.75               //armature circuit
   resistance
4 Rf=125;             //field resistance
5 Po=10e3;            //power in watt
6 V=250;              //supply voltage
7 C=600;              //iron, friction and windage
   losses in watt
8 I=Po/V;             //load current
9 If=V/Rf;           //field current
10 Ia=If+I;           //armature current
11 n=(Po/(Po+(Ia^2*R)+(If*V)+C))*100; //
   efficiency
12 printf("Efficiency = %f percent",n);

```

Scilab code Exa 22.13 Example 13

```

1 //Chapter 22, Problem 13
2 clc;
3 V=240;              //supply voltage
4 Ia=50;              //armature current
5 Ra=0.2;             //armature resistance
6 E=V-(Ia*Ra);       //back e.m.f
7 printf("Back emf = %d V",E);

```

Scilab code Exa 22.14 Example 14

```
1 //Chapter 22, Problem 14
2 clc;
3 Ra=0.25; //armature
   resistance
4 V=300; //supply voltage
5 Ia1=100; //current 1
6 Ia2=80; //current 2
7 E1=V+(Ia1*Ra); //e.m.f (generator)
8 E2=V-(Ia2*Ra); //e.m.f (motor)
9 printf("(a) As a generator, generated e.m.f = %d V\n
   \n",E1);
10 printf("(b) As a motor, generated e.m.f = %d V",E2)
```

Scilab code Exa 22.15 Example 15

```
1 //Chapter 22, Problem 15
2 clc;
3 p=8/2; //pairs of poles
4 c=2;
5 phi=25e-3; //flux
6 Ia=30; //armature current
7 Z=900;
8 T=(p*phi*Z*Ia)/(%pi*c); //torque
9 printf("Torque = %.1 f Nm",T);
```

Scilab code Exa 22.16 Example 16


```

1 //Chapter 22, Problem 16
2 clc;
3 V=350; //supply voltage
4 Ra=0.5; //armature
   resistance
5 n=15; //motor speed in rev
   /sec
6 Ia=60; //armature current
7 E=V-Ia*Ra; //back e.m.f
8 T=(E*Ia)/(2*pi*n); //torque
9 printf(" Torque ,T = %.1 f Nm" ,T);

```

Scilab code Exa 22.17 Example 17

```

1 //Chapter 22, Problem 17
2 clc;
3 V=250; //supply
   voltage
4 p=6/2; //pairs of
   poles
5 Z=500; //conductors
6 Ra=1; //armature
   resistance
7 phi=20*10^-3; //flux
8 Ia=40; //armature
   current
9 c=2*p;
10 E=V-(Ia*Ra); //back e.m.f
11 n=E*c/(2*p*phi*Z); //rotating
   speed
12 T=(E*Ia)/(2*pi*n); //torque
13 printf(" (a) Speed = %f rev/min\n\n" ,n*60);
14 printf(" (b) Torque , T = %.2 f Nm" ,T);

```

Scilab code Exa 22.18 Example 18

```
1 //Chapter 22, Problem 18
2 clc;
3 T1=25; //torque of a shaft 1
4 T2=35; //torque of a shaft 2
5 Ia1=16; //armature current 1
6 phi2=0.85; //flux
7 Ia2=Ia1*T2/(phi2*T1); //armature current 2
8 printf("Armature current = %.2f A",Ia2);
```

Scilab code Exa 22.19 Example 19

```
1 //Chapter 22, Problem 19
2 clc
3 V=100 //supply voltage
4 I=15 //current in ampere
5 T=12 //torque in Nm
6 n=1500/60
7 n1=((V*I)/(T*2*pi*n))*100
8 los=((T*2*pi*n)-(V*I))
9 printf("(a) Efficiency = %.2f percent \n\n",n1)
10 printf("(b) Power loss = %f W",los)
```

Scilab code Exa 22.20 Example 20

```
1 //Chapter 22, Problem 20
2 clc;
3 Ra=0.4; //armature
    resistance
```

```

4 V=240; //supply voltage
5 Rf=150; //field resistance
6 I=30; //total current
7 If=V/Rf; //field current
8 Ia=I-If; //armature current
9 E=V-(Ia*Ra); //generated e.m.f
10 printf("(a) Armature current = %.1f A\n\n",Ia);
11 printf("(b) Back emf = %.2f V",E)

```

Scilab code Exa 22.21 Example 21

```

1 //Chapter 22, Problem 21
2 clc;
3 V=200; //supply voltage
4 Ra=0.4; //armature
   resistance
5 Ia=30; //armature current
6 n1=1350/60; //rotating speed
7 Ia2=45; //armature current 2
8 E1=V-(Ia*Ra); //e.m.f 1
9 E2=V-(Ia2*Ra); //e.m.f 2
10 n2=(n1*E2)/E1; //speed of the motor
   due to armature current 2
11 printf("Speed of the motor = %.3f rev/min",n2*60);

```

Scilab code Exa 22.23 Example 23

```

1 //Chapter 22, Problem 23
2 clc;
3 n1=24; //rotating speed due
   to Ia = 15A
4 phi2=2; //flux
5 V=240; //supply voltage

```

```

6 Ia=15; //armature current
7 I2=30; //current
8 Ra=0.2; //armature
    resistance
9 Rf=0.3; //field resistance
10 E1=V-(Ia*(Ra+Rf)); //e.m.f 1
11 E2=V-(I2*(Ra+Rf)); //e.m.f 2
12 n2=n1*E2/(E1*phi2); //speed of motor
13 printf("(a) Generated e.m.f = %f V\n\n",E1);
14 printf("(b) Speed of motor n2 = %.1f rev/s",n2);

```

Scilab code Exa 22.24 Example 24

```

1 //Chapter 22, Problem 24
2 clc;
3 Ra=0.2 //armature resistance
4 V=320; //supply voltage
5 Rf=40; //field resistance
6 I=80; //current
7 If=V/Rf; //field current
8 Ia=I-If; //armature current
9 C=1500;
10 n=((V*I)-(Ia^2*Ra)-(If*V)-C)/(V*I)*100;
    //overall efficiency
11 printf("Efficiency = %.3f percent",n);

```

Scilab code Exa 22.25 Example 25

```

1 //Chapter 22, Problem 25
2 clc;
3 V=250; //supply voltage
4 I=40; //current
5 Ra=0.15; //armature resistance

```

```

6 Rf=0.05; //field resistance
7 n=((V*I)-(2*I^2*(Ra+Rf))/(V*I))*100; //
  overall efficiency
8 printf("Efficiency = %.1f percent",n);

```

Scilab code Exa 22.26 Example 26

```

1 //Chapter 22, Problem 26
2 clc;
3 T=15; //torque
4 V=200; //supply voltage
5 n1=1200/60; //speed of motor
6 n=80; //efficiency
7 I=((T*2*pi*n1)/(V*n))*100; //current
  supplied
8 printf("Current supplied = %.2f A",I);

```

Scilab code Exa 22.27 Example 27

```

1 //Chapter 22, Problem 27
2 clc;
3 V=400; //supply voltage
4 I=10; //current
5 R=2; //total
  resistance
6 C=300; //iron, friction
  and windage losses
7 n=((V*I)-(I^2*R)-C)/(V*I))*100; //
  overall efficiency
8 printf("Efficiency = %.1f percent",n);

```

Scilab code Exa 22.28 Example 28

```
1 //Chapter 22, Problem 28, Fig.22.29(b)
2 clc;
3 V=500; //supply voltage
4 Ia=120; //armature current
5 Ia2=60; //armature current 2
6 Ra=0.2; //armature resistance
7 Ra1=0.5; //armature resistance 2
8 n1=10; //speed of motor
9 phi3=0.8; //flux
10 E1=V-(Ia*Ra); //e.m.f
11 E2=V-(Ia2*(Ra+Ra1)); //e.m.f 2
12 n2=n1*E2/E1; //speed of motor 2
13 E3=V-(Ia2*Ra); //e.m.f 3
14 n3=(n1*E3)/(phi3*E1); //speed of motor 2
15 printf("(a) Speed n2 = %.2 f rev/s\n\n",n2);
16 printf("(b) Speed n3 = %.2 f rev/s\n\n",n3);
```

Scilab code Exa 22.29 Example 29

```
1 //Chapter 22, Problem 29
2 clc;
3 V=300; //supply voltage
4 I=90; //total current
5 Ra=0.1; //armature
   resistance
6 n1=15; //speed of motor
7 Rse=0.05; //series winding
   resistance
8 R1=0.2; //diverter
9 E1=V-(I*(Ra+Rse)); //e.m.f
10 R=(R1*Rse)/(R1+Rse); //equivalent
   resistance
11 I1=(R1/(R1+Rse)); //current
```

```

12 Ia=sqrt(I^2/I1); //armature
    current
13 E2=V-(Ia*(Ra+R)); //e.m.f
14 n2=(E2*I*n1)/(E1*I1*Ia); //speed of
    motor 2
15 printf("Speed n2 = %.3f rev/s\n\n",n2);
16 printf("Speed of the motor from %d rev/s to %.3f rev
    /s by inserting 0.2 ohm diverter resistance in
    parallel with the series winding.",n1,n2);

```

Scilab code Exa 22.30 Example 30

```

1 //Chapter 22, Problem 30
2 clc;
3 V=400; //supply voltage
4 I=25; //current
5 Ra=0.4; //armature resistance
6 n1=800; //motor speed 1
7 n2=600; //motor speed 2
8 Rse=0.2; //series winding
    resistance
9 R1=0.2; //series field
    resistance
10 E1=V-(I*(Ra+Rse)); //e.m.f 1
11 E2=E1*n2/n1; //e.m.f 2
12 R=((V-E2)/I)-(Ra+Rse); //resistance
13 printf("Resistance = %f ohms\n\n",R);
14 printf("Thus the addition of a series resistance of
    %fohm has reduced the speed from 800 rev/min to
    600 rev/min.",R);

```

Chapter 23

Three phase induction motors

Scilab code Exa 23.1 Example 1

```
1 //Chapter 23, Problem 1
2 clc;
3 f=50;           //supply frequency
4 p=1;           //pairs of poles
5 ns=(50/1)*60;  //synchronous speed
6 printf("The motor has a two-pole system, hence p,
   the number of pairs of poles, is 1. \nThus,\n\n")
   ;
7 printf("Synchronous speed = %f rev/min",ns);
```

Scilab code Exa 23.2 Example 2

```
1 //Chapter 23, Problem 2
2 clc;
3 ns=900/60;     //synchronous speed
4 f=60;         //supply frequency
5 p=f/ns;       //no of pole pairs
6 printf("number of pole pairs = %d\n",p);
7 printf("therefore, number of poles = %d",p*2);
```

Scilab code Exa 23.3 Example 3

```
1 //Chapter 23, Problem 3
2 clc;
3 ns=6000/60;           //synchronous speed
4 p=2/2;               //pairs of poles
5 f=p*ns;              //supply frequency
6 printf("Frequency = %f Hz",f);
```

Scilab code Exa 23.4 Example 4

```
1 //Chapter 23, Problem 4
2 clc;
3 f=50;                //supply
   frequency
4 p=4/2;               //pairs of poles
5 nr=1455/60;          //rotor speed
6 ns=f/p;              //synchronous
   speed
7 s=((ns-nr)/ns)*100;  //slip
8 printf("(a) synchronous speed = %f rev/s\n\n",ns);
9 printf("(b) Slip , s = %d percent",s);
```

Scilab code Exa 23.5 Example 5

```
1 //Chapter 23, Problem 5
2 clc;
3 f=60;                //supply
   frequency
```

```

4 p=2/2; //pairs of poles
5 ns=(f/p)*60; //synchronous
    speed
6 s=2; //slip
7 nr=ns-((s*ns)/100); //rotor speed
8 printf("(a) synchronous speed = %d rev/min\n\n",ns);
9 printf("(b) Speed of the rotor = %d rev/sec\n\n",nr)
    ;
10 printf("(c) Frequency of the induced emf of the
    rotor = %.1f Hz\n\n", (ns-nr)/60);

```

Scilab code Exa 23.6 Example 6

```

1 //Chapter 23, Problem 6
2 clc;
3 f=50; //supply
    frequency
4 nr=1200/60; //rotor
    speed
5 s=4; //slip
6 ns=(nr/(1-(s/100))); //
    synchronous speed
7 printf("synchronous speed = %d rev/min",ns*60);

```

Scilab code Exa 23.7 Example 7

```

1 //Chapter 23, Problem 7
2 clc;
3 f=50; //supply frequency
4 fr=3; //rotor frequency
5 p=8/2; //pairs of poles
6 s=fr/f; //slip
7 ns=(f/p)*60; //synchronous speed

```

```

8 nr=ns-(s*ns); //rotor speed
9 printf("(a) Slip , s = %f \n\n",s);
10 printf("(b) rotor speed = %f rev/min",nr);

```

Scilab code Exa 23.8 Example 8

```

1 //Chapter 23, Problem 8
2 clc;
3 Psi = 32000; // in Watts
4 Psl = 1200; // in Watts
5 s = 0.05; // slip
6 Pfl = 750; // in Watts
7 //Input power to rotor = stator input power - stator
  losses
8 Pi = Psi - Psl
9 //slip = rotor copper loss/rotor input
10 Pl = s*Pi
11 //Total mechanical power developed by the rotor =
  rotor input power - rotor losses
12 Pr = Pi - Pl
13 //Output power of motor = power developed by the
  rotor - friction and windage losses
14 Po = Pr - Pfl
15 //Efficiency of induction motor = (output power/
  input power)*100
16 eff = (Po/Psi)*100 // in percent
17 printf("\n\n(a) Rotor copper loss is %f kW",Pl/1000)
18 printf("\n\n(b) Total mechanical power developed by
  the rotor is %f kW",Pr/1000)
19 printf("\n\n(c) Output power of motor is %f kW",Po
  /1000)
20 printf("\n\n(d) Efficiency of induction motor is %.2
  f percent",eff)

```

Scilab code Exa 23.9 Example 9

```
1 //Chapter 23, Problem 9
2 clc
3 pi=30.8e3 //input power to rotor
4 pi1=32e3 //stator input power
5 ns=0.35 //percent
6 l=0.75e3 //friction and windage
   losses
7 s=1-ns
8 cl=s*pi
9 P=pi-cl
10 Po=P-l
11 n=(Po/pi1)*100
12 printf("(a) Rotor copper loss = %.3f kW\n\n",cl
   /1000)
13 printf("(b) Efficiency = %.2f percent",n)
```

Scilab code Exa 23.10 Example 10

```
1 //Chapter 23, Problem 10
2 clc;
3 nr = 24; // in rev/sec
4 p = 4/2; // no. of pole
   pairs
5 R2 = 0.35; // in Ohms
6 X2 = 3.5; // in Ohms
7 V = 415; // in Volts
8 tr = 0.85; // turn ratio N2/N1
9 f = 50 ; // in Hz
10 P1 = 770; // in Watt
11 m = 3; // no. of phases
```

```

12
13 //ns is the synchronous speed, f is the frequency in
    hertz of the supply to the stator and p is the
    number of pairs of poles.
14 ns = f/p
15 //The slip, s
16 s = ((ns - nr)/ns)*100 // in percent
17 //Phase voltage, E1 = V/(3^0.5)
18 E1 = V/(3^0.5)
19 //Full load torque
20 T = [m*(tr^2)/(2*pi*ns)]*[(s/100)*E1*E1*R2/(R2*R2 +
    (X2*(s/100))^2)]
21 //Output power, including friction losses
22 Pm = 2*pi*nr*T
23 //power output
24 Po = Pm - P1
25 //Maximum torque occurs when R2 = Xr = 0.35 ohm
26 //Slip
27 sm = R2/X2
28 //maximum torque, Tm
29 Tm = [m*(tr^2)/(2*pi*ns)]*[sm*E1*E1*R2/(R2*R2 + (X2
    *sm)^2)]
30 //speed at which maximum torque occurs
31 nrm = ns*(1 - sm)
32 nrmrpm = nrm*60
33 //At the start, i.e., at standstill, slip, s=1
34 ss = 1
35 //starting torque
36 Ts = [m*(tr^2)/(2*pi*ns)]*[ss*E1*E1*R2/(R2*R2 + (X2
    *ss)^2)]
37 printf("\n\n(a) Synchronous speed is %.0f rev/sec", ns
    )
38 printf("\n\n(b) Slip is %.0f percent", s)
39 printf("\n\n(c) Full load torque is %.2f Nm", T)
40 printf("\n\n(d) power output is %.2E W", Po)
41 printf("\n\n(e) maximum torque is %.2f Nm", Tm)
42 printf("\n\n(f) speed at which maximum torque occurs
    is %.0f rev/min", nrmrpm)

```

```
43 printf("\n\n(g) starting torque is %.2f Nm",Ts)
```

Scilab code Exa 23.11 Example 11

```
1 //Chapter 23, Problem 11
2 clc;
3 nr = 24; // in rev/sec
4 f = 50; // in Hz
5 p = 4/2; // no. of pole pairs
6 V = 415; // in Volts
7 R2 = 0.35; // in Ohms
8 X2 = 3.5; // in Ohms
9 tr = 0.85; // turn ratio N2/N1
10 m = 3; // no. of phases
11 //ns is the synchronous speed, f is the frequency in
    hertz of the supply to the stator and p is the
    number of pairs of poles.
12 ns = f/p
13 //The slip, s
14 s = ((ns - nr)/ns)*100 // in percent
15 //Phase voltage, E1 = V/(3^0.5)
16 E1 = V/(3^0.5)
17 //rotor current,
18 Ir = (s/100)*E1*tr/((R2^2 + (X2*(s/100))^2)^0.5)
19 //Rotor copper loss
20 Pcl = m*R2*(Ir^2)
21 //starting current,
22 ss =1
23 I2 = ss*tr*E1/((R2^2 + (X2*ss)^2)^0.5)
24 printf("\n\n(a) Rotor current is %.2f A",Ir)
25 printf("\n\n(b) Total copper loss is %.2f W",Pcl)
26 printf("\n\n(c) Starting current is %.2f A",I2)
```

Scilab code Exa 23.12 Example 12

```
1 //Chapter 23, Problem 12
2 clc;
3 V = 415; // in Volts
4 Psl = 650; // in Watt
5 pf = 0.87; // power factor
6 Pm = 11770; // watts from part (d),
   Problem 22.10
7 Pcl = 490.35; // watts, Rotor copper loss
   , from part (b), Problem 22.11
8
9 //Stator input power
10 P1 = Pm + Pcl + Psl
11
12 Po = 11000 // watts, Net power output,
   from part (d), Problem 22.10
13 //efficiency = (output/input) *100
14 eff = (Po/P1)*100 // in percent
15
16 //Power input,  $P1 = (3^{0.5}) * VL * IL * \cos(\phi)$ 
17 // pf =  $\cos(\phi)$ 
18 //supply current, IL
19 I = P1/((3^0.5)*V*pf)
20 printf("\\n\\n(a) Stator input power is %.2f kW",P1
   /1000)
21 printf("\\n\\n(b) Efficiency is %.2f percent",eff)
22 printf("\\n\\n(c) Supply current is %.2f A",I)
```

Scilab code Exa 23.13 Example 13

```
1 //Chapter 23, Problem 13
2 clc;
3 p = 4/2; // no. of pole pairs
4 f = 50 ; // in Hz
```

```
5 nr = 24;           // in rev/sec
6 V = 415;          // in Volts
7 R2 = 0.35;        // in Ohms
8 X2 = 3.5;         // in Ohms
9
10 //At the moment of starting , slip ,
11 s = 1
12
13 //Maximum torque occurs when rotor reactance equals
    rotor resistance
14 //for maximum torque
15 R2 = s*X2
16 printf("\n\nResistance of the rotor is %.1f Ohm",R2)
```
