

Scilab Textbook Companion for
Power Electronics
by B. R. Gupta And V. Singhal¹

Created by
Avishek Goyal
Electrical
Electrical Engineering
Thapar University patiala
College Teacher
Dr. Sunil Kumar Singla
Cross-Checked by
Prof. Chaya S

May 26, 2014

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Power Electronics

Author: B. R. Gupta And V. Singhal

Publisher: S. K. Kataria & Sons, New Delhi

Edition: 3

Year: 2002

ISBN: 8185749531

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Power electronics devices	11
2 Controlled Rectifiers	28
3 Inverters	50
4 Choppers	59
5 AC Regulators	68
6 Cycloconverters	76
7 Applications of Thyristors	78
8 Integrated circuits and operational amplifiers	92
9 Number systems	102

List of Scilab Codes

Exa 1.1	Calculate the equivalent capacitance of depletion layer	11
Exa 1.2	Calculate the voltage required to Turn ON the thyristor	11
Exa 1.3	Find gate voltage gate current and resistance to be connected in series	12
Exa 1.4	Calculate the minimum width of the gate pulse	12
Exa 1.5	Calculate the minimum width of the gate pulse	13
Exa 1.6	Find if thyristor will turn ON and the value of resistance	13
Exa 1.7	Find if thyristor will turn OFF and maximum value of resistance	14
Exa 1.8	Can a negative gate current turn off a thyristor	14
Exa 1.9	Find RMS current and form factor	15
Exa 1.10	Find the power supplied to load and average current .	15
Exa 1.11	Calculate the average power loss	16
Exa 1.12	Find the resistance to be connected in series and average power loss	16
Exa 1.13	Find the value of power dissipation when the current flows for different periods of cycle	17
Exa 1.14	Find different current ratings	17
Exa 1.15	Find source resistance gate current and voltage	18
Exa 1.16	Find the thermal resistance and temperature	18
Exa 1.17	Find the maximum loss	19
Exa 1.18	Find the maximum loss	19
Exa 1.19	Design a UJT relaxation oscillator	20
Exa 1.20	Find the values of different components of circuit	20
Exa 1.21	Find the time of conduction of thyristor	21
Exa 1.22	Find the values of L and C	21
Exa 1.23	Find the value of C	22
Exa 1.24	Calculate the value of C and L	22

Exa 1.25	Find the commutation time and the current rating of the thyristor	23
Exa 1.26	Find the value of R and C	23
Exa 1.27	Find the value of R C and snubber power loss and power rating of resistance	24
Exa 1.28	Find the maximum permissible values	24
Exa 1.29	Find number of thyristor in series and parallel	25
Exa 1.30	Find the value of R and C for static and dynamic equalizing circuits	25
Exa 1.31	Find the value of resistance to be connected in series	26
Exa 1.32	Find the steady and transient state rating and derating of thyristor	26
Exa 1.33	Find number of thyristor in series and parallel	27
Exa 1.34	Find Stored charge and peak reverse current	27
Exa 2.3	Calculate the different parameters of half wave diode rectifier	28
Exa 2.4	Calculate the different parameters of full wave centre tapped diode rectifier	29
Exa 2.5	Find the RMS and average voltage and current	30
Exa 2.6	Find the average current	30
Exa 2.7	Find the average current	31
Exa 2.8	Calculate the various parameters of a single phase half wave rectifier	31
Exa 2.9	Find the RMS and average voltage and current of a single phase full wave rectifier	32
Exa 2.10	Calculate the different parameters of full wave converter with centre tapped transformer	32
Exa 2.11	Calculate the voltage rating of full wave central tap and bridge rectifiers	33
Exa 2.12	Find the output voltage firing angle and load current	33
Exa 2.13	Find the average power output of full wave mid point and bridge converter	34
Exa 2.14	Find dc output voltage and power	34
Exa 2.15	Find dc output voltage and power	35
Exa 2.16	Calculate the firing angle and power factor	35
Exa 2.17	Find the average value of load current	36
Exa 2.18	Calculate the different parameters of full wave converter with bridge transformer	36

Exa 2.19	Find the value of dc voltage rms voltage and form factor of a single phase semi converter	37
Exa 2.20	Calculate the different parameters of single phase semi converter bridge	37
Exa 2.21	Calculate the different parameters of single phase full converter	38
Exa 2.22	Calculate the different parameters of single phase full controlled bridge converter	38
Exa 2.23	Calculate the different parameters of single phase full controlled bridge converter	40
Exa 2.24	Calculate peak circulating current and peak current of converter	40
Exa 2.25	Calculate inductance of current limiting reactor and peak current of converter	41
Exa 2.26	Calculate inductance of current limiting reactor and resistance	42
Exa 2.27	Find the parameters of three phase bridge rectifier circuit	42
Exa 2.28	Find the parameters of three phase full converter	43
Exa 2.29	Find the firing angle of a 3 phase fully controlled bridge converter	44
Exa 2.30	Find the parameters of six pulse thyristor converter	44
Exa 2.31	Find the parameters of three phase semi converter bridge circuit	45
Exa 2.32	Find the parameters of three phase fully controlled bridge converter	46
Exa 2.33	Calculate the overlap angles	47
Exa 2.34	Find the value of circulating currents for 3 phase dual converter	47
Exa 2.35	Find the value of inductance	48
Exa 3.1	Find the maximum output frequency	50
Exa 3.2	Find the frequency of output	50
Exa 3.3	Find the available circuit turn off time and maximum possible frequency	51
Exa 3.4	Design a parallel inverter	51
Exa 3.5	Calculate the various parameters of single phase half bridge inverter	52
Exa 3.6	Calculate the various parameters of single phase full bridge inverter	53

Exa 3.7	Calculate the various parameters of full bridge inverter	53
Exa 3.8	Calculate the value of C for proper load commutation	54
Exa 3.9	Calculate peak value of load current	55
Exa 3.10	Find the different parameters of 3 phase bridge inverter for 120degree conduction mode	55
Exa 3.11	Find the different parameters of 3 phase bridge inverter for 180degree conduction mode	56
Exa 3.12	Find the RMS value of load current and thyristor current of 3 phase bridge inverter for 180degree conduction mode	56
Exa 3.13	Find the parameters of single phase full bridge inverter	57
Exa 3.14	Calculate the RMS value of the output voltage	57
Exa 3.15	Calculate the RMS value of the output voltage	58
Exa 4.1	Calculate the period of conduction and blocking	59
Exa 4.2	Calculate the period of conduction and blocking	59
Exa 4.3	Calculate the duty cycle for the rated torque and half of rated torque	60
Exa 4.4	Find the different parameters of a dc chopper	60
Exa 4.5	Find the chopper frequency	61
Exa 4.6	Find the different parameters of a chopper feeding a RL load	61
Exa 4.7	Calculate the load inductance	62
Exa 4.8	Calculate the current	63
Exa 4.9	Find the speed of motor	63
Exa 4.10	Calculate average load voltage	64
Exa 4.11	Find maximum minimum and average load current and load voltage	64
Exa 4.12	Find maximum minimum and average output voltage	65
Exa 4.13	Calculate the series inductance in the circuit	65
Exa 4.14	Calculate the motor speed and current swing	66
Exa 4.15	Calculate the value of capacitance and inductance	66
Exa 4.16	Calculate the period of conduction of a step up chopper	67
Exa 4.17	Calculate the period of conduction of a step up chopper	67
Exa 5.1	Calculate the different parameters of AC voltage regulator using integral cycle control	68
Exa 5.2	Calculate the different parameters of single phase half wave AC regulator	69

Exa 5.3	Calculate the different parameters of single phase full wave AC regulator	70
Exa 5.4	Calculate the different parameters of single phase full wave AC regulator	70
Exa 5.5	Find RMS output voltage and average power	71
Exa 5.6	Find the firing angle	72
Exa 5.7	Find the conduction angle and RMS output voltage	72
Exa 5.8	Calculate the different parameters of single phase full wave AC regulator	73
Exa 5.10	Find the current and voltage rating	73
Exa 5.11	Calculate the different parameters of 3 phase star connected resistance load with firing angle 30 degree	74
Exa 5.12	Calculate the different parameters of 3 phase star connected resistance load with firing angle 60 degree	75
Exa 6.1	Find the input voltage SCR rating and Input Power Factor	76
Exa 6.2	Find RMS value of output voltage for firing angle 30 and 45 degree	76
Exa 6.3	Find RMS value of output voltage for firing angle 0 and 30 degree	77
Exa 7.1	Find the value of Voltage which will turn On the crowbar	78
Exa 7.2	Find the value of input voltage	78
Exa 7.3	Find the value of R and C	79
Exa 7.4	Find Duty cycle and Ratio for different output powers	79
Exa 7.5	Find RMS value of output voltage	80
Exa 7.6	Find the power supplied to heater for different firing angles	80
Exa 7.7	Find the firing angles when different powers are supplied to heater	81
Exa 7.8	Find the current rating and peak inverse voltage	82
Exa 7.9	Find firing angle and power factor of converter in the armature circuit	82
Exa 7.10	Find the torque developed and motor speed	83
Exa 7.11	Find armature current and Firing angle of the semi converter	84
Exa 7.12	Find the firing angle of converter in the armature circuit and power fed back to the source	84
Exa 7.13	Find the firing angle of converter in the armature circuit	85

Exa 7.14	Find the input power speed and torque of separately excited dc motor	85
Exa 7.15	Find the average voltage power dissipated and motor speed of the chopper	86
Exa 7.16	Find the speed for different values of torque	87
Exa 7.17	Find the speed at no load and firing angle	88
Exa 7.18	Find the motor speed	89
Exa 7.19	Find the load torque stator applied voltage and rotor current	89
Exa 7.20	Find the load torque stator applied voltage and rotor current	90
Exa 7.21	Find the starting torques at different frequencies	91
Exa 8.1	Find dc currents and voltages	92
Exa 8.2	Calculate the different parameters of differential amplifier	92
Exa 8.3	Find the closed loop gain output and error voltage	93
Exa 8.4	Find the closed loop gain output and error voltage	94
Exa 8.5	Find the input and output impedances	94
Exa 8.6	Find closed loop gain and desensitivity	95
Exa 8.7	Find the closed loop gain and upper cut off frequency	95
Exa 8.8	Find the slew rate	96
Exa 8.9	Find the slew rate distortion of the op amp	96
Exa 8.10	Find the slew rate distortion of the op amp and amplitude of the input signal	97
Exa 8.11	Find the different parameters of inverting amplifier	97
Exa 8.12	Find the different parameters of non inverting amplifier	98
Exa 8.13	Find the different parameters of ac amplifier	98
Exa 8.14	Find the output voltage	99
Exa 8.17	Find the output voltage	100
Exa 8.18	Find CMRR in dB	100
Exa 8.21	Find the different parameters of high pass filter	100
Exa 8.22	Find the different parameters of low pass filter	101
Exa 9.1	Convert decimal number into equivalent binary number	102
Exa 9.2	Convert decimal number into equivalent binary number	102
Exa 9.3	Convert binary number into equivalent decimal number	103
Exa 9.4	Convert decimal number into equivalent binary number	103
Exa 9.5	Calculate the subtraction of two binary numbers	103
Exa 9.6	Calculate the subtraction of two binary numbers	104
Exa 9.7	Express the decimals in 16 bit signed binary system	104

Exa 9.8	Calculate the twos complement representation	105
Exa 9.9	Find the largest positive and negative number for 8 bits	106
Exa 9.10	Calculate addition and subtraction of the numbers . .	106
Exa 9.11	Calculate addition and subtraction of the numbers . .	107
Exa 9.12	Convert decimal number into equivalent binary number	107
Exa 9.13	Convert decimal number into equivalent binary number	108
Exa 9.14	Convert decimal number into equivalent binary number	109
Exa 9.15	Find the addition of binary numbers	110
Exa 9.16	Convert binary number into equivalent decimal number	110
Exa 9.17	Convert hexadecimal number into equivalent decimal number	112
Exa 9.18	Convert decimal number into equivalent hexadecimal number	112
Exa 9.19	Convert decimal number into equivalent hexadecimal number	112
Exa 9.20	Convert hexadecimal number into equivalent decimal number	113

Chapter 1

Power electronics devices

Scilab code Exa 1.1 Calculate the equivalent capacitance of depletion layer

```
1 //1.1
2 clc;
3 Ic=8*10^-3;
4 //let dv/dt =A
5 A=190*10^6;
6 C=Ic/A*10^12;
7 printf("Equivalent capacitance of depletion layer =
   %.1f uF", C)
```

Scilab code Exa 1.2 Calculate the voltage required to Turn ON the thyristor

```
1 //1.2
2 clc;
3 disp('When thyristor is not conducting there is no
   current through it')
4 disp('so Vo=20V')
5 VG=0.75;
```

```

6 IG=7*10^-3;
7 RG=2000;
8 Vs=VG+IG*RG;
9 printf(" Voltage required to Turn On The thyristor =
    %.2f V", Vs)
10 R= 200;
11 VR=5*10^-3*R;
12 printf("/nVoltage drop across R = %.0f V", VR)
13 disp('Hence Vcc should be reduced to less than 1V')
14 Vconduct=0.7;
15 Vreq=VR+Vconduct;
16 printf(" Voltage required = %.1f V", Vreq)
17 disp('Hence Vcc should be reduced to less than 1.7V'
    )

```

Scilab code Exa 1.3 Find gate voltage gate current and resistance to be connected in series

```

1 //1.3
2 clc;
3 P_loss_avg=0.6;
4 P_loss_conduction=0.6*2*%pi/%pi;
5 Ig=0.314;
6 printf(" Ig=%.3f A", Ig)
7 Vg=1+9*Ig;
8 printf("\nVg=%.3f V", Vg)
9 Rg=(24-9*Ig)/Ig;
10 printf("\nResistance to be connected in series=%.2f
    ohm", Rg)

```

Scilab code Exa 1.4 Calculate the minimum width of the gate pulse

```

1 //1.4

```

```

2  clc;
3  V=100;
4  L=10;
5  i=80*10-3;
6  t=i*L/V*103;
7  printf("t= %.0f ms", t)
8  disp('So the width of the pulse should be more than
      8 ms')

```

Scilab code Exa 1.5 Calculate the minimum width of the gate pulse

```

1  // 1.5
2  clc;
3  V=100;
4  R=10;
5  i=50*10-3;
6  t=-0.5*log(1-((i*R/V)))*103
7  printf("t= %.1f ms", t)
8  disp('So the minimum width of the gate pulse is 2.5
      ms')

```

Scilab code Exa 1.6 Find if thyristor will turn ON and the value of resistance

```

1  // 1.6
2  clc;
3  V=90;
4  R=25;
5  t=40*10-6;
6  L=0.5;
7  i=(V/R)*(1-exp(-R*t/L))
8  iL=40*10-3;
9  printf("The circuit current is= %.4f A", i)

```

```

10 disp('Since the circuit current is less than
        latching current of 40mA so thyristor will not
        turn ON')
11 R=V/(iL-i);
12 printf("R= %.0f Ohm", R)
13 disp('R should be less than 2743 ohm')

```

Scilab code Exa 1.7 Find if thyristor will turn OFF and maximum value of resistance

```

1 //1.7
2 clc;
3 V=100;
4 R=20;
5 t=50*10^-6;
6 L=0.5;
7 i=(V/R)*(1-exp(-R*t/L))
8 iH=50*10^-3;
9 printf("The circuit current is= %.5f A", i)
10 disp('Since the circuit current is less than holding
        current of 50mA so thyristor will turn OFF')
11 R=V/(iH-i);
12 printf("Maximum value of R= %.3f Ohm", R)

```

Scilab code Exa 1.8 Can a negative gate current turn off a thyristor

```

1 //1.8
2 clc;
3 disp('A negative gate current cannot turn off a
        thyristor. This is due to the reason that cathode
        region is much bigger in area than gate region')

```

Scilab code Exa 1.9 Find RMS current and form factor

```
1 //1.9
2 clc;
3 I=120;
4 gama=180;
5 th=360;
6 I_rms=I*(gama/th)^0.5;
7 printf("The RMS value of current= %.2 f A",I_rms)
8 I_avg=I*(gama/th);
9 Form_factor=I_rms/I_avg;
10 printf("\nForm factor= %.3 f A",Form_factor)
```

Scilab code Exa 1.10 Find the power supplied to load and average current

```
1 //1.10
2 clc;
3 disp('If the thyristor is fired at 60 degree')
4 Irms=(0.8405*((%pi-%pi*60/180)-sin(2*%pi)/2+sin(2*
   %pi*60/180)/2))^0.5;
5 R=100;
6 P=Irms^2*R;
7 printf("Power supplied to load=%.0 f W",P)
8 disp('If the thyristor is fired at 45 degree')
9 Irms=(0.8405*((%pi-%pi*45/180)-sin(2*%pi)/2+sin(2*
   %pi*45/180)/2))^0.5;
10 R=100;
11 P=Irms^2*R;
12 printf("Power supplied to load=%.1 f W",P)
13 disp('If the thyristor is fired at 60 degree')
14 Iavg=3.25/(2*%pi)*(-cos(%pi)+cos(%pi*60/180))
15 printf("Average Current=%.3 f A",Iavg)
```



```

16 disp('If the thyristor is fired at 45 degree')
17 Iavg=3.25/(2*%pi)*(-cos(%pi)+cos(%pi*45/180))
18 printf("Average Current=%.3f A",Iavg)

```

Scilab code Exa 1.11 Calculate the average power loss

```

1 //1.11
2 clc;
3 //when conduction period is 2*pi
4 amplitude=200;
5 pd=1.8;
6 power_loss_average= amplitude*pd*2*%pi/(2*%pi);
7 printf("power loss average when conduction period is
      2*pi= %.0f W",power_loss_average)
8
9 //when conduction period is pi
10 amplitude=400;
11 pd=1.9;
12 power_loss_average= amplitude*pd*%pi/(2*%pi);
13 printf("\npower loss average when conduction period
      is pi= %.0f W",power_loss_average)

```

Scilab code Exa 1.12 Find the resistance to be connected in series and average power loss

```

1 //1.12
2 clc;
3 P_loss_peak=6;
4 Ig=0.763;
5 Vg=1+9*Ig;
6 Rg=(11-9*Ig)/Ig;
7 printf("\nResistance to be connected in series=%.3f
      ohm", Rg)

```

```

8 duty=0.3;
9 P_loss_average=P_loss_peak*duty;
10 printf("\nAverage power loss =%.1f W",
        P_loss_average)

```

Scilab code Exa 1.13 Find the value of power dissipation when the current flows for different periods of cycle

```

1 //1.13
2 clc;
3 disp('when current is constant 20A')
4 It=20;
5 Vt=0.9+0.02*It;
6 P_dissipation=Vt*It;
7 printf("Power dissipation=%.0f W",P_dissipation)
8 disp('when current is constant 20A for one half
        cycle in each full cycle')
9 P_dissipation=Vt*It/2;
10 printf("Power dissipation=%.0f W",P_dissipation)
11 disp('when current is constant 20A for one third
        cycle in each full cycle')
12 P_dissipation=Vt*It/3;
13 printf("Power dissipation=%.2f W",P_dissipation)

```

Scilab code Exa 1.14 Find different current ratings

```

1 //1.14
2 clc;
3 Isub=2000;
4 T=10*10^-3;
5 t=5*10^-3;
6 I=(Isub^2*t/T)^0.5;
7 printf("one cycle surge current rating=%.1f A", I)

```

```

8 //a=I^2t
9 a=I^2*T;
10 printf("\nI^2t=%0.1 f A^2Sec", a)

```

Scilab code Exa 1.15 Find source resistance gate current and voltage

```

1 //1.15
2 clc;
3 P=0.3;
4 Vs=12;
5 disp('Since load line has a slope of -100V/A, the
      source resistance for the gate is 100 ohm')
6 Rs=100;
7 // since Vs=Vg+Ig*Rs
8 // on solving Ig=35.5 mA
9 Ig=35.5*10^-3;
10 printf("\nGate current=%0.4 f A", Ig)
11 Vg=P/Ig;
12 printf("\nGate voltage=%0.2 f V", Vg)

```

Scilab code Exa 1.16 Find the thermal resistance and temperature

```

1 //1.16
2 clc;
3 l=0.2;
4 w=0.01;
5 d=0.01;
6 the_cond=220;
7 the_res=1/(the_cond*w*d);
8 printf("Thermal resistance = %0.3f degree C/W",
      the_res)
9 T1=30;
10 P=3;

```

```
11 T2=P*the_res+T1;
12 printf("\nTemperature of the surface = %.2f degree C
    ", T2)
```

Scilab code Exa 1.17 Find the maximum loss

```
1 // 1.17
2 clc;
3 l=2*10^-3;
4 A=12*10^-4;
5 the_cond=220;
6 the_res=1/(the_cond*A);
7 T=4; //T=T2-T1
8 P=T/the_res;
9 printf("Maximum loss which can be handled by module=
    %.2f W", P)
```

Scilab code Exa 1.18 Find the maximum loss

```
1 // 1.18
2 clc;
3 T2=125;
4 T1=50;
5 T=T2-T1;
6 P=30;
7 Total_the_res=T/P;
8 the_res=Total_the_res-1-0.3;
9 printf("Thermal resistance of heat sink= %.1f degree
    C/W", the_res)
```

Scilab code Exa 1.19 Design a UJT relaxation oscillator

```
1 // 1.19
2 clc;
3 T=1/50;
4 V=32;
5 Vp=0.63*V+0.5;
6 C=0.4*10^-6;
7 Ip=10*10^-6;
8 Rmax=(V-Vp)/Ip;
9 printf("Rmax=%0.0 f ohm", Rmax)
10 Vv=3.5;
11 Iv=10*10^-3;
12 Rmin=(V-Vv)/Iv;
13 printf("\nRmin=%0.0 f ohm", Rmin)
14 R=T/(C*log(1/(1-0.63)));
15 printf("\nR=%0.0 f ohm", R)
16 disp('since the value of R is between Rmin and Rmax
       so the value is suitable')
17 R4=50*10^-6/C;
18 printf("\nR4=%0.0 f ohm", R4)
19 R3=10^4/(0.63*V);
20 printf("\nR3=%0.0 f ohm", R3)
```

Scilab code Exa 1.20 Find the values of different components of circuit

```
1 // 1.20
2 clc;
3 T=.5*10^-3;
4 V=10;
5 Vp=0.6*V+0.5;
6 Ip=5*10^-3;
7 Rmax=(V-Vp)/Ip;
8 printf("Rmax=%0.0 f ohm", Rmax)
9 C=1*10^-6;
```

```

10 R=T/(C*log(1/(1-0.6)));
11 printf("\nR=%0.1f ohm", R)
12 disp('since the value of R is less than Rmax so the
      value is suitable')

```

Scilab code Exa 1.21 Find the time of conduction of thyristor

```

1 //1.21
2 clc;
3 R=0.8;
4 L=10*10^-6;
5 C=50*10^-6;
6 t0=10^6*pi/((1/(L*C))-(R^2/(4*L^2)))^0.5;
7 printf("Time of conduction of thyristor= %0.2f us",
      t0)

```

Scilab code Exa 1.22 Find the values of L and C

```

1 //1.22
2 clc;
3 Ip=16;
4 V=90;
5 // C/L=(Ip/V)^2; (i)
6 // Assume that circuit is reverse biased for one-
      fourth period of resonant circuit. thus
7 // %pi/2*(L*C)^0.5=40*10^-6; (ii)
8 // on solving (i) and (ii)
9 C=4.527*10^-6;
10 L=C/(Ip/V)^2*10^6;
11 C=4.527*10^-6*10^6;
12 printf("C=%0.3f uF", C)
13 printf("\nL=%0.2f uH", L)

```

Scilab code Exa 1.23 Find the value of C

```
1 // 1.23
2 clc;
3 t_off=50*10^-6;
4 R1=10;
5 a=log(2);
6 C=t_off/(a*R1)*10^6;
7 printf("The value of C= %.2f uF",C)
```

Scilab code Exa 1.24 Calculate the value of C and L

```
1 // 1.24
2 clc;
3 Vc=100;
4 IL=40;
5 t_off=40*10^-6*1.5;
6 C=IL*t_off/Vc;
7 printf("The value of capacitor= %.6f F",C)
8 //L>(VC^2*C/IL^2);
9 //IC_peak=Vc*(C/L)^0.5;
10 //IC_peak should be less than maximum load current
    so if L=2*10^-4
11 L=2*10^-4;
12 IC_peak=Vc*(C/L)^0.5;
13 printf("\nPeak capacitor current= %.2f A",IC_peak)
14 disp('Since the peak capacitor current less than
    maximum load current 40 A so L=2*10^-4 and C=24
    uF')
```

Scilab code Exa 1.25 Find the commutation time and the current rating of the thyristor

```
1 //1.25
2 clc;
3 L=0.1*10^-3;
4 Vc=100;
5 C=10*10^-6;
6 IL=10;
7 t_off=Vc*C/IL*10^6;
8 printf("Commutation time= %.0f us",t_off)
9 disp('The commutation time of the thyristor is more
      than the turn off time of the main thyristor i.e
      . 25us and is thus sufficient to commutate the
      main thyristor ')
10 IC_peak= Vc*(C/L)^0.5;
11 printf("Peak capacitor current= %.2f A",IC_peak)
12 disp('The maximum current rating of the thyristor
      should be more than 31.62A')
```

Scilab code Exa 1.26 Find the value of R and C

```
1 //1.26
2 clc;
3 Vm=230*2^0.5;
4 L=0.2*10^-3;
5 //a=dv/dt
6 a=25*10^6;
7 sig=0.65;
8 C=(1/(2*L))*(0.564*Vm/a)^2*10^9;
9 R=2*sig*(L/(C*10^-9))^0.5;
10 printf("The value of capacitor= %.2f nF",C)
11 printf("\nThe value of Resistor= %.1f Ohm",R)
```

Scilab code Exa 1.27 Find the value of R C and snubber power loss and power rating of resistance

```
1 // 1.27
2 clc;
3 f=2000;
4 V=300;
5 RL=10;
6 //a=dv/dt
7 a=100*10^6;
8 R=300/100;
9 C=(0.632*V*RL)/(a*(R+RL)^2)*10^6;
10 printf("The value of capacitor= %.3f uF",C)
11 Power_Loss_snubber=0.5*C*10^-6*V^2*f;
12 printf("\nSnubber Power Loss= %.2f W",
        Power_Loss_snubber)
13 disp('All the energy stored in the capacitance C is
        dissipated in resistance R. Hence power Rating of
        R is 10.1W')
```

Scilab code Exa 1.28 Find the maximum permissible values

```
1 // 1.28
2 clc;
3 C=6*10^-6;
4 R=4;
5 V=300;
6 L=6*10^-6;
7 b_max=V/L*10^-6; // b=di/dt
8 printf("The maximum permissible value of di/dt = %.0
        f MA/s",b_max)
9 I_sc=V/R;
```

```

10 //a=dv/dt
11 a=((R*b_max*10^6)+(Isc/C))*10^-6;
12 printf("\nThe maximum permissible value of dv/dt = %
    .1 f MV/s",a)

```

Scilab code Exa 1.29 Find number of thyristor in series and parallel

```

1 //1.29
2 clc;
3 Im=750;
4 De=0.25;
5 It=175;
6 np=(Im/It)/(1-De);
7 printf("np = %.2 f ",np)
8 disp('so the no. of thyristors in parallel are 6')
9 Vs=3000;
10 De=0.25;
11 Vd=800;
12 ns=(Vs/Vd)/(1-De);
13 printf("ns = %.2 f ",ns)
14 disp('so the no. of thyristors in series are 5')

```

Scilab code Exa 1.30 Find the value of R and C for static and dynamic equalizing circuits

```

1 //1.30
2 clc;
3 ns=5;
4 Vd=800;
5 Vs=3000;
6 Ib=8*10^-3;
7 dQ=30*10^-6;
8 R=(ns*Vd-Vs)/((ns-1)*Ib)

```

```

9 C=((ns-1)*dQ)/(ns*Vd-Vs)*10^6;
10 printf("The value of resistance = %.2f ohm ",R)
11 printf("\nThe value of capacitance = %.2f uF ",C)

```

Scilab code Exa 1.31 Find the value of resistance to be connected in series

```

1 //1.31
2 clc;
3 R=(1.5-1.2)/100;
4 printf(" The value of resistance to be connected in
   series= %.3f ohm" ,R)

```

Scilab code Exa 1.32 Find the steady and transient state rating and derating of thyristor

```

1 //1.32
2 clc;
3 ns=12;
4 Vd=800;
5 V=16000;
6 Ib=10*10^-3;
7 dQ=150*10^-6;
8 C=0.5*10^-6;
9 R=56*10^3;
10 Vd=(V+(ns-1)*R*Ib)/ns;
11 printf("maximum steady state voltage rating of each
   thyristor = %.2f V",Vd)
12 De=1-(V/(ns*Vd));
13 printf("\nSteady state voltage derating = %.3f ",De)
14 Vd=(V+(ns-1)*(dQ/C))/ns;
15 printf("\nmaximum transient state voltage rating of
   each thyristor = %.2f V",Vd)
16 De=1-(V/(ns*Vd));

```

```
17 printf("\ntransient state voltage derating = %.3f ",
    De)
```

Scilab code Exa 1.33 Find number of thyristor in series and parallel

```
1 //1.33
2 clc;
3 Im=1000;
4 De=0.14;
5 It=75;
6 np=(Im/It)/(1-De);
7 printf("np = %.2f ",np)
8 disp('so the no. of thyristors in parallel are 16')
9 Vs=7500;
10 De=0.14;
11 Vd=500;
12 ns=(Vs/Vd)/(1-De);
13 printf("ns = %.2f ",ns)
14 disp('so the no. of thyristors in series are 18')
```

Scilab code Exa 1.34 Find Stored charge and peak reverse current

```
1 //1.34
2 clc;
3 trr=2.5*10^-6;
4 //b=di/dt
5 b=35*10^6;
6 Qrr=0.5*trr^2*b*10^6;
7 printf(" Stored charge= %.3f uC",Qrr)
8 Irr=(2*Qrr*10^-6*b)^0.5;
9 printf(" Peak reverse current= %.1f A",Irr)
```

Chapter 2

Controlled Rectifiers

Scilab code Exa 2.3 Calculate the different parameters of half wave diode rectifier

```
1 //2.3
2 clc;
3 Vp_sec=230*2^0.5/4;
4 alph=asind(12/Vp_sec);
5 alph1=180-alph;
6 //the diode will conduct from 8.89 degree to 171.51
  degree
7 Angle_conduction=alph1-alph;
8 printf("Conduction Angle = %.2f degree",
  Angle_conduction)
9 Idc=4;
10 R=1/(2*Idc*pi)*(2*Vp_sec*cosd(alph)+(2*12*alph*pi
  /180)-12*pi);
11 printf("\nResistance = %.2f ohm", R)
12 Irms=((1/(2*pi*R^2))*(((Vp_sec^2/2+12^2)*(%pi-2*
  alph*pi/180))+(Vp_sec^2/2*sind(2*alph))-(4*
  Vp_sec*12*cosd(alph))))^0.5;
13 P_rating=Irms^2*R;
14 printf("\nPower rating of resistor = %.2f W",
  P_rating)
```

```

15 Pdc=12*Idc;
16 t_charging=150/Pdc;
17 printf("\nCharging time = %.3f h", t_charging)
18 Rectifier_efficiency= Pdc/(Pdc+Irms^2*R);
19 printf("\nRectifier efficiency = %.2f ",
    Rectifier_efficiency)
20 PIV=Vp_sec+12;
21 printf("\nPIV = %.3f V",PIV)

```

Scilab code Exa 2.4 Calculate the different parameters of full wave centre tapped diode rectifier

```

1 //2.4
2 clc;
3 Vm=100;
4 R=5;
5 Idc=2*Vm/(%pi*R);
6 printf("\nIdc = %.3f A",Idc)
7 Vdc=Idc*R;
8 printf("\nVdc = %.3f V",Vdc)
9 Irms=0.707*Vm/R;
10 printf("\nIrms = %.3f A",Irms)
11 Vrms=Irms*R;
12 printf("\nVrms = %.3f V",Vrms)
13 Pdc=Idc^2*R;
14 printf("\nPdc = %.3f W",Pdc)
15 Pac=Irms^2*R;
16 printf("\nPac = %.3f W",Pac)
17 FF=Vrms/Vdc;
18 printf("\nFF = %.3f ",FF)
19 RF=(FF^2-1)^0.5;
20 printf("\nRF = %.3f ",RF)
21 TUF=0.5732;
22 printf("\nTUF = %.3f ",TUF)
23 PIV=2*Vm;

```

```

24 printf("\nPIV = %.0 f V",PIV)
25 CF=0.707;
26 printf("\nCF = %.3 f ",CF)

```

Scilab code Exa 2.5 Find the RMS and average voltage and current

```

1 //2.5
2 clc;
3 Vm=400;
4 alpha=30;
5 R=50;
6 Vdc=(Vm/(2*pi))*(1+cosd(alpha));
7 printf("Average Load voltage = %.1 f V", Vdc)
8 Load_current_average=Vdc/R;
9 printf("\nAverage Load current = %.3 f A",
    Load_current_average)
10 V=400*(((pi-(pi/6))/(4*pi))+sind(60)/(8*pi))
    ^0.5;
11 printf("\nRMS voltage = %.1 f V", V)
12 RMS_current=V/R;
13 printf("\nRMS current = %.3 f A", RMS_current)

```

Scilab code Exa 2.6 Find the average current

```

1 //2.6
2 clc;
3 current_average=(1/(2*pi))*(-10*cos(5*pi/6)+10*cos
    (pi/6)-(5*5*pi/6)+(5*pi/6));
4 printf("\nAverage current = %.3 f A",
    current_average)

```

Scilab code Exa 2.7 Find the average current

```
1 //2.7
2 clc;
3 // the thyristor will conduct when instantaneous
   value of source emf is more than the back emf i.e
   .  $2^{0.5} \times 100 \sin wt = 55.5$ 
4 wt1=asind(55.5/(2^0.5*110));
5 wt2=180-wt1;
6 current_average=(1/(2*pi))*(-15.554*(cosd(wt2)-cosd
   (wt1))-5.55*(2.7768-0.3684));
7 printf("\nAverage current = %.2f A",
   current_average)
```

Scilab code Exa 2.8 Calculate the various parameters of a single phase half wave rectifier

```
1 //2.8
2 clc;
3 Vm=230*2^0.5;
4 Vdc=(Vm/(2*pi))*(1+cosd(90));
5 Idc=Vdc/15;
6 Vrms=Vm*(((%pi-(%pi/2))/(4*pi))+ (sin(2*pi)/(8*pi)
   ))^0.5;
7 Irms=Vrms/15;
8 Pdc=Vdc*Idc;
9 Pac=Vrms*Irms;
10 Rec_effi=Pdc/Pac;
11 Form_factor=Vrms/Vdc;
12 printf("\n Form Factor = %.1f ", Form_factor)
13 ripple_factor=(Form_factor^2-1)^0.5;
14 printf("\n Ripple Factor = %.1f ", ripple_factor)
15 VA_rating=230*7.66;
16 printf("\n VA rating = %.1f VA", VA_rating)
17 TUF=Pdc/VA_rating;
```



```

18 printf("\n TUF = %.3 f ", Form_factor)
19 PIV=Vm;
20 printf("\n PIV = %.1 f V", PIV)

```

Scilab code Exa 2.9 Find the RMS and average voltage and current of a single phase full wave rectifier

```

1 //2.9
2 clc;
3 Vm=150*2^0.5;
4 Vdc=(Vm/(%pi))*(1+cosd(45));
5 R=30;
6 Load_current_average=Vdc/R;
7 printf("\nAverage Load current = %.2 f A",
        Load_current_average)
8 Vrms=Vm*(((%pi-(%pi/4))/(2*%pi))+(sind(90)/(4*%pi)))
        ^0.5;
9 printf("\nRMS voltage = %.1 f V", Vrms)
10 RMS_current=Vrms/R;
11 printf("\nRMS current = %.3 f A", RMS_current)

```

Scilab code Exa 2.10 Calculate the different parameters of full wave converter with centre tapped transformer

```

1 //2.10
2 clc;
3 Vdc=100;
4 Vm=(Vdc+1.7)*%pi/(2*cosd(30));
5 Vrms_sec=Vm/2^0.5;
6 Vrms_pri=230;
7 Turn_ratio=Vrms_pri/Vrms_sec;
8 printf("\nTurn Ratio = %.2 f ", Turn_ratio)
9 Ip=15;

```

```

10 Irms_sec=(Ip^2/2)^0.5;
11 Trans_rating=2*Vrms_sec*Irms_sec;
12 printf("\nTransformer rating = %.2f VA",
    Trans_rating)
13 PIV=2*Vm;
14 printf("\nPIV = %.2f V", PIV)
15 printf("\nRMS value of thyristor current = %.2f A",
    Irms_sec)

```

Scilab code Exa 2.11 Calculate the voltage rating of full wave central tap and bridge rectifiers

```

1 //2.11
2 clc;
3 Idc=50;
4 Vdc=10*1000/Idc;
5 Vm=200*%pi/2;
6 PIV_central_tap=2*Vm;
7 V_rating_central_tap =2*PIV_central_tap;
8 printf("The rated voltage of full wave central tap
    transformer rectifier = %.2f V",
    V_rating_central_tap )
9 PIV_bridge=Vm;
10 V_rating_bridge=2*PIV_bridge;
11 printf("\nThe rated voltage of full wave bridge
    rectifier = %.2f V", V_rating_bridge )

```

Scilab code Exa 2.12 Find the output voltage firing angle and load current

```

1 //2.12
2 clc;
3 Vm=230*2^0.5;

```

```

4 Vrms=(800/1000*230^2)^0.5;
5 printf("Output Voltage = %.2f V", Vrms )
6 //Vrms=Vm*((%pi-alpha)/(2*%pi)+sind(2*alpha)/(4*%pi))
  ^0.5 on solving
7 alph=61;
8 printf("\nFiring angle = %.0f degree", alph )
9 I=800/Vrms;
10 printf("\nLoad current = %.2f A", I )

```

Scilab code Exa 2.13 Find the average power output of full wave mid point and bridge converter

```

1 //2.13
2 clc;
3 disp('For Mid point converter')
4 Vm=800/(2*2.5);
5 alph=0;
6 Vo=Vm/(%pi)*(1+cosd(alph));
7 Idc=30/2.5;
8 Pdc=Idc*Vo;
9 printf("Average output power = %.2f W", Pdc )
10 disp('For bridge converter')
11 Vm=800/(2.5);
12 alph=0;
13 Vo=Vm/(%pi)*(1+cosd(alph));
14 Idc=30/2.5;
15 Pdc=Idc*Vo;
16 printf("Average output power = %.2f W", Pdc )

```

Scilab code Exa 2.14 Find dc output voltage and power

```

1 //2.14
2 clc;

```

```

3 Vm=230*2^0.5;
4 alph=30;
5 Vo=Vm/(2*%pi)*(3+cosd(alph));
6 Idc=Vo/10;
7 printf("dc output voltage = %.1f V", Vo )
8 Pdc=Idc*Vo;
9 printf("\ndc power = %.2f W", Pdc )

```

Scilab code Exa 2.15 Find dc output voltage and power

```

1 //2.15
2 clc;
3 Vm=230*2^0.5;
4 Vo=2*Vm/%pi;
5 Idc=Vo/10;
6 printf("dc output voltage = %.2f V", Vo )
7 Pdc=Idc*Vo;
8 printf("\ndc power = %.2f W", Pdc )

```

Scilab code Exa 2.16 Calculate the firing angle and power factor

```

1 //
2 clc;
3 disp(' If E=100 V')
4 Vm=230*2^0.5;
5 E=100;
6 R=0.5;
7 Io=15;
8 alph=acosd((E+15*0.5)*%pi/(2*Vm));
9 printf("Firing Angle = %.2f degree", alph)
10 pf=(100*15+15^2*0.5)/(230*15);
11 printf("\nPower factor = %.3f lagging", pf)
12 disp(' If E=-100 V')

```

```

13 E=-100;
14 alph=acosd((E+15*0.5)*%pi/(2*Vm));
15 printf("\nFiring Angle when E is -100 = %.2 f W",
        alph)
16 pf=(100*15-15^2*0.5)/(230*15);
17 printf("\nPower factor = %.3 f lagging", pf)

```

Scilab code Exa 2.17 Find the average value of load current

```

1 //2.17
2 clc;
3 Vm=230*2^0.5;
4 alph=40;
5 Io=((2*Vm/%pi*cosd(alph))-50)/5;
6 printf("Average value of load current = %.2 f A", Io)

```

Scilab code Exa 2.18 Calculate the different parameters of full wave converter with bridge transformer

```

1 //2.18
2 clc;
3 Vdc=100;
4 Vm=(Vdc+2*1.7)*%pi/(2*cosd(30));
5 Vrms_sec=Vm/2^0.5;
6 Vrms_pri=230;
7 Turn_ratio=Vrms_pri/Vrms_sec;
8 printf("\nTurn Ratio = %.2 f ", Turn_ratio)
9 Irms_sec=15/2^0.5;
10 Ip=15;
11 Trans_rating=Vrms_sec*Ip;
12 printf("\nTransformer rating = %.2 f VA",
        Trans_rating)
13 PIV=Vm;

```

```

14 printf("\nPIV = %.2 f V", PIV)
15 printf("\nRMS value of thyristor current = %.2 f A",
    Irms_sec)

```

Scilab code Exa 2.19 Find the value of dc voltage rms voltage and form factor of a single phase semi converter

```

1 //2.19
2 clc;
3 Vm=230*2^0.5;
4 Vdc=Vm/%pi*(1+cosd(90));
5 printf("dc value of voltage = %.2 f V", Vdc)
6 Vrms=230*((1/%pi)*(%pi-(%pi/2)+sin(%pi)/2))^0.5;
7 printf("\n RMS value of voltage= %.2 f V", Vrms)
8 form_factor=Vrms/Vdc;
9 printf("\nForm factor = %.2 f ", form_factor)

```

Scilab code Exa 2.20 Calculate the different parameters of single phase semi converter bridge

```

1 //2.20
2 clc;
3 Vm=230*2^0.5;
4 Vdc=Vm/%pi*(1+cosd(90));
5 printf("dc value of voltage = %.2 f V", Vdc)
6 Vrms=230*((1/%pi)*(%pi-(%pi/2)+sin(%pi)/2))^0.5;
7 printf("\n RMS value of voltage= %.2 f V", Vrms)
8 Is=(1-(%pi/2)/%pi)^0.5;
9 Is1=2/%pi*2^0.5*cos(%pi/4);
10 HF=((Is/Is1)^2-1)^0.5;
11 printf("\n Harmonic factor= %.3 f ", HF)
12 Displacement_factor=cos(-%pi/4);

```

```

13 printf("\n Displacement factor= %.4f ",
    Displacement_factor)
14 Power_factor=Is1/Is*cos(-%pi/4);
15 printf("\n Power factor= %.4f lagging", Power_factor
    )

```

Scilab code Exa 2.21 Calculate the different parameters of single phase full converter

```

1 //2.21
2 clc;
3 Vm=230*2^0.5;
4 Vdc=2*Vm/%pi*cosd(60);
5 printf("dc value of voltage = %.2f V", Vdc)
6 Vrms=230;
7 printf("\n RMS value of voltage= %.2f V", Vrms)
8 Is1=2*2^0.5/%pi;
9 Is=1;
10 HF=((Is/Is1)^2-1)^0.5;
11 printf("\n Harmonic factor= %.3f ", HF)
12 Displacement_factor=cos(-%pi/3);
13 printf("\n Displacement factor= %.1f ",
    Displacement_factor)
14 Power_factor=Is1/Is*cos(-%pi/3);
15 printf("\n Power factor= %.2f lagging", Power_factor
    )

```

Scilab code Exa 2.22 Calculate the different parameters of single phase full controlled bridge converter

```

1 //2.22
2 clc;
3 Vm=230*2^0.5;

```

```

4 Vdc=2*Vm/%pi*cosd(30);
5 R=Vdc/4;
6 printf("dc value of voltage = %.1f V", Vdc)
7 IL=4;
8 I=2*2^0.5/%pi*IL;
9 P_input_active=230*I*cosd(30);
10 printf("\n Active input power= %.2f W",
        P_input_active)
11 P_input_reactive=230*I*sind(30);
12 printf("\n reactive input power= %.2f Vars",
        P_input_reactive)
13 P_input_apparent=230*I;
14 printf("\n Active input power= %.2f VA",
        P_input_apparent)
15
16 disp('When freewheeling diode is present')
17 Vm=230*2^0.5;
18 Vdc=Vm/%pi*(1+cosd(30));
19 printf("dc value of voltage = %.1f V", Vdc)
20 IL=Vdc/R;
21 I=2*2^0.5/%pi*IL*cosd(15);
22 P_input_active=230*I*cosd(15);
23 printf("\n Active input power= %.2f W",
        P_input_active)
24 P_input_reactive=230*I*sind(15);
25 printf("\n reactive input power= %.2f Vars",
        P_input_reactive)
26 P_input_apparent=230*I;
27 printf("\n Active input power= %.2f VA",
        P_input_apparent)
28 disp('When Th3 get open circuit')
29 Vdc=230/(2^0.5*%pi)*(1+cosd(30));
30 printf("dc value of voltage = %.3f V", Vdc)
31 Idc=Vdc/R;
32 printf("\nAverage dc output current = %.2f A", Idc)

```

Scilab code Exa 2.23 Calculate the different parameters of single phase full controlled bridge converter

```
1 //2.23
2 clc;
3 Vm=230*2^0.5;
4 Vdc=2*Vm/%pi*cosd(30);
5 printf("dc value of voltage = %.1f V", Vdc)
6 Irms=10;
7 I=10;
8 printf("\n RMS value of current= %.0f A", Irms)
9 Is1=2*2^0.5/%pi*I;
10 printf("\n Fundamental component of input current= %
    .0f A", Is1)
11 Is=10;
12 HF=((Is/Is1)^2-1)^0.5;
13 printf("\n Harmonic factor= %.3f ", HF)
14 Displacement_factor=cosd(-30);
15 printf("\n Displacement factor= %.3f ",
    Displacement_factor)
16 Power_factor=Is1/Is*cos(-%pi/6);
17 printf("\n Power factor= %.3f lagging", Power_factor
    )
18 Out_rms=230;
19 Form_factor=Out_rms/Vdc;
20 Ripple_factor=(Form_factor^2-1)^0.5;
21 printf("\n Ripple factor= %.3f ", Ripple_factor)
```

Scilab code Exa 2.24 Calculate peak circulating current and peak current of converter

```
1 //2.24
```

```

2  clc;
3  Vm=230*2^0.5;
4  alph1=60;
5  alph2=120;
6  w=100*%pi;
7  L=50*10^-3;
8  wt=2*%pi;
9  R=15;
10 Ip_circulating=2*Vm/(w*L)*(cos(wt)-cosd(alph1));
11 printf("\n Peak circulating current= %.1f A",
        Ip_circulating)
12 Ip_load=Vm/R;
13 Ip_converter1=Ip_circulating+Ip_load;
14 printf("\n Peak current of converter 1= %.2f A",
        Ip_converter1)

```

Scilab code Exa 2.25 Calculate inductance of current limiting reactor and peak current of converter

```

1  //2.25
2  clc;
3  Vm=230*2^0.5;
4  alph1=30;
5  alph2=150;
6  w=100*%pi;
7  wt=2*%pi;
8  R=10;
9  Ip_circulating=10.2;
10 L=2*Vm/(w*Ip_circulating)*(cos(wt)-cosd(alph1));
11 printf("\n Inductance of current limiting Reactor= %
        .4f H",L)
12 Ip_load=Vm/R;
13 Ip_converter1=Ip_circulating+Ip_load;
14 printf("\n Peak current of converter 1= %.2f A",
        Ip_converter1)

```

Scilab code Exa 2.26 Calculate inductance of current limiting reactor and resistance

```
1 //2.26
2 clc;
3 Vm=230*2^0.5;
4 alph1=45;
5 alph2=135;
6 w=100*%pi;
7 wt=2*%pi;
8 R=10;
9 Ip_circulating=11.5;
10 L=2*Vm/(w*Ip_circulating)*(cos(wt)-cosd(alph1));
11 printf("\n Inductance of current limiting Reactor= %
    .4 f H",L)
12 Ip_converter1=39.7;
13 Ip_load= Ip_converter1-Ip_circulating ;
14 R=Vm/Ip_load;
15 printf("\n Load resistance= %.3 f ohm", R)
```

Scilab code Exa 2.27 Find the parameters of three phase bridge rectifier circuit

```
1 //2.27
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 Vdc=360;
5 alph=acosd(Vdc*%pi/(3*3^0.5*Vm));
6 printf("Firing Angle = %.1 f degree", alph)
7 VL=400;
8 IL=200;
```

```

9 S=3^0.5*VL*IL;
10 printf("\nApparent Power = %.0f VA",S)
11 P=S*cosd(alph);
12 printf("\nActive Power = %.1f W",P)
13 Q=(S^2-P^2)^0.5;
14 printf("\nReactive Power = %.1f VA",Q)
15 disp('When AC line voltage is 440V')
16 V=440;
17 alph=acosd(Vdc*%pi/(3*2^0.5*V));
18 printf("Firing Angle = %.1f degree", alph)
19 disp('When AC line voltage is 360V')
20 V=360;
21 alph=acosd(Vdc*%pi/(3*2^0.5*V));
22 printf("Firing Angle = %.1f degree", alph)

```

Scilab code Exa 2.28 Find the parameters of three phase full converter

```

1 //2,28
2 clc;
3 Vm=2^0.5*400/3^0.5;
4 Vdc=3*3^0.5*Vm/%pi*cos(%pi/3);
5 Idc=150;
6 Pdc=Vdc*Idc;
7 printf("Output Power = %.1f W", Pdc)
8 Iavg_thy=Idc/3;
9 printf("\nAverage thyristor current = %.0f A",
    Iavg_thy)
10 Irms_thy=Idc*(2/6)^0.5;
11 printf("\nRMS value of thyristor current = %.1f A",
    Irms_thy)
12 Ip_thy=Idc;
13 printf("\nPeak current through thyristor = %.0f A",
    Ip_thy)
14 PIV=2^0.5*400;
15 printf("\nPeak inverse voltage = %.1f V", PIV)

```

Scilab code Exa 2.29 Find the firing angle of a 3 phase fully controlled bridge converter

```
1 //2.29
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 Vrms=(400*100)^0.5;
5 alph=acosd(((Vrms/(Vm*3^0.5))^2-0.5)/(3*3^0.5/(4*%pi
   ))) /2;
6 printf("Firing angle = %.2f degree", alph)
```

Scilab code Exa 2.30 Find the parameters of six pulse thyristor converter

```
1 //2.30
2 clc;
3 Vm=415*2^0.5/3^0.5;
4 Vdc=460;
5 Idc=200;
6 alph=acosd(Vdc*%pi/(3*3^0.5*Vm));
7 printf("Firing Angle = %.2f degree", alph)
8 Pdc=Vdc*Idc;
9 printf("\ndc Power = %.2f W", Pdc)
10 Iac=Idc*(120/180)^0.5;
11 printf("\nAC line current = %.2f A", Iac)
12 Ip=Idc;
13 Irms_thy=Ip*(120/360)^0.5;
14 printf(" \nRMS thyristor current = %.1f A", Irms_thy
   )
```

Scilab code Exa 2.31 Find the parameters of three phase semi converter bridge circuit

```

1 //2.31
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 alph=0;
5 Vdc_max=3*3^0.5*Vm/(2*%pi)*(1+cosd(alph));
6 Vdc=0.5*Vdc_max;
7 alph=acosd((Vdc/(3*3^0.5*Vm/(2*%pi)))-1)
8 printf("Firing Angle = %.2f degree", alph)
9 R=10;
10 Idc=Vdc/R;
11 disp('For discontinuous load')
12 Vrms=(3^0.5*Vm)*((3/(4*%pi))*(%pi-(%pi/2)+0.5*sin(
    %pi)))^0.5;
13 printf("\nRMS value of voltage = %.2f V", Vrms)
14 Irms=Vrms/R;
15 printf("\nRMS value of current = %.2f A", Irms)
16 I_avg=Idc/3;
17 printf("\nAverage value of thyristor current = %.2f
    A", I_avg)
18 I_rms=Irms/3^0.5;
19 printf("\nRMS value of thyristor current = %.2f A",
    I_rms)
20 efficiency=Vdc*Idc/(Vrms*Irms);
21 printf("\nRectification efficiency = %.3f A",
    efficiency)
22 Irms_line_current=Irms*(120/180)^0.5;
23 VA_input=3*400/3^0.5*Irms_line_current;
24 TUF=Vdc*Idc/VA_input;
25 printf("\nTransformer utilization factor = %.2f ",
    TUF)
26 output_power_active=Irms^2*R;
27 input_power_active=output_power_active;
28 pf_input=input_power_active/VA_input;
29 printf("\ninput power factor = %.2f lagging",
    pf_input)

```

Scilab code Exa 2.32 Find the parameters of three phase fully controlled bridge converter

```
1 //2.31
2 clc;
3 Vm=400*2^0.5/3^0.5;
4 alph=0;
5 Vdc_max=3*3^0.5*Vm/(%pi)*cosd(alph);
6 Vdc=0.5*Vdc_max;
7 alph=acosd(0.5);
8 printf("Firing Angle = %.2f degree", alph)
9 R=10;
10 Idc=Vdc/R;
11 disp('For discontinuous load')
12 Vrms=(3^0.5*Vm)*(3*3^0.5/(4*%pi)*cosd(2*alph)+0.5)
    ^0.5;
13 printf("\nRMS value of voltage = %.2f V", Vrms)
14 Irms=Vrms/R;
15 printf("\nRMS value of current = %.2f A", Irms)
16 I_avg=Idc/3;
17 printf("\nAverage value of thyristor current = %.2f
    A", I_avg)
18 I_rms=Irms/3^0.5;
19 printf("\nRMS value of thyristor current = %.2f A",
    I_rms)
20 efficiency=Vdc*Idc/(Vrms*Irms);
21 printf("\nRectification efficiency = %.3f A",
    efficiency)
22 Irms_line_current=Irms*(120/180)^0.5;
23 VA_input=3*400/3^0.5*Irms_line_current;
24 TUF=Vdc*Idc/VA_input;
25 printf("\nTransformer utilization factor = %.2f ",
    TUF)
26 output_power_active=Irms^2*R;
```

```

27 input_power_active=output_power_active;
28 pf_input=input_power_active/VA_input;
29 printf("\ninput power factor = %.2f lagging",
        pf_input)

```

Scilab code Exa 2.33 Calculate the overlap angles

```

1 //2.33
2 clc;
3 Vm=326.56;
4 f=50;
5 Ls=0.2*10^-3;
6 Io=200;
7 w=2*%pi*f;
8 a=3*w*Ls*Io/%pi;
9 b=3*3^0.5*Vm/%pi;
10 disp('For firing angle 20 degree')
11 alph=20;
12 Angle_overlap= acosd((b*cosd(alph)-a)/b)-alph;
13 printf("Overlap angle= %.1f degree", Angle_overlap)
14 disp('For firing angle 30 degree')
15 alph=30;
16 Angle_overlap= acosd((b*cosd(alph)-a)/b)-alph;
17 printf("Overlap angle= %.2f degree", Angle_overlap)
18 disp('For firing angle 60 degree')
19 alph=60;
20 Angle_overlap= acosd((b*cosd(alph)-a)/b)-alph;
21 printf("Overlap angle= %.4f degree", Angle_overlap)

```

Scilab code Exa 2.34 Find the value of circulating currents for 3 phase dual converter

```

1 //2.34

```



```

2  clc;
3  Vm=400*2^0.5/3^0.5;
4  f=50;
5  w=2*%pi*f;
6  L=60*10^-3;
7  alph=0;
8  disp('Circulating current at wt=0')
9  wt=0;
10 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
11 printf("Circulating current at wt 0 is= %.3f A", ir)
12 disp('Circulating current at wt=30')
13 wt=30;
14 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
15 printf("Circulating current at wt 30 is= %.3f A", ir
    )
16 disp('Circulating current at wt=90')
17 wt=90;
18 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
19 printf("Circulating current at wt 90 is= %.3f A", ir
    )
20 disp('Maximum Circulating current will occur at wt
    =120')
21 wt=120;
22 ir=3*Vm/(w*L)*(sind(wt-30)-sind(alph))
23 printf("Maximum Circulating current is= %.3f A", ir)

```

Scilab code Exa 2.35 Find the value of inductance

```

1  //2.35
2  clc;
3  Vm=400*2^0.5/3^0.5;
4  f=50;
5  w=2*%pi*f;
6  ir=42;
7  L=3*Vm/(w*ir)*(sind(120-30)-sind(0))

```

```
8 printf("Inductance= %.3f H", L)
```

Chapter 3

Inverters

Scilab code Exa 3.1 Find the maximum output frequency

```
1 //3.1
2 clc;
3 R=80;
4 L=8*10^-3;
5 C=1.2*10^-6;
6 a=R^2;
7 b=4*L/C;
8 printf("R^2 = %.0f ", a)
9 printf("4*L/C = %.0f ", b)
10 disp('since R^2<4L/C it will work as series inverter
      ')
11 fmax=(1/(L*C)-(R^2/(4*L^2)))^0.5;
12 printf("Maximum frequency = %.2f rad/sec", fmax)
```

Scilab code Exa 3.2 Find the frequency of output

```
1 //3.2
2 clc;
```

```

3 f=1416.16;
4 T=1/f;
5 Toff=14*10^-6;
6 fo=1/(T+2*Toff);
7 printf("output frequency = %.1f Hz", fo)

```

Scilab code Exa 3.3 Find the available circuit turn off time and maximum possible frequency

```

1 //3.3
2 clc;
3 R=4;
4 L=50*10^-6;
5 C=6*10^-6;
6 a=R^2;
7 b=4*L/C;
8 wr=(1/(L*C)-(R^2/(4*L^2)))^0.5;
9 fr=wr/(2*%pi);
10 Tr=1/fr;
11 fo=6000;
12 wo=2*%pi*fo;
13 toff=%pi*(1/wo-1/wr);
14 printf("Avialable circuit turn off time = %.8f sec",
        toff)
15 fmax=1/(2*(%pi/wr+6*10^-6));
16 printf("\nMaximum frequency = %.1f Hz", fmax)

```

Scilab code Exa 3.4 Design a parallel inverter

```

1 //3.4
2 clc;
3 tq=50*10^-6;
4 Vin=40;

```

```

5 Vo=230;
6 IL=2;
7 IL_ref=2*Vo/Vin;
8 // C/L=(IL_ref/Vin)^2;           (i)
9 // Assume that circuit is reverse biased for one-
  fourth period of resonant circuit. thus
10 //%pi/3*(L*C)^0.5=50*10^-6;     (ii)
11 // on solving (i) and (ii)
12 C=13.73*10^-6;
13 L=C/(IL_ref/Vin)^2*10^6;
14 C=13.73*10^-6*10^6;
15 printf("C=%0.3 f uF" ,C)
16 printf("\nL=%0.2 f uH" ,L)

```

Scilab code Exa 3.5 Calculate the various parameters of single phase half bridge inverter

```

1 //3.5
2 clc;
3 V=30;
4 Vrms1=2*V/(2^0.5*pi);
5 printf("RMS value of fundamental component of input
  voltage = %0.1 f V" , Vrms1)
6 VL=V/2;
7 R=3;
8 Pout=VL^2/R;
9 printf("\nOutput Power = %0.0 f W" , Pout)
10 Ip_thy=VL/R;
11 printf("\nPeak current in each thyristor = %0.0 f A" ,
  Ip_thy)
12 Iavg=Ip_thy/2;
13 printf("\naverage current in each thyristor = %0.1 f A
  " , Iavg)
14 PIV=2*VL;
15 printf("\nPeak reverse blocking voltahe = %0.0 f V" ,

```

PIV)

Scilab code Exa 3.6 Calculate the various parameters of single phase full bridge inverter

```
1 //3.6
2 clc;
3 V=30;
4 Vrms1=4*V/(2^0.5*pi);
5 printf("RMS value of fundamental component of input
   voltage = %.1f V", Vrms1)
6 VL=V;
7 R=3;
8 Pout=VL^2/R;
9 printf("\nOutput Power = %.0f W", Pout)
10 Ip_thy=VL/R;
11 printf("\nPeak current in each thyristor = %.0f A",
   Ip_thy)
12 Iavg=Ip_thy/2;
13 printf("\naverage current in each thyristor = %.1f A
   ", Iavg)
14 PIV=VL;
15 printf("\nPeak reverse blocking voltage = %.0f V",
   PIV)
```

Scilab code Exa 3.7 Calculate the various parameters of full bridge inverter

```
1 //3.7
2 clc;
3 R=10;
4 V=200;
5 IL_rms_funda=9.28/2^0.5;
```

```

6 printf("RMS value of fundamental component of load
  current=%0.2 f A", IL_rms_funda)
7 IL_peak=(9.28^2+6.55^2+1.89^2+0.895^2+0.525^2);
8 printf("\nPeak value of load current=%0.2 f A",
  IL_peak)
9 Irms_harmonic=(11.56^2-9.28^2)^0.5/2^0.5;
10 printf("\nRMS harmonic current=%0.3 f A",Irms_harmonic
  )
11 TMH=(11.56^2-9.28^2)^0.5/9.28;
12 printf("\nTotal harmonic distortion=%0.3 f",TMH)
13 IL_rms=11.56/2^0.5;
14 Po=IL_rms^2*R;
15 printf("\nTotal output power=%0.1 f W",Po)
16 Po_funda=IL_rms_funda^2*R;
17 printf("\nFundamental Component of power=%0.3 f W",
  Po_funda)
18 Iavg=Po/V;
19 printf("\nAverage input current=%0.4 f A",Iavg)
20 Ip_thy=11.56;
21 printf("\nPeak thyristor current=%0.2 f A", Ip_thy)

```

Scilab code Exa 3.8 Calculate the value of C for proper load commutation

```

1 //3.8
2 clc;
3 toff=12*1.5*10^-6;
4 f=4000;
5 wt=2*pi*f*toff;
6 Xl=10;
7 R=2;
8 Xc=R*tan(wt)+Xl;
9 C=1/(2*pi*f*Xc)*10^6;
10 printf("Value of C for proper load commutation = %0.2
  f uF", C)

```

Scilab code Exa 3.9 Calculate peak value of load current

```
1 //3.9
2 clc;
3 I1=6.84;
4 I3=0.881;
5 I5=0.32;
6 I7=0.165;
7 Ip=(I1^2+I3^2+I5^2+I7^2)^0.5;
8 printf("Peak value of load current=%.2f A", Ip)
```

Scilab code Exa 3.10 Find the different parameters of 3 phase bridge inverter for 120degree conduction mode

```
1 //3.10
2 clc;
3 Ip_load=400/(2*10);
4 Irms_load=(Ip_load^2*2/3)^0.5;
5 printf("RMS value of the load current = %.2f A",
        Irms_load)
6 Po=Irms_load^2*10*3;
7 printf("\nOutput power = %.2f W", Po)
8 Iavg_thy=Ip_load/3;
9 printf("\nAverage thyristor current = %.2f A",
        Iavg_thy)
10 Irms_thy=(Ip_load^2/3)^0.5;
11 printf("\nRMS value thyristor current = %.2f A",
        Irms_thy)
```

Scilab code Exa 3.11 Find the different parameters of 3 phase bridge inverter for 180degree conduction mode

```
1 //3.11
2 clc;
3 R=10;
4 RL=R+R/2;
5 i1=400/15;
6 i2=i1;
7 i3=i1;
8 Irms_load=(1/(2*pi)*(i1^2*2*pi/3+(i1/2)^2*4*pi/3)
9 )^0.5;
10 printf("RMS value of the load current = %.3 f A",
11 Irms_load)
12 Po=i1^2*R*3;
13 printf("\nOutput power = %.2 f W", Po)
14 Iavg_thy=1/(2*pi)*(i1*pi/3+(i1/2*2*pi/3));
15 printf("\nAverage thyristor current = %.2 f A",
16 Iavg_thy)
17 Irms_thy= (1/(2*pi)*(i1^2*pi/3+(i1/2)^2*2*pi/3))
18 ^0.5;
19 printf("\nRMS value thyristor current = %.2 f A",
20 Irms_thy)
```

Scilab code Exa 3.12 Find the RMS value of load current and thyristor current of 3 phase bridge inverter for 180degree conduction mode

```
1 //3.12
2 clc;
3 R=10;
4 RL=R+R/2;
5 i1=450/15;
6 Irms_load=(1/(2*pi)*(i1^2*2*pi/3+(i1/2)^2*4*pi/3)
7 )^0.5;
8 printf("RMS value of the load current = %.2 f A",
```

```

    Irms_load)
8 Irms_thy= (1/(2*pi)*(i1^2*pi/3+(i1/2)^2*pi/3))
    ^0.5;
9 printf("\nRMS value thyristor current = %.0f A",
    Irms_thy)

```

Scilab code Exa 3.13 Find the parameters of single phase full bridge inverter

```

1 //3.13
2 clc;
3 Vdc=200;
4 VL=Vdc*(5*30/180)^0.5;
5 printf("RMS value of the output voltage = %.2f V",
    VL)
6 Vdc=220;
7 delta=(VL/Vdc)^2*180/5;
8 printf("\nPulse width = %.2f degree", delta)
9 V=VL/((5*33/180)^0.5);
10 printf("\nMaximum possible input voltage = %.2f V",
    V)

```

Scilab code Exa 3.14 Calculate the RMS value of the output voltage

```

1 //3.14
2 clc;
3 Vdc=200;
4 delta=120;
5 VL=Vdc*(delta/180)^0.5;
6 printf("RMS value of the output voltage = %.1f V",
    VL)

```

Scilab code Exa 3.15 Calculate the RMS value of the output voltage

```
1 //3.15
2 clc;
3 Vdc=150;
4 VL=Vdc*(20/180+60/180+20/180)^0.5;
5 printf("RMS value of the output voltage = %.2f V",
        VL)
```

Chapter 4

Choppers

Scilab code Exa 4.1 Calculate the period of conduction and blocking

```
1 // 4.1
2 clc;
3 f=1000;
4 T=1/f;
5 Vav=150;
6 V=230;
7 Ton=(Vav/V)*T;
8 printf("Period of conduction = %.6f sec", Ton)
9 Toff=T-Ton;
10 printf("\nPeriod of blocking = %.6f sec", Toff)
```

Scilab code Exa 4.2 Calculate the period of conduction and blocking

```
1 // 4.2
2 clc;
3 f=500;
4 T=1/f;
5 Vav=15*(0.06+0.03)+100;
```

```

6 V=200;
7 Ton=(Vav/V)*T;
8 printf("Period of conduction = %.7f sec", Ton)
9 Toff=T-Ton;
10 printf("\nPeriod of blocking = %.7f sec", Toff)

```

Scilab code Exa 4.3 Calculate the duty cycle for the rated torque and half of rated torque

```

1 //4.3
2 clc;
3 Vs=240;
4 emf_800=Vs-20*0.5;
5 emf_600=230*600/800;
6 Vav=emf_600+20*0.5;
7 Duty_cycle=Vav/Vs;
8 printf("Duty cycle when motor develop the rated
    torque = %.4f ", Duty_cycle)
9 //when motor develop half of the rated torque
10 Vav=emf_600+10*0.5;
11 Duty_cycle=Vav/Vs;
12 printf("\nDuty cycle when motor develop half of the
    rated torque = %.4f ", Duty_cycle)

```

Scilab code Exa 4.4 Find the different parameters of a dc chopper

```

1 //4.4
2 clc;
3 Duty_cycle=0.4;
4 Vs=200;
5 Vd=2;
6 Vav=Duty_cycle*(Vs-Vd);
7 printf("Average output voltage = %.1f V", Vav)

```

```

8 VL=Duty_cycle^0.5*(Vs-Vd);
9 printf("\nRMS output voltage = %.3f V", VL)
10 R=8;
11 Po=VL^2/R;
12 Pi=Duty_cycle*Vs*(Vs-Vd)/R;
13 Chopper_efficiency=Po/Pi*100;
14 printf("\nChopper efficiency = %.0f percent",
        Chopper_efficiency)
15 Rin=R/Duty_cycle;
16 printf("\nInput resistance = %.0f Ohm", Rin)
17 V1=126.05/2^0.5;
18 printf("\nRMS value of fundamental component = %.3f
        V", V1)

```

Scilab code Exa 4.5 Find the chopper frequency

```

1 //4.5
2 clc;
3 Duty_cycle=0.25;
4 V=400;
5 Vav=Duty_cycle*V;
6 Vn=V-Vav;
7 L=0.05;
8 di=10;
9 Ton=L*di/Vn;
10 T=Ton/Duty_cycle;
11 f=1/T;
12 printf("\nChopper frequency = %.0f Hz", f)

```

Scilab code Exa 4.6 Find the different parameters of a chopper feeding a RL load

```

1 //4.6

```

```

2  clc;
3  V=200;
4  R=4;
5  L=6*10^-3;
6  f=1000;
7  T=1/f;
8  Duty_cycle=0.5;
9  E=0;
10 Imax=V/R*((1-exp(-Duty_cycle*T*R/L))/(1-exp(-T*R/L))
    )-E/R;
11 printf("\nImax = %.2f A", Imax)
12 Imin=V/R*((exp(Duty_cycle*T*R/L)-1)/(exp(T*R/L)-1))-
    E/R;
13 printf("\nImin = %.2f A", Imin)
14 Maximum_ripple=V/(R*f*L);
15 printf("\nMaximum ripple = %.2f A", Maximum_ripple)
16 IL_avg=(Imax+Imin)/2;
17 printf("\nAverage Load current = %.0f A", IL_avg)
18 iL=(Imin^2+(Imax-Imin)^2/3+Imin*(Imax-Imin))^0.5;
19 printf("\nRMS value of Load current = %.2f A", iL)
20 Iavg=0.5*IL_avg;
21 printf("\nAverage value of input current = %.2f A",
    Iavg)
22 Irms=Duty_cycle^0.5*iL;
23 printf("\nRMS value of input current = %.3f A", Irms
    )

```

Scilab code Exa 4.7 Calculate the load inductance

```

1  // 4.7
2  clc;
3  V=300;
4  E=0;
5  R=5;
6  f=250;

```

```
7 Id=0.2*30;
8 L=V/(4*f*Id);
9 printf("Load inductance = %.3f H", L)
```

Scilab code Exa 4.8 Calculate the current

```
1 //4.8
2 clc;
3 V=200;
4 E=100;
5 R=0.5;
6 t=2*10^-3;
7 L=16*10^-3;
8 Imin=10;
9 i=(V-E)/R*(1-exp(-R*t/L))+Imin*exp(-R*t/L);
10 printf("Current at the instant of turn off thyristor
    = %.2f A", i)
11 t=5*10^-3;
12 i_5=i*exp(-R*t/L);
13 printf("\nCurrent after 5ms of turn off thyristor =
    %.2f A", i_5)
```

Scilab code Exa 4.9 Find the speed of motor

```
1 //4.9
2 clc;
3 emf=220;
4 duty_cycle=0.6;
5 Vi=220*duty_cycle;
6 Ra=1;
7 I=20;
8 emf_back=Vi-I*Ra;
9 N_no_load=1000;
```



```

10 N=emf_back*N_no_load/emf;
11 printf("\nSpeed of motor = %.1f rpm", N)

```

Scilab code Exa 4.10 Calculate average load voltage

```

1 //4.10
2 clc;
3 Ton=25*10^-3;
4 Toff=10*10^-3;
5 V=230;
6 VL=V*Ton/(Ton+Toff);
7 printf("\nAverage value of Load voltage = %.3f V",
      VL)

```

Scilab code Exa 4.11 Find maximum minimum and average load current and load voltage

```

1 //4.11
2 clc;
3 V=100;
4 R=0.5;
5 L=1*10^-3;
6 T=3*10^-3;
7 Duty_cycle=0.3333;
8 E=0;
9 Imax=V/R*((1-exp(-Duty_cycle*T*R/L))/(1-exp(-T*R/L))
      )-E/R;
10 printf("\nImax = %.2f A", Imax)
11 Imin=V/R*((exp(Duty_cycle*T*R/L)-1)/(exp(T*R/L)-1))-
      E/R;
12 printf("\nImin = %.1f A", Imin)
13 IL_avg=(Imax+Imin)/2;
14 printf("\nAverage Load current = %.1f A", IL_avg)

```

```
15 Vavg=Duty_cycle*V;
16 printf("\nAverage Load Voltage = %.2f V", Vavg)
```

Scilab code Exa 4.12 Find maximum minimum and average output voltage

```
1 //4.12
2 clc;
3 V=100;
4 R=0.2;
5 L=0.8*10^-3;
6 T=2.4*10^-3;
7 Duty_cycle=1/2.4;
8 E=0;
9 Imax=V/R*((1-exp(-Duty_cycle*T*R/L))/(1-exp(-T*R/L))
   )-E/R;
10 printf("\nImax = %.2f A", Imax)
11 Imin=V/R*((exp(Duty_cycle*T*R/L)-1)/(exp(T*R/L)-1))-
   E/R;
12 printf("\nImin = %.2f A", Imin)
13 Vavg=Duty_cycle*V;
14 printf("\nAverage output Voltage = %.2f V", Vavg)
```

Scilab code Exa 4.13 Calculate the series inductance in the circuit

```
1 //4.13
2 clc;
3 V=500;
4 f=400;
5 I=10;
6 L=V/(4*f*I);
7 printf("Series inductance = %.5f H", L)
```

Scilab code Exa 4.14 Calculate the motor speed and current swing

```
1 //4.14
2 clc;
3 Motor_output=300*735.5/1000;
4 efficiency=0.9;
5 Motor_input=Motor_output/efficiency;
6 Vdc=800;
7 Rated_current=Motor_input*1000/800;
8 R=0.1;
9 L=100*10^-3;
10 T=1/400;
11 emf=Vdc-Rated_current*0.1;
12 Duty_cycle=0.2;
13 emf_n=Duty_cycle*Vdc-Rated_current*0.1;
14 N=900/(emf/emf_n);
15 printf("\nSpeed of motor = %.2f rpm", N)
16 dia=(Vdc-Duty_cycle*Vdc)/L*Duty_cycle*T;
17 printf("\nCurrent swing = %.1f A", dia)
```

Scilab code Exa 4.15 Calculate the value of capacitance and inductance

```
1 //4.15
2 clc;
3 Vc=200;
4 Im=60;
5 toff=15*10^-6;
6 C1=toff*Im/Vc;
7 C=5*10^-6*10^6;
8 printf("\nCapacitance = %.0f uF", C)
9 Ipc=Im*1.5-Im;
10 L=C/(Ipc/Vc)^2*10^6;
```

```
11 printf("\nInductance = %.1f uH", L)
```

Scilab code Exa 4.16 Calculate the period of conduction of a step up chopper

```
1 //4.16
2 clc;
3 Vav=250;
4 V=200;
5 Toff=0.6*10^-3;
6 Ton=(Vav/V)*Toff-Toff;
7 printf("Period of conduction = %.5f sec", Ton)
```

Scilab code Exa 4.17 Calculate the period of conduction of a step up chopper

```
1 //4.16
2 clc;
3 Vav=250;
4 V=150;
5 Toff=1*10^-3;
6 Ton=(Vav/V)*Toff-Toff;
7 printf("Period of conduction = %.6f sec", Ton)
```

Chapter 5

AC Regulators

Scilab code Exa 5.1 Calculate the different parameters of AC voltage regulator using integral cycle control

```
1 // 5.1
2 clc;
3 Vin=150;R=8;
4 duty_cycle=36/(36+64);
5 VL=Vin*duty_cycle^0.5;
6 printf("RMS output voltage=%0.0 f V", VL)
7 Po=VL^2/R;
8 printf("\nPower output =%0.1 f W", Po)
9 // since losses are neglected
10 Pi=Po;
11 printf("\nPower Input =%0.1 f W", Pi)
12 Irms_load=VL/R;
13 Irms_input=11.25;
14 VA_input=Irms_input*Vin;
15 pf_input=Po/VA_input;
16 printf(" \nInput Power factor =%0.1 f lagging",
    pf_input)
17 Ip_thy=2^0.5*Vin/R;
18 Iavg_thy=duty_cycle*Ip_thy/%pi;
19 printf("\nAverage thyristor Current =%0.3 f A",
```

```

    Iavg_thy)
20 Irms_thy=Ip_thy*duty_cycle^0.5/2;
21 printf("\nRMS thyristor Current =%.3f A", Irms_thy)

```

Scilab code Exa 5.2 Calculate the different parameters of single phase half wave AC regulator

```

1 //5.2
2 clc;
3 Vm=2^0.5*150;
4 alph=60;
5 R=8;
6 Vin=150;
7 Vavg_out=Vm*(cosd(alph)-1)/(2*%pi);
8 printf("Average output voltage =%.2f V", Vavg_out)
9 disp('The average output voltage is negative only a
    part of positive half cycle appears at the output
    whereas the whole negative half cycle appears at
    the output')
10 VL=Vm*(1/(4*%pi)*(2*%pi-60*%pi/180+sind(120)/2))
    ^0.5;
11 printf("\nRMS output voltage =%.2f V", VL)
12 Po=VL^2/R;
13 printf("\nPower output =%.1f W", Po)
14 Iin=VL/R;
15 VA_input=Iin*Vin;
16 pf_input=Po/VA_input;
17 printf(" \nInput Power factor =%.2f lagging",
    pf_input)
18 Iavg_out=Vavg_out/R;
19 Iavg_input=Iavg_out;
20 printf(" \nAverage input current =%.2f A",
    Iavg_input)
21 disp('The average input current is negative because
    input current during positive half cycle is less

```

than during negative half cycle ')

Scilab code Exa 5.3 Calculate the different parameters of single phase full wave AC regulator

```
1 //5.3
2 clc;
3 Vin=150;
4 Vm=2^0.5*Vin;
5 alph=60;
6 R=8;
7 Vavg_out=Vm*(cosd(alph)+1)/(%pi);
8 printf("Average output voltage over half cycle =%.2f
   V", Vavg_out)
9 VL=Vm*(1/(2*%pi)*(%pi-60*%pi/180+sind(120)/2))^0.5;
10 printf("\nRMS output voltage =%.2f V", VL)
11 Po=VL^2/R;
12 printf("\nPower output =%.1f W", Po)
13 Iin=VL/R;
14 VA_input=Iin*Vin;
15 pf_input=Po/VA_input;
16 printf(" \nInput Power factor =%.1f lagging",
   pf_input)
17
18 Iavg_thy=Vm*(1+cosd(alph))/(2*%pi*R);
19 printf("\nAverage thyristor Current =%.2f A",
   Iavg_thy)
20 Irms_thy=Vm/(2*R)*(1/(%pi)*(%pi-%pi/3+sind(120)/2))
   ^0.5;
21 printf("\nRMS thyristor Current =%.3f A", Irms_thy)
```

Scilab code Exa 5.4 Calculate the different parameters of single phase full wave AC regulator

```

1 //5.4
2 clc;
3 Vin=120;
4 Vm=2^0.5*Vin;
5 alph=90;
6 R=10;
7
8 VL=Vm*(1/(2*pi)*(pi-90*pi/180+sind(180)/2))^0.5;
9 printf("\nRMS output voltage =%.2f V", VL)
10 Po=VL^2/R;
11 IL=VL/R;
12 VA_input=IL*Vin;
13 pf_input=Po/VA_input;
14 printf(" \nInput Power factor =%.3f lagging",
        pf_input)
15
16 Iavg_thy=Vm*(1+cosd(alph))/(2*pi*R);
17 printf("\nAverage thyristor Current =%.2f A",
        Iavg_thy)
18 Irms_thy=IL/2^0.5;
19 printf("\nRMS thyristor Current =%.3f A", Irms_thy)
20 Irms_load=VL/R;
21 printf("\nRMS Load Current =%.3f A", Irms_load)

```

Scilab code Exa 5.5 Find RMS output voltage and average power

```

1 //5.5
2 clc;
3 Vin=110;
4 Vm=2^0.5*Vin;
5 alph=60;
6 R=400;
7 VL=Vm*(1/(2*pi)*(pi-60*pi/180+sind(120)/2))^0.5;
8 printf("\nRMS output voltage =%.2f V", VL)
9 Po=VL^2/R;

```



```
10 printf("\nPower output =%.2f W", Po)
```

Scilab code Exa 5.6 Find the firing angle

```
1 // 5.6
2 clc;
3 disp('When the power delivered is 80% we have')
4 //0.8=1/(%pi)*(%pi-alph+sin(2*alph)/2)
5 //on solving
6 alph=60.5;
7 printf("Firing angle=%.1f degree",alph)
8 disp('When the power delivered is 30% we have')
9 //0.3=1/(%pi)*(%pi-alph+sin(2*alph)/2)
10 //on solving
11 alph=108.6;
12 printf("Firing angle=%.1f degree",alph)
```

Scilab code Exa 5.7 Find the conduction angle and RMS output voltage

```
1 // 5.7
2 clc;
3 f=50;
4 Vin=150;
5 w=2*%pi*f;
6 L=22*10^-3;R=4;
7 th=atand(w*L/R);
8 Beta=180+th;
9 printf("Conduction angle of thyristor=%.0f degree",
    Beta)
10 Vm=2^0.5*Vin;
11 VL=Vm*(1/(2*%pi)*(%pi++sind(120)/2-sind(2*240)/2))
    ^0.5;
12 printf("\nRMS output Voltage=%.0f V", VL)
```

Scilab code Exa 5.8 Calculate the different parameters of single phase full wave AC regulator

```
1 //5.8
2 clc;
3 f=50;
4 Vin=230;
5 w=2*%pi*f;
6 L=20*10^-3;R=5;
7 th=atand(R/(w*L));
8 printf(" Firing angle=%0.2 f degree",th)
9 disp('Therefore, Range of firing angle is 38.51
      degree to 180 degree')
10 Beta=180;
11 printf(" Conduction angle of thyristor=%0.0 f degree",
      Beta)
12 IL=Vin/((R^2+w^2*L^2))^0.5;
13 printf(" \nRMS load current =%0.2 f A", IL)
14 Po=IL^2*R;
15 printf(" \nPower Output =%0.2 f W", Po)
16 pf_input=Po/(Vin*IL);
17 printf(" \nInput Power factor =%0.3 f lagging",
      pf_input)
```

Scilab code Exa 5.10 Find the current and voltage rating

```
1 //5.10
2 clc;
3 V=415;
4 P=20*10^3;
5 disp('For Triacs')
```

```

6 I_line=P/(3^0.5*V);
7 Irms=I_line*1.5;
8 printf("RMS current rating of each triac=%0.2f A",
    Irms)
9 Vrms=1.5*V;
10 printf("\nRMS Voltage rating of each triac=%0.2f V",
    Vrms)
11 disp('For reverse connected thyristors')
12 Irms_thy=1.5*I_line/2^0.5;
13 printf("RMS current rating of each thyristor=%0.2f A"
    , Irms_thy)
14 Vrms_thy=1.5*V;
15 printf("\nRMS voltage rating of each thyristor=%0.2f
    V", Vrms_thy)

```

Scilab code Exa 5.11 Calculate the different parameters of 3 phase star connected resistance load with firing angle 30 degree

```

1 //5.11
2 clc;
3 R=15;
4 Vrms_input_phase=415/3^0.5;
5 VL=3^0.5*2^0.5*Vrms_input_phase*(1/(%pi)*(%pi/6-30*
    %pi/(180*4)+sind(60)/8))^0.5;
6 printf("\nRMS value of output voltage per phase=%0.2f
    V", VL)
7 Po=3*VL^2/R;
8 printf("\nPower output =%0.1f W", Po)
9 I_line=VL/R;
10 printf("\nLine Current =%0.2f A", I_line)
11 VA_input=3*Vrms_input_phase*I_line;
12 pf_input=Po/VA_input;
13 printf("\nInput Power Factor =%0.3f lagging",
    pf_input)

```

Scilab code Exa 5.12 Calculate the different parameters of 3 phase star connected resistance load with firing angle 60 degree

```
1 //5.12
2 clc;
3 R=15;
4 Vrms_input_phase=415/3^0.5;
5 VL=3^0.5*2^0.5*Vrms_input_phase*(1/(%pi)*(%pi/6-60*
    %pi/(180*4)+sind(120)/8))^0.5;
6 printf("\nRMS value of output voltage per phase=%0.2 f
    V", VL)
7 Po=3*VL^2/R;
8 printf("\nPower output =%0.1 f W", Po)
9 I_line=VL/R;
10 printf("\nLine Current =%0.2 f A", I_line)
11 VA_input=3*Vrms_input_phase*I_line;
12 pf_input=Po/VA_input;
13 printf("\nInput Power Factor =%0.3 f lagging",
    pf_input)
```

Chapter 6

Cycloconverters

Scilab code Exa 6.1 Find the input voltage SCR rating and Input Power Factor

```
1 // 6.1
2 clc;
3 Vo_max=250;
4 Vm=Vo_max*%pi*2^0.5/(3*sin(%pi/3));
5 Vrms=Vm/2^0.5;
6 printf("RMS value of input voltage =%.1f V", Vrms)
7 I=50;
8 Irms=I*2^0.5/3^0.5;
9 PIV=3^0.5*Vm;
10 Irms_input=(I^2/3)^0.5;
11 Po=Vo_max*I*0.8;
12 Pi_per_phase=1/3*Po;
13 pf_input=Pi_per_phase/(Irms_input*Vrms)
14 printf("\nInput power factor =%.3f lagging",
        pf_input)
```

Scilab code Exa 6.2 Find RMS value of output voltage for firing angle 30 and 45 degree

```

1 //6.2
2 clc;
3 Vo_max=250;
4 alph=30;
5 Vo=Vo_max*cosd(alph);
6 printf("RMS value of output voltage for firing angle
       30 degree =%.1f V", Vo)
7 alph=45;
8 Vo=Vo_max*cosd(alph);
9 printf("\nRMS value of output voltage for firing
       angle 45 degree =%.2f V", Vo)

```

Scilab code Exa 6.3 Find RMS value of output voltage for firing angle 0 and 30 degree

```

1 //6.3
2 clc;
3 Vrms=230;
4 alph=0;
5 Vo=6*2^0.5*Vrms/(%pi*2^0.5)*sin(%pi/6)*cosd(alph);
6 printf("RMS value of output voltage for firing angle
       0 degree =%.2f V", Vo)
7 alph=30;
8 Vo=6*2^0.5*Vrms/(%pi*2^0.5)*sin(%pi/6)*cosd(alph);
9 printf("\nRMS value of output voltage for firing
       angle 30 degree =%.1f V", Vo)

```

Chapter 7

Applications of Thyristors

Scilab code Exa 7.1 Find the value of Voltage which will turn On the crowbar

```
1 //7.1
2 clc;
3 Vz=14.8;
4 Vt=0.85;
5 V=Vz+Vt;
6 printf("The value of Voltage which will turn On the
   crowbar=%0.2 f V",V)
```

Scilab code Exa 7.2 Find the value of input voltage

```
1 //7.2
2 clc;
3 Rth=50*15/(50+15);
4 I=20*10^-3;
5 Vz=14.8;
6 Vt=0.85;
7 V=Rth*I; // Voltage drop across the thevenin's
   resistance
```

```
8 Vi=V+Vzb+Vt;  
9 printf("The value of input voltage Vi=%0.3f V",Vi)
```

Scilab code Exa 7.3 Find the value of R and C

```
1 //7.3  
2 clc;  
3 V=200;  
4 I=4*10^-3;  
5 R=V/I;  
6 printf("Resistance=%0.0f ohm", R)  
7 Vc=0;  
8 RL=V/10;  
9 tq=15*10^-6;  
10 C=tq/(RL *log(2))*10^6;  
11 printf("\nCapacitance=%0.3f uF", C)
```

Scilab code Exa 7.4 Find Duty cycle and Ratio for different output powers

```
1 //7.4  
2 clc;  
3 V=230;  
4 R=60;  
5 Po_max=V^2/R;  
6 disp('When power output is 400')  
7 Po=400;  
8 Duty_cycle=Po/Po_max;  
9 printf("Duty cycle=%0.4f", Duty_cycle)  
10 Ton=0.4537;  
11 T=1;  
12 Toff=1-Ton;  
13 Ratio=Ton/Toff;
```



```

14 printf("\nRatio of Ton and Toff when power output is
      400=%0.4f", Ratio)
15 disp('When power output is 700')
16 Po=700;
17 Duty_cycle=Po/Po_max;
18 printf("Duty cycle=%0.4f", Duty_cycle)
19 Ton=0.794;
20 T=1;
21 Toff=1-Ton;
22 Ratio=Ton/Toff;
23 printf("\nRatio of Ton and Toff when power output is
      700=%0.4f", Ratio)

```

Scilab code Exa 7.5 Find RMS value of output voltage

```

1 // 7.5
2 clc;
3 V=230;
4 Ton=12;
5 Toff=19;
6 Duty_cycle=Ton/(Ton+Toff);
7 printf("Duty cycle=%0.4f", Duty_cycle)
8 Vrms_output=V*Duty_cycle^0.5;
9 printf("\nRMS output voltage=%0.1f V", Vrms_output)

```

Scilab code Exa 7.6 Find the power supplied to heater for different firing angles

```

1 // 7.6
2 clc;
3 Vin=230;
4 Vm=2^0.5*Vin;
5 alph=90;

```

```

6 R=50;
7 VL=Vm*(1/(2*pi)*(pi-90*pi/180+sind(180)/2))^0.5;
8 Po=VL^2/R;
9 printf("Power supplied when firing angle is 90
    degree =%.2 f W", Po)
10 alph=120;
11 R=50;
12 VL=Vm*(1/(2*pi)*(pi-120*pi/180+sind(240)/2))^0.5;
13 Po=VL^2/R;
14 printf("\nPower supplied when firing angle is 120
    degree =%.2 f W", Po)

```

Scilab code Exa 7.7 Find the firing angles when different powers are supplied to heater

```

1 // 7.7
2 clc;
3 V=230;
4 R=10;
5 Pmax=V^2/R;
6 P=2645;
7 VL=(P*R)^2;
8 //VL=Vm*(1/(2*pi)*(pi-alph*pi/180+sind(2*alph)/2)
    )^0.5;
9 //on solving
10 alph=90;
11 printf("Firing angle when 2645 W Power is supplied =
    %.0 f degree", alph)
12 P=1587;
13 VL=(P*R)^2;
14 //VL=Vm*(1/(2*pi)*(pi-alph*pi/180+sind(2*alph)/2)
    )^0.5;
15 //on solving
16 alph=108.6;
17 printf("\nFiring angle when 2645 W Power is supplied

```

```
=%.1f degree", alph)
```

Scilab code Exa 7.8 Find the current rating and peak inverse voltage

```
1 //7.8
2 clc;
3 disp('For triac ')
4 P=20000;
5 V=400;
6 I=P/(V*3^0.5);
7 printf("Current rating of traic=%.2f A",I)
8 PIV=2^0.5*V;
9 printf("\nPIV of traic=%.2f V",PIV)
10 disp('When two thyristors are connected in
      antiparallel ')
11 I=I/2^0.5; //since each thyristor will conduct for
      half cycle
12 printf("Current rating =%.2f A",I)
13 PIV=2^0.5*V;
14 printf("\nPIV =%.2f V",PIV)
```

Scilab code Exa 7.9 Find firing angle and power factor of converter in the armature circuit

```
1 //7.9
2 clc;
3 Vm=230*2^0.5;
4 Vf=2*Vm/%pi;
5 Rf=200;
6 If=Vf/Rf;
7 T=50;
8 Kt=0.8;
9 Ia=T/(Kt*If);
```

```

10 w=2*%pi*900/60;
11 Vb=Kt*w*If;
12 Ra=0.3;
13 Va=Vb+Ia*Ra;
14 alph_a=acosd(Va*%pi/Vm-1)
15 printf("Firing angle of converter in the armature
        circuit=%0.3f degree",alph_a)
16 Po_a=Va*Ia;
17 Iin=Ia*((%pi-alph_a*%pi/180)/%pi)^0.5;
18 VA_input=Iin*230;
19 pf=Po_a/VA_input;
20 printf("\npower factor of converter in the armature
        circuit=%0.3f lagging",pf)

```

Scilab code Exa 7.10 Find the torque developed and motor speed

```

1 //7.10
2 clc;
3 Vm=230*2^0.5;
4 Vf=2*Vm/%pi;
5 alph_a=%pi/4;
6 Va=(2*Vm/%pi)*cos(alph_a);
7 Rf=200;
8 If=Vf/Rf;
9 Kt=1.1;
10 Ia=50;
11 T=Ia*(Kt*If);
12 printf("Torque of motor=%0.3f Nm", T)
13 Ra=0.25;
14 Vb=Va-Ia*Ra-2;
15 w=Vb/(Kt*If);
16 N=w*60/(2*%pi);
17 printf("\nSpeed of motor=%0.1f rpm", N)

```

Scilab code Exa 7.11 Find armature current and Firing angle of the semi converter

```
1 //7.11
2 clc;
3 Vm=675*2^0.5;
4 Ia1=30;
5 N1=350;
6 N2=500;
7 Ia2=Ia1*N2/N1;
8 printf("Armature current of the semi converter=%0.2f
   A",Ia2)
9 Va1=(1+cos(90.5*%pi/180))*Vm/%pi;
10 Eb1=Va1-Ia1*(0.22+0.22);
11 Eb2=Eb1*Ia2*N2/(Ia1*N1);
12 Va2=Eb2+Ia2*(0.22+0.22);
13 alph_a=acosd(Va2*%pi/Vm-1);
14 printf("\nFiring angle of the semi converter=%0.2f
   degree",alph_a)
```

Scilab code Exa 7.12 Find the firing angle of converter in the armature circuit and power fed back to the source

```
1 //7.12
2 clc;
3 Vm=230*2^0.5;
4 Eg=-131.9
5 Ia=50;
6 Ra=0.25;
7 Va=Eg+Ia*Ra+2;
8 alph_a=acosd(Va*%pi/(2*Vm))
```

```

9 printf("Firing angle of converter in the armature
   circuit=%0.2f degree",alph_a)
10 Po=abs(Va*Ia);
11 printf("\npower back to source=%0.3f W",Po)

```

Scilab code Exa 7.13 Find the firing angle of converter in the armature circuit

```

1 //7.13
2 clc;
3 Vm=400*2^0.5/(3^0.5);
4 Vf=3*3^0.5*Vm/%pi;
5 Rf=250;
6 If=Vf/Rf;
7 Kt=1.33;
8 Ia=50;
9 w=2*%pi*1200/60;
10 Vb=Kt*w*Ia;
11 Ra=0.3;
12 Va=Vb+Ia*Ra;
13 alph_a=acosd(Va/Vf);
14 printf("Firing angle of converter in the armature
   circuit=%0.3f degree",alph_a)

```

Scilab code Exa 7.14 Find the input power speed and torque of separately excited dc motor

```

1 //7.14
2 clc;
3 V=500;
4 Ia=200;
5 Ra=0.1;
6 Pi=V*Ia*0.5;

```

```

7 printf("Input power=%0.0 f W", Pi)
8 Va=0.5*500;
9 Eb=Va-Ia*Ra;
10 If=2;
11 Kt=1.4;
12 w=Eb/(Kt*If)
13 N=w*60/(2*%pi)
14 printf("\nSpeed=%0.2 f rpm", N)
15 T=Kt*If*Ia;
16 printf("\nTorque=%0.0 f N-m", T)

```

Scilab code Exa 7.15 Find the average voltage power dissipated and motor speed of the chopper

```

1 //7.15
2 clc;
3 Rb=7.5;
4 Ra=0.1;
5 Kt=1.4;
6 Ia=120;
7 If=1.6;
8 Duty_cycle=0.35;
9 Vavg=Rb*Ia*(1-Duty_cycle);
10 printf("Average voltage across chopper=%0.0 f V", Vavg
)
11 Pb=Rb*Ia^2*(1-Duty_cycle);
12 printf("\nPower dissipated in breaking resistance=%0
.0 f W", Pb)
13 Eb=Vavg+Ia*Ra;
14 w=Eb/(Kt*If);
15 N=w*60/(2*%pi);
16 printf("\nSpeed=%0.2 f rpm", N)

```

Scilab code Exa 7.16 Find the speed for different values of torque

```
1 //7.16
2 clc;
3 Vm=220*2^0.5;
4 alph=90;
5 Va=3*3^0.5*Vm*(1+cosd(alph))/(2*%pi);
6 Kt=2;
7 Ra=0.72;
8 disp('For armature current of 5A')
9 Ia=5;
10 T=Ia*Kt;
11 printf("\nTorque=%0.2 f N-m", T)
12 Eb=Va-Ia*Ra;
13 w=Eb/(Kt);
14 N=w*60/(2*%pi);
15 printf("\nSpeed=%0.2 f rpm", N)
16 disp('For armature current of 10A')
17 Ia=10;
18 T=Ia*Kt;
19 printf("\nTorque=%0.2 f N-m", T)
20 Eb=Va-Ia*Ra;
21 w=Eb/(Kt);
22 N=w*60/(2*%pi);
23 printf("\nSpeed=%0.2 f rpm", N)
24 disp('For armature current of 20A')
25 Ia=20;
26 T=Ia*Kt;
27 printf("\nTorque=%0.2 f N-m", T)
28 Eb=Va-Ia*Ra;
29 w=Eb/(Kt);
30 N=w*60/(2*%pi);
31 printf("\nSpeed=%0.2 f rpm", N)
32 disp('For armature current of 30A')
33 Ia=30;
34 T=Ia*Kt;
35 printf("\nTorque=%0.2 f N-m", T)
36 Eb=Va-Ia*Ra;
```



```

37 w=Eb/(Kt);
38 N=w*60/(2*%pi);
39 printf("\nSpeed=%0.2 f rpm", N)
40 disp('For armature current of 50A')
41 Ia=50;
42 T=Ia*Kt;
43 printf("\nTorque=%0.2 f N-m", T)
44 Eb=Va-Ia*Ra;
45 w=Eb/(Kt);
46 N=w*60/(2*%pi);
47 printf("\nSpeed=%0.2 f rpm", N)
48 disp('For armature current of 60A')
49 Ia=60;
50 T=Ia*Kt;
51 printf("\nTorque=%0.2 f N-m", T)
52 Eb=Va-Ia*Ra;
53 w=Eb/(Kt);
54 N=w*60/(2*%pi);
55 printf("\nSpeed=%0.2 f rpm", N)

```

Scilab code Exa 7.17 Find the speed at no load and firing angle

```

1 //7.17
2 clc;
3 Vm=400*2^0.5;
4 alph=30;
5 Vavg=3*3^0.5*Vm/(2*%pi*3^0.5)*(1+cosd(alph));
6 I=5;
7 R=0.1;
8 Eb=Vavg-I*R;
9 N=Eb/0.3;
10 printf("Speed at no load=%0.0 f rpm",N)
11 N=1600;
12 Eb=N*0.3;
13 I=50;

```

```

14 V=Eb+I*R;
15 alph=acosd(3^0.5*2*%pi*V/(Vm*3*3^0.5)-1)
16 printf("\nFiring angle =%.2f degree",alph)

```

Scilab code Exa 7.18 Find the motor speed

```

1 //7.18
2 clc;
3 Vdc=2*2^0.5*230/%pi;
4 TL=25;
5 Kt=0.25;
6 Ia=(TL/Kt)^0.5;
7 w=(Vdc-1.5*Ia)/(Kt*Ia);
8 N=w*60/(2*%pi);
9 printf("Motor speed=%.2f rpm",N)

```

Scilab code Exa 7.19 Find the load torque stator applied voltage and rotor current

```

1 //7.19;
2 clc;
3 p=4
4 f=50;
5 ns=2*f*60/p;
6 TL_1300=40*(1300/1440)^2;
7 printf("Load torque=%.2f Nm",TL_1300)
8 n=1300;
9 s=(ns-n)/ns;
10 r2s=0.08*2^2; // in book r2'=r2s
11 x2s=0.12*2^2;
12 I2s=(TL_1300*2*%pi*s*25/(3*r2s))^0.5;
13 I2=2*I2s;
14 printf("\nRotor current=%.2f A",I2)

```

```

15 r1=0.64;
16 x1=1.1;
17 V1=I2s*((r1+r2s/s)^2+(x1+x2s)^2)^0.5;
18 Vstator=3^0.5*V1;
19 printf("\nStator applied voltage=%.1f V",Vstator)

```

Scilab code Exa 7.20 Find the load torque stator applied voltage and rotor current

```

1 //7.20
2 clc;
3 r2s=0.32;
4 r1=0.64;
5 x2s=0.48;
6 x1=1.1;
7 s=r2s/(r1^2+(x1+x2s)^2)^0.5;
8 printf("\nSlip=%.4f ",s)
9 V1=400/3^0.5;
10 Tmax=1.5*V1^2/(2*pi*25)*(1/(r1+(r1^2+(x1+x2s)^2)^0.5))
11 printf("\nMaximum Torque=%.2f Nm",Tmax)
12 n=25*(1-s);
13 N=n*60;
14 printf("\nSpeed=%.2f rpm",N)
15 disp('at 25 Hz')
16 x1=0.55;
17 x2s=0.24;
18 s=r2s/(r1^2+(x1+x2s)^2)^0.5;
19 printf("\nSlip=%.4f ",s)
20 V1=0.5*400/3^0.5;
21 Tmax=1.5*V1^2/(2*pi*12.5)*(1/(r1+(r1^2+(x1+x2s)^2)^0.5))
22 printf("\nMaximum Torque=%.2f Nm",Tmax)
23 n=12.5*(1-s);
24 N=n*60;

```

```
25 printf("\nSpeed=%.3 f rpm",N)
```

Scilab code Exa 7.21 Find the starting torques at different frequencies

```
1 //7.21
2 clc;
3 r2s=0.32;
4 r1=0.64;
5 x2s=0.48;
6 x1=1.1;
7
8 V1=400/3^0.5;
9 Tstarting=3*V1^2*r2s/(2*pi*25)*(1/((r1+r2s)^2+(x1+
    x2s)^2))
10 printf("\nStarting Torque=%.2 f Nm",Tstarting)
11
12 disp('at 25 Hz')
13 x1=0.55;
14 x2s=0.24;
15 V1=0.5*400/3^0.5;
16 Tstarting=3*V1^2*r2s/(2*pi*12.5)*(1/((r1+r2s)^2+(x1
    +x2s)^2))
17 printf("\nStarting Torque=%.2 f Nm",Tstarting)
```

Chapter 8

Integrated circuits and operational amplifiers

Scilab code Exa 8.1 Find dc currents and voltages

```
1 //8.1
2 clc;
3 Vcc=12;
4 Re=3.8*10^3;
5 Rc=4.1*10^3;
6 Ie=(Vcc-0.7)/Re*10^3;
7 printf(" Ie=%3f mA" ,Ie)
8 Ic=0.5*Ie;
9 printf("\nIc=%3f mA" ,Ic)
10 Vo=Vcc-Ic*Rc*10^-3;
11 printf("\nVo=%1f V" ,Vo)
```

Scilab code Exa 8.2 Calculate the different parameters of differential amplifier

```
1 //8.2
```

```

2  clc;
3  Vcc=12;
4  Re=1*10^6;
5  Rc=1*10^6;
6  Ie=(Vcc-0.7)/Re*10^3;
7  re=25*2/Ie;
8  printf("re=%0.0f ohm",re)
9  Vgd=Rc/(2*re);
10 printf("\nVoltage gain for the differential input=%0
    .1f ",Vgd)
11 Vi=2.1*10^-3;
12 Vo_Ac=Vgd*Vi;
13 printf("\nAC output voltage=%0.4f V",Vo_Ac)
14 Beta=75;
15 Zi=2*Beta*re;
16 printf("\nInput impedance=%0.0f ohm",Zi)
17 Rc=1*10^6;
18 RE=10^6;
19 CMG=Rc/(re+2*RE);
20 printf("\nCommon mode gain=%0.3f ",CMG)
21 CMRR=Vgd/CMG;
22 printf("\nCommon mode rejection ratio=%0.2f ",CMRR)

```

Scilab code Exa 8.3 Find the closed loop gain output and error voltage

```

1  //8.3
2  clc;
3  open_loop_gain=100000;
4  FF=0.01;
5  Closed_loop_gain=open_loop_gain/(1+open_loop_gain*FF
    );
6  printf("Closed loop gain=%0.1f",Closed_loop_gain)
7  Vi=2*10^-3;
8  output=Vi*Closed_loop_gain;
9  printf("\nOutput=%0.4f V",output)

```

```
10 Error_voltage=output/open_loop_gain*10^6;
11 printf("\nError voltage=%0.3f uV",Error_voltage)
```

Scilab code Exa 8.4 Find the closed loop gain output and error voltage

```
1 //8.4
2 clc;
3 open_loop_gain=15000;
4 FF=0.01;
5 Closed_loop_gain=open_loop_gain/(1+open_loop_gain*FF
   );
6 printf("Closed loop gain=%0.3f",Closed_loop_gain)
7 Vi=2*10^-3;
8 output=Vi*Closed_loop_gain;
9 printf("\nOutput=%0.4f V",output)
10 Error_voltage=output/open_loop_gain*10^6;
11 printf("\nError voltage=%0.3f uV",Error_voltage)
```

Scilab code Exa 8.5 Find the input and output impedances

```
1 //8.5
2 clc;
3 Av=100000;
4 beta=0.01;
5 Zi=2*10^6;
6 Closed_loop_input_imped=Zi*(1+Av*beta)*10^-6;
7 printf("Closed loop input impedance=%0.0f Mega-ohm",
   Closed_loop_input_imped)
8 Zo=75;
9 Closed_loop_output_imped=Zo/(1+Av*beta);
10 printf("\nClosed loop output impedance=%0.4f ohm",
   Closed_loop_output_imped)
```

Scilab code Exa 8.6 Find closed loop gain and desensitivity

```
1 //8.6
2 clc;
3 Av=100000;
4 beta=0.001;
5 Closed_loop_gain=Av/(1+Av*beta);
6 printf("\nClosed loop gain=%0.1f ",Closed_loop_gain)
7 Desensitivity=(1+Av*beta);
8 printf("\nDesensitivity=%0.0f",Desensitivity)
```

Scilab code Exa 8.7 Find the closed loop gain and upper cut off frequency

```
1 //8.7
2 clc;
3 f_unity=10^6;
4 Av=100000;
5 open_loop_upper_cutoff_f=f_unity/Av;
6 printf("open loop upper cutoff frequency=%0.0f Hz",
    open_loop_upper_cutoff_f)
7 disp('when beta=0.001')
8 beta=0.001;
9 Closed_loop_gain=Av/(1+Av*beta);
10 printf("\nClosed loop gain=%0.1f ",Closed_loop_gain)
11 upper_cutoff_frequency=f_unity/Closed_loop_gain;
12 printf("\nUpper cutoff frequency=%0.0f Hz",
    upper_cutoff_frequency)
13 disp('when beta=0.01')
14 beta=0.01;
15 Closed_loop_gain=Av/(1+Av*beta);
16 printf("\nClosed loop gain=%0.1f ",Closed_loop_gain)
17 upper_cutoff_frequency=f_unity/Closed_loop_gain;
```



```

18 printf("\nUpper cutoff frequency=%0.0f Hz",
    upper_cutoff_frequency)
19 disp('when beta=0.1')
20 beta=0.1;
21 Closed_loop_gain=Av/(1+Av*beta);
22 printf("\nClosed loop gain=%0.3f ",Closed_loop_gain)
23 upper_cutoff_frequency=f_unity/Closed_loop_gain;
24 printf("\nUpper cutoff frequency=%0.0f Hz",
    upper_cutoff_frequency)

```

Scilab code Exa 8.8 Find the slew rate

```

1 //8.8
2 clc;
3 Imax=10*10^-6;
4 C=4000*10^-12;
5 Slew_rate=Imax/C;
6 printf("Slew rate=%0.0f V/s", Slew_rate)

```

Scilab code Exa 8.9 Find the slew rate distortion of the op amp

```

1 //8.9
2 clc;
3 f=10*10^3;
4 Vp=6
5 Initial_slope_of_sine_wa=2*pi*f*Vp*10^-6;
6 printf("Initial slope of sine wave= %0.5f V/us",
    Initial_slope_of_sine_wa)
7 disp('Since slew rate of the amplifier is 0.4V/us,
    there is no slew rate distortion')

```

Scilab code Exa 8.10 Find the slew rate distortion of the op amp and amplitude of the input signal

```
1 //8.10
2 clc;
3 f=10*103;
4 Vp=10;
5 Initial_slope_of_sine_wa=2*%pi*f*Vp*10-6;
6 printf("Initial slope of sine wave= %.3f V/us",
       Initial_slope_of_sine_wa)
7 disp('Since slew rate of the amplifier is 0.5V/us,
       so slew rate distortion will occur')
8 Sr=0.5*106;
9 Vp=Sr/(2*%pi*f);
10 printf("Amplitude of the input signal=%.2f V",Vp)
```

Scilab code Exa 8.11 Find the different parameters of inverting amplifier

```
1 //8.11
2 clc;
3 Rf=100*103;
4 R1=1000;
5 Gain=-Rf/R1;
6 printf("Closed loop gain=%.0f", Gain)
7 Av=100000;
8 Zo=75;
9 f_unity=106;
10 beta=R1/(R1+Rf);
11 Z_closed=Zo/(1+Av*beta);
12 printf("\nClosed loop output impedance=%.6f ohm",
       Z_closed)
13 closed_loop_upper_cut_f=f_unity*beta;
14 printf("\nClosed loop upper cutoff frequency=%.0f
       Hz", closed_loop_upper_cut_f)
15 closed_loop_input_impe=1000;
```

```
16 printf("\nClosed loop input impedance=%0.0 f ohm",
        closed_loop_input_impe)
```

Scilab code Exa 8.12 Find the different parameters of non inverting amplifier

```
1 //8.12
2 clc;
3 R2=100*10^3;
4 R1=100;
5 Zin=2*10^6;
6 Zo=75;
7 Gain=(R1+R2)/R1;
8 printf("Closed loop voltage gain=%0.0 f", Gain)
9 Av=100000;
10
11 beta=R1/(R1+R2);
12 Z_closed=Zin*(1+Av*beta)*10^-6;
13 printf("\nClosed loop input impedance=%0.1 f mega-ohm"
        , Z_closed)
14
15 closed_loop_output_impe=Zo/(1+Av*beta);
16 printf("\nClosed loop output impedance=%0.3 f ohm",
        closed_loop_output_impe)
```

Scilab code Exa 8.13 Find the different parameters of ac amplifier

```
1 //8.13
2 clc;
3 R1=1000;
4 R2=100000;
5 Avf=(R1+R2)/R1;
6 printf("Closed loop gain=%0.0 f", Avf)
```

```

7 beta=R1/(R1+R2);
8 f_unity=1000000;
9 f2=f_unity*beta;
10 printf("\nUpper cut off frequency=%0.0 f Hz", f2)
11 disp('Critical frequencies')
12 C1=10^-6;
13 R3=150*10^3;
14 fc=1/(2*%pi*R3*C1);
15 printf("\nCritical frequency when R is 150 Kohm=%0.3 f
      Hz", fc)
16 R3=15*10^3;
17 fc=1/(2*%pi*R3*C1);
18 printf("\nCritical frequency when R is 15 Kohm=%0.2 f
      Hz", fc)
19 R3=1*10^3;
20 fc=1/(2*%pi*R3*C1);
21 printf("\nCritical frequency when R is 1 Kohm=%0.2 f
      Hz", fc)
22 disp('The lower cutt off frequency is the highest of
      the above three critical frequencies i.e.159.15
      Hz')

```

Scilab code Exa 8.14 Find the output voltage

```

1 //8.14
2 clc;
3 Rf=50*10^3;
4 R1=10*10^3;
5 R2=R1;
6 R3=R1;
7 V1=0.5;
8 V2=1.5;
9 V3=0.2;
10 Vo=-Rf*((V1/R1)+(V3/R3)+(V2/R2));
11 printf("Output voltage=%0.0 f V",Vo)

```

Scilab code Exa 8.17 Find the output voltage

```
1 //8.17
2 clc;
3 R1=50*10^3;
4 R=10*10^3;
5 Vs1=4.5;
6 Vs2=5;
7 Vo=R1/R*(Vs2-Vs1);
8 printf("Output voltage=%0.1 f V", Vo)
```

Scilab code Exa 8.18 Find CMRR in dB

```
1 //8.18
2 clc;
3 Vcom=0.5*(2+2);
4 Acom=5*10^-3/Vcom;
5 CMRR=20*log10(50/Acom);
6 printf("CMRR=%0.2 f dB", CMRR)
```

Scilab code Exa 8.21 Find the different parameters of high pass filter

```
1 //8.21
2 clc;
3 R2=5.6*10^3;
4 R1=1*10^3;
5 Avf=1+R2/R1;
6 printf("Mid band Gain=%0.2 f", Avf)
7 Vin=1.6;
```

```

8 Vo=Avf*Vin;
9 printf("\nOutput voltage=%0.3 f mV", Vo)
10 R=1000;
11 C=0.001*10^-6;
12 fc=1/(2*pi*R*C);
13 printf("\nCutt off frequency=%0.2 f Hz", fc)
14 Gain=0.707*Avf;
15 printf("\nGain=%0.3 f", Gain)

```

Scilab code Exa 8.22 Find the different parameters of low pass filter

```

1 //8.22
2 clc;
3 R2=5.6*10^3;
4 R1=10*10^3;
5 Avf=1+R2/R1;
6 printf("Mid band Gain=%0.2 f", Avf)
7 Vin=1.1;
8 Vo=Avf*Vin;
9 printf("\nOutput voltage=%0.3 f mV", Vo)
10 R=10000;
11 C=0.001*10^-6;
12 fc=1/(2*pi*R*C);
13 printf("\nCutt off frequency=%0.2 f Hz", fc)
14 Vo=0.707*Avf;
15 printf("\nOutput voltage=%0.3 f mV", Vo)

```

Chapter 9

Number systems

Scilab code Exa 9.1 Convert decimal number into equivalent binary number

```
1 //9.1
2 clc;
3 x=10;
4 disp('The binary number is ')
5 a=dec2bin(x);
6 disp(' ',a)
```

Scilab code Exa 9.2 Convert decimal number into equivalent binary number

```
1 //9.2
2 clc;
3 x=25;
4 disp('The binary number is ')
5 a=dec2bin(x);
6 disp(' ',a)
```

Scilab code Exa 9.3 Convert binary number into equivalent decimal number

```
1 //9.3
2 clc;
3 a='101110';
4 disp('The decimal no. is ')
5 x=bin2dec(a);
6 disp('',x)
```

Scilab code Exa 9.4 Convert decimal number into equivalent binary number

```
1 //9.4
2 clc;
3 x=15;
4 disp('The binary number of decimal 15 is ')
5 a=dec2bin(x);
6 disp('',a)
7 x=31;
8 disp('The binary number of decimal 31 is ')
9 a=dec2bin(x);
10 disp('',a)
```

Scilab code Exa 9.5 Calculate the subtraction of two binary numbers

```
1 //9.5
2 clc;
3 a='11001';
```



```

4 b=bin2dec(a);
5 c='10001';
6 f=bin2dec(c);
7 d=b-f;
8 s=dec2bin(d);
9 disp('Subtraction of two binary numbers=')
10 disp(s)

```

Scilab code Exa 9.6 Calculate the subtraction of two binary numbers

```

1 //9.6
2 clc;
3 a='1010';
4 b=bin2dec(a);
5 c='0111';
6 f=bin2dec(c);
7 d=b-f;
8 s=dec2bin(d);
9 disp('Subtraction of two binary numbers=')
10 disp(s)

```

Scilab code Exa 9.7 Express the decimals in 16 bit signed binary system

```

1 //9.7
2 clc;
3 a=8;
4 b=dec2bin(a);
5 disp(b)
6 disp('The 16 bit signed binary number of +8=0000
       0000 0000 1000')
7 disp('The 16 bit signed binary number of -8=1000
       0000 0000 1000')
8 a=165;

```

```

9 b=dec2bin(a);
10 disp(b)
11 disp('The 16 bit signed binary number of +165=0000
        0000 1010 0101 ')
12 disp('The 16 bit signed binary number of -165=1000
        0000 1010 0101 ')

```

Scilab code Exa 9.8 Calculate the twos complement representation

```

1 //9.8
2 clc;
3 a='0001 1111';
4 disp(a)
5 disp('Since the MSB is 0 so this is a positive
        number and its 2 s complement representation is')
6 b=bin2dec(a);
7 disp(b)
8 a='1110 0101';
9 disp(a)
10 disp('Since the MSB is 1 so this is a negative
        number and its 2 s complement representation is')
11 c=bin2dec(a);
12 xc= bitcmp (c ,8);
13 b=xc+1;
14 disp(b)
15 a='1111 0111';
16 disp(a)
17 disp('Since the MSB is 1 so this is a negative
        number and its 2 s complement representation is')
18 c=bin2dec(a);
19 xc= bitcmp (c ,8);
20 b=xc+1;
21 disp(b)

```

Scilab code Exa 9.9 Find the largest positive and negative number for 8 bits

```
1 //9.9
2 clc;
3 disp('The largest 8 bit positive number is +127 and
      is represented in binary as')
4 a='0111 1111';
5 disp(a)
6 disp('The largest 8 bit negative number is -128 and
      is represented in binary as')
7 a='1000 0000';
8 disp(a)
```

Scilab code Exa 9.10 Calculate addition and subtraction of the numbers

```
1 //9.10
2 clc;
3 c=24;
4 xc= bitcmp (c ,8);
5 A=xc+1;
6 B=16;
7 Ans=A+B;
8 a=dec2bin(Ans)
9 disp(a)
10 disp('Since the MSB is 1 so the number is negative
      and equal to -8')
11
12 Ans=A-B;
13 a=dec2bin(Ans)
14 disp(a)
```

```
15 disp('Since the MSB is 1 so the number is negative
    and equal to -40')
```

Scilab code Exa 9.11 Calculate addition and subtraction of the numbers

```
1 //9.11
2 clc;
3 c=60;
4 xc= bitcmp (c ,8);
5 A=xc+1;
6 d=28;
7 xd= bitcmp (d ,8);
8 B=xd+1;
9 Ans=B+A;
10 a=dec2bin(Ans)
11 disp(a)
12 disp('Since the MSB is 1 so the number is negative
    and equal to -88')
13 Ans=B-A;
14 a=dec2bin(Ans,8)
15 disp(a)
16 disp('Since the MSB is 0 so the number is positive
    and equal to +32')
```

Scilab code Exa 9.12 Convert decimal number into equivalent binary number

```
1 // 9.12
2 clc;
3 q =0;
4 b =0;
5 s =0;
```

```

6 a =0.6875;    // accepting the decimal input from
    user
7 d = modulo (a ,1) ;
8 a = floor ( a ) ;
9 while (a >0)
10 x = modulo (a ,2) ;
11 b = b + (10^ q ) * x ;
12 a = a /2;
13 a = floor ( a ) ;
14 q = q +1;
15 end
16 for i =1:10
17 // for fractional part
18 d = d *2;
19 q = floor ( d ) ;
20 s = s + q /(10^ i ) ;
21 if d >=1 then
22 d =d -1;
23 end
24 end
25 m=b+s;
26 printf("Equivalent binary number=%0.4f",m)

```

Scilab code Exa 9.13 Convert decimal number into equivalent binary number

```

1 // 9.13
2 clc;
3 q =0;
4 b =0;
5 s =0;
6 a =0.634;    // accepting the decimal input from user
7 d = modulo (a ,1) ;
8 a = floor ( a ) ;
9 while (a >0)

```

```

10 x = modulo (a ,2) ;
11 b = b + (10^ q ) * x ;
12 a = a /2;
13 a = floor ( a ) ;
14 q = q +1;
15 end
16 for i =1:10
17 // for fractional part
18 d = d *2;
19 q = floor ( d ) ;
20 s = s + q /(10^ i ) ;
21 if d >=1 then
22 d =d -1;
23 end
24 end
25 m=b+s;
26 printf("Equivalent binary number=%0.7f",m)

```

Scilab code Exa 9.14 Convert decimal number into equivalent binary number

```

1 // 9.14
2 clc;
3 clear;
4 q =0;
5 b =0;
6 s =0;
7 a =39.12; // accepting the decimal input from user
8 d = modulo (a ,1) ;
9 a = floor ( a ) ;
10 while (a >0)
11 x = modulo (a ,2) ;
12 b = b + (10^ q ) * x ;
13 a = a /2;
14 a = floor ( a ) ;

```

```

15  q = q +1;
16  end
17  for i =1:10
18  // for fractional part
19  d = d *2;
20  q = floor ( d ) ;
21  s = s + q /(10^ i ) ;
22  if d >=1 then
23  d =d -1;
24  end
25  end
26  m=b+s;
27  printf(" Equivalent binary number=%0.7f" ,m)

```

Scilab code Exa 9.15 Find the addition of binary numbers

```

1  //9.15
2  clc;
3  a='1011010101';
4  d=bin2dec(a);
5  c='100011010';
6  b=bin2dec(c);
7  e=d+b;
8  f=dec2bin(e);
9  disp('addition of binary numbers =')
10 disp(f)

```

Scilab code Exa 9.16 Convert binary number into equivalent decimal number

```

1  //9.16
2  clc;
3  p =1;

```

```

4  q =1;
5  z =0;
6  b =0;
7  w =0;
8  f =0;
9  bin =11001.001011; // binary input
10 d = modulo (bin ,1) ;
11 d= d *10^10;
12 a = floor ( bin ) ;
13 while (a >0)
14 r = modulo (a ,10) ;
15 b(1,q) = r ;
16 a=a /10;
17 a= floor ( a ) ;
18 q = q +1;
19 end
20 for m =1: q -1
21 c=m -1;
22 f=f+b(1,m) *(2^ c);
23 end
24 while (d >0)
25 e = modulo (d ,2)
26 w (1 , p ) = e
27 d = d /10;
28 d = floor ( d )
29 p = p +1;
30 end
31 for n =1: p -1
32 z = z + w (1 , n ) *(0.5) ^(11 - n ) ;
33 end
34 z = z *10000;
35 z = round ( z ) ;
36 z = z /10000;
37 x=f+z;
38 printf("Equivalent decimal number=%0.6 f" ,x)

```

Scilab code Exa 9.17 Convert hexadecimal number into equivalent decimal number

```
1 //9.17
2 clc;
3 a='8A3';
4 disp('The decimal no. is ')
5 x=hex2dec(a);
6 disp('',x)
```

Scilab code Exa 9.18 Convert decimal number into equivalent hexadecimal number

```
1 //9.18
2 clc;
3 a=268;
4 disp('The hexa decimal no. is ')
5 x=dec2hex(a);
6 disp('',x)
```

Scilab code Exa 9.19 Convert decimal number into equivalent hexadecimal number

```
1 //9.19
2 clc;
3 a=5741;
4 disp('The hexa decimal no. is ')
5 x=dec2hex(a);
6 disp('',x)
```

Scilab code Exa 9.20 Convert hexadecimal number into equivalent decimal number

```
1 //9.20
2 clc;
3 a='D70';
4 disp('The decimal no. is ')
5 x=hex2dec(a);
6 disp('',x)
```
