

Scilab Textbook Companion for  
Modern Electronic Instrumentation And  
Measurement Techniques  
by A. D. Helfrick And W. D. Cooper<sup>1</sup>

Created by  
Abhijith C D  
B.E  
Electronics Engineering  
National Institute of Engineering  
College Teacher  
M.s. Vijaykumar  
Cross-Checked by  
TechPassion

August 10, 2013

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Modern Electronic Instrumentation And Measurement Techniques

**Author:** A. D. Helfrick And W. D. Cooper

**Publisher:** Dorling Kindersly Pvt. Ltd. India

**Edition:** 1

**Year:** 2009

**ISBN:** 978-81-317-0888-0

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Measurement and Error	6
2 Systems of Units of Measurement	23
4 Electromechanical Indicating Instruments	28
5 Bridge Measurements	43
6 Electronic Instruments for Measuring Basic Parameters	52
7 Oscilloscopes	61
9 Signal Analysis	63
11 Transducers as Input Elements to Instrumentation Systems	67
12 Analog and Digital Data Acquisition Systems	69
14 Fiber Optics Measurements	71

# List of Scilab Codes

Exa 1.1	To find Average voltage Range of error . . . . .	6
Exa 1.2	To find Total resistance . . . . .	7
Exa 1.3	To find voltage drop across resistor . . . . .	8
Exa 1.4	To find sum with range of doubt . . . . .	9
Exa 1.5	To find difference with range of doubt . . . . .	10
Exa 1.6	To find difference with range of doubt . . . . .	11
Exa 1.7	To find Apparent and actual resistance . . . . .	12
Exa 1.8	To find Apparent and actual resistance . . . . .	14
Exa 1.9	To find Arithmetic mean and deviation from mean . . . . .	15
Exa 1.10	To find Average deviation . . . . .	17
Exa 1.11	To find Std deviation and Probable error . . . . .	18
Exa 1.12	To find Limiting error . . . . .	19
Exa 1.13	To find the maximum error . . . . .	20
Exa 1.14	To find limiting error . . . . .	21
Exa 2.1	To convert area in metre to feet . . . . .	23
Exa 2.2	To convert flux density to different units . . . . .	24
Exa 2.3	To convert velocity to a different unit . . . . .	24
Exa 2.4	To convert density to a different unit . . . . .	25
Exa 2.5	To convert speed limit to a different unit . . . . .	26
Exa 4.1	To find Shunt resistance required . . . . .	28
Exa 4.2	To design Ayrton shunt . . . . .	29
Exa 4.3	To design multirange dc voltmeter . . . . .	31
Exa 4.4	To design multirange dc voltmeter . . . . .	32
Exa 4.5	To find voltage reading and Error . . . . .	34
Exa 4.6	To find the value of unknown resistor . . . . .	36
Exa 4.7	To find the scale error . . . . .	37
Exa 4.8	To find shunt and current limiting resistor . . . . .	39
Exa 4.9	To find multiplier resistor . . . . .	40

Exa 4.10	To find voltmeter sensitivity on AC range . . . . .	41
Exa 5.1	To find deflection caused by the given unbalance . . . .	43
Exa 5.2	To check the capability of detecting unbalance . . . . .	44
Exa 5.3	To find the unknown impedance . . . . .	46
Exa 5.4	To find the unknown impedance . . . . .	48
Exa 5.5	To balance the unbalanced bridge . . . . .	49
Exa 6.1	To find the form factor and error . . . . .	52
Exa 6.2	To find the form factor and error . . . . .	53
Exa 6.3	To find the maximum time . . . . .	55
Exa 6.4	To find the distributed capacitance . . . . .	56
Exa 6.5	To find the self capacitance . . . . .	57
Exa 6.6	To find percentage error . . . . .	58
Exa 6.7	To find percentage error . . . . .	59
Exa 7.1	To find minimum distance . . . . .	61
Exa 9.1	To find dynamic range of spectrum analyser . . . . .	63
Exa 9.2	To find minimum detectable signal . . . . .	64
Exa 9.3	To find dynamic range and total frequency display . .	65
Exa 11.1	To find change in resistance . . . . .	67
Exa 12.1	To find percentage error . . . . .	69
Exa 14.1	To find acceptance angle and numerical aperture . . . .	71
Exa 14.2	To find loss in the fiber . . . . .	72
Exa 14.3	To find current developed in photodiode . . . . .	73
Exa 14.4	To find elapsed time . . . . .	74

# Chapter 1

## Measurement and Error

**Scilab code Exa 1.1** To find Average voltage Range of error

```
1 // To find Average voltage Range of error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-1 in Page 3
7
8
9 clear; clc; close;
10
11 // Given data
12 E_1 = 117.02; // Voltage observed by 1st observer is
   117.02V
13 E_2 = 117.11; // Voltage observed by 2nd observer is
   117.11V
14 E_3 = 117.08; // Voltage observed by 3rd observer is
   117.08V
15 E_4 = 117.03; // Voltage observed by 4th observer is
   117.03V
16
```

```

17 // Calculations
18 E_av = (E_1+E_2+E_3+E_4)/4;
19 printf("(a) The average voltage , E_av = %0.2f V\n "
    ,E_av);
20
21 E_max = max (E_1,E_2,E_3,E_4); // Maximum value
    among the 4 nos
22 E_min = min (E_1,E_2,E_3,E_4); // Minimum value
    among the 4 nos
23
24 range_1 = E_max - E_av; // Range calculated using
    two different formulae
25 range_2 = E_av - E_min; // Range calculated using
    two different formulae
26
27 avg_range = (range_1+range_2)/2
28 printf("(b) The average range of error = +/- %0.2f
    V",avg_range);
29
30 // Result
31 // (a) The average voltage , E_av = 117.06 V
32 // (b) The average range of error = +/- 0.05 V

```

---

**Scilab code Exa 1.2** To find Total resistance

```

1 // To find Total resistance
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-2 in Page 4
7

```



```

8
9 clear; clc; close;
10
11 // Given data
12 R_1 = 18.7; // The first resistance is 18.7ohm
13 R_2 = 3.624; // The second resistance is 3.624ohm
14
15 // Calculations
16 R_T = R_1 + R_2; // formula to calculate total
    resistance in series
17 printf("The total resistance connected in series =
    %0.3f ohm\n",R_T);
18 printf("As one of the resistance is accurate to only
    tenths of an ohm, The result should be reduced
    to the nearest tenth. \n Hence ")
19 printf("the total resistance is = %0.1f ohm",R_T);
20
21 //Result
22 // The total resistance connected in series = 22.324
    ohm
23 // As one of the resistance is accurate to only
    tenths of an ohm, The result should be reduced to
    the nearest tenth.
24 // Hence the total resistance is = 22.3 ohm

```

---

**Scilab code Exa 1.3** To find voltage drop across resistor

```

1 // To find voltage drop across resistor
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India

```

```

6 // Example 1-3 in Page 4
7
8
9 clear; clc; close;
10
11 // Given data
12 I = 3.18; //Current flowing through the resistor =
    3.18A
13 R = 35.68; // The value of resistor = 35.68ohm
14
15 // Calculations
16 E = I*R;
17 printf("The voltage drop across the resistor = %0.4f
    volts",E);
18 disp('Since there are 3 significant figures involved
    in the multiplication , the result can be written
    only to a max of 3 significant figures ');
19 printf("Hence the voltage drop across the resistor =
    %0.0f volts",E);
20
21 //Result
22 // The voltage drop across the resistor = 113.4624
    volts
23 // Since there are 3 significant figures involved in
    the multiplication , the result can be written
    only to a max of 3 significant figures
24 // Hence the voltage drop across the resistor = 113
    volts

```

---

**Scilab code Exa 1.4** To find sum with range of doubt

```

1 // To find sum with range of doubt
2 // Modern Electronic Instrumentation And Measurement

```

```

Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-4 in Page 5
7
8
9 clear; clc; close;
10
11 // Given data
12 // let N_1 = X_1 +/- Y_1
13 //      N_2 = X_2 +/- Y_2
14 X_1 = 826;
15 Y_1 = 5;
16 X_2 = 628;
17 Y_2 = 3;
18
19 // Calculations
20 X = (X_1 + X_2);
21 Y = (Y_1 + Y_2);
22 printf("SUM = %d +/- %d\n",X,Y);
23 %doubt = Y/X*100;
24 printf("The percentage range of doubt = +/-%0.2f%%",
        %doubt);
25
26 // Result
27 // SUM = 1454 +/- 8
28 // The percentage range of doubt = +/-0.55%

```

---

**Scilab code Exa 1.5** To find difference with range of doubt

```

1 // To find difference with range of doubt
2 // Modern Electronic Instrumentation And Measurement

```

```

Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-5 in Page 5
7
8
9 clear; clc; close;
10
11 // Given data
12 // let N_1 = X_1 +/- Y_1
13 //      N_2 = X_2 +/- Y_2
14 X_1 = 826;
15 Y_1 = 5;
16 X_2 = 628;
17 Y_2 = 3;
18
19 // Calculations
20 X = (X_1 - X_2);
21 Y = (Y_1 + Y_2);
22 printf(" Difference = %d +/- %d\n" ,X,Y);
23 %doubt = Y/X*100;
24 printf("The percentage range of doubt = +/-%0.2f%%" ,
    %doubt);
25
26 //Result
27 // Difference = 198 +/- 8
28 // The percentage range of doubt = +/-4.04%

```

---

**Scilab code Exa 1.6** To find difference with range of doubt

```

1 // To find difference with range of doubt
2 // Modern Electronic Instrumentation And Measurement

```

```

Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-6 in Page 5
7
8
9 clear; clc; close;
10
11 // Given data
12 // let N_1 = X_1 +/- Y_1
13 //      N_2 = X_2 +/- Y_2
14 X_1 = 462;
15 Y_1 = 4;
16 X_2 = 437;
17 Y_2 = 4;
18
19 // Calculations
20 X = (X_1 - X_2);
21 Y = (Y_1 + Y_2);
22 printf(" Difference = %d +/- %d\n" ,X,Y);
23 %doubt = Y/X*100;
24 printf("The percentage range of doubt = +/-%0.2f%%" ,
    %doubt);
25
26 //Result
27 // Difference = 25 +/- 8
28 // The percentage range of doubt = +/-32.00%

```

---

**Scilab code Exa 1.7** To find Apparent and actual resistance

```

1 // To find Apparent and actual resistance
2 // Modern Electronic Instrumentation And Measurement

```

```

Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-7 in Page 6
7
8
9 clear; clc; close;
10
11 // Given data
12 I_T = 5*(10^-3); // Reading of the milliammeter in
    ampere
13 V_T = 100; // Reading of the voltmeter in volt
14 sensitivity = 1000; // sensitivity of voltmeter in
    ohm/volt
15 scale = 150; // scale of the voltmeter
16
17 // Calculations
18 R_T = V_T / I_T; // formula to calculate total
    circuit resistance
19 printf("(a) The apparent circuit resistance
    neglecting the resistance of milliammeter , R_T =
    %d ohm\n",R_T);
20
21 R_V = sensitivity * scale; // calculating resistance
    of voltmeter
22 R_X = (R_T * R_V)/(R_V - R_T); // effective circuit
    resistance due to loading effect
23 printf("(b) The actual circuit resistance with the
    loading effect of voltmeter , R_X = %0.2f ohm\n",
    R_X);
24
25 percentage_error = (R_X - R_T)*100/ R_X;
26 // %error = (actual-apparent)/ actual
27 printf("(c) The percentage error due to loading
    effect of voltmeter = %0.2f%%",percentage_error);
28
29 //result

```

```

30 // (a) The apparent circuit resistance neglecting
    the resistance of milliammeter , R_T = 20000 ohm
31 // (b) The actual circuit resistance with the
    loading effect of voltmeter , R_X = 23076.92 ohm
32 // (c) The percentage error due to loading effect
    of voltmeter = 13.33%
33
34
35 // The result shown in the textbook is printed
    incorrectly and does not match with the correct
    result

```

---

**Scilab code Exa 1.8** To find Apparent and actual resistance

```

1 // To find Apparent and actual resistance
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-8 in Page 7
7
8
9 clear; clc; close;
10
11 // Given data
12 I_T = 800*(10^-3); // Reading of the milliammeter in
    ampere
13 V_T = 40; // Reading of the voltmeter in volt
14 sensitivity = 1000; // sensitivity of voltmeter in
    ohm/volt
15 scale = 150; // scale of the voltmeter
16

```

```

17 // Calculations
18 R_T = V_T / I_T; // formula to calculate total
    circuit resistance
19 printf("(a) The apparent circuit resistance
    neglecting the resistance of milliammeter, R_T =
    %0.2f ohm\n", R_T);
20
21 R_V = sensitivity * scale; // calculating resistance
    of voltmeter
22 R_X = (R_T * R_V) / (R_V - R_T); // effective circuit
    resistance due to loading effect
23 printf("(b) The actual circuit resistance with the
    loading effect of voltmeter, R_X = %0.2f ohm\n",
    R_X);
24
25 percentage_error = (R_X - R_T) * 100 / R_X;
26 // %error = (actual - apparent) / actual
27 printf("(c) The percentage error due to loading
    effect of voltmeter = %0.2f%%", percentage_error);
28
29 // result
30 // (a) The apparent circuit resistance neglecting
    the resistance of milliammeter, R_T = 50.00 ohm
31 // (b) The actual circuit resistance with the
    loading effect of voltmeter, R_X = 50.02 ohm
32 // (c) The percentage error due to loading effect
    of voltmeter = 0.03%
33
34
35 // The result shown in the textbook is printed
    incorrectly and does not match with the correct
    result

```

---



**Scilab code Exa 1.9** To find Arithmetic mean and deviation from mean

```
1 // To find Arithmetic mean and deviation from mean
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-9 in Page 9
7
8
9 clear; clc; close;
10
11 // Given data
12 // Independent current measurements taken by six
   observers
13 I_1 = 12.8*(10^-3);
14 I_2 = 12.2*(10^-3);
15 I_3 = 12.5*(10^-3);
16 I_4 = 13.1*(10^-3);
17 I_5 = 12.9*(10^-3);
18 I_6 = 12.4*(10^-3);
19
20 // Calculations
21 arithmetic_mean = (I_1 +I_2 +I_3 +I_4 +I_5 +I_6)/6;
22 printf("(a) The arithmetic mean of the observations
   =%0.5f A",arithmetic_mean);
23
24 d_1 = I_1 - arithmetic_mean;
25 d_2 = I_2 - arithmetic_mean;
26 d_3 = I_3 - arithmetic_mean;
27 d_4 = I_4 - arithmetic_mean;
28 d_5 = I_5 - arithmetic_mean;
29 d_6 = I_6 - arithmetic_mean;
30
31 //deviation calculated using the formula d_n = x_n -
   arithmetic_mean
32 disp('(b) The deviations from the mean are: ');
```

```

33 printf("d_1 = %0.5 f A\n d_2 = %0.5 f A\n d_3 = %0.5 f
    A\n d_4 = %0.5 f A\n d_5 = %0.5 f A\n d_6 = %0.5 f A
    \n", d_1, d_2, d_3, d_4, d_5, d_6);
34
35 //Result
36 // (a) The arithmetic mean of the observations
    =0.01265 A
37 // (b) The deviations from the mean are:
38 // d_1 = 0.00015 A
39 // d_2 = -0.00045 A
40 // d_3 = -0.00015 A
41 // d_4 = 0.00045 A
42 // d_5 = 0.00025 A
43 // d_6 = -0.00025 A

```

---

**Scilab code Exa 1.10** To find Average deviation

```

1 // To find Average deviation
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-10 in Page 10
7
8
9 clear; clc; close;
10
11 // Given data
12 // These are the data found out from the example_1-9
13 d_1 = 0.000150;
14 d_2 = -0.000450;
15 d_3 = -0.000150;

```

```

16 d_4 = 0.000450;
17 d_5 = 0.000250;
18 d_6 = -0.000250;
19
20 // Calculation
21 D = (abs(d_1) +abs(d_2) +abs(d_3) +abs(d_4) +abs(d_5
    ) +abs(d_6))/6;
22 printf("The average deviation , D = %0.2e A",D);
23
24 //Result
25 // The average deviation , D = 2.83e-004 A

```

---

**Scilab code Exa 1.11** To find Std deviation and Probable error

```

1 // To find Std deviation and Probable error
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-11 in Page 14
7
8
9 clear; clc; close;
10
11 // Given data
12 // let the 10 resistance measurements in ohm be
  taken as elements of matrix
13 x = [101.2 101.7 101.3 101.0 101.5 101.3 101.2 101.4
    101.3 101.1];
14
15 //Calculations
16 arithmetic_mean = mean(x);

```

```

17 sigma = st_deviation(x);
18 probable_error = 0.6745 * sigma;
19 printf("(a) The arithmetic mean of the readings =
    %0.1f ohm\n", arithmetic_mean);
20 printf("(b) The standard deviation of the readings
    = %0.1f ohm\n", sigma);
21 printf("(c) The probable error of the readings = %0
    .4f ohm", probable_error);
22
23 //Result
24 // (a) The arithmetic mean of the readings = 101.3
    ohm
25 // (b) The standard deviation of the readings = 0.2
    ohm
26 // (c) The probable error of the readings = 0.1349
    ohm

```

---

**Scilab code Exa 1.12** To find Limiting error

```

1 // To find Limiting error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-12 in Page 14
7
8
9 clear; clc; close;
10
11 // Given data
12 scale = 150;
13 percentage_accuracy = 1/100; // accuracy of 1% full

```

```

    scale reading
14 V = 83; //voltage measured by instrument = 83 volt
15
16 //Calculations
17 limiting_error = percentage_accuracy * scale;
18 printf("The magnitude of the limiting error = %0.1f
    V\n",limiting_error);
19
20 percentage_error = limiting_error/V * 100;
21 printf("The percentage limiting error = %0.2f
    percent",percentage_error);
22
23 //Result
24 // The magnitude of the limiting error = 1.5 V
25 // The percentage limiting error = 1.81 percent

```

---

**Scilab code Exa 1.13** To find the maximum error

```

1 // To find the maximum error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-13 in Page 15
7
8
9 clear; clc; close;
10
11 // Given data
12 // For the given tolerance of 0.1%
13 // highest value of resistor is 1.001 times the
    nominal value

```

```

14 // lowest value of resistor is 0.999 times the
    nominal value
15
16 // Calculations
17 V_out_max = 1.001 * 1.001/ 0.999;
18 V_out_min = 0.999 * 0.999/ 1.003;
19 total_var = 0.1 * 3; // total variation of the
    resultant voltage is sum of tolerences
20 printf("The total variation of the resultant voltage
    = +/- %0.1f %%",total_var);
21
22 // Result
23 // The total variation of the resultant voltage =
    +/- 0.3 %

```

---

**Scilab code Exa 1.14** To find limiting error

```

1 // To find limiting error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 1-14 in Page 16
7
8
9 clear; clc; close;
10
11 // Given data
12 // let I = X_1 +/- Y_1
13 //      R = X_2 +/- Y_2
14 X_1 = 2.00;
15 Y_1 = 0.5;

```

```

16 X_2 = 100;
17 Y_2 = 0.2;
18
19 // Calculations
20 P_1 = ((1+0.005)^2)*(1+0.002);
21 printf("For the worst possible combination of the
        values of current and resistance ,\nThe highest
        power dissipation becomes ,\n");
22 printf("P = %0.3f (I^2)*R Watts\n",P_1);
23 P_2 = ((1-0.005)^2)*(1-0.002);
24 printf("For the lowest power dissipation .\nP = %0.3f
        (I^2)*R Watts\n",P_2)
25 lim_error = 2 * Y_1 + Y_2;
26 printf("The limiting error = +/- %0.1f%%",lim_error)
        ;
27
28 // Result
29 // For the worst possible combination of the values
        of current and resistance ,
30 // The highest power dissipation becomes ,
31 // P = 1.012 (I^2)*R Watts
32 // For the lowest power dissipation .
33 // P = 0.988 (I^2)*R Watts
34 // The limiting error = +/- 1.2%

```

---

# Chapter 2

## Systems of Units of Measurement

Scilab code Exa 2.1 To convert area in metre to feet

```
1 // To convert area in metre to feet
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-1 in Page 29
7
8 clear; clc; close;
9
10 // Given data
11 A_m = 5000; // area in metre^2 unit
12
13 // Calculation
14 A_ft = A_m * (1/0.3048)^2; // As 1 ft = 0.3048m
15 printf("The area in feet = %d sq.ft", round(A_ft));
16
17 //Result
18 // The area in feet = 53820 sq.ft
```



---

**Scilab code Exa 2.2** To convert flux density to different units

```
1 // To convert flux density to different units
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-2 in Page 29
7
8 clear; clc; close;
9
10 // Given data
11 B_cm = 20; // flux density in maxwell/sq.cm
12
13 // Calculations
14
15 B_in = B_cm *2.54^2; // converting to lines/sq.inch
16 printf("The flux density in lines/sq.in = %d lines/(
   in ^2)",B_in);
17
18 //Result
19 // The flux density in lines/sq.in = 129 lines/(in
   ^2)
```

---

**Scilab code Exa 2.3** To convert velocity to a different unit

```

1 // To convert velocity to a different unit
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-3 in Page 29
7
8 clear; clc; close;
9
10 // Given data
11 c_s = 2.997925 * 10^8; // velocity in m/s
12
13 // Calculations
14 c_hr = 2.997925 *10^8* 1/10^3* 3.6*10^3; // velocity
  in km/hr
15 printf("The velocity of light in km/hr = %0.3e km/hr
  ",c_hr);
16
17 //Result
18 // The velocity of light in km/hr = 1.079e+009 km/hr

```

---

**Scilab code Exa 2.4** To convert density to a different unit

```

1 // To convert density to a different unit
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-4 in Page 29
7
8 clear; clc; close;

```

```

9
10 // Given data
11 Density_ft = 62.5;
12
13 // Calculations
14 Density_in = 62.5 * (1/12)^3;
15 Density_cm = Density_in * 453.6 * (1/2.54)^3;
16 printf("(a) The density of water in lb/cubic inch =
        %f lb/(in^3).\n",Density_in);
17 printf("(b) The density of water in g/cubic cm = %f
        g/(cm^3).",Density_cm);
18
19 //Result
20 // (a) The density of water in lb/cubic inch =
        0.036169 lb/(in^3).
21 // (b) The density of water in g/cubic cm =
        1.001171 g/(cm^3).

```

---

**Scilab code Exa 2.5** To convert speed limit to a different unit

```

1 // To convert speed limit to a different unit
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 2-5 in Page 30
7
8 clear; clc; close;
9
10 // Given data
11 speed_km = 60; // speed limit in km/hr
12

```

```
13 // Calculations
14 speed_m = 60 *10^3 *10^2 *(1/2.54) *(1/12)*(1/5280);
15 speed_ft = 37.3 *5280 *(1/(3.6*10^3));
16
17 printf("(a) The speed limit in m/hr = %0.1f mi/hr\n
    ",speed_m);
18 printf("(b) The speed limit in ft/s = %0.1f ft/s",
    speed_ft);
19
20 // Result
21 // (a) The speed limit in m/hr = 37.3 mi/hr
22 // (b) The speed limit in ft/s = 54.7 ft/s
23
24
25 //The answer given in textbook is printed
    incorrectly and does not match with calculated
    answer
```

---

## Chapter 4

# Electromechanical Indicating Instruments

Scilab code Exa 4.1 To find Shunt resistance required

```
1 // To find Shunt resistance required
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-1 in Page 56
7
8
9 clear; clc; close;
10
11 // Given data
12 I_m = 1*(10^-3); //Full scale deflection of the
  movement in ampere
13 R_m = 100; //Internal resistance of the movement(the
  coil) in ohm
14 I = 100*(10^-3); //Full scale of the ammeter
  including the shunt in Ampere
15
```

```

16 // Calculations
17 I_s = I - I_m; // calculating current through shunt
18 R_s = I_m * R_m / I_s; // calculating shunt to be
    added
19 printf("The value of the shunt resistance required ,
    R_s = %0.2f ohm", R_s);
20
21 // Result
22 // The value of the shunt resistance required , R_s =
    1.01 ohm

```

---

**Scilab code Exa 4.2** To design Ayrton shunt

```

1 // To design Ayrton shunt
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-2 in Page 57
7
8
9 clear; clc; close;
10
11 // Given data
12 I_1 = 1; // Full scale currents of the ammeter in amp
13 I_2 = 5;
14 I_3 = 10;
15 R_m = 50; // Internal resistance of the movement (the
    coil) in ohm
16 I_m = 1*(10^-3); // Full scale deflection of the
    movement in ampere
17

```

```

18 // Calculations
19 // On the 1-A range:
20 I_s1 = I_1 - I_m; // calculating current through
    shunt
21 // Using the eq.  $R_s = I_m * R_m / I_s$ 
22 //1  $R_a + R_b + R_c = I_m * R_m /$ 
    I_s; // As  $(R_a + R_b + R_c)$  are parallel with  $R_m$ 
23
24 // On the 5-A range
25 I_s2 = I_2 - I_m;
26 //2  $R_a + R_b = I_m * (R_c + R_m$ 
    )/ I_s; // As  $(R_a + R_b)$  in parallel with  $(R_c + R_m$ 
    )
27
28 // On the 10-A range
29 I_s3 = I_3 - I_m;
30 //3  $R_a = I_m * (R_b + R_c + R_m$ 
    )/ I_s; // As  $R_a$  is parallel with  $(R_b + R_c + R_m$ 
    )
31
32
33 // Solving the 3 simultaneous linear equations
34 function y = rr(R);
35 y(1) = R(1) + R(2) + R(3) - (I_m * R_m / I_s1);
36 y(2) = R(1) + R(2) - (I_m * (R(3) + R_m) / I_s2);
37 y(3) = R(1) - (I_m * (R(2) + R(3) + R_m) / I_s3);
38 endfunction
39
40 answer = fsolve([0.1; 0.1; 0.1], rr);
41 R_a = answer([1]);
42 R_b = answer([2]);
43 R_c = answer([3]);
44
45 disp('The different resistors used for the ayrtton
    shunt for different ranges are:');
46 printf("R_a = %f ohm\n", R_a);
47 printf("R_b = %f ohm\n", R_b);
48 printf("R_c = %f ohm", R_c);

```

```

49
50 //Result
51 // The different resistors used for the ayrton shunt
    for different ranges are:
52 // R_a = 0.005005 ohm
53 // R_b = 0.005005 ohm
54 // R_c = 0.040040 ohm

```

---

**Scilab code Exa 4.3** To design multirange dc voltmeter

```

1 // To design multirange dc voltmeter
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-3 in Page 60
7
8
9 clear; clc; close;
10
11 // Given data
12 R_m = 100; // internal resistance of movement
13 I_fsd = 1*(10^-3); //full-scale current in Amp
14 V_1 = 10; //different ranges in volt
15 V_2 = 50;
16 V_3 = 250;
17 V_4 = 500;
18
19 //Calculations
20
21 //For the 10-V range
22 R_T = V_1 / I_fsd;

```



```

23 R_4 = R_T - R_m;
24 printf("The value of the resistance R_4 = %d ohm\n",
        R_4);
25
26 //For the 50-V range
27 R_T = V_2 / I_fsd;
28 R_3 = R_T - (R_4 +R_m);
29 printf("The value of the resistance R_3 = %dk ohm\n"
        ,R_3/1000);
30
31 //For the 250-V range
32 R_T = V_3 / I_fsd;
33 R_2 = R_T -(R_3 +R_4 +R_m);
34 printf("The value of the resistance R_2 = %dk ohm\n"
        ,R_2/1000);
35
36 //For the 500-V range
37 R_T = V_4 / I_fsd;
38 R_1 = R_T - (R_2 +R_3 +R_4 +R_m);
39 printf("The value of the resistance R_1 = %dk ohm",
        R_1/1000);
40
41 //Result
42 // The value of the resistance R_4 = 9900 ohm
43 // The value of the resistance R_3 = 40k ohm
44 // The value of the resistance R_2 = 200k ohm
45 // The value of the resistance R_1 = 250k ohm

```

---

**Scilab code Exa 4.4** To design multirange dc voltmeter

```

1 // To design multirange dc voltmeter
2 // Modern Electronic Instrumentation And Measurement
  Techniques

```

```

3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-4 in Page 62
7
8
9 clear; clc; close;
10
11 // Given data
12 // This is a repetition of example_4-3 with
    sensitivity method
13 R_m = 100; // internal resistance of movement
14 I_fsd = 1*(10^-3); //full-scale current in Amp
15 V_1 = 10; //different ranges in volt
16 V_2 = 50;
17 V_3 = 250;
18 V_4 = 500;
19
20 // Calculations
21 S = 1/ I_fsd; // sensitivity in ohm/V
22 R_4 = (S * V_1)-R_m;
23 R_3 = (S * V_2)-(R_4 +R_m);
24 R_2 = (S * V_3)-(R_3 +R_4 +R_m);
25 R_1 = (S * V_4)-(R_2 +R_3 +R_4 +R_m);
26
27 printf("The value of the resistance R_4 = (%dohm/V *
    %dV)- %dohm = %d ohm\n",S,V_1,R_m,R_4);
28 printf("The value of the resistance R_3 = (%dohm/V *
    %dV)- %dohm = %dK ohm\n",S,V_2,(R_4+R_m),R_3
    /1000);
29 printf("The value of the resistance R_2 = (%dohm/V *
    %dV)- %dohm = %dK ohm\n",S,V_3,(R_3 +R_4 +R_m),
    R_2/1000);
30 printf("The value of the resistance R_1 = (%dohm/V *
    %dV)- %dohm = %dK ohm",S,V_4,(R_2 +R_3 +R_4 +R_m
    ),R_1/1000);
31
32 // Result

```

```

33 // The value of the resistance R_4 = (1000ohm/V *10V
    )- 100ohm = 9900 ohm
34 // The value of the resistance R_3 = (1000ohm/V *50V
    )- 10000ohm = 40K ohm
35 // The value of the resistance R_2 = (1000ohm/V *250
    V)- 50000ohm = 200K ohm
36 // The value of the resistance R_1 = (1000ohm/V *500
    V)- 250000ohm = 250K ohm

```

---

**Scilab code Exa 4.5** To find voltage reading and Error

```

1 // To find voltage reading and Error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-5 in Page 62
7
8 clear; clc; close;
9
10 // Given data
11 // resistances in series
12 R_1 = 100 * 10^3;
13 R_2 = 50 *10^3;
14 // sensitivity of two voltmeters
15 S_1 = 1000;
16 S_2 = 20000;
17 V = 50; // range of the voltmeters
18 E = 150; // voltage of battery in volt
19
20 //Calculations
21 //By voltage divider rule

```

```

22 V_true = R_2 / (R_1 + R_2) * E;
23 printf("The true voltage across resistor R_2 = %d V\n", V_true);
24
25 // Reading of the first voltmeter
26 R_T1 = S_1 * V; // resistance of voltmeter =
    sensitivity * range
27 R_p = (R_2 * R_T1) / (R_2 + R_T1) // effective parallel
    resistance
28 R_c1 = R_1 + R_p // The total circuit resistance
29 V_1 = 25 * 10^3 / R_c1 * E;
30 printf("The reading of the first voltmeter = %d V\n", V_1);
31
32 // Reading of the second voltmeter
33 R_T2 = S_2 * V; // resistance of voltmeter =
    sensitivity * range
34 R_p = (R_2 * R_T2) / (R_2 + R_T2)
35 R_c2 = R_1 + R_p // The total circuit resistance
36 V_2 = 47.6 * 10^3 / R_c2 * E;
37 printf("The reading of the second voltmeter = %0.2f
    V\n", V_2);
38
39 %error_1 = (V_true - V_1) / V_true * 100;
40 printf("The error in the reading due to voltmeter 1
    = %d%%\n", %error_1);
41 %error_2 = (V_true - V_2) / V_true * 100;
42 printf("The error in the reading due to voltmeter 2
    = %0.2f%%", %error_2);
43
44 // Results
45 // The true voltage across resistor R_2 = 50 V
46 // The reading of the first voltmeter = 30 V
47 // The reading of the second voltmeter = 48.37 V
48 // The error in the reading due to voltmeter 1 = 40%
49 // The error in the reading due to voltmeter 2 = 3.26
    %
50

```

```
51 //The answers are varying as approximation is not
    done
```

---

**Scilab code Exa 4.6** To find the value of unknown resistor

```
1 // To find the value of unknown resistor
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4–6 in Page 64
7
8
9 clear; clc; close;
10
11 // Given data
12 S = 100; //Sensitivity of the voltmeter
13 // Three ranges of the voltmeter
14 V_1 = 50;
15 V_2 = 150;
16 V_3 = 300;
17 V_p = 4.65; //Reading of the meter on its 50–V scale
18 R_s = 100*10^3;
19 E = 100; //emf applied in volt
20 //Calculations
21 R_V = S * V_1;
22 R_p = ceil(V_p *R_s/ (E -V_p)); //R_p is the
  parallel resistance of R_x and R_v
23 R_x = R_p *R_V/ (R_V -R_p);
24 printf("The value of the unknown resistance R_x = %0
  .1e ohm", ceil(R_x));
25
```

```

26 //Result
27 // The value of the unknown resistance R_x = 2.0e
    +005 ohm

```

---

**Scilab code Exa 4.7** To find the scale error

```

1 // To find the scale error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-7 in Page 67
7
8
9 clear; clc; close;
10
11 // Given data
12 R_h = 2000; //The desired scale marking for the half
    scale deflection
13 E = 3; //The internal battery voltage in volt
14 I_fsd = 1 *(10^-3); //Current for full scale
    deflection in ampere
15 R_m = 50; //resistance of the basic movement in ohm
16
17 //Calculations
18 I_t = E / R_h; //Total battery current at FSD
19 I_2 = I_t - I_fsd; // Current through zero-adjust
    resistor R_2
20 R_2 = I_fsd * R_m/I_2;
21 R_p = R_2*R_m/(R_2 + R_m);
22 R_1 = R_h - R_p;
23 printf("(a) The value of R_1 and R_2 is")

```

```

24 printf("The value of zero-adjust resistor R2 =%0.1f
    ohm\n",R_2);
25 printf("The value of current-limiting resistor R1 =
    %0.1f ohm\n",R_1);
26
27 //At a 10% drop in battery voltage
28 E = 3- 0.3;
29 I_t = E / R_h; //Total battery current in A
30 I_2 = I_t - I_fsd; //Shunt current in A
31 R_2 = ceil(I_fsd * R_m/I_2);
32 R_p = R_2 *R_m/(R_2+R_m);
33 R_h = R_1 + R_p;
34 %error = (2000-2003.7)/2003.7*100;
35 printf("\n(b) The maximum value of R2 to compensate
    the drop in battery voltage = %d ohm\n",R_2);
36 printf("The true value of the half-scale mark on the
    meter is = %0.3f ohm\n",R_h);
37 printf("\n(c) The percentage error = %0.3f%%\n",
    %error);
38 disp('The negative sign indicates that the meter
    reading is low');
39
40 //Result
41 // (a) The value of R_1 and R_2 isThe value of zero
    -adjust resistor R2 =100.0 ohm
42 // The value of current-limiting resistor R1 =1966.7
    ohm
43
44 // (b) The maximum value of R2 to compensate the
    drop in battery voltage = 143 ohm
45 // The true value of the half-scale mark on the
    meter is = 2003.713 ohm
46
47 // (c) The percentage error = -0.185%
48
49 // The negative sign indicates that the meter
    reading is low

```

---

**Scilab code Exa 4.8** To find shunt and current limiting resistor

```
1 // To find shunt and current limiting resistor
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-8 in Page 70
7
8
9 clear; clc; close;
10
11 // Given data
12 I_fsd = 10*(10^-3); // current for full scale
   deflection in ampere
13 R_m = 5; //internal resistance of the d'Arsonval
   movement in ohm
14 E = 3; //Battery voltage in volt
15 R_h = 0.5; //The desired scale marking for the half
   scale deflection in ohm
16
17 //Calculations
18 I_m = 0.5 * I_fsd; // Current for half scale
   deflection of movement
19 E_m = I_m * R_m; //The voltage across movement
20 I_x = E_m / R_h; // Voltage across unknown resistor
   R_x
21 I_sh = I_x - I_m; //As I_x = I_sh + I_m
22 R_sh = E_m / I_sh;
23 I_t = I_m + I_sh + I_x; //The total battery current
24 R_1 = (E - E_m)/I_t;
```



```

25 printf("(a) The value of the shunt resistor , R_sh =
    %0.3f ohm\n",R_sh);
26 printf("(b) The value of the current limiting
    resistor , R_1 = %0.2f ohm",R_1);
27
28 //Result
29 // (a) The value of the shunt resistor , R_sh =
    0.556 ohm
30 // (b) The value of the current limiting resistor ,
    R_1 = 29.75 ohm

```

---

**Scilab code Exa 4.9** To find multiplier resistor

```

1 // To find multiplier resistor
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-9 in Page 79
7
8
9 clear; clc; close;
10
11 // Given data
12 R_m = 50; //Internal resistance of the movement in
    ohm
13 I_fsd = 1 *(10^-3); //current for full scale
    deflection in ampere
14 E_rms = 10; // AC voltage applied to input terminals
    in volt
15
16 //Calculation

```

```

17 disp('Assuming zero forward resistance and infinite
      reverse resistance');
18 E_dc = round(2 *sqrt(2)*E_rms/%pi);
19 R_t = E_dc / I_fsd; //Total circuit resistance
20 R_s = R_t - R_m; //Calculating multiplier resistor
21 printf("The value of the multiplier resistor , R_s =
      %d ohm",R_s);
22
23 //Result
24 // Assuming zero forward resistance and infinite
      reverse resistance
25 // The value of the multiplier resistor , R_s = 8950
      ohm

```

---

**Scilab code Exa 4.10** To find voltmeter sensitivity on AC range

```

1 // To find voltmeter sensitivity on AC range
2 // Modern Electronic Instrumentation And Measurement
      Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 4-10 in Page 81
7
8
9 clear; clc; close;
10
11 // Given data
12 R_m = 100; //Internal resistance of the movement in
      ohm
13 R_sh = 100;
14 I_fsd = 1*(10^-3); //current for full scale
      deflection

```

```

15 R_D1 = 400;
16 R_D2 = 400;
17 E_rms = 10; //AC range of the voltmeter
18
19 //Calculations
20 disp('Assuming infinite reverse resistance');
21 I_t = 2 * I_fsd;
22 E_dc = 0.45 * E_rms;
23 R_t = E_dc / I_t;
24 R_p = R_m * R_sh / (R_m + R_sh);
25 R_s = R_t - (R_D1 + R_p);
26 printf("(a) The value of the multiplier resistor
        required, R_s = %d ohm\n", R_s);
27 S = R_t / E_rms;
28 printf("(b) The sensitivity of the voltmeter on ac
        range, S = %d ohm/V", S);
29
30 //Result
31 // Assuming infinite reverse resistance
32 // (a) The value of the multiplier resistor
        required, R_s = 1800 ohm
33 // (b) The sensitivity of the voltmeter on ac range
        , S = 225 ohm/V

```

---

# Chapter 5

## Bridge Measurements

**Scilab code Exa 5.1** To find deflection caused by the given unbalance

```
1 // To find deflection caused by the given unbalance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-1 in Page 101
7
8
9 clear; clc; close;
10
11 // Given data
12 // Resistances of the 4 arms in ohm
13 R_1 = 1000;
14 R_2 = 100;
15 R_3 = 200;
16 R_4 = 2005;
17
18 E = 5; // battery EMF in volt
19 S_I = 10*(10^-3)/(10^-6); //Current sensitivity in m
   /A
```

```

20 R_g = 100; //Internal resistance of galvanometer in
    ohm
21
22 //Calculations
23
24 //Calculations are made wrt fig 5-3 in page 103
25 //Bridge balance occurs if arm BC has a resistance
    of 2000 ohm. The diagram shows arm BC has as a
    resistance of 2005 ohm
26
27 //To calculate the current in the galvanometer, the
    ckt is thevenised wrt terminals B and D.
28 //The potential from B to D, with the galvanometer
    removed is the Thevenin voltage
29
30 // E_TH = E_AD - E_AB
31
32 E_TH = E * ((R_2/(R_2+R_3)) - (R_1/ (R_1+R_4)));
33 R_TH = ((R_2 * R_3/(R_2+R_3)) + (R_1 * R_4/ (R_1+R_4
    )));
34
35 //When the galvanometer is now connected to the
    output terminals, The current through the
    galvanometer is
36
37 I_g = E_TH /(R_TH +R_g);
38 d = I_g * S_I;
39 printf("The deflection of the galvanometer = %0.2 f
    mm", (d*1000));
40
41 //Result
42 // The deflection of the galvanometer = 33.26 mm

```

---

**Scilab code Exa 5.2** To check the capability of detecting unbalance

```
1 // To check the capability of detecting unbalance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-2 in Page 102
7
8
9 clear; clc; close;
10
11 // Given data
12 // Resistances of the 4 arms in ohm
13 R_1 = 1000;
14 R_2 = 100;
15 R_3 = 200;
16 R_4 = 2005;
17
18 E = 5; // battery EMF in volt
19 S_I = 1*(10^-3)/(10^-6); //Current sensitivity in m/
   A
20 R_g = 500; //Internal resistance of galvanometer in
   ohm
21
22
23
24
25 //Calculations
26
27 //Calculations are made wrt fig 5-3 in page 103
28 //Bridge balance occurs if arm BC has a resistance
   of 2000 ohm. The diagram shows arm BC has as a
   resistance of 2005 ohm
29
30 //To calculate the current in the galvanometer, the
   ckt is thevenised wrt terminals B and D.
```

```

31 //The potential from B to D, with the galvanometer
    removed is the Thevenin voltage
32
33 // E_TH = E_AD - E_AB
34
35 E_TH = E * ((R_2/(R_2+R_3)) - (R_1/ (R_1+R_4)));
36 R_TH = ((R_2 * R_3/(R_2+R_3)) + (R_1 * R_4/ (R_1+R_4
    )));
37
38 //When the galvanometer is now connected to the
    output terminals, The current through the
    galvanometer is
39
40 I_g = E_TH /(R_TH +R_g);
41 d = I_g * S_I;
42 printf("The deflection of the galvanometer = %0.3f
    mm",d*1000);
43 disp('Given that galvanometer is capable of
    detecting a deflection of 1mm');
44 disp('Hence looking at the result ,it can be seen
    that this galvanometer produces a deflection that
    can be easily observed');
45
46 //Result
47 // The deflection of the galvanometer = 2.247 mm
48 // Given that galvanometer is capable of detecting a
    deflection of 1mm
49
50 // Hence looking at the result ,it can be seen that
    this galvanometer produces a deflection that can
    be easily observed

```

---

**Scilab code Exa 5.3** To find the unknown impedance

```

1 // To find the unknown impedance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-3 in Page 111
7
8
9 clear; clc; close;
10
11 // Given data
12 // The given polar forms in textbook is represented
   in rect form
13 Z_1 = 17.36482 +%i *98.48078;
14 Z_2 = 250;
15 Z_3 = 346.4102 +%i *200;
16
17 // Calculations
18 //The first condition for bridge balance is  $Z_1 \cdot Z_4 = Z_2 \cdot Z_3$ 
19 mod_Z_4 = (abs(Z_2) *abs(Z_3)/abs(Z_1));
20
21 //The second condition for bridge balance requires
   that sum of the phase angles of opposite arms be
   equal
22 theta_Z_4 = (atan(imag(Z_2),real(Z_2)) +atan(imag(
   Z_3),real(Z_3)) -atan(imag(Z_1),real(Z_1)))*180/
   %pi;
23
24 printf("The impedance of the unknown arm = %d ohm / _
   %d deg\n",mod_Z_4,theta_Z_4);
25 printf("Here the magnitude of impedance is 1000 and
   phase angle is 50 in degrees\n");
26 printf("The above value indicates that we are
   dealing with a capacitive element, possibly
   consisting of a series combination of a resistor
   and capacitance");

```



```

27
28 //Result
29 // The impedance of the unknown arm = 1000 ohm /-
    -50 deg
30 // Here the magnitude of impedance is 1000 and phase
    angle is 50 in degrees
31 // The above value indicates that we are dealing
    with a capacitive element, possibly consisting of
    a series combination of a resistor and
    capacitance

```

---

**Scilab code Exa 5.4** To find the unknown impedance

```

1 // To find the unknown impedance
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-4 in Page 112
7
8
9 clear; clc; close;
10
11 // Given data
12 // The notations are wrt to the figure 5-10 in page
    109
13
14 //Arm AB
15 R_1 = 450;
16 //Arm BC
17 R_2 = 300;
18 C = 0.265 *(10^-6);

```

```

19 //Arm DA
20 R_3 = 200;
21 L = 15.9*(10^-3);
22 f = 1000;
23
24 //Calculations
25 w = 2*%pi*f;
26 Z_1 = 450;
27 Z_2 = R_2 - %i *floor(1/(w*C));
28 Z_3 = R_3 + %i*ceil(w*L);
29
30 Z_4 = Z_1*Z_3/Z_2;
31 printf("The impedance of the unknown arm = %di ohm\n
", imag(Z_4));
32 printf("The result indicates that Z_4 is a pure
inductance with an inductive reactance of 150 ohm
at a frequency of 1 khz.\n")
33
34 L_ans = imag(Z_4)/w;
35 printf("The inductance present in the arm CD = %0.1
fm H", L_ans*1000);
36
37 //Result
38 // The impedance of the unknown arm = 150i ohm
39 // The result indicates that Z_4 is a pure
inductance with an inductive reactance of 150 ohm
at a frequency of 1 khz.
40 // The inductance present in the arm CD = 23.9m H

```

---

**Scilab code Exa 5.5** To balance the unbalanced bridge

```

1 // To balance the unbalanced bridge
2 // Modern Electronic Instrumentation And Measurement

```

```

Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 5-5 in Page 119
7
8
9 clear; clc; close;
10
11 // Given data
12 Z_1 = -1000*%i;
13 Z_2 = 500;
14 Z_3 = 1000;
15 Z_4 = 100+500*%i;
16
17 // The balance is not possible with this condition
    as theta_1+theta_4 will be slightly negative than
    theta_2+theta3
18 // Balance can be achieved by 2 methods:
19 disp('First option is to modify Z_1 so that its
    phase angle is decreased to less than 90deg by
    placing a resistor in parallel with the capacitor
    .')
20 // The resistance R_1 can be determined by the
    standard approach
21
22 // Calculations
23 Y_1 = Z_4/(Z_2*Z_3);
24 //Also ,
25 //  $Y_1 = (1/R) + \%i/1000;$ 
26 // equating both the equations and solving for R_1
27
28 R_1 = 1/(Y_1-(%i/1000 ));
29 printf("The value of the resistor R_1 in parallel
    with capacitor = %d ohm\n",R_1);
30
31 // It should be noted that the addition of R_1
    upsets the first balance condition as the

```

```

    magnitude of Z_1 is changed
32 // Hence the variable R_3 should be adjusted to
    compensate this effect
33
34 disp('The second option is to modify the phase angle
    of arm 2 or arm 3 by adding series capacitor');
35 Z_3_1 = Z_1 *Z_4/Z_2;
36 // substituting for the component values and solving
    for X_C yeilds
37
38 X_C = abs(1000- Z_3_1)/-%i;
39 printf("The value of the reactance of the capacitor
    used , X_C = %d ohm", imag(X_C));
40
41
42 //In this case the magnitude of the Z_3 is increased
    so that the first balance condition is changed
43 //A small adjustment of R_3 is necessary to restore
    balance
44
45 //Result
46 // First option is to modify Z_1 so that its phase
    angle is decreased to less than 90deg by placing
    a resistor in parallel with the capacitor.
47 // The value of the resistor R_1 in parallel with
    capacitor = 5000 ohm
48
49 // The second option is to modify the phase angle of
    arm 2 or arm 3 by adding series capacitor
50 // The value of the reactance of the capacitor used ,
    X_C = 200 ohm

```

---

# Chapter 6

## Electronic Instruments for Measuring Basic Parameters

Scilab code Exa 6.1 To find the form factor and error

```
1 // To find the form factor and error
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-1 in Page 131
7
8
9 clear; clc; close;
10
11 // Given data
12 //let
13 E_m = 10; //Let the peak amplitude of the square
   wave be 10V
14 T = 1; //Let the time period of the square wave be 1
   s
15
16 function y= f(t),y=(E_m)^2 ,endfunction
```

```

17 E_rms = sqrt(1/T * intg(0,T,f));
18 printf("(a) The rms value of the square wave = %d V
    \n",E_rms);
19
20 function x = ff(t),x =(E_m) ,endfunction
21 E_av = (2/T * intg(0,T/2,ff));
22 printf(" The average value of the square wave = %d
    V\n",E_av);
23
24 k = E_rms/E_av;
25 printf(" The form factor of the square wave =%d\n",
    k);
26
27 k_sine = 1.11;
28 k_square = 1;
29 %error = (k_sine - k_square)/k_square*100;
30 printf("(b) The percentage error in meter
    indication = %d %%",%error);
31
32 //Result
33 // (a) The rms value of the square wave = 10 V
34 // The average value of the square wave = 10 V
35 // The form factor of the square wave =1
36 // (b) The percentage error in meter indication =
    11 %

```

---

**Scilab code Exa 6.2** To find the form factor and error

```

1 // To find the form factor and error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009

```

```

5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-2 in Page 132
7
8
9 clear; clc; close;
10
11 // Given data
12 E_m = 150; //Let the peak amplitude of the sawtooth
    wave be 150V
13 T = 3; //Let the time period of the sawtooth wave be
    3s
14 // e = 50*t; As seen from the figure 6-7b in page
    131
15
16 // Calculations
17 function y= f(t),y=(50*t)^2 ,endfunction
18 E_rms = sqrt(1/T * intg(0,T,f));
19 printf("(a) The rms value of the sawtooth wave = %d
    V \n",E_rms);
20
21 function x = ff(t),x =(50*t) ,endfunction
22 E_av = (1/T * intg(0,T,ff));
23 printf("The average value of the sawtooth wave = %d
    V\n",E_av);
24
25 k_st = E_rms/E_av;
26 printf("The form factor of the sawtooth wave =%0.3f\
    n",k_st);
27
28 k_sine = 1.11;
29 r = k_sine/k_st;
30 printf("(b) The ratio of the two form factors = %0
    .3f\n",r);
31
32 printf("The meter indication is low by a factor of
    %0.3f\n",r);
33 %error = (r - 1)/1*100;
34 printf("The percentage error in meter indication =

```

```

    %0.1 f %%",%error);
35
36 // Result
37 // (a) The rms value of the sawtooth wave = 86 V
38 // The average value of the sawtooth wave = 75 V
39 // The form factor of the sawtooth wave =1.155
40 // (b) The ratio of the two form factors = 0.961
41 // The meter indication is low by a factor of 0.961
42 // The percentage error in meter indication = -3.9 %

```

---

**Scilab code Exa 6.3** To find the maximum time

```

1 // To find the maximum time
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-3 in Page 144
7
8
9 clear; clc; close;
10
11 // Given data
12 R = 100*(10^3); // Value of resistance in ohm
13 C = 0.1*(10^-6); // The value of integrating
   capacitor in F
14 V_ref = 2; // The reference voltage in V
15 V_out = 10; // The maximum limit of the output in V
16
17 // Calculations
18 T = R*C;
19 printf("The integrator time constant = %0.3 f s\n",T)

```



```

;
20 V_s = V_ref/T; //Unit is V/s
21 V = 1/V_s;
22 printf("Therefore the integrator output = %0.3f s/V"
,V)
23 disp('Therefore to integrate 10V');
24 T_max = V*V_out; //The max time the ref voltage can
    be integrated
25 printf("The time required = %0.4f s",T_max);
26
27 //Result
28 // The integrator time constant = 0.010 s
29 // Therefore the integrator output = 0.005 s/V
30 // Therefore to integrate 10V
31 // The time required = 0.0500 s

```

---

**Scilab code Exa 6.4** To find the distributed capacitance

```

1 // To find the distributed capacitance
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-4 in Page 162
7
8
9 clear; clc; close;
10
11 // Given data
12 // Frequency measurements in Hz
13 f_1 = 2*10^6;
14 f_2 = 4*10^6;

```

```

15 // Value of tuning capacitor in F
16 C_1 = 460*10^-12;
17 C_2 = 100*10^-12;
18
19 // Calculations
20 C_d = (C_1 - (4*C_2))/3;
21 printf("C_d = %0.0E F\n", C_d);
22 printf("i.e The value of the distributed capacitance
    = %d pF", (C_d*10^12));
23
24 // Result
25 // C_d = 2E-011 F
26 // i.e The value of the distributed capacitance = 20
    pF

```

---

**Scilab code Exa 6.5** To find the self capacitance

```

1 // To find the self capacitance
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-5 in Page 162
7
8
9 clear; clc; close;
10
11 // Given data
12 // Values of frequencies in Hz
13 f_1 = 2*10^6;
14 f_2 = 5*10^6;
15 // Values of the tuning capacitors in F

```

```

16 C_1 = 450*10^-12;
17 C_2 = 60*10^-12;
18
19 // Calculations
20
21 //Using the equation  $f = 1/(2*\%pi*\text{sqrt}(L*(C_2+C_d)))$ 
    ;
22 //Since  $f_2 = 2.5*f_1$ 
23 //Equating & reducing the equations
24 //  $1/(C_2 +C_d) = 6.25/(C_1 +C_d)$ 
25
26 C_d = (C_1 -6.25*C_2)/5.25
27 printf("C_d = %0.2E F\n",C_d);
28 printf("i.e The value of the distributed capacitance
    = %0.1 f pF" ,(C_d*10^12));
29
30 //Result
31 // C_d = 1.43E-011 F
32 // i.e The value of the distributed capacitance =
    14.3 pF

```

---

**Scilab code Exa 6.6** To find percentage error

```

1 // To find percentage error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-6 in Page 163
7
8
9 clear; clc; close;

```

```

10
11 // Given data
12 R = 10; //Resistance of the coil in ohm
13 f = 1*10^6; //The oscillator frequency in Hz
14 C = 65*10^-12; //The value of resonating capacitor
    in F
15 R_i = 0.02; //The value of the insertion resistor in
    ohm
16
17 // Calculations
18 w = 2*pi*f;
19 Q_e = 1/(w*C*R);
20 printf("The effective Q of the coil = %0.1f\n",Q_e);
21 Q_i = 1/(w*C*(R+R_i));
22 printf("The indicated Q of the coil = %0.1f\n",Q_i);
23 %error = (Q_e - Q_i)/Q_e*100;
24 printf("The percentage error is = %0.1f %%",%error);
25
26 //Result
27 // The effective Q of the coil = 244.9
28 // The indicated Q of the coil = 244.4
29 // The percentage error is = 0.2 %

```

---

**Scilab code Exa 6.7** To find percentage error

```

1 // To find percentage error
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 6-7 in Page 163
7

```

```

8
9 clear; clc; close;
10
11 // Given data
12 R = 0.1; //Resistance of the coil in ohm
13 f = 40*10^6; //The frequency at resonance in Hz
14 C = 135*10^-12; //The value of tuning capacitor in F
15 R_i = 0.02; //The value of the insertion resistor in
    ohm
16
17
18 // Calculations
19 w = 2*%pi*f;
20 Q_e = 1/(w*C*R);
21 printf("The effective Q of the coil = %d\n",ceil(Q_e
    ));
22 Q_i = 1/(w*C*(R+R_i));
23 printf("The indicated Q of the coil = %d\n",ceil(Q_i
    ));
24 %error = (Q_e - Q_i)/Q_e*100;
25 printf("The percentage error is = %d %%",ceil(%error
    ));
26
27 //Result
28 // The effective Q of the coil = 295
29 // The indicated Q of the coil = 246
30 // The percentage error is = 17 %

```

---

# Chapter 7

## Oscilloscopes

Scilab code Exa 7.1 To find minimum distance

```
1 // To find minimum distance
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 7-1 in Page 184
7
8
9 clear; clc; close;
10
11 // Given data
12 D = 4*10^-2; //Deflection on the screen in m
13 G = 100*100; // Deflection factor in V/m
14 E_a = 2000; //Accelarating potential in V
15
16 // Calculations
17 // wkt.  $L = 2*d*E_a/(G*I_d)$ 
18
19 //Also  $L/D = I_d / d$ 
20 //Therefore
```

```
21
22 L = sqrt(2*D*E_a/G);
23 printf("The distance from the deflection plates to
    the oscilloscope tube screen = %0.3f m",L);
24
25 //Result
26 // The distance from the deflection plates to the
    oscilloscope tube screen = 0.126 m
```

---

# Chapter 9

## Signal Analysis

Scilab code Exa 9.1 To find dynamic range of spectrum analyser

```
1 // To find dynamic range of spectrum analyser
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 9-1 in Page 277
7
8
9 clear; clc; close;
10
11 // Given data
12 I_p = +25; //Third order intercept point in dBm
13 MDS = -85; //noise level in dBm
14
15 //Calculations
16
17 dynamic_range = 2/3*(I_p -MDS);
18 printf("The dynamic range of the spectrum analyser =
   %d dB",dynamic_range);
19
```



```
20 //Result
21 // The dynamic range of the spectrum analyser = 73
    dB
```

---

**Scilab code Exa 9.2** To find minimum detectable signal

```
1 // To find minimum detectable signal
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 9-2 in Page 277
7
8
9 clear; clc; close;
10
11 // Given data
12 NF = 20; //Noise figure in dB
13 BW = 1*10^3; //Bandwidth in Hz
14
15 //Calculations
16 MDS = -114 +10* log10 ([BW/(1*10^6)]) +NF;
17 printf("The minimum detectable signal of the
    spectrum analyser = %d dBm",MDS);
18
19 //Result
20 // The minimum detectable signal of the spectrum
    analyser = -124 dBm
```

---

**Scilab code Exa 9.3** To find dynamic range and total frequency display

```
1 // To find dynamic range and total frequency display
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 9-3 in Page 285
7
8
9 clear; clc; close;
10
11 // Given data
12 T = 4; //Sample window in s
13 f_s = 20*10^3; // sample frequency in Hz
14 N = 10; //no of bits
15
16 //Calculations
17 f_r = 1/T;
18 f_h = f_s/2;
19 R_d = 20*log10(2^N);
20
21 printf("The ratio of the spectral calculation = %0.2
   f Hz\n",f_r);
22 printf("The maximum calculated spectral frequency =
   %d Hz\n",f_h);
23 printf("The dynamic range = %d dB",R_d);
24
25 //Result
26 // The ratio of the spectral calculation = 0.25 Hz
27 // The maximum calculated spectral frequency = 10000
```

28 // Hz  
The dynamic range = 60 dB

---

# Chapter 11

## Transducers as Input Elements to Instrumentation Systems

Scilab code Exa 11.1 To find change in resistance

```
1 // To find change in resistance
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 11-1 in Page 317
7
8
9 clear; clc; close;
10
11 // Given data
12 K =2; //Gauge factor
13 s = 1050; //stress in kg/cm^2
14 E = 2.1*10^6; //modulus of elasticity of steel in kg
  /cm^2
15
16 //Calculations
17 strain = s/E; //Hooke's law
```

```
18 change_in_resistance = K*strain;
19 %change = change_in_resistance * 100;
20
21 printf("The change in resistance = %0.3f\n",
        change_in_resistance);
22 printf("The percentage change in resistance = %0.1f
        %%", %change);
23
24 //Result
25 // The change in resistance = 0.001
26 // The percentage change in resistance = 0.1 %
```

---

# Chapter 12

## Analog and Digital Data Acquisition Systems

Scilab code Exa 12.1 To find percentage error

```
1 // To find percentage error
2 // Modern Electronic Instrumentation And Measurement
  Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 12-1 in Page 360
7
8
9 clear; clc; close;
10
11 // Given data
12 R = 1; //Resistance of the wire in ohm
13 R_L = 10*10^3; //Load resistance in ohm
14 I_supply = 50*10^-3; //power supply current in A
15 V_out = 1; //output of the amplifier in V
16
17 //Calculations
18 V_L = (V_out+(I_supply*R))*R_L/(2*R+R_L);
```

```
19 printf("The load voltage calculated = %0.2f\n",V_L);
20
21 %error = ceil((V_L -V_out)/V_L*100);
22 printf("The percentage error is about %d%%, which
        is unacceptable in most systems",%error);
23
24 //Result
25 // The load voltage calculated = 1.05
26 // The percentage error is about 5 %, which is
    unacceptable in most systems
```

---

# Chapter 14

## Fiber Optics Measurements

Scilab code Exa 14.1 To find acceptance angle and numerical aperture

```
1 // To find acceptance angle and numerical aperture
2 // Modern Electronic Instrumentation And Measurement
   Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-1 in Page 392
7
8
9 clear; clc; close;
10
11 // Given data
12 n_2 = 1.45; //Core index of refraction
13 n_1 = 1.47; //Cladding index of refraction
14
15 //Calculation
16 theta_c = acos(n_2/n_1);
17 theta_A = 2*asin(n_1*sin(theta_c));
18 NA = sqrt(n_1^2 -n_2^2);
19
20 printf("The critical angle of the fiber = %0.2 f
```



```

    degree\n",theta_c*180/%pi);
21 printf("The acceptance angle of the fiber = %0.2f
    degree\n",theta_A*180/%pi);
22 printf("The numerical aperture of the fiber = %0.3f
    ",NA);
23
24 //Result
25 // The critical angle of the fiber = 9.46 degree
26 // The acceptance angle of the fiber = 27.97 degree
27 // The numerical aperture of the fiber = 0.242

```

---

**Scilab code Exa 14.2** To find loss in the fiber

```

1 // To find loss in the fiber
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-2 in Page 393
7
8
9 clear; clc; close;
10
11 // Given data
12 NA_1 = 0.3; // numerical apertures of Source fiber
13 NA_2 = 0.242; //numerical apertures of receiving
    fiber
14
15 //Calculations
16 loss = 20*log10(NA_1/NA_2);
17 printf("The energy that is lost through the cladding
    of the receiving fiber = %0.2f dB",loss);

```

```

18
19 //Result
20 // The energy that is lost through the cladding of
    the receiving fiber = 1.87 dB

```

---

**Scilab code Exa 14.3** To find current developed in photodiode

```

1 // To find current developed in photodiode
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-3 in Page 395
7
8
9 clear; clc; close;
10
11 // Given data
12 h = 6.63*10^-34; //Planck's constant
13 c = 3*10^8; //Speed of light in m/s
14 lambda = 1.3*10^-6; // photon wavelength in m
15 QE = 0.82; //Quantum efficiency
16 p = 75*10^-6; //Power in W
17 q = 1.6*10^-19; //Charge of an electron
18
19 //Calculations
20 e = h*c/lambda;
21 N = p/e;
22 N_QE= QE*N;
23 I = N_QE*q;
24 printf("The current developed in a PIN photodiode =
    %0.2e A",I);

```

```
25
26 //Result
27 // The current developed in a PIN photodiode = 6.43e
    -005 A
```

---

**Scilab code Exa 14.4** To find elapsed time

```
1 // To find elapsed time
2 // Modern Electronic Instrumentation And Measurement
    Techniques
3 // By Albert D. Helfrick , William D. Cooper
4 // First Edition Second Impression , 2009
5 // Dorling Kindersly Pvt. Ltd. India
6 // Example 14-4 in Page 401
7
8
9 clear; clc; close;
10
11 // Given data
12 n = 1.55; //index of refraction
13 c = 3*10^8; //speed of light in m/s
14 d = 1.4*10^3; //Distance in m
15
16 //Calculations
17 v = c/n;
18 t = d/v;
19 printf("t = %0.1e s",t);
20 disp('Since twice the time to reach the break is
    required for the reflection to arrive at the
    reflectometer , ' )
21 printf("Hence the total elapsed time = %0.3e s",2*t)
    ;
22
```

```
23 //Result
24 // t = 7.2e-006 s
25 // Since twice the time to reach the break is
    required for the reflection to arrive at the
    reflectometer ,
26 // Hence the total elapsed time = 1.447e-005 s
```

---