

Scilab Textbook Companion for  
Basic Electronics  
by D. De<sup>1</sup>

Created by  
Adithya R.k  
B.E (pursuing)  
Electronics Engineering  
The National Institute Of Engineering  
College Teacher  
M.S Vijaykumar  
Cross-Checked by  
TechPassion

May 20, 2016

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Basic Electronics

**Author:** D. De

**Publisher:** Pearson Education India, New Delhi

**Edition:** 1

**Year:** 2010

**ISBN:** 9788131710685

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Semiconductor Fundamentals	5
2 Diode Fundamentals	32
3 Diode Circuits	65
4 BJT Fundamentals	89
5 BJT Circuits	102
6 Field Effect Transistor	111
7 FET Circuits	132
8 Special Semiconductor Devices	173

# List of Scilab Codes

Exa 1.1	Calculate wave vector carried by photon . . . . .	5
Exa 1.2	Calculate semiconductor band gap . . . . .	6
Exa 1.3	Calculate E k relation of conduction electrons . . . . .	7
Exa 1.4	Energies of electrons in conduction band . . . . .	8
Exa 1.5	Energies of electrons in conduction band . . . . .	9
Exa 1.6	Estimation of smallest k vector along x direction . . . . .	10
Exa 1.7	Energies of electrons in conduction band . . . . .	11
Exa 1.8	Find position of Fermi level . . . . .	12
Exa 1.9	Find Fermi level at room temperature . . . . .	13
Exa 1.10	Position of Fermi energy at 0K . . . . .	14
Exa 1.11	Time taken to reach Brillouin zone . . . . .	15
Exa 1.12	Calculate drift velocity . . . . .	15
Exa 1.13	Compute conductivity drift velocity current density . . . . .	17
Exa 1.14	Calculate drift velocity in copper conductor . . . . .	18
Exa 1.16	Calculate drift velocity in copper . . . . .	19
Exa 1.17	Equilibrium hole concentration in Si . . . . .	20
Exa 1.18	Time taken to reach Brillouin zone . . . . .	20
Exa 1.20	Electron hole concentration at minimum conductivity . . . . .	21
Exa 1.21	Position of Fermi level at room temperature . . . . .	22
Exa 1.22	Mobility of free electrons in Alluminium . . . . .	23
Exa 1.23	Percentage of increase in carrier concentration . . . . .	24
Exa 1.24	Previous problem calculated for intrinsic silicon . . . . .	25
Exa 1.25	Find drift velocity mobility conductivity . . . . .	26
Exa 1.26	Determine concentration of electrons and holes . . . . .	27
Exa 1.27	Concentration of holes and electrons . . . . .	28
Exa 1.28	To prove resistivity is 45 ohm cm . . . . .	29
Exa 1.29	Find conductivity of intrinsic germanium . . . . .	30
Exa 2.1	Calculate width of depletion layer . . . . .	32

Exa 2.2	Width of depletion zone at 300K . . . . .	33
Exa 2.3	Find thermal and barrier volatge . . . . .	34
Exa 2.4	Barrier potential for silicon junction . . . . .	35
Exa 2.5	Find depletion layer capacitance . . . . .	36
Exa 2.6	Compute decrease in capacitance . . . . .	37
Exa 2.7	Calculate barrier capacitance of Ge . . . . .	38
Exa 2.8	Calculate width of depletion layer . . . . .	39
Exa 2.10	Reverse saturation point of current . . . . .	40
Exa 2.12	Find reverse saturation current . . . . .	41
Exa 2.13	Ratio of reverse saturation current . . . . .	42
Exa 2.14	Calculate the current flowing . . . . .	43
Exa 2.15	Find voltage to be applied . . . . .	43
Exa 2.16	Find current when forward biased . . . . .	44
Exa 2.17	Calculate current and voltage . . . . .	45
Exa 2.18	Calculate forward currents for voltages . . . . .	46
Exa 2.19	Factor to be multiplied with reverse saturation current . . . . .	47
Exa 2.20	Leakage resistance shunting the diode . . . . .	48
Exa 2.21	Maximum reverse bias voltage to be maintained . . . . .	49
Exa 2.22	Factor to be multiplied with current . . . . .	50
Exa 2.24	Find the diffusion length . . . . .	51
Exa 2.25	Find static resistance . . . . .	52
Exa 2.26	Dynamic resistance in Forward Reverse direction . . . . .	53
Exa 2.27	Dynamic resistance at forward bias . . . . .	54
Exa 2.28	Maximum forward current forward resistance . . . . .	55
Exa 2.29	Height of potential energy barrier . . . . .	56
Exa 2.30	Dynamic resistance in forward reverse direction . . . . .	57
Exa 2.31	Maximum and minimum Zener currents . . . . .	58
Exa 2.32	Find the range for R . . . . .	59
Exa 2.33	Find breakdown voltage . . . . .	60
Exa 2.35	Calculate $V_z$ . . . . .	61
Exa 2.37	Find the ideality factor . . . . .	62
Exa 2.38	Temperature coefficient of Avalanche diode . . . . .	62
Exa 2.39	Limits for varying V . . . . .	63
Exa 3.1	Calculate the dc load current . . . . .	65
Exa 3.2	Find the diode currents . . . . .	66
Exa 3.3	Calculate break region . . . . .	68
Exa 3.4	Calculate the peak load current . . . . .	69
Exa 3.8	Calculate the dc load current . . . . .	70

Exa 3.10	Full scale reading of dc meter . . . . .	71
Exa 3.11	Find dc output Peak inverse voltage . . . . .	72
Exa 3.12	Determine maximum and average values of power . . .	73
Exa 3.13	Find maximum value of ac voltage . . . . .	74
Exa 3.14	Calculate ac voltage rectification efficiency . . . . .	74
Exa 3.15	Find current dc voltage voltage across load . . . . .	75
Exa 3.16	Estimate value of capacitance needed . . . . .	76
Exa 3.17	Calculate the ripple factor . . . . .	77
Exa 3.18	Find DC output voltage pulse frequency . . . . .	78
Exa 3.19	Find maximum dc voltage . . . . .	79
Exa 3.20	Calculate input voltage value of filter . . . . .	80
Exa 3.21	Calculate inductance for L section filter . . . . .	81
Exa 3.22	DC output voltage and ripple voltage . . . . .	82
Exa 3.23	Sketch steady state output . . . . .	83
Exa 3.24	Sketch output voltage $V_o$ . . . . .	83
Exa 3.25	Devise a circuit . . . . .	84
Exa 3.27	Find currents and voltages . . . . .	85
Exa 3.28	Find voltage across diode . . . . .	86
Exa 3.30	Calculate $R_{II\ max}$ . . . . .	87
Exa 4.1	Calculate Base and Collector Currents . . . . .	89
Exa 4.2	Calculate alpha using beta . . . . .	90
Exa 4.3	Collector Current in C E mode . . . . .	91
Exa 4.4	Calculate beta for the BJT . . . . .	92
Exa 4.5	To Compute Alpha Beta and Emitter Current . . . . .	92
Exa 4.6	Calculate alpha reverse and beta reverse . . . . .	93
Exa 4.7	Calculate Labeled Currents and Voltages . . . . .	94
Exa 4.8	Calculate labeled Voltages . . . . .	96
Exa 4.9	Calculating BJT parameters assuming $V_{be}$ . . . . .	97
Exa 4.10	Measurement of Circuit Voltage changes . . . . .	98
Exa 4.11	To Determine mode of operation of BJT . . . . .	99
Exa 5.1	Calculate BJT parameters using beta gain . . . . .	102
Exa 5.4	To establish Operating Point and Stability Factor . . .	104
Exa 5.5	Design Bias Circuit for given Stability Factor . . . . .	105
Exa 5.8	Calculate circuit parameters of a Emitter Follower . .	107
Exa 5.9	Design of an Emitter Follower . . . . .	109
Exa 6.1	Determine approximate drain source resistance . . . . .	111
Exa 6.2	Find $I_d$ and $V_{ds}$ . . . . .	112
Exa 6.3	Find the value of $R_d$ . . . . .	113

Exa 6.4	Find $i_d$ $V_{ds}$ slope of operation of JFET . . . . .	114
Exa 6.5	Find $i_d$ $V_{gs}$ $R_d$ $V_{ds}$ . . . . .	115
Exa 6.6	Determine $V_{gs}$ $I_d$ $V_{ds}$ operating region . . . . .	116
Exa 6.7	Determine $V_{gs}$ $I_d$ $V_{ds}$ . . . . .	117
Exa 6.8	Determine $R$ $I_{ds}$ $V_{gs}$ . . . . .	118
Exa 6.9	Find $I_d$ $V_{gs}$ $V_{ds}$ region of operation . . . . .	119
Exa 6.10	Find pinch off saturation voltage . . . . .	120
Exa 6.11	Determine drain source resistance . . . . .	121
Exa 6.12	Determine approximate $R_{ds}$ . . . . .	122
Exa 6.13	Find $V_{gs}$ operating region $I_d$ $R_d$ . . . . .	122
Exa 6.14	Find operating region $V_{gs}$ $V_{ds}$ $R_d$ . . . . .	123
Exa 6.15	Find $I_d$ when $V_{gs}$ equals 4V . . . . .	124
Exa 6.16	Determine $R_d$ . . . . .	125
Exa 6.17	Determine $R_d$ . . . . .	126
Exa 6.18	Find $I_d$ $V_{ds1}$ $V_{ds2}$ . . . . .	127
Exa 6.19	Find operating region $V_{gs}$ $V_{ds}$ $I_d$ . . . . .	128
Exa 6.20	Find $V_{gs}$ $I_d$ operating region . . . . .	129
Exa 6.21	Find operating region $V_{gs}$ $V_{ds}$ $I_d$ . . . . .	130
Exa 7.2	Find amplification . . . . .	132
Exa 7.3	Find amplification with 40k resistor instead . . . . .	133
Exa 7.6	Find gain if $v_2$ $v_1$ are zero . . . . .	133
Exa 7.11	Find voltage gain output impedance . . . . .	134
Exa 7.12	Find voltage gain $A_1$ and $A_2$ . . . . .	135
Exa 7.13	Determine $V_{gs}$ $I_d$ $V_{ds}$ $A_v$ . . . . .	136
Exa 7.14	Find the value of $R_1$ . . . . .	137
Exa 7.15	Find $V_o$ for given $V_i$ . . . . .	138
Exa 7.16	Calculate quiescent values of $I_d$ $V_{gs}$ $V_{ds}$ . . . . .	139
Exa 7.20	Calculate transconductance amplification factor . . . . .	140
Exa 7.21	Calculate dynamic resistance . . . . .	141
Exa 7.22	Calculate $R_d$ $g_m$ $\mu$ . . . . .	142
Exa 7.23	Find the value of $R_s$ . . . . .	143
Exa 7.24	Find voltage gain of amplifier . . . . .	143
Exa 7.25	Find pinch off voltage . . . . .	144
Exa 7.26	Calculate quiescent values of $I_d$ $V_{ds}$ $V_{gs}$ . . . . .	145
Exa 7.27	Find $I_d$ $V_{ds}$ $V_{gs}$ $A_v$ . . . . .	146
Exa 7.28	Calculate $A_v$ $Z_o$ $Z_i$ . . . . .	147
Exa 7.29	Calculate $V_o$ $V_i$ . . . . .	148
Exa 7.30	Calculate $A_v$ $Z_o$ . . . . .	149



Exa 7.31	Calculate $V_{gsq}$ $g_m$ $R_s$ $V_{dsq}$ $R_l$ . . . . .	150
Exa 7.32	Calculate $Z_o$ for $r_d$ equals 50 k ohms . . . . .	151
Exa 7.33	Find voltage gain Current gain ratio . . . . .	152
Exa 7.34	Determine $Z_o$ draw small signal model . . . . .	153
Exa 7.35	Find values of $R_2$ $V_{dd}$ $V_{ds}$ . . . . .	153
Exa 7.36	Equation for drain current . . . . .	155
Exa 7.37	Find $V_{gs}$ $V_p$ . . . . .	156
Exa 7.38	Find the values of $R_s$ and $R_d$ . . . . .	156
Exa 7.39	Find the value of $R_s$ . . . . .	157
Exa 7.40	Calculate voltage gain $A_v$ . . . . .	158
Exa 7.41	Calculate voltage amplification in circuit . . . . .	159
Exa 7.43	Find the value of $R_s$ . . . . .	160
Exa 7.44	Calculate value of $I_d$ $V_{gs}$ $V_{ds}$ . . . . .	161
Exa 7.45	Calculate input admittance . . . . .	162
Exa 7.47	Calculate gain and frequency . . . . .	164
Exa 7.48	Calculate the values of $I_d$ $V_{gs}$ $V_{ds}$ . . . . .	165
Exa 7.52	Calculate complex voltage gain Input admittance . . . . .	166
Exa 7.54	Find the maximum transconductance . . . . .	167
Exa 7.55	Evaluate $V_{ds}$ and $R_d$ . . . . .	168
Exa 7.56	Verify FET operation in pinch off region . . . . .	169
Exa 7.57	Calculate voltage gain $A_v$ . . . . .	170
Exa 7.59	Design a source follower . . . . .	171
Exa 8.1	Calculate the Gate Source Resistance . . . . .	173
Exa 8.2	Firing angle of Thyristor . . . . .	174
Exa 8.3	Calculate width of Gating pulse . . . . .	175
Exa 8.4	To calculate required Gate source Resistance . . . . .	176
Exa 8.5	To calculate series Resistance across SCR . . . . .	177
Exa 8.6	To determine critical value of $dv$ by $dt$ . . . . .	178
Exa 8.7	Calculate surge current and $I_2t$ ratings . . . . .	179
Exa 8.8	Max and Min firing delays . . . . .	180
Exa 8.10	Design of Triggering Circuit for a UJT . . . . .	181
Exa 8.11	To determine Emitter source voltage of UJT . . . . .	182

# Chapter 1

## Semiconductor Fundamentals

Scilab code Exa 1.1 Calculate wave vector carried by photon

```
1 // Calculate wave vector carried by photon
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-1 in page 7
7
8 clear; clc; close;
9
10 // Given data
11 c=3*10^8; // Speed of light in m/s
12 h=6.64*10^-34; // Planks constant in Js
13 E_photon=2*1.6*10^-19; // Energy of photon in J
14
15 // Calculations
16 lambda=(c*h)/E_photon;
17 k=(2*%pi/lambda);
18
19 printf("The wavelenght of a 2.0eV photon = %0.3e m\n",lambda);
20 printf("The magnitude of k vector = %0.2e m^-1",k);
```

```

21
22 // Results
23 // The wavelength of a 2.0 eV photon is 6225
    Angstrom
24 // The magnitude of k-vector is  $1.01 * 10^7 \text{ m}^{-1}$ 

```

---

**Scilab code Exa 1.2** Calculate semiconductor band gap

```

1 // Calculate semiconductor band gap
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-2 in page 7
7
8 clear; clc; close;
9
10 // Data given
11 lambda=0.5*10^-6; // Wavelength of emitted light in
    m
12 c=3*10^8; // Speed of light in vacuum in m/s
13 h=1.05*10^-34; // Constant of calculation
14
15 // Calculation
16 E_g= (2*pi*h*c)/lambda;
17 A= E_g*10^19/1.6;
18
19 printf("The material band gap has to be %0.3f eV",A)
    ;
20
21 // Result
22 //The material band gap is 2.474 eV
23 // Semiconductors like C,BN,GaN,SiC meet this

```

**Scilab code Exa 1.3** Calculate E k relation of conduction electrons

```
1 // Calculate E-k relation of conduction electrons
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-3 in page 20
7
8 clear; clc; close;
9
10 // Data given
11 m_c=0.1*0.91*10^-30; // Effective mass of conduction
    electron in kg
12 k=0.3*10^10; // Wave vector in /m
13 h=1.05*10^-34; // Constant of calculation in Js
14
15 // Calculation
16 E= (h^2*k^2)/(2*m_c);
17 A= E/(1.6*10^-19);
18
19 printf("Energy of conduction electrons = %0.1f eV",A
    );
20
21 // Result
22 //Energy of the conduction electrons in vertically
    upward direction is 3.4 eV
```

---

#### Scilab code Exa 1.4 Energies of electrons in conduction band

```
1 // Energies of electrons in conduction band
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-4 in page 21
7
8 clear; clc; close;
9
10 // Data given
11 k=0.01*10^10; // k-vector value /m
12 h=1.05*10^-34; // Constant of calculation Js
13 m_0=0.91*10^-30; // Mass of conduction electron Kg
14 m_c1=0.067*m_0; // Effective mass of GaAs conduction
    electron Kg
15 m_c2=0.01*m_0; // Effective mass if InAs conduction
    electron Kg
16
17 // Calculation
18 E_1=(h^2*(9*k^2))/(2*m_c1);
19 A_1=(E_1)/(1.6*10^-19);
20
21 printf("(a)Energy of conduction electron in GaAs =
    %0.2e eV\n",A_1);
22
23 E_2=(h^2*(9*k^2))/(2*m_c2);
24 A_2=(E_2)/(1.6*10^-19);
25
26 printf("(b)Energy of conduction electron in InAs =
    %0.3e eV",A_2);
```

```

27
28 // Results
29 // (a) Energy of conduction electron in GaAs is 50.9
    meV
30 // (b) Energy of conduction electron in InAs is
    340.7 meV

```

---

### Scilab code Exa 1.5 Energies of electrons in conduction band

```

1 // Energies of electrons in conduction band
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-5 in page 21
7
8 clear; clc; close;
9
10 // Data given
11 h=1.05*10^-34; // Constant of calculation Js
12 k=0.1,0.1,0,0; // Values of k-vector
13 m_c=0.067*0.091*10^-30; // Effective mass of
    conduction electron
14
15 // Calculation
16 E=(h^2*(((0.1*10^10)^2)+((0.1*10^10)^2)))/(2*m_c);
17 A= E/(1.6*10^-19);
18
19 printf("Energy of conduction electron is %0.3f eV",A
    );
20
21 // Result
22 // Energy of conduction electron in the vertically

```

```
    upward direction = 11.302 eV
23 // The non parabolic E-k dispersion relation is more
    appropriate here
```

---

**Scilab code Exa 1.6** Estimation of smallest k vector along x direction

```
1 // Estimation of smallest k-vector along x-direction
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-6 in page 21
7
8 clear; clc; close;
9
10 // Data given
11 x=1; // x-coordiante
12 y=1; // y-coordinate
13 z=1; // z-coordinate
14 E=0.3*1.6*10^-19; // Energy separation in eV
15 m_c=0.067*0.91*10^-30; // Effective mass of
    conduction electron in kg
16 h=1.05*10^-34; // Constant of calculation in Js
17
18 // Calculation
19 k_x=(2*m_c*E)/(3*h^2);
20 A=sqrt(k_x);
21
22 printf("K vector along (111) direction is %0.1e m^-1
    ",A);
23
24 // Result
25 //Value of k-vector along (111) direction is
```

```

    4.2*10^8 m^-1
26 //Parabolic expression has been used to compute the
    k-vector

```

---

**Scilab code Exa 1.7** Energies of electrons in conduction band

```

1 // Energies of electrons in conduction band
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-7 in page 22
7
8 clear; clc; close;
9
10 // Data given
11 k=0.01*10^10; // k-vector value /m
12 h=1.05*10^-34; // Constant of calculation Js
13 m_0=0.91*10^-30; // Mass of conduction electron Kg
14 m_c1=0.067*m_0; // Effective mass of GaAs conduction
    electron Kg
15 m_c2=0.01*m_0; // Effective mass if InAs conduction
    electron Kg
16
17 // Calculation
18 E_1=(h^2*(9*k^2))/(2*m_c1);
19 A_1=(E_1)/(1.6*10^-19);
20
21 printf("(a)Energy of conduction electron in GaAs =
    %0.2e eV\n",A_1);
22
23 E_2=(h^2*(9*k^2))/(2*m_c2);
24 A_2=(E_2)/(1.6*10^-19);

```



```

25
26 printf("(b)Energy of conduction electron in InAs =
    %0.3e eV",A_2);
27
28 // Results
29 // (a) Energy of conduction electron in GaAs is 50.9
    meV
30 // (b) Energy of conduction electron in InAs is
    340.7 meV

```

---

#### Scilab code Exa 1.8 Find position of Fermi level

```

1 // Find position of Fermi level
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-8 in page 33
7
8 clear; clc; close;
9
10 // Data given
11 n_0=6*10^17; // Electron concentration in the
    conduction band /cm^3
12 k_bT=0.026; // Expressed in eV at room temperature
13 N_c=4.45*10^17; // Constant of Calculation /cm^3
14
15 // Calculation
16 E_f=k_bT*log(n_0/N_c);
17 A=E_f*10^3;
18
19 printf("Position of Fermi level is %0.2f meV",A);
20

```

```

21 // Result
22 // Position of Fermi level is 7.77 meV
23 // Intrinsic carrier density is lesser than dopant
    density
24 // Hence semiconductor is non-degenerate

```

---

**Scilab code Exa 1.9** Find Fermi level at room temperature

```

1 // Find Fermi level at room temperature
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-9 in page 34
7
8 clear; clc; close;
9
10 // Data given
11 k=1; // Assumed constant
12 m_e=2*k; // Effective mass of an electron in Kg
13 m_h=k; // Effective mass of only heavy hole in Kg
14 k_bT=0.026; // Expressed in eV at room temperature
15
16 // Calculation
17 E_f=(3/4)*0.026*log(m_e/m_h);
18 printf("E_f = ((-E_g/2) - %0.3f) eV\n",E_f);
19 printf("Thus Fermi level is below center of
    forbidden gap by 0.014 eV");
20
21 // Result
22 // Fermi level in the intrinsic semiconductor is ((-
    E_g/2) - 0.014) eV

```

---

**Scilab code Exa 1.10** Position of Fermi energy at 0K

```
1 //Position of Fermi energy at 0K
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-10 in page 34
7
8 clear; clc; close;
9
10 // Data given
11 h=1.5*10^-34; // Constant of calculation in Js
12 m_c=0.067*0.91*10^-30; // Effective mass of
    conduction electron in Kg
13 n_0=10^24; // Electron concentration at 0K /m^3
14
15 // Calculation
16 E_f= ((h^2*(3*pi^2*n_0)^(2/3))/(2*m_c));
17 A=E_f/(1.6*10^-19);
18
19 printf("Position of Fermi level at 0K is %0.4f eV",A
    );
20
21 // Result
22 // Fermi energy at 0K as measured from edge of
    conduction band is 0.11 eV
23 // Fermi energy is placed 0.11 eV above the edge of
    conduction band
24 // Fermi energy is within the conduction band
```

---

**Scilab code Exa 1.11** Time taken to reach Brillouin zone

```
1 // Time taken to reach Brillouin zone
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-11 in page 46
7
8 clear; clc; close;
9
10 // Data given
11 h=1.05*10^-34; // Constant of calculation in Js
12 Kb=1.112*10^8; // Wave vector at Brillouin zone
    along x-axis /cm
13 E_0=10^4; // External electric field applied in V/cm
14 e=1.6*10^-19; // Charge on an electron in C
15
16 // Calculation
17 tou=(h*Kb)/(e*E_0);
18
19 printf("Time taken by electron is %0.3e s",tou);
20
21 // Result
22 // Time taken by electron to reach Brillouin zone is
    7.297 ps
```

---

**Scilab code Exa 1.12** Calculate drift velocity

```

1 // Calculate drift velocity
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1–12 in page 46
7
8 clear; clc; close;
9
10 // Data given
11 m_c=0.067*0.91*10^-30; // Effective electron mass in
    Kg
12 e=1.6*10^-19; // Charge on an electron in C
13 E_0=10^5; // External electric field in KV/m
14 tou1=10^-13; // First Brillouin zone time in s
15 tou2=10^-12; // Second Brillouin zone time in s
16 tou3=10^-11; // Third Brillouin zone time in s
17
18 // Calculation
19 v_01=(e*tou1*E_0)/m_c;
20 v_02=(e*tou2*E_0)/m_c;
21 v_03=(e*tou3*E_0)/m_c;
22
23 printf("(a) Drift velocity in first case is %0.2e m/s
    \n",v_01);
24 printf("(b) Drift velocity in second case is %0.2e m/
    s\n",v_02);
25 printf("(c) Drift velocity in third case is %0.2e m/s
    ",v_03);
26
27 // Result
28 // (a) Drift velocity in first case is 2.62*10^4 cm/
    s
29 // (b) Drift velocity in second case is 2.62*10^5 cm
    /s
30 // (c) Drift velocity in third case is 2.62*10^6 cm/
    s

```

---

**Scilab code Exa 1.13** Compute conductivity drift velocity current density

```
1 // Compute conductivity , drift velocity , current
  density
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-13 in page 47
7
8 clear; clc; close;
9
10 // Data given
11 mu=35.2*10^-4; // Mobility of electrons in m^2/Vs
12 n_0=7.87*10^28; // Number of free electrons per
  cubic meter
13 e=1.6*10^-19; // Charge on an electron in C
14 E_0=30*10^2; // External electric field applied in V
  /m
15
16 // Calculation
17 sigma=n_0*e*mu;
18 printf("(a) Mobility = %0.1e m^2/Vs\n",mu);
19 printf("Conductivity of the specimen is %0.2e s/m\n\
  n",sigma);
20 V_0=mu*E_0;
21 J=sigma*E_0;
22 printf("(b) Electric field Eo = %0.0e V/m\n",E_0);
23 printf("Drift velocity of free electrons is %0.2f m/
  s\n",V_0);
24 printf("Current density is %0.2e A/meter^3",J);
25
```

```
26 // Result
27 // (a) Conductivity of specimen is  $4.43 \times 10^7$  s/m
28 // (b) Drift velocity of free electrons is 10.56 m/s
29 // (c) Current density is  $13.3 \times 10^{10}$  A/meter cube
```

---

**Scilab code Exa 1.14** Calculate drift velocity in copper conductor

```
1 // Calculate drift velocity in copper conductor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-14 in page 47
7
8 clear; clc; close;
9
10 // Data given
11 A=10^-5; // Cross sectional area in m^2
12 I=100; // Current flowing in A
13 n_0=8.5*10^28; // Free electron concentration of
    copper per cubic meter
14 e=1.6*10^-19; // Charge on an electron in C
15
16 // Calculation
17 V_d=I/(n_0*A*e);
18
19 printf("The drift velocity in copper is %0.3e m/s",
    V_d);
20
21 // Result
22 // Drift velocity in copper is  $7.353 \times 10^{-4}$  m/s
```

---

**Scilab code Exa 1.16** Calculate drift velocity in copper

```
1 // Calculate drift velocity in copper
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-16 in page 47
7
8 clear; clc; close;
9
10 // Data given
11 tau=10^-14; // Relaxation time in s
12 m_c=0.02*9.1*10^-31; // Effective mass of electron
    in Kg
13 E_0=0.1; // Electric field across conductor in V/m
14 e=1.6*10^-19; // Charge on an electron in C
15
16 // Calculation
17 V_0=(e*E_0*tau)/m_c;
18
19 printf("The drift velocity of electrons in copper is
    %0.3f m/s",V_0);
20
21 // Result
22 // Drift velocity of electrons in copper is 0.009 m/
    s
```

---



**Scilab code Exa 1.17** Equilibrium hole concentration in Si

```
1 // Equilibrium hole concentration in Si
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-17 in page 48
7
8 clear; clc; close;
9
10 // Data given
11 n_0=10^17; // Free electron concentration /cm^3
12 n_i=1.5*10^10; // Constant of calculation
13 // Calculation
14 p_0= n_i^2/n_0;
15
16 printf("Equilibrium hole concentration is %0.2e cm
    ^-3",p_0);
17
18 // Result
19 // Equilibrium hole concentration in Si sample is
    2.25*10^3 cm^-3
```

---

**Scilab code Exa 1.18** Time taken to reach Brillouin zone

```
1 // Time taken to reach Brillouin zone
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-18 in page 48
7
```

```

8 clear; clc; close;
9
10 // Data given
11 h=1.05*10^-34; // Constant of calculation in Js
12 kB=1.112*10^8; // Brillouin zone edge along x-axis
13 e=1.6*10^-19; // Charge on an electron in C
14 E_0=10^4; // External electric field in V/m
15
16 // Calculation
17 tou=(h*kB)/(e*E_0);
18 printf("Time taken to reach Brillouin zone is %0.3e
      s", tou);
19
20 // Result
21 // Time taken by GaAs electron to reach Brillouin
      zone is 7.298 ps

```

---

**Scilab code Exa 1.20** Electron hole concentration at minimum conductivity

```

1 // Electron, hole concentration at minimum
      conductivity
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-20 in page 49
7
8 clear; clc; close;
9
10 // Data given
11 mu_n=1350; // Mobility of electrons in cm^2/Vs
12 mu_p=450; // Movility of holes in cm^2/Vs

```

```

13 n_i=1.5*10^10; // Intrinsic carrier concentration /
    cm^3
14
15 // Calculation\
16 //Minimum conductivity of Si when slightly p-type
    has been proved in text
17 //Thus the electron and hole concentrations are
    derived as below
18 n_0=n_i*sqrt(mu_p/mu_n);
19 p_0=n_i*sqrt(mu_n/mu_p);
20
21 printf("(a) Electron concentration is %0.2e cm^-3\n",
    n_0);
22 printf("(b) Hole concentration is %0.2e cm^-3",p_0);
23
24 // Result
25 // (a) Electron concentration is 8.66*10^9 cm^-3
26 // (b) Hole concentration is 2.6*10^10 cm^-3

```

---

**Scilab code Exa 1.21** Position of Fermi level at room temperature

```

1 // Position of Fermi level at room temperature
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-22 in page 50
7
8 clear; clc; close;
9
10 // Data given
11 C_Ge=4.41*10^22; // Concentration of Ge atom /cm^3
12 N_D=4.41*10^15; // Number of free donor atoms

```

```

13 N_C=8.87*10^18; // Number of conduction electrons
    assuming full ionization
14 K_BT=0.026; // Measured in eV at room temperature
15
16 // Calculation
17 E_F=K_BT*log(N_D/N_C);
18
19 printf("Position of fermi level is %0.4f",E_F);
20
21 // Result
22 // Position of Fermi level from edge of conduction
    band is -0.1977
23 // Thus E_F is below E_C

```

---

**Scilab code Exa 1.22** Mobility of free electrons in Alluminium

```

1 // Mobility of free electrons in Alluminium
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-22 in page 50
7
8 clear; clc; close;
9
10 // Data given
11 n_0=18*10^28; // Derived from the given formula in
    textbook
12 rho=3.44*10^-6; // Resistivity in ohm-cm
13 e=1.6*10^-19; // Charge on an electron in C
14
15 // Calculation
16 mu=10^2/(n_0*e*rho);

```

```

17
18 printf("Mobility of free electrons is %0.0e m^2/V-s"
    ,mu);
19
20 // Result
21 // Mobility of free electrons in Alluminium is 10^-3
    m^2/V-s

```

---

**Scilab code Exa 1.23** Percentage of increase in carrier concentration

```

1 // Percentage of increase in carrier concentration
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-23 in page 51
7
8 clear; clc; close;
9
10 // Data given
11 kT=0.026; // Value at T=300K
12 T=300; // Room temperature in K
13 dT=1/300; // Rate of change of temperature
14 E_g=0.785; // Band gap energy in germanium in eV
15
16 // Calculation
17 dni=((1.5+(E_g/(2*kT)))*dT)*100;
18
19 printf("Rise in intrinsic carrier concentration is
    %0.1f percent/degree",dni);
20
21 // Result
22 // Percentage rise in intrinsic carrier

```

concentration is 5.5 %/degree

---

**Scilab code Exa 1.24** Previous problem calculated for intrinsic silicon

```
1 // Previous problem calculated for intrinsic silicon
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-24 in page 51
7
8 clear; clc; close;
9
10 // Data given
11 kT=0.026; // Value at T=300K
12 T=300; // Room temperature in K
13 dT=1/300; // Rate of change of temperature
14 E_g=1.21; // Band gap energy in silicon in eV
15
16 // Calculation
17 dni=((1.5+(E_g/(2*kT)))*dT)*100;
18
19 printf("Rise in intrinsic carrier concentration is
    %0.1f percent/degree",dni);
20
21 // Result
22 // Percentage rise in intrinsic carrier
    concentration is 8.3 %/degree
```

---

**Scilab code Exa 1.25** Find drift velocity mobility conductivity

```
1 // Find drift velocity ,mobility ,conductivity
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-25 in page 51
7
8 clear; clc; close;
9
10 // Data given
11 A=0.835*10^-6; // Cross section of wire in m^2
12 J=2.4*10^6; // Current density in A/m^2
13 n_0=8.4*10^27; // Concentration of electrons in
    copper in electrons/m^3
14 e=1.6*10^-19; // Charge on an electron in C
15 ohm=0.0214; // Resistance per meter
16 E_0=2*ohm; // Electric field in V/m
17
18 // Calculations
19 v_0=(J)/(n_0*e);
20 printf("(a)The drift velocity is %0.2e m/s\n",v_0);
21 mu=v_0/E_0;
22 printf("(b)The mobility of electrons is %0.2e m^2/V-
    s\n",mu);
23 sigma=(n_0*10*e*mu);
24 printf("(c)Therefore the conductivity is %0.2e /ohm-
    m",sigma);
25
26 // Result
27 // (a) The drift velocity is 1.78*10^-3 m/s
28 // (b) Mobility in this case is 4.16*10^-2 m^2/V-s
29 // (c) Conductivity is 5.61*10^8 1/ohm-m
```

---

**Scilab code Exa 1.26** Determine concentration of electrons and holes

```
1 // Determine concentration of electrons and holes
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-26 in page 52
7
8 clear; clc; close;
9
10 // Data given
11 N_D=2*10^14; // Number of donor atoms in atoms/cm^2
12 N_A=3*10^14; // Number of acceptor atoms in atoms/cm
    ^2
13 ni=2.5*10^19; // number of intrinsic atoms in atoms/
    cm^2
14
15 // Calculation
16 p_0=(0.5*10^14)+sqrt(0.25*10^28 + 6.25*10^26);
17 n_0=-(0.5*10^14)+sqrt(0.25*10^28 + 6.25*10^26);
18 printf("(a) Concentration of free electrons is %0.3e
    cm^-3\n", n_0);
19 printf("(b) Concentration of holes is %0.3e cm^-3\n",
    p_0);
20 printf("since p_0>n_0 the sample is p-type\n");
21 printf("When N_A=N_D=10^15,\n n_0=p_0 from the
    neutrality equation\n");
22 printf("Thus the germanium sample in this question
    is intrinsic by compensation");
23 printf("When N_D=10^16,\n");
24 p_0=(6.25*10^26)/10^16;
```



```

25 printf("(c) p_0=%0.2e cm^-3\n", p_0);
26 printf("Since n_0>p_0, germanium sample in this case
    is n-type");
27
28 // Result
29 // (a) Number of free electrons are 0.058*10^14 cm
    ^-3
30 // (b) Number of holes are 1.058*10^14 cm^-3
31 // Semiconductor can be made intrinsic without
    doping or by equal doping

```

---

**Scilab code Exa 1.27** Concentration of holes and electrons

```

1 // Concentration of holes and electrons
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-27 in page 52
7
8 clear; clc; close;
9
10 // Data given
11 sigma=100; // Conductivity of p-type germanium
12 e=1.6*10^-19; // Charge on an electron in eV
13 mu_p=1800; // Mobility of holes in cm^2/Vs
14 ni=2.5*10^13; // Number of intrinsic atoms in
    germanium
15 mu_n=1300; // Mobility of electrons in cm^2/Vs
16 sigma1=0.1; // Conductivity in n-type silicon in /
    ohm-cm
17 ni1=1.5*10^10; // Number of intrinsic atoms in
    silicon

```

```

18 P_p=3.47*10^17; // Constant of calculation
19
20 // Calculation
21 printf("For Germanium:\n");
22 p_0=sigma/(e*mu_p);
23 n_0=(ni^2)/P_p;
24 printf("(a) Concentration of holes is %0.2e cm^-3\n",
        p_0);
25 printf("(b) Concentration of electrons is %0.2e m^-3\n",
        n_0);
26 printf("For Silicon:\n");
27 n_0=sigma1/(e*mu_n);
28 p_0=(ni1^2)/(4.81*10^14);
29 printf("(c) Concentration of electrons is %0.2e cm
        ^-3\n",n_0);
30 printf("(d) Concentration of holes is %0.2e m^-3",p_0
        );
31
32 // Result
33 // (a) For Ge, Hole conc. = 3.47*10^17 cm^-3,
        Electron conc. = 1.8*10^15 m^-3
34 // (b) For Si, Hole conc. = 4.68*10^5 cm^-3, Electron
        conc. = 4.81*10^14 cm^-3

```

---

**Scilab code Exa 1.28** To prove resistivity is 45 ohm cm

```

1 // To prove, resistivity is 45 ohm-cm
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-28 in page 53
7

```

```

8 clear; clc; close;
9
10 // Data given
11 ni=2.5*10^13; // Intrinsic concentration /cm^3
12 mu=5600; // Sum of mobilities of holes and electrons
13 e=1.6*10^-19; // Charge on an electron in C
14
15 // Calculation
16 sigma=e*ni*mu;
17 printf("Conductivity of germanium is %0.3f (s/cm)
    ^-1\n",sigma);
18 rho=1/sigma;
19 printf("Therefore resistivity is %0.1f ohm-cm",rho);
20
21 // Result
22 // Conductivity of germanium = 0.0232 (s/cm)^-1
23 // Resistivity = 44.6 ohm-cm

```

---

**Scilab code Exa 1.29** Find conductivity of intrinsic germanium

```

1 // Find conductivity of intrinsic germanium
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 1-29 in page 53
7
8 clear; clc; close;
9
10 // Data given
11 ni=2.5*10^13; // Intrinsic concentration /cm^3
12 e=1.6*10^-19; // Charge on an electron in C
13 mu_n=3800; // Mobility of electrons in cm^2/Vs

```

```

14 mu_p=1800; // Mobility of holes in cm^2/Vs
15 N_D=4.41*10^15; // Concentration of donor atoms in
    Ge /cm^3
16
17 // Calculation
18 sigma=(ni*e)*(mu_n+mu_p);
19 printf("(a) Intrinsic conductivity=%0.4f s/cm\n",
    sigma);
20 p_0=(ni^2)/N_D;
21 printf("p_0=%0.2e /cm^3\n",p_0);
22 sigma1=N_D*e*mu_n;
23 printf("(b) Since n_0>p_0, Conductivity=%0.2f s/cm\n"
    ,sigma1);
24 n_0=(ni^2)/N_D;
25 printf("With given acceptor impurity,\nn_0=%0.2e /cm
    ^3\n",n_0);
26 sigma2=N_D*e*mu_p;
27 printf("(c) Since p_0>n_0, Conductivity=%0.2f s/cm",
    sigma2);
28
29 // Result
30 // (a) Conductivity in first case is 0.0224 s/cm
31 // (b) Conductivity in second case is 2.68 s/cm
32 // (c) Conductivity in third case is 1.27 s/cm

```

---

# Chapter 2

## Diode Fundamentals

Scilab code Exa 2.1 Calculate width of depletion layer

```
1 // Calculate height of potential-energy barrier
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-1 in page 77
7
8 clear; clc; close;
9
10 // Given data
11 rho1=1.5; // Resistivity of p-side of Ge diode in
           ohm-cm
12 rho2=1; // Resistivity of n-side of Ge diode in ohm-
           cm
13 e=1.6*10^-19; // Charge on an electron in C
14 mu_p=1800; // Mobility of holes
15 mu_n=3800; // Mobility of electrons
16
17 // Calculation
18 N_A=1/(rho1*e*mu_p);
19 N_D=1/(rho2*e*mu_n);
```

```

20 printf("(a) rho = 2 ohm-cm\n");
21 printf("N_A=%0.2e /cm^3\n",N_A);
22 printf("N_D=%0.2e /cm^3\n",N_D);
23 printf("The height of the potential energy barrier
    is:\n");
24 V_0=0.026*log((N_A*N_D)/(2.5*10^13)^2);
25 printf("V_0=%0.3f eV\n\n",V_0);
26 printf("(b)For silicon:\n");
27 N_A1=1/(rho1*e*500);
28 N_D1=1/(2*e*1300);
29 printf("N_A=%0.2e /cm^3\n",N_A1);
30 printf("N_D=%0.2e /cm^3\n",N_D1);
31 V_01=0.026*log((N_A1*N_D1)/(1.5*10^10)^2);
32 printf("The height of the potential energy barrier
    is:\n");
33 printf("V_0=%0.3f eV",V_01);
34
35 // Result
36 // (a) For Ge, V_0 = 0.226 eV
37 // (b) For Si, V_0 = 0.655 eV

```

---

### Scilab code Exa 2.2 Width of depletion zone at 300K

```

1 // Width of depletion zone at 300K
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-2 in page 83
7
8 clear; clc; close;
9
10 // Given data

```

```

11 N_d=10^16; // Donor concentration /cm^3
12 N_a=5*10^18; // Acceptor concentration /cm^3
13 ni=1.5*10^10; // Intrinsic concentration /cm^3
14 e=1.6*10^-19; // Charge on an electron in C
15 epsln=11.8*8.85*10^-14; // Constant of calculation
16
17 // Calculation
18 V_0=0.0259*log((N_d*N_a)/(ni^2));
19 printf("The height of the barrier energy is %0.2f V\
n",V_0);
20
21 W=sqrt(2*((epsln*V_0)/(e)*((1/N_a)+(1/N_d))));
22 printf("Width of depletion zone is %0.3e cm",W);
23
24 // Result
25 // The height of the barrier energy is 0.86 V
26 // Width of depletion zone in n-type Si is
3.354*10^-5 cm

```

---

### Scilab code Exa 2.3 Find thermal and barrier volatge

```

1 // Find thermal and barrier volatge
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-3 in page 84
7
8 clear; clc; close;
9
10 // Given data
11 T=303; // Temperature in K
12 ni=1.5*10^16; // Intrinsic concentration /cm^3

```

```

13 e=1.6*10^-19; // Charge on an electron in C
14 k_BT=1.38*10^-23; // Measured in eV at 303K
15 N_A=10^22; // Acceptor concentration /cm^3
16 N_D=1.2*10^21; // Donor concentration /cm^3
17
18 // Calculation
19 V_T=(k_BT*T)/e;
20 printf("Thermal voltage = %0.2e V\n",V_T);
21 ni1=ni^2;
22 printf("ni^2 = %0.3e\n",ni1);
23 V_0=V_T*log((N_A*N_D)/(ni1));
24 printf("Barrier voltage = %0.3f V",V_0);
25
26 // Result
27 // Thermal voltage = 26.1 mV
28 // Barrier voltage = 0.635 V

```

---

#### Scilab code Exa 2.4 Barrier potential for silicon junction

```

1 // Barrier potential for silicon junction
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-4 in page 84
7
8 clear; clc; close;
9
10 // Given data
11 t=[70 0]; // Declaring the variables
12 t1=25; // Given temperature in K
13
14 // Calculation

```



```

15 alp=[1 2];
16 for i=1:2
17 delta_V=-0.002*(t(i)-t1);
18 Vb=0.7+delta_V;
19 printf("(%.0f) delta_V at %d degrees = %.2f V\n",
        alp(i),t(i),delta_V);
20 printf("Thus the barrier potential at %d degress =
        %.2f V\n",t(i),Vb);
21 end
22
23 // Result
24 // (a) Barrier potential at 70 degrees is 0.61 V
25 // (b) Barrier potential at 0 degrees is 0.75 V

```

---

### Scilab code Exa 2.5 Find depletion layer capacitance

```

1 // Find depletion layer capacitance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-5 in page 86
7
8 clear; clc; close;
9
10 // Given data
11 epsln=12/(36*%pi*10^11); // Constant for Si in F/cm
12 A=8.11058*10^-1; // Cross sectional area in m^2
13 mu_p=500; // Mobility of holes
14 e=1.6*10^-19; // Charge on an electron in C
15 V_j=4.9; // Junction potential in V
16
17 // Calculation

```

```

18 printf("(a)We have C_t/A = sqrt((e*epsln)/2)*sqrt(Na
    /Vj)\n");
19 K=sqrt((e*epsln)/2);
20 printf("sqrt((e*epsln)/2) = %0.2e\n",K);
21 printf("Hence C_t = %0.2e * sqrt(Na/Vj) F/cm^2\n",K)
    ;
22 K1=K*10^12;
23 printf("Or C_t = %0.2e * sqrt(Na/Vj) pF/cm^2\n",K1);
24 N_A=1/(3*mu_p*e);
25 C_T=(2.9*10^-4)*sqrt(N_A/V_j)*(8.14*10^-3);
26 printf("(b)The depletion layer capacitance = %0.2f
    pF",C_T);
27
28 // Result
29 // (a) The expression for depletion layer
    capacitance is proved
30 // (b) The depletion layer capacitance in silicon is
    68.84 pF

```

---

### Scilab code Exa 2.6 Compute decrease in capacitance

```

1 // Compute decrease in capacitance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-6 in page 87
7
8 clear; clc; close;
9
10 // Given data
11 V=6.5; // Increased bias voltage in V
12 lambda=(20*sqrt(5)); // Constant of calculation

```

```

13
14 // Calculation
15 C_T=lambda/sqrt(V);
16
17 printf("Transition capacitance of abrupt junction at
        6.5 V = %0.2f pF\n",C_T);
18 printf("This corresponds to a decrease of 2.46 pF");
19
20 // Result
21 // Transition capacitance = 17.54 pF
22 // This corresponds to a decrease of 2.46 pF

```

---

**Scilab code Exa 2.7** Calculate barrier capacitance of Ge

```

1 // Calculate barrier capacitance of Ge
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-7 in page 87
7
8 clear; clc; close;
9
10 // Given data
11 epsln=1.41*10^-12; // Dielectric constant
12 A=0.0225; // Junction area in cm^2
13 W=2*10^-4; // Space-charge thickness in cm
14
15 // Calculation
16 C_T=epsln*(A/W);
17
18 printf("Barrier capacitance = %0.2e F",C_T);
19

```

```
20 // Result
21 // Barrier capacitance = 159.3 pF
```

---

**Scilab code Exa 2.8** Calculate width of depletion layer

```
1 // Calculate width of depletion layer
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-8 in page 87
7
8 clear; clc; close;
9
10 // Given data
11 V=[10.2 0.3 0.1]; // Applied voltages in V
12 epsln=16; // Constant of calculation
13 A=1*10^-6; // Cross sectional area in m^2
14
15 // Calculation
16 alp=[1 2 3];
17 for i=1:3
18     W=sqrt((V(i)*10^-10)/14.3);
19     printf("(%.0f)Width of depletion layer for %.2
20           f V = %.2e mu-m\n\n",alp(i),V(i),W);
21 end
22 W=[8.5 1.45];
23 alp1=[1 2];
24 for j=1:2
25     C_T=(epsln*10^-9)/(36*%pi*W(j));
26     printf("(%.0f)Space charge capacitance for %.2
27           f mu-m = %.2e F\n\n",alp(j),W(j),C_T);
28 end
```

```

27
28 // Result
29 // Widths of depletion layer are:
30 // (a) 8.5 mu-m
31 // (b) 1.45 mu-m
32 // (c) 0.84 mu-m respectively
33 // Space charge capacitances are:
34 // (a) 16.65 pF
35 // (b) 97.6 pF respectively

```

---

#### Scilab code Exa 2.10 Reverse saturation point of current

```

1 // Reverse saturation point of current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-10 in page 93
7
8 clear; clc; close;
9
10 // Given data
11 b=2.11; // Constant
12 Lsigma=3*10^-4; // Constant
13 Vt=0.026; // Threshold voltage in V
14 A=1.5*10^-6; // Cross sectional area in mm^2
15 sigma_i=2.24; // Intrinsic conductivity /ohm-cm
16
17 // Calculation
18 I_0=((A*Vt*b*sigma_i^2)/(1+b)^2)*((1/0.45)+(1/0.015))
19 ;
20 printf("Reverse saturation point of current is %0.2e

```

```

    A", I_0);
21
22 // Result
23 // Reverse saturation point of current is 2.94  $\mu\text{A}$ 

```

---

**Scilab code Exa 2.12** Find reverse saturation current

```

1 // Find reverse saturation current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-12 in page 94
7
8 clear; clc; close;
9
10 // Given data
11 A=5*10^-2; // Cross sectional area in  $\text{m}^2$ 
12 b=2.6; // Constant of calculation
13 Lsigma=10^-4; // Constant of calculation
14 sigmai=4.32*10^-6; // Intrinsic conductivity in ohm/
    cm
15 Vt=0.026; // Constant in eV
16
17 // Calculation
18 I_0=A*Vt*(b/(1+b)^2)*sigmai^2*(2*10^4);
19
20 printf("The reverse saturation current = %0.2e A",
    I_0);
21
22 // Result
23 // The reverse saturation current = 97.25 pA

```

---

### Scilab code Exa 2.13 Ratio of reverse saturation current

```
1 // Ratio of reverse saturation current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-13 in page 95
7
8 clear; clc; close;
9
10 // Given data
11 b1=2.6; // Constant of calculation
12 b2=2.11; // Constant of calculation
13 sigma1=4.32*10^-6; // Intrinsic conductivity for Si
    /ohm-cm
14 sigma2=2.24*10^-2; // Intrinsic conductivity for Ge
    /ohm-cm
15
16 // Calculation
17 printf("For Si:\n");
18 Y1=((b1*sigma1^2)/(1+b1)^2)*(2*10^4);
19 printf("Y_Si = %0.2e ohm-cm^2\n",Y1);
20 printf("For Ge:\n");
21 Y2=((b2*sigma2^2)/(1+b2)^2)*(2*10^2);
22 printf("Y_Ge = %0.2e ohm-cm^2\n",Y2);
23 Y=Y2/Y1;
24 printf("Therefore the ratio is %0.1e",Y);
25
26
27 // Result
28 // Y_Si = 7.49*10^-8 ohm-cm^2
```

```
29 // Y_Ge = 2.189*10^-2 ohm-cm^2
30 // Ratio = 0.29*10^6
```

---

**Scilab code Exa 2.14** Calculate the current flowing

```
1 // Calculate the current flowing
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-14 in page 96
7
8 clear; clc; close;
9
10 // Given data
11 I_0=9*10^-7; // Current flowing in A
12 V=0.1; // Applied forward bias in V
13
14 // Calculation
15 I=I_0*(exp(40*V)-1);
16 printf("Current flowing through diode = %0.2e A",I);
17
18 // Result
19 // Current flowing through the diode under forward
    bias = 48.15 mu-A
```

---

**Scilab code Exa 2.15** Find voltage to be applied

```
1 // Find voltage to be applied
```



```

2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-15 in page 96
7
8 clear; clc; close;
9
10 // Given data
11 J_0=500*10^-3; // Saturation current density in mA/m
    ^2
12 J=10^5; // Forward current density in A/m^2
13 e=1.6*10^-19; // Charge on an electron in C
14 etaK=1.38*10^-23; // Constant of calculation
15 T=350; // Temperature in K
16
17 // Calculation
18 A=2.303*log10(2*10^5);
19 V=(A*etaK*T)/e;
20
21 printf("Voltage to be applied = %0.4f V",V);
22
23 // Result
24 // The voltage to be applied = 0.3685 V

```

---

**Scilab code Exa 2.16** Find current when forward biased

```

1 // Find current when forward biased
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-16 in page 97

```

```

7
8 clear; clc; close;
9
10 // Given data
11 k_T=1.38*10^-23; // Constant of calculation
12 T=293; // Temperature in K
13 I_s=1.5*10^-13; // Saturation current in A
14 e=1.6*10^-19; // Charge on an electron in C
15 V=0.55; // Forward bias voltage in V
16
17 // Calculation
18 printf("At T = 20 degrees:\n");
19 V_T=(k_T*T)/e;
20 I=I_s*(exp(V/0.02527)-1);
21 printf("V_T = %0.4f V\n",V_T);
22 printf("(a)I = %0.3e A\n",I);
23 printf("At T = 100 degrees:\n");
24 V_T=(k_T*373)/e;
25 printf("V_T = %0.4f V\n",V_T);
26 printf("I_s doubles 8 times ie I_s = 256. Therefore,\n
n");
27 I=1.5*256*10^-13*(exp(0.55/0.032)-1);
28 printf("(b)I = %0.3f A",I);
29
30 // Result
31 // (a) At T=20 degrees , I = 4.251*10^-4 A
32 // (b) At T=100 degrees , I = 0.001 A

```

---

**Scilab code Exa 2.17** Calculate current and voltage

```

1 // Calculate current and voltage
2 // Basic Electronics
3 // By Debashis De

```

```

4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-17 in page 97
7
8 clear; clc; close;
9
10 // Given data
11 I1=2*10^-6; // Saturation current in A
12 I2=4*10^-6; // Saturation current in A
13 Vz=100; // Breakdown voltages are equal
14 eta=2; // Constant of calculation
15
16 // Calculation
17 printf("At V=90V, none of the diodes will break down.
        I is determined by the diode with the smallest
        I_0\n");
18 printf("Thus for D1, I = 1 mu-A and for D2, I = -1 mu-
        A\n");
19 V2=eta*0.026*log(1-(I1/I2));
20 printf("(a) V2 = %0.1e V\n", V2);
21 printf("(b) V1 = -89.964 V");
22
23 // Result
24 // (a) V2 = -36 mV
25 // (b) V1 = -89.964 V

```

---

**Scilab code Exa 2.18** Calculate forward currents for voltages

```

1 // Calculate forward currents for voltages
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India

```

```

6 // Example 2-18 in page 98
7
8 clear; clc; close;
9
10 // Given data
11 Vt=0.026; // Thermal voltage at room temperature in
    eV
12 V=[0.1 0.2 0.3]; // Given voltages in V
13
14 // Calculation
15 V1=0.026*-2.3;
16 printf("(a)V=%0.2 f V\n",V1);
17 R=(exp(1.92)-1)/(exp(-1.92)-1);
18 printf("(b)Ration of forward bias current to reverse
    bias current=%0.2 f\n",R);
19 printf("(c):\n")
20 for i=1:3
21     I=15*(exp(V(i)/0.026)-1);
22     printf("I = %0.3 e A\n",I);
23 end
24
25 // Result
26 // (a) V = -0.060 V
27 // (b) Ratio = -6.83
28 // (c) Forward currents = 0.687 mA, 32.86 mA and
    1.539 A respectively

```

---

**Scilab code Exa 2.19** Factor to be multiplied with reverse saturation current

```

1 // Factor to be multiplied with reverse saturation
    current
2 // Basic Electronics

```

```

3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-19 in page 98
7
8 clear; clc; close;
9
10 // Given data
11 T1=25; // Initial temperature for Ge in degree
    celcius
12 T2=70; // Final temperature for Ge in degree celcius
13 T_2=150; // Final temperature for Si in degree
    celcius
14
15 // Calculation
16 printf("(a)Let the reverse saturation current for Ge
    at 25 degrees be Io(25)\n");
17 A=2^((T2-T1)/10);
18 printf("The factor to be multiplied when temperature
    is raised to 70 degrees is %0.0f\n",A);
19 printf("Therefore , Io(70) = %0.0f*Io(25)\n\n",A);
20 printf("(b)Let the reverse saturation current for Si
    at 25 degrees be Io(25)\n");
21 A1=2^((T_2-T1)/10);
22 printf("The factor to be multiplied when temperature
    is raised to 150 degrees is %0.0f\n",A1);
23 printf("Therefore , Io(150) = %0.0f*Io(25)",A1);
24
25 // Results
26 // (a) Io(70) = 23*Io(25)
27 // (b) Io(150) = 5793*Io(25)

```

---

**Scilab code Exa 2.20** Leakage resistance shunting the diode

```

1 // Leakage resistance shunting the diode
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-20 in page 99
7
8 clear; clc; close;
9
10 // Given data
11 // Kirchoff's law has been applied and equations
    solved to get final expression
12
13 // Calculation
14 I_R=(0.08*5*10^-6)/0.15;
15 R=10/I_R;
16 printf("Leakage resistance = %0.2e Mohm",R);
17
18 // Result
19 // Leakage resistance shunting the diode = 3.75 Mohm

```

---

**Scilab code Exa 2.21** Maximum reverse bias voltage to be maintained

```

1 // Maximum reverse-bias voltage to be maintained
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-21 in page 99
7
8 clear; clc; close;
9
10 // Given data

```

```

11 Rt=0.15*10^-3; // Thermal resistance of mechanical
    contact between diode and surroundings in mW/
    degree celcius
12 T1=25; // Ambient temperature in degree celcius
13 T2=35; // Rise in ambient temperature in degree
    celcius
14 I_25=5*10^-6; // Reverse saturation current at 25
    degrees in mu-A
15
16 // Calculation
17 Po=Rt*(T2-T1);
18 printf("P_out = %0.2e mW\n",Po);
19 printf("We know that reverse saturation current
    doubles for every 10 degree rise in temperature\n
    ");
20 I_35=2*I_25;
21 V=Po/I_35;
22 printf("Thus the maximum reverse bias voltage to be
    maintained is %0.0f V",V);
23
24 // Result
25 // Maximum reverse bias voltage that can be
    maintained across diode is 150V

```

---

**Scilab code Exa 2.22** Factor to be multiplied with current

```

1 // Factor to be multiplied with current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-22 in page 100
7

```

```

8  clear; clc; close;
9
10 // Given data
11 V_T=0.0364; // Thermal voltage in V
12 // Simplified expression for I has been derived
13 I_25=0.01; // Current at 25 degrees in mA
14 I_150=2.42; // Current at 150 degrees in mA
15
16 // Calculation
17 printf("At 150 degrees:\n");
18 I=5792*(exp(0.4/0.0728)-1);
19 printf("I = %0.0f * Io(25)\n",I);
20 printf("At 25 degrees:\n");
21 I=exp(0.4/0.0514)-1;
22 printf("I = %0.0f * Io(25)\n",I);
23 R=I_150/I_25;
24 printf("Factor to be multiplied with current = %0.0f
    ",R);
25
26 // Result
27 // When temp is increased from 25–150 degrees ,
    current has to be multiplied by 242

```

---

**Scilab code Exa 2.24** Find the diffusion length

```

1 // Find the diffusion length
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2–24 in page 101
7
8 clear; clc; close;

```



```

9
10 // Given data
11 C_D=1.5*10^-6; // Diffusion capacitance in F
12 D_p=13; // Constant
13 eta=2; // Constant
14 V_t=0.026; // Voltage at room temperature in V
15 I=1*10^-3; // Current in mA
16
17 // Calculation
18 L_p=sqrt((C_D*D_p*eta*V_t)/I);
19
20 printf(" Diffusion length = %0.3e m",L_p);
21
22 // Result
23 // Diffusion length = 31.84*10^-3 m

```

---

#### Scilab code Exa 2.25 Find static resistance

```

1 // Find static resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-25 in page 103
7
8 clear; clc; close;
9
10 // Given data
11 I_0=20*10^-6; // Current in micro A
12 V_F=0.2; // Forward voltage in V
13
14 // Calculation
15 I=I_0*(exp(40*V_F)-1);

```

```

16 r_dc=(0.0343/(80*10^-6))*exp(0.2/0.0343);
17
18 printf("Forward current through the diode = %0.3e A\
n",I);
19 printf("Static resistance = %0.3e ohm",r_dc);
20
21 // Result
22 // Forward current = 59.599 mA
23 // Static resistance = 0.146 Mohm

```

---

**Scilab code Exa 2.26** Dynamic resistance in Forward Reverse direction

```

1 // Dynamic resistance in forward ,reverse direction
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-26 in page 103
7
8 clear; clc; close;
9
10 // Given data
11 T=398; // Temperature in K
12 I_0=80*10^-6; // Current in micro A
13 eta=1; // Constant
14 V_F=[-0.2 0.2]; // Forward voltages in Volts
15 V_T=0.0343; // Thermal voltage in volts
16
17 // Calculation
18 alp=[1 2];
19 for i=1:2
20     R_ac=(V_T/I_0)*exp(V_F(i)/V_T);
21     printf("(%0.0f)Dynamic resistance = %0.3e ohm\n"

```

```

        ,alp(i),R_ac);
22 end
23
24 // Result
25 // (a) Dynamic resistance in forward direction =
    1.258 ohm
26 // (b) Dynamic resistance in reverse direction =
    0.146 Mohm

```

---

**Scilab code Exa 2.27** Dynamic resistance at forward bias

```

1 // Dynamic resistance at forward bias
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-27 in page 103
7
8 clear; clc; close;
9
10 // Given data
11 k_BT=25.86*10^-3; // Constant
12 I_0=1.5*10^-6; // Current in microA
13 V=0.15; // Forward bias voltage in volts
14 V_T=0.02586; // Thermal voltage in volts
15
16 // Calculation
17 R_ac=k_BT/(I_0*exp(V/V_T));
18
19 printf("Dynamic resistance = %0.2f W",R_ac);
20
21 // Result
22 // Dynamic resistance at forward bias = 52.17 W

```

---

**Scilab code Exa 2.28** Maximum forward current forward resistance

```
1 // Maximum forward current ,forward resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-28 in page 104
7
8 clear; clc; close;
9
10 // Given data
11 P_max=2.5; // Maximum power in watt
12 V_f=0.9; // Forward voltage in V
13 I_max=2.2; // Maximum current in A
14
15 // Calculation
16 I_fmax=P_max/V_f;
17 R_f=P_max/(I_max)^2;
18
19 printf("(a)Maximum forward current = %0.2f A\n",
        I_fmax);
20 printf("(b)Forward diode resistance = %0.3f ohm",R_f
        );
21
22 // Result
23 // Forward current = 2.78 A
24 // Diode forward resistance = 0.517 ohm
```

---

### Scilab code Exa 2.29 Height of potential energy barrier

```
1 // Height of potential energy barrier
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-29 in page 104
7
8 clear; clc; close;
9
10 // Given data
11 rho1=2; // Resistivity of p-side in ohm-cm
12 rho2=1; // Resistivity of n-side in ohm-cm
13 e=1.6*10^-19; // Charge on an electron in C
14
15 // Calculation
16 N_A1=1/(rho1*e*1800);
17 N_D1=1/(rho2*e*3800);
18 N_A2=1/(rho1*e*500);
19 N_D2=1/(rho2*e*1300);
20 V_01=0.026*log((N_A1*N_D1)/(2.5*10^13)^2);
21 V_02=0.026*log((N_A2*N_D2)/(1.5*10^10)^2);
22 printf("(a) For Ge:\n");
23 printf("N_A = %0.2e /cm^3\nN_D = %0.2e /cm^3\n", N_A1
    , N_D1);
24 printf("Therefore barrier potential energy for Ge =
    %0.2f eV\n\n", V_01);
25 printf("(b) For Si:\n");
26 printf("N_A = %0.2e /cm^3\nN_D = %0.2e /cm^3\n", N_A2
    , N_D2);
27 printf("Therefore barrier potential energy for Si =
```

```

    %0.3 f eV",V_02);
28
29 // Result
30 // (a) Height of barrier potential energy for Ge =
    0.22 eV
31 // (b) Height of barrier potential energy for Si =
    0.667 eV

```

---

**Scilab code Exa 2.30** Dynamic resistance in forward reverse direction

```

1 // Dynamic resistance in forward ,reverse direction
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-30 in page 105
7
8 clear; clc; close;
9
10 // Given data
11 V_T=0.0343; // Thermal voltage at 398K in V
12 eta=1; // Constant for Ge
13
14 // Calculation
15 // Final expression for r derived after
    differentiating w.r.t V
16 r1=((35*10^-6)/(34.3*10^-3))*exp(5.83);
17 A1=1/r1;
18 r2=3.185*10^-6
19 A2=1/r2;
20
21 printf("(a)Dynamic resistance in forward direction =
    %0.3 f ohm\n",A1);

```

```

22 printf("(b)Dynamic resistance in reverse direction =
    %0.3e ohm",A2);
23
24 // Result
25 // (a) Resistance in forward direction = 2.879 ohm
26 // (b) Resistance in reverse direction = 0.314 Mohm

```

---

### Scilab code Exa 2.31 Maximum and minimum Zener currents

```

1 // Maximum and minimum Zener currents
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-31 in page 110
7
8 clear; clc; close;
9
10 // Given data
11 V_z=10; // Zener voltage in V
12 R_s=1*10^3; // Shunt resistance in K-ohm
13 R_l=10*10^3; // Load resistance in K-ohm
14 Vi_max=40; // Maximum input voltage in V
15 Vi_min=25; // Minimum input voltage in V
16
17 // Calculation
18 I_zmax=((Vi_max-V_z)/1000)-(5*10^-3);
19 I_zmin=((Vi_min-V_z)/R_s)-(5*10^-3);
20
21 printf("Maximum value of zener current = %0.2e A\n",
    I_zmax);
22 printf("Minimum value of zener current = %0.2e A",
    I_zmin);

```

```
23
24 // Result
25 // Maximum zener current = 25 mA
26 // Minimum zener current = 10 mA
```

---

**Scilab code Exa 2.32** Find the range for R

```
1 // Find the range for R
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-32 in page 110
7
8 clear; clc; close;
9
10 // Given data
11 P=250; // Maximum power dissipation in mW
12 V=15; // Supply voltage in V
13
14 // Caluclation
15 I=(250*10^-3)/5;
16 printf("Maximum permissible current = %0.3e A\n",I);
17 printf("10 percent of 50mA = 5mA\n");
18 I1=I-(5*10^-3);
19 printf("Maximum current through diode to maintain
    constant voltage = %0.1e A",I1);
20
21 // Result
22 // Maximum current to maintain constant voltage = 45
    mA
```

---



**Scilab code Exa 2.33** Find breakdown voltage

```
1 // Find breakdown voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-33 in page 111
7
8 clear; clc; close;
9
10 // Given data
11 E=1.5*10^5; // Electric field in V/cm
12 epsln=11.9*8.854*10^-16; // Constant
13 e=1.6*10^-19; // Charge on an electron in eV
14 N_d=2*10^15; // Doping concentration /cm^3
15
16 // Calculation
17 W=(E*epsln)/(e*N_d);
18 V_b=(W*E)/2;
19
20 printf("Width of depletion region = %0.3e m\n",W);
21 printf("Therefore ,breakdown voltage Vbr = %0.4f V",
    V_b);
22
23 // Result
24 // Breakdown voltage = 0.3704 V
```

---

### Scilab code Exa 2.35 Calculate Vz

```
1 // Calculate Vz
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-35 in page 112
7
8 clear; clc; close;
9
10 // Given data
11 // (a) Proof of  $V_z=51/\sigma_i$  has been given
12  $\sigma_i=1/45$ ; // Intrinsic conductivity in 1/ohm-cm
13  $\sigma_p=1/3.9$ ; // Conductivity of p material in 1/ohm-
    cm
14  $I_0=6*10^{-6}$ ; // Current in microA
15
16 // Calculation
17  $Vz1=51/\sigma_i$ ;
18  $Vz2=51/\sigma_p$ ;
19  $I=I_0*(\exp(100/26)-1)$ ;
20 printf("(a) Proof of  $V_z=51/\sigma_p$  has been given\n")
    ;
21 printf("(b) When material is intrinsic ,  $V_z = \%0.3f$  V\
    n", Vz1);
22 printf("(c) When resistivity drops ,  $V_z = \%0.1f$  V\n",
    Vz2);
23 printf("(d)  $I = \%0.3e$  A", I);
24
25 // Result
26 // (a)  $V_z = 51/\sigma_p$  is proved
27 // (b)  $Vz1 = 2300V$ 
28 // (c)  $Vz2 = 198.9V$ 
29 // (d)  $I = 0.274$  mA
```

---

**Scilab code Exa 2.37** Find the ideality factor

```
1 // Find the ideality factor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-37 in page 112
7
8 clear; clc; close;
9
10 // Given data
11 I1=0.5*10^-3; // Diode current in mA at 340mV
12 I2=15*10^-3; // Diode current in mA at 465mV
13 kb_T=5*10^-3; // Constant in mV
14
15 // Calculation
16 // After simplifying the current equation we get an
    expression for eta
17 eta=5/(2.303*log10(30));
18
19 printf("Ideality factor = %0.2f",eta);
20
21 // Result
22 // Ideality factor = 1.47
```

---

**Scilab code Exa 2.38** Temperature coefficient of Avalanche diode

```

1 // Temperature coefficient of Avalanche diode
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-38 in page 113
7
8 clear; clc; close;
9
10 // Given data
11 V=12; // Voltage of avalanche diode in V
12 T=1.7*10^-3; // Temperature coeff of Si diode
13
14 // Calculation
15 A=(T/V)*100;
16 printf("Temperature coeff in percentage = %0.4f
    percent/degree-C",A);
17
18 // Result
19 // Temperature coeff in percentage = 0.0142 %/degree
    -C

```

---

**Scilab code Exa 2.39** Limits for varying V

```

1 // Limits for varying V
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 2-39 in page 113
7
8 clear; clc; close;
9

```

```

10 // Given data
11 I_d=5*10^-3; // Diode current in mA
12 R=2.5*10^3; // Resistance in K-ohm
13 I_T=40*10^-3; // Diode current in mA
14
15 // Calculation
16 I_max=I_T-I_d;
17 printf("(a)I_max = %0.2e A\n",I_max);
18 printf("(b)Minimum I_d for good regulation is 5 mA,
    hence I_T=30 mA\n");
19 V_max1=(30*3.5)+60;
20 printf("V_max = %0.0f V\n",V_max1);
21 printf("Maximum I_d for good regulation is 40 mA,
    hence I_T=65 mA\n");
22 V_max2=(65*3.5)+60;
23 printf("V_max = %0.1f V",V_max2);
24
25 // Result
26 // (a) I_max = 35 mA
27 // (b) V_max1 = 165 V
28 // (c) V_max2 = 287.5 V

```

---

# Chapter 3

## Diode Circuits

Scilab code Exa 3.1 Calculate the dc load current

```
1 // Find current if diode is forward-biased
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-1 in page 143
7
8 clear; clc; close;
9
10 // Given data
11 I=29.8*10^-3; // Current in mA
12 V=0.208; // Voltage in V
13
14 // Calculation
15 I=(45-V)/(1.5*10^3);
16 printf("I = %0.2e A\n",I);
17 printf("For this current ,V = 0.2 V\n");
18 printf("(a) Therefore I = 29.8 mA\n");
19 printf("(b) If battery is inserted with reverse
    polarity ,voltage drop across the 1.5 K resistors
    is only 15 mV and may be neglected\n");
```

```

20 printf("(c)In forward direction , I=29.8 mA\n");
21 printf("In reverse direction we draw a load line
    from V=-30 V to I=-30 mA\n");
22 y=[-30 -25 -20 -15 -10 -5 0];
23 x=[-30 -25 -20 -15 -10 -5 0];
24 x=-30-y;
25 plot(x,y);
26 xlabel('Voltage');
27 ylabel('Current');
28 title('Current in forward direction');
29 I=-30*(20/30);
30 printf("Then, I = %0.0f mA\n",I);
31 printf("Current=20 mA as there is a 10 V drop");
32
33 // Result
34 // Graph shows current in reverse direction
35 // I' = -20 mA
36 // Set axis positions to 'origin' in axis properties
    to view the graph correctly

```

---

### Scilab code Exa 3.2 Find the diode currents

```

1 // Find the diode currents
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-2 in page 144
7
8 clear; clc; close;
9
10 // Given data
11 R=10*10^3; // Resistance in K-ohms

```

```

12
13 // Calculation
14 printf("(a) R = 10K. Assume both diodes are
    conducting. We have:\n");
15 printf("100 = 10.02*I1 + 10*I2 + 0.2\n 100 = 10.01*
    I2 + 10*I1 + 0.6\n");
16 function y=f(i);
17     y(1)=10.02*i(1)+10*i(2)+0.2-100
18     y(2)=10.015*i(2)+10*i(1)+0.6-100
19 endfunction
20 ans=fsolve([0.1;0.1],f);
21 I1=ans([1]);
22 I2=ans([2]);
23 printf("I1 = %0.3f A, I2 = %0.3f A\n",I1,I2);
24 printf("Solving , we find I2 < 0. Thus D is not ON\n");
25 I1=(100-0.2)/10.02;
26 printf("I1 = %0.2e A and I2 = 0\n\n",I1);
27 printf("(b) R=1K. Assume both diodes are ON, we have:\n
    n");
28 printf("100 = 1.52*I1 + 1.5*I2 + 0.2\n 100 = 1.515*
    I2 + 1.5*I1 + 0.6\n");
29 function y1=g(j);
30     y1(1)=1.52*j(1)+1.5*j(2)+0.2-100
31     y1(2)=1.515*j(2)+1.5*j(1)+0.6-100
32 endfunction
33 ans1=fsolve([0.1;0.1],g);
34 I1=ans1([1]);
35 I2=ans1([2]);
36 printf("Solving , we find\n I1 = %0.3f A and I2 = %0.3f
    A. Hence assumption is valid",I1,I2);
37
38 // Result
39 // Since both currents are positive , assumption is
    valid for I1 = 39.717 mA and I2 = 26.287 mA

```

---



This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 3.3 Calculate break region

```
1 // Calculate break region
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-3 in page 145
7
8 clear; clc; close;
9
10 // Given data
11 R=10^4; // Factor multiplied with dynamic resistance
        of diode
12 Vt=26; // Thermal voltage in volts
13 eta1=2; // Constant at room temperature for Si
14 eta2=1; // Constant at room temperature for Ge
15
16 // Calculation
17 printf("r1/r2 = 10^4\n");
18 V1=eta1*Vt*4*2.3;
19 V2=eta2*Vt*4*2.3;
20 printf("Break region for silicon = %0.0f mV\n",V1);
21 printf("Break region for Germanium = %0.0f mV",V2);
22
23 // Result
24 // Break region for silicon = 478 mV
25 // Break region for Germanium = 239 mV
```

---

**Scilab code Exa 3.4** Calculate the peak load current

```
1 // Calculate the peak load current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-4 in page 153
7
8 clear; clc; close;
9
10 // Given data
11 Rf=30; // Internal resistance in ohms
12 Rl=990; // Load resistance in ohms
13 Vm=110; // Rms supply voltage in in V
14
15 // Calculation
16 Im=(Vm/2)/(Rf+Rl);
17 I_dc=Im/%pi;
18 I_rms=Im/2;
19 V_dc=(Im*Rl)/%pi;
20 Pi=I_rms^2*(Rf+Rl);
21 R=((Vm/%pi)-(I_dc*Rl))/(I_dc*Rl))*100;
22
23 printf("(a)Im = %0.2e A\n",Im);
24 printf("(b)I_dc = %0.2e A\n",I_dc);
25 printf("(c)I_rms = %0.2e A\n",I_rms);
26 printf("(d)V_dc = %0.3e V\n",V_dc);
27 printf("(e)Input power = %0.2f W\n",Pi);
28 printf("(f)Percentage regulation = %0.3f percent",R)
29 ;
```

```

30 // Result
31 // (a) Im=53.9mA
32 // (b) Idc=17.2mA
33 // (c) Irms=27mA
34 // (d) Vdc=16.99V
35 // (e) Pi=0.74W
36 // (f) Percentage regulation=106%

```

---

**Scilab code Exa 3.8** Calculate the dc load current

```

1 // Calculate the dc load current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-8 in page 157
7
8 clear; clc; close;
9
10 // Given data
11 Vm=280; // Supply voltage in V
12 Rl=2000; // Load resistance in ohms
13 Rf=500; // Internal resistance of the diodes in ohms
14
15 // Calculation
16 Idc=(2*Vm)/(2*pi*2500);
17 Idc_t=Idc/2;
18 printf("(a) I_dc = %0.2e A\n(b) I_dc(tube) = %0.2e A\n",
        Idc, Idc_t);
19 printf("(c) Voltage across conducting diode is
        sinusoidal with a peak value 0.2 Vm\n");
20 V_rms=0.905*(280*sqrt(2));
21 Pdc=Idc^2*Rl;

```

```

22 R=(Rf/Rl)*100;
23 printf("Rms voltage V_rms = %0.0f V\n",V_rms);
24 printf("(d)DC output power = %0.1f W\n",Pdc);
25 printf("(e)Percentage regulation = %0.0f percent",R)
    ;
26
27 // Result
28 // (a) Idc = 71 mA,
29 // (b) Idc_tube = 35.7 mA,
30 // (c) V_rms = 358 V,
31 // (d) P_dc = 10.167W,
32 // (e) Percentage regulation = 25%

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 3.10 Full scale reading of dc meter

```

1 // Full scale reading of dc metere
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-10 in page 158
7
8 clear; clc; close;
9
10 // Given data
11 R=5020; // Total resistance in ohm
12 Vrms=5.58; // Input rms voltage in V
13 // Calculation
14 I_dc=(2*sqrt(2)*Vrms)/(%pi*5020);
15 V_0=R*I_dc;

```

```
16 printf(" Full scale reading = %0.2f V",V_0);
17
18 // Result
19 // Full scale reading = 5.58 V
```

---

**Scilab code Exa 3.11** Find dc output Peak inverse voltage

```
1 // Find dc output ,Peak inverse voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-11 in page 159
7
8 clear; clc; close;
9
10 // Given data
11 Vi=220; // AC input voltage in V
12 N=10; // Turn ratio of transformer
13
14 // Calculation
15 V2=Vi/N;
16 Vm=sqrt(2)*V2;
17 V_dc=0.318*Vm;
18 PIV=Vm;
19
20 printf("(a)DC output voltage = %0.2f V\n",V_dc);
21 printf("(b)PIV = %0.2f V",Vm);
22
23 // Result
24 // (a) Dc output voltage = 9.89V
25 // (b) PIV = 31.11 V
```

---

**Scilab code Exa 3.12** Determine maximum and average values of power

```
1 // Determine maximum and average values of power
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-12 in page 159
7
8 clear; clc; close;
9
10 // Given data
11 V1=230; // Input voltage in V
12 N=1/3; // Turn ratio
13 R1=200; // Load resistance in ohms
14
15 // Calculation
16 V2=V1*N;
17 Vm=sqrt(2)*V2;
18 Im=Vm/R1;
19 P=Im^2*R1;
20 Vdc=0.318*Vm;
21 Idc=Vdc/R1;
22 Pdc=Idc^2*R1;
23 printf("Maximum load power = %0.2 f W\n",P);
24 printf("Average load power = %0.2 f W",Pdc);
25
26 // Result
27 // Maximum power = 58.78 W
28 // Average power = 5.94 W
```

---

**Scilab code Exa 3.13** Find maximum value of ac voltage

```
1 // Find maximum value of ac voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-13 in page 160
7
8 clear; clc; close;
9
10 // Given data
11 Vdc=30; // DC voltage in V
12 Rf=25; // Internal resistance in ohms
13 Rl=500; // Load resistance in ohms
14
15 // Calculation
16 Idc=Vdc/Rl;
17 Im=%pi*Idc;
18 Vi=Im^2*(Rf+Rl);
19 printf("Voltage required at the input = %0.2f V",Vi)
20 ;
21 // Result
22 // Voltage required at the input is = 18.65 V
```

---

**Scilab code Exa 3.14** Calculate ac voltage rectification efficiency

```

1 // Calculate ac voltage ,rectification efficiency
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-14 in page 160
7
8 clear; clc; close;
9
10 // Given data
11 Vdc=100; // DC voltage in V
12 Rl=500; // Load resistance in ohms
13 Rf=20; // Internal resistance in ohms
14
15 // Calculation
16 Idc=Vdc/Rl;
17 Im=Idc*%pi;
18 Vm=Im*(Rl+Rf);
19 eta=(0.406/(1+(Rf/Rl)))*100;
20
21 printf("(a)AC voltage required = %0.2f V\n",Vm);
22 printf("(b) Rectification efficiency = %0.0f percent"
    ,eta);
23
24 // Result
25 // (a) Vm = 326.73V
26 // (b) Rectification efficiency = 39 percent

```

---

**Scilab code Exa 3.15** Find current dc voltage voltage across load

```

1 // Find current ,dc voltage ,voltage across load
2 // Basic Electronics
3 // By Debashis De

```



```

4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-15 in page 150
7
8 clear; clc; close;
9
10 // Given data
11 Vm=50; // Maximum voltage in V
12 f=50; // Frequency in Hz
13 Rf=20; // Internal resistance in ohms
14 Rl=5000; // Load resistance in ohms
15
16 // Calculation
17 Im=Vm/(Rl+Rf);
18 printf("Since diode conducts only during positive
        half of the input ,Im = %0.0e A\n",Im);
19 printf("(a)Hence i = 10*sin100*pi*t\n");
20 Vdc=(Im/%pi)*Rl;
21 printf("(b)V_dc = %0.1f V\n",Vdc);
22 printf("Hence V_0v=15.9 sin100*pi*t\n");
23 printf("(c)When diode is reverse biased ,voltage
        across diode = %0.1f*sin100*pi*t for 0<100*pi*t<
        pi and 0 for pi,100*pi*t<2*pi",Vdc);
24
25 // Result
26 // (a) Current in the circuit = 10 sin100*pi*t
27 // (b) DC output voltage across load = 15.9 sin100*pi
    *t
28 // (c) Voltage across diode = 15.9 sin100*pi*t for
    0<100*pi*t and 0 for pi<100*pi*t<2*pi

```

---

**Scilab code Exa 3.16** Estimate value of capacitance needed

```

1 // Estimate value of capacitance needed
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-16 in page 161
7
8 clear; clc; close;
9
10 // Given data
11 Vrms=230; // RMS voltage in V
12 f=50; // Frequency in Hz
13 gamma_hwr=0.003; // Ripple factor assumed
14 I=0.5; // Load current in A
15
16 // Calculation
17 Vm=sqrt(2)*Vrms;
18 Vdc=(Vm/%pi);
19 Rl=Vdc/I;
20 C=1/(2*sqrt(3)*f*gamma_hwr*Rl);
21 printf("Capacitance needed = %0.2e F",C);
22
23 // Result
24 // Capacitance needed = 9.29 mF

```

---

**Scilab code Exa 3.17** Calculate the ripple factor

```

1 // Calculate the ripple factor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-17 in page 161

```

```

7
8 clear; clc; close;
9
10 // Given data
11 Rl=3.15*10^3; // Load resistance in K-ohms
12 Rf=20; // Internal resistance in ohms
13 Vm=230; // Maximum voltage in volts
14 f=50; // Frequency in Hertz
15
16 // Calculation
17 Irms=0.707*(Vm/(Rl+Rf));
18 Idc=0.637*(Vm/(Rl+Rf));
19 gamma_fwr=sqrt((Irms/Idc)^2-(1));
20
21 printf("Ripple factor = %0.2f",gamma_fwr);
22
23 // Result
24 // Ripple factor = 0.48

```

---

**Scilab code Exa 3.18** Find DC output voltage pulse frequency

```

1 // Find DC output voltage , pulse frequency
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-18 in page 162
7
8 clear; clc; close;
9
10 // Given data
11 Vp=230; // Peak voltage in V
12 f=50; // Frequency in Hz

```

```

13 Rl=200; // Load resistance in ohms
14 N=1/4; // Turn ratio
15
16 // Calculation
17 Vs=Vp*N;
18 Vm=Vs*sqrt(2);
19 Idc=(2*Vm)/(pi*Rl);
20 Vdc=Idc*Rl;
21 fout=2*f;
22 printf("(a)DC output voltage = %0.2f V\n",Vdc);
23 printf("(b)Pulse frequency of output = %0.0f Hz",
    fout);
24
25 // Result
26 // (a) Vdc = 51.77 V
27 // (b) F_out = 100 HZ

```

---

**Scilab code Exa 3.19** Find maximum dc voltage

```

1 // Find maximum dc voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-19 in page 162
7
8 clear; clc; close;
9
10 // Given data
11 Vp=220; // Peak voltage in V
12 f=50; // Frequency in Hz
13 Rl=1.5*10^3; // Load resistance in ohms
14 N=0.1; // Turn ratio

```

```

15
16 // Calculation
17 Vs=Vp*N;
18 Vrms=Vs*sqrt(2);
19 Vm=Vrms/2;
20 Idc=(2*Vm)/(pi*Rl);
21 Vdc=Idc*Rl;
22 printf("Maximum dc output voltage = %0.2f V",Vdc);
23
24 // Result
25 // Dc output voltage = 9.9 V

```

---

**Scilab code Exa 3.20** Calculate input voltage value of filter

```

1 // Calculate input voltage ,value of filter
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-20 in page 163
7
8 clear; clc; close;
9
10 // Given data
11 Vdc=30; // DC voltage in volts
12 Rl=1000; // Load resistance in ohms
13 gamma_fwr=0.015; // Ripple factor
14
15 // Calculation
16 Idc=Vdc/Rl;
17 C=2900/(gamma_fwr*Rl);
18 Vm=Vdc+((5000*Idc)/C);
19 Vi=(2*Vm)/sqrt(2);

```

```

20 printf("Value of capacitor filter = %0.0f mu-F",C);
21 printf("Input voltage required = %0.2f V\n",Vi);
22
23
24 // Result
25 // V_in = 43.52 V
26 // C = 193 mu-F

```

---

**Scilab code Exa 3.21** Calculate inductance for L section filter

```

1 // Calculate inductance for L-section filter
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-21 in page 163
7
8 clear; clc; close;
9
10 // Given data
11 C=40*10^-6; // Capacitance in micro-F
12 r=0.0001; // Ripple factor
13 Vm=40; // Maximum voltage in V
14 Idc=0.1; // DC current in A
15 R=40; // Circuit resistance in ohms
16
17 // Calculation
18 L=(1.76/C)*sqrt(0.472/r);
19 Vdc=((2*sqrt(2)*Vm)/%pi)-(Idc*R);
20
21 printf("(a) Inductance L = %0.2e H\n",L);
22 printf("(b) Output voltage = %0.0f V",Vdc);
23

```

```
24 // Result
25 // (a) L = 3.02*10^6 H
26 // (b) V_dc = 32 V
```

---

**Scilab code Exa 3.22** DC output voltage and ripple voltage

```
1 // DC output voltage and ripple voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-22 in page 164
7
8 clear; clc; close;
9
10 // Given data
11 C=4; // Capacitances in micro-F
12 L=20; // Inductance choke in H
13 I1=50*10^-6; // Load current in micro-A
14 R=200; // Resistance of choke in ohm
15
16 // Calculation
17 Vdc=(300*sqrt(2))-((4170/C)*0.05)-(0.05*R);
18 r=(3300*0.05)/(4*4*20*353);
19 Vrms=r*Vdc;
20
21 printf("(a) Output voltage = %0.2f V\n",Vdc);
22 printf("(b) Ripple voltage = %0.3f V",Vrms);
23
24 // Result
25 // (a) Output voltage = 362.13 V
26 // (b) Ripple voltage = 0.529 V
```

---

**Scilab code Exa 3.23** Sketch steady state output

```
1 // Sketch steady state output
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3–23 in page 168
7
8 clear; clc; close;
9
10 // Given data
11 Rf=0; // Forward resistance of diode
12 Rr=2*10^6; // Reverse resistance of diode
13
14 // Calculation
15 printf("Diode conducts when Vi<2.5 V\n");
16 printf("Diode is open when Vi>2.5 V and Vo = 2.5+((
    Vi-2.5)/3)\n");
17 printf("Diode conducts when Vi>2.5 V");
18
19 // Result
20 // Diagram shows the output of the clipping circuit
    to a sinusoidal input
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)



### Scilab code Exa 3.24 Sketch output voltage $V_o$

```
1 // Sketch output voltage  $V_o$ 
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-24 in page 169
7
8 clear; clc; close;
9
10 // Given data
11 // Data is provided in the diagrams
12
13 // Calculation
14 printf("(a)When  $V_i < 50$  V, Second diode conducts\n");
15  $V_o = 100 - ((2/3) * 27)$ ;
16 printf("Vo = %0.0 f V\n",  $V_o$ );
17 printf("When  $50 < V_i < 100$  both diodes conduct and  $V_o = V_i$ 
    .When  $V_i > 100$ , only the first diode conducts.Hence
     $V_o = 100$  V\n");
18 printf("(b)When  $V_i < 25$  V, neither diodes conduct and
     $V_o = 25$  V.When  $V_i > 25$ , upper diode conducts\n");
19  $V_i = ((100 - 25) * (3/2)) + 25$ ;
20 printf("When  $V_o$  reaches 100 V,  $V_i$  rises to %0.1 f V",
     $V_i$ );
21
22 // Result
23 // The output voltage is shown in the xcos diagrams
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 3.25** Devise a circuit

```
1 // Devise a circuit
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3–25 in page 169
7
8 clear; clc; close;
9
10 // The xcos diagram shows the devised circuit
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 3.27** Find currents and voltages

```
1 // Find currents and voltages
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3–27 in page 179
7
8 clear; clc; close;
9
10 // Given data
11 //Diode acts as short circuited.Both diodes are
    forward biased
12 V1=0; // Voltage at junction 1 in V
13 V2=0; // Voltage at junction 2 in V
14
15 //Calculation
16 I1=(20-V1)/(20*10^3);
```

```

17 I2=(V2-(-10))/(20*10^3);
18
19 printf(" I1 = %0.0 e A\n",I1);
20 printf(" I2 = %0.1 e A",I2);
21
22 // Result
23 // I1 = 1 mA
24 // I2 = 0.5 mA

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 3.28** Find voltage across diode

```

1 // Find voltage across diode
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-28 in page 180
7
8 clear; clc; close;
9
10 // Given data
11 I=0.1075; // Cirremt across diode in A
12 Rd=1; // Internal resistance of diode in ohm
13
14 // Calculation
15 Vd=I*Rd;
16 printf(" Voltage across diode = %0.4 f V",Vd);
17
18 // Result
19 // Voltage across diode = 0.1075 V

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 3.30** Calculate R Il max

```
1 // Calculate R, I_L(max)
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 3-30 in page 181
7
8 clear; clc; close;
9
10 // Given data
11 V_0=50; // Zener diode voltage in V
12 I_L=0; // Load current in A
13
14 // Calculation
15 R=(150)/(40*10^-3);
16 printf("(a)R = %0.2e ohm\n",R);
17 printf("I_L = I_max when Id = Id_min = 10mA\n");
18 I_Lmax=40-10;
19 printf("(b)Maximum load current = %0.0f mA",I_Lmax);
20
21 // Result
22 // (a) R = 3.75 K-ohms
23 // (b) I_Lmax = 30 mA
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

# Chapter 4

## BJT Fundamentals

Scilab code Exa 4.1 Calculate Base and Collector Currents

```
1 // Calculate Base and Collector Currents
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-1 in page 208
7
8 clear; clc; close;
9
10 // Given Data
11 alpha=0.90; // Current Gain in CB mode
12 Ico=15*10^-6; // Reverse saturation Current in micro
    -A
13 Ie=4*10^-3; // Emitter Current in mA
14
15 // Calculations
16 Ic=Ico+(alpha*Ie);
17 Ib=Ie-Ic;
18
19 printf("(a)The value of the Base Current is %0.2e A
    \n",Ib);
```

```

20 printf("(b)The value of the Collector Current is %0
    .3e A \n",Ic);
21
22 // Results
23 // (a) The value of the Base Current is 385 mu-A
24 // (b) The value of the Collector Current is 3.615
    mA

```

---

#### Scilab code Exa 4.2 Calculate alpha using beta

```

1 // Calculate alpha using beta
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-2 in page 209
7
8 clear; clc; close;
9
10 // Given Data
11 beta_bjt=90; // beta gain for the BJT
12 Ic=4*10^-3; // Collector Current in mA
13
14 // Calculations
15 alpha=beta_bjt/(1+beta_bjt);
16 Ib=Ic/beta_bjt;
17 Ie=Ic+Ib;
18
19 printf("(a)The Current gain alpha for BJT is %0.3f \
    n",alpha);
20 printf("(b)The value of the base Current is %0.2e A
    \n",Ib);
21 printf("(c)The value of the Emitter Current is %0.2e

```

```

    A \n",Ie);
22
23 // Results
24 // (a) The Current Gain alpha for BJT is 0.989
25 // (b) The value of the Base Current is 44.44 mu-A
26 // (c) The value of the Emitter Current is 4.04 mA

```

---

### Scilab code Exa 4.3 Collector Current in C E mode

```

1 // Collector Current in C-E mode
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-3 in page 209
7
8 clear; clc; close;
9
10 // Given Data
11 alpha=0.90; // Current Gain of BJT
12 Ico=15*10^-6; // Reverse Saturation Current of BJT
    in micro-A
13 Ib=0.5*10^-3; // Base Current in C-E mode in mA
14
15 // Calculations
16 beta_bjt=alpha/(1-alpha);
17 Ic=(beta_bjt*Ib)+(beta_bjt+1)*Ico;
18
19 printf("(a)The value of Current gain beta for BJT is
    %0.0f \n",beta_bjt);
20 printf("(b)The value of the Collector Current is %0
    .2e A \n",Ic);
21

```



```
22 // Results
23 // (a) The value of Current Gain beta for BJT is 9
24 // (b) The value of the Collector Current is 4.65 mA
```

---

#### Scilab code Exa 4.4 Calculate beta for the BJT

```
1 // Calculate beta for the BJT
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-4 in page 209
7
8 clear; clc; close;
9
10 // Given Data
11 Ib=20*10^-6; // Base current in micro-A
12 Ic=5*10^-3; // Collector Current in mA
13
14 // Calculations
15 beta_bjt=Ic/Ib;
16
17 printf("The Current gain beta for the Device is %0.0
18       f \n",beta_bjt);
19
20 // Results
21 // The Current Gain beta for the Device is 250
```

---

#### Scilab code Exa 4.5 To Compute Alpha Beta and Emitter Current

```

1 // To Compute alpha , beta and Emitter Current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-5 in page 209
7
8 clear; clc; close;
9
10 // Given Data
11 Ib=50*10^-6; // Base Current in mu-A
12 Ic=5*10^-3; // Collector Current in mA
13
14 // Calculations
15 Ie=Ic+Ib;
16 beta_bjt=Ic/Ib;
17 alpha=Ic/Ie;
18
19 printf("(a)The value of the Emitter Current is %0.2e
        A \n",Ie);
20 printf("(b)The value of beta gain of the BJT is %0.0
        f \n",beta_bjt);
21 printf("(c)The value of alpha gain of the BJT is %0
        .3f \n",alpha);
22
23 // Results
24 // (a) The value of the Emitter Current is 5.05 mA
25 // (b) The value of the beta gain of the BJT is 100
26 // (c) The value of the alpha gain of the BJT is
        0.990

```

---

**Scilab code Exa 4.6** Calculate alpha reverse and beta reverse

```

1 // Calculate alpha reverse and beta reverse
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-6 in page 210
7
8 clear; clc; close;
9
10 // Given Data
11 Ie=10*10^-3; // Emitter Current in mA
12 Ib=5*10^-3; // Base Current in mu-A
13
14 // Calculations
15 Ic=Ie-Ib;
16 beta_reverse=Ib/Ic;
17 alpha_reverse=Ie/Ic;
18
19 printf("The value of inverse beta of the BJT is %0.0
    f \n",beta_reverse);
20 printf("The value of inverse alpha of the BJT is %0
    .0f \n",alpha_reverse);
21
22 // Results
23 // The value of inverse beta of the BJT is 1
24 // The value of inverse alpha of the BJT is 2

```

---

**Scilab code Exa 4.7** Calculate Labeled Currents and Voltages

```

1 // Calculate Labeled Currents and Voltages
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010

```

```

5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-7 in page 210
7
8 clear; clc; close;
9
10 // Given Data
11 beta_bjt=100; // beta gain of BJT
12 Vbe=0.7; // Base-Emitter voltage of BJT in V
13
14 // Calculation
15 Vcc1=10;
16 Vee1=-10;
17 Ve1=-0.7;
18 R1=10*10^3;
19 Ie1=(Vcc1-Vbe)/R1;
20 Ib1=Ie1/(beta_bjt+1);
21 Vc1=Vcc1-R1*(Ie1-Ib1);
22 Vcc2=10;
23 Vee2=-15;
24 Ve2=-0.7;
25 R2=5*10^3;
26 Ie2=(Vcc2-Vbe)/R2;
27 Ic2=(beta_bjt/(beta_bjt+1))*Ie2;
28 Vc2=Vee2+R2*(Ie2);
29 printf(" Circuit 1:\n(a) Emitter Current=%0.2e A\n(b)
      Base Current=%0.2e A\n(c) Collector Voltage=%0.3f
      V\n\n", Ie1, Ib1, Vc1);
30 printf(" Circuit 2:\n(a) Emitter Current=%0.2e A\n(b)
      Collector Current=%0.3e A\n(c) Collector Voltage=
      %0.3f V\n", Ie2, Ic2, Vc2);
31
32 // Results
33 // (a) Circuit 1 : Emitter Current = 0.93 mA
34 // (b) Circuit 1 : Base Current = 9.2 mu-A
35 // (c) Circuit 1 : Collector Voltage = 0.792 V
36
37 // (a) Circuit 2 : Emitter Current = 1.86 mA
38 // (b) Circuit 2 : Collector Current = 1.842 mA

```

39 `//(c) Circuit 2 : Collector Voltage : -5.7 V`

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

#### Scilab code Exa 4.8 Calculate labeled Voltages

```
1 // Calculate labeled Voltages
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-8 in page 211
7
8 clear; clc; close;
9
10 // Given Data
11 Vbe=0.7; // Base-Emitter voltage of BJT in V
12 Vcc2=10; // DC voltage across Collector in V
13 Vee2=-15; // DC voltage across Emitter in V
14 Rc2=5*10^3; // Collector Resistance in K-ohms
15 // Beta Current Gain of BJT is Infinity
16
17 // Calculations
18 Vb1=0;
19 Ve1=-0.7;
20 Ve2=0.7;
21 Vc2=Vee2+Rc2*((Vcc2-Vbe)/Rc2);
22
23 printf("Circuit 1:\n(a)Base Voltage = %0.1f V\n(b)
    Emitter Voltage = %0.1f V\n",Vb1,Ve1);
24 printf("Circuit 2:\n(a)Emitter Voltage = %0.1f V\n(b
    )Collector Voltage = %0.1f V\n",Ve2,Vc2);
```

```

25
26 //Results
27 // Circuit 1 : Base Voltage = 0 V
28 // Circuit 1 : Emitter Voltage = -0.7 V
29 // Circuit 2 : Emitter Voltage = 0.7 V
30 // Circuit 2 : Collector Voltage = -5.7 V

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 4.9** Calculating BJT parameters assuming Vbe

```

1 // Calculating BJT parameters assuming Vbe
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-9 in page 211
7
8 clear; clc; close;
9
10 // Given Data
11 Ve=1; // Emitter Voltage of BJT in V
12 Vbe=0.7; // Base-Emitter Voltage of BJT in V
13 Rb=20*10^3; // Base Resistance of Circuit in K-ohms
14 Rc=5*10^3; // Collector Resistance of Circuit in K-
    ohms
15 Re=5*10^3; // Emitter Resistance of Circuit in K-
    ohms
16 Vcc=5; // DC voltage across Collector in V
17 Vee=-5; // DC voltage across Emitter in V
18
19 // Calculations

```

```

20 Vb=Ve-Vbe;
21 Ib=Vb/Rb;
22 Ie=(Vcc-1)/Re;
23 Ic=Ie-Ib;
24 Vc=(Rc*Ic)-Vcc;
25 beta_bjt=Ic/Ib;
26 alpha=Ic/Ie;
27
28 printf("Circuit Parameters:\n(a)Base Voltage = %0.3f
      V\n(b)Base Current = %0.3e A\n(c)Emitter Current
      = %0.3e A\n(d)Collector Current = %0.3e A\n(e)
      Collector Voltage = %0.3f V\n(f)beta gain = %0.3f
      \n(g)alpha gain = %0.3f\n",Vb,Ib,Ie,Ic,Vc,
      beta_bjt,alpha);
29
30 // Results
31 // For the BJT Circuit ,
32 // (a) Base Voltage = 0.3 V
33 // (b) Base Current = 0.015 mA
34 // (c) Emitter Current = 0.8 mA
35 // (d) Collector Current = 0.785 mA
36 // (e) Collector Voltage = -1.075 volt
37 // (f) Beta gain = 52.3
38 // (g) Alpha gain = 0.98

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

#### Scilab code Exa 4.10 Measurement of Circuit Voltage changes

```

1 // Measurement of Circuit Voltage changes
2 // Basic Electronics
3 // By Debashis De

```

```

4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-10 in page 211
7
8 clear; clc; close;
9
10 // Given Data
11 Vb=-5; // Base Voltage of BJT in V
12 Rc=1*10^3; // Collector Resistance in K-ohms
13 Ie=2*10^-3; // Emitter Current of BJT in mA
14 delB=+0.4; // Change in Base Voltage
15
16 // Calculations
17 delE=+0.4;
18 delC=0;
19
20 printf("(a)Change in Emitter voltage is +%0.2f V\n",
        delE);
21 printf("(b)Change in Collector Voltage is %0.2f V\n"
        ,delC);
22
23 // Results
24 // (a) Change in Emitter Voltage in the Circuit =
        +0.4 V
25 // (b) Change in Collector Voltage in the Circuit =
        0.0 V

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 4.11** To Determine mode of operation of BJT

```

1 // Determine mode of operation of BJT

```



```

2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 4-11 in page 212
7
8 clear; clc; close;
9
10 // Given Data
11 Vbe=0.7; // Base-Emitter Voltage in V
12 beta_bjt=100; // beta gain of BJ
13
14 // Calculation
15 printf("Assume active mode for circuit 1\n");
16 Vb1=2;
17 Ve_1=Vb1-Vbe;
18 Ie1=1*10^-3;
19 Ic1=Ie1*(beta_bjt/(1+beta_bjt));
20 Ve1=6-(3*0.99);
21 printf("(a)Ve = %0.2f V\n(b)Ic = %0.2e A\n(c)Ve = %0
    .2f V\n",Ve_1,Ic1,Ve1);
22 printf("Thus the circuit operates in an active mode\
    n\n");
23
24 printf("For circuit 2,assume active mode\n");
25 Vcc=1;
26 Ve2=Vcc+Vbe;
27 Ie2=(6-Ve2)/(10*10^3);
28 Vc=0+(10*0.43);
29 printf("(a)Ve = %0.1f V\n(b)Ie = %0.2e A\n(c)Vc = %0
    .2f V\n",Ve2,Ie2,Vc);
30 printf("This circuit operates in a saturated mode\n\
    n");
31
32 printf("For circuit 3,assume active mode\n");
33 Ve3=-5+Vbe;
34 Ie3=(9.5-Ve3)/(200*10^3);
35 Ic=Ie3*(beta_bjt/(1+beta_bjt));

```

```

36 Vc3=-50+(0.492*20);
37 printf("(a)Ve = %0.1f V\n(b)Ie = %0.4e A\n(c)Ic = %0
    .3e A\n(d)Vc = %0.1f V\n",Ve3,Ie3,Ic,Vc3);
38 printf("The circuit operates in an active mode\n\n")
    ;
39
40 printf("For circuit 4,assume active mode\n");
41 Ve4=-20.7;
42 Ie4=(30+Ve4)/(5*10^3);
43 Vc4=(-Ie4*(beta_bjt/(1+beta_bjt))*(2*10^3))-10;
44 printf("(a)Ie = %0.2e A\n(b)Vc = %0.2f V\n",Ie4,Vc4)
    ;
45 printf("The circuit operates in an active mode");
46
47 // Result
48 // (a) Circuit 1 operates in active mode
49 // (b) Circuit 2 operates in saturation mode
50 // (c) Circuit 3 operates in active mode
51 // (d) Circuit 4 operates in active mode

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

# Chapter 5

## BJT Circuits

Scilab code Exa 5.1 Calculate BJT parameters using beta gain

```
1 // Calculate BJT parameters using beta gain
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 5-1 in page 235
7
8 clear; clc; close;
9
10 // Part 1
11 // Given Data
12 beta_bjt=100; // Beta Gain of BJT
13 Vcc=10; // DC voltage across Collector in V
14 Rb=100000; // Base Resistance of BJT in ohm
15 Rc=2000; // Collector Resistance of BJT in ohm
16 Vbe=0.7; // Base-Emmitter voltage of BJT
17
18 // Calculations
19 Ib=(Vcc-Vbe)/((beta_bjt*Rc)+Rc+Rb);
20 Ic=beta_bjt*Ib;
21
```

```

22 Vce=Vcc-(Ib+Ic)*Rc;
23
24 printf("Part 1 \n");
25 printf("(a)The value of Base Current in the BJT
    circuit is %0.3e A \n",Ib);
26 printf("(b)The value of Collector Current in the BJT
    circuit is %0.3e A \n",Ic);
27 printf("(c)The value of Collector-Emmitter voltage in
    the circuit is %0.3f V \n",Vce);
28
29 // Part 2
30 // Given Data
31 Vce2=7; // Collector-Emmitter voltage of BJT
32 Vcc=10; // DC voltage across Collector in V
33 Rc=2000; // Collector Resistance of BJT in ohm
34 Vbe=0.7; // Base-Emmitter voltage of BJT
35 Rc2=2000; // Collector Resistance of BJT in ohm
36
37 // Calculations
38 constant=(Vcc-Vce2)/Rc;
39 Ib2=constant/101;
40 Ic2=100*Ib2;
41 Rb2=(Vcc-Vbe-(Rc2*constant))/Ib2;
42
43 printf("\nPart 2 \n");
44 printf("(a)The value of the Base Resistance of the
    Circuit is %0.3e ohm \n ",Rb2);
45
46 // Results
47 // Circuit 1: Value of Base Current of circuit =
    0.031 mA
48 // Circuit 1: Value of Collector Current of circuit
    = 3.1 mA
49 // Circuit 1: Value of Collector-Emmitter voltage of
    BJT circuit = 3.779 V
50 // Circuit 2: Value of BAse Resistance required =
    424.24 K-ohm

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 5.4** To establish Operating Point and Stability Factor

```
1 // To establish Operating Point & Stability Factor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 5-4 in page 238
7
8 clear; clc; close;
9
10 // Given Data
11 beta_bjt=50; // Beta Gain of the BJT circuit
12 Vbe=0.7; // Base-Emitter voltage of BJT in V
13 Vcc=22.5; // DC voltage across Collector in V
14 Rc=5600; // Resistance across Collector in ohm
15 Vce=12; // Operating Collector-Emitter voltage of
    circuit in V
16 Ic=1.5*10^-3; // Operating Collector current of
    circuit in mA
17 sfactor=3; // Stability factor of the circuit
18
19 // Calculations
20 Re=((Vcc-Vce)/Ic)-Rc;
21 constant=((beta_bjt+1)*(sfactor-1))/((beta_bjt+1)-
    sfactor);
22 Rb=constant*Re;
23 Ib=Ic/beta_bjt;
24 voltage=(Ib*Rb)+Vbe+((Ib+Ic)*Re);
```

```

25 R1=Rb*(Vcc/voltage);
26 R2=(R1*voltage)/(Vcc-voltage);
27
28 printf("(a)The value of Emitter Resistance of the
    BJT circuit is %0.2e ohm \n",Re);
29 printf("(b)The value of Resistance-1 of the BJT
    circuit is %0.2e ohm \n",R1);
30 printf("(c)The value of Resistance-2 of the BJT
    circuit is %0.2e ohm \n",R2);
31
32 // Results
33 // The value of Emitter Resistance of the BJT
    circuit is 1.4 K-ohm
34 // The value of Resistance-1 of the BJT circuit is
    22.8 K-ohm
35 // The value of Resistance-2 of the BJT circuit is
    3.4 K-ohm

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 5.5 Design Bias Circuit for given Stability Factor

```

1 // Design Bias Circuit for given Stability Factor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 5-5 in page 239
7
8 clear; clc; close;
9
10 // Given data

```

```

11 Vcc=20; // Supply DC Voltage in V
12 Rc=1.5*10^3; // Collector Resistance in ohm
13 Vce=8; // Collector-Emmitter Resistance in V
14 Ic=4*10^-3; // Collector Current in A
15 S=12; // Stability Factor of circuit
16 beta_bjt=50; // Beta Gain of BJT
17
18 // Calculations
19 Ib=Ic/beta_bjt;
20 Re=(Vcc-Vce-Ic*Rc)/(Ib+Ic);
21 Rb=Re*((S*beta_bjt)/((beta_bjt+1)-S));
22 Ie=Ic+Ib;
23 Vbn=0.2+Ie*Re;
24 Vth=Vbn+Ib*Rb;
25 R1=(Vcc*Rb)/Vth;
26 Ir1=(Vcc-Vbn)/R1;
27 Ir2=Ir1-Ib;
28 R2=Vbn/Ir2;
29
30 // For S=3
31 S_2=3;
32 Rc_2=1.47*10^3;
33 Re_2=Re;
34 Rb_2=Re*((S_2*beta_bjt)/((beta_bjt+1)-S_2));
35 Vth_2=Vbn+(Ib*Rb_2)+6.16;
36 R1_2=(Vcc*Rb_2)/Vth_2;
37 Ir1_2=(Vcc-Vbn)/R1_2;
38 Ir2_2=Ir1_2-Ib;
39 R2_2=Vbn/Ir2_2;
40
41 printf("For S=12 \n");
42 printf("(a) Ib = %0.2e A \n(b) Ir1 = %0.2e A \n(c) Ir2
    = %0.2e A \n", Ib, Ir1, Ir2);
43 printf("(d) Re = %0.2e ohm \n(e) Rb = %0.2e ohm \n(f)
    R1 = %0.2e ohm \n(g) R2 = %0.2e ohm \n", Re, Rb, R1,
    R2);
44 printf("(h) Base-Ground Voltage Vbn = %0.2f V \n(i)
    Thevenin Voltage Vth = %0.2f V \n", Vbn, Vth);

```

```

45 printf("\n For S=3 \n");
46 printf("(a)Re = %0.2e ohm \n(b)Rb = %0.2e ohm \n(c)
    R1 = %0.2e ohm \n(d)R2 = %0.2e ohm \n",Re_2,Rb_2,
    R1_2,R2_2);
47 printf("(e)Thevenin Voltage Vth = %0.2f V \n(f)Ir1 =
    %0.2e A \n(g)Ir2 = %0.2e A \n",Vth_2,Ir1_2,Ir2_2
    );
48
49 // Results
50 // S=12
51 // (a) Ib=80 mu-A
52 // (b) Re=1.47 K-ohm
53 // (c) Rb=21.17 K-ohm
54 // (d) Vbn=5.91 V
55 // (e) Vth=7.60 V
56 // (f) R1=55.71 K-ohm
57 // (g) R2=37.16 K-ohm
58 // (h) IR1=0.253 mA
59 // (i) IR2=0.173 mA
60 // S=3
61 // (a) Rb=3.13 K-ohm
62 // (b) R1=10.16 K-ohm
63 // (c) IR1=1.387 mA
64 // (d) R2=4.52 K-ohm
65 // (e) IR2=1.307 mA

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 5.8 Calculate circuit parameters of a Emitter Follower

```

1 // Calculate circuit parameters of a Emitter
  Follower

```



```

2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 5-8 in page 251
7
8 clear; clc; close;
9
10 // Given data
11 Rs=0.5*10^3; // Source resistance in ohm
12 Rl=5*10^3; // Load resistance in ohm
13 hfe=50; // h-parameter value of the BJT
14 hie=1*10^3; // h-parameter value of the BJT in ohm
15 hoe=25*10^-6; // h-parameter value of the BJT in A/V
16
17 // Calculations
18 Ai=(1+hfe)/(1+hoe*Rl);
19 Ri=hie+Ai*Rl;
20 Av=1-(hie/Ri);
21 Avs=Av*(Ri/(Ri+Rs));
22
23 printf("(a)The current gain of circuit Ai = %0.1f \n
    ",Ai);
24 printf("(b)The input resistance of circuit Ri = %0.2
    e ohm \n",Ri);
25 printf("(c)The voltage gain of circuit Av = %0.4f \n
    ",Av);
26 printf("(d)The voltage gain of circuit Avs = %0.4f \
    n",Avs);
27
28 // Results
29 // (a) The current gain of circuit Ai=45.3
30 // (b) The input resistance of circuit Ri=227 ohm
31 // (c) The voltage gain of circuit Av=0.9956
32 // (d) The voltage gain of circuit Avs=0.9934

```

---

### Scilab code Exa 5.9 Design of an Emitter Follower

```
1 // Design of an Emitter Follower
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 5-9 in page 252
7
8 clear; clc; close;
9
10 // Given data
11 Ri=500*10^3; // Input Resistance in ohm
12 Ro=20; // Output Resistance in ohm
13 hfe=50; // h-parameter of BJT
14 hie=1*10^3; // h-parameter of BJT in ohm
15 hoe=25*10^-6; // h-parameter of BJT in A/V
16 const=499*10^3; // Product of Ai and Rl in ohm
17 Av=0.999; // Voltage gain of circuit
18 const_2=10^6; // Product of Ai and Rl in ohm for Av
    =0.999
19
20 // Calculations
21 Ai=1+hfe-(const*hoe);
22 Rl=const/Ai;
23 Rs=((hfe+1)*hoe*Ro)-hie;
24 Ri_2=hie/(1-Av);
25 Rl_2=((1+hfe)/const_2)-1)/hoe;
26
27 printf("The current gain of circuit=%0.1f \n",Ai);
28 printf("When Av=0.999, \n(a)Ri=%0.2e ohm \n(b)Rl=%0
    .2e ohm \n",Ri_2,Rl_2);
```

```
29
30 // Results
31 // The current gain of circuit = 38.5
32 // For Av = 0.999,
33 // (a) Ri = 1 M-ohm,
34 // (b) Rl = -40.0 K-ohm
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

# Chapter 6

## Field Effect Transistor

Scilab code Exa 6.1 Determine approximate drain source resistance

```
1 // Determine approximate drain-source resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-1 in page 274
7
8 clear; clc; close;
9
10 // Given data
11 I_ds=10*10^-3; // Drain current in mA
12 Vp=-2; // Peak voltage in V
13 Vgs=[0 -0.5]; // Values of Vgs in V
14
15 // Calculation
16 alp=[1 2];
17 for i=1:2
18     r=Vp^2/(2*I_ds*(Vgs(i)-Vp));
19     printf("(%.0f) r_ds when Vgs = %d V is %.2f ohm
20         \n",alp(i),Vgs(i),r);
21 end
```

```
21
22 // Result
23 // (a) When  $V_{gs} = 0$  V,  $r_{ds} = 100$  ohms
24 // (b) When  $V_{gs} = 0.5$  V,  $r_{ds} = 133.33$  ohms
```

---

### Scilab code Exa 6.2 Find $I_d$ and $V_{ds}$

```
1 // Find  $I_d$  and  $V_{ds}$ 
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-2 in page 274
7
8 clear; clc; close;
9
10 // Given data
11  $I_{ds}=12*10^{-3}$ ; // Drain current in mA
12  $V_p=-4$ ; // Peak voltage in V
13  $V_{gs}=-2$ ; // Gate to source voltage in V
14  $R_d=3*10^3$ ; // Drain resistance in K-ohms
15  $V_{cc}=15$ ; // Supply voltage in V
16
17 // Calculation
18  $id=I_{ds}*(1-(V_{gs}/V_p))^2$ ;
19  $V_{ds}=-id*R_d+V_{cc}$ ;
20
21 printf("(a)  $I_d = %0.0e$  A\n",id);
22 printf("(b)  $V_{ds} = %0.0f$  V",Vds);
23
24 // Result
25 // (a)  $I_d = 3mA$ 
26 // (b)  $V_{ds} = 6V$ 
```

---

**Scilab code Exa 6.3** Find the value of Rd

```
1 // Find the value of Rd
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-3 in page 275
7
8 clear; clc; close;
9
10 // Given data
11 Ids=12*10^-3; // Drain current in mA
12 Vp=-4; // Peak voltage in V
13 Rs=0; // Source resistance in ohms
14 Vds=0.1; // Drain-source voltage in V
15 Vgg=0; // Gate voltage in V
16
17 // Calculation
18 id=Ids*(50*10^-3-625*10^-6);
19 Rd=(15-Vds)/id;
20
21 printf("(a) i_d = %0.3e A\n",id);
22 printf("(b) Rd = %0.3e ohm",Rd);
23
24 // Result
25 // (a) i_d = 592.6 mu-A
26 // (b) Rd = 25.15 k-ohm
```

---

**Scilab code Exa 6.4** Find  $i_d$   $V_{ds}$  slope of operation of JFET

```
1 // Find  $i_d$ ,  $V_{ds}$ , slope of operation of JFET
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-4 in page 275
7
8 clear; clc; close;
9
10 // Given data
11 Ids=12*10^-3; // Drain current in mA
12 Vp=-4; // Peak voltage in V
13 Rd=1*10^3; // Drain resistance in k-ohm
14 Vdd=15; // Drain voltage in V
15
16 // Calculation
17 Id=Ids;
18 Vds=(-Rd*Id)+Vdd;
19 printf("Id = %0.2e A\n", Id);
20 printf("Vds = %0.0f V\n", Vds);
21 printf("Consider it to be operating in the ohmic
    region\n");
22 Vds1=(7+sqrt(49-45))/(3/2);
23 Vds2=(7-sqrt(49-45))/(3/2);
24 printf("Then Vds = %0.2f V, %0.2f V\n", Vds1, Vds2);
25 printf("6V is neglected since it is lesser than -Vp\
    n");
26 id=(15-Vds2)/(1*10^3);
27 Vds=Vds2;
28 printf("(a) Id = %0.3e A\n", id);
```

```

29 printf("(b)Vds = %0.2f V",Vds);
30 printf("Since Vds<Vgs-Vp,operation region is
    confirmed in the ohmic region");
31
32 // Result
33 // (a) Id = 11.67 mA
34 // (b) Vds = 3.33 V
35 // (c) Operation region is in the ohmic region

```

---

#### Scilab code Exa 6.5 Find id Vgs Rd Vds

```

1 // Find id ,Vgs ,Rd ,Vds
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-5 in page 276
7
8 clear; clc; close;
9
10 // Given data
11 Ids=10*10^-3; // Drain current in mA
12 Vp=-4; // Peak voltage in V
13 Vdd=12; // Drain voltage in V
14 Vgg=0; // Gate voltage in V
15
16 // Calculation
17 id=10*10^-3*(1-(2/4))^2;
18 Vgs=(sqrt(9/10)-1)*4;
19 Rd=(12-7.5)/(0.625*10^-3);
20 Vds=12-2-(3*0.625);
21 printf("(a)Id = %0.2e A\n",id);
22 printf("(b)Vgs = %0.3f V\n",Vgs);

```



```

23 printf("(c)Rd = %0.2e ohm\n",Rd);
24 printf("(d)Vds = %0.3f V",Vds);
25
26 // Result
27 // (a) Id = 2.5 mA
28 // Vgs = -0.205 V
29 // (c) Rd = 7.2 k-ohm
30 // (d) Vds = 8.125 V

```

---

**Scilab code Exa 6.6** Determine Vgs Id Vds operating region

```

1 // Determine Vgs,Id,Vds,operating region
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-6 in page 276
7
8 clear; clc; close;
9
10 // Given data
11 Ids=16*10^-3; // Drain current in mA
12 Vp=-4; // Peak voltage in V
13 Vdd=18; // Drain voltage in V
14 Rd=500; // Drain resistance in ohms
15
16 // Calculation
17 vgs1=(-10+sqrt(100-64))/2;
18 vgs2=(-10-sqrt(100-64))/2;
19 printf("(a)Vgs = %d V,%d V\n",vgs1,vgs2);
20 id=-vgs1/500;
21 Vds=18-((1*10^3)*(4*10^-3));
22 printf("(b)id = %0.0e A\n",id);

```

```

23 printf("(c)Vds = %0.0f V\n",Vds);
24 printf("Saturation region operation is confirmed
    from above results");
25
26 // Result
27 // (a) Vgs = -2V
28 // (b) Id = 4 mA,
29 // (c) Vds = 14 V,

```

---

#### Scilab code Exa 6.7 Determine Vgs Id Vds

```

1 // Determine Vgs,Id,Vds
2 // Determine Vgs,Id,Vds,operating region
3 // Basic Electronics
4 // By Debashis De
5 // First Edition , 2010
6 // Dorling Kindersley Pvt. Ltd. India
7 // Example 6-7 in page 277
8
9 clear; clc; close;
10
11 // Given data
12 Ids=8*10^-3; // Drain current in mA
13 Vp=-4; // Peak voltage in V
14 Vdd=18; // Drain voltage in V
15 Rd=8*10^3; // Drain resistance in K-ohms
16
17 // Calculation
18 vgs1=(-214+sqrt(214^2-(4*63*180)))/(2*63);
19 vgs2=(-214-sqrt(214^2-(4*63*180)))/(2*63);
20 printf("(a)Vgs = %0.2f V,%0.2f V\n",vgs1,vgs2);
21 id1=-vgs1/(1*10^3);
22 id2=-vgs2/(1*10^3);

```

```

23 printf("(b) Id = %0.2e A,%0.2e A\n",id1,id2);
24 Vds1=(-9*10^3)*id1)+18;
25 Vds2=(-9*10^3)*id2)+18;
26 printf("(c) Vds = %0.2f V,%0.2f V",Vds1,Vds2);
27
28 // Result
29 // (a) Vgs = -1.53 V,-1.86 V
30 // (b) Id = 1.53 mA,1.86 mA
31 // (c) Vds = 4.23 V,1.26 V

```

---

#### Scilab code Exa 6.8 Determine R Ids Vgs

```

1 // Determine R,Ids ,Vgs
2 // Determine Vgs,Id ,Vds,operating region
3 // Basic Electronics
4 // By Debashis De
5 // First Edition , 2010
6 // Dorling Kindersley Pvt. Ltd. India
7 // Example 6-8 in page 277
8
9 clear; clc; close;
10
11 // Given data
12 Vp=-3; // Peak voltage in V
13 Vgg=5; // Gate voltage in V
14 Ids=10*10^-3; // Drain current in mA
15
16 // Calculation
17 R=5/(10*10^-3);
18 printf("(a)R = %0.0f ohm\n",R);
19 Ids=5/400;
20 Vds=(2*Ids*R)+15;
21 printf("(b) Idss = %0.2e A\n",Ids);

```

```

22 printf("(c)Vds = %0.0f V\n",Vds);
23 printf("This confirms active region\n");
24 Rid=14/2;
25 Vgs=Vgg-Rid;
26 printf("(d)Vgs = %0.0f V\n",Vgs);
27 printf("Vds=2>Vgs-Vp=-1.5+3=1.5 -> Active region");
28
29 // Result
30 // (a) R = 500ohm,
31 // (b) Ids = 12.5mA,
32 // (c) Vgs = -2V

```

---

#### Scilab code Exa 6.9 Find Id Vgs Vds region of operation

```

1 // Find Id,Vgs,Vds,region of operation
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-9 in page 277
7
8 clear; clc; close;
9
10 // Given data
11 Idss=4*10^-3; // Drain current in mA
12 Vp=-2; // Peak voltage in V
13 Vdd=10; // Supply voltage in V
14 Vgs=0; // Gate source voltage in V
15
16 // Calculation
17 Id=Idss*(1-(Vgs/Vp));
18 printf("(a)Id = %0.0e A\n",Id);
19 printf("(b)Since Id=Idss , Vgs=0 V\n");

```

```

20 Vds=10-Vgs;
21 printf("(c)Vds = %0.0f V\n",Vds);
22 printf("Since Vds=10V>Vgs-Vp=2V, Active region
        operation of upper JFET is confirmed");
23
24 // Result
25 // (a) Id = 4 mA,
26 // (b) Vgs = 0 V,
27 // (c) Vds = 10 V

```

---

**Scilab code Exa 6.10** Find pinch off saturation voltage

```

1 // Find pinch off ,saturation voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-10 in page 279
7
8 clear; clc; close;
9
10 // Given data
11 Nd=3*10^21; // Donor concentration in /m^3
12 epsln=12; // Dielectric constant of silicon
13 epsln_0=12*8.85*10^-12; // Constant of calculation
14 e=1.6*10^-19; // Charge on an electron in C
15 a=2*10^-6; // Constant of calculation
16
17 // Calculation
18 Vp=(e*Nd*(a)^2)/(2*epsln_0);
19 printf("(a)Pinch off voltage = %0.3f V\n",Vp);
20 Vds=Vp-2;
21 printf("(b) Saturation voltage = %0.3f V",Vds);

```

```
22
23 // Result
24 // (a) Pinch off voltage = 9.040 V
25 // (b) Saturation voltage = 7.040 V
```

---

**Scilab code Exa 6.11** Determine drain source resistance

```
1 // Determine drain-source resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-11 in page 287
7
8 clear; clc; close;
9
10 // Given data
11 Ids=10*10^-3; // Drain current in mA
12 Vp=-2; // Peak voltage in V
13 Vgs=[1 2]; // Gate-source voltage in V
14
15 // Calculation
16 for i=1:2
17     rds=Vp^2/(2*Ids*(Vgs(i)-Vp));
18     printf("Rds = %0.1f ohm\n",rds);
19 end
20
21 // Result
22 // Rds = 66.7 ohm, 50 ohm
```

---

**Scilab code Exa 6.12** Determine approximate Rds

```
1 // Determine approximate Rds
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-12 in page 287
7
8 clear; clc; close;
9
10 // Given data
11 K=0.25*10^-3; // Constant in mA/V^2
12 Vt=2; // Voltage in V
13 Vgs=[4 6 10]; // Drain-source voltage in V
14
15 // Calculation
16 for i=1:3
17     rds=1/(2*K*(Vgs(i)-Vt));
18     printf("Rds = %0.0f ohm\n",rds);
19 end
20
21 // Result
22 // Rds = 1 K-ohm, 500 ohm, 250 ohm
```

---

**Scilab code Exa 6.13** Find Vgs operating region Id Rd

```
1 // Find Vgs, operating region ,Id ,Rd
```

```

2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-13 in page 288
7
8 clear; clc; close;
9
10 // Given data
11 Vdd=10; // Drain voltage in in V
12 Vds=6; // Drain-source voltage in V
13 K=0.2*10^-3; // Constant in mA/V^2
14 Vt=1; // Voltage given
15
16 // Calculation
17 Vgs=Vds;
18 printf("(a)Vgs = %0.0 f V\n",Vgs);
19 printf("Vds=6V>Vgs-Vt=5V\n");
20 Id=K*(Vgs-Vt)^2;
21 Rd=(Vdd-Vds)/Id;
22 printf("(b)Id = %0.0 e A\n",Id);
23 printf("(c)Rd = %0.0 f ohms",Rd);
24
25 // Result
26 // (a) Vgs = 6 V
27 // (b) Id = 5 mA
28 // (c) Rd = 800 ohms

```

---

**Scilab code Exa 6.14** Find operating region Vgs Vds Rd

```

1 // Find operating region ,Vgs,Vds,Rd
2 // Basic Electronics
3 // By Debashis De

```



```

4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-14 in page 288
7
8 clear; clc; close;
9
10 // Given data
11 K=0.2*10^-3; // Constant in mA/V^2
12 Vt=1; // Given voltage in V
13 Vdd=10; // Drain voltage in V
14 Id=3.2*10^-3; // Drain current in mA
15
16 // Calculation
17 printf("Vds=Vgs>Vgs-Vt=Active region operation\n");
18 Vgs=Vt+sqrt(Id/K);
19 Vds=Vgs;
20 Rd=(Vdd-Vds)/Id;
21 printf("(a) Vgs = %0.0 f V,\n(b) Vds = %0.0 f V,\n(c) Rd
    = %0.2 e ohm" ,Vgs ,Vds ,Rd);
22
23 // Result
24 // (a) Vgs = 5 V
25 // (b) Vds = 5 V
26 // (c) Rd = 1.56 K-ohms

```

---

**Scilab code Exa 6.15** Find Id when Vgs equals 4V

```

1 // Find Id when Vgs=4V
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-15 in page 288

```

```

7
8 clear; clc; close;
9
10 // Given data
11 K=0.15*10^-3; // Constant in mA/V^2
12 Vt=2; // Given voltage in V
13 Vdd=12; // Drain voltage in V
14 Vgs=4; // Gate-source voltage in V
15
16 // Calculation
17 Vgg=sqrt(5.4/0.15)+2;
18 Id=K*(Vgs-Vt)^2;
19 printf("(a)Vgg = %0.0f V,\n(b)Id = %0.1e A",Vgg,Id);
20
21 // Result
22 // (a) Vgg = 8 V
23 // (b) Id = 0.6 mA

```

---

#### Scilab code Exa 6.16 Determine Rd

```

1 // Determine Rd
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-16 in page 289
7
8 clear; clc; close;
9
10 // Given data
11 K=0.25*10^-3; // Constant in mA/V^2
12 Vt=2; // Voltage given in V
13 Vdd=16; // Drain voltage in V

```

```

14 Vgg=[4 10]; // Gate voltage values in V
15
16 // Calculation
17 for i=1:2
18     id=K*(Vgg(i)-2)^2;
19     rd=(16-(Vgg(i)-2))/id;
20     printf("Rd when Vgg is %d V = %0.1e ohm\n",Vgg(i)
21         ),rd);
22
23 // Result
24 // (a) Rd = 14 K-ohm
25 // (b) 500 ohm

```

---

#### Scilab code Exa 6.17 Determine Rd

```

1 // Determine Rd
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-17 in page 289
7
8 clear; clc; close;
9
10 // Given data
11 K=0.25*10^-3; // Constant in mA/V^2;
12 Vt=2; // Given voltage in V
13 Rd=1*10^3; // Drain resistance in ohms
14 Vdd=16; // Drain voltage in V
15 Vgg=4; // Gate voltage in V
16
17 // Calculation

```

```

18 id=K*(4-Vt)^2;
19 Vd=(-1*10^3*id)+16;
20 printf("(a)Id = %0.0e A,\n(b)Vd = %0.0f V\n",id,Vd);
21 printf("Since Vds=15>Vgs-Vt=2,active region
    operation is confirmed");
22
23 // Result
24 // (a) Id = 1 mA
25 // (b) Vds = 15 V

```

---

#### Scilab code Exa 6.18 Find Id Vds1 Vds2

```

1 // Find Id,Vds1,Vds2
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-18 in page 289
7
8 clear; clc; close;
9
10 // Given data
11 Ids1=8*10^-3; // Drain-source current of M1 in mA
12 Vp=-4; // Peak voltage in V
13 Ids2=16*10^-3; // Drain-source current of M2 in mA
14 Vdd=11; // Drain voltage in V
15 Vgg=10; // Gate voltage in V
16
17 // Calculation
18 Id=Ids2;
19 printf("(a)Id = %0.2e A\n",Id);
20 Vds=(28+sqrt(28^2-128))/2;
21 Vds1=(28-sqrt(28^2-128))/2;

```

```

22 printf("(b)Vds1 = %0.2f V, %0.2f V\n",Vds,Vds1);
23 printf("For ohmic operation Vds1 = 1.19 V\n");
24 Vds2=Vdd-1.19;
25 printf("(c)Vds2 = %0.2f V",Vds2);
26
27 // Result
28 // (a) Id = 16 mA
29 // (b) Vds1 = 1.19 V
30 // (c) Vds2 = 9.81 V

```

---

**Scilab code Exa 6.19** Find operating region Vgs Vds Id

```

1 // Find operating region ,Vgs,Vds,Id
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-19 in page 290
7
8 clear; clc; close;
9
10 // Given data
11 Ids = 4*10^-3; // Drain-source current in mA
12 Vp=-4; // Peak voltage in V
13 Vdd=10; // Drain voltage in V
14 Rd=1*10^3; // Drain resistance in K-ohms
15
16 // Calculation
17 printf("(a)Vd=Vgs<Vgs-Vp.Hence ohmic region
    operation is confirmed\n");
18 Vgs1=(-12+sqrt(12^2+160))/2;
19 Vgs2=(-12-sqrt(12^2+160))/2;
20 printf("(b)Vgs = %0.2f V,%0.2f V\n",Vgs1,Vgs2);

```

```

21 Vds=Vgs1;
22 id=(10-Vds)/(1*10^3);
23 printf("(c)Vds = %0.2f V,\n(d)Id = %0.2e A",Vds,id);
24
25 // Result
26 // (a) Ohmic region operation is confirmed
27 // (b) Vgs = 2.72V
28 // (c) Vds = 2.72V
29 // (d) Id = 7.28mA

```

---

#### Scilab code Exa 6.20 Find Vgs Id operating region

```

1 // Find Vgs,Id,operating region
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-20 in page 290
7
8 clear; clc; close;
9
10 // Given data
11 Ids=4*10^-3; // Drain-source current in mA
12 Vp=-4; // Peak voltage in V
13 Vdd=10; // Drain voltage in V
14 Vds=6; // Drain-source voltage in V
15
16 // Calculation
17 Vgs=Vds;
18 printf("(a)Vgs = %0.0f V\n",Vgs);
19 printf("(b)Vds=Vgs<Vgs-Vp.Hence ohmic region
    operation\n");
20 Id=4*10^-3*((2*(5/2)*(3/2))-(9/4));

```

```

21 printf("(c) Id = %0.1e A", Id);
22
23 // Result
24 // (a) Vgs = 6 V
25 // Ohmic region operation is confirmed
26 // (c) Id = 21 mA

```

---

**Scilab code Exa 6.21** Find operating region Vgs Vds Id

```

1 // Find operating region , Vgs, Vds, Id
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 6-21 in page 290
7
8 clear; clc; close;
9
10 // Given data
11 K=0.2*10^-3; // Constant in mA/V^2
12 Vt=1; // Voltage in V
13 Vdd=10; // Drain voltage in V
14 Rd=1*10^3; // Drain resistance in ohms
15
16 // Calculation
17 printf("(a) Vds=Vgs>Vgs-Vt. Hence active region
    operation\n");
18 printf("0.2*Vgs^2+0.6*Vgs-9.8=0\n");
19 Vgs1=(-0.6+sqrt(0.6^2-4*0.2*-9.8))/(2*0.2);
20 Vgs2=(-0.6-sqrt(0.6^2-4*0.2*-9.8))/(2*0.2);
21 printf("(b) Vgs = %0.2f V or %0.2f V\n", Vgs1, Vgs2);
22 printf("Since 0<Vgs<10, Vgs = %0.2f V\n", Vgs1);
23 Id=(Vdd-5.66)/Rd;

```

```
24 printf("(c)Vds = Vgs = 5.66 V\n(d)Id = %0.2e A",Id);
25
26 //Result
27 // (a) The region of operation is active
28 // (b) Vgs = 5.66 V
29 // (c) Vds = 5.66 V
30 // (c) Id = 4.34 mA
```

---



# Chapter 7

## FET Circuits

Scilab code Exa 7.2 Find amplification

```
1 // Find amplification
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-2 in page 312
7
8 clear; clc; close;
9
10 // Given data
11 mu=30; // FET parameter
12 rd=5; // FET parameter
13 Rd=10; // FET parameter value in ohms
14 R=50; // Resistor value in ohms
15
16 // Calculation
17 Av=(-299/50)/((1/rd)+(1/Rd)+(1/R));
18 printf("Amplification Av = %0.1f",Av);
19
20 // Result
21 // Av = -18.7
```

---

**Scilab code Exa 7.3** Find amplification with 40k resistor instead

```
1 // Find amplification with 40k resistor instead
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-3 in page 313
7
8 clear; clc; close;
9
10 // Given data
11 Av=-18.7; // Amplification from prev problem
12 R1=2.54; // Resistance value in ohms
13 R=40; // Load resistor in K-ohms
14
15 // Calculation
16 Avs=(Av)*(R1/(R1+R));
17 printf(" Amplification Avs = %0.2 f" ,Avs);
18
19 // Result
20 // Avs = -1.11
```

---

**Scilab code Exa 7.6** Find gain if v2 v1 are zero

```
1 // Find gain if v2,v1 are zero
2 // Basic Electronics
```

```

3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-6 in page 315
7
8 clear; clc; close;
9
10 // Given data
11 mu=30; // FET parameter
12 rd=15; // Resistance value in k-ohms
13 Rd=1; // Drain resistance value in k-ohms
14 Rs=0.5; // Source resistance in k-ohms
15
16 // Calculation
17 Av1=(-mu*(rd+Rd))/(Rd+((mu+1)^2*Rs)+((mu+2)*rd));
18 Av2=((mu/(mu+1))*(((mu+1)*Rs)+rd))/(((Rd+rd)/(mu+1))
    +((mu+1)*Rs)+rd);
19 printf("(a)Av when v2 is zero = %0.3f\n",Av1);
20 printf("(b)Av when v1 is zero = %0.3f",Av2);
21
22 // Result
23 // (a) Av1 = -0.499
24 // (b) Av2 = 0.952

```

---

**Scilab code Exa 7.11** Find voltage gain output impedance

```

1 // Find voltage gain ,output impedance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-11 in page 320
7

```

```

8  clear; clc; close;
9
10 // Given data
11 // The Thevenin equivalent of fig. is derived
12
13 // Calculation
14 A=(9.5*10)/(10+20);
15 R_0=(1/(10*10^3))+1/(20*10^3);
16 R=1/R_0;
17 printf("(a) Voltage gain = %0.2f\n",A);
18 printf("(b) Output impedance = %0.2e",R);
19
20 // Result
21 // (a) A = 3.17
22 // (b) R_0 = 6.67 K

```

---

**Scilab code Exa 7.12** Find voltage gain A1 and A2

```

1 // Find voltage gain A1 and A2
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-12 in page 321
7
8 clear; clc; close;
9
10 // Given data
11 Rd=30*10^3; // Drain resistance in K-ohm
12 Rs=2*10^3; // Source resistance in K-ohm
13 mu=19; // Constant for FET
14 rd=10*10^3; // Dynamic resistance in K-ohm
15

```

```

16 // Calculation
17 A1=(-mu*(Rd+rd+((mu+1)*Rs))*Rd)/((rd+Rd)*(Rd+rd+(2*(
    mu+1)*Rs)));
18 A2=(mu*(mu+1)*Rs*Rd)/((rd+Rd)*(Rd+rd+(2*(mu+1)*Rs)))
    ;
19 printf("(a)For the given values of Rd,Rs,rd and mu
    we have:\n");
20 printf("A1 = %0.2 f\nA2 = %0.2 f\n\n",A1,A2);
21 printf("(b) If Rs—>infinity ,\n");
22 A_1=(-mu*Rd)/(2*(rd+Rd));
23 printf("A1 = %0.2 f = -A2\nOr A1 = -A2 = %0.2 f",A_1,
    A_1);
24
25 // Result
26 // (a) A1 = -9.5; A2 = 4.75
27 // (b) A1 = -A2 = -7.13

```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

### Scilab code Exa 7.13 Determine Vgs Id Vds Av

```

1 // Determine Vgs,Id,Vds,Av
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-13 in page 322
7
8 clear; clc; close;
9
10 // Given data
11 Rd=12; // Drain resistance in K-ohms

```

```

12 Rg=1; // Gate resistance in M-ohms
13 Rs=0.47; // Source resistance in ohms
14 Vdd=30; // Drain voltage in volts
15 Ids=3*10^-3; // Drain-source current in mA
16
17 // Calculation
18 printf("Vgs=-1.41* (1+ 2Vgs/2.4 + Vgs^2/2.4)\n");
19 Vgs1=(-1.175+sqrt(1.175^2-4*0.245*1.41))/(2*0.245);
20 Vgs2=(-1.175-sqrt(1.175^2-4*0.245*1.41))/(2*0.245);
21 printf("(a)Upon solving we get Vgs = %0.3f V or %0.3
    f V\n",Vgs1,Vgs2);
22 Id=3*(1-(2.398/2.4))^2;
23 Vds=Vdd-Id*(Rd+Rs);
24 gm=((2*Ids)/2.4)*(1-(2.398/2.4));
25 Av=gm*12;
26 printf("(b)Drain current Ids = %0.1e A\n",Id);
27 printf("(c)Vds = %0.2f V\n",Vds);
28 printf("(d)Small signal voltage gain Av = %0.2e",Av)
    ;
29
30 // Result
31 // (a) Vgs = -2.398 V
32 // (b) Ids = 2.1*10^-6 A
33 // (c) Vds = 30 V
34 // (d) Av = 2.5*10^-5

```

---

**Scilab code Exa 7.14** Find the value of R1

```

1 // Find the value of R1
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India

```

```

6 // Example 7-14 in page 322
7
8 clear; clc; close;
9
10 // Given data
11 Idss=2*10^-3; // Drain-source current in mA
12 Vp=-1; // Voltage in volts
13 Rd=56*10^3; // Drain resistance in K-ohms
14 Vdn=10; // Drain to ground voltage in volts
15 Vdd=24; // Drain voltage in volts
16
17 // Calculation
18 Id=(Vdd-Vdn)/Rd;
19 Vgs=-0.65;
20 R1=-Vgs/Id;
21 printf("R1 = %0.1e ohms",R1);
22
23 // Result
24 // R1 = 2.6 K-ohms

```

---

**Scilab code Exa 7.15** Find  $V_o$  for given  $V_i$

```

1 // Find Vo for given Vi
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-15 in page 323
7
8 clear; clc; close;
9
10 // Given data
11 Idss=5.6*10^-3; // Drain-source current in mA

```

```

12 Vp=-4; // Peak voltage in V
13 Vi=[0 10]; // Input voltage values in V
14
15 // Calculation
16 alp=[1 2];
17 for i=1:2
18     Vg=(-2.8+sqrt(2.8^2-(4*0.35*5.6)))/(2*0.35);
19     Id=(Vi(i)+12-Vg)/10;
20     Vo=(10*Id)-12;
21     printf("(%.0f) For Vi = %d V, Vo = %.1f V\n",
22         alp(i),Vi(i),Vo);
23 end
24 printf(" If Vo = 0,\n");
25 Vgs=4*(sqrt(0.214)-1);
26 printf("(3) Then Vi = Vgs = %.2f V",Vgs);
27 // Result
28 // When Vi=0,V0=4V
29 // When Vi=10,V0=14V
30 // When Vo=0,Vi=-2.15V

```

---

**Scilab code Exa 7.16** Calculate quiescent values of Id Vgs Vds

```

1 // Calculate quiescent values of Id ,Vgs ,Vds
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-16 in page 324
7
8 clear; clc; close;
9
10 // Given data

```



```

11 // We find Thevenins equivalent to the left of the
    gate
12
13 // Calculation
14 Rth=(1/(200*10^3))+(1/(1.3*10^6));
15 A=1/Rth;
16 Vth=(200/1500)*60;
17 printf("(a)Rth = %0.3e ohms and Vth = %0.0f V\n",A,
    Vth);
18 Vgs=(8+sqrt(8^2-(4*16)))/2;
19 Id=-2-(Vgs/4);
20 printf("(b)Vgs = %0.0f V and Id = %0.2f mA\n",Vgs,Id
    );
21 Vds=-60+((18+4)*2.25);
22 printf("(c)Vds = %0.1f V",Vds);
23
24 // Result
25 // (a) Id = -3 mA
26 // (b) Vgs = 4 V
27 // (c) Vds = -10.5 V

```

---

**Scilab code Exa 7.20** Calculate transconductance amplification factor

```

1 // Calculate transconductance , amplification factor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-20 in page 328
7
8 clear; clc; close;
9
10 // Given data

```

```

11 Id=2*10^-3; // Drain current in mA
12 Vgs=2; // Gate-source voltage in V
13 Rd=200*10^3; // Drain resistance in K-ohms
14
15 // Calculation
16 gm=Id/Vgs;
17 mu=gm*Rd;
18 printf("(a) Transconductance gm = %0.0e A/V\n",gm);
19 printf("(b) Amplification factor mu = %0.0f",mu);
20
21 // Result
22 // (a) gm = 1 mA/V
23 // (b) mu = 200

```

---

**Scilab code Exa 7.21** Calculate dynamic resistance

```

1 // Calculate dynamic resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-21 in page 328
7
8 clear; clc; close;
9
10 // Given data
11 mu=80; // Amplification factor
12 gm=400*10^-6; // Transconductance in micro-mho
13
14 // Calculation
15 rd=mu/gm;
16 printf("Dynamic resistance Rd = %0.1e ohm",rd);
17

```

```
18 // Result
19 // Rd = 0.2*10^6 ohm
```

---

### Scilab code Exa 7.22 Calculate Rd gm mu

```
1 // Calculate Rd, gm, mu
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-22 in page 329
7
8 clear; clc; close;
9
10 // Given data
11 Vds1=6; // Drain-source voltage when Vgs is zero
12 Vds2=16; // Drain-source voltage when Vgs is 0.3
13 Id1=12*10^-3; // Drain current in mA when Vgs is
    zero
14 Id2=12.3*10^-3; // Drain current in mA when Vgs is
    zero
15
16 // Calculation
17 rd=(Vds2-Vds1)/(Id2-Id1);
18 gm=(Id2-Id1)/(0-0.3*10^-3);
19 mu=-gm*rd*10^-4;
20 printf("(a) Drain resistance Rd = %0.2e ohms\n", rd);
21 printf("(b) Transconductance gm = %0.0f (neglecting
    the sign)\n", -gm);
22 printf("(c) Amplification factor mu = %0.2f", mu);
23
24 // Result
25 // (a) Rd = 33.33k-ohms
```

```
26 // (b) gm = 1
27 // (c) mu = 3.33
```

---

**Scilab code Exa 7.23** Find the value of Rs

```
1 // Find the value of Rs
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-23 in page 329
7
8 clear; clc; close;
9
10 // Given data
11 Vgs=1.5; // Gate-source voltage in V
12 Id=2*10^-3; // Drain saturation current in mA
13
14 // Calculation
15 Rs=Vgs/Id;
16 printf("Rs = %0.0 f ohm" ,Rs);
17
18 // Result
19 // Rs = 750 ohm
```

---

**Scilab code Exa 7.24** Find voltage gain of amplifier

```
1 // Find voltage gain of amplifier
2 // Basic Electronics
```

```

3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-24 in page 329
7
8 clear; clc; close;
9
10 // Given data
11 R1=250; // Load resistance in k-ohms
12 gm=0.5; // Transconductance in mA/V
13 rd=200; // Dynamic resistance in k-ohms
14
15 // Calculation
16 mu=rd*gm;
17 Av=(-mu*R1)/(rd+R1);
18 printf("Voltage gain Av = %0.2 f" ,Av);
19
20 // Result
21 // Voltage gain Av = -55.55

```

---

**Scilab code Exa 7.25** Find pinch off voltage

```

1 // Find pinch off voltage
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-25 in page 330
7
8 clear; clc; close;
9
10 // Given data
11 Idss=10; // Drain-source current in mA

```

```

12 Vp=-4; // Original pinch off voltage in V
13 Vgs=-2; // Gate-source voltage in V
14 gm=4; // Transcondonductance in m-mho
15
16 // Calculation
17 Ids=Idss*(1-(Vgs/Vp))^2;
18 A=(-2*Ids)/gm;
19 printf("Pinch off voltage Vp = %0.0 f V",A);
20
21 // Result
22 // Vp at gm = 4 m-mho is -1V

```

---

**Scilab code Exa 7.26** Calculate quiescent values of Id Vds Vgs

```

1 // Calculate quiescent values of Id ,Vds ,Vgs
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-26 in page 330
7
8 clear; clc; close;
9
10 // Given data
11 Ids=20*10^-3; // Drain-souce current in mA
12 Vp=-4; // Pinch off voltage in volts
13
14 // Calculation
15 printf("We get the equation:\n0.3125*Id^2-6*Id+20=0\n");
16 Id1=(6+sqrt(6^2-4*0.3125*20))/(2*0.3125);
17 Id2=(6-sqrt(6^2-4*0.3125*20))/(2*0.3125);
18 printf("Id = %0.1 f mA and %0.1 f mA\n",Id1,Id2);

```

```

19 printf("We consider only %0.1f mA\n", Id2);
20 Vgs=-Id2*0.5;
21 Vds=30-(Id2*(5+0.5));
22 printf("Vgs = %0.2f V\n(c)Vds = %0.2f V", Vgs, Vds);
23
24 // Result
25 // Id = 4.3 mA
26 // Vgs = -2.15 V
27 // Vds = 6.35 V

```

---

#### Scilab code Exa 7.27 Find Id Vds Vgs Av

```

1 // Find Id, Vds, Vgs, Av
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-27 in page 331
7
8 clear; clc; close;
9
10 // Given data
11 Idss=3; // Drain-source current in mA
12 Vp=-2.4; // Pinch off voltage in volts
13
14 // Calculation
15 printf("Id^2-6.73*Id+5.76=0\n");
16 Id1=(6.73+sqrt(6.73^2-4*1*5.76))/2;
17 Id2=(6.73-sqrt(6.73^2-4*1*5.76))/2;
18 printf("Id = %0.2f mA or %0.2f mA\n", Id1, Id2);
19 printf("(a)The possible value is 1.01 mA\n");
20 Vgs=-Id2*1;
21 Vds=20-(1.09*(1+10));

```

```

22 printf("Vgs = %0.2 f V\nVds = %0.2 f V\n",Vgs ,Vds);
23 gm=(-2/Vp)*sqrt(Id2*Idss);
24 Av=gm*10;
25 printf("(b) Voltage gain Av = %0.1 f",Av);
26
27 // Result
28 // Id = 1.01 mA
29 // Vgs = -1.01 V
30 // (a) Vds = 8.01 V
31 // (b) Av = 14.5

```

---

#### Scilab code Exa 7.28 Calculate Av Zo Zi

```

1 // Calculate Av,Zo,Zi
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-28 in page 332
7
8 clear; clc; close;
9
10 // Given data
11 Rd=15; // Drain resistance in k-ohms
12 Rg=1; // Gate resistance in M-ohms
13 rd=5; // Dynamic resistance in k-ohms
14 gm=5; // Transconductance in m-mho
15 Vdd=20; // Drain voltage in volts
16
17 // Calculation
18 mu=rd*gm;
19 Av=(mu*Rd)/(rd+Rd);
20 Zo=rd;

```



```

21 Zi=Rg;
22 printf("(a)Av = %0.2 f\n(b)Zo = %0.0 f k-ohms\n(c) Zi =
    %0.0 f M-ohms",Av,Zo,Zi);
23
24 // Result
25 // (a) Av = 18.75
26 // (b) Zo = 5 K-ohms
27 // (c) Zi = 1 M-ohms

```

---

#### Scilab code Exa 7.29 Calculate $V_o$ $V_i$

```

1 // Calculate  $V_o, V_i$ 
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-29 in page 333
7
8 clear; clc; close;
9
10 // Given data
11 Idss=5*10^-3; // Drain-source current in mA
12 Vp=-4.5; // Pinch off voltage in V
13
14 // Calculation
15 printf("When  $V_i$  is zero:\n");
16 Vgs1=(-25.67+sqrt(25.67^2-(4*2.963*55)))/(2*2.963);
17 Vgs2=(-25.67-sqrt(25.67^2-(4*2.963*55)))/(2*2.963);
18 printf("(a)  $V_{gs} = %0.2 f$  V or  $%0.2 f$  V\n",Vgs1,Vgs2);
19 printf("Since the gate is connected to ground,  $V_o = -$ 
     $V_{gs}$ . Hence  $V_o = %0.2 f$  V or  $%0.2 f$  V\n",-Vgs1,-Vgs2)
    ;
20 printf("When  $V_o$  is zero:\n");

```

```

21 Id=5/(12*10^3);
22 Vgs=4.5*(0.288-1);
23 Vi=Vgs;
24 printf("(b)Vi = %0.1 f V",Vi);
25
26 // Result
27 // (a) When Vi is zero , Vo = 4.78V or 3.88V
28 // (b) When Vo is zero , Vi = -3.2V

```

---

#### Scilab code Exa 7.30 Calculate Av Zo

```

1 // Calculate Av,Zo
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-30 in page 334
7
8 clear; clc; close;
9
10 // Given data
11 gm=5; // Transconductance in mA/V
12 rd=10*10^3; // Dynamic resistance in K-ohms
13 mu=50; // Amplification factor
14 Rd=5*10^3; // Drain resistance in K-ohms
15
16 // Calculation
17 Av=(-mu*Rd)/(rd+Rd+((mu+1)*0.1*10^3));
18 Avs=Av*(100/110);
19 Zo=rd+((mu+1)*0.1*10^3);
20 Zo1=(1/15.1)+(1/5);
21 A=1/Zo1;
22 printf("Av = %0.2 f\n",Av);

```

```

23 printf("Over all voltage gain Avs = %0.1f\n",Avs);
24 printf("Output impedance = %0.2e K\n",Zo);
25 printf("Effective output impedance Zo = %0.2f k-ohms
    ",A);
26
27 // Result
28 // (a) Avs = -11.3
29 // (b) Zo = 3.75 K-ohms

```

---

**Scilab code Exa 7.31** Calculate Vgsq gm Rs Vdsq Rl

```

1 // Calculate Vgsq ,gm ,Rs ,Vdsq ,Rl
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-31 in page 335
7
8 clear; clc; close;
9
10 // Given data
11 Vp=-4; // Pinch off voltage in V
12 Idss=1.65*10^-3; // Drain-source current in mA
13 Idq=0.8*10^-3; // Desired operating point of current
    in mA
14 Av=10; // Voltage gain in dB
15
16 // Calculation
17 printf("We know that Id = Idss*(1-(Vgs/Vp))^2\n");
18 Vgs=4*(sqrt(0.485)-1);
19 gmo=(-2*Idss)/Vp;
20 gm=gmo*(1-(Vgs/Vp));
21 Rs=Vgs/-Idq;

```

```

22 Rl=Av/gm;
23 Vds=24-(Idq*Rl)-(Idq*Rs);
24 printf("(a)Vgsq = %0.3 f V\n(b)gm = %0.3 e A/V\n(c)Rs
    = %0.3 e ohms\n(d)Rl = %0.2 e ohms\n(e)Vds = %0.3 f
    V\n",Vgs, gm, Rs, Rl, Vds);
25 printf("Therefore, \n(e)Vdsq = 16.48 V");
26
27 // Result
28 // (a) Vgsq = -1.214 V
29 // (b) gm = 0.575 mA/V
30 // (c) Rs = 1.518 K-ohm
31 // (d) Rl = 17.4 K-ohm
32 // (e) Vdsq = 16.48 V

```

---

**Scilab code Exa 7.32** Calculate  $Z_o$  for  $r_d$  equals 50 k ohms

```

1 // Calculate Zo for rd=50k-ohms
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-32 in page 337
7
8 clear; clc; close;
9
10 // Given data
11 rd=50*10^3; // Dynamic resistance in K-ohms
12 Rd=20*10^3; // Drain resistance in K-ohms
13
14 // Calculation
15 Zo=(rd*Rd)/(rd+Rd);
16 printf("Output impedance Zo = %0.3 e ohms",Zo);
17

```

```
18 // Result
19 // Zo = 14.28 K-ohms
```

---

**Scilab code Exa 7.33** Find voltage gain Current gain ratio

```
1 // Find voltage gain ,Current gain ratio
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-33 in page 337
7
8 clear; clc; close;
9
10 // Given data
11 Rd=5*10^3; // Drain resistance in K-ohms
12 Rg=500*10^3; // Gate resistance in K-ohms
13 mu=60; // Amplification factor
14 rds=30*10^3; // Dynamic resistance in K-ohms
15
16 // Calculation
17 Av=(mu*Rd)/(Rd+rds);
18 Ai=(mu*Rg)/(rds+Rd);
19 printf("(a) Voltage gain Av = %0.2 f\n(b) Current gain
    Ai = %0.2 f", Av, Ai);
20
21 // Reuslt
22 // (a) Av = 8.57
23 // (b) Ai = 857.14
```

---

**Scilab code Exa 7.34** Determine  $Z_o$  draw small signal model

```
1 // Determine  $Z_o$ , draw small signal model
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-34 in page 338
7
8 clear; clc; close;
9
10 // Given data
11 gm=1; // Transconductance in m-mho
12 rd=50*103; // Dynamic resistance in K-ohms
13 Rd=5*103; // Drain resistance in K-ohms
14
15 // Calculation
16 printf("The equivalent circuit at low-frequency
    small signal model is as shown in the figure\n");
17 Zo=(rd*Rd)/(Rd+rd);
18 printf("Zo = %0.2e ohms", Zo);
19
20 // Result
21 // Zo = 4.54 K-ohms
```

---

This code can be downloaded from the website [www.scilab.in](http://www.scilab.in)

**Scilab code Exa 7.35** Find values of R2 Vdd Vds

```
1 // Find values of R2,Vdd,Vds
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-35 in page 338
7
8 clear; clc; close;
9
10 // Given data
11 Vp=-5; // Pinch off voltage in V
12 Idss=12*10^-3; // Drain-source current in mA
13 Vdd=18; // Drain voltage in V
14 Rs=2*10^3; // Source resistance in K-ohms
15 Rd=2*10^3; // Drain resistance in K-ohms
16 R2=90*10^3; // Original value of R2 in K-ohms
17
18 // Calculation
19 Vgs1=(-5.3+sqrt(5.3^2-(4*0.48*10.35)))/(2*0.48);
20 Vgs2=(-5.3-sqrt(5.3^2-(4*0.48*10.35)))/(2*0.48);
21 printf("Vgs = %0.2f V or %0.2f V\nTherefore Vgs =
    -2.53 V\n",Vgs1,Vgs2);
22 Id=(3.306-Vgs2)/2;
23 Vds=18-(Id*Rd)-(Id*Rs);
24 r2=(13.47*400)/4.53;
25 vdd=((16-2.53)*(400+90))/90;
26 vds=vdd-16-16;
27 printf("(a)The new value of R2 is %0.1f K-ohm\n",r2)
    ;
28 printf("(b)The new value of Vdd = %0.2f V\n",vdd);
29 printf("(c)The new value of Vds = %0.2f V",vds);
30
31 // Result
32 // (a) R2 = 1189.4 K-ohm
33 // (b) Vdd = 73.34 V
34 // (c) Vds = 41.34 V
```

---

**Scilab code Exa 7.36** Equation for drain current

```
1 // Equation for drain current
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-36 in page 340
7
8 clear; clc; close;
9
10 // Given
11 Idss=12; // Drain source current in mA
12 Vgs=-5; // Gate source voltage in V when off
13
14 // Calculation
15 printf("Equation for drain current: Id = %0.0f*(1-(
    Vgs/%0.0f))^2", Idss, Vgs);
16 x=[-5 -4 -3 -2 -1 0];
17 y=[12 11 10 9 8 7 6 5 4 3 2 1 0];
18 y=12*(1+(x/5))^2;
19 plot(x,y);
20 xlabel('Vgs');
21 ylabel('Id');
22 title('Transfer characteristics of FET');
23
24 // Result
25 // Graph shows the transfer characteristics of FET
    for the given values
26 // Set axis properties to 'origin' to view graph
    correctly
```

---



**Scilab code Exa 7.37** Find  $V_{gs}$   $V_p$

```
1 // Find  $V_{gs}, V_p$ 
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-37 in page 340
7
8 clear; clc; close;
9
10 // Given data
11 Idss=12; // Drain-source current in mA
12 Vgs_off=-6; // Gate-source voltage when FET is off
13
14 // Calculation
15 Vgs=6*(sqrt(5/12)-1);
16 Vp=Vgs_off;
17 printf("(a)  $V_{gs} = %0.2f$  V\n(b)  $V_p = -V_{gs}(\text{off}) = 6V$ ",
18         Vgs);
19
20 // Result
21 // (a)  $V_{gs} = -2.13$  V
22 // (b)  $V_p = 6$  V
```

---

**Scilab code Exa 7.38** Find the values of  $R_s$  and  $R_d$

```
1 // Find the values of  $R_s$  and  $R_d$ 
```

```

2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-38 in page 341
7
8 clear; clc; close;
9
10 // Given data
11 Id=1.5*10^-3; // Drain current in mA
12 Vds=10; // Drain-source voltage in V
13 Idss=5*10^-3; // Drain-source current in mA
14 Vp=-2; // Pinch off voltage in V
15 Vdd=20; // Drain voltage in V
16
17 // Calculation
18 Vgs=2*(sqrt(1.5/5)-1);
19 Vs=-Vgs;
20 Rs=Vs/Id;
21 Rd=(20-10.9)/Id;
22 printf("Rs = %0.1e ohms\nRd = %0.2e ohms",Rs,Rd);
23
24 // Result
25 // Rs = 0.6 K-ohms
26 // Rd = 6.06 K-ohms

```

---

**Scilab code Exa 7.39** Find the value of Rs

```

1 // Find the value of Rs
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India

```

```

6 // Example 7-39 in page 341
7
8 clear; clc; close;
9
10 // Given data
11 Id=2.5*10^-3; // Drain current in mA
12 Vds=8; // Drain-source voltage in V
13 Vdd=30; // Drain voltage in V
14 R1=1*10^6; // R1 value in M-ohms
15 R2=500*10^3; // R2 value in K-ohms
16 Idss=15*10^-3; // Drain-source current in mA
17 Vp=-5; // Pinch off voltage in volts
18
19 // Calculation
20 Vgs=5*(sqrt(5/30)-1);
21 V2=(Vdd*R2)/(R1+R2);
22 Rs=(V2-Vgs)/Id;
23 printf("Rs = %0.2e ohms\n",Rs);
24 Rd=(Vdd-Vds-(Id*Rs))/Id;
25 printf("Rd = %0.2e ohms",Rd);
26
27 // Result
28 // Rs = 5.18 K-ohms
29 // Rd = 3.62 K-ohms

```

---

**Scilab code Exa 7.40** Calculate voltage gain Av

```

1 // Calculate voltage gain Av
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-40 in page 342

```

```

7
8 clear; clc; close;
9
10 // Given data
11 gm=2*10^-3; // Transconductance in mA/V
12 rd=10*10^3; // Dynamic resistance in K-ohms
13 Zc=31.83*10^3; // Capacitive impedance in K-ohms
14 Vth=16.67; // Thevenin voltage in V at 1 KHz
15
16 // Calculation
17 R=(rd*25*10^3)/(rd+(25*10^3));
18 Av=-gm*R;
19 printf("(a)Av after neglecting capacitance = %0.2f\n",Av);
20 Rth=(rd*50*10^3)/(rd+50*10^3);
21 Av1=(-50*10^3*Vth)/((50*10^3+Rth)-%i*Zc);
22 printf("(b)Av after considering capacitance = %0.2f",Av1);
23
24 // Result
25 // Av after neglecting capacitance = -14.28
26 // Av after considering capacitance = -11.01

```

---

**Scilab code Exa 7.41** Calculate voltage amplification in circuit

```

1 // Calculate voltage amplification in circuit
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-41 in page 343
7
8 clear; clc; close;

```

```

9
10 // Given data
11 gfs=2*10^-3; // Transconductance in mS
12 Rl=10*10^3; // Load resistance
13
14 // Calculation
15 Av=gfs*Rl;
16 printf("Av = %0.0 f",Av);
17
18 // Result
19 // Av = 20

```

---

**Scilab code Exa 7.43** Find the value of Rs

```

1 // Find the value of Rs
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-43 in page 344
7
8 clear; clc; close;
9
10 // Given data
11 Idss=10*10^-3; // Drain-source current in mA
12 Vp=-5; // Pinch off voltage in V
13
14 // Calculation
15 Vgs = 5*(sqrt(6.4/10)-1);
16 Rs=-Vgs/(6.4*10^-3);
17 printf("Rs = %0.0 f ohms",Rs);
18
19 // Result

```

20 // Rs = 156 ohms

---

**Scilab code Exa 7.44** Calculate value of Id Vgs Vds

```
1 // Calculate value of Id ,Vgs ,Vds
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-44 in page 345
7
8 clear; clc; close;
9
10 // Given data
11 Idss=4*10^-3; // Drain-source current in mA
12 Vp=4; // Pinch off voltage in V
13
14 // Calculation
15 Rth=(200*10^3*1.3*10^6)/((200*10^3)+(1.3*10^6));
16 Vth=(200/1500)*(1-60);
17 Vgs=1;
18 Id=(-8-Vgs)/4;
19 Vds=-60-((18+4)*Id);
20 printf(" Id = %0.2 f mA\nVgs = %0.0 f V\nVds = %0.1 f V"
        ,Id ,Vgs ,Vds);
21
22 // Result
23 // Vgs = 1 V
24 // Vds = -10.5 V
25 // Id = -2.25 mA
```

---

### Scilab code Exa 7.45 Calculate input admittance

```
1 // Calculate input admittance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-45 in page 348
7
8 clear; clc; close;
9
10 // Given data
11 mu=20; // Amplification factor
12 rd=10*10^3; // Dynamic resistance in K-ohms
13 gm=2*10^-3; // Transconductance in mA/V
14 Cgs=3*10^-12; // Gate-source capacitance in pF
15 Cds=1*10^-12; // Drain-source capacitance in pF
16 Cgd=2*10^-12; // Gate-drain capacitance in pF
17
18 // Calculation
19 printf("(a)Rd = 50 K\n");
20 printf("At f=1000Hz\n");
21 Ygs=%i*2*%pi*10^3*Cgs;
22 Yds=%i*2*%pi*10^3*Cds;
23 Ygd=%i*2*%pi*10^3*Cgd;
24 Yd=2*10^-6;
25 gd=10^-4;
26 Av=(-gm+Ygd)/(gd+Yd+Yds+Ygs);
27 C1=Cgs+(17.7*Cgd);
28 printf("Av = %0.1 f\nC1 = %0.1 e F\n\n",Av,C1);
29 printf("At f=10^6Hz\n");
30 Ygs1=%i*1.88*10^-6;
```

```

31 Yds1=%i*0.628*10^-6;
32 Ygd1=%i*1.26*10^-6;
33 Av1=(-gm+Ygd1)/(gd+Yd+Yds+Ygs);
34 R1=10^6/2.48;
35 C2=37.6*10^-12;
36 printf("Av = %0.1f\nR1 = %0.2e ohm\nC1=%0.1e F\n\n",
    Av1,R1,C2);
37 Z1=%i*5*10^4;
38 Y1=%i*2*10^-6;
39 printf("(b) Z1 = j5*10^4;Y1 = j2*10^-6\n");
40 printf("For f=1000Hz\n");
41 Av2=-gm/(gd+Y1);
42 C3=Cgs+(20.2*Cgd);
43 R2=20.8*10^6;
44 printf("Av = %0.2f\nR1 = %0.2e ohm\nC1 = %0.1e F\n\n",
    Av2,R2,C3);
45 printf("For f=10^6Hz\n");
46 Av3=(-200+(%i*1.26))/(10+(%i*3.88));
47 C4=Cgs+(18.4*Cgd);
48 R3=10^6/8.64;
49 printf("Av = %0.2f\nR1 = %0.2e ohm\nC1 = %0.2e F",
    Av3,R3,C4);
50
51 // Result
52 // (a)Rd = 50 K
53 // At f=1000Hz
54 // Av = -19.6
55 // C1 = 3.8e-011 F
56
57 // At f=10^6Hz
58 // Av = -19.6
59 // R1 = 4.03e+005 ohm
60 // C1=3.8e-011 F
61
62 // (b) Z1 = j5*10^4;Y1 = j2*10^-6
63 // For f=1000Hz
64 // Av = -19.99
65 // R1 = 2.08e+007 ohm

```



```

66 // C1 = 4.3e-011 F
67
68 // For f=10^6Hz
69 // Av = -17.34
70 // R1 = 1.16e+005 ohm
71 // C1 = 3.98e-011 F

```

---

**Scilab code Exa 7.47** Calculate gain and frequency

```

1 // Calculate gain and frequency
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-47 in page 351
7
8 clear; clc; close;
9
10 // Given data
11 gm=2*10^-3; // Transconductance in mA/V
12 Rs=100*10^3; // Source resistance in K-ohms
13 rd=50*10^3; // Dynamic resistance in K-ohms
14 Ct=9*10^-12; // Total capacitance in pF
15 gd=2*10^-5; // Constant
16
17 // Calculation
18 omega=(gm+gd)/Ct;
19 f=omega/(2*pi);
20 printf(" (a) f = %0.1e Hz\n",f);
21 Av=gm*Rs/(1+(gm+gd)*Rs);
22 printf(" For f=35.6MHz,\n");
23 Av1=(10^2*(sqrt(4.45)))/(202*sqrt(2));
24 printf(" (b) Av = %0.3 f", Av1);

```

```

25
26 // Result
27 // (a) f = 35.6 MHz
28 // (b) Av = 0.738

```

---

**Scilab code Exa 7.48** Calculate the values of Id Vgs Vds

```

1 // Calculate the values of Id ,Vgs ,Vds
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-48 in page 351
7
8 clear; clc; close;
9
10 // Given data
11 Vp=3; // Pinch off voltage in V
12 // Id = 0.2(Vgs-3)^2
13
14 // Calculation
15 Id1=(25+7)/10;
16 Id2=(25-7)/10;
17 printf("Id = %0.1 f mA or %0.1 f mA\n", Id1, Id2);
18 printf("FET will be cut off at Id=3.2mA.Hence Id=1.8
    mA\n");
19 Vgs=0.5*(30-18);
20 Vds=30-(1.8*10);
21 printf("Vgs = %0.0 f V\nVds = %0.0 f V", Vgs, Vds);
22
23 // Result
24 // Id = 1.8 mA
25 // Vgs = 6 V

```

26 // Vds = 12 V

---

**Scilab code Exa 7.52** Calculate complex voltage gain Input admittance

```
1 // Calculate complex voltage gain, Input admittance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-52 in page 355
7
8 clear; clc; close;
9
10 // Given data
11 mu=100; // Amplification factor
12 rd=40*10^3; // Dynamic resistance in K-ohms
13 gm=2.5*10^-3; // Transconductance in mA/V
14 Cgs=4*10^-12; // Gate-source capacitance in pF
15 Cds=0.6*10^-12; // Drain-source capacitance in pF
16 Cgd=2.4*10^-12; // Gate-drain capacitance in pF
17
18 // Calculation
19 Ygs=%i*2*%pi*10^2*4*10^-12;
20 Yds=%i*2*%pi*10^2*0.6*10^-12;
21 Ygd=%i*2*%pi*10^2*2.4*10^-12;
22 gd=2.5*10^-5;
23 Yd=10^-5;
24 Av=(-2.5/3.5)*10^2;
25 Ci=Cgs+(1-Av)*Cgd;
26 printf("Av = %0.2f\nCi = %0.3e F\n", Av, Ci);
27 printf("For f=10^6 Hz,\n");
28 Ygs1=%i*2.51*10^-6;
29 Yds1=%i*0.377*10^-6;
```

```

30 Ygd=%i*1.51*10^-6;
31 Av=((-2.5*3.5*10^2)/12.30)+%i*((2.5*0.188*10^2)
    /12.30);
32 C1=Cgs+(72*Cgd);
33 G1=2*%pi*2.4*10^-12*3.82;
34 R1=1/G1;
35 printf("Av =");
36 disp(Av);
37 printf("C1 = %0.3e F\nR1 = %0.3e ohms",C1,R1);
38
39 // Result
40 // Av = -71.4
41 // Ci = 177.8 pF
42 // At f=10^6 Hz,
43 // Av = -71.2+j3.82
44 // C1 = 177 pF
45 // R1 = 173.5 K-ohms

```

---

**Scilab code Exa 7.54** Find the maximum transconductance

```

1 // Find the maximum transconductance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-54 in page 358
7
8 clear; clc; close;
9
10 // Given data
11 Idss=1*10^-3; // Drain-source current in mA
12 Vp=-5; // Pinch off voltage in V
13

```

```

14 // Calculation
15 gm=(2*Idss)/-Vp;
16 printf("gm = %0.1e mho",gm);
17
18 // Result
19 // gm = 0.4 m-mho

```

---

#### Scilab code Exa 7.55 Evaluate Vds and Rd

```

1 // Evaluate Vds and Rd
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-55 in page 358
7
8 clear; clc; close;
9
10 // Given data
11 b=10^-4; // Constant in A/V^2
12 Vdd=10; // Drain voltage in V
13 Vt=1; // Voltage expressed in volts
14 Ids=0.5*10^-3; // Drain-source current in mA
15
16 // Calculation
17 Vds=1+sqrt(5);
18 Rd=(Vdd-Vds)/Ids;
19 printf("Vds = Vgs = %0.2f V\nRd = %0.2e ohm",Vds,Rd)
20 ;
21 // Result
22 // Vds = 3.24 V
23 // Rd = 13.5 K-ohm

```

---

**Scilab code Exa 7.56** Verify FET operation in pinch off region

```
1 // Verify FET operation in pinch-off region
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-56 in page 358
7
8 clear; clc; close;
9
10 // Given data
11 Vp=-2; // Pinch off voltage in V
12 Idss=4*10^-3; // Drain-source current in mA
13 Rd=910; // Drain resistance in ohms
14 Rs=3*10^3; // Source resistance in K-ohms
15 R1=12*10^6; // R1 value in M-ohms
16 R2=8.57*10^6; // R2 value in M-ohms
17 Vdd=24; // Drain voltage in V
18
19 // Calculation
20 Vgg = Vdd*R2/(R1+R2);
21 Id1=(73+sqrt(73^2-(4*9*144)))/(2*9);
22 Id2=(73-sqrt(73^2-(4*9*144)))/(2*9);
23 printf("Id = %0.2e A or %0.2e A\n",Id1,Id2);
24 printf("A value of 3.39 mA is selected\n");
25 Vgsq=10-(3.39*10^-3*3*10^3);
26 Vdsq=Vdd-(3.39*10^-3*3.91*10^3);
27 Vdgq=Vdsq-Vgsq;
28 printf("Vgsq = %0.2fV\nVdsq = %0.2fV\nVdgq = %0.3 f V
   \n",Vgsq,Vdsq,Vdgq);
29 printf("Vdgq>Vd.Hence the FET is in the pinch off
```

```

    region");
30
31 // Result
32 // FET operates in the pinch off region

```

---

### Scilab code Exa 7.57 Calculate voltage gain Av

```

1 // Calculate voltage gain Av
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-57 in page 359
7
8 clear; clc; close;
9
10 // Given data
11 gm=2*10^-3; // Transconductance in mA/V
12 rd=10*10^3; // Dynamic resistance in K-ohms
13 C=0.025*10^-6; // Capacitance in microF
14
15 // Calculation
16 Rl=(30*30)/(30+30);
17 Av=(-gm*rd*Rl*10^3)/(Rl+rd);
18 f1=1/(2*pi*37.5*10^3*C);
19 Avl=Av/sqrt(1+(f1/(5*10^3))^2);
20 printf("(a)Av = %0.0 f\n(b)Avl = %0.2 f",Av,Avl);
21
22 // Result
23 // (a) Av = -30
24 // (b) Avl = -29.94

```

---

**Scilab code Exa 7.59** Design a source follower

```
1 // Design a source follower
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 7-59 in page 361
7
8 clear; clc; close;
9
10 // Given data
11 Vds=14; // Drain-source voltage in V
12 Idq=3*10^-3; // Drain-source current in mA
13 Vdd=20; // Drain voltage in V
14 gm=2*10^-3; // Transconductance in mS
15 rd=50*10^3; // Dynamic resistance in K-ohms
16 Vgs=-1.5; // Gate-source voltage in V
17
18 // Calculation
19 R=(20-14)/Idq;
20 R1=Vgs/-Idq;
21 R2=R-R1;
22 Ro=1/gm;
23 Av=R/(R+Ro);
24 R_1=1/(1-(Av*(R2/R)));
25 printf("R1 = %0.1e ohms\nR2 = %0.1e ohms\nRo = %0.1e
        ohms\n",R1,R2,Ro);
26 printf("Av = %0.1f*Av1\n",Av);
27 printf("Effective input resistance R1 = %0.1f*R3",
        R_1);
28
```



```
29 // Result
30 // R1 = 0.5 K
31 // R2 = 1.5 K
32 // Ro = 0.5 K
33 // Av = 0.8*Av'
34 // R1(effective) = 2.5*R3
```

---

# Chapter 8

## Special Semiconductor Devices

Scilab code Exa 8.1 Calculate the Gate Source Resistance

```
1 // Calculate the Gate Source Resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-1 in page 376
7
8 clear; clc; close;
9
10 // Given Data
11 P=0.5; // Value of Allowable Gate Power Dissipation
    in watt
12 Es=14; // Trigger Source Voltage in V
13 slope=130; // Slope of Gate-Cathode Characteristic
    line
14
15 // Calculations
16 Ig=sqrt(P/slope);
17 Vg=slope*Ig;
18 Rs=(Es-Vg)/Ig;
19
```

```

20 printf("(a)The value of Gate Resistance for the
    Circuit is %0.2e ohm \n",Rs);
21 printf("(b)The value of the Gate Voltage is %0.2e V
    \n",Vg);
22 printf("(c)The value of the Gate Current is %0.2e A
    \n",Ig);
23
24 // Results
25 // (a) The value of Gate Resistance for the Circuit
    is 95.3 ohm
26 // (b) The value of the Gate Voltage is 8.06 V
27 // (c) The value of the Gate Current is 62 mA

```

---

### Scilab code Exa 8.2 Firing angle of Thyristor

```

1 // Firing angle of Thyristor
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-2 in page 377
7
8 clear; clc; close;
9
10 // Given Data
11 Il=50^10*-3; // Latching current of the Thyristor in
    mA
12 t=50^10*-6; // Duration of firing pulse in second
13 Es=50; // DC voltage of the circuit in V
14 R=10; // Resistance of the circuit in ohm
15 L=0.25; // Inductance of the circuit in H
16 e=2.718282; // Constant of calculation
17

```

```

18 // Calculations
19 tou=0.025;
20 i=(Es/R)*(1-exp(-(50*10^-6)/tou));
21 printf("(a) i = %0.3e A\n",i);
22
23 if(i<I1)
24     printf("Since the Gate current is less than
           Latching Current, SCR will not get fired \n");
25 else
26     printf("Since the Gate current is more than
           Latching Current, SCR will get fired \n");
27 end
28
29 // Results
30 // SCR will not get fired in the Circuit

```

---

### Scilab code Exa 8.3 Calculate width of Gating pulse

```

1 // Calculate width of Gating pulse
2 // Basic Electronics
3 // By Debashis De
4 // First Edition, 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-3 in page 377
7
8 clear; clc; close;
9
10 // Given Data
11 I1=4*10^-3; // Latching current of SCR in A
12 V=100; // DC voltage of the circuit in V
13 L=0.1; // Inductance of the circuit in H
14
15 // Calculations

```

```

16 t=(L/V)*I1;
17
18 printf("Required width of the gating pulse is %0.2e
    s",t);
19
20 // Results
21 // Required width of the gating pulse is 4 mu-s

```

---

**Scilab code Exa 8.4** To calculate required Gate source Resistance

```

1 // To calculate required Gate source Resistance
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-4 in page 378
7
8 clear; clc; close;
9
10 // Given Data
11 P=0.012; // Value of Allowable Gate Power
    Dissipation in watt
12 Es=10; // Trigger Source Voltage in V
13 slope=3*10^3; // Slope of Gate-Cathode
    Characteristic line
14
15 // Calculations
16 Ig=sqrt(P/slope);
17 Vg=slope*Ig;
18 Rs=(Es-Vg)/Ig;
19
20 printf("(a)The value of Gate Resistance for the
    Circuit is %0.0f ohm \n",Rs);

```

```

21 printf("(b)The value of the Gate Voltage is %0.2e V
    \n",Vg);
22 printf("(c)The value of the Gate Current is %0.2e A
    \n",Ig);
23
24
25 // Results
26 // (a) The value of Gate Resistance for the Circuit
    is 2 K-ohm
27 // (b) The value of the Gate Voltage is 6 V
28 // (c) The value of the Gate Current is 2 mA

```

---

**Scilab code Exa 8.5** To calculate series Resistance across SCR

```

1 // To calculate series Resistance across SCR
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-5 in page 378
7
8 clear; clc; close;
9
10 // Given Data
11 Ig_min=0.5; // Minimum gate current for quick ON, in
    A
12 Vs=15; // Gate source voltage in V
13 slope=16; // Slope of Gate-Cathode Characteristic
    line
14
15 // Calculations
16 Vg=slope*Ig_min;
17 Rg=(Vs-Vg)/Ig_min;

```

```

18
19 printf("The value of Gate Resistance is %0.2f ohm \n
    ",Rg);
20
21 // Results
22 // The value of Gate Resistance is 14 ohm

```

---

**Scilab code Exa 8.6** To determine critical value of  $dv/dt$

```

1 // To determine critical value of dv/dt
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-6 in page 379
7
8 clear; clc; close;
9
10 // Given Data
11 ij2=32*10^-3; // Limiting value of the charging
    current in A
12 Cj2=40*10^-12; // Capacitance of reverse biased
    junction J2 in F
13
14 // Calculations
15 dv_dt=ij2/Cj2;
16
17 printf("The value of dv/dt of the given SCR is %0.2e
    volt/second \n",dv_dt);
18
19 // Results
20 // The value of dv/dt of the given SCR is 800 V/mu-s

```

---

**Scilab code Exa 8.7** Calculate surge current and I2t ratings

```
1 // Calculate surge current & I2t ratings
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-7 in page 379
7
8 clear; clc; close;
9
10 // Given Data
11 ish=3000; // half cycle surge current rating of SCR
    in A
12 f=50; // Frequency of operation of supply in Hz
13
14 // Calculations
15 I=ish*sqrt(2*f)/sqrt(4*f);
16 I2t_rate=(I*I)/(2*f);
17
18 printf("(a)The surge current rating of one cycle for
    the SCR is %0.2f A \n",I);
19 printf("(b)The I2t rating of one cycle for the SCR
    is %0.2f A^2-second \n",I2t_rate);
20
21 // Results
22 // (a) The surge current rating of one cycle for the
    SCR is 2121.32 A
23 // (b) The I2t rating of one cycle for the SCR is
    45000 A^2-second
```

---



### Scilab code Exa 8.8 Max and Min firing delays

```
1 // Max and Min firing delays
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8–8 in page 386
7
8 clear; clc; close;
9
10 // Given Data
11 Vc=40; // Breakdown voltage of DIAC in V
12 C=470*10^-9; // Capacitance in nF
13 E=240; // Rms voltage at 50 Hz in V
14 omga=2*pi*50; // Angular frequency
15
16 // Calculation
17 printf("When DIAC is not conducting:\n")
18 A=asind(40/335.8)+8.4;
19 Z=1/(omga*C);
20 R1=atand(1/(omga*1000*C));
21 Zd=sqrt(R1^(2+(1/omga^2*C^2)));
22 printf("Minimum delay = %0.2f degrees\n\n",A);
23 printf("When DIAC conducts:\n");
24 A1=asind(40/88.6)+74.84;
25 printf("Maximum delay = %0.2f degrees",A1);
26
27 // Result
28 // Minimum delay = 15.24 degrees
29 // Maximum delay = 101.6 degrees
```

---

**Scilab code Exa 8.10** Design of Triggering Circuit for a UJT

```
1 // Design of Triggering Circuit for a UJT
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-10 in page 390
7
8 clear; clc; close;
9
10 // Given Data
11 Vs=30; // DC source voltage in V
12 eta=0.51; // Intrinsic stand off ratio
13 Ip=10*10^-6; // Peak Emitter current of UJT in mu-A
14 Vv=3.5; // Valley voltage in V
15 Iv=10*10^-3; // Valley current in A
16 f=60; // Source frequency in Hz
17 tg=50*10^-6; // width of triggering pulse in seconds
18 C=0.5*10^-6; // Assumption for circuit Capacitance
    in mu-F
19 Vd=0.5; // Fixed value of Vb in V
20
21 // Calculations
22 Vp=(eta*Vs)+Vd;
23 Rlow=(Vs-Vp)/Ip;
24 Rup=(Vs-Vv)/Iv;
25 tou=1/f;
26 R=(tou/C)*(1/log(1/(1-eta)));
27 Rb1=tg/C;
28 Rb2=10^4/(eta*Vs);
29
```

```

30 printf("(a)The value of Base-1 Resistance of UJT is
    %0.2f ohm \n",Rb1);
31 printf("(b)The value of Base-2 Resistance of UJT is
    %0.2f ohm \n",Rb2);
32 printf("(c)Circuit resistance of the arrangement is
    %0.2e ohm \n",R);
33
34 // Results
35 // (a) The value of Base-1 Resistance of UJT is 100
    ohm
36 // (b) The value of Base-2 Resistance of UJT is 654
    ohm
37 // (c) Circuit resistance of the arrangement is 46.7
    K-ohm

```

---

**Scilab code Exa 8.11** To determine Emitter source voltage of UJT

```

1 // To determine Emitter source voltage of UJT
2 // Basic Electronics
3 // By Debashis De
4 // First Edition , 2010
5 // Dorling Kindersley Pvt. Ltd. India
6 // Example 8-11 in page 391
7
8 clear; clc; close;
9
10 // Given Data
11 Re=1*10^3; // Emitter Resistance of UJT in ohm
12 Iv=5*10^-3; // Valley current of UJT in A
13 Vv=2; // Valley voltage of UJT in V
14
15 // Calculations
16 Ve=Vv;

```

```
17 Ie=Iv;
18 Vee=(Ie*Re)+Ve;
19
20 printf("The value of Emitter source voltage of UJT
    for turn-off is %0.2f V",Vee);
21
22 // Results
23 // The value of Emitter source voltage of UJT for
    turn-off is 7 V
```

---