

Scilab Textbook Companion for
Schaum's Outlines Of Electronic Devices And
Circuits
by J. J. Cathey¹

Created by
Mayur Ganesh Sabban
B.Tech
Electronics Engineering
Vishwakarma Institute of Technology, Pune
College Teacher
Prof. Vijay Mane
Cross-Checked by
Mehta Prathan

February 8, 2015

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Schaum's Outlines Of Electronic Devices And Circuits

Author: J. J. Cathey

Publisher: McGraw Hill, New York

Edition: 2

Year: 2002

ISBN: 0-07-139830-9

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

| | |
|------------------------------------------------------------------|-----------|
| List of Scilab Codes | 4 |
| 1 Circuit Analysis Port point of view | 8 |
| 2 Semiconductor Diodes | 17 |
| 3 CHARACTERISTICS OF BIPOLAR JUNCTION TRANSISTORS | 25 |
| 4 CHARACTERISTICS OF FIELD EFFECT TRANSISTORS AND TRIODES | 34 |
| 5 TRANSISTOR BIAS CONSIDERATIONS | 41 |
| 6 SMALL SIGNAL MIDFREQUENCY BJT AMPLIFIERS | 48 |
| 7 SMALL SIGNAL MIDFREQUENCY FET AND TRIODE AMPLIFIERS | 55 |
| 8 FREQUENCY EFFECTS IN AMPLIFIERS | 62 |
| 9 OPERATIONAL AMPLIFIERS | 64 |
| 10 Switched Mode Power Supplies | 66 |

List of Scilab Codes

| | | |
|----------|---------------------------------------------------------------------------------------------------------------|----|
| Exa 1.2 | Find the current i by superposition theorem | 8 |
| Exa 1.3 | Find the Thevenin equivalent voltage VTh and impedance ZTh for the network to the left of terminals | 9 |
| Exa 1.4 | For the circuit find vab | 9 |
| Exa 1.5 | For the circuit find vab | 10 |
| Exa 1.6 | For the circuit find iL by the method of node voltages | 10 |
| Exa 1.7 | find the Thevenin equivalent for the network to the left of terminals a and b | 11 |
| Exa 1.8 | find the Norton equivalent for the network to the left of terminals a andb | 12 |
| Exa 1.9 | find the Thevenin impedance as the ratio of open circuit voltage to short circuit current | 12 |
| Exa 1.11 | Determine the z parameters for the two port network . | 13 |
| Exa 1.12 | Solve Problem using a SPICE method | 14 |
| Exa 1.13 | Determine the h parameters for the two port network | 15 |
| Exa 1.15 | Find the voltage gain ratio V2 by V1 | 15 |
| Exa 1.19 | Find the average value of the current and the rms value of the current | 16 |
| Exa 2.1 | what range of forward voltage drop vD can be approximated | 17 |
| Exa 2.2 | find the forward current and the reverse saturation current | 17 |
| Exa 2.3 | find the Vl | 18 |
| Exa 2.5 | In the circuit D1 and D2 are ideal diodes and Find iD1 and iD2 | 18 |
| Exa 2.7 | Find iD and vD analytically | 19 |
| Exa 2.9 | Use the small signal technique to find iD and vD . . . | 19 |
| Exa 2.11 | Find the value of Rl | 20 |

| | | |
|----------|-------------------------------------------------------------------------------------|----|
| Exa 2.13 | Find the regulation of v_o when V_b increases | 20 |
| Exa 2.14 | Find the percentage change in the average value of v_L | 21 |
| Exa 2.15 | find the average value of v_L | 22 |
| Exa 2.26 | Find the value of R_2 and R_{th} | 22 |
| Exa 2.30 | Find the value of V_z | 23 |
| Exa 2.31 | Find the maximum allowable current i_Z | 23 |
| Exa 3.1 | Find I_b and I_e | 25 |
| Exa 3.2 | Find the collector current | 25 |
| Exa 3.3 | Find I_{cq} and I_{eq} | 26 |
| Exa 3.4 | Find beta I_{cq} and I_{eq} | 26 |
| Exa 3.5 | Find the required value of R_B | 27 |
| Exa 3.6 | Find VCEQ if RC is changed to 6 k | 27 |
| Exa 3.7 | Find V_{ceq} | 28 |
| Exa 3.8 | Find R_C and beta | 28 |
| Exa 3.9 | Find the Q point collector current I_{CQ} | 29 |
| Exa 3.12 | Solved Example Ex12 page no 87 Find R_E | 29 |
| Exa 3.13 | Solved Example Ex 13 page no 88 Find R_E | 30 |
| Exa 3.16 | Solved Example Ex 16 page no 89 Find the minimum value of R_C | 30 |
| Exa 3.19 | Find the value of R_B that just results in saturation | 31 |
| Exa 3.20 | Find the value of R_1 needed to bias the circuit so that $V_{CEQ} = 6V$ | 31 |
| Exa 3.23 | Solved Example Ex 23 page no 94 find I_{BQ} and V_{CEQ} | 32 |
| Exa 3.26 | Solved Example Ex 26 page no 96 Find R_1 and R_2 | 32 |
| Exa 3.32 | Solved Example Ex 32 page no 99 Determine the value of R_B | 33 |
| Exa 4.2 | Calculate I_{DQ} from the analog | 34 |
| Exa 4.5 | Find V_{GG} R_S and R_D | 34 |
| Exa 4.8 | Determine appropriate values of R_S and R_D | 35 |
| Exa 4.10 | Solved Example Ex 10 page no 121 Find V_{dd} and V_{dsq} | 35 |
| Exa 4.11 | Find V_{GSQ} I_{DQ} and V_{DSQ} | 36 |
| Exa 4.13 | Find V_{GSQ} if $I_{DQ} = 16mA$ and I_{DQ} if $V_{GSQ} = 5V$ | 37 |
| Exa 4.14 | find I_{DQ} and V_{GSQ} | 37 |
| Exa 4.18 | find V_{DSQ1} I_{DQ1} V_{GSQ1} V_{GSQ2} and V_{DSQ2} | 37 |
| Exa 4.19 | Find V_{gsq1} V_{gsq2} V_{dsq1} V_{dsq2} I_{dq2} | 38 |
| Exa 4.20 | Find V_{gsq} | 39 |
| Exa 4.23 | Find V_{dsq} V_{gsq} and I_{dq} | 39 |
| Exa 4.24 | find the perveance and the amplification factor m | 40 |

| | | |
|----------|---------------------------------------------------------------------------------------------------------------------------|----|
| Exa 4.26 | Calculate the plate efficiency of the amplifier | 40 |
| Exa 5.1 | Find leakage current at 90 c | 41 |
| Exa 5.6 | Find ICQ and VCEQ | 41 |
| Exa 5.8 | Example 5.8 page no 146 Find ICQ IBQ and VCEQ . | 42 |
| Exa 5.9 | Find the sensitivity factor S _b and use it to calculate the change in ICQ | 43 |
| Exa 5.11 | Example 11 page no 148 Find the exact change in ICQ | 44 |
| Exa 5.16 | Find an expression for ICQ at any temperature | 44 |
| Exa 5.19 | Predict the change that will occur in ICQ as RE changes | 45 |
| Exa 5.25 | Find V _{dssmax} and V _{dssmin} | 46 |
| Exa 5.26 | Find the Range of V _{dss} | 46 |
| Exa 5.28 | Find the range of I _{dq} | 47 |
| Exa 6.2 | Find an expression for the current gain ratio A _i | 48 |
| Exa 6.7 | Calculate the voltage gain A _v and the current gain A _i | 48 |
| Exa 6.8 | determine the voltage gain A _v | 49 |
| Exa 6.18 | Find A _i and A _v | 49 |
| Exa 6.19 | Find A _i and i _L | 50 |
| Exa 6.22 | Find the overall voltage gain A _v | 50 |
| Exa 6.24 | Find the overall voltage gain A _v | 51 |
| Exa 6.26 | Find the overall voltage gain A _v | 52 |
| Exa 6.27 | Find the overall voltage gain A _v and overall current gain ratio | 53 |
| Exa 7.1 | Determine the small signal equivalent circuit constants g _m and r _{ds} | 55 |
| Exa 7.3 | Find the overall voltage gain A _v and overall current gain ratio | 56 |
| Exa 7.4 | Find the overall voltage gain A _v and overall current gain ratio | 56 |
| Exa 7.7 | Find the overall voltage gain A _v and overall current gain ratio | 57 |
| Exa 7.10 | Find the overall voltage gain A _v and overall current gain ratio and output impedance R _O | 57 |
| Exa 7.11 | Find the overall voltage gain A _v and overall current gain ratio and output impedance R _O | 58 |
| Exa 7.12 | Find I _{dm} | 59 |
| Exa 7.18 | Find the perveance k and the amplification factor m . | 59 |
| Exa 7.20 | Evaluate the plate resistance | 60 |
| Exa 7.22 | Calculate the voltage gain | 60 |

| | | |
|----------|--------------------------------------------------------------------------------------------------------|----|
| Exa 8.6 | Determine the low frequency voltage gain ratio if h_{ie} | 62 |
| Exa 8.8 | Determine the low frequency gain the midfrequency gain and the low frequency cutoff point | 63 |
| Exa 9.2 | Evaluate the gain of this inverting amplifier | 64 |
| Exa 9.9 | Find the regulated output v_o in terms of V_Z | 64 |
| Exa 9.12 | Find the value of C | 65 |
| Exa 9.25 | Find the value of A_v | 65 |
| Exa 10.1 | Find the average values of input voltage and input cur- rent | 66 |
| Exa 10.2 | Determine the smallest value of duty cycle possible | 66 |
| Exa 10.4 | Determine the duty cycle and the output power | 67 |
| Exa 10.7 | Find the maximum and minimum values of the inductor current | 67 |
| Exa 10.9 | Example 10 page no 298 | 68 |

Chapter 1

Circuit Analysis Port point of view

Scilab code Exa 1.2 Find the current i by superposition theorem

```
1 //Solved Example 1.2
2 //Page no 4
3 //Find the current i2 by superposition theorem
4 clear
5 clc
6 printf("\n Find the current i2 by superposition
    theorem")
7 R1=1          //ohm
8 R2=1          //ohm
9 R3=1          //ohm
10 Vs=10         //simWtv
11 Vb=10         //v
12 a=0
13 V21=1/3*Vs //simWtv
14 i21=V21/R2
15 Is=3 //A
16 temp=R1*R2/(R1+R2) //Temp=R1 || R2
17 i32=Vb/(R3+temp)
18 i22=(R1/(R1+R2))*i32
```

```
19 i2=i21+i22
20 i1=(Vs/(R1+R2))
21 printf("\n the current i2 by superposition theorem =
%1.2f A",i2)
```

Scilab code Exa 1.3 Find the Thevenin equivalent voltage VTh and impedance ZTh for the network to the left of terminals

```
1 //Solved Example 1.3 Page no 5
2 //Find the Thevenin equivalent voltage VTh and
   impedance ZTh
3 clear
4 clc
5 printf("\n Find the Thevenin equivalent voltage VTh
      and impedance ZTh")
6 Va=4//V
7 Ia=2//A
8 R1=2//ohm
9 R2=3//ohm
10 Vth=Va+Ia*R1
11 Zth=R1+R2
12 printf("\n Thevenin equivalent voltage VTh is = %.2
      f V",Vth)
13 printf("\n Impedance ZTh is = %1.1f Ohm",Zth)
```

Scilab code Exa 1.4 For the circuit find vab

```
1 //Solved Example 1.4
2 //Page no 6
3 //Findthe Thevenin equivalent voltage VTh and
   impedance ZTh
4 clear
5 clc
```

```

6 printf("\n Find the Thevenin equivalent voltage VTh
    and impedance ZTh")
7 Va=4 //V
8 a=0.25 //A/V
9 R1=2 //ohm
10 R2=3 //ohm
11 Vth=Va/(1-a*R1)
12 Vdp=R1+R2
13 Idp=1-a*R1
14 Zth=Vdp/Idp
15 printf("\n Thevenin equivalent voltage VTh is = %.f
    V",Vth)
16 printf("\n Impedance ZTh is = %.f Ohm",Zth)

```

Scilab code Exa 1.5 For the circuit find vab

```

1 //For the circuit find vab
2 //Solved Example 1.5 page no 17
3 clear
4 clc
5 printf("\n For the circuit find vab")
6 printf("\n The SPICE netlist code for k 0:001
    follows")
7 printf("\n vab=V(3)=-101 V")
8 printf("\n The SPICE netlist code for k 0:05
    follows")
9 printf("\n vab=V(3)=-200 V")

```

Scilab code Exa 1.6 For the circuit find iL by the method of node voltages

```

1 //Solved Example 1.6
2 //Page no 7

```

```

3 //Find the Norton equivalent current IN and
   admittance YN
4 clear
5 clc
6 printf("\n Find the Norton equivalent current IN and
   admittance YN")
7 Va=4.0 //V
8 a=0.25 //A/V
9 R1=2 //ohm
10 R2=3 //ohm
11 I=2
12 Zth=5
13 Ia=(Va/(R1+R2))+((R1*I)/(R1+R2))
14 Yn=1/Zth
15 printf("\n Norton equivalent current IN is = %.2f V
   ",Ia)
16 printf("\n admittance YN is = %.2f Ohm" ,Yn)

```

Scilab code Exa 1.7 find the Thevenin equivalent for the network to the left of terminals a and b

```

1
2 //find the Thevenin equivalent for the network to
   the left of terminals a; b.
3 //Solved Example 1.7
4 //page no 19
5 clear
6 clc
7 printf("\n find the Thevenin equivalent for the
   network to the left of terminals a; b .")
8 V1=10 //V
9 V2=15 //V
10 R1=4 //ohm
11 R2=6 //ohm
12 I=(V1-V2)/(R1+R2)

```

```

13 printf("\n The value of I is =%0.2f A",I)
14 Vth=V1-I*R1
15 printf("\n The value of Thevenin Equivalent voltage=
    %0.2f V",Vth)
16 Zth=(R1*R2)/(R1+R2)
17 printf("\n The value of Thevenin Impedance =%0.2f
    ohm",Zth)

```

Scilab code Exa 1.8 find the Norton equivalent for the network to the left of terminals a and b

```

1
2 // find the Norton equivalent for the network to the
   left of terminals a; b.
3 //Solved Example 1.8 page no 19
4 clear
5 clc
6 printf("\n find the Norton equivalent for the
   network to the left of termin")
7 V1=10 //V
8 V2=15 //V
9 R1=4 //ohm
10 R2=6 //ohm
11 Iab1=V1/R1
12 Iab2=V2/R2
13 printf("\n Then by superpostion ")
14 In=Iab1+Iab2
15 Zth=(R1*R2)/(R1+R2)
16 Yn=1/Zth //Rth=Zth
17 printf("\n The value of In =%0.2f A and Yn= %0.4f A"
    ,In,Yn)

```

Scilab code Exa 1.9 find the Thevenin impedance as the ratio of open circuit voltage to short circuit current

```
1 // find the Thevenin impedance as the ratio of open
2 // -circuit voltage to short-circuit current
3 //Solved Example 1.9 page no 20
4 clear
5 clc
6 printf("\n find the Thevenin impedance as the
7 ratio of open-circuit voltage to short-circuit
8 current")
9 V1=10//V
10 V2=15//V
11 R1=4//ohm
12 R2=6//ohm
13 I=(V1-V2)/(R1+R2)
14 printf("\n The value of I is =%0.2f A",I)
15 Vth=V1-I*R1
16 Iab1=V1/R1
17 Iab2=V2/R2
18 printf("\n Then by superposition ")
19 In=Iab1+Iab2
20 Zth=Vth/In
21 printf("\n The value of Zth is =%0.2f ohm",Zth)
```

Scilab code Exa 1.11 Determine the z parameters for the two port network

```
1 //Solved Example 1.11 Page no 14
2 //Find the half-cycle average value of the current
3 // through a resistance R
4 clear
5 clc
6 printf("\n Find the Norton equivalent current IN and
```

```

        admittance YN" )
6  Va=4.0 //V
7  a=0.25 //A/V
8  R1=2 //ohm
9  R2=3 //ohm
10 I=2
11 Zth=5
12 Ia=(Va/(R1+R2))+((R1*I)/(R1+R2))
13 Yn=1/Zth
14 printf("\n Norton equivalent current IN is = %.2f V
      ",Ia)
15 printf("\n admittance YN is = %.2f Ohm" ,Yn)

```

Scilab code Exa 1.12 Solve Problem using a SPICE method

```

1 //Solve Problem 1.11 using a SPICE method
2 //Solved Example 1.12 page no 21
3 clear
4 clc
5 printf("\nSolve Problem 1.11 using a SPICE method")
6 V1=1.231*(10^-2)      //V
7 I1=1*(10^-3)          //A
8 Z11=V1/I1              //Ohm
9 printf("\n The value of Z11=%0.2f Ohm" ,Z11)
10 V1=2.308*(10^-3)     //V
11 I2=1*(10^-3)          //A
12 Z12=V1/I2              //Ohm
13 printf("\n The value of Z12=%0.3f Ohm" ,Z12)
14 V2=4.615*(10^-3)     //V
15 I1=1*(10^-3)          //A
16 Z21=V2/I1              //Ohm
17 printf("\n The value of Z21=%0.3f Ohm" ,Z21)
18 V2=4.615*(10^-3)     //V
19 I2=1*(10^-3)          //A
20 Z22=V2/I2              //Ohm

```

```
21 printf("\n The value of Z22=%0.3f Ohm" ,Z22)
```

Scilab code Exa 1.13 Determine the h parameters for the two port network

```
1 //Determine the h parameters for the two-port
   network
2 //Solved Example 1.13 page no 22
3 clear
4 clc
5 printf("\nDetermine the h parameters for the two-
   port network")
6 V2=0          //V
7 Ia=0          //A
8 //h11=V1/I1
9 h11=10        //ohm
10 //Here I2=-I1
11 //Therefor h21=I2/I1  h21=-1
12 h21=-1        //ohm
13 Ia=V2/6       //A
14 I1=0          //A
15 V1=V2-10*(0.3) //V
16 //h12=V1/V2
17 h12=0.5        //Ohm
18 I2=1.3         //A
19 V2=6           //V
20 h22=I2/V2      //Ohm
21 printf("\nThe value of h11=%1.3f ohm h21=%1.3f ohm
   h12=%1.3f ohm h22=%1.3f" ,h11 ,h21 ,h12 ,h22)
```

Scilab code Exa 1.15 Find the voltage gain ratio V2 by V1

```
1 //Find the voltage-gain ratio V2/V1
```

```

2 //Solved Example 1.15 page no 23
3 clear
4 clc
5 printf("\nFind the voltage-gain ratio V2/V1")
6 //Let V=V2/V1
7 RL=2000
8 h11=100 //ohm
9 h12=0.0025 //ohm
10 h21=20 //ohm
11 h22=0.001 //mS
12 V=1/(h12-(h11/h21)*((1/RL)+h22))
13 printf("\n The value of V2/V1=%0.1f",V)

```

Scilab code Exa 1.19 Find the average value of the current and the rms value of the current

```

1
2 //Find (a) the average value of the current and (b)
   the rms value of the current..
3 //Solved Example 1.19 page no 25
4 clear
5 clc
6 printf("\nFind (a) the average value of the current
   and (b) the rms value of the current .")
7 T=1
8 I0=(1/T)*(4*(T/2)+1*(T/2))//A
9 printf("\nI0=%0.1f A",I0)
10 I=(2*(1/T)*((4^2)*(T/2)+(1^2)*(T/2)))^(1/2)//A
11 printf("\nI=%0.2f A",I)

```

Chapter 2

Semiconductor Diodes

Scilab code Exa 2.1 what range of forward voltage drop v_D can be approximated

```
1 //what range of forward voltage drop vD can (2.1) be
2 //approximated
3 //Solved Example Ex2.1 page no 48
4 clear
5 clc
6 printf("\n what range of forward voltage drop vD can
7 (2.1) be approximated")
8 n=1
9 k=1.38 //x 10^-23
10 T=25+273
11 q=1.6 //x 10^-19
12 vd=((k*T)/(1.6*(10^4))*4.6151)
13 printf("\n vd = %0.4f V",vd)
```

Scilab code Exa 2.2 find the forward current and the reverse saturation current

```
1
2 // (a) find the forward current .
3 // (b) Find the reverse saturation current .
4 // Solved Example Ex2.2 page no 48
5 clear
6 clc
7 printf("\n find the forward and reverse saturation
         current")
8 iD2=(47.73*10)//mA
9 printf("\n iD2= %0.2 f",iD2)
10 printf("\n iD1/(e^(0.3/0.02587)-1)=91nA")
```

Scilab code Exa 2.3 find the Vl

```
1
2 //find the Vl
3 //Solved Example Ex2.3 page no 48
4 clear
5 clc
6 printf("\n find the value of Vl")
7 Rl=100          // k
8 Rs=10          // k
9 Vl=(Rl/(Rl+Rs))
10 printf("\n The value of Vl = %0.4 f vs",Vl)
```

Scilab code Exa 2.5 In the circuit D1 and D2 are ideal diodes and Find iD1 and iD2

```
1
2 //In the circuit D1 and D2 are ideal diodes . Find
   iD1 and iD2 .
3 //Solved Example Ex2.5 page no 50
4 clear
```

```

5 clc
6 printf("\n In the circuit D1 and D2 are ideal diodes
. Find iD1 and iD2 .")
7 Vs=5 //V
8 V2=3 //V
9 iD2=((Vs-V2)/500)*1000 //mA
10 printf("\n iD2= %d mA", iD2)

```

Scilab code Exa 2.7 Find iD and vD analytically

```

1 //Find iD and vD analytically
2 //Solved Example Ex2.7 page no 51
3 clear
4 clc
5 printf("\n Find iD and vD analytically")
6 vs=0.1 //cos wtV
7 Vb=2 //V
8 printf("\n (100/200)*(2+0.1 cos wt) V")
9 Rth=(100^2)/200 // k
10 printf("\n Rth= %d ohm", Rth)
11 printf("\n Rf=%d ohm", (0.7-0.5)/0.004)

```

Scilab code Exa 2.9 Use the small signal technique to find iD and vD

```

1 //Use the small-signal technique to find iD and vD
2 //Solved Example Ex2.9 page no 52
3 clear
4 clc
5 printf("\n Use the small-signal technique to find iD
and vD")
6 Idq=5 //mA
7 Vdq=0.75 //V
8 vh=0.05 //cos wt

```

```

9 Rth=50           // k
10 rd=50
11 rd=(0.7-0.5)/0.004
12 printf("\n rd= %d ohm",rd)
13 id=(vh/(Rth+rd))*1000
14 vd=(rd*id)/1000//cos wt V
15 printf("\n id= %0.1f cos wt mA",id)
16 printf("\n vd= %0.3f cos wt V",vd)
17 printf("\n iD = Idq + id = 5+0.5 cos wt mA")
18 printf("\n vD = Vdq + vd = 0.75+0.025 cos wt V")

```

Scilab code Exa 2.11 Find the value of R_l

```

1
2 //Solved Example Ex2.11 page no 54
3 clear
4 clc
5 Rs=200 //
6 R1=200 //
7 Rl=50 // k
8 vs=400 //sin wt V
9 vth=(R1/(R1+Rs))*vs
10 printf("\n vth =%d sin wt V",vth)
11 Rth=((R1*Rs)/(R1+Rs))
12 printf("\n Rth =%d ohm",Rth)
13 id=-2*10^(-6)
14 Rl=Rl*(10^3)
15 vD=vth-(id)*(Rth+Rl)
16 printf("\n vD =%0.1f V",vD)

```

Scilab code Exa 2.13 Find the regulation of v_o when V_b increases

```

1 //Find the regulation of vo when Vb increases from
   its nominal value of 4V to the value 6 V.
2 //Solved Example Ex2.13 page no 55
3 clear
4 clc
5 Vf1=1//v
6 Vf2=2//v
7 Rf1=100//
8 Rf2=200//
9 Vb1=4//v
10 Vb2=6//v
11 R=2000
12 V01=Vf2+((Vb1-Vf1-Vf2)*Rf2)/(R+Rf1+Rf2)
13 V02=Vf2+((Vb2-Vf1-Vf2)*Rf2)/(R+Rf1+Rf2)
14 Reg=((V02-V01)/V01)*100
15 printf("V01 is %0.3 f and %0.3 f",V01,V02)
16 printf("Reg = %0.3 f",Reg)

```

Scilab code Exa 2.14 Find the percentage change in the average value of vL

```

1 //Find the percentage change in the average value of
   vL over the range of load variation ,
2 //Solved Example Ex2.14 page no 56
3 clear
4 clc
5 Rl=10//
6 Rs=10//
7 Vs=10//v
8 Vl=(Rl/(Rl+Rs))*Vs      //V
9 printf("Vl = %0.3 f",Vl)
10 Vl01=2.5//V
11 printf("\n For Rl=1000")
12 Rl=1000
13 Vs=10

```

```

14 Rs=10
15 Vl=(Rl/(Rl+Rs))*Vs
16 printf("\nVl = %0.3f",Vl)
17 Vl02=4.9//V
18 Reg=((Vl02-Vl01)/Vl01)*100
19 printf("Reg = %0.3f",Reg)

```

Scilab code Exa 2.15 find the average value of vL

```

1 //find the averagevalue of vL.
2 //Solved Example Ex2.15 page no 56
3 clear
4 clc
5 Rl=10 //
6 Rs=10 //
7 Vs=-10 //v
8 Vl=(Rl/(Rl+Rs))*Vs
9 printf("Vl = %0.3f",Vl)
10 Vl0=2.5//V
11 printf("\n Vl0 Rl=%0.3f",Vl0)

```

Scilab code Exa 2.26 Find the value of R2 and Rth

```

1 //Solved Example Ex2.26 page no 61
2 clear
3 clc
4 R1=6 // k
5 R2=3 // k
6 V1=5 //v
7 V2=10 //v
8 Rth=(R1*R2/(R1+R2))
9 printf("Rth = %0.3f",Rth)
10 R2=(R1*Rth/(R1-Rth))

```

```
11 printf("\nR2 = %0.3f", R2)
```

Scilab code Exa 2.30 Find the value of Vz

```
1
2 //Solved Example Ex2.30 page no 65
3 clear
4 clc
5 Vz=8.2          //V
6 Rl=9            // k
7 iL=Vz/Rl        //mA
8 printf("iL = %0.3f A", iL)
9 iZ=1
10 Vb=13.2
11 Rs=((Vb-Vz)/(iZ+iL))
12 printf("\n Rs = %0.3f ohm", Rs)
13 Vb=11.7
14 iZ=((Vb-Vz)/Rs)-iL
15 printf("\n iZ = %0.3f", iZ)
```

Scilab code Exa 2.31 Find the maximum allowable current iZ

```
1 //Find the maximum allowable current iZ when the
   Zener diode is acting as a regulator
2 //Solved Example Ex2.31 page no 65
3 clear
4 clc
5 Vz=5.2          //V
6 Pdmax=260         //mW
7 iZmax=Pdmax/Vz    //mA
8 printf("iZmax = %0.3f mA", iZmax)
9 Vs=15
10 R=(Vs-Vz)*1000/iZmax
```

```
11 printf("\n R = %0.3f ohm",R)
```

Chapter 3

CHARACTERISTICS OF BIPOLEAR JUNCTION TRANSISTORS

Scilab code Exa 3.1 Find Ib and Ie

```
1 //Find IB and IE.
2 //Solved Example Ex3.1 page no 83
3 clear
4 clc
5 betaa=50
6 Ic=1.2          //mA
7 Icko=3*10^-3    //mA
8 Ib=((Ic-Icko)/betaa)*1000      //mA
9 printf(" Ib = %0.2 f X 10^-3 mA" , Ib)
10 IE=(Ic)-(Ib*10^-3)
11 printf("\n IE = %0.2 f mA" , IE)
```

Scilab code Exa 3.2 Find the collector current

```

1 // find the collector current for (a) IB = 0 and (b)
   IB = 40 A.
2 //Solved Example Ex3.2 page no 83
3 clear
4 clc
5 betaa=100
6 Ib=0           //mA
7 Icbo=5 //V      //mA
8 Ic eo=(betaa+1)*Icbo //mA
9 printf("\n When Ib =0 Ic eo = %0.2f mA", Ic eo)
10 Ib=40
11 Ic=((betaa*Ib)+(betaa+1)*Icbo)/1000
12 printf("\n When Ib =40 Ic = %0.3f mA", Ic)

```

Scilab code Exa 3.3 Find Icq and Ieq

```

1 //Find ICQ and IEQ.
2 //Solved Example Ex3.3 page no 83
3 clear
4 clc
5 alpha=0.98
6 beta a=alpha/(1-alpha)
7 Icbo=(5*10^-3) //mA
8 Ic eo=(betaa+1)*Icbo //mA
9 printf("\n Ic eo = %0.2f mA", Ic eo)
10 Ibq=100*10^-3
11 Icq=(betaa*Ibq)+Ic eo
12 printf("\n Icq = %0.2f mA", Icq)
13 Ieq=Icq+Ibq
14 printf("\n Ieq = %0.2f mA", Ieq)

```

Scilab code Exa 3.4 Find beta Icq and Ieq

```

1 //Find ( a ) Beta ; b() ICQ ,and ( c ) IEQ .
2 //Solved Example Ex3.4 page no 83
3 clear
4 clc
5 alpha=0.98
6 betaa=alpha/(1-alpha)
7 printf("\n Beta = %0.3f ", betaa)
8 Icq=1.47           //mA
9 Ieq=Icq/alpha      //mA
10 printf("\n Ieq = %0.3f mA", Ieq)

```

Scilab code Exa 3.5 Find the required value of RB

```

1 //Find the required value of RB.
2 //Solved Example Ex3.5 page no 84
3 clear
4 clc
5 Vbb=6             //V
6 Vbeq=0.7          //V
7 Ibq=40//10^-6
8 Rb=((Vbb-Vbeq)/Ibq)*1000
9 printf("\n Rb = %0.1f k ohm", Rb)

```

Scilab code Exa 3.6 Find VCEQ if RC is changed to 6 k

```

1 // find ( a ) IEQ and ( b ) VCEQ. ( c ) Find VCEQ if RC is
   changed to 6 k and all else remains the same.
2 //Solved Example Ex3.6 page no 84
3 clear
4 clc
5 b=100
6 a=b/(b+1)
7 Ibq=20//10^-6           //mA

```

```

8 Icq=(b*Ibq)/1000          //mA
9 Ieq=Icq/a                  //mA
10 printf("\n  Icq = %0.1f mA", Icq)
11 printf("\n  Ieq = %0.2f mA", Ieq)

```

Scilab code Exa 3.7 Find Vceq

```

1 // find ( a) IEQ and (b) RB.(c) find VCEQ
2 //Solved Example Ex3.7 page no 85
3 clear
4 clc
5 b=80
6 a=b/(b+1)
7 Ibq=40//10^-6           //mA
8 Ieq=(Ibq/(1-a))/1000    //mA
9 printf("\n  Ieq = %0.2f mA", Ieq)
10 Icq=(b*Ibq)/1000
11 printf("\n  Icq = %0.2f mA", Icq)

```

Scilab code Exa 3.8 Find Rc and beta

```

1 //find graphically (a) ICQ;   b   RC;   c   IEQ, and
   (d) if leakage current is negligible .
2 //Solved Example Ex3.8 page no 85
3 clear
4 clc
5 Vcc=14                   //V
6 Rc=(14/(6.5*10^-3))/1000 // k
7 Icq=2.25                 //mA
8 Ibq=20*10^-3              //mA
9 Ieq=Icq+Ibq               //mA
10 printf("\n  Ieq = %0.2f mA", Ieq)
11 b=Icq/Ibq

```

```
12 printf("\n Beta = %0.2f mA", b)
```

Scilab code Exa 3.9 Find the Q point collector current ICQ

```
1 //Find the Q-point collector current ICQ.
2 //Solved Example Ex3.9 page no 85
3 clear
4 clc
5 b=70
6 Vcc=15          //V
7 Vbeq=0.7        //V
8 Ic eo=1.42      //mA
9 Rb=500 /*10^3    // k
10 Ibq=((Vcc-Vbeq)/Rb)*1000
11 printf("\n Ibq = %0.2f mA", Ibq)
12 Icq=((b*Ibq/1000)+Ic eo)
13 printf("\n Icq = %0.2f mA", Icq)
```

Scilab code Exa 3.12 Solved Example Ex12 page no 87 Find Re

```
1 //Find KVL around the emitter-base loop
2 //Solved Example Ex3.12 page no 87
3 clear
4 clc
5 Vceq=-6.4        //V
6 Vbeq=-0.3         //V
7 Vcbq=Vceq-Vbeq   //V
8 printf("\n Vcbq = %0.2f V", Vcbq)
9 Vee=2
10 Ieq=3
11 Re=((Vee+Vbeq)/Ieq)*1000
12 printf("\n Re = %0.2f Ohm", Re)
```

Scilab code Exa 3.13 Solved Example Ex 13 page no 88 Find Re

```
1 // Find KVL around the transistor terminals ,  
2 //Solved Example Ex3.13 page no 88  
3 clear  
4 clc  
5 Vcc=12          //V  
6 Vceq=6          //V  
7 hf=100  
8 Rc=2//*10^3     // k  
9 Ibq=((Vcc-Vceq)/((hf+1)*Rc))*1000  
10 printf("\n Ibq = %0.2 f mA", Ibq)  
11 Vbeq=0.7  
12 Rf=((Vceq-Vbeq)/Ibq)*1000  
13 printf("\n Rf = %0.2 f Ohm", Rf)
```

Scilab code Exa 3.16 Solved Example Ex 16 page no 89 Find the minimum value of RC

```
1 //Solved Example Ex3.16 page no 89  
2 clear  
3 clc  
4 b=80  
5 a=(b/(b+1))  
6 Ibq=30  
7 Icq=Ibq*b/1000  
8 printf("\n Icq = %0.2 f mA", Icq)  
9 Ieq=(Icq/a)  
10 printf("\n Ieq = %0.2 f OmA", Ieq)
```

Scilab code Exa 3.19 Find the value of RB that just results in saturation

```
1 //Find the value of RB that just results in  
    saturation if (a) the capacitor is present , and  
2 // (b) the capacitor is replaced with a short circuit  
.  
3 //Solved Example Ex3.19 page no 91  
4 clear  
5 clc  
6 b=50  
7 Vbeq=0.3 //V  
8 Vcc=12 //v  
9 Vs=2 //v  
10 Rc=4 //Kohm  
11 Rs=100 //Kohm  
12 Vce=0.2  
13 Icq=(Vcc-Vce)/Rc  
14 printf("\n Icq = %0.2 f mA",Icq)  
15 Rb=((Vcc-Vbeq)/(Icq/b))  
16 printf("\n Rb = %0.2 f Ohm",Rb)
```

Scilab code Exa 3.20 Find the value of R1 needed to bias the circuit so that VCEQ2 6V

```
1 //Find the value of R1 needed to bias the circuit so  
    that VCEQ2 = 6V. (b) with R1 as found in part a,  
    find VCEQ1.  
2 //Solved Example Ex3.20 page no 91  
3 clear  
4 clc  
5 b=50  
6 b2=50  
7 Vce=6 //V  
8 Re=1 // k  
9 Vcc=12 //v //V
```

```

10 Ieq2=(Vcc-Vce)/Re
11 printf("\n  Ieq2 = %0.2f mA", Ieq2)
12 Ibq2=(Ieq2/((b+1)*(b2+1)))*1000
13 printf("\n  Ibq2 = %0.2f mA", Ibq2)

```

Scilab code Exa 3.23 Solved Example Ex 23 page no 94 find IBQ and VCEQ

```

1 //Find the minimum value of RC that will maintain
   the transistor quiescent point at saturation ,
2 //Solved Example Ex3.16 page no 89
3 clear
4 clc
5 b=80
6 a=(b/(b+1))
7 Ibq=30           //mA
8 Icq=Ibq*b/1000  //mA
9 printf("\n  Icq = %0.2f mA", Icq)
10 Ieq=(Icq/a)
11 printf("\n  Ieq = %0.2f OmA", Ieq)

```

Scilab code Exa 3.26 Solved Example Ex 26 page no 96 Find R1 and R2

```

1 //Find R1 and R2
2 //Solved Example Ex3.26 page no 96
3 clear
4 clc
5 b=100
6 Vbeq=0.7          //V
7 Vcc=15             //V
8 Re=300              // k
9 Rc=500              // k
10 Icq=((Vcc)/(2*(Re+Rc)))*1000

```

```

11 printf("\n  Icq = %0.2f mA", Icq)
12 Rb=(b*Re/10)/1000
13 printf("\n  Rb = %0.2f Kohm", Rb)
14 Vbb=Vbeq+Icq*(1.1*Re)/1000
15 printf("\n  Vbb = %0.2f V", Vbb)
16 R1=Rb/(1-Vbb/Vcc)
17 printf("\n  R1 = %0.2f Kohm", R1)
18 R2=Rb*(Vcc/Vbb)
19 printf("\n  R2 = %0.2f Kohm", R2)

```

Scilab code Exa 3.32 Solved Example Ex 32 page no 99 Determine the value of RB

```

1 // Find the value of . (c) Determine the value of RB
.
2 //Solved Example Ex3.32 page no 99
3 clear
4 clc
5 Vcc=12          //v
6 Vbeq=0.7        //v
7 Re=1*10^3       // k
8 Icq=6*10^3      //mA
9 Ibq=50*10^-3   //mA
10 b=Icq/Ibq
11 printf("\n  B = %0.2f mA", b)

```

Chapter 4

CHARACTERISTICS OF FIELD EFFECT TRANSISTORS AND TRIODES

Scilab code Exa 4.2 Calculate IDQ from the analog

```
1 //Calculate IDQ from the analog
2 //Solved Example Ex4.2 page no 118
3 clear
4 clc
5 Idon=5 /*10^-3           //mA
6 Vgsq=6.90          //V
7 Vt=4               //V
8 Idq=Idon*((1-(Vgsq/Vt))^2)
9 printf("\n Idq = %0.2 f mA", Idq)
```

Scilab code Exa 4.5 Find VGG RS and RD

```

1 //Find ( a ) VGG;    b    RS, and ( c ) RD.
2 //Solved Example Ex4.5 page no 118
3 clear
4 clc
5 Vgg=10          //V
6 Vgsq=8           //V
7 Idq=1*10^-3      //mA
8 Rs=((Vgg-Vgsq)/Idq)/1000      // k
9 printf("\n  Rs = %0.2 f  K ohm" ,Rs)
10 Vdd=16          //V
11 Vdsq=12          //V
12 Idq=1
13 Rd=((Vdd-Vdsq-(Idq*Rs))/Idq)
14 printf("\n  Rd = %0.2 f  K ohm" ,Rd)

```

Scilab code Exa 4.8 Determine appropriate values of RS and RD

```

1 //Determine appropriate values of RS and RD.
2 //Solved Example Ex4.8 page no 120
3 clear
4 clc
5 Rs=750          // k
6 printf("\n  Rs = %0.2 f  K ohm" ,Rs)
7 Vdd=24          //V
8 Vdsq=15          //V
9 Idq=0.002        //mA
10 Rd=((Vdd-Vdsq-(Idq*Rs))/Idq)/1000
11 printf("\n  Rd = %0.2 f  K ohm" ,Rd)

```

Scilab code Exa 4.10 Solved Example Ex 10 page no 121 Find Vdd and Vdsq

```

1 //find ( a ) VGG and ( b ) VDSQ

```

```

2 // Solved Example Ex4.10 page no 121
3 clear
4 clc
5 Idq=-8          //mA
6 Idss=-10         //mA
7 Vp0=-4           //V
8 Vgsq=Vp0*((Idq/Idss)^(1/2))-1
9 printf("\n Vgsq = %0.2f V", Vgsq)
10 Vdd=-20
11 Rd=1.5
12 Vdsq=Vdd-Idq*Rd
13 printf("\n Vdsq = %0.2f V", Vdsq)

```

Scilab code Exa 4.11 Find VGSQ IDQ and VDSQ

```

1 //Find (a) VGSQ; b IDQ, and (c) VDSQ.
2 //Solved Example Ex4.11 page no 121
3 clear
4 clc
5 Vt=4 //V
6 R1=50 //k ohm
7 R2=0.4 //M ohm
8 Rs=0
9 Rd=2 //k ohm
10 Vdd=15 //V
11 Vgsq=(R1/(R1+R2*10^3))*Vdd
12 printf("\n Vgsq = %0.2f V", Vgsq)
13 Idon=10 /*10^-3
14 Idq=Idon*(1-(Vgsq/Vt))^2
15 printf("\n Idq = %0.2f mA", Idq)
16 Vdsq=Vdd-(Idq*Rd)
17 printf("\n Vdsq = %0.2f V", Vdsq)

```

Scilab code Exa 4.13 Find VGSQ if IDQ 16mA and IDQ if VGSQ 5V

```
1 //Find (a) VGSQ if IDQ      16mA and (b) IDQ if VGSQ= - 5V.
2 //Example 4.13 page no 122
3 Vgsq=-4.5          //V
4 Idq=-8            //mA
5 VT=-3             //V
6 Idon=(Idq/(1-Vgsq/VT)^2)
7 printf("\n Idon=%0.2f mA" ,Idon)
8 Idq=-16
9 Vgsq=VT*(1-(Idq/Idon)^(1/2))
10 printf("\n Vgsq=%0.2f V" ,Vgsq)
11 Vgsq=-5
```

Scilab code Exa 4.14 find IDQ and VGSQ

```
1 //find IDQ and VGSQ.
2 //Example 4.14 page no 123
3 clear
4 clc
5 Vdd=15           //v
6 Vdsq=7            //v
7 Rs=3              // k
8 Rd=1              // k
9 Idq=((Vdd-Vdsq)/(Rs+Rd))
10 printf("\n Idq=%0.2f mA" ,Idq)
11 Vgsq=-(Idq*Rd)
12 printf("\n Vgsq=%0.2f V" ,Vgsq)
```

Scilab code Exa 4.18 find VDSQ1 IDQ1 VGSQ1 VGSQ2 and VDSQ2

```

1 // find ( a ) VDSQ1; ( b ) IDQ1; ( c ) VGSQ1, ( d ) VGSQ2,
   and ( e ) VDSQ2
2 //Example 4.18 page no 126
3 clear
4 clc
5 Idq1=1.22           //mA
6 Vdsq1=0             //V
7 Vdd=15              //V
8 Rs=2                // k
9 Rd=5                // k
10 Vgsq1=-(Idq1*Rs)
11 printf("\n Vgsq=%0.2f V" ,Vgsq1)
12 Vdsq2=Vdd-Vdsq1-Idq1*(Rs+Rd)
13 printf("\n Vdsq2=%0.2f V" ,Vdsq2)

```

Scilab code Exa 4.19 Find Vgsq1 Vgsq2 Vdsq1 Vdsq2 Idq2

```

1 // find ( a ) VGSQ1; b) IDQ2, ( c ) VGSQ2; d) VDSQ1, and
   ( e ) VDSQ2.
2 //Example 4.19 page no 127
3 clear
4 clc
5 Idq1=0           //mA
6 Idq2=2.92        //mA
7 Vdd=15           //V
8 Vgsq1=-4         //V
9 Rs=2             // k
10 Rd=1             // k
11 Vgsq2=-Vgsq1-Idq2*Rs
12 printf("\n Vgsq2=%0.2f V" ,Vgsq2)
13 Vdsq1=Vdd-(Idq1+Idq2)*Rd-Idq2*Rs-Vgsq2
14 printf("\n Vdsq1=%0.2f V" ,Vdsq1)
15 Rd=1
16 Idq1=0
17 Vdsq2=Vdd-(Idq1+Idq2)*Rd-Idq2*Rs

```

```
18 printf("\n Vdsq2=%0.2f V" ,Vdsq2)
```

Scilab code Exa 4.20 Find Vgsq

```
1 //Find VGSQ
2 //Example 4.20 page no 128
3 clear
4 clc
5 Vdd=15          //V
6 R2=40           // k
7 R1=60           // k
8 Vgsq=(R2/(R2+R1))*Vdd
9 printf("\n Vgsq=%0.2f V" ,Vgsq)
```

Scilab code Exa 4.23 Find Vdsq Vgsq and Idq

```
1 //determine (a) VGSQ, (b) IDQ, and (c) VDSQ.
2 //Example 4.23 page no 130
3
4 clear
5 clc
6 Idss=10          //mA
7 Vgsq=-1.34       //V
8 Vp0=4            //V
9 Rs=2             // k
10 Vdd=15          //V
11 Rd=500          // k
12 Idq=Idss*((1+(Vgsq/Vp0))^2)
13 Vdsq=Vdd-Idq*10^-3*(Rs*10^3+Rd)
14 printf("\n Idq=%0.2f mA" ,Idq)
15 printf("\n Vdsq=%0.2f V" ,Vdsq)
```

Scilab code Exa 4.24 find the perveance and the amplification factor m

```
1 // find (a) the perveance and (b) the amplification
   factor
2 //Example 4.24 page no 130
3 clear
4 clc
5 Ip=15           //mA
6 Vp=100          //v
7 Vp0=4           //v
8 Vg=-4           //v
9 k=(Ip/(Vp^(3/2)))*1000
10 m=-(Vp/Vg)
11 printf("\n the perveance k=%0.2f mA/V^3/2" ,k)
12 printf("\n the amplification factor m=%0.2f mA" ,m)
```

Scilab code Exa 4.26 Calculate the plate efficiency of the amplifier

```
1 //Calculate the plate efficiency of the amplifier
2 //Example 4.26 page no 130
3
4 clear
5 clc
6 Ip=(1/20)        //mA
7 Rl=10            // k
8 Vpp=2.4          //v
9 n=((Ip*Rl)/Vpp)
10 printf("\n the perveance n=%0.3f percent" ,n)
```

Chapter 5

TRANSISTOR BIAS CONSIDERATIONS

Scilab code Exa 5.1 Find leakage current at 90 °C

```
1 //find its leakage current at 90 degree C.  
2 //Example 5.1 page no 143  
3 clear  
4 clc  
5 Icbo=(500*(2^((90-25)/10)))/1000  
6 printf("\n The value of Icbo=%0.3f mA" ,Icbo)
```

Scilab code Exa 5.6 Find ICQ and VCEQ

```
1 //Find ICQ and VCEQ (a) for bet 50 and (b) for beta  
100  
2 //Example 5.6 page no 145  
3 clear  
4 clc  
5 Vee=4           //v  
6 Vbeq=0.7       //v
```

```

7 Rb=25*10^3           // k
8 b=50 //Beta
9 Re=2*10^3           // k
10 Icq=((Vee-Vbeq)/((Rb/b)+((b+1)/b)*Re))*1000
11 printf("\n The value of Icq=%0.3f mA" ,Icq)
12 Vcc=18             //v
13 Rc=6               // k
14 Re=2//*10^3         // k
15 Vceq=Vcc+Vee-(Rc+((b+1)/b)*Re)*Icq           //v
16 printf("\n For beta=100")
17 printf("\n The value of Vceq=%0.3f V" ,Vceq)
18 printf("\n For beta=100")
19 b=100
20 Re=2*10^3
21 Icq=((Vee-Vbeq)/((Rb/b)+((b+1)/b)*Re))*1000
22 printf("\n The value of Icq=%0.3f mA" ,Icq)
23 Re=2//*10^3
24 Vceq=Vcc+Vee-(Rc+((b+1)/b)*Re)*Icq
25 printf("\n The value of Vceq=%0.3f V" ,Vceq)

```

Scilab code Exa 5.8 Example 5.8 page no 146 Find ICQ IBQ and VCEQ

```

1 //Find ICQ; IBQ, and VCEQ if (a) beta 50 and (b)
   beta 100.
2 //Example 5.8 page no 146
3 clear
4 clc
5 Vcc=15             //v
6 Vee=4               //v
7 Vbeq=0.7            //v
8 b=50 //Beta
9 Re=3*10^3           // k
10 Rc=7                // k
11 Ieq=(Vee-Vbeq)/Re*1000
12 printf("\n For beta=50")

```

```

13 printf("\n The value of Ieq=%0.3f mA" ,Ieq)
14 Icq=(b/(b+1))*Ieq
15 printf("\n The value of Icq=%0.3f mA" ,Icq)
16 Ibq=Icq/b
17 printf("\n The value of Ibq=%0.3f mA" ,Ibq)
18 Vee=5
19 Re=3//*10^3
20 Vceq=Vcc+Vee-(Ieq*Re)-(Icq*Rc)
21 printf("\n The value of Vceq=%0.3f V" ,Vceq)
22 printf("\n For beta=100")
23 b=100
24 printf("\n The value of Ieq=%0.3f mA" ,Ieq)
25 Icq=(b/(b+1))*Ieq
26 printf("\n The value of Icq=%0.3f mA" ,Icq)
27 Ibq=Icq/b
28 printf("\n The value of Ibq=%0.3f mA" ,Ibq)
29 Vee=5
30 Re=3//*10^3
31 Vceq=Vcc+Vee-(Ieq*Re)-(Icq*Rc)
32 printf("\n The value of Vceq=%0.3f V" ,Vceq)

```

Scilab code Exa 5.9 Find the sensitivity factor S_b and use it to calculate the change in ICQ

```

1 //Example 5.9 page no 147
2 clear
3 clc
4 Vcc=15
5 Vee=4
6 Vbeq=0.7
7 Rb=500
8 Sb=((Vcc-Vbeq)/Rb)*10^3
9 printf("\n The value of Sb=%0.3f " ,Sb)
10 Icq=(Sb*(100-50))/1000
11 printf("\n The value of Icq=%0.3f mA" ,Icq)

```

Scilab code Exa 5.11 Example 11 page no 148 Find the exact change in ICQ

```
1 // (a) Find the exact change in ICQ. (b) Predict the
2 // new value of ICQ using stability-factor analysis.
3 //Example 5.11 page no 148
4 clear
5 clc
6 Vbb=6
7 Vbeq1=0.7
8 Icbo1=0.5
9 Rb=50
10 Re=1
11 B=75 //Beta
12 Icq1=((Vbb-Vbeq1+Icbo1*(0.5*51*10^-3))/((Rb*10^3/B)+Re*10^3))*10^3
13 printf("\n The value of Icq1=%0.3f mA" ,Icq1)
14 Icbo2=(Icbo1*10^-6*2^2)*10^6
15 printf("\n The value of Icbo=%0.3f mA" ,Icbo2)
16 Vbeq=(-2*10^-3)*20
17 printf("\n The value of Vbeq=%0.3f V" ,Vbeq)
18 Vbeq2=Vbeq1+Vbeq
19 printf("\n The value of Vbeq2=%0.3f V" ,Vbeq2)
20 Icq2=((Vbb-Vbeq2+Icbo2*(2*51*10^-3))/((Rb*10^3/B)+Re*10^3))*10^3
21 printf("\n The value of Icq2=%0.3f mA" ,Icq2)
```

Scilab code Exa 5.16 Find an expression for ICQ at any temperature

```
1 //Find an expression for ICQ at any temperature.
2 //Example 5.16 page no 150
```

```

3 clear
4 clc
5 B=50 //beta
6 Vee=5
7 Vbeq1=0.7
8 T2=125
9 Re=3*10^3
10 Icbo1=0.5 /*10^-6
11 Icq2=((((B+1)/B)*((Vee-Vbeq1+0.002*(T2-25))/Re)+(2^((T2-25)/10))*Icbo1*10^-6)*10^3
12 printf("\n The value of Icq2=%0.3f mA" ,Icq2)

```

Scilab code Exa 5.19 Predict the change that will occur in ICQ as RE changes

```

1 //Determine a first-order approximation for the
   change in ICQ1
2 //Example 5.19 page no 152
3 clear
4 clc
5 B=75 //beta
6 Rb=454.5           // k
7 Icbo=0.2*10^-6
8 Vbb=1.818
9 Vbeq=0.7
10 Re=90
11 deltaRe=110-90
12 Sre=((B*Rb*Icbo-B^2*(Vbb-Vbeq+Icbo*Rb))/((Rb+B*Re)^2))*10^4
13 printf("\n The value of Sre=%0.3f * 10^-4 A/Ohm" ,
      Sre)
14 Icq=(Sre*deltaRe)/10
15 printf("\n The value of Icq=%0.3f * 10^-4 mA" ,Icq)

```

Scilab code Exa 5.25 Find Vdsqmax and Vdsqmin

```
1 // (a) Find the range of values of IDQ that could be  
    expected in using this FET. (b) Find the  
    corresponding range of VDSQ. (c) Comment on the  
2 // desirability of this bias arrangement.  
3 //Example 5.25 page no 156  
4 clear  
5 clc  
6 Vdd=15  
7 Idqmax=5.5  
8 Idqmin=1.3  
9 Rd=2.5          // k  
10 Vdsqmax=Vdd-Idqmax*Rd  
11 Vdsqmin=Vdd-Idqmin*Rd  
12 printf("\n The value of Vdsqmax=%0.3f V" ,Vdsqmax)  
13 printf("\n The value of Vdsqmin=%0.3f V" ,Vdsqmin)
```

Scilab code Exa 5.26 Find the Range of Vdsq

```
1 // (a) Find the range of IDQ that can be expected. (b)  
    ) Find the range of VDSQ that can be expected. (c)  
    ) Discuss  
2 //the idea of reducing IDQ variation by increasing  
    the value of RS.  
3 //Example 5.26 page no 157  
4 clear  
5 clc  
6 Vdd=24          //V  
7 Idqmax=2.5  
8 Idqmin=1.2  
9 Rs=1           // k
```

```
10 Rd=3          // k
11 Vdsqmax=Vdd-Idqmax*(Rs+Rd)
12 Vdsqmin=Vdd-Idqmin*(Rs+Rd)
13 printf("\n The value of Vdsqmax=%0.3f V" ,Vdsqmax)
14 printf("\n The value of Vdsqmin=%0.3f V" ,Vdsqmin)
```

Scilab code Exa 5.28 Find the range of Idq

```
1 //a) Find the range of IDQ that can be expected if
   R1    1M and R2    3M. (b) Find the range of IDQ
   that can be expected if R1    1M
2 //and R2 = 7M. (c) Discuss the significance of the
   results of parts a and b.
3 //Example 5.28 page no 159
4 clear
5 clc
6 Vdd=24
7 Idqmax=4
8 Idqmin=2.8
9 Rs=2          // M
10 Rd=1         // M
11 Vdsqmax=Vdd-Idqmax*(Rs+Rd)
12 Vdsqmin=Vdd-Idqmin*(Rs+Rd)
13 printf("\n The value of Vdsqmax=%0.3f V" ,Vdsqmax)
14 printf("\n The value of Vdsqmin=%0.3f V" ,Vdsqmin)
```

Chapter 6

SMALL SIGNAL MIDFREQUENCY BJT AMPLIFIERS

Scilab code Exa 6.2 Find an expression for the current gain ratio A_i

```
1 //Find an expression for the current-gain ratio Ai
  iL=is and evaluate it
2 //Example 6.2 page no 175
3 clear
4 clc
5 a=0.99 //alpha
6 Rc=4*10^3      // k
7 Rl=4*10^3      // k
8 Re=5*10^3      // k
9 re=30          //
10 rb=300         //
11 Ai=(a*Rc*Re)/((Rc+Rl)*(Re+re+(1-a)*rb))
12 printf("\n The value of Ai=%0.3f ",Ai)
```

Scilab code Exa 6.7 Calculate the voltage gain Av and the current gain Ai

```
1 //Calculate (a) the voltage gain Av and (b) the
  current gain Ai.
2 //Example 6.7 page no 178
3 clear
4 clc
5 hfe=90
6 Rl=800 //
7 Rc=800 //
8 Rb=831 // k
9 hie=200
10 hoe=100*10^-6
11 Av=-((hfe*Rl*Rc)/(hie*(Rc+Rl+hoe*Rl*Rc)))    //
      voltage gain Av
12 Ai=((Rb*hie)/(Rl*(Rb+hie)))*Av                  //
      current gain Ai
13 printf("\n The value of Av=%0.3f ",Av)
14 printf("\n The value of Ai=%0.3f ",Ai)
```

Scilab code Exa 6.8 determine the voltage gain Av

```
1 //Determine the voltage gain Av
2 //Example 6.8 page no 179
3 clear
4 clc
5 v1=1.1528      //output voltage
6 vi=0.250       //input voltage
7 Av=(v1/vi)     //voltage gain
8 printf("\n The value of Av=%0.3f ",Av)
```

Scilab code Exa 6.18 Find Ai and Av

```

1
2 //Example 6.18 page no 185
3 clear
4 clc
5 Rs=5          // k
6 Rf=100         // k
7 hie=1.1
8 Rc=10          // k
9 Rl=10          // k
10 hfe=50
11 d=((1/Rs)+(1/Rf)+(1/hie))*((1/Rf)+((Rc+Rl)/(Rc*Rl)))
   +((1/Rf)*((hfe/hie)-(1/Rf)))
12 printf("\n The value of d=%0.3f ",d)

```

Scilab code Exa 6.19 Find Ai and iL

```

1 //Example 6.19 page no 186
2 clear
3 clc
4 hfb=-0.99
5 Rc=2.2*10^3
6 Rl=1.1*10^3
7 Re=3.3*10^3
8 hib=25
9 hob=10^-6
10 Av=((Rc*Rl*hfb)/(hib*(Rc+Rl+hob*(Rc*Rl))))
11 Ai=-((Re*Rc*hfb)/((Re+hib)+(Rc+Rl+hob*Rl*Rc)))
12 printf("\n The value of Av=%0.3f ",Av)
13 printf("\n The value of Ai=%0.3f ",Ai)

```

Scilab code Exa 6.22 Find the overall voltage gain Av

```

1 //Find (a) the final-stage voltage gain Av2 vo=vo1;
   (b) the final-stage input impedance Zin2;
2 //(c) the initial-stage voltage gain Av1 vo1=vin; (
   d) the amplifier input impedance Zin1; and
3 //(e) the amplifier voltage gain Av vo=vi.
4 //Example 6.22 page no 189
5 clear
6 clc
7 hfe=40
8 Rc2=20*10^3      //
9 Rc1=10^4          //
10 hie=1500
11 hoe=30*10^-6
12 Av2=-((hfe*Rc2)/(hie*(1+hoe*Rc2)))           //final-
   stage voltage gain
13 printf("\n The value of Av2=%0.3f ",Av2)
14 Rb2=5*10^3      //
15 hie=1500
16 hfe=40
17 Zin2=(((Rb2*hie)/(Rb2+hie))/1000            //final-
   stage input impedance Zin2
18 printf("\n The value of Zin2=%0.3f Kohm ",Zin2)
19 Zin2=Zin2*1000
20 Av1=-((hfe*Zin2*Rc1)/(hie*(Rc1+Zin2+hoe*Zin2*Rc1))) //initial-
   stage voltage gain
21 printf("\n The value of Av1=%0.3f ",Av1)

```

Scilab code Exa 6.24 Find the overall voltage gain Av

```

1 //Example 6.24 page no 191
2 clear
3 clc
4 R11=90*10^3
5 R12=100*10^3
6 R22=90*10^3

```

```

7 R21=10*10^3
8 Av1=0.9879
9 hfe=100
10 Rl=5*10^3
11 Rc=5*10^3
12 hie=1*10^3
13 Rb1=((R11*R12)/(R11+R12))/1000
14 printf("\n The value of Rb1=%0.3f Kohm" ,Rb1)
15 Rb2=((R22*R21)/(R22+R21))/1000
16 printf("\n The value of Rb2=%0.3f Kohm" ,Rb2)
17 Av2=-((hfe*Rl*Rc)/(hie*(Rl+Rc)))
18 printf("\n The value of Av2=%0.3f " ,Av2)
19 Av=Av1*Av2
20 printf("\n The value of Av=%0.3f Kohm" ,Av)

```

Scilab code Exa 6.26 Find the overall voltage gain Av

```

1 //Determine (a) the overall voltage-gain ratio Av =
   vL=vs, and (b) the overall current-gain ratio Ai
   = iL=is.
2 //Example 6.26 page no 193
3 clear
4 clc
5 hfe=100
6 Rl=3*10^3           // k
7 Rc=3*10^3           // k
8 hie=1*10^3
9 Av2=-((hfe*Rl*Rc)/(hie*(Rl+Rc)))
10 printf("\n The value of Av2=%0.3f " ,Av2)
11 Rc1=10*10^3         // k
12 Re1=1*10^3          // k
13 Av1=-((hfe*Rc1*hie)/((Rc1+hie)*((hfe+1)*Re1+hie)))
14 printf("\n The value of Av1=%0.3f " ,Av1)
15 Av=Av1*Av2
16 printf("\n The value of Av=%0.3f " ,Av)

```

```

17 Ai1=-(hfe*Rc1)/(Rc1+hie))
18 printf("\n The value of Ai1=%0.3f ",Ai1)
19 Rc2=3*10^3 // k
20 Ai2=-(hfe*Rc2)/(Rc2+Rl))
21 printf("\n The value of Ai2=%0.3f ",Ai2)
22 Ai=Ai1*Ai2
23 printf("\n The value of Ai=%0.3f ",Ai)

```

Scilab code Exa 6.27 Find the overall voltage gain Av and overall current gain ratio

```

1 //Find (a) the overall voltage-gain ratio
2 //Av      vL=vS and (b) the overall current-gain ratio
3 //Example 6.27 page no 194
4 clear
5 clc
6 hfb1=-0.99
7 hfc2=-100
8 Rb=33.3*10^3
9 Re1=5*10^3
10 Re2=2*10^3
11 Rl=2*10^3
12 hic2=500
13 hib1=50
14 hic2=500
15 Av1=-(hfb1*Rb*hic2)/(hib1*(Rb+hic2)))
16 Av2=0.995
17 Av=Av1*Av2
18 printf("\n The value of Av1=%0.3f ",Av1)
19 printf("\n The value of Av1=%0.3f ",Av)
20 Ai1=-(hfb1*Re1*Rb)/((Re1+hib1)*(Rb+hic2)))
21 printf("\n The value of Ai1=%0.3f ",Ai1)
22 Ai2=-(hfc2*Re2)/(Re2+Rl))
23 printf("\n The value of Ai2=%0.3f ",Ai2)

```

```
24 Ai=Ai1*Ai2
25 printf("\n The value of Ai=%0.3f ",Ai)
```

Chapter 7

SMALL SIGNAL MIDFREQUENCY FET AND TRIODE AMPLIFIERS

Scilab code Exa 7.1 Determine the small signal equivalent circuit constants gm and rds

```
1 //determine
2 //the small-signal equivalent-circuit constants gm
   and rds. (b) Alternatively , evaluate gm from the
3 //transfer characteristic .
4 //Example 7.1 page no 207
5 clear
6 clc
7 Did=(3.3-0.3)*10^-3
8 Vgs=2
9 gm=Did/Vgs*1000
10 printf("\n The value of gm=%0.3f mS" ,gm)
11 Dvds=20-5
12 Did=(1.6-1.4)*10^-3
13 rds=Dvds/Did/1000
14 printf("\n The value of rds=%0.3f kOhm" ,rds)
15 Did=(2-1)*10^-3
```

```
16 Dvgs=-1.75-(-2.4)
17 gm=Did/Dvgs*1000           //mS
18 printf("\n The value of gm=%0.3f mS" ,gm)
```

Scilab code Exa 7.3 Find the overall voltage gain Av and overall current gain ratio

```
1 //Find (a) Av      vds=vi; (b) Zin; (c) Zo looking
   back through the drain-source
2 //terminals, and (d) Ai      ii=iL .
3 //Example 7.3 page no 208
4 clear
5 clc
6 Rl=14*10^3
7 rds=40*10^3
8 Rf=5*10^6
9 gm=1*10^-3
10 Av=((Rl*rds*(1-Rf*gm))/(Rf*rds+Rl*rds+Rl*Rf))
11 printf("\n The value of Av=%0.3f " ,Av)
12 Zin=(Rf/(1-Av))/1000
13 printf("\n The value of Zin=%0.3f kOhm" ,Zin)
14 Ai=(Av*Zin)/Rl*1000
15 printf("\n The value of Ai=%0.3f " ,Ai)
```

Scilab code Exa 7.4 Find the overall voltage gain Av and overall current gain ratio

```
1
2 //Example 7.4 page no 209
3 clear
4 clc
5 R1=200*10^3
6 R2=800*10^3
```

```

7 Zin=(R1*R2/(R1+R2))/1000
8 printf("\n The value of Zin=%0.3f Kohm",Zin)
9 Rg=160*10^3
10 r1=5*10^3
11 vgs=Rg/(Rg+r1)
12 printf("\n The value of vgs=%0.3f vi",vgs)
13 Av=-1.88
14 Rl=2*10^3
15 Ai=(Av*(Rg+r1))/Rl
16 printf("\n The value of ai=%0.3f vi",Ai)

```

Scilab code Exa 7.7 Find the overall voltage gain Av and overall current gain ratio

```

1 //Example 7.7 page no 211
2 clear
3 clc
4 m=2*10^-3
5 Rg=30*10^3
6 Rd=2
7 Rl=4
8 Rg=160
9 r1=5
10 rds=30
11 Rs=3
12 Av=(-m*Rg*Rd*Rl)/((Rg+r1)*((Rd+Rl)*(rds+(m+1)*Rs+Rd*
    Rl)))*1000
13 printf("\n The value of Av=%0.3f ",Av)

```

Scilab code Exa 7.10 Find the overall voltage gain Av and overall current gain ratio and output impedance R0

```

1 //Find (a) the voltage-gain ratio Av      vL=vi , (b)
   the current-gain ratio Ai      iL=ii , and (c) the
   output impedance Ro.
2 //Example 7.10 page no 213
3 clear
4 clc
5 Rg=100          // k
6 ri=5
7 vgs=(Rg/(Rg+ri))
8 gm=0.0025
9 printf("\n The value of vgs=%0.3f vi",vgs)
10 rds=25
11 Rd=2           // k
12 Rl=2           // k
13 Req=(rds*Rd*Rl*10^3)/(2*Rl*Rd+rds*(Rl+Rd))
14 printf("\n The value of Req=%0.3f Kohm",Req)
15 Av=-2*gm*vgs*Req
16 printf("\n The value of Av=%0.3f ",Av)
17 Ai=((Av*(Rg+ri))/Rl)
18 printf("\n The value of Ai=%0.3f ",Ai)
19 R0=(Rd*rds)/(2*Rd+rds)
20 printf("\n The value of R0=%0.3f kOhm",R0)

```

Scilab code Exa 7.11 Find the overall voltage gain Av and overall current gain ratio and output impedance R0

```

1 //Find a current-source small-signal equivalent
   circuit for the CD FET amplifier.
2 //Example 7.11 page no 214
3 clear
4 clc
5 rds=30*10^3
6 Rs2=1.2*10^3
7 Rl=1*10^3          // k
8 gm=0.002

```

```

9 Rg=1*10^6           // k
10 Req=1/((1/rds)+(1/Rs2)+(1/R1))
11 printf("\n The value of Req=%0.3f ",Req)
12 Av=((gm*Rg+1)*Req)/(Rg+(gm*Rg+1)*Req)
13 printf("\n The value of Av=%0.3f ",Av)
14 Ai=(Av*Rg/((1-Av)*R1))
15 printf("\n The value of Ai=%0.3f ",Ai)
16 Rin=Rg/(1-Av)/10^6
17 printf("\n The value of Rin=%0.3f mOhm",Rin)
18 R0=1/(1/Rs2+1/rds+1/Rg+gm)
19 printf("\n The value of R0=%0.3f Ohm",R0)

```

Scilab code Exa 7.12 Find Idm

```

1 //determine the voltage gain of this amplifier
   circuit using SPICE methods.
2 //Example 7.12 page no 215
3 clear
4 clc
5 gm=1.5*10^-3
6 rds=75*10^3
7 Rd=3*10^3           // k
8 rds=75*10^3
9 vds=-(gm*rds*Rd)/(rds+Rd)
10 printf("\n The value of vds=%0.3f vgs",vds)
11 Vdsm=-1*vds        //V
12 idm=(gm+(Vdsm/rds))*1000
13 printf("\n The value of idm=%0.3f mA",idm)

```

Scilab code Exa 7.18 Find the perveance k and the amplification factor m

```

1 // (a) the perveance and (b) the amplification
   factor .
2 //Example 7.18 page no 219
3 clear
4 clc
5 ip=15*10^-3      //mA
6 vp=100            //v
7 k=(ip/(vp^(3/2)))*10^6
8 vg=-4
9 printf("\n The value of k=%0.3f mA/v^3/2" ,k)
10 m=-(vp/vg)
11 printf("\n The value of m=%0.3f " ,m)

```

Scilab code Exa 7.20 Evaluate the plate resistance

```

1 //to evaluate the plate resistance and (b) use (7.10)
   to find the transconductance .
2 //Example 7.20 page no 219
3 clear
4 clc
5 dvp=218-152
6 dip=(14.7-8.1)*10^-3
7 rp=dvp/dip/1000      // k
8 dvg=-2-(-6)
9 gm=dip/dvg*1000      //mS
10 printf("\n The value of rp=%0.3f kOhm" ,rp)
11 printf("\n The value of gm=%0.3f mS" ,gm)

```

Scilab code Exa 7.22 Calculate the voltage gain

```

1 //determine the voltage gain . (c) Calculate the
   voltage gain using small-signal analysis
2 //Example 7.22 page no 220

```

```

3 clear
4 clc
5 Vpp=300 //V
6 Vgq=4 //V
7 Rl=11.6*10^3 //
8 Vpm=34 //V
9 Vgm=2
10 Av=-(2*Vpm/2*Vgm)
11 dvp=202-168
12 dip=(15-8)*10^-3
13 rp=dvp/dip/1000 // k
14 dip=(15.5-6.5)*10^-3
15 dvg=-3-(-5)
16 gm=dip/dvg*1000 //ms
17 m=21.87
18 Rl=11.6 //
19 Av=-(m*Rl*10^3)/((Rl+rp)*10^3) // Voltage gain
20 printf("\n The value of rp=%0.3f kOhm",rp)
21 printf("\n The value of gm=%0.3f mS",gm)
22 printf("\n The value of Av=%0.3f ",Av)

```

Chapter 8

FREQUENCY EFFECTS IN AMPLIFIERS

Scilab code Exa 8.6 Determine the low frequency voltage gain ratio if hie

```
1 //determine the low-frequency voltage-gain ratio if
   hie and hfe have median values.
2 //Example 8.6 page no 242
3 clear
4 clc
5 hie=1000    //
6 hfe=75      //
7 Av=50
8 Req=Av*(hie/hfe)    //
9 printf("\n The value of Req=%0.3f Ohm",Req)
10 Rl=10000   // k
11 Rc=Req*Rl/(Rl-Req) // k
12 printf("\n The value of Rc=%0.3f Ohm",Rc)
13 hie=300    //
14 hfe=100    //
15 Re=1000    // k
16 wL=2*pi*200
17 Ce=(hie+(hfe+1)*Re)/(wL*Re*hie)*10^6
18 printf("\n The value of Ce=%0.3f mF",Ce)
```

```
19 Av=(hfe*Req)/(hie+(hfe+1)*Re)
20 printf("\n The value of Av=%0.3f ",Av)
```

Scilab code Exa 8.8 Determine the low frequency gain the midfrequency gain and the low frequency cutoff point

```
1 //Determine (a) the low-frequency gain , (b) the
   midfrequency gain , and (c) the low-frequency
   cutoff point .
2 //Example 8.8 page no 244
3 clear
4 clc
5 hie2=1500      //
6 Rb2=5000      // k
7 Z01=10
8 C2=1*10^-6
9 Zin2=(hie2*Rb2/(hie2+Rb2))
10 printf("\n The value of Zin2=%0.3f Ohm",Zin2)
11 Av=7881.3
12 f1=1/(2*pi*C2*(Zin2+Z01*10^3))
13 printf("\n The value of f1=%0.3f Hz",f1)
```

Chapter 9

OPERATIONAL AMPLIFIERS

Scilab code Exa 9.2 Evaluate the gain of this inverting amplifier

```
1 // derive an exact formula for the gain of a
   practical inverting op amp.
2 //Example 9.2 page no 268
3 clear
4 clc
5 Aol=-10^4
6 Rl=1           // k
7 Rf=10          // k
8 Rd=1           // k
9 Av=(Aol/(1+(Rl/Rf)*(1-Aol)+(Rl/Rd)))
10 printf("\n The value of Av=%0.3f ",Av)
```

Scilab code Exa 9.9 Find the regulated output v_o in terms of V_Z

```
1 //Find the regulated output  $v_o$  in terms of  $V_Z$ . (b)
   Given a specific Zener diode and the values of  $R_S$ 
   and  $R_1$ 
```

```
2 //Example 9.9 page no 272
3 clear
4 clc
5 Aol=-10^4
6 Rl=1
7 Rf=10
8 Rd=1
9 Av=(Aol/(1+(Rl/Rf)*(1-Aol)+(Rl/Rd)))
10 printf("\n The value of Av=%0.3f ",Av)
```

Scilab code Exa 9.12 Find the value of C

```
1
2 //Example 9.12 page no 274
3 clear
4 clc
5 R=10*10^3    //
6 f=100          //Hz
7 C=(0.1/(2*pi*f*R))*10^9      //Capicitor
8 printf("\n The value of C=%0.3f nF",C)
```

Scilab code Exa 9.25 Find the value of Av

```
1 //Use SPICE methods to simulate this amplifier
2 //Example 9.25 page no 281
3 clear
4 clc
5 R1=10*10^3    //
6 R2=20*10^3    //
7 R3=20*10^3    //
8 Av=-((R2*R3)/(R1*(R2+R3)))
9 printf("\n The value of Av=%0.3f ",Av)
```

Chapter 10

Switched Mode Power Supplies

Scilab code Exa 10.1 Find the average values of input voltage and input current

```
1 //Find the average values of (a) input voltage and (b) input current.  
2 //Example 10.1 page no 296  
3 clear  
4 clc  
5 V2=12          //load  
6 D=0.8          //duty cycle  
7 V1=V2/D        //V  
8 P0=20          //average power  
9 I1=P0/V1  
10 printf("\n The value of I1=%0.3f A", I1)
```

Scilab code Exa 10.2 Determine the smallest value of duty cycle possible

```
1 //Determine the smallest value of duty cycle possible  
2 //Example 10.2 page no 296
```

```

3 clear
4 clc
5 fs=30*10^3           //kHz .
6 Lc=50*10^-6          // Inductor H
7 Rl=7                  //Load
8 D=1-((2*fs*Lc)/Rl)
9 printf("\n The value of D=%0.3f ",D)

```

Scilab code Exa 10.4 Determine the duty cycle and the output power

```

1 // Determine (a) the duty cycle and (b) the output
   power .
2 //Ts for the buck converter .
3 //Example 10.4 page no 296
4 clear
5 clc
6 V2=5           //V
7 V1=12          //V
8 D=V2/V1
9 Rl=5           //
10 V2=5          //V
11 p0=V2^2/Rl
12 printf("\n The value of D=%0.3f ",D)
13 printf("\n The value of p0=%0.3f ",p0)

```

Scilab code Exa 10.7 Find the maximum and minimum values of the inductor current

```

1 //Find the maximum and minimum values of the
   inductor current
2 //Example 10.7 page no 297
3 clear
4 clc

```

```

5 D=0.6           //Duty cycle
6 V1=24            //V
7 Rl=7
8 fs=30*10^3
9 L=50*10^-6
10 V2=D*V1
11 Imax=V2/Rl+((V1-V2)*D)/(2*fs*L)           //maximum
      values of the inductor current
12 Imin=V2/Rl-((V1-V2)*D)/(2*fs*L)           // minimum
      values of the inductor current
13 printf("\n The value of Imax=%0.3f A ",Imax)
14 printf("\n The value of Imin=%0.3f A",Imin)

```

Scilab code Exa 10.9 Example 10 page no 298

```

1 //Determine (a) the output voltage , (b) the load
   resistance , and (c) the load current .
2 //Example 10.9
3 //page no 298
4 clear
5 clc
6 V1=12
7 D=0.6
8 V2=V1/(1-D)           //output voltage
9 P0=60                  //w Supplying power
10 Rl=V2^2/P0             //load resistance
11 I2=V2/Rl               //load current
12 printf("\n The value of V2=%0.3f V ",V2)
13 printf("\n The value of Rl=%0.3f ohm",Rl)
14 printf("\n The value of I2=%0.3f A ",I2)

```
