

Scilab Textbook Companion for
Engineering Circuit Analysis
by W. Hayt, J. Kemmerly And S. Durbin¹

Created by
Dhaivat Udayan Mandavia
B.E
Electronics Engineering
B.V.B.College of Engineering and Technology
College Teacher
Prof.sujata Kotabagi
Cross-Checked by

May 19, 2016

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Engineering Circuit Analysis

Author: W. Hayt, J. Kemmerly And S. Durbin

Publisher: Tata McGraw - Hill Education, New Delhi

Edition: 6

Year: 2008

ISBN: 0070611054

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 Basic components and Electric Circuits	6
3 Voltage and Current laws	10
4 Basic Nodal and Mesh Analysis	26
6 Network Theorems and useful Circuit Analysis Techniques	43
7 Capacitors and Inductors	70
8 Basic RL and RC circuits	77
9 The RLC Circuit	87
10 Sinusoidal Steady state Analysis	98
11 AC Circuit Power Analysis	108
12 Polyphase Circuits	117
13 Magnetically coupled circuits	124
14 Complex frequency and the Laplace Transform	129
15 Circuit Analysis in the s domain	135
16 Frequency Response	139

17 Two Port Networks	148
18 Fourier Circuit Analysis	155

List of Scilab Codes

Exa 2.1	Power	6
Exa 2.2	Dependent sources	7
Exa 2.3	Ohm law	7
Exa 2.4	Ohm law	8
Exa 6.10	The Superposition principle	51
Exa 6.17	Reciprocity Theorem	57
Exa 6.18	Reciprocity Theorem	60
Exa 6.19	Millman Theorem	61
Exa 6.22	Tellegen Theorem	64
Exa 7.1	The Capacitor	70
Exa 7.2	The Capacitor	70
Exa 7.3	The Capacitor	73
Exa 7.7	The Inductor	74
Exa 9.1	The Source free parallel circuit	87
Exa 9.4	Graphical Representation of Overdamped response	88
Exa 10.4	The Inductor	98
Exa 11.1	Instantaneous Power	108
Exa 11.2	Average Power	110
Exa 11.3	Average Power	111
Exa 11.4	Average Power	112
Exa 11.6	Average Power for Non periodic Functions	113
Exa 11.7	Average Power for Non periodic Functions	114
Exa 11.8	Apparent Power and Power factor	114
Exa 11.9	Complex Power	115
Exa 12.2	Three phase Wye connection	117
Exa 12.3	Three phase Wye connection	119
Exa 12.4	Three phase Wye connection	120
Exa 12.5	The Delta connection	121

Exa 12.6	The Delta connection	121
Exa 12.7	Power measurement in three phase systems	122
Exa 13.2	Mutual Inductance	124
Exa 13.4	Energy considerations	125
Exa 13.5	T and PI equivalent networks	125
Exa 13.6	T and PI equivalent networks	126
Exa 13.8	Equivalent Circuits	128
Exa 14.2	Definition of the Laplace Transform	129
Exa 14.3	Inverse Transform Techniques	129
Exa 14.4	Inverse Transform Techniques	130
Exa 14.5	Inverse Transform Techniques	130
Exa 14.6	Inverse Transform Techniques	131
Exa 14.7	Basic Theorems for the Laplace Transform	131
Exa 14.8	Basic Theorems for the Laplace Transform	132
Exa 14.9	Basic Theorems for the Laplace Transform	132
Exa 14.10	The time shift theorem	133
Exa 14.11	The Initial and Final value theorems	133
Exa 15.1	Modeling Inductors in the s domain	135
Exa 15.2	Modeling capacitors in the s domain	136
Exa 15.4	Nodal and Mesh analysis in s domain	136
Exa 15.6	Additional circuit analysis techniques	137
Exa 15.9	Convolution and Laplace Transform	137
Exa 15.10	Convolution and Laplace Transform	138
Exa 16.1	Parallel Resonance	139
Exa 16.2	Bandwidth and high Q circuits	139
Exa 16.3	Series Resonance	140
Exa 16.4	Other resonant forms	141
Exa 16.5	Equivalent Series and parallel combination	142
Exa 16.6	Scaling	142
Exa 16.8	Bode diagrams	143
Exa 16.10	Bode diagrams	145
Exa 16.11	Filters	145
Exa 16.12	Filters	146
Exa 16.13	Filters	146
Exa 17.1	One port networks	148
Exa 17.2	One port networks	149
Exa 17.3	One port networks	149
Exa 17.7	Some equivalent networks	150

Exa 17.8	Impedance parameters	152
Exa 17.9	Hybrid parameters	153
Exa 17.10	Transmission parameters	154
Exa 18.1	Trigonometric form of the Fourier Series	155
Exa 18.5	Definition of the Fourier Transform	157
Exa 18.6	Physical significance of Fourier Transform	160

List of Figures

3.1	Kirchoff current law	11
3.2	Kirchoff current law	12
3.3	Kirchoff voltage law	13
3.4	Kirchoff voltage law	14
3.5	Kirchoff voltage law	15
3.6	Kirchoff voltage law	16
3.7	Kirchoff voltage law	17
3.8	Kirchoff voltage law	17
3.9	The Single Loop Circuit	18
3.10	The Single Loop Circuit	18
3.11	The single node pair circuit	19
3.12	The single node pair circuit	19
3.13	Series and Parallel connected sources	20
3.14	Series and Parallel connected sources	21
3.15	Resistors in series and parallel	22
3.16	Resistors in series and parallel	22
3.17	Voltage and Current division	23
3.18	Voltage and Current division	23
3.19	Voltage and Current division	24
3.20	Voltage and Current division	25
4.1	Nodal analysis	27
4.2	Nodal analysis	27
4.3	Nodal analysis	28
4.4	Nodal analysis	28
4.5	The supernode	29
4.6	The supernode	30
4.7	The supernode	31
4.8	The supernode	31

4.9	Mesh analysis	32
4.10	Mesh analysis	33
4.11	Mesh analysis	34
4.12	Mesh analysis	35
4.13	Mesh analysis	36
4.14	Mesh analysis	37
4.15	Mesh analysis	38
4.16	Mesh analysis	39
4.17	The Supermesh	40
4.18	The Supermesh	41
4.19	The Supermesh	42
4.20	The Supermesh	42
6.1	The Superposition principle	44
6.2	The Superposition principle	44
6.3	The Superposition principle	45
6.4	The Superposition principle	45
6.5	The Superposition principle	46
6.6	The Superposition principle	46
6.7	The Superposition principle	47
6.8	The Superposition principle	48
6.9	The Superposition principle	48
6.10	The Superposition principle	49
6.11	The Superposition principle	49
6.12	The Superposition principle	50
6.13	Thevenin and Norton Equivalent circuit	52
6.14	Thevenin and Norton Equivalent circuit	53
6.15	Thevenin and Norton Equivalent circuit	54
6.16	Thevenin and Norton Equivalent circuit	54
6.17	Thevenin and Norton Equivalent circuit	55
6.18	Thevenin and Norton Equivalent circuit	56
6.19	Thevenin and Norton Equivalent circuit	57
6.20	Thevenin and Norton Equivalent circuit	58
6.21	Maximum power transfer	59
6.22	Maximum power transfer	59
6.23	Compensation Theorem	62
6.24	Compensation Theorem	63
6.25	Compensation Theorem	64

6.26	Compensation Theorem	65
6.27	Source Transformations	66
6.28	Source Transformations	67
6.29	Source Transformations	67
6.30	Source Transformations	68
7.1	The Capacitor	71
7.2	The Capacitor	71
7.3	The Capacitor	72
7.4	The Capacitor	73
7.5	Modeling Capacitors and Inductors	75
7.6	Modeling Capacitors and Inductors	76
8.1	The Source free RL Circuit	78
8.2	The Source free RL Circuit	78
8.3	The Source free RL Circuit	79
8.4	The Source free RL Circuit	79
8.5	The Source free RC Circuit	80
8.6	The Source free RC Circuit	81
8.7	A more General Perspective	82
8.8	A more General Perspective	82
8.9	Natural and Forced Response	83
8.10	Natural and Forced Response	83
8.11	Driven RC circuits	84
8.12	Driven RC circuits	85
8.13	Driven RC circuits	86
8.14	Driven RC circuits	86
9.1	The Overdamped parallel circuit	88
9.2	The Overdamped parallel circuit	89
9.3	The Overdamped parallel circuit	90
9.4	The Overdamped parallel circuit	90
9.5	Graphical Representation of Overdamped response	91
9.6	The Underdamped parallel RLC circuit	92
9.7	The Underdamped parallel RLC circuit	93
9.8	The Source free series RLC Circuit	93
9.9	The Source free series RLC Circuit	94
9.10	The Source free series RLC Circuit	95

9.11	The Source free series RLC Circuit	96
9.12	The Complete response of RLC circuit	97
9.13	The Complete response of RLC circuit	97
10.1	Forced Response to sinusoidal functions	99
10.2	Forced Response to sinusoidal functions	99
10.3	Impedance	100
10.4	Impedance	101
10.5	Nodal and Mesh analysis	101
10.6	Nodal and Mesh analysis	102
10.7	Nodal and Mesh analysis	103
10.8	Nodal and Mesh analysis	103
10.9	Superposition Source Transformations and Thevenin theorem	104
10.10	Superposition Source Transformations and Thevenin theorem	105
10.11	Superposition Source Transformations and Thevenin theorem	106
10.12	Superposition Source Transformations and Thevenin theorem	106
10.13	Superposition Source Transformations and Thevenin theorem	107
10.14	Superposition Source Transformations and Thevenin theorem	107
11.1	Average Power	109
11.2	Average Power	110
11.3	Average Power	112
11.4	Average Power	113
12.1	Single phase three wire systems	118
13.1	The Ideal Transformer	127
13.2	The Ideal Transformer	127
16.1	Bode diagrams	143
16.2	Bode diagrams	144
17.1	Admittance parameters	151
17.2	Admittance parameters	151
18.1	Trigonometric form of the Fourier Series	156
18.2	Complete Response to periodic Forcing Functions	157
18.3	Complete Response to periodic Forcing Functions	158
18.4	Definition of the Fourier Transform	158
18.5	The physical significance of system function	161

18.6 The physical significance of system function 161

Chapter 2

Basic components and Electric Circuits

Scilab code Exa 2.1 Power

```
1 //Example 2.1
2 //Computation of power absorbed by each part
3 //From figure 2.13a
4 V=2;I=3;
5 //We have Power(P)=V*I
6 P=V*I
7 printf("a) Power =%dW\n",P)
8 if P>0 then
9     printf("Power is absorbed by the element\n")
10 else
11     printf("Power is supplied by the element\n");
12 end
13
14 clear P;
15 //From figure 2.13b
16 V=-2;I=-3;
17 //We have Power(P)=V*I
18 P=V*I
19 printf("b) Power =%dW\n",P)
```

```

20 if P>0 then
21     printf("Power is absorbed by the element\n")
22 else
23     printf("Power is supplied by the element\n")
24 end
25
26 //From figure 2.13c
27 V=4; I=-5;
28 //We have Power(P)=V*I
29 P=V*I
30 printf("c) Power =%dW\n",P)
31 if P>0 then
32     printf("Power is absorbed by the element\n")
33 else
34     printf("Power is supplied by the element\n")
35 end

```

Scilab code Exa 2.2 Dependent sources

```

1 //Example 2.2
2 // Calculate vL
3 disp(" Given")
4 disp(" v2=3V")
5 v2=3;
6 //From figure 2.19b
7 disp(" Considering the right hand part of the circuit
      ")
8 disp(" vL=5v2")
9 vL=5*v2;
10 disp(" On substitution")
11 printf(" vL=%dV\n", vL);

```

Scilab code Exa 2.3 Ohm law

```

1 //Example 2.3
2 //Calculate the voltage and power dissipated across
   the resistor terminals
3 //From figure 2.24b
4 disp(" Given")
5 disp("R=560 ohm ; i=428mA")
6 R=560; i=428*10^-3;
7 //Voltage across a resistor is
8 disp("v=R*i")
9 v=R*i;
10 printf(" Voltage across a resistor=%3.3fV\n",v)
11
12 //Power dissipated by the resistor is
13 disp(" p=v*i")
14 p=v*i;
15 printf(" Power dissipated by the resistor=%3.3fW\n",p
   )

```

Scilab code Exa 2.4 Ohm law

```

1 //Example 2.4
2 //Calculate the power dissipated within the wire
3 //From figure 2.27
4 disp(" Given")
5 disp(" Total length of the wire is 4000 feet")
6 disp(" Current drawn by lamp is 100A")
7 //Considering American Wire Gauge system (AWG)
8 //Referring Table 2.4
9 disp(" 4AWG=0.2485ohms/1000 ft")
10 l=4000; i=100 ; r1=0.2485/1000;
11 //Let R be the wire resistance
12 R=l*r1;
13 //Let p be the power dissipated within the wire
14 disp(" p=i^2*R")
15 p=i^2*R

```



```
16 printf("Power dissipated within the wire=%dW\n",p)
```

Chapter 3

Voltage and Current laws

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

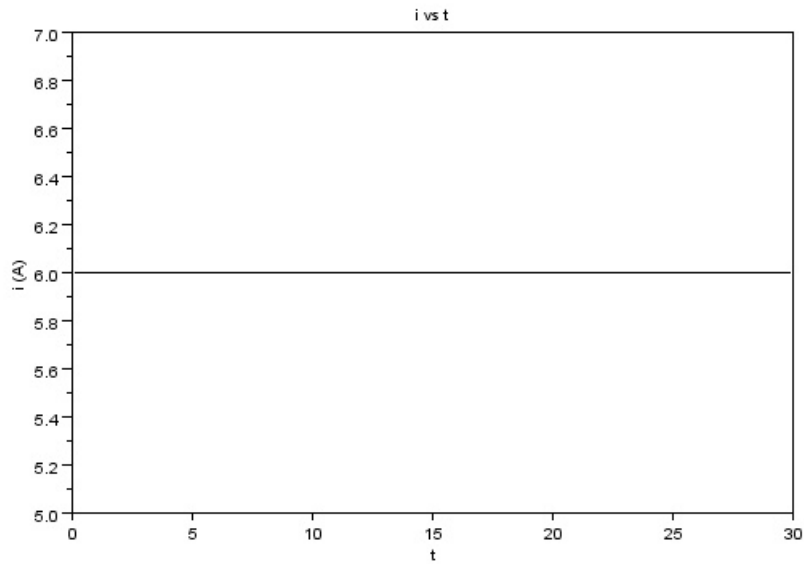


Figure 3.1: Kirchoff current law

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

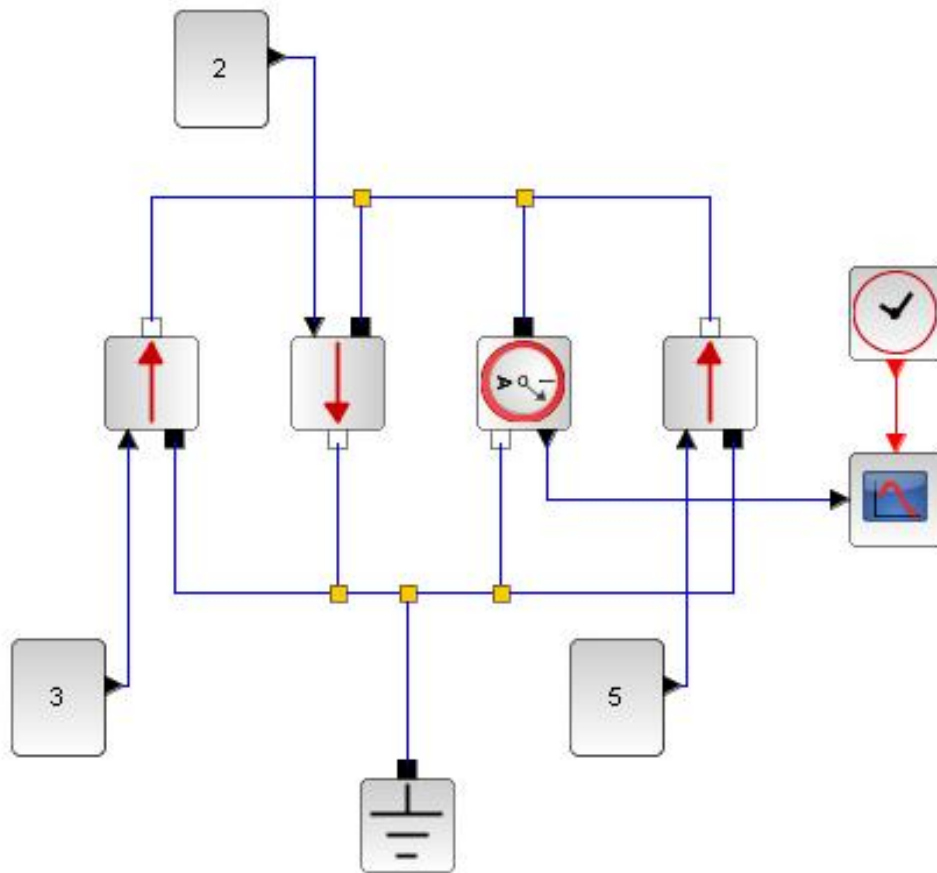


Figure 3.2: Kirchoff current law

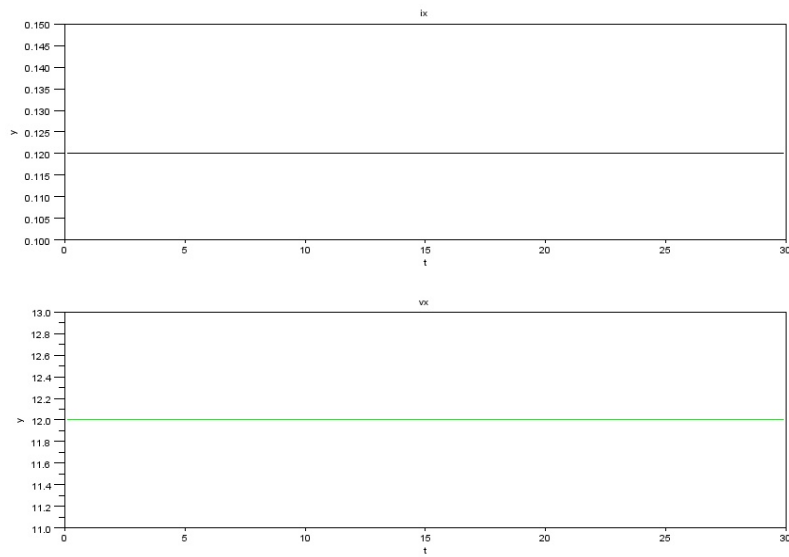


Figure 3.3: Kirchoff voltage law

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

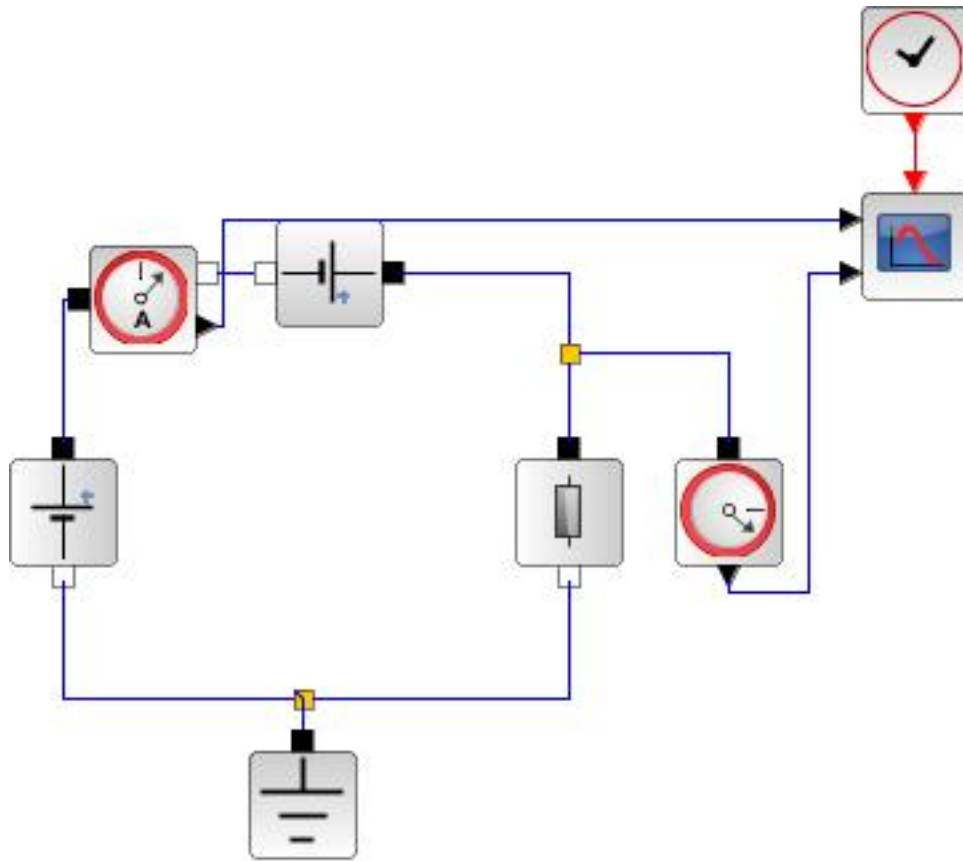


Figure 3.4: Kirchoff voltage law

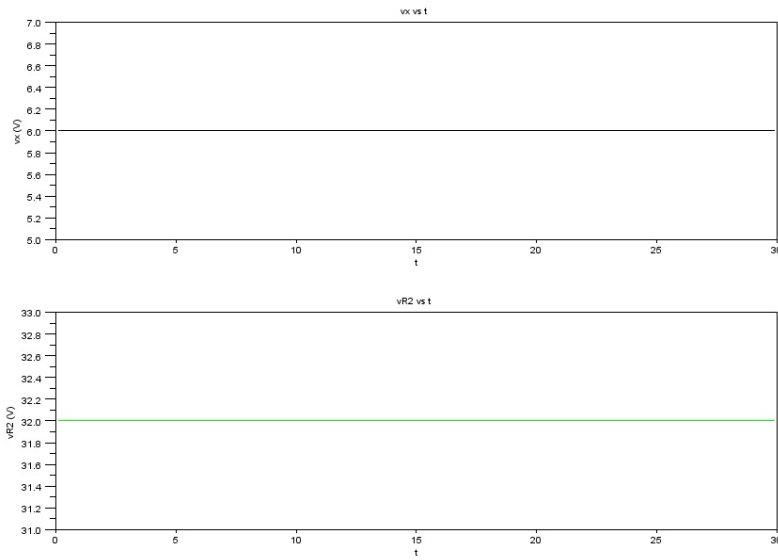


Figure 3.5: Kirchoff voltage law

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

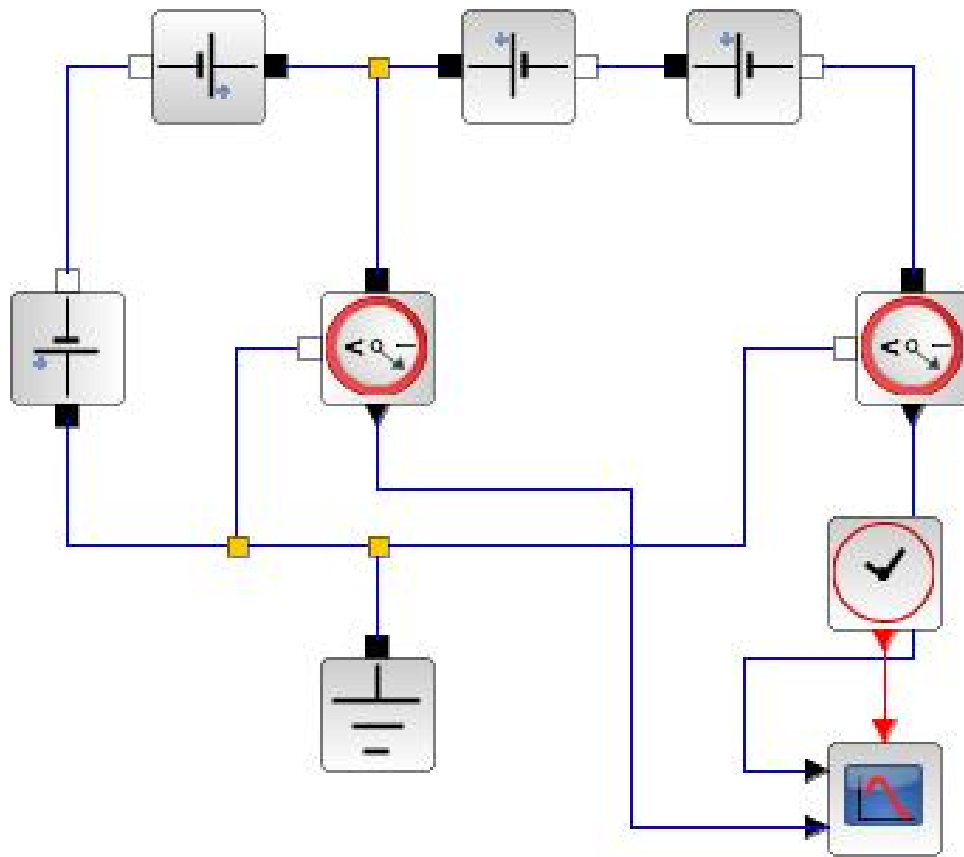


Figure 3.6: Kirchoff voltage law

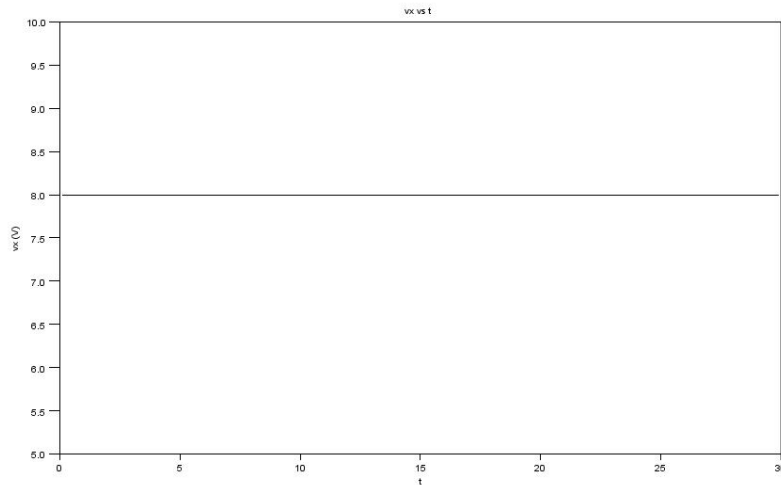


Figure 3.7: Kirchoff voltage law

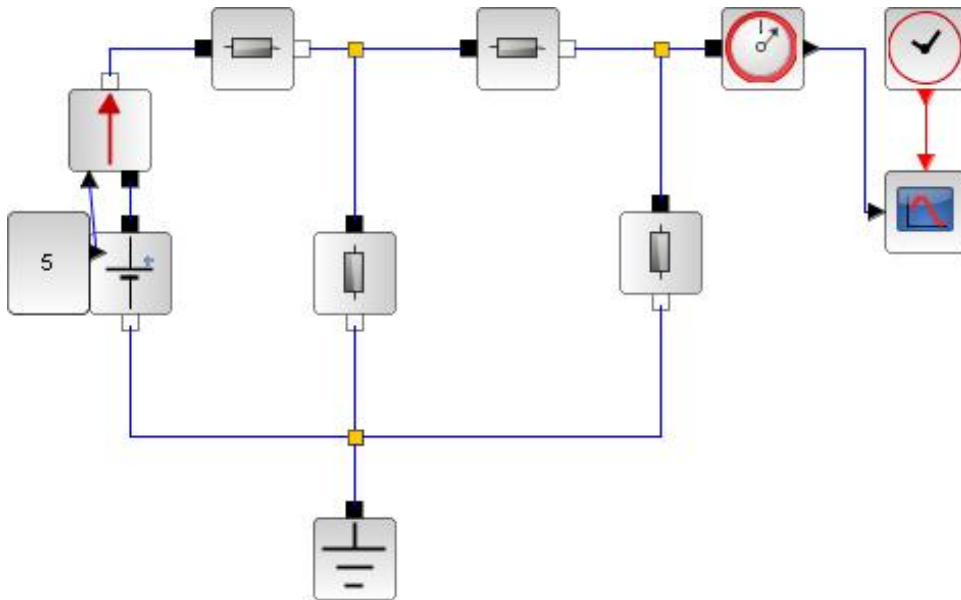


Figure 3.8: Kirchoff voltage law

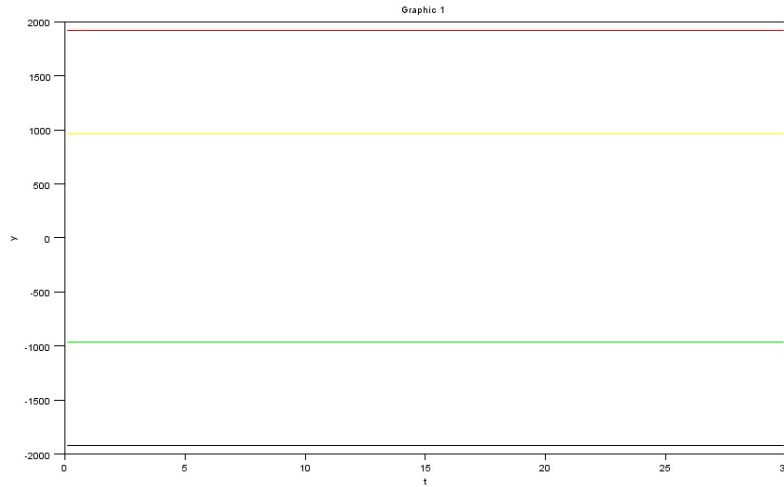


Figure 3.9: The Single Loop Circuit

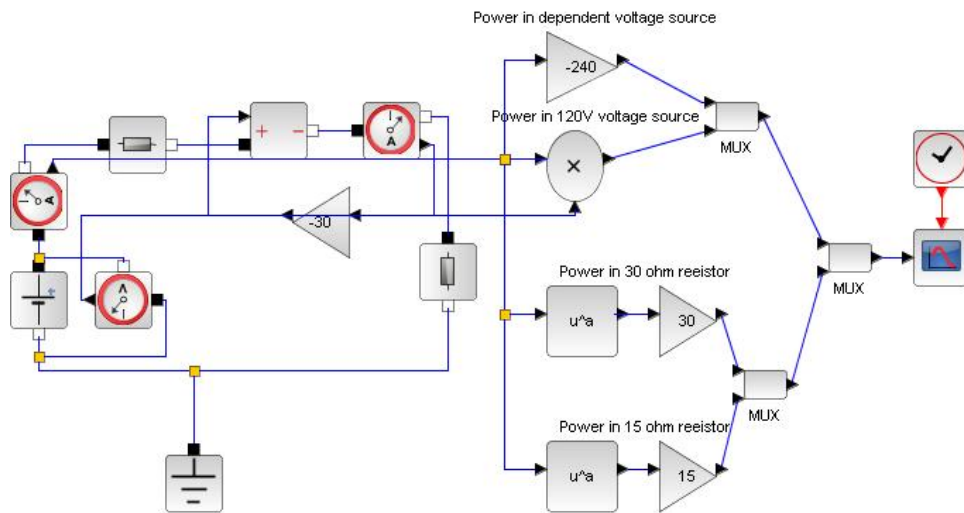


Figure 3.10: The Single Loop Circuit

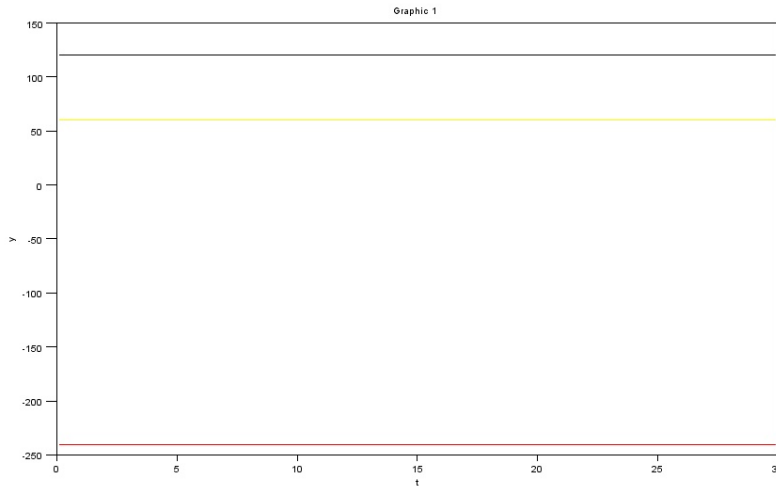


Figure 3.11: The single node pair circuit

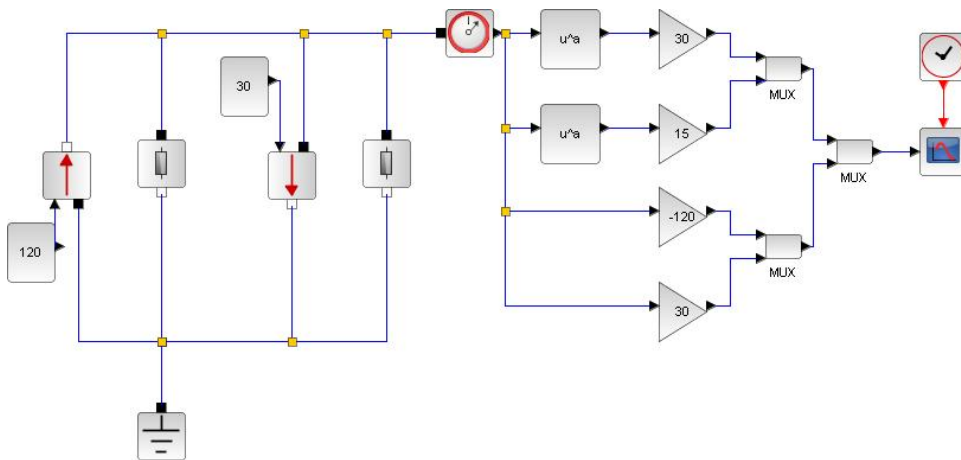


Figure 3.12: The single node pair circuit

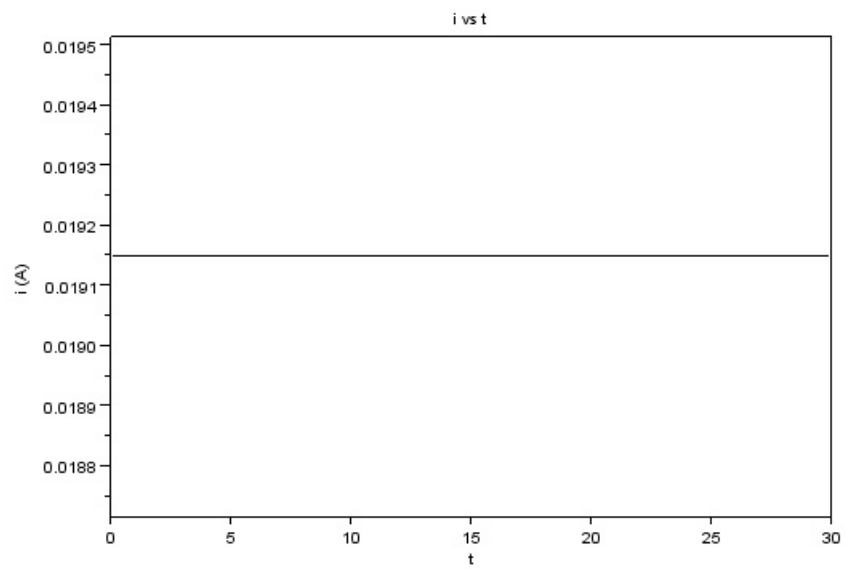


Figure 3.13: Series and Parallel connected sources

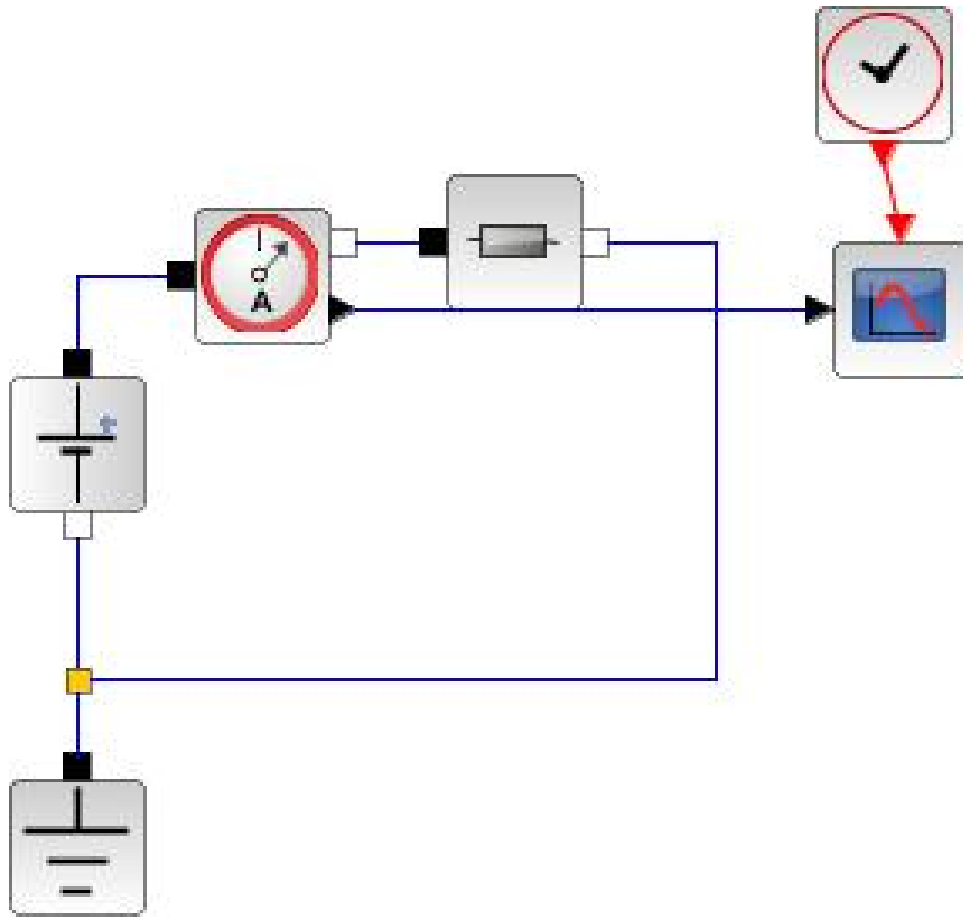


Figure 3.14: Series and Parallel connected sources

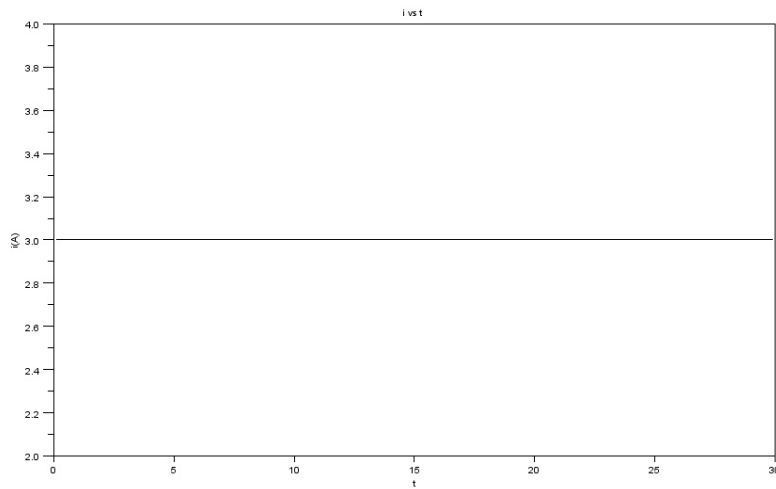


Figure 3.15: Resistors in series and parallel

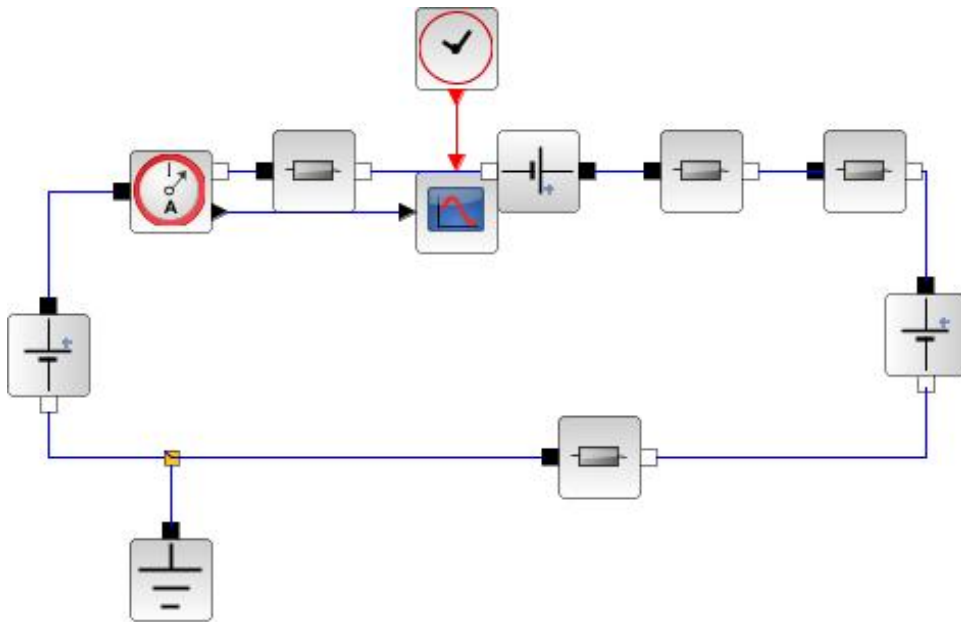


Figure 3.16: Resistors in series and parallel

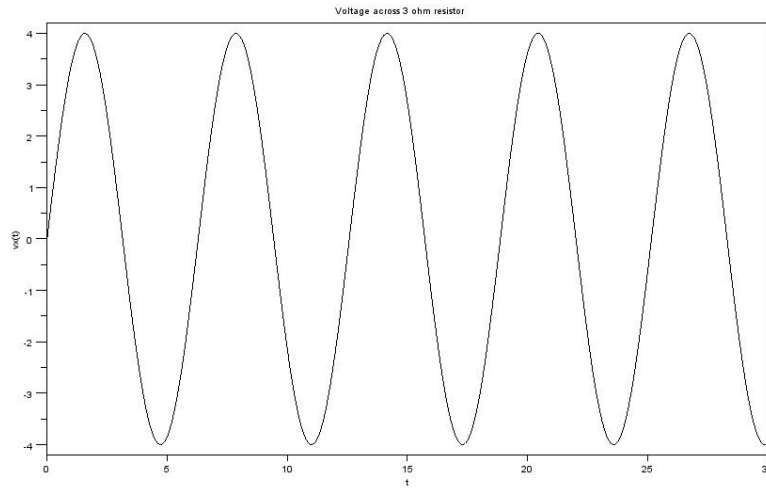


Figure 3.17: Voltage and Current division

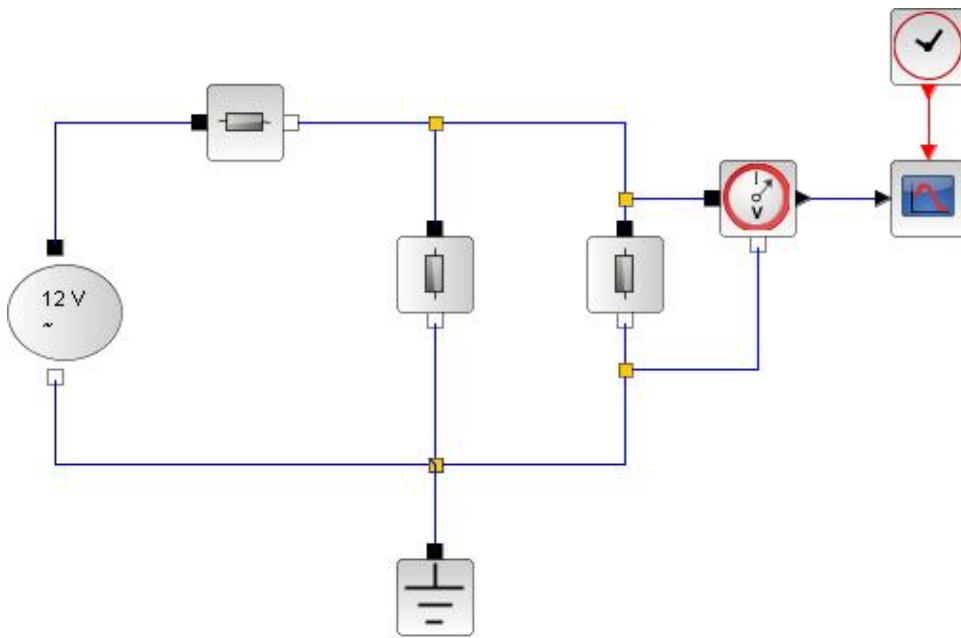


Figure 3.18: Voltage and Current division

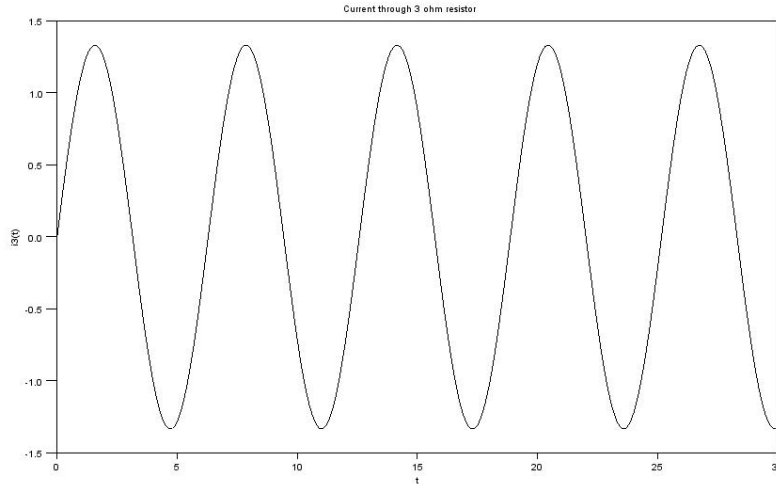


Figure 3.19: Voltage and Current division

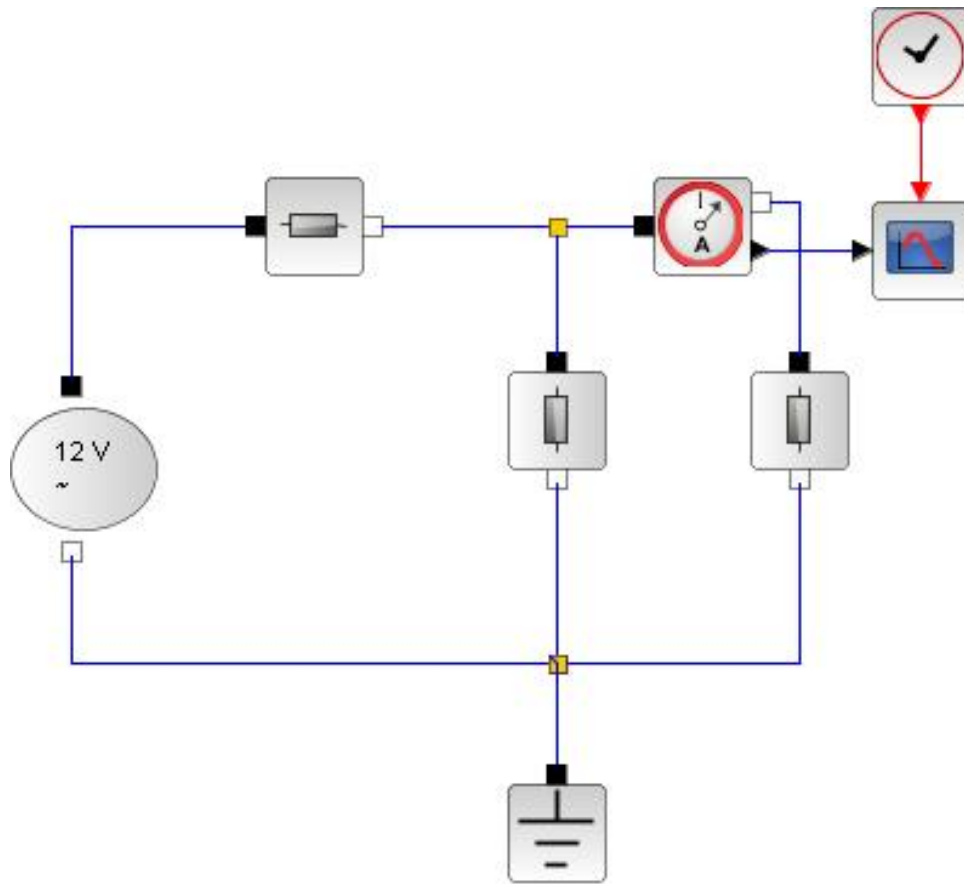


Figure 3.20: Voltage and Current division

Chapter 4

Basic Nodal and Mesh Analysis

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

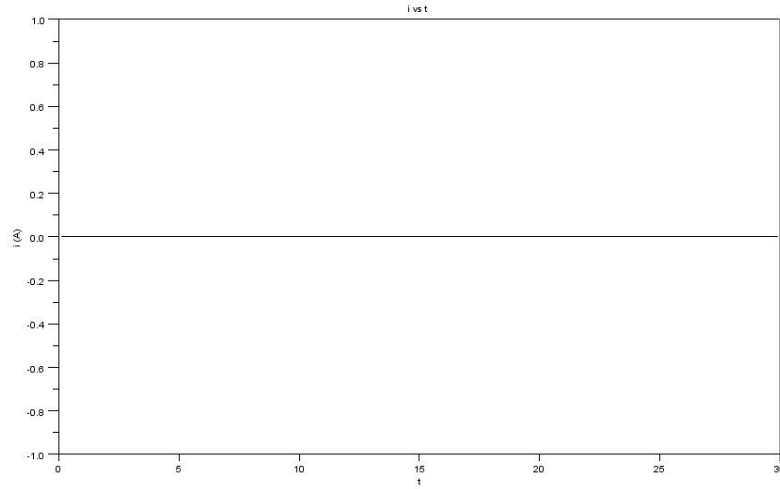


Figure 4.1: Nodal analysis

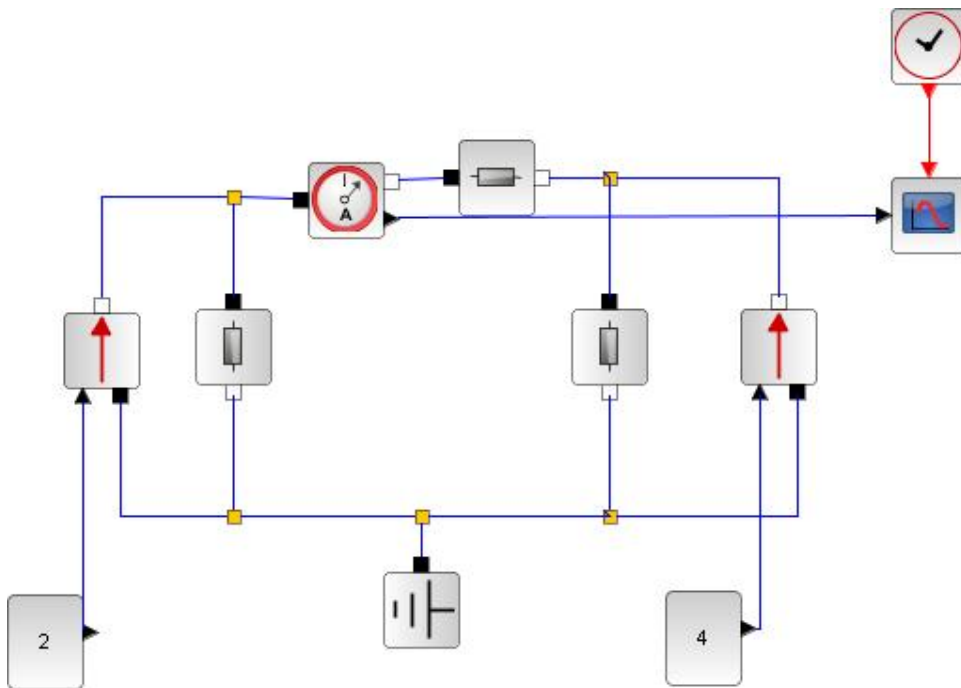


Figure 4.2: Nodal analysis

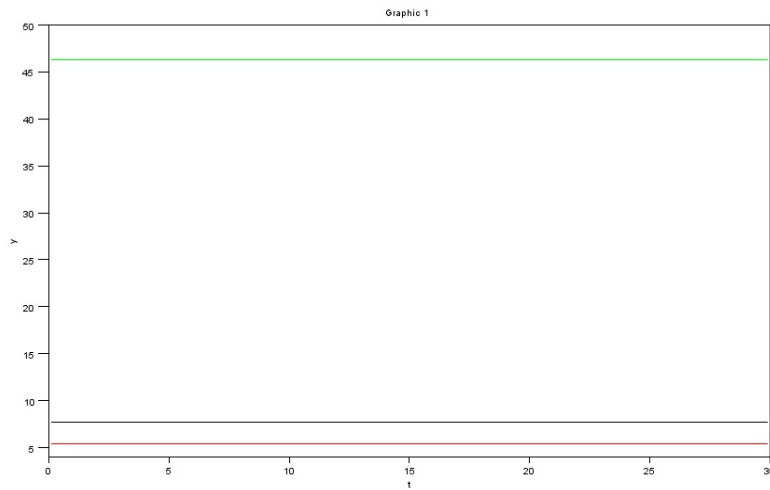


Figure 4.3: Nodal analysis

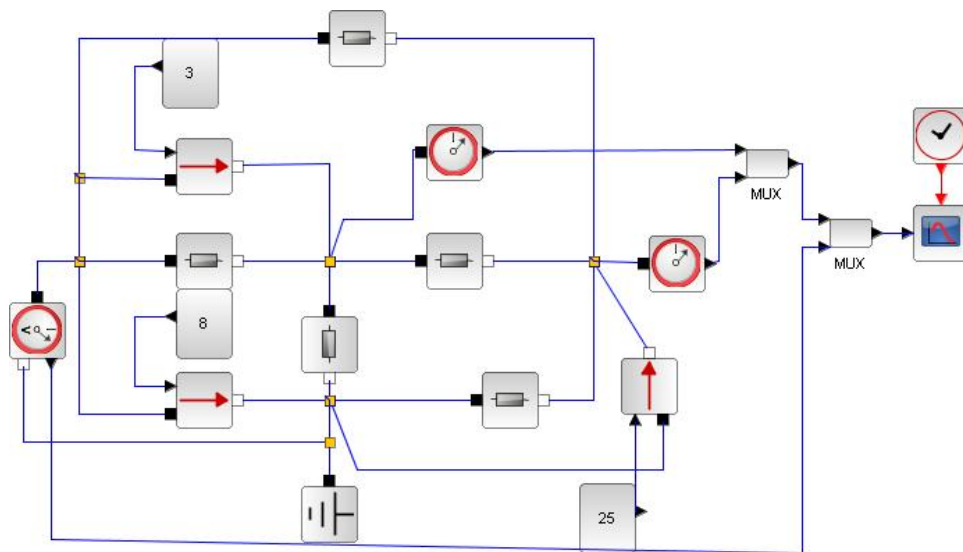


Figure 4.4: Nodal analysis

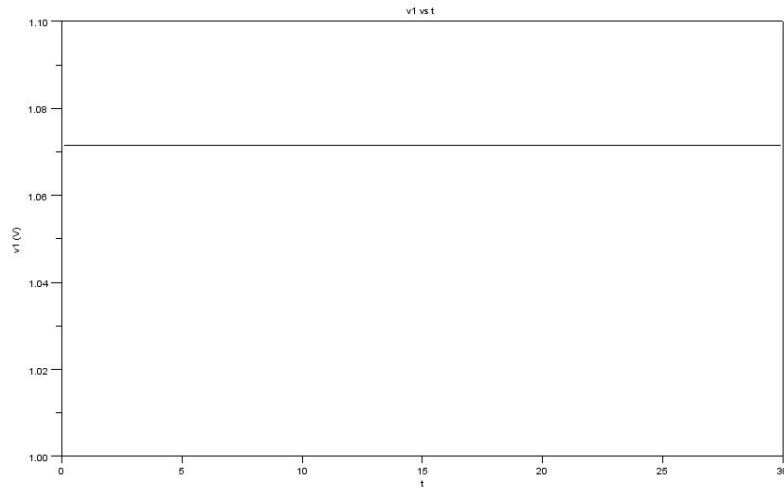


Figure 4.5: The supernode

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

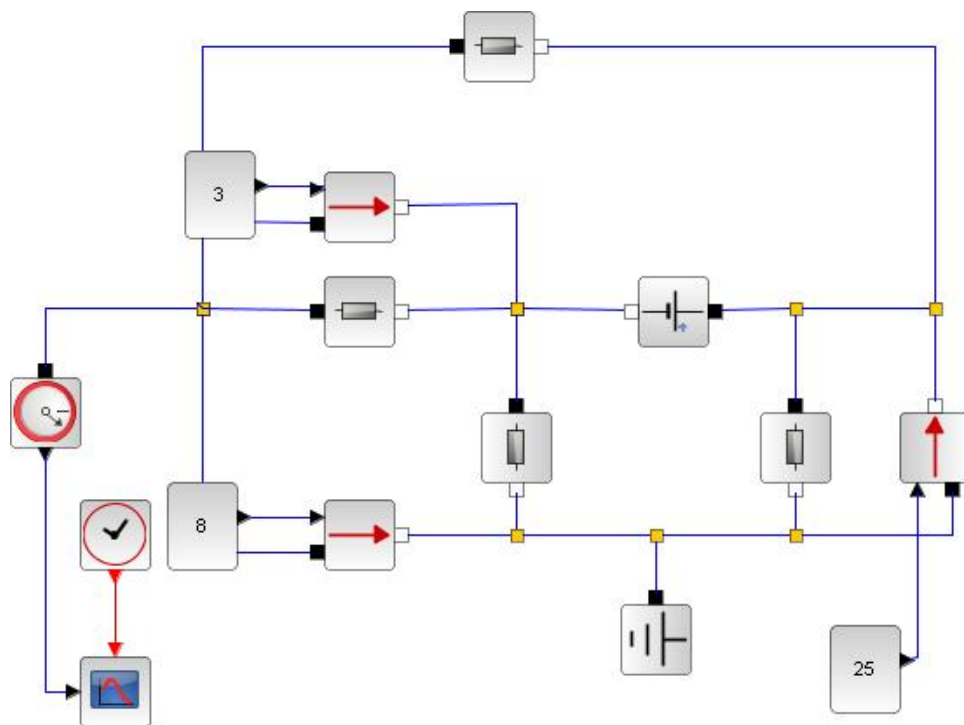


Figure 4.6: The supernode

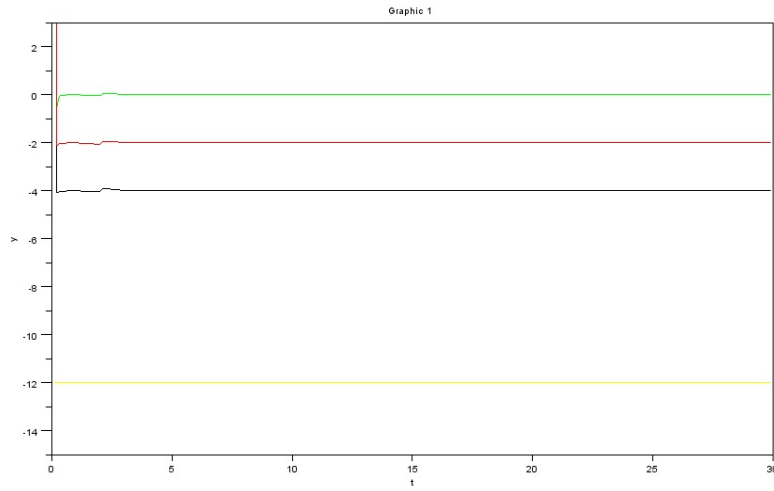


Figure 4.7: The supernode

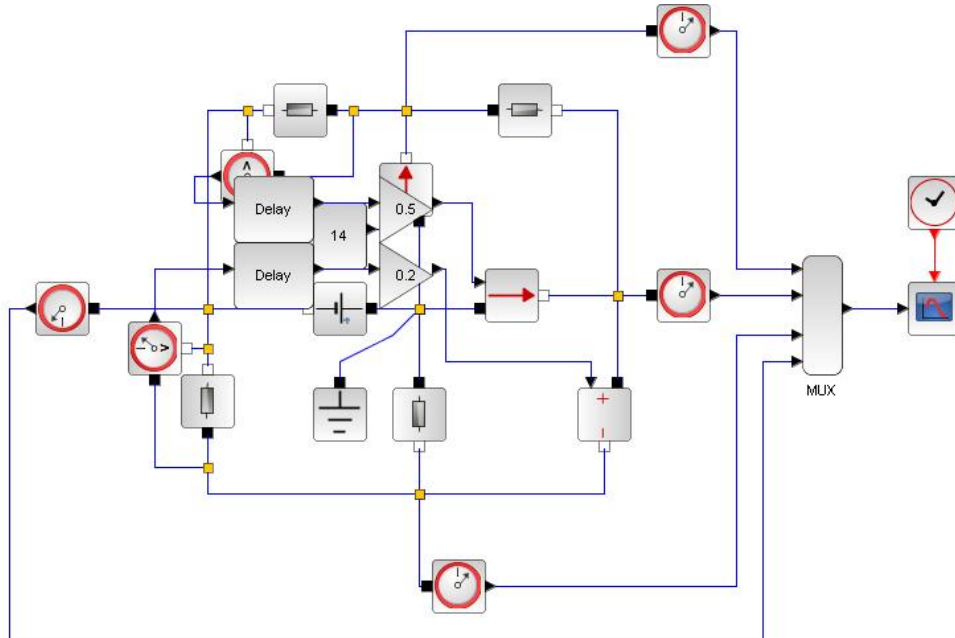


Figure 4.8: The supernode

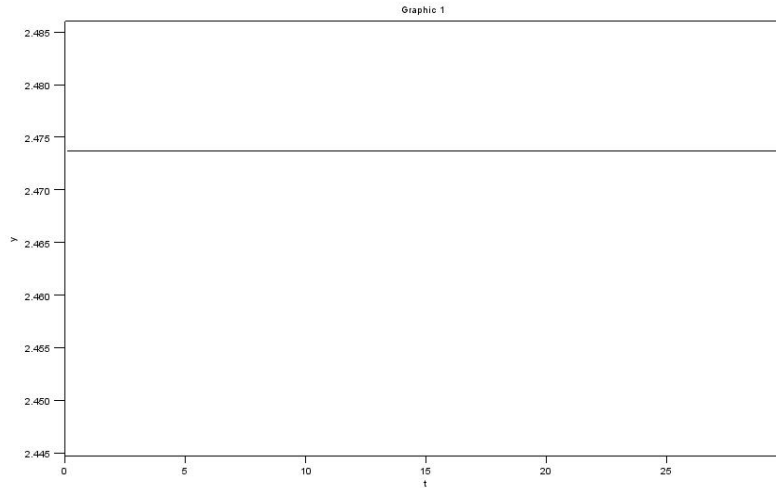


Figure 4.9: Mesh analysis

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

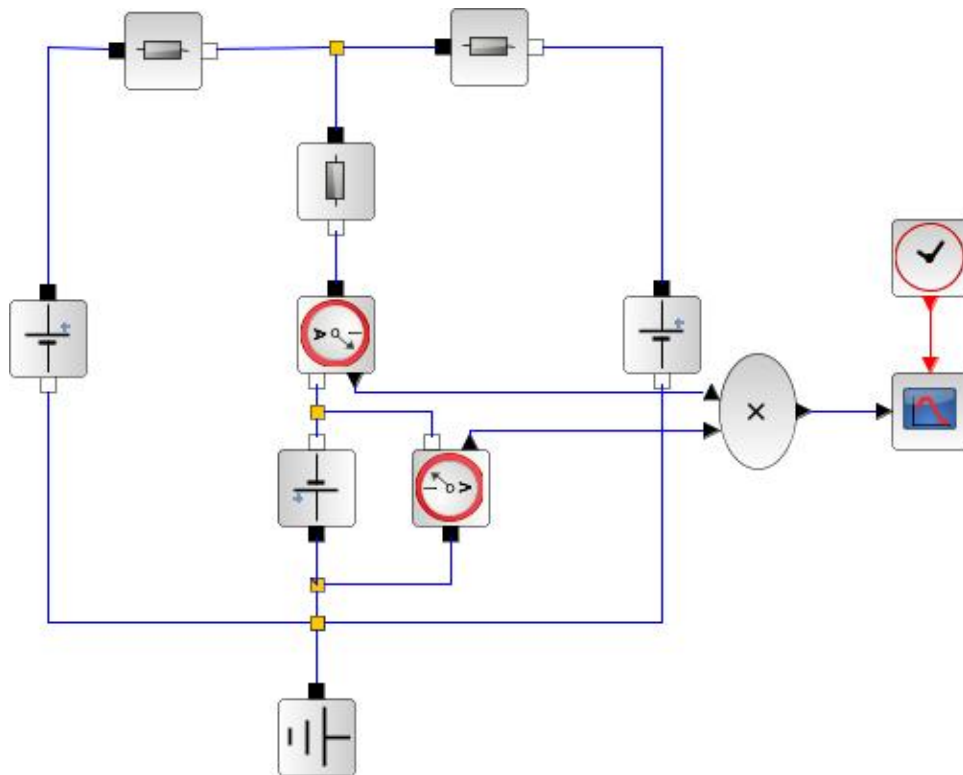


Figure 4.10: Mesh analysis

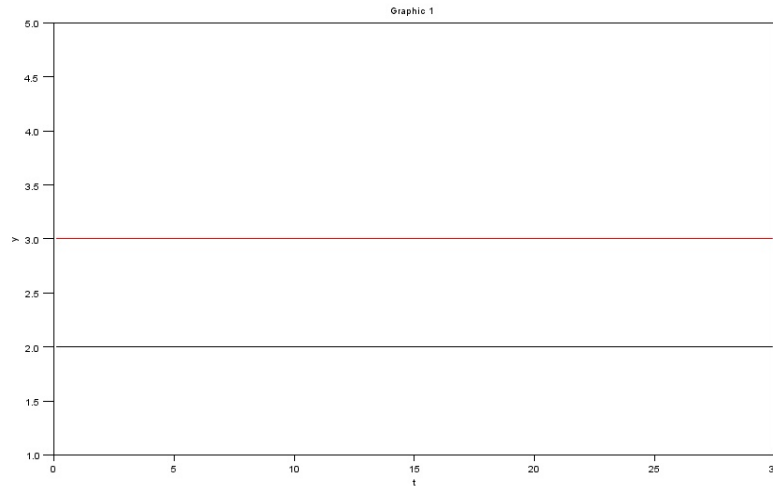


Figure 4.11: Mesh analysis

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

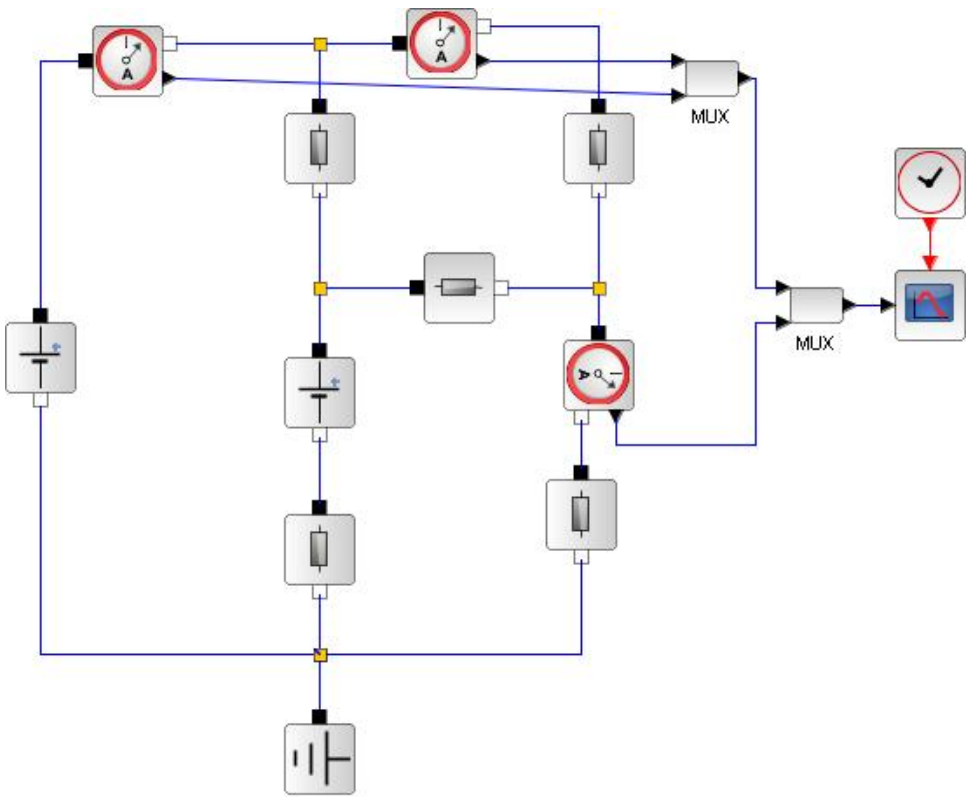


Figure 4.12: Mesh analysis

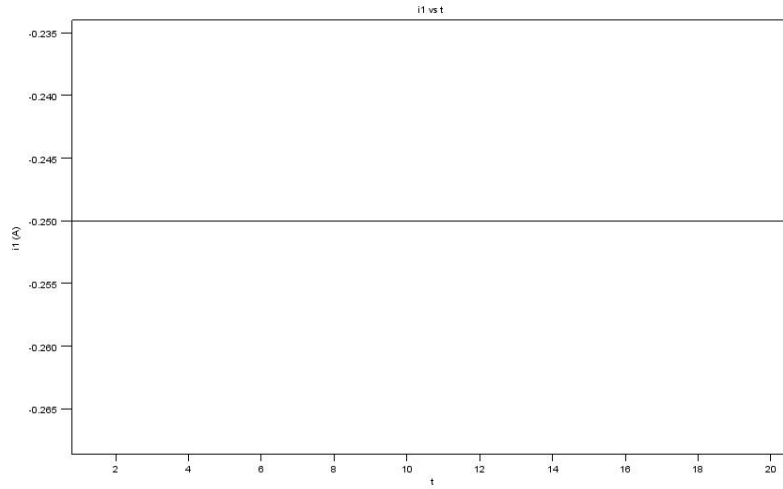


Figure 4.13: Mesh analysis

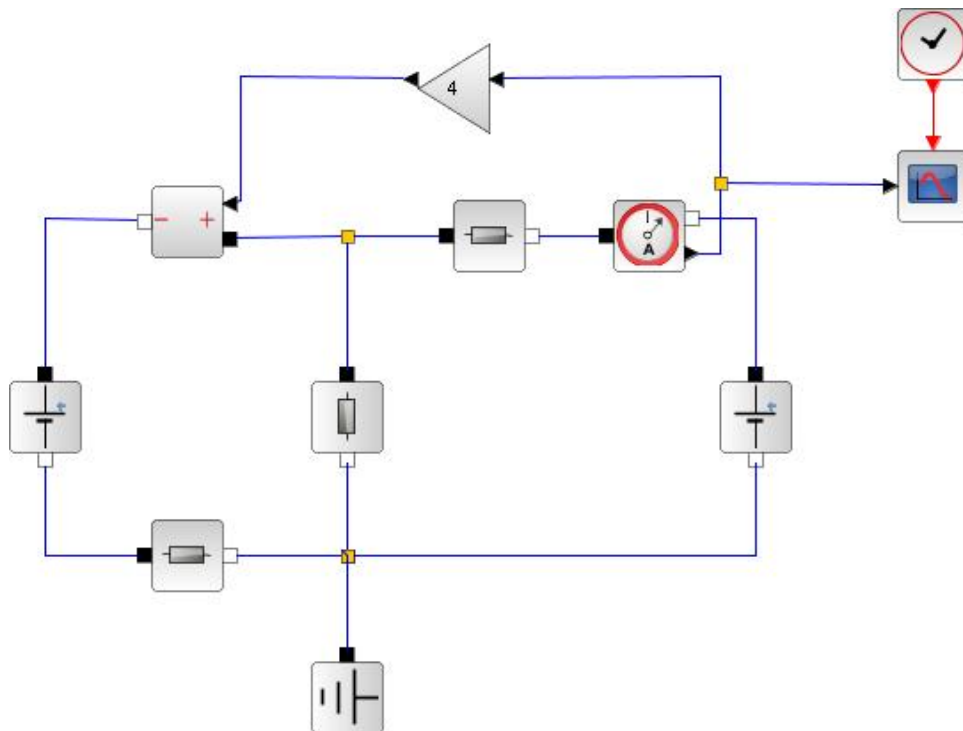


Figure 4.14: Mesh analysis

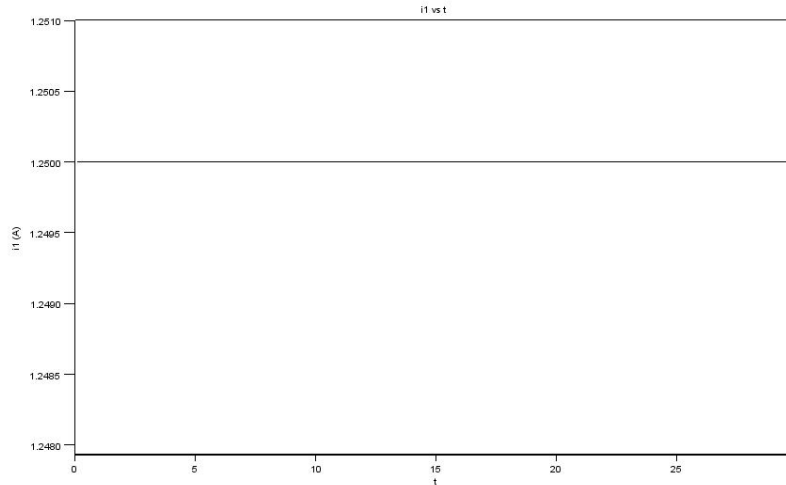


Figure 4.15: Mesh analysis

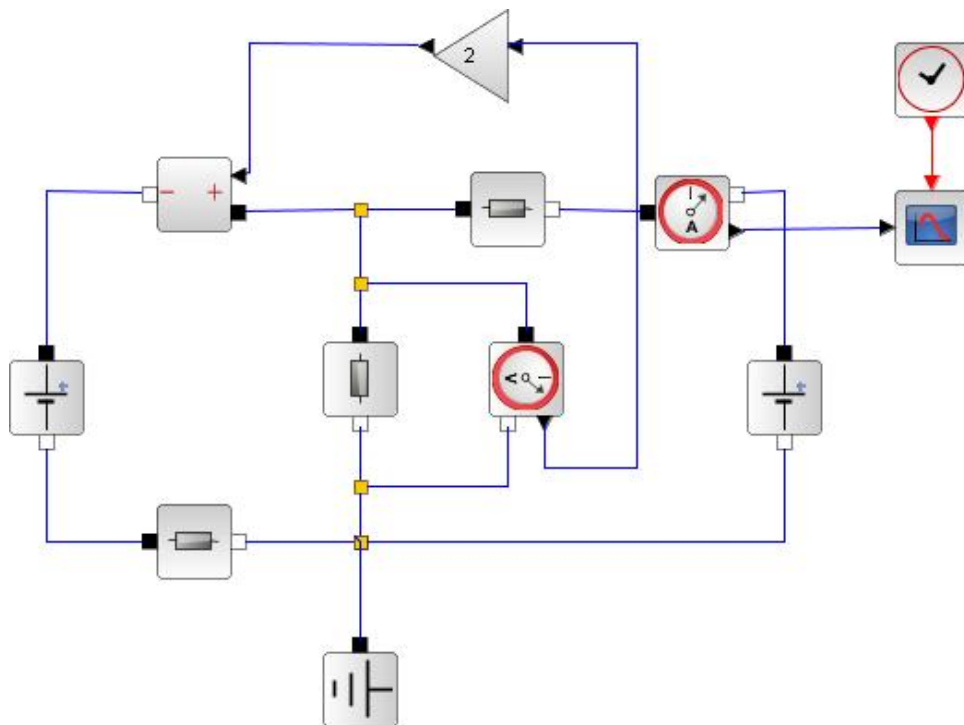


Figure 4.16: Mesh analysis

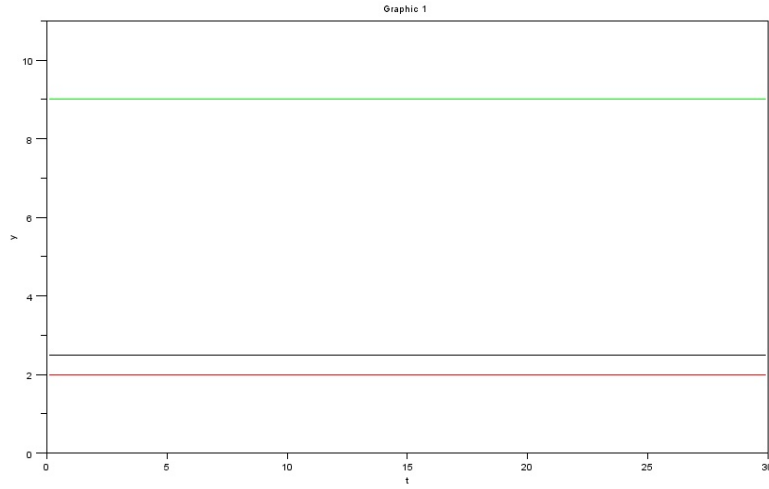


Figure 4.17: The Supermesh

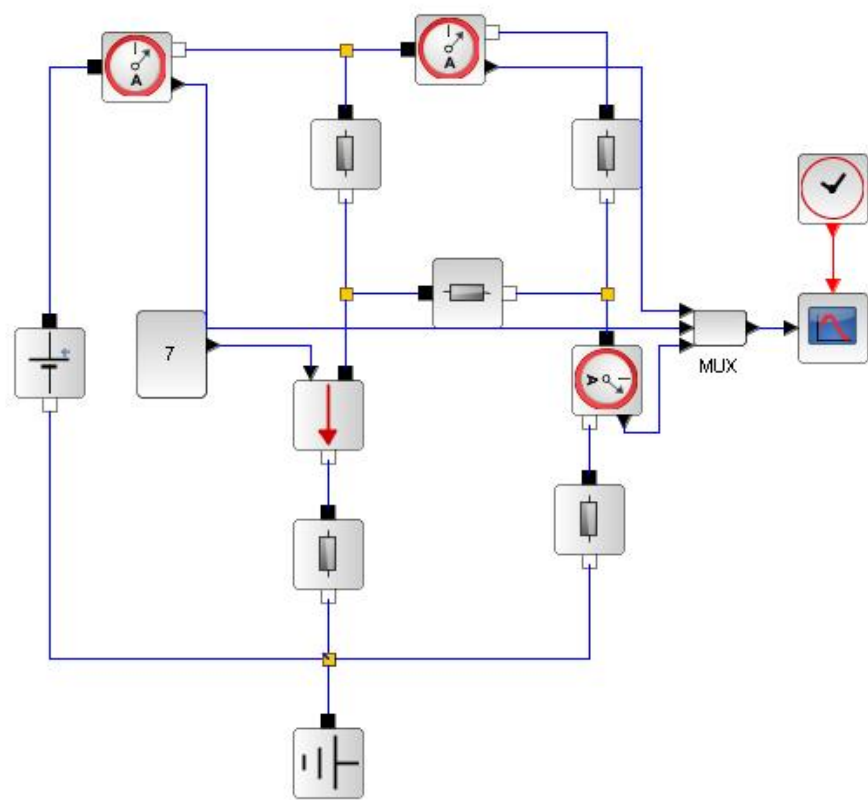


Figure 4.18: The Supermesh

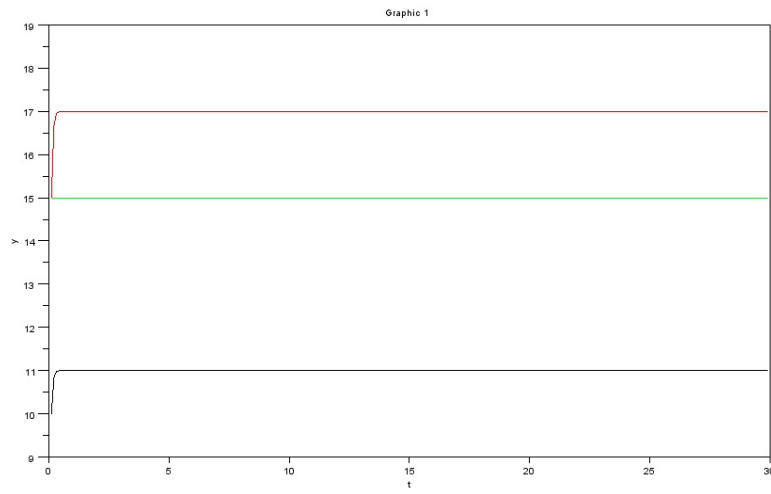


Figure 4.19: The Supermesh

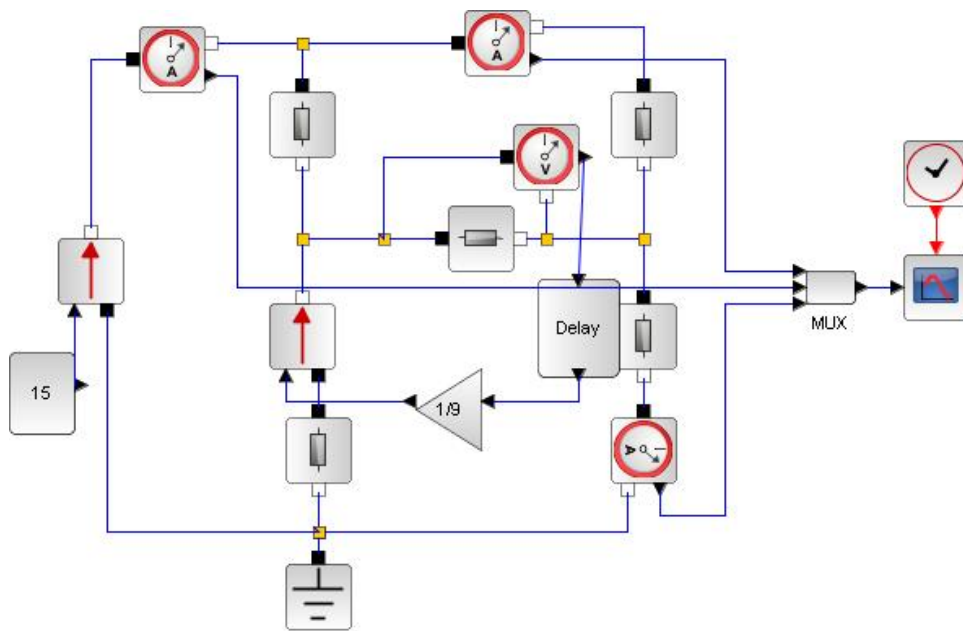


Figure 4.20: The Supermesh

Chapter 6

Network Theorems and useful Circuit Analysis Techniques

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

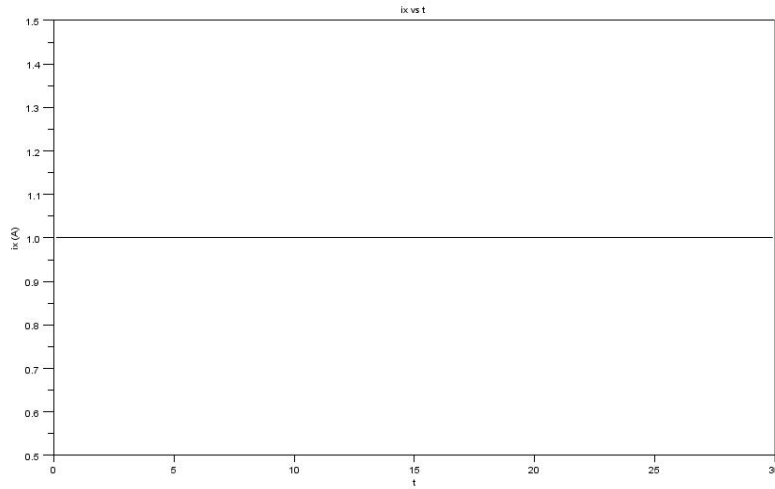


Figure 6.1: The Superposition principle

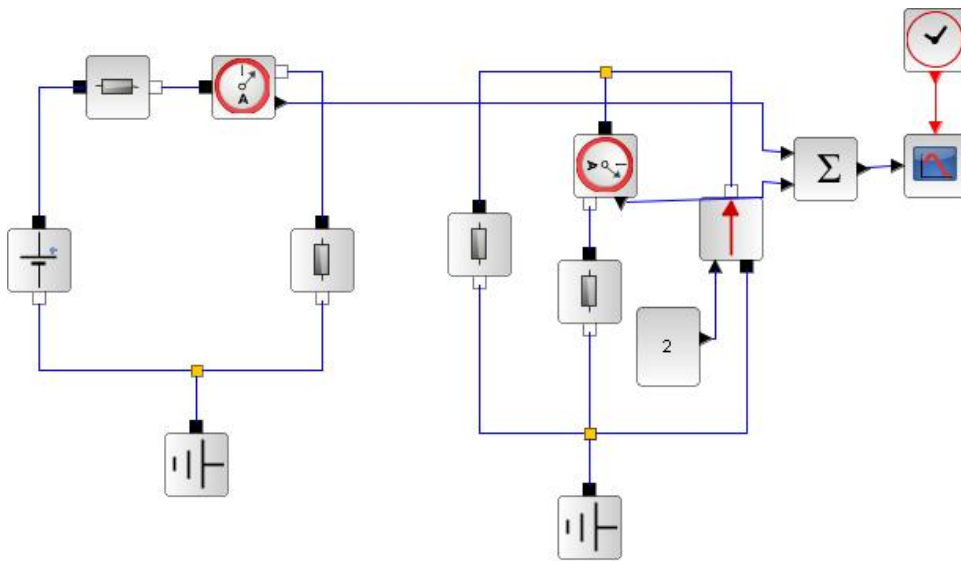


Figure 6.2: The Superposition principle

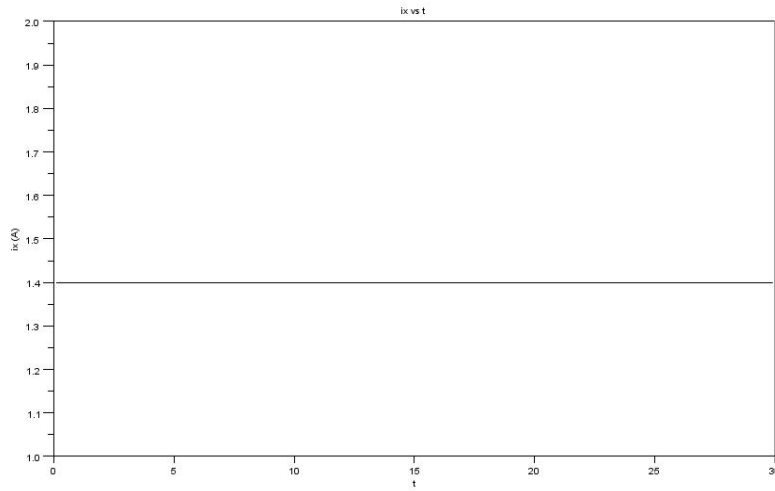


Figure 6.3: The Superposition principle

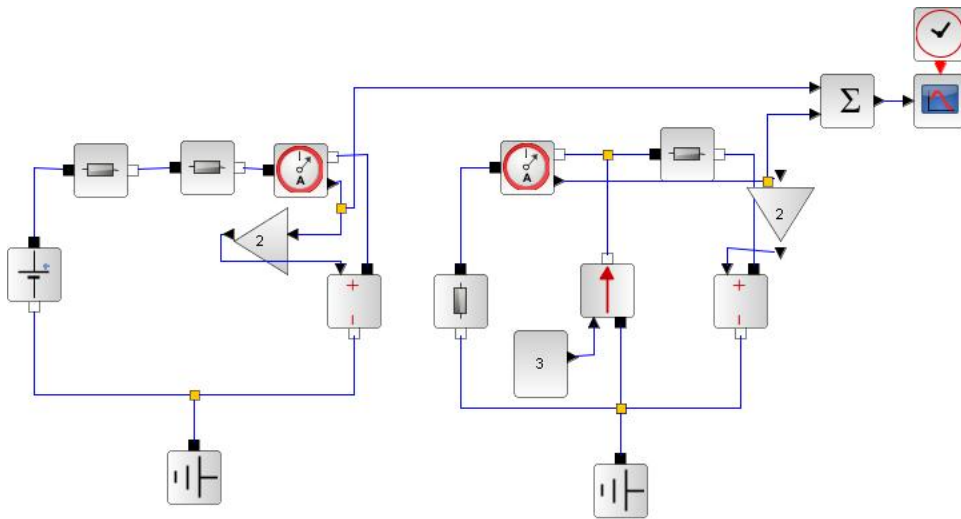


Figure 6.4: The Superposition principle

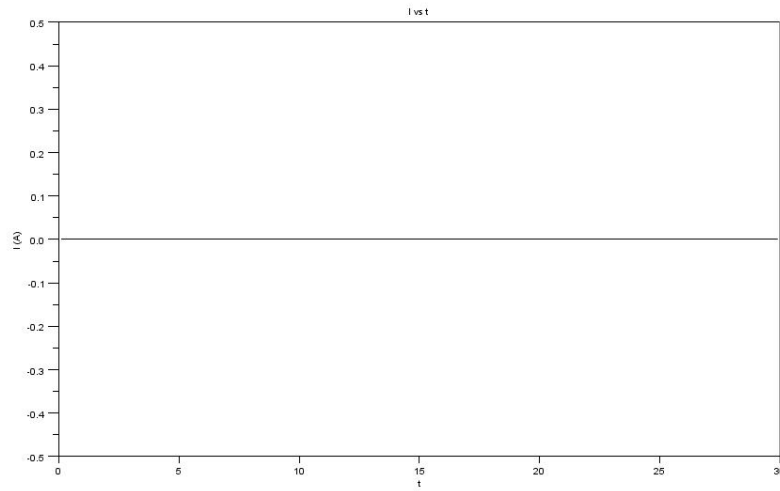


Figure 6.5: The Superposition principle

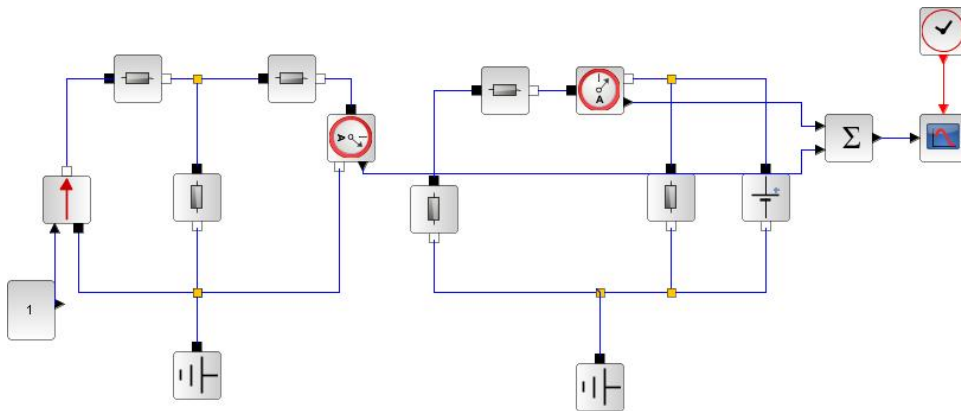


Figure 6.6: The Superposition principle

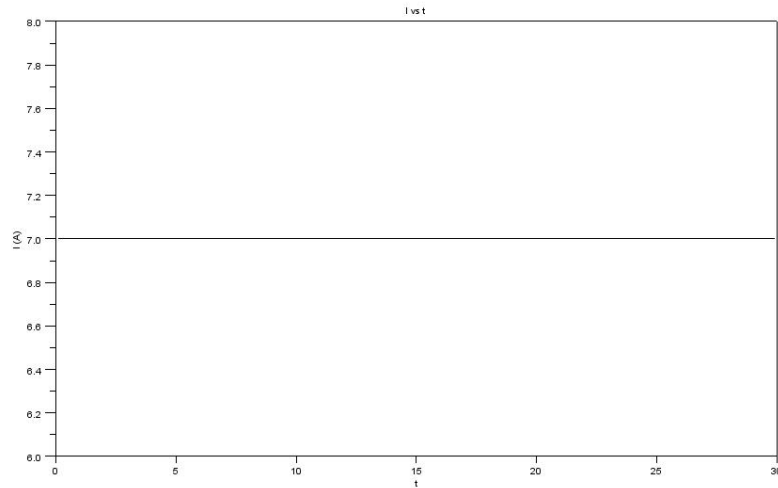


Figure 6.7: The Superposition principle

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

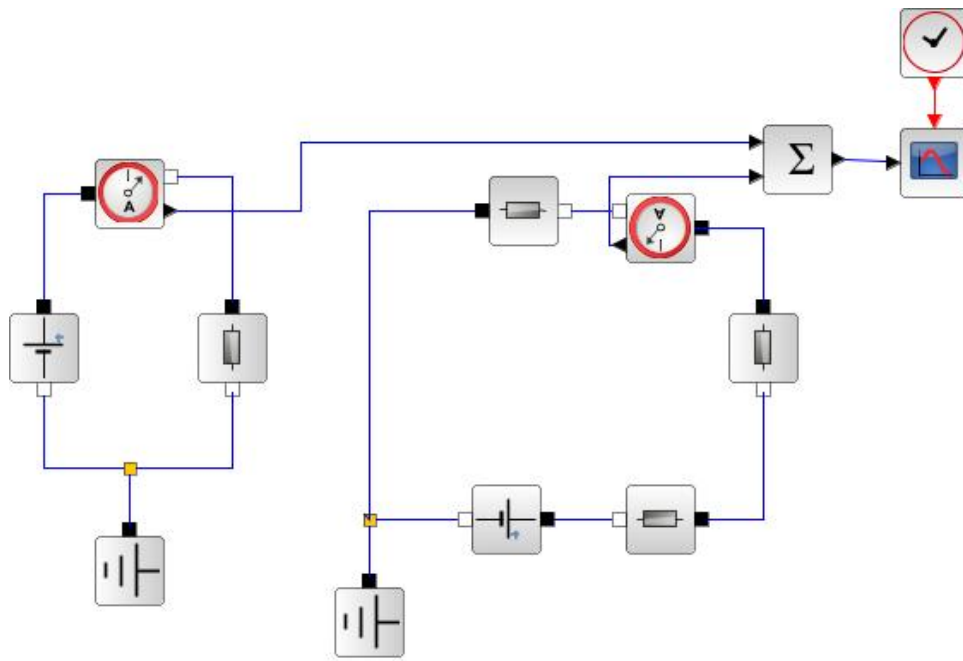


Figure 6.8: The Superposition principle

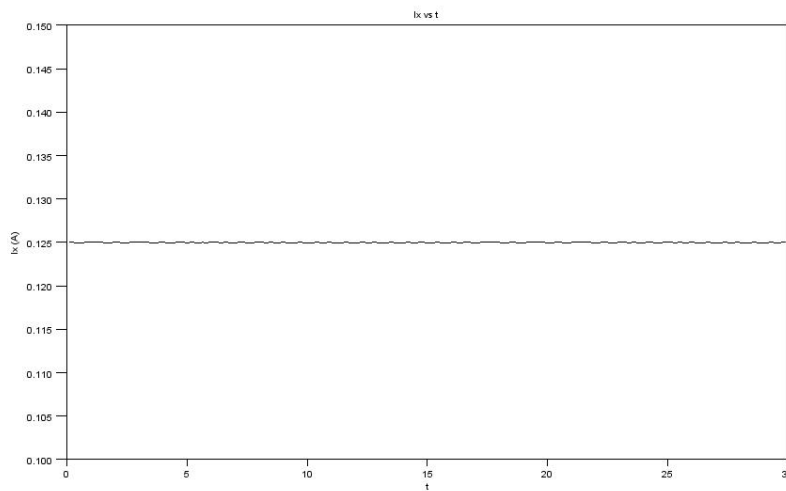


Figure 6.9: The Superposition principle

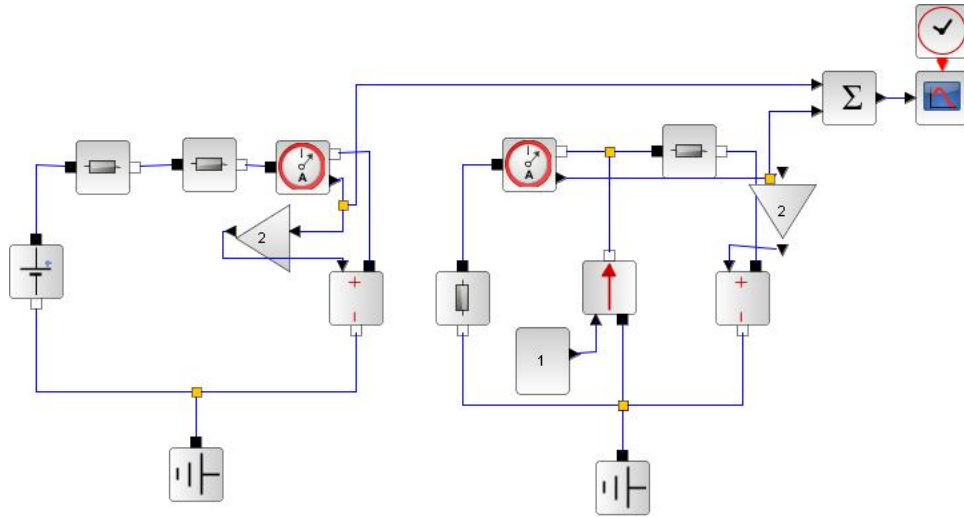


Figure 6.10: The Superposition principle

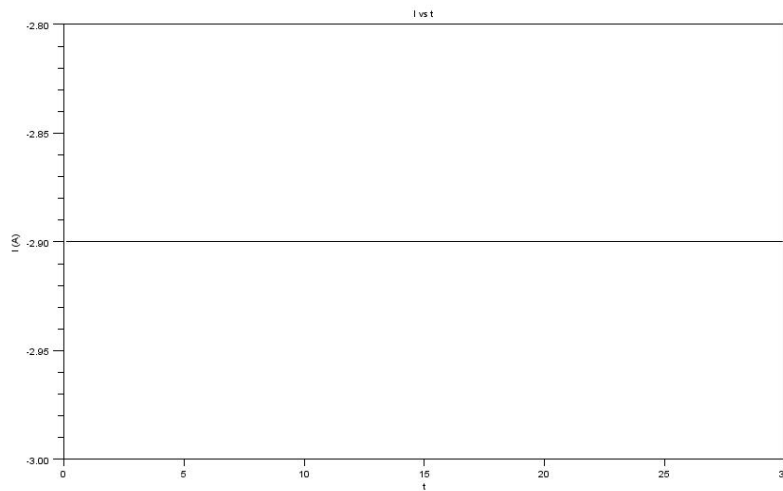


Figure 6.11: The Superposition principle

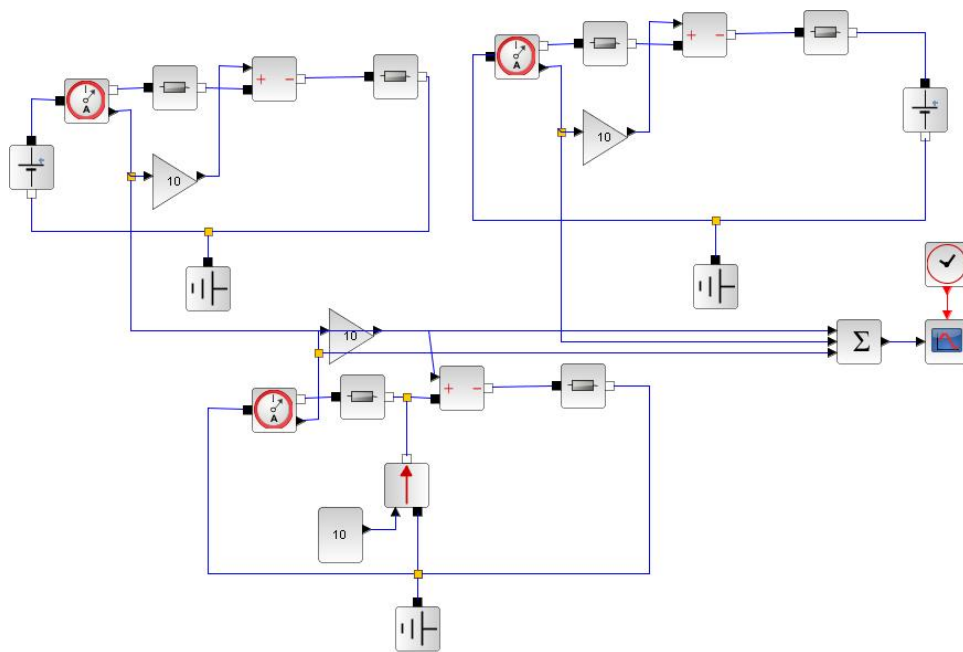


Figure 6.12: The Superposition principle

This code can be downloaded from the website www.scilab.in

Scilab code Exa 6.10 The Superposition principle

```
1  clc
2  //Example 6.10
3  //Calculate the voltage across 20 ohm capacitor
4  //Consider the circuit to be solved by superposition
   principle
5  disp('Consider the current source 2(90 deg)only')
6  //From figure 6.32
7  //Let I1 be the current through -i*4 capacitive
   reactance
8  Imag=2; Iph=90;
9  i=%i
10 x=Imag * cos (( Iph * %pi ) /180) ;
11 y=Imag * sin (( Iph * %pi ) /180) ;
12 I= complex (x,y)
13 I1=(I*(i*15))/(i*5+i*15-i*4)
14 //Let V20 be the voltage across -i*4 capacitive
   reactance
15 V20=(-i*4)*I1
16 printf("V20=%3.2fV \n",V20)
17 disp('Consider the 20 V voltage source only')
18 V=20;
19 //From figure 6.35
20 //let V201 be the voltage across -i*5 capacitive
   reactance
21 V201=-V
22 printf("V201=%d V \n",V201)
23 disp('Consider the current source 1(90 deg)only')
24 I1mag=1; I1ang=90;
25 //From figure 6.37
```

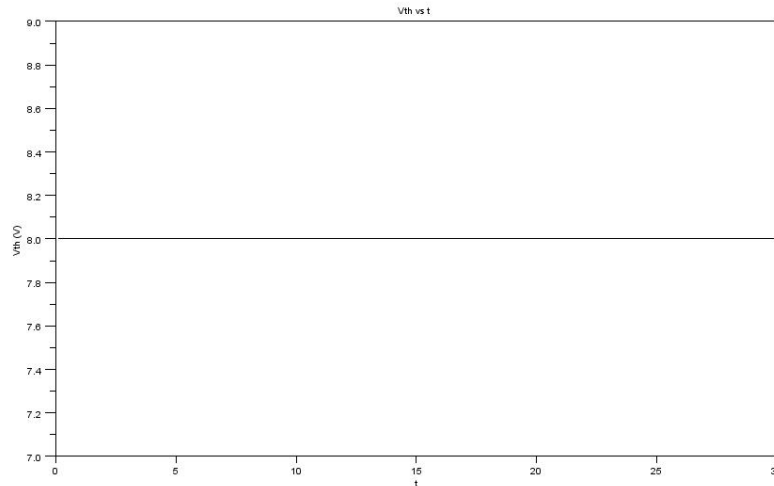


Figure 6.13: Thevenin and Norton Equivalent circuit

```

26 //Let V202 be the voltage across  $-i*5$  capacitive
    reactance
27 V202= $(-i*5)*I1mag*i$ 
28 printf("V202=%3.2fV \n",V202)
29 //Let V20 be the voltage across  $-i*20$  capacitive
    reactance
30 V20=V200+V201+V202
31 printf("\n V20=%3.2fV \n",V20)

```

This code can be downloaded from the website www.scilab.in

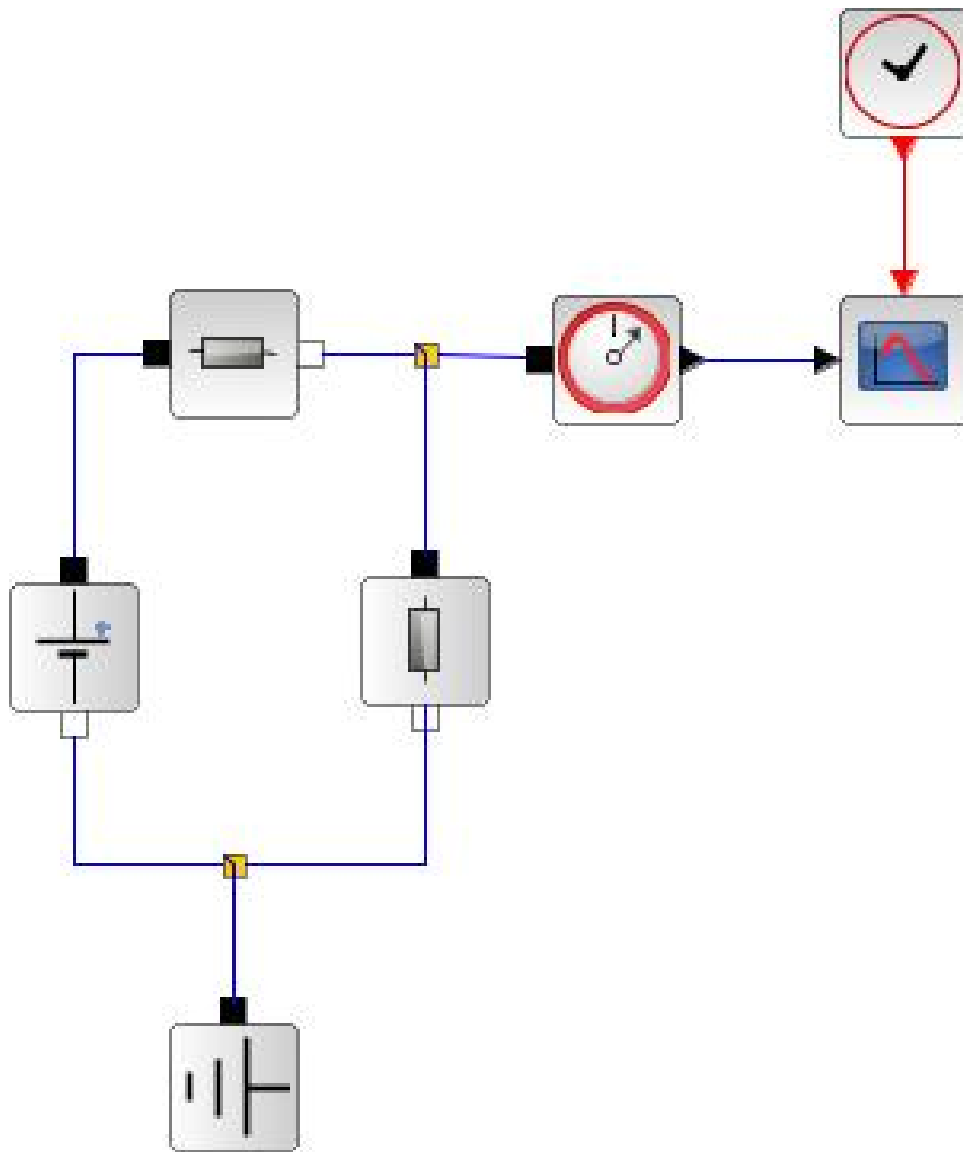


Figure 6.14: Thevenin and Norton Equivalent circuit

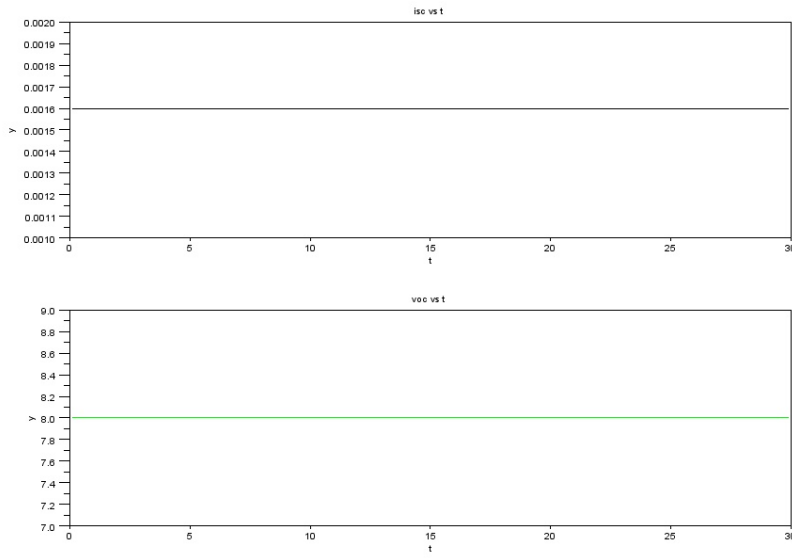


Figure 6.15: Thevenin and Norton Equivalent circuit

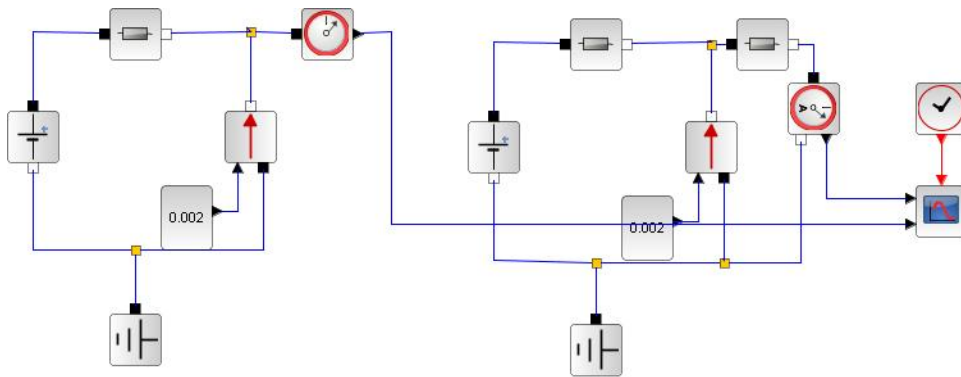


Figure 6.16: Thevenin and Norton Equivalent circuit

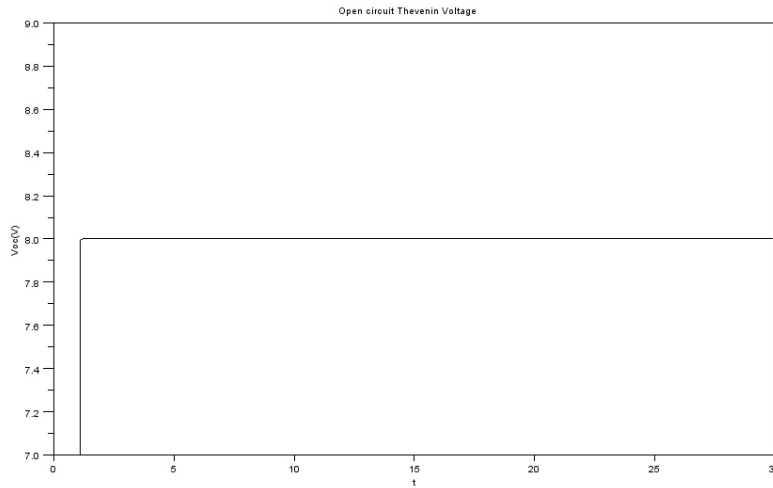


Figure 6.17: Thevenin and Norton Equivalent circuit

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

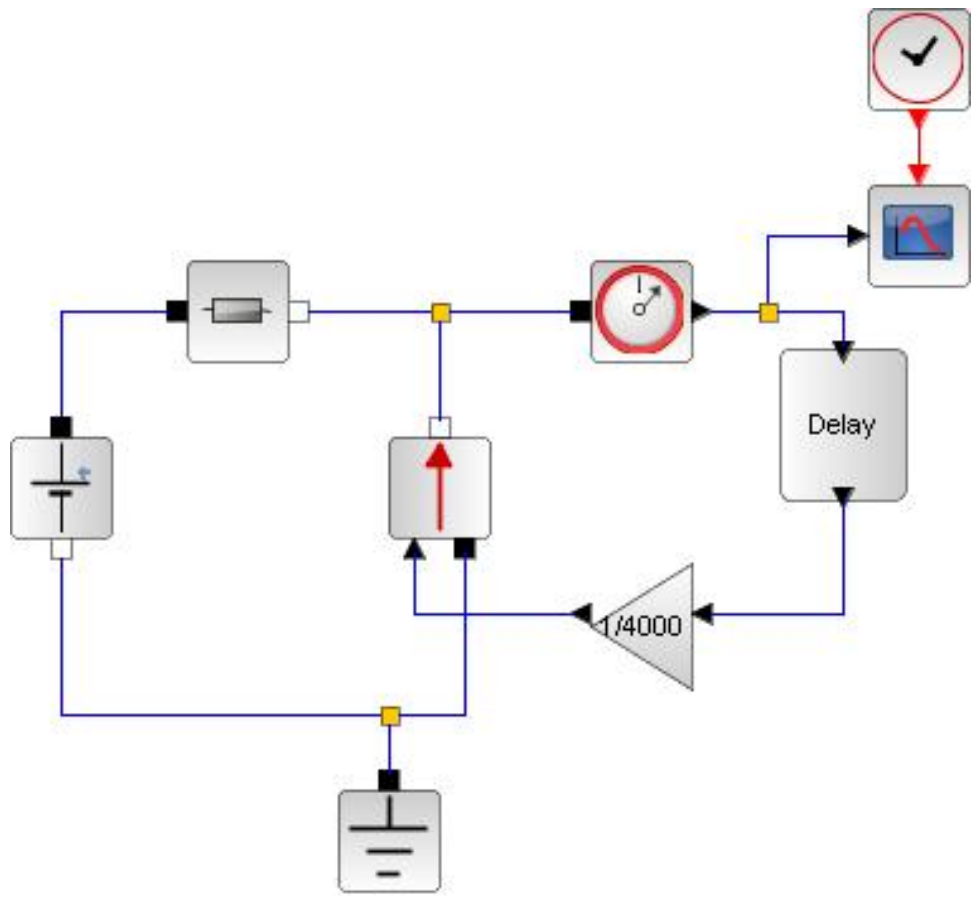


Figure 6.18: Thevenin and Norton Equivalent circuit

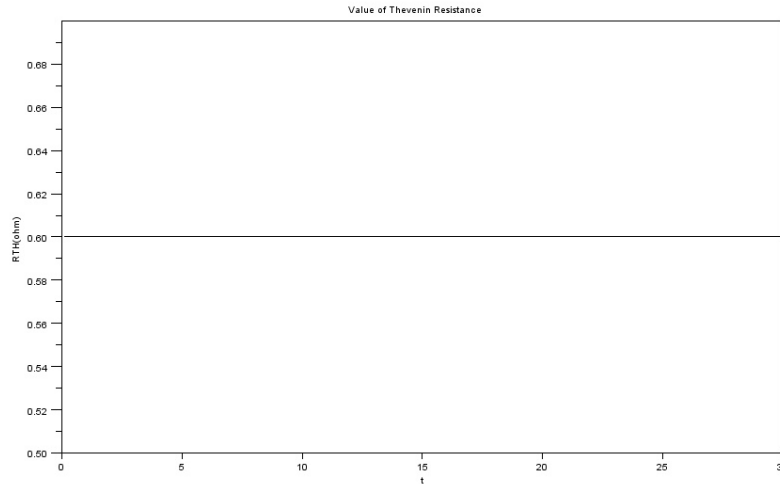


Figure 6.19: Thevenin and Norton Equivalent circuit

This code can be downloaded from the website www.scilab.in

Scilab code Exa 6.17 Reciprocity Theorem

```

1  clc
2  //Example 6.17
3  //Verification of Reciprocity theorem
4  I=20
5  //From figure 6.59
6  disp('The current divides between the two parallel
       impedances ')
7  //Let I2 be the current through i5 ohm
8  I2=(20*%i*(10+%i*5))/(10+%i*5+%i*5-%i*2)

```

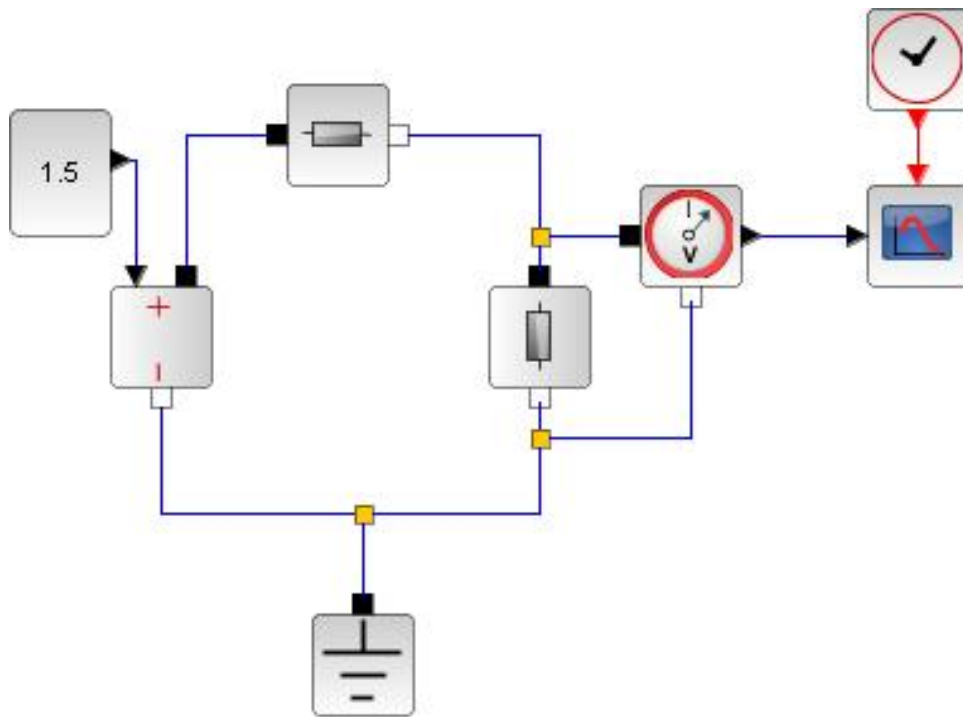


Figure 6.20: Thevenin and Norton Equivalent circuit

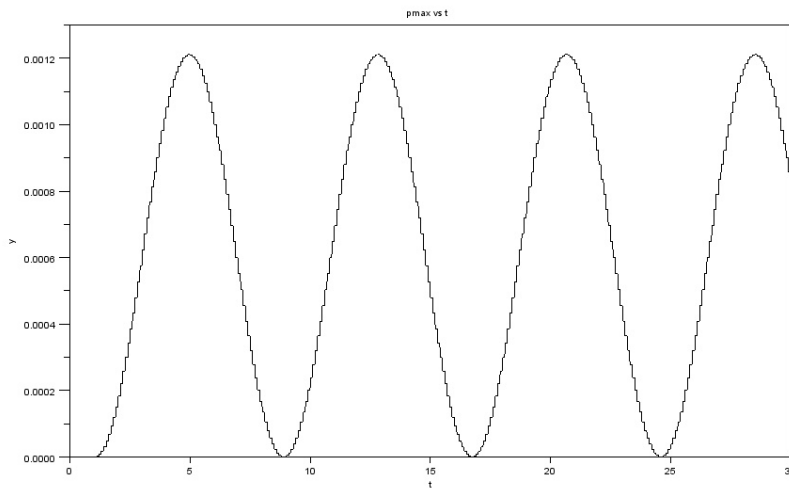


Figure 6.21: Maximum power transfer

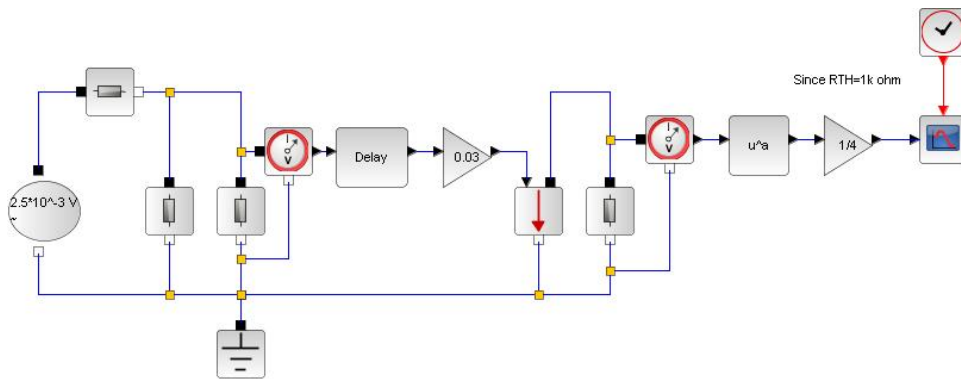


Figure 6.22: Maximum power transfer

```

9 //Let Vx be the voltage across -i2 ohm capacitive
  reactance
10 Vx=I2*(-%i*2)
11 [Vxmag Vxang]=polar(Vx)
12 printf("Vx=%3.2f(%3.2f deg)V \n",Vxmag,(Vxang*180)/
  %pi)
13 //To verify Reciprocity theorem remove the current
  source and place it parallel with -i2 ohm
  capacitive reactance
14 //From figure 6.60
15 //Let I2 be the current flowing through resistor of
  10 ohm
16 I2=(20*%i*(-%i*2))/(10+%i*5+%i*5-%i*2)
17 //let Vx1 be the deired output voltage across 10 ohm
  resistor and i5 inductive reactance
18 Vx1=I2*(10+%i*5)
19 [Vx1mag Vx1ang]=polar(Vx1)
20 printf("Vx1=%3.2f(%3.2f deg)V \n",Vx1mag,(Vx1ang
  *180)/%pi)
21 //Comparing the values of Vx and Vx1
22 disp('Vx=Vx1')
23 disp('Hence Reciprocity theorem is verified')

```

Scilab code Exa 6.18 Reciprocity Theorem

```

1 clc
2 //Example 6.18
3 //Verification of Reciprocity theorem
4 I=10
5 //From figure 6.61
6 disp('The current divides between the two parallel
  impedances')
7 //Let I2 be the current through 4 ohm
8 I2=(10*5)/(4-%i*4+5)
9 //Let Vx be the voltage across -i4 ohm capacitive

```

```

    reactance
10 Vx=I2*(-%i*4)
11 [Vxmag Vxang]=polar(Vx)
12 printf("Vx=%3.2 f(%3.2 f deg)V \n",Vxmag,(Vxang*180)/
    %pi)
13 //To verify Reciprocity theorem remove the current
    source and place it parallel with -i4 ohm
    capacitive reactance
14 //From figure 6.62
15 //Let I1 be the current flowing through resistor of
    5 ohm
16 I1=(10*(-%i*4))/(5+4-%i*4)
17 //let Vx1 be the deired output voltage across 5 ohm
    resistor
18 Vx1=I1*5
19 [Vx1mag Vx1ang]=polar(Vx1)
20 printf("Vx1=%3.2 f(%3.2 f deg)V \n",Vx1mag,(Vx1ang
    *180)/%pi)
21 //Comparing the values of Vx and Vx1
22 disp('Vx=Vx1')
23 disp('Hence Reciprocity theorem is verified')

```

Scilab code Exa 6.19 Millman Theorem

```

1 clc
2 //Example 6.19
3 //Calculate total current through load
4 //On applying source transformation
5 //From figure 6.65
6 i=%i
7 V1=10; V2mag=5; V2ph=90; V3mag=14.4; V3ph=225;
8 x=V2mag * cos (( V2ph * %pi ) /180) ;
9 y=V2mag * sin (( V2ph * %pi ) /180) ;
10 V2= complex (x,y)
11 a=V3mag * cos (( V3ph * %pi ) /180) ;

```

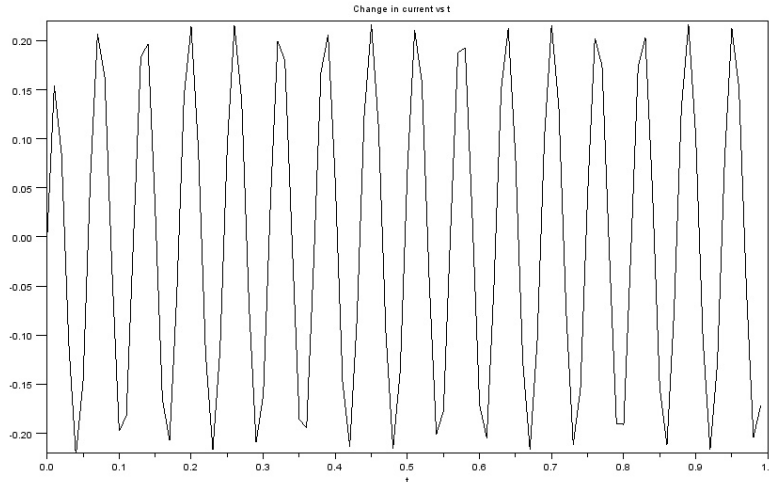


Figure 6.23: Compensation Theorem

```

12 b=V3mag * sin (( V3ph * %pi ) /180) ;
13 V3= complex (a,b)
14 G1=1/2;G2=1/(2+i*3);G3=1/(2-i*2);
15 //By applying Millman Theorem
16 disp('V=((V1*G1)+(V2*G2)+(V3*G3))/(G1+G2+G3)')
17 V=((V1*G1)+(V2*G2)+(V3*G3))/(G1+G2+G3)
18 [Vmag Vang]=polar(V)
19 R=1/(G1+G2+G3)
20 printf("V=%3.2 f (%3.2 f deg)V",Vmag,(Vang*180)/%pi)
21 disp(R,'R=')
22 //Consider the resultant circuit from figure 6.66
23 disp('Let the total current through 3+i4 be I')
24 //Applying KVL to the circuit
25 I=V/(3+i*4+R)
26 [Imag Iang]=polar(I)
27 printf("I=%3.2 f (%3.2 f deg)V",Imag,(Iang*180)/%pi)

```

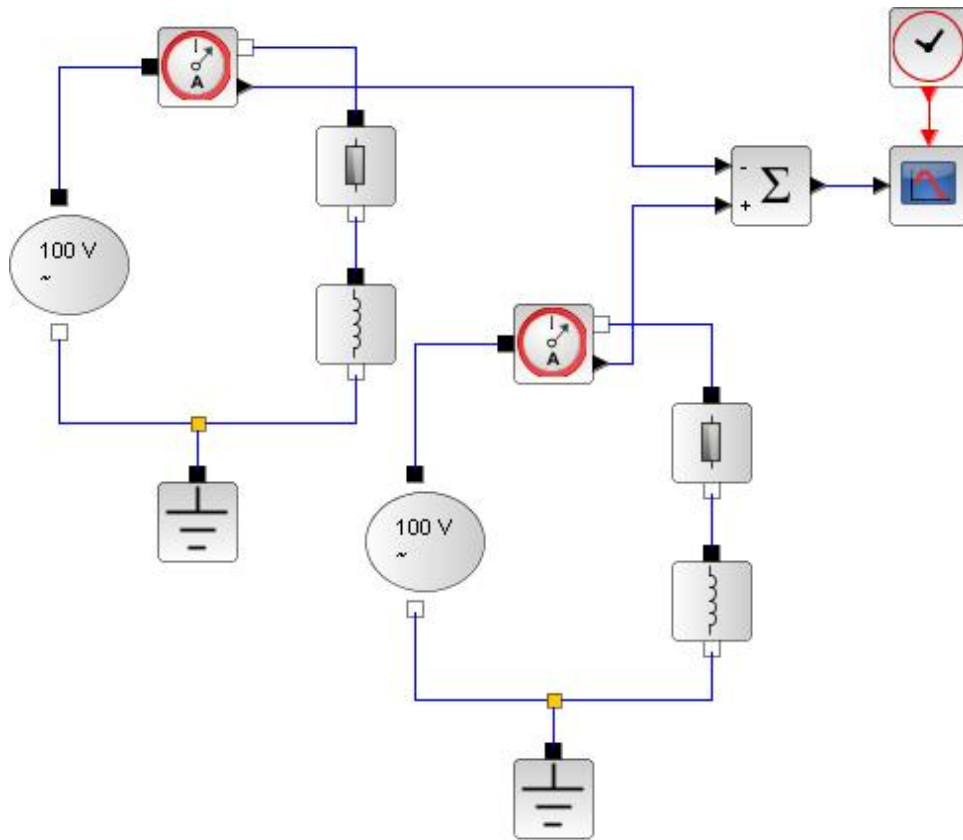


Figure 6.24: Compensation Theorem

This code can be downloaded from the website www.scilab.in

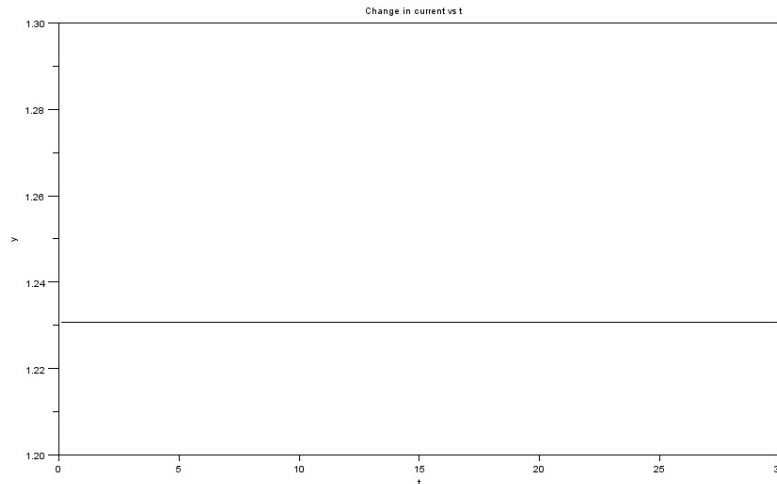


Figure 6.25: Compensation Theorem

This code can be downloaded from the website www.scilab.in

Scilab code Exa 6.22 Tellegen Theorem

```

1  clc
2  //Example 6.22
3  //Writing KVL for the circuit
4  disp('10*i=30')
5  //On solving
6  i=3;R=10;V1=25;V2=5;
7  printf("Power absorbed by 10 ohm resistor is %d W \n",i^2*R)
8  printf("Power delivered by 25 V source is %d W \n",V1*i)
9  printf("Power delivered by 5 V source is %d W \n",V2

```

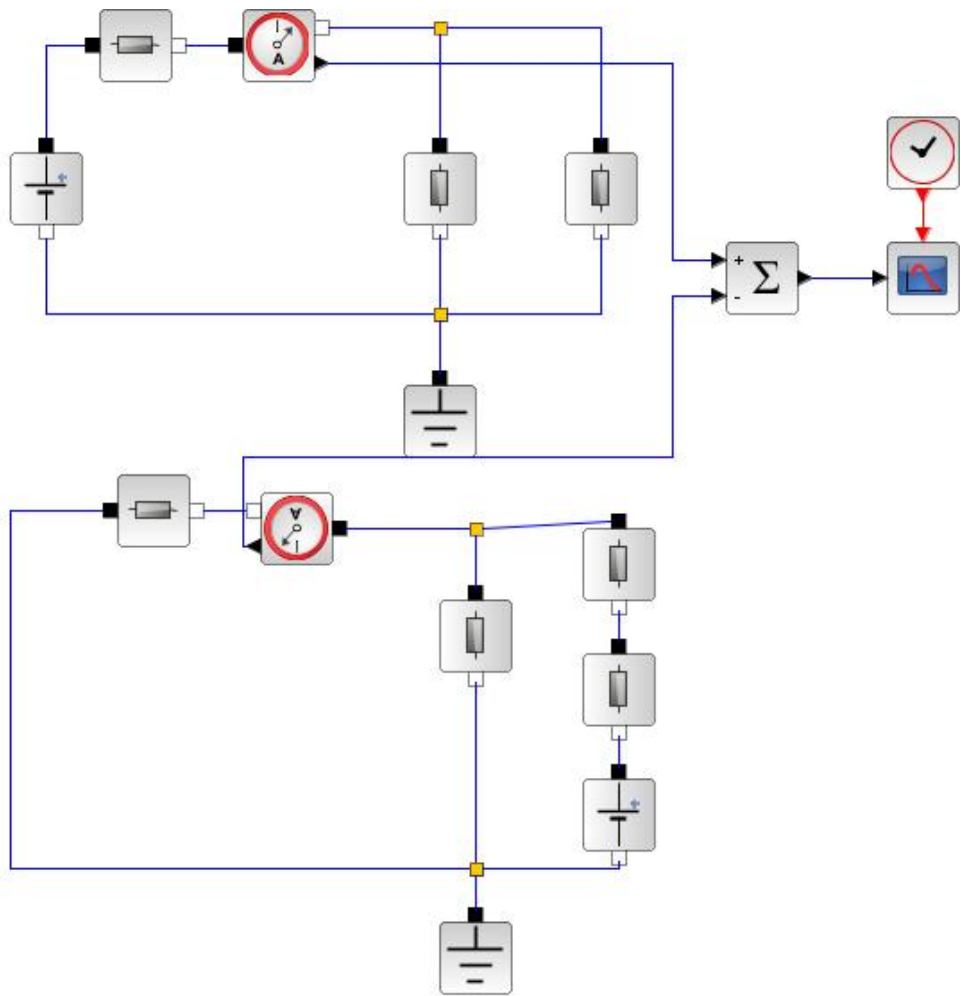



Figure 6.26: Compensation Theorem

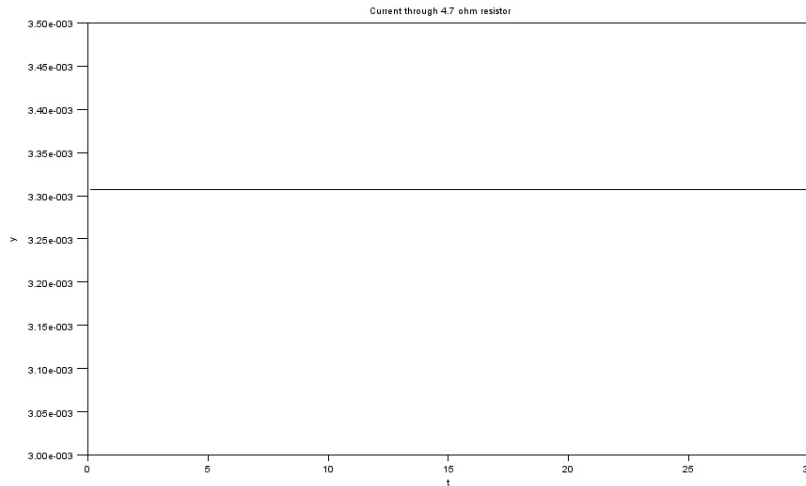


Figure 6.27: Source Transformations

```

    *i)
10 //Let P be the total power
11 P=i^2*R-(V1*i+V2*i)
12 if P==0 then
13     disp('Tellegen theorem is valid')
14 else
15     disp('Tellegen theorem is not valid')
16 end

```

This code can be downloaded from the website www.scilab.in

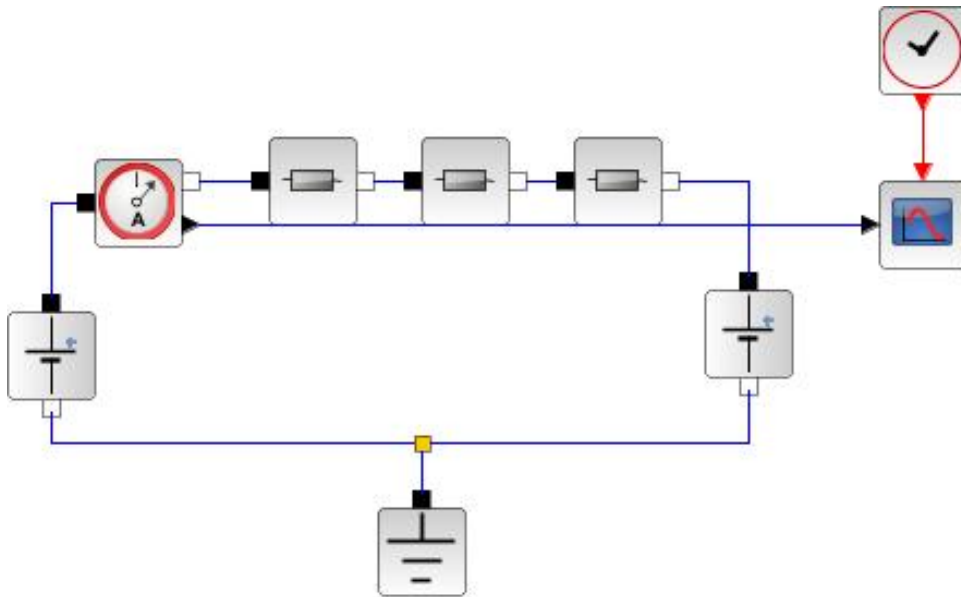


Figure 6.28: Source Transformations

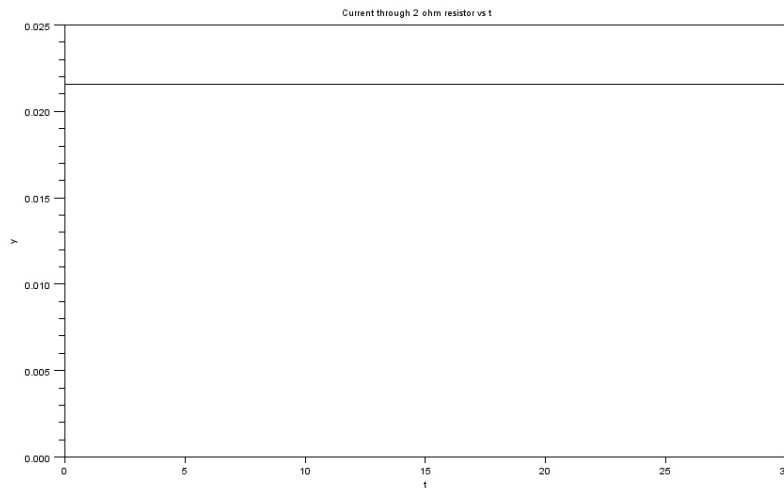


Figure 6.29: Source Transformations

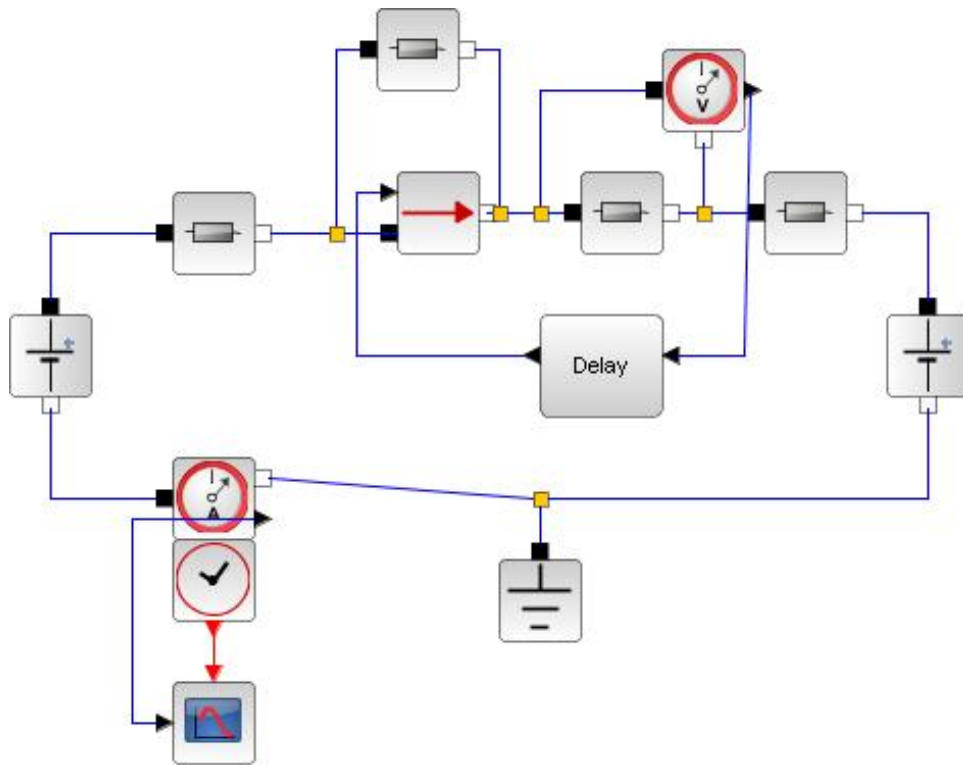


Figure 6.30: Source Transformations

This code can be downloaded from the website www.scilab.in

Chapter 7

Capacitors and Inductors

Scilab code Exa 7.1 The Capacitor

```
1 clc
2 syms s t
3 //part(a)
4 i=diff(5*s^0,s)
5 disp(i,'i=')
6 //prt(b)
7 i1=diff(4*sin(3*t),t)
8 t=-2:.1:5
9 plot(t,12*cos(3*t))
10 xtitle('i vs t','t(s)','i(A)')
```

Scilab code Exa 7.2 The Capacitor

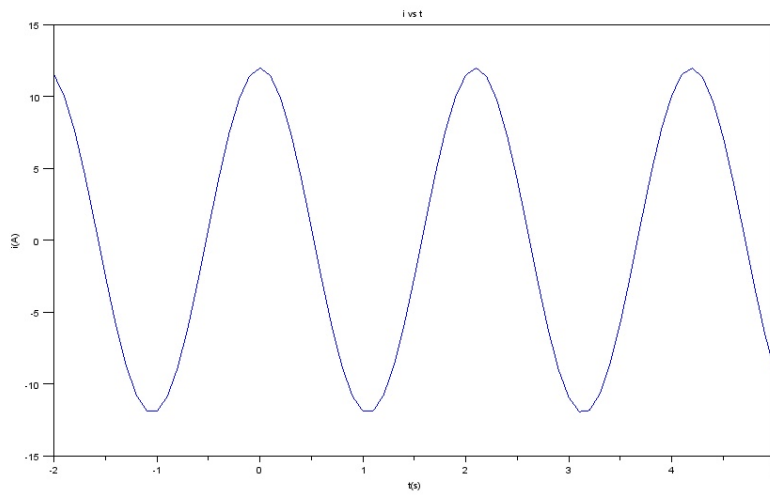


Figure 7.1: The Capacitor

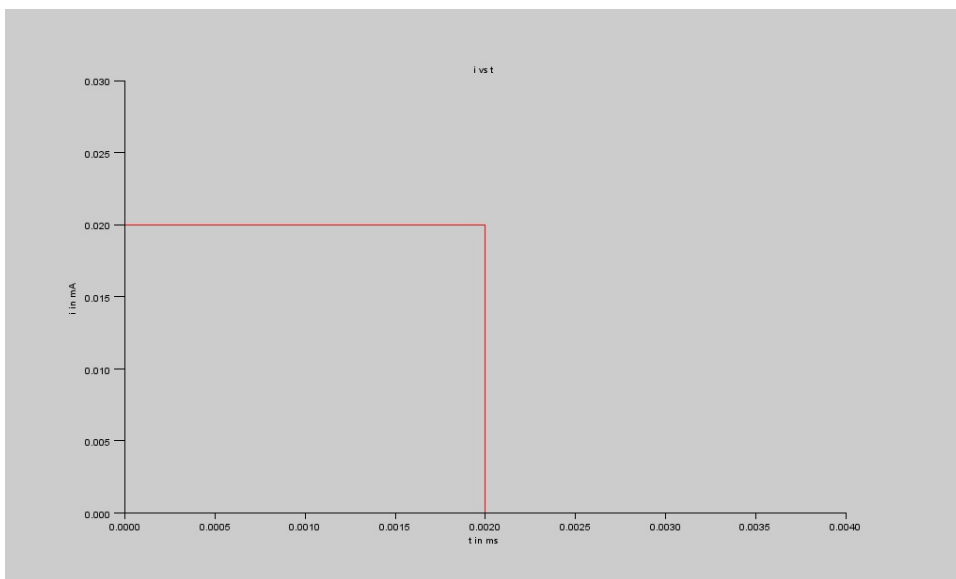


Figure 7.2: The Capacitor

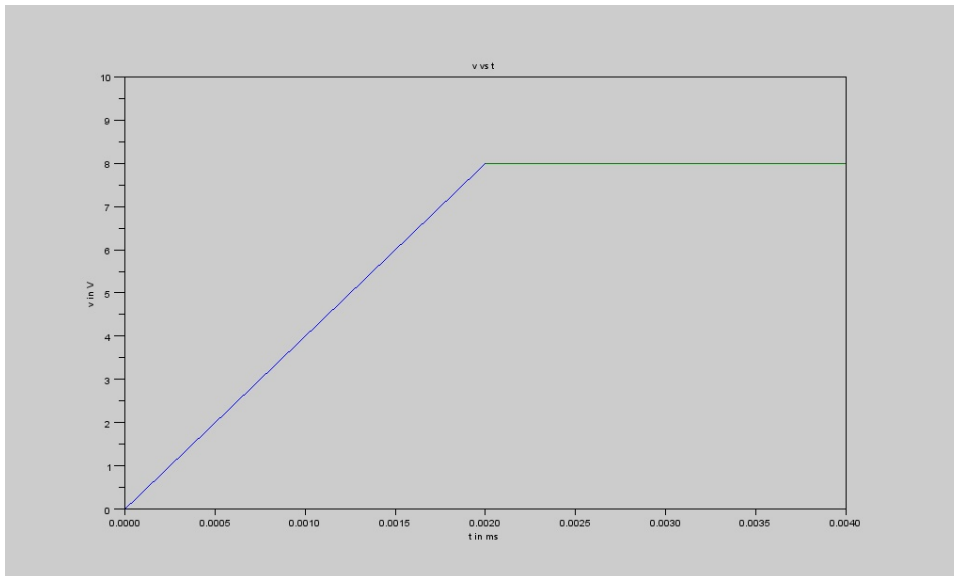


Figure 7.3: The Capacitor

```

1  clc
2  t = 0:0.000001:0.002;
3  deff('y=u(t)', 'y=1*(t>=0)');
4  y = 0.02*(u(t) - u(t-0.002));
5  figure
6  a=gca()
7  subplot(111)
8  plot2d(t,y,5,rect=[0 0 0.004 0.03])
9  xtitle('i vs t', 't in ms', 'i in mA')
10
11 syms s
12 //For t<=0 ms
13 v=0
14 //For the region in the rectangular pulse i.e 0<t<=2
    ms
15 v=integ(s^0,s)*4000
16 //For t>2 ms
17 v=8
18 s=0:0.000001:0.002

```

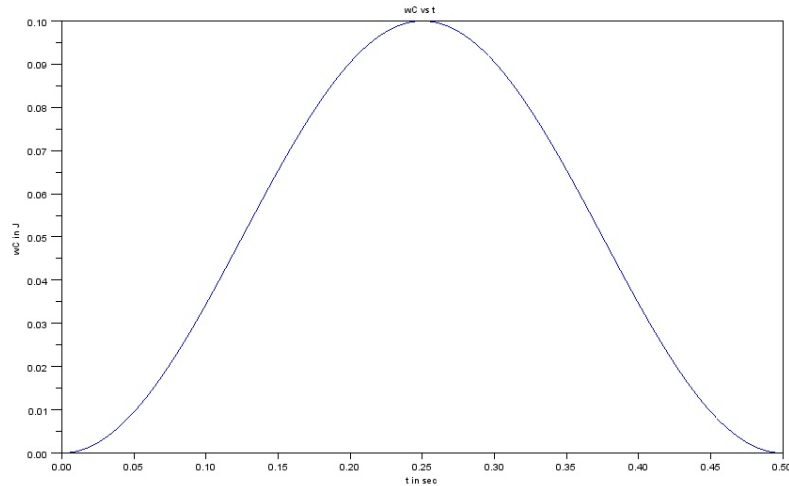



Figure 7.4: The Capacitor

```

19
20 figure
21 a=gca()
22 subplot(111)
23 plot(s,(4000*s),s+0.002,8)
24 xtitle('v vs t','t in ms','v in V')

```

Scilab code Exa 7.3 The Capacitor

```

1 clc
2 //Example 7.3
3 //Let wc be the energy stored in capacitor
4 C=20*10^-6; R=10^6;
5 t=0:0.001:0.5
6 v=100*sin(2*%pi*t)

```

```

7  wC=0.5*C*v^2
8  plot(t,wC)
9  xtitle('wC vs t','t in sec','wC in J')
10 //Let iR be the current in the resistor
11 iR=v/R
12 //Let pR be the power dissipated in the resistor
13 pR=iR^2*R
14 //If wR is the energy dissipated in the resistor
15 syms s
16 wR=integ(100*(sin(2*pi*s))^2,s,0,0.5)
17 disp(wR,'wR=')

```

Scilab code Exa 7.7 The Inductor

```

1  clc
2  //Example 7.7
3  printf("Given")
4  disp('i=12*sin(%pi*t/6),R=0.1 ohm,L=3H')
5  t=0:.1:6
6  i=12*sin(%pi*t/6),R=0.1;L=3;
7  //Let wL be the energy stored in the inductor
8  wL=0.5*L*i^2
9  plot(t,wL)
10 //From the above graph
11 wLmax=216;tmax=3;
12 printf("Maximum value at %d J at %d sec",wLmax,tmax)
13 //Let pR be the power dissipated in the resistor
14 pR=i^2*R
15 //Energy converted to heat in 6 sec interval in the
    resistor is
16 syms s
17 wR=integ(14.4*(sin(%pi/6*s))^2,s,0,6)
18 disp(wR,'wR')

```

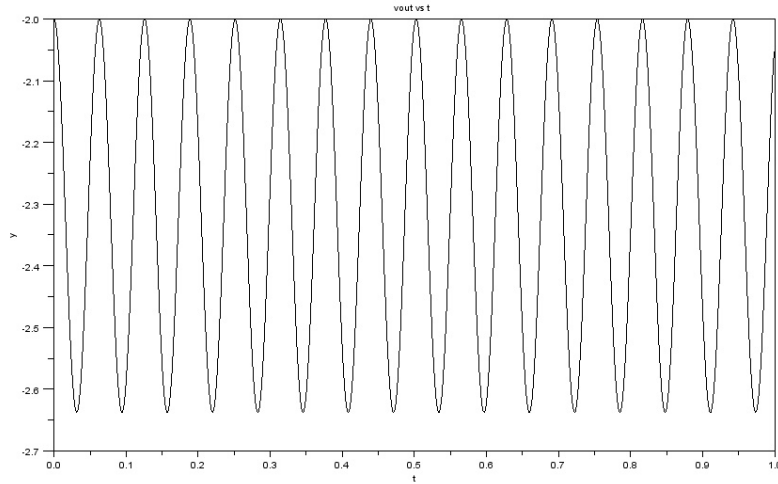


Figure 7.5: Modeling Capacitors and Inductors

This code can be downloaded from the website www.scilab.in

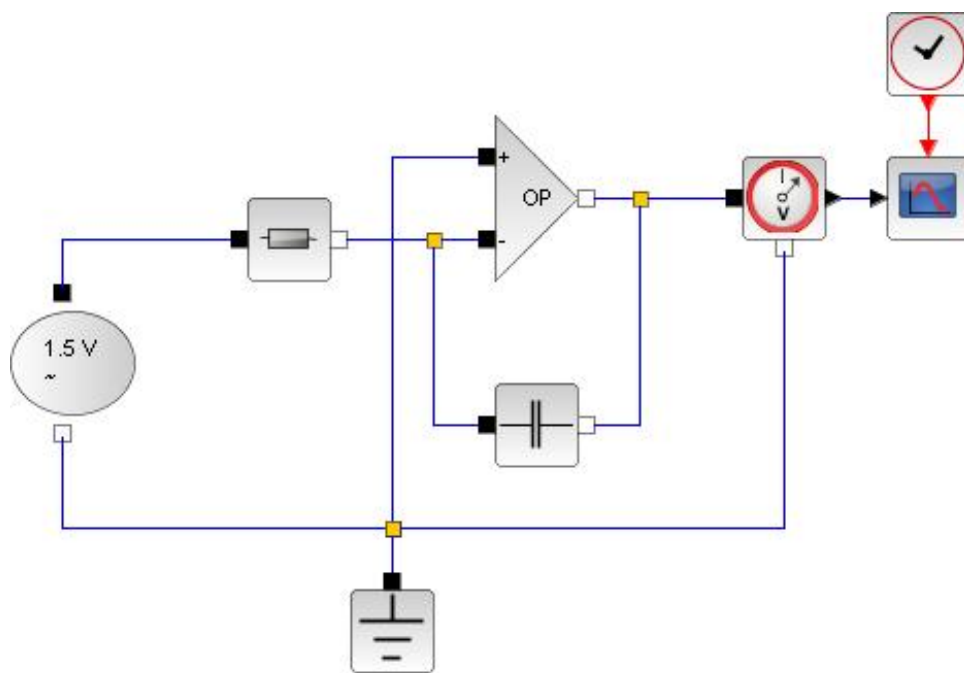


Figure 7.6: Modeling Capacitors and Inductors

Chapter 8

Basic RL and RC circuits

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

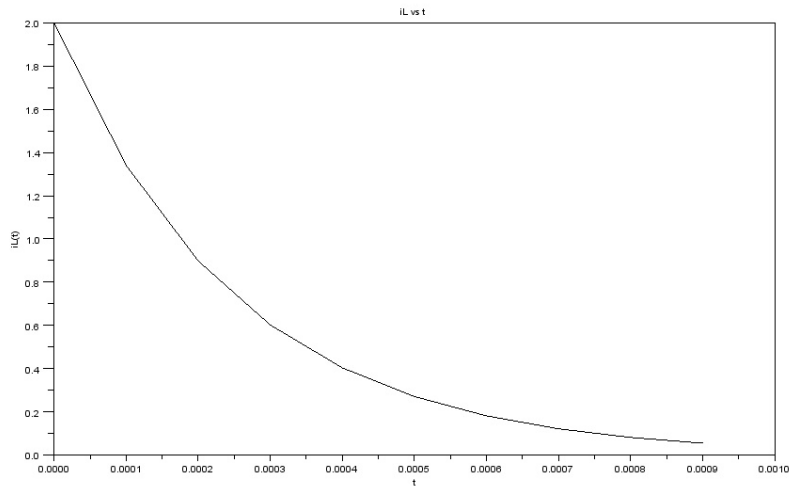


Figure 8.1: The Source free RL Circuit

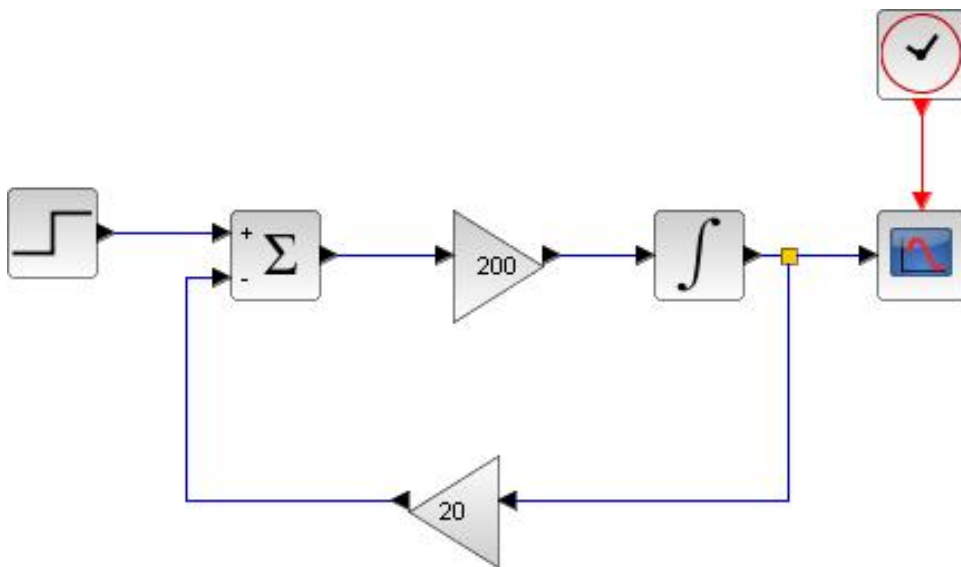


Figure 8.2: The Source free RL Circuit

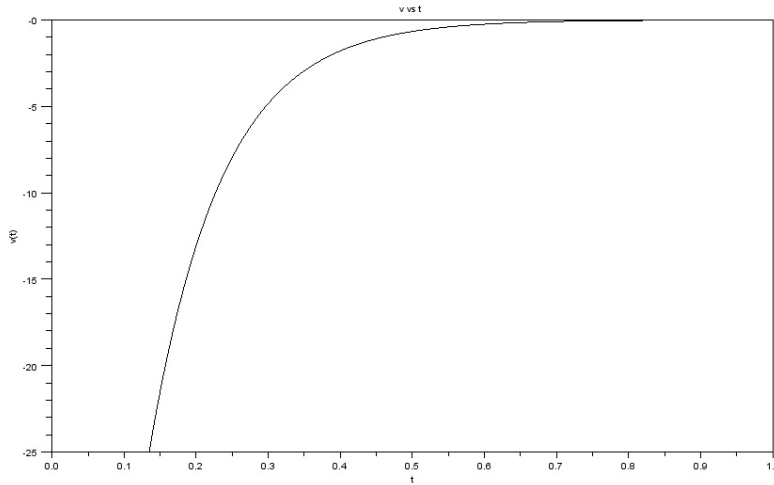


Figure 8.3: The Source free RL Circuit

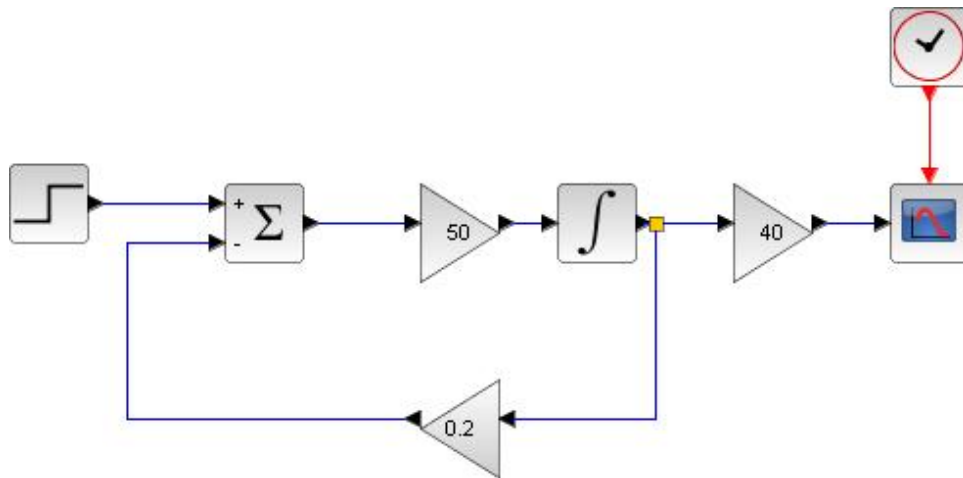


Figure 8.4: The Source free RL Circuit

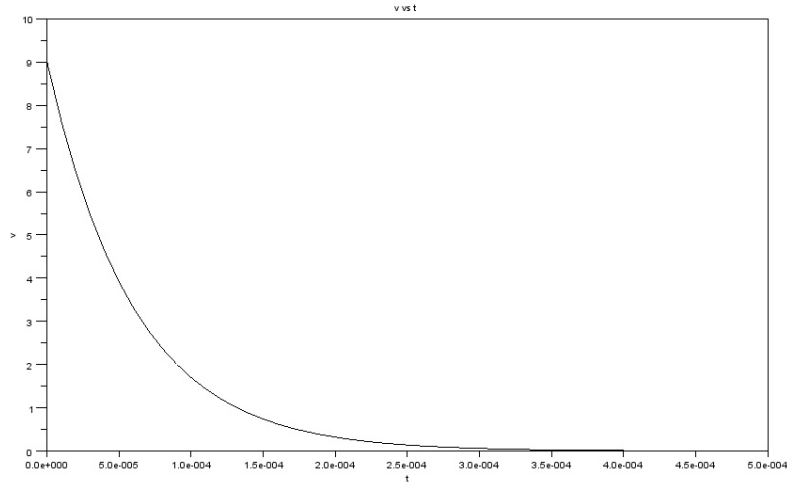


Figure 8.5: The Source free RC Circuit

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

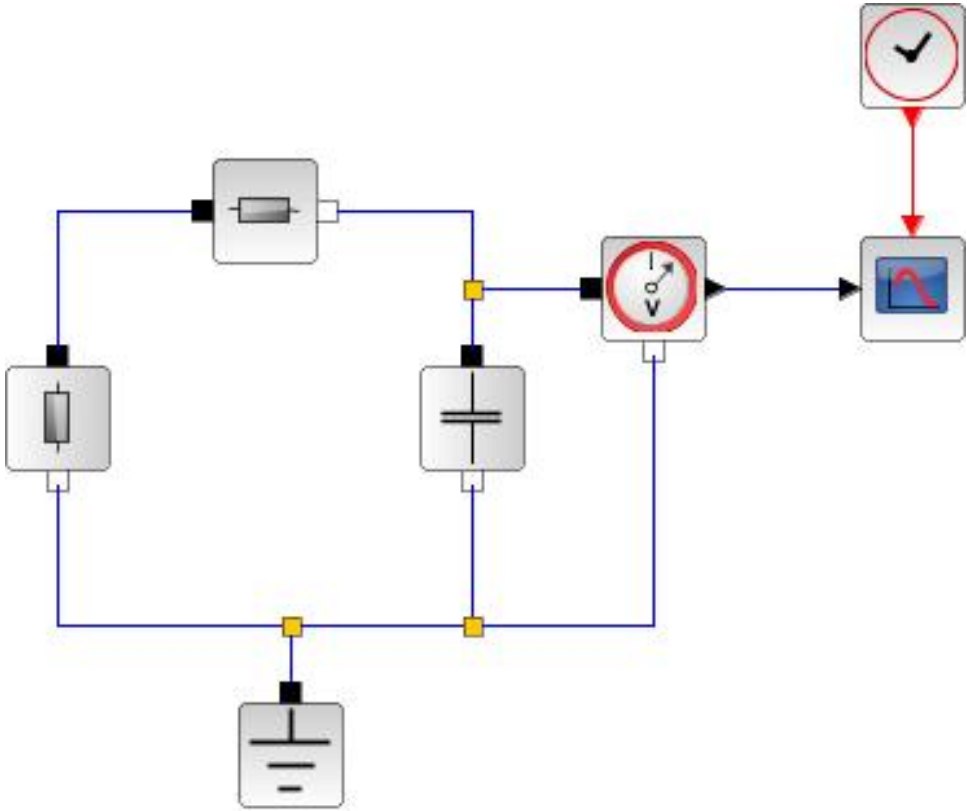


Figure 8.6: The Source free RC Circuit

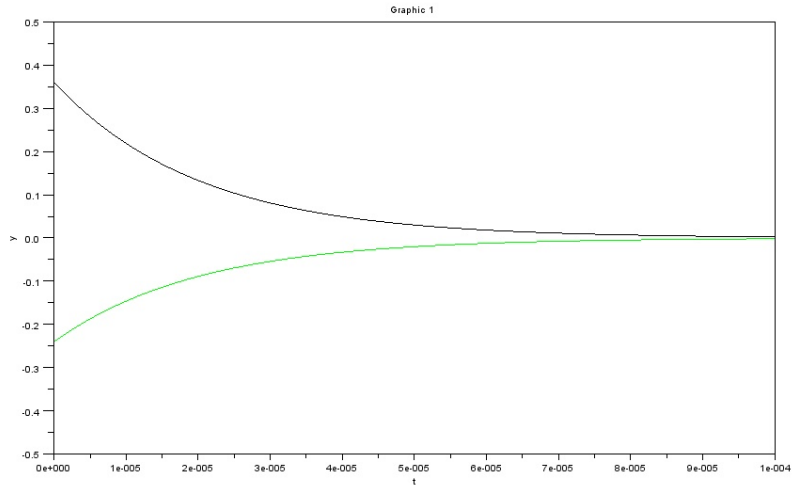


Figure 8.7: A more General Perspective

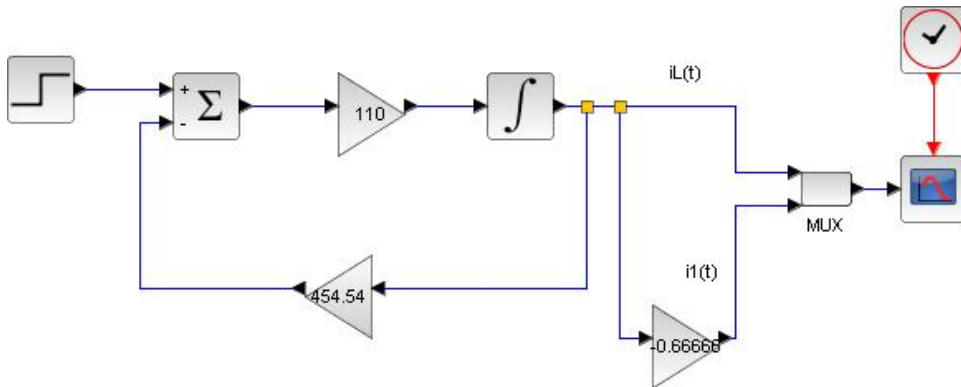


Figure 8.8: A more General Perspective

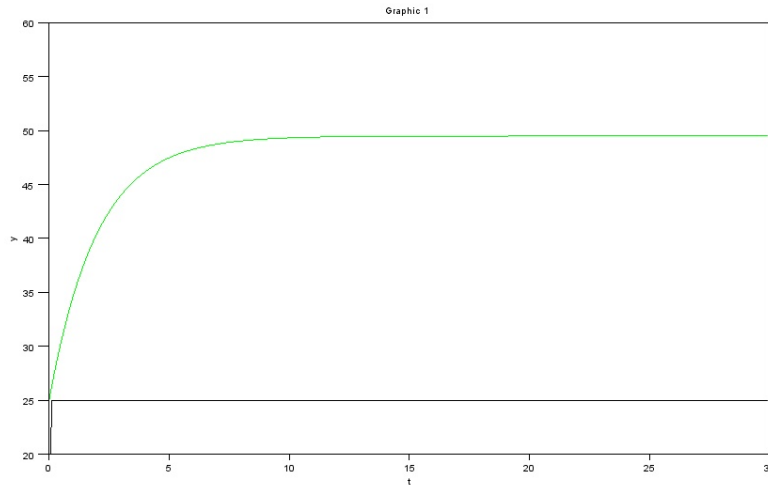


Figure 8.9: Natural and Forced Response

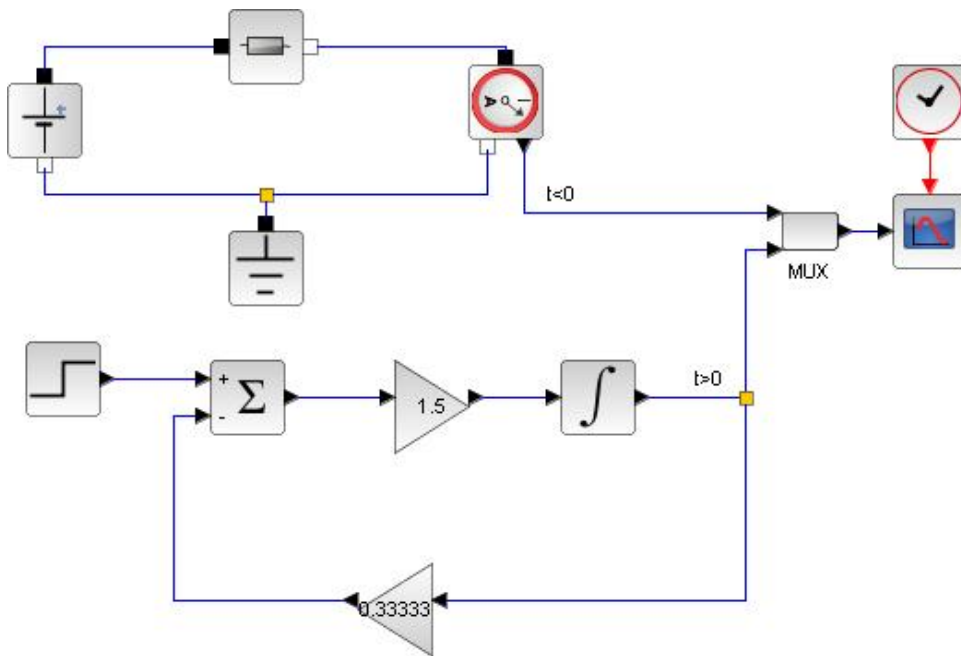


Figure 8.10: Natural and Forced Response

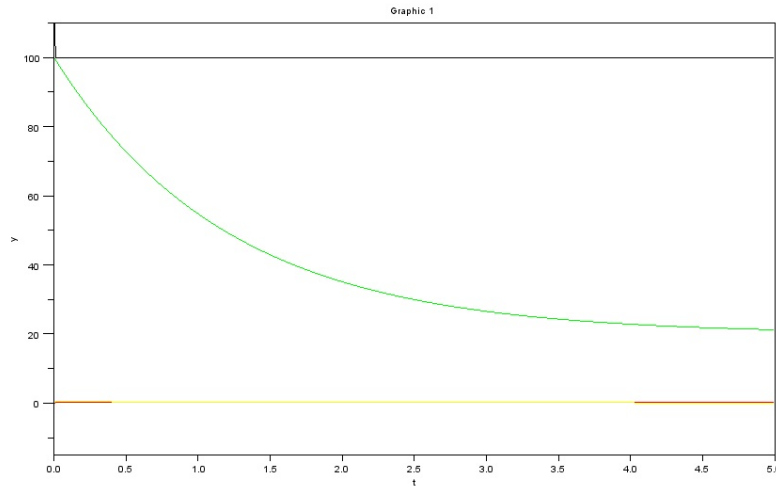


Figure 8.11: Driven RC circuits

This code can be downloaded from the website www.scilab.in

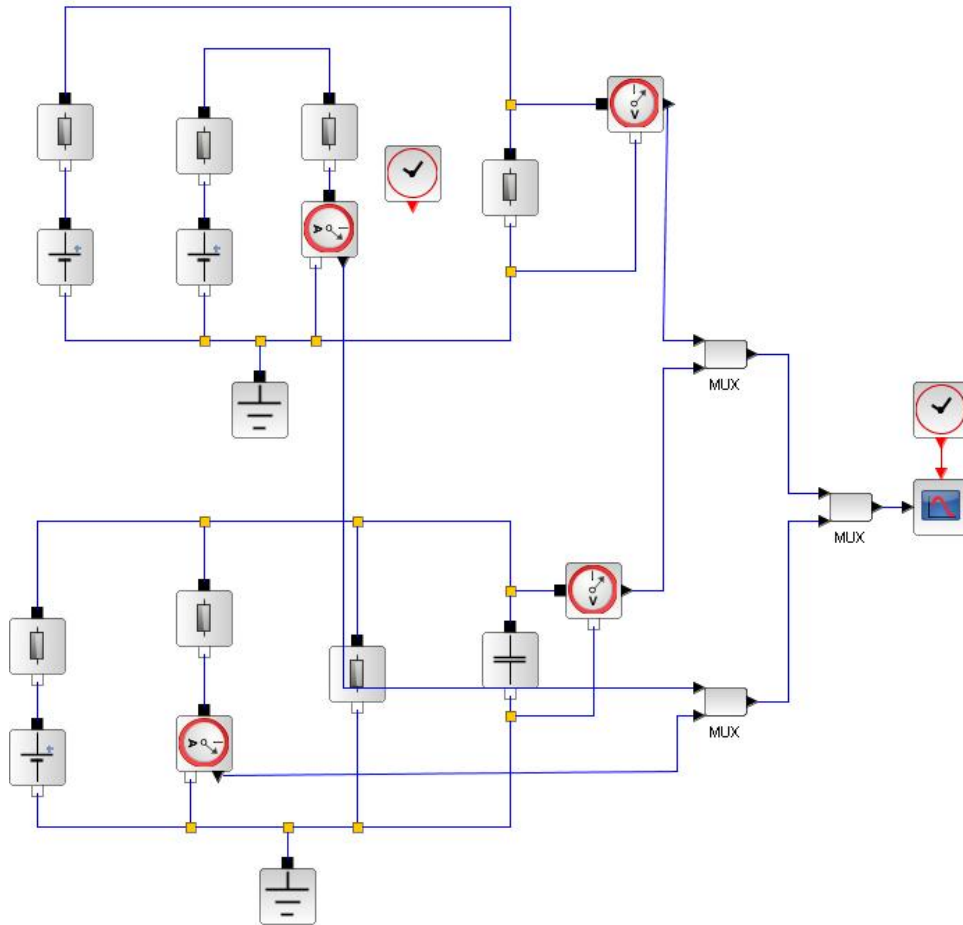


Figure 8.12: Driven RC circuits

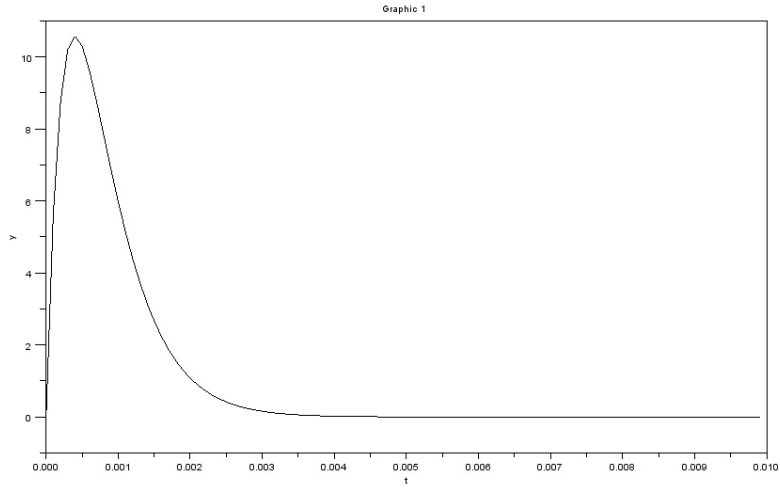


Figure 8.13: Driven RC circuits

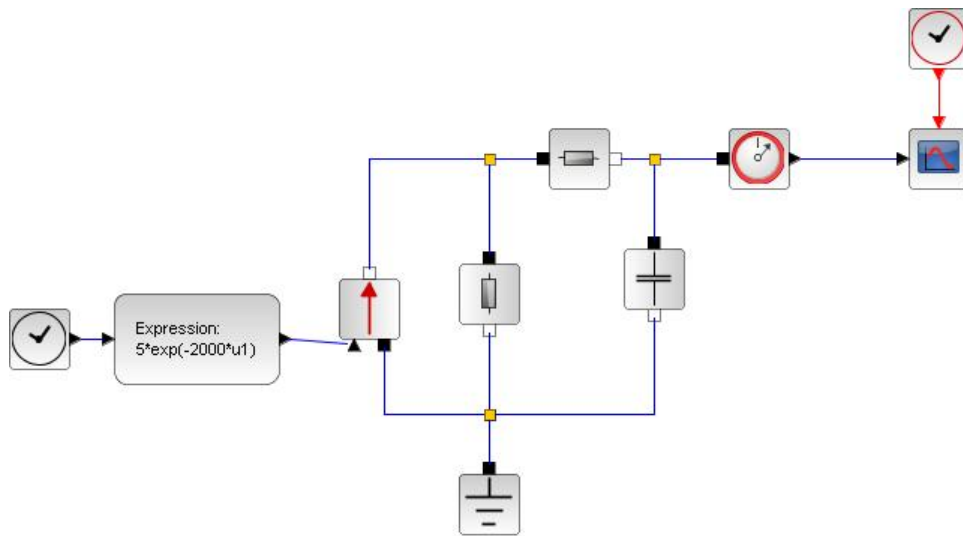


Figure 8.14: Driven RC circuits

Chapter 9

The RLC Circuit

Scilab code Exa 9.1 The Source free parallel circuit

```
1 //Example 9.1
2 // Calculate resistor values for underdamped and
   overdamped responses
3 printf(" Given")
4 disp('L=10mH and C=100uF')
5 L=10*10^-3; C=100*10^-6
6 w0=sqrt(1/(L*C))
7 printf("w0=%drad/s\n",w0)
8 //alpha(a)=1/(2*R*C)
9 disp('For an overdamped response')
10 disp('a > w0')
11 //On solving
12 disp('Hence')
13 disp('R<5ohm')
14 disp('For an underdamped response')
15 disp('a < w0')
16 //On solving
17 disp('Hence')
18 disp('R>5ohm')
```

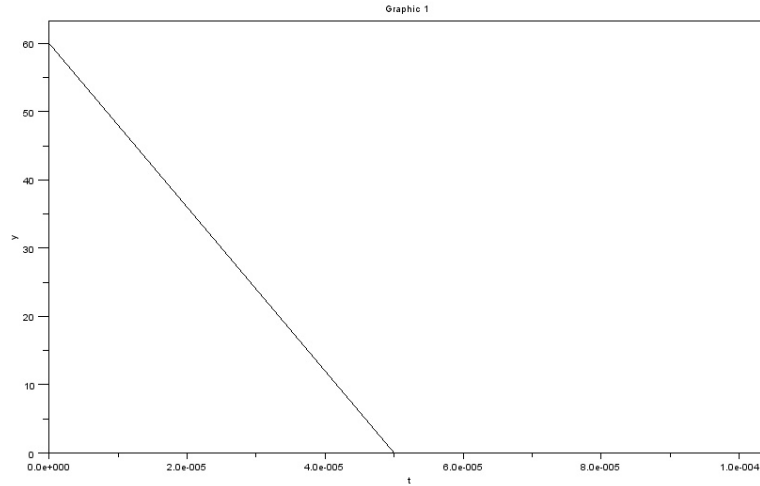


Figure 9.1: The Overdamped parallel circuit

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

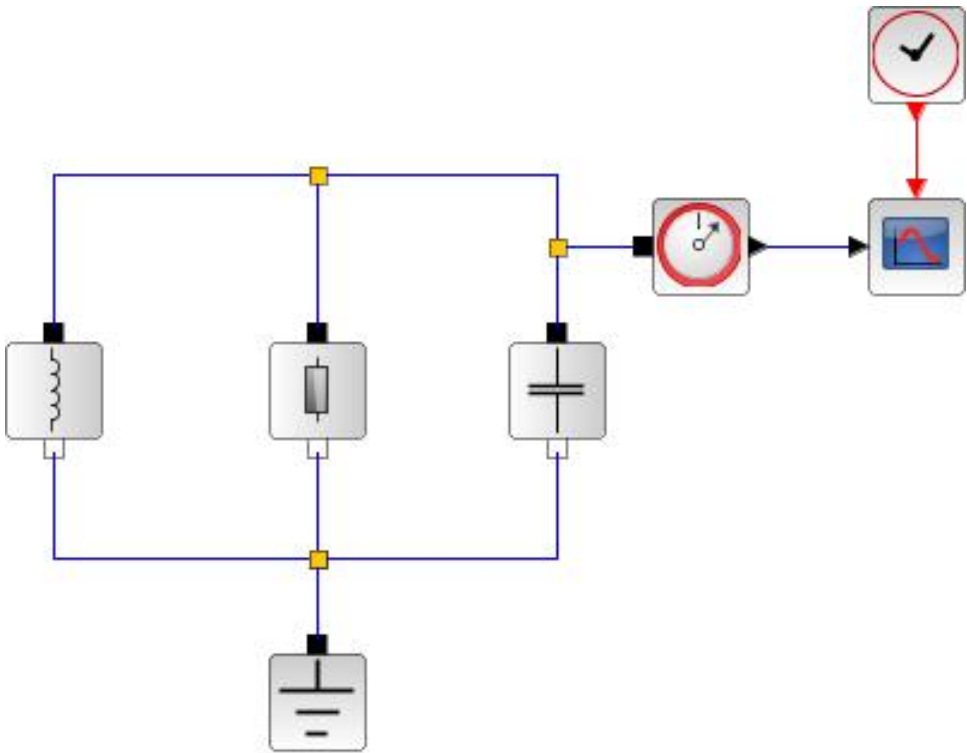


Figure 9.2: The Overdamped parallel circuit

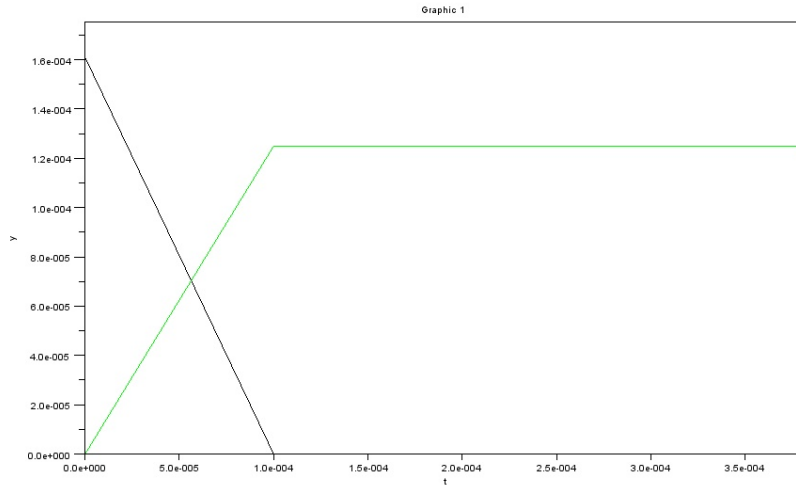


Figure 9.3: The Overdamped parallel circuit

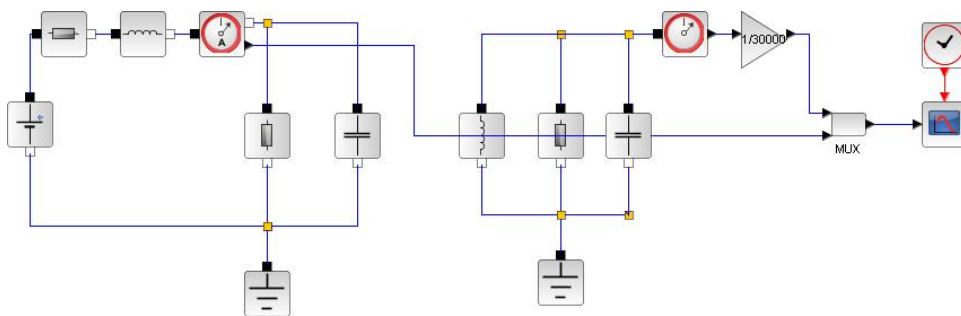


Figure 9.4: The Overdamped parallel circuit

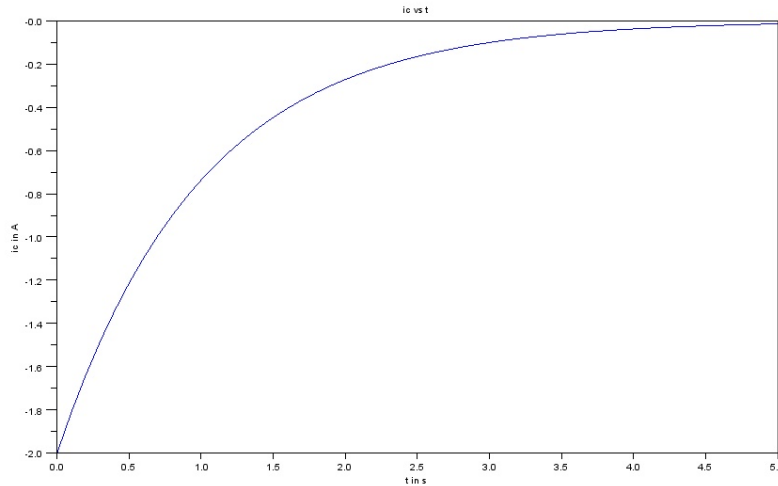


Figure 9.5: Graphical Representation of Overdamped response

Scilab code Exa 9.4 Graphical Representation of Overdamped response

```

1  clc
2  //Example 9.4
3  //Calculate settling time
4  t=0:0.1:5
5  ic=2*exp(-t)-4*exp(-t)
6  plot(t,ic)
7  xtitle('ic vs t','t in s','ic in A')
8  //Let ts be the settling time
9  //From the graph the maximum value is  $|-2|=2A$ 
10 // 'ts' is the time when ic has decreased to 0.02A
11 //On solving for 'ts'
12 ts=-log(0.02/4)
13 printf("ts=%3.2f s\n",ts)

```

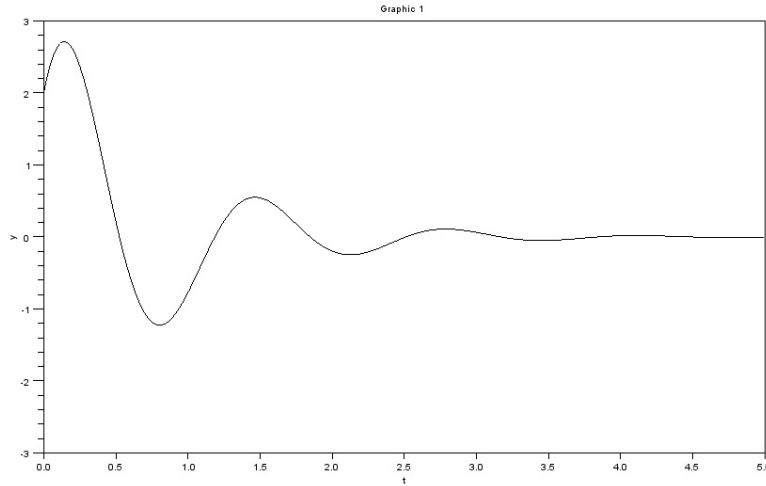


Figure 9.6: The Underdamped parallel RLC circuit

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

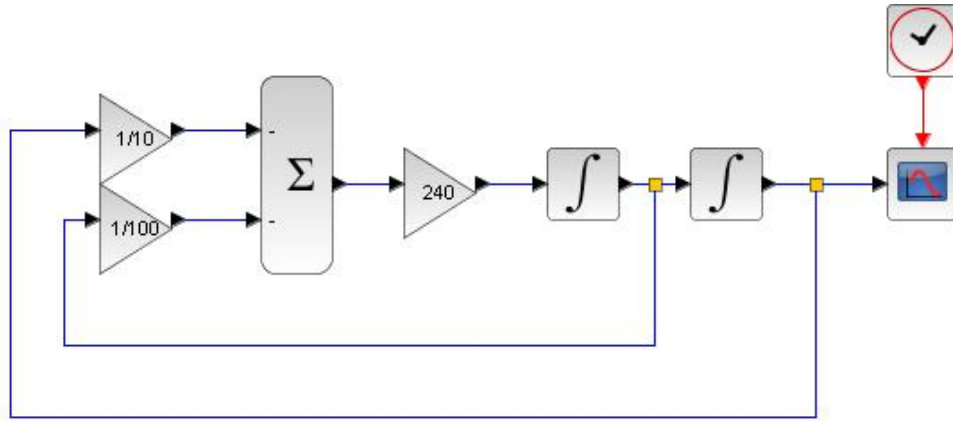


Figure 9.7: The Underdamped parallel RLC circuit

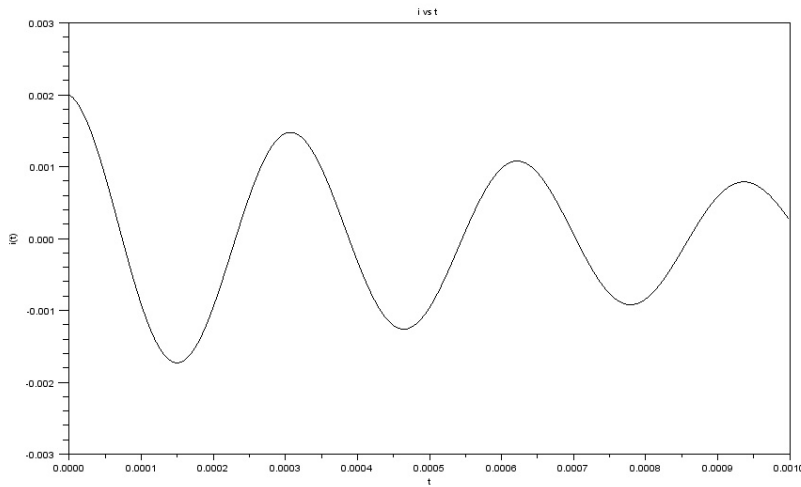


Figure 9.8: The Source free series RLC Circuit

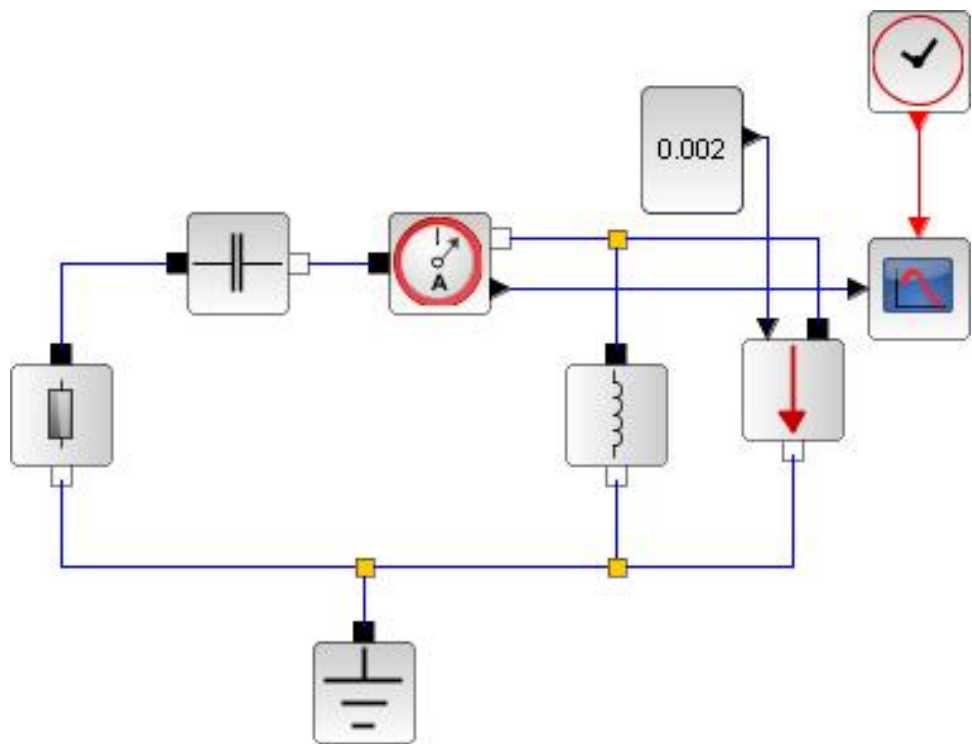


Figure 9.9: The Source free series RLC Circuit

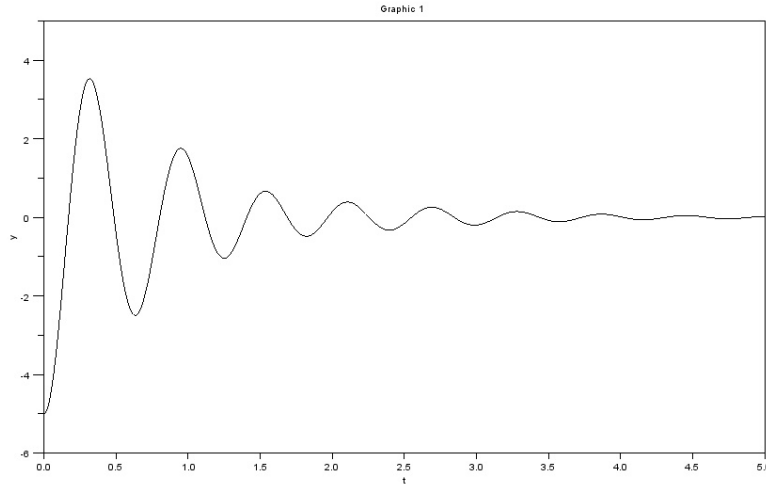


Figure 9.10: The Source free series RLC Circuit

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

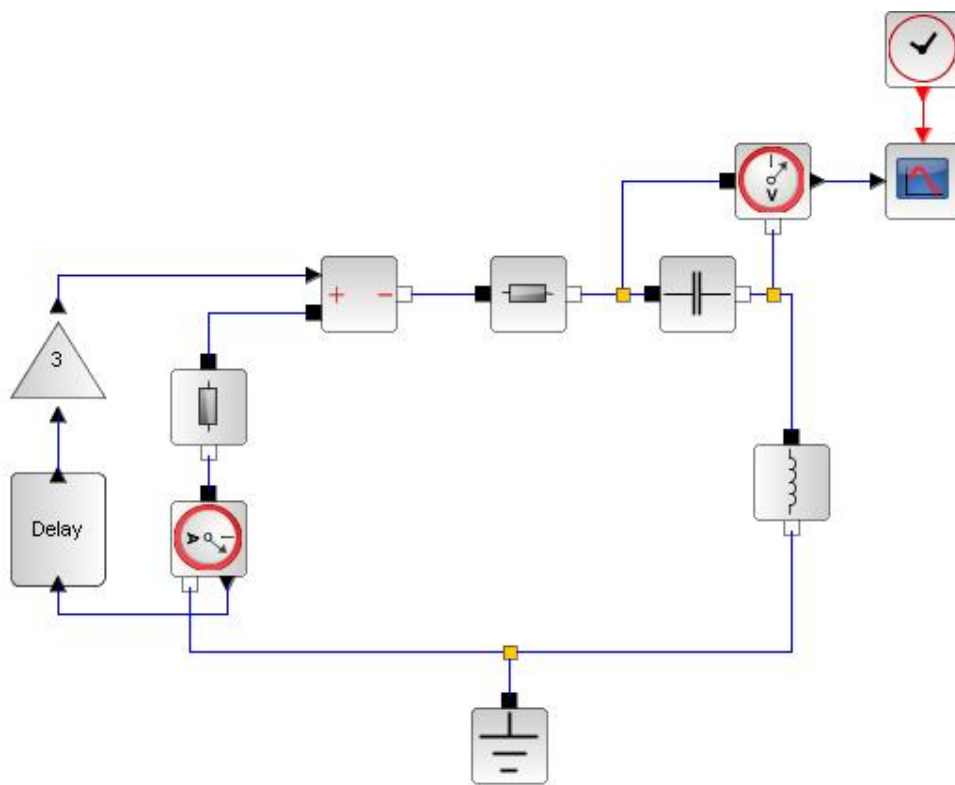


Figure 9.11: The Source free series RLC Circuit

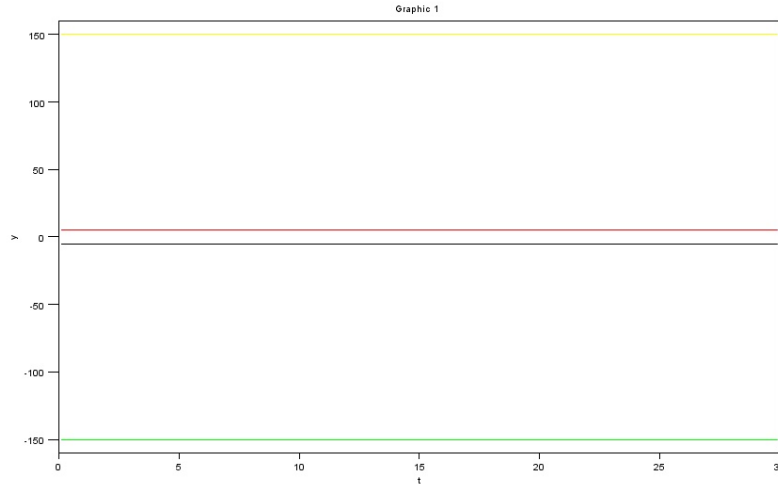


Figure 9.12: The Complete response of RLC circuit

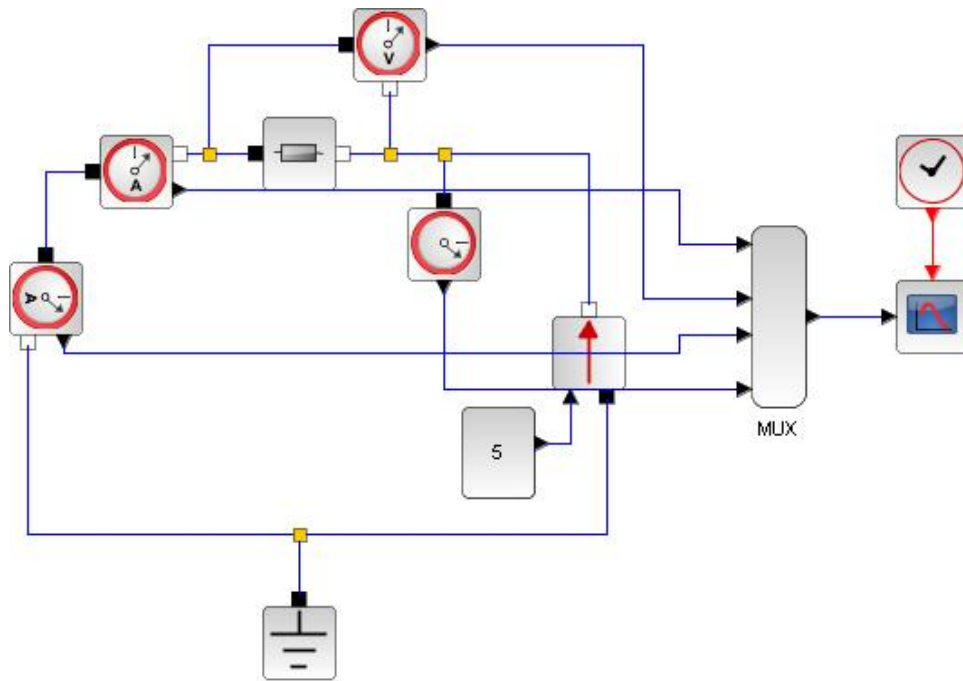


Figure 9.13: The Complete response of RLC circuit

Chapter 10

Sinusoidal Steady state Analysis

This code can be downloaded from the website www.scilab.in

Scilab code Exa 10.4 The Inductor

```
1  clc
2  //Example 10.4
3  //Determine phasor current and time-domain current
4  printf(" Given")
5  disp('Voltage is 8(-50 deg),Frequency is 100rad/s,
        Inductance is 4H')
6  L=4;
7  w=100;
8  Vamp=8;Vang=-50;
9  //Let current be I
10 Iamp=Vamp/(w*L)
```

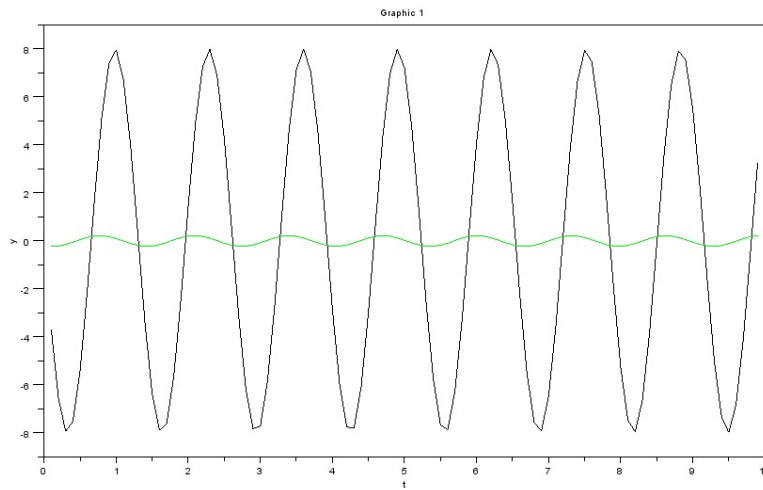


Figure 10.1: Forced Response to sinusoidal functions

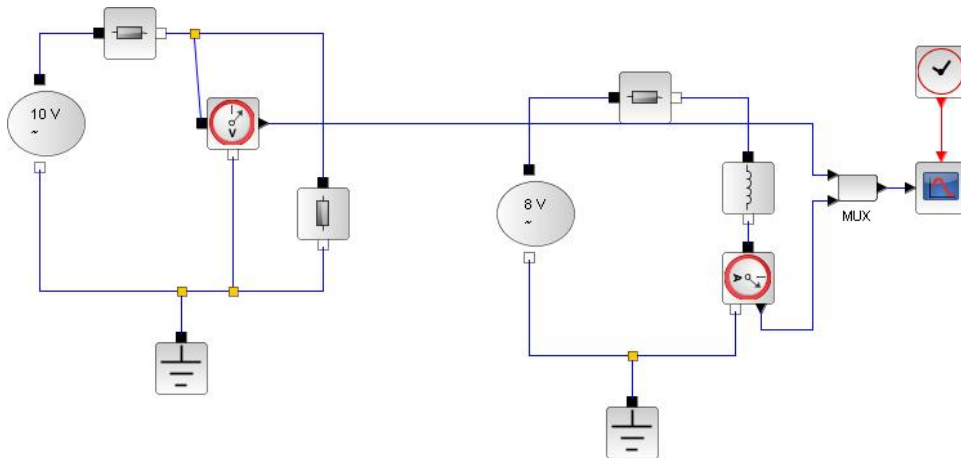


Figure 10.2: Forced Response to sinusoidal functions

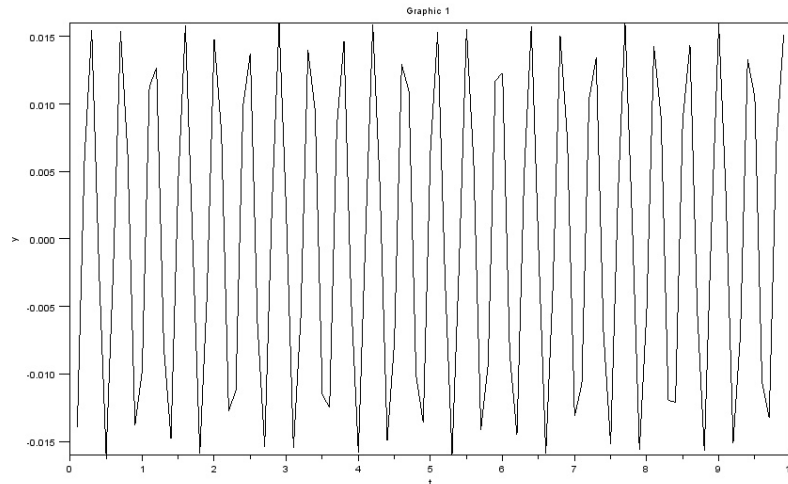


Figure 10.3: Impedance

```

11 Iang=-90+Vang
12 printf(" I=%3.2 f(%d deg) A \n",Iamp ,Iang)
13 //In time domain
14 printf(" i (t)=%3.2 f *cos (%d*t%d) A",Iamp ,w ,Iang);

```

This code can be downloaded from the website www.scilab.in

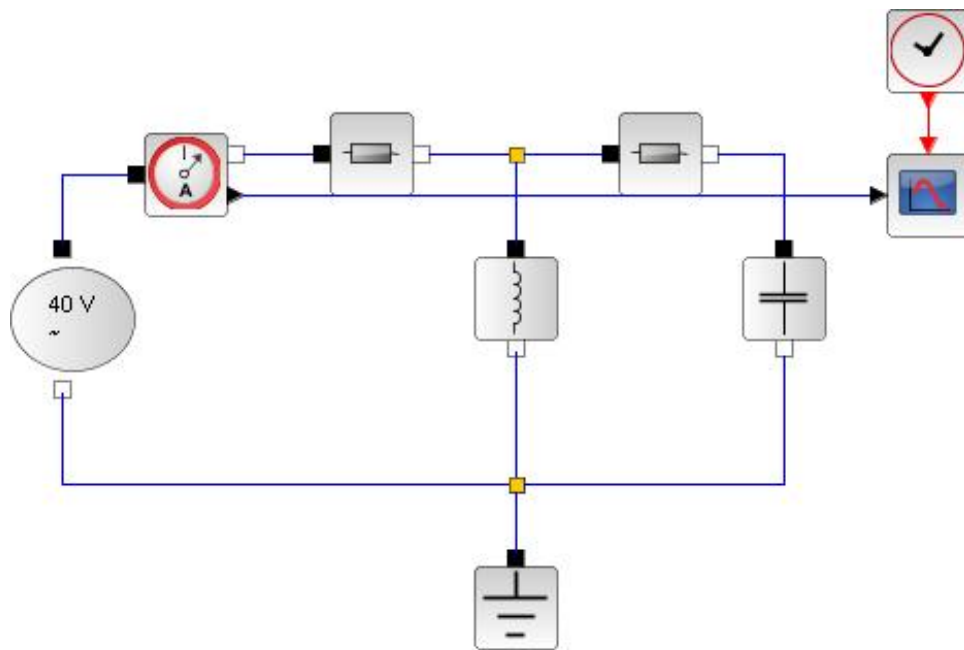


Figure 10.4: Impedance

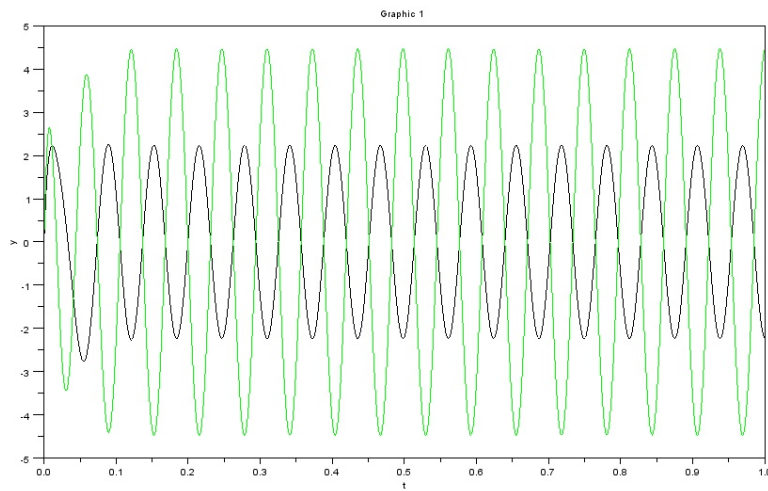


Figure 10.5: Nodal and Mesh analysis

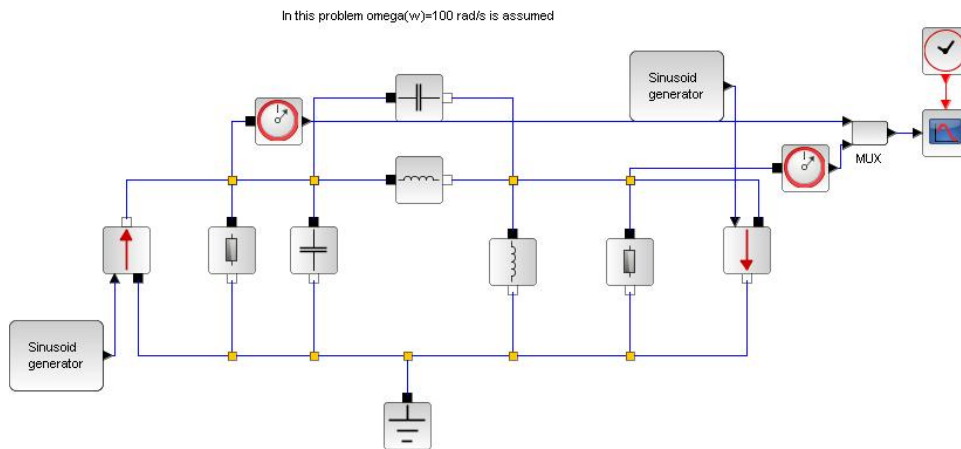


Figure 10.6: Nodal and Mesh analysis

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

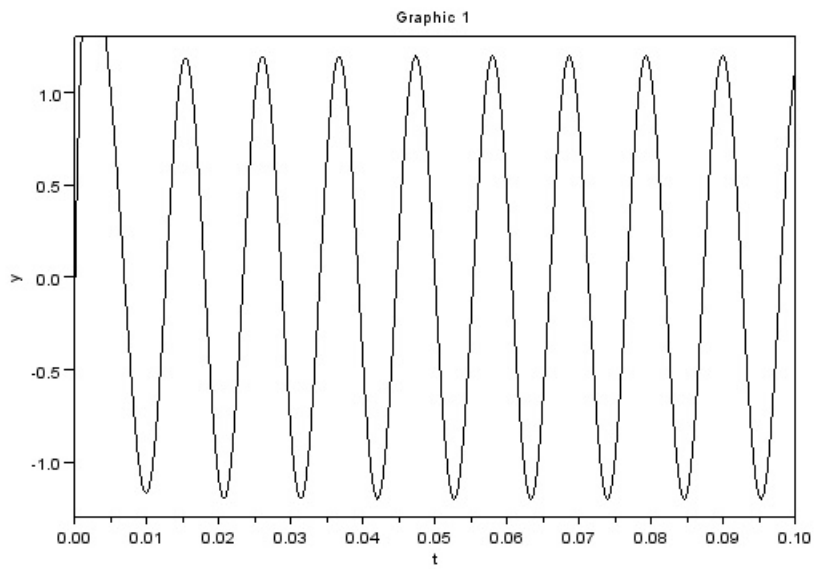


Figure 10.7: Nodal and Mesh analysis

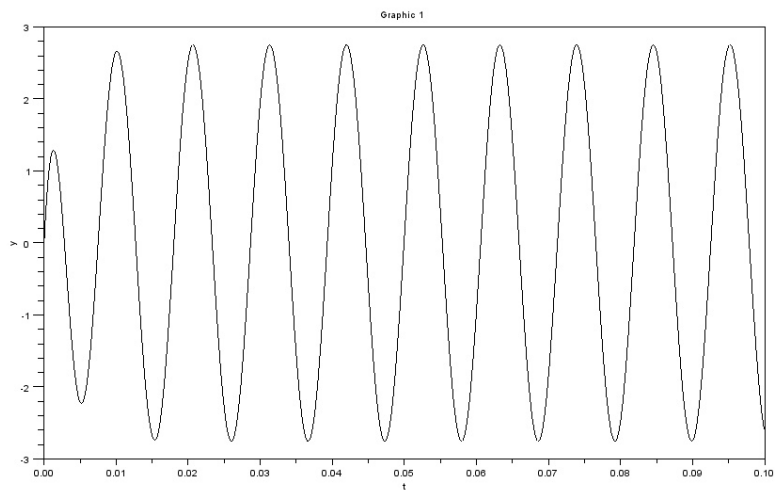


Figure 10.8: Nodal and Mesh analysis

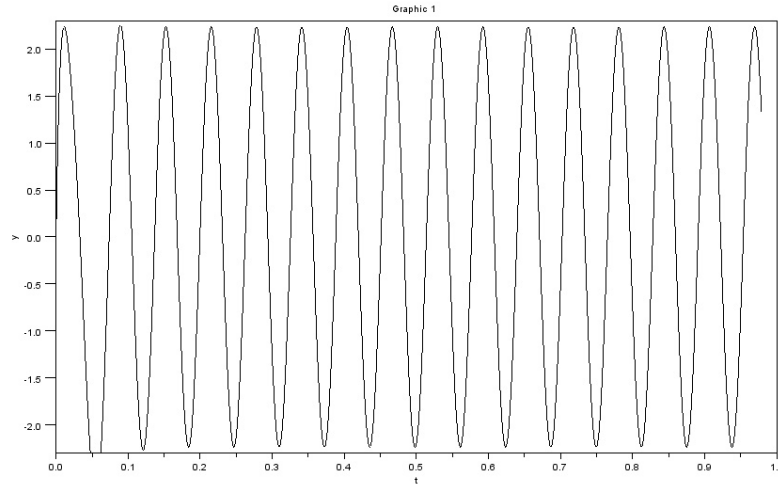


Figure 10.9: Superposition Source Transformations and Thevenin theorem

This code can be downloaded from the website www.scilab.in

This code can be downloaded from the website www.scilab.in

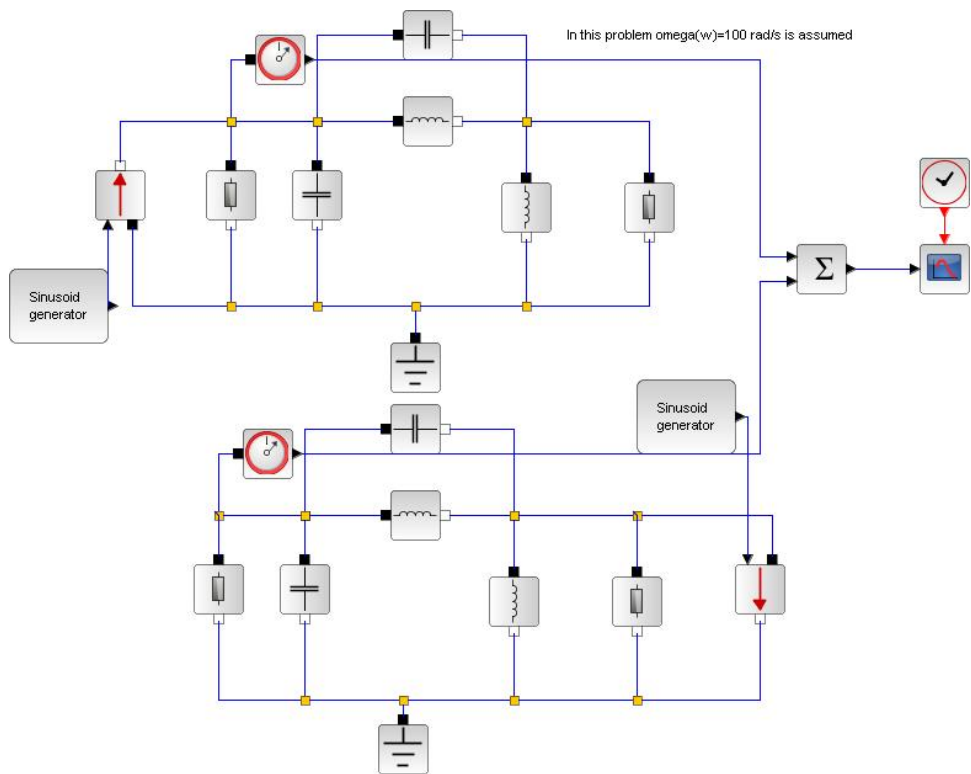


Figure 10.10: Superposition Source Transformations and Thevenin theorem

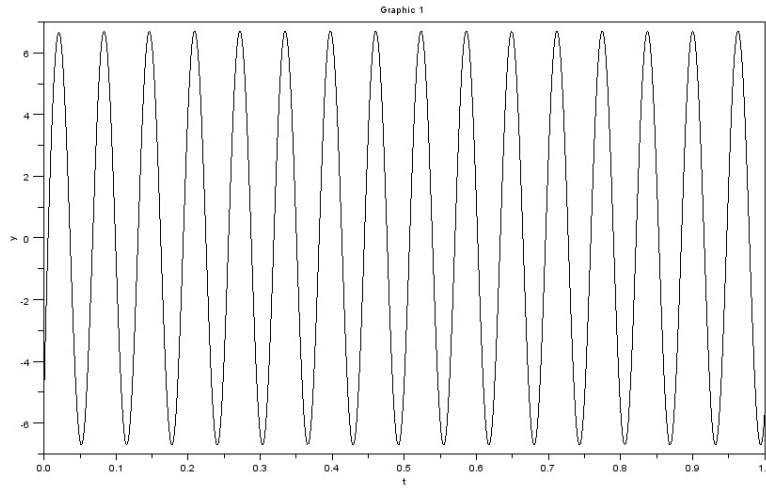


Figure 10.11: Superposition Source Transformations and Thevenin theorem

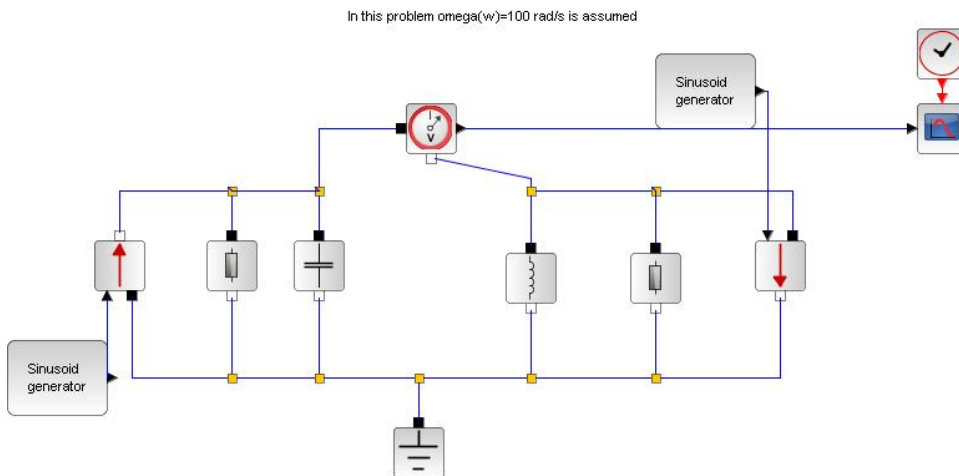


Figure 10.12: Superposition Source Transformations and Thevenin theorem

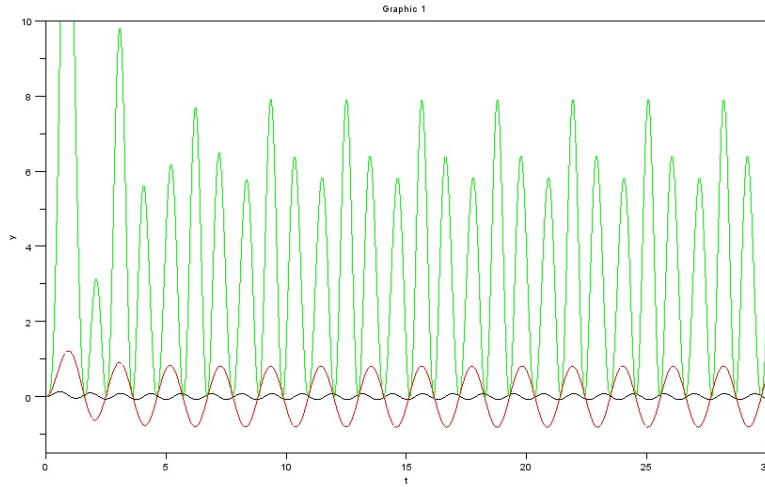


Figure 10.13: Superposition Source Transformations and Thevenin theorem

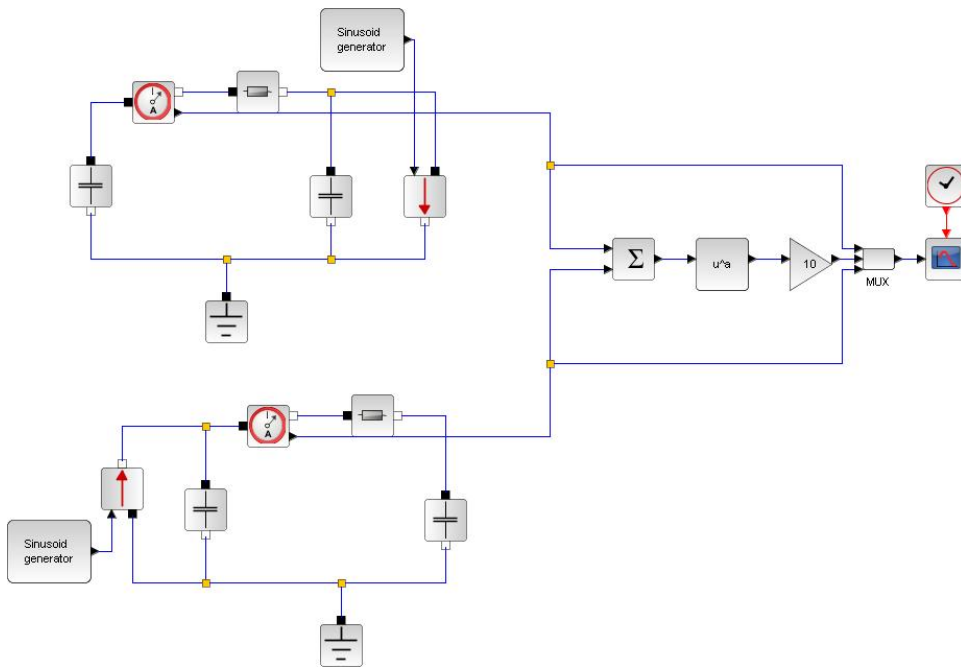


Figure 10.14: Superposition Source Transformations and Thevenin theorem

Chapter 11

AC Circuit Power Analysis

Scilab code Exa 11.1 Instantaneous Power

```
1 clc
2 //Example 11.1
3 //Calculate the powerr absorbed by capacitor and
  resistor
4 printf(" Given")
5 disp(' Capacitor 5uF, Resistor 200 ohm, Voltage
  source is 40+60*u(t) ')
6 C=5*10^-6;R=200;
7 //For t<0 the value of u(t) is zero hence at t=0-
  the value of voltage is 40V
8 //For t=0+ the voltage is 100V
9 //At t=0+ the capacitor cannot charge
  instantaneously hence resistor voltage is 60V
10 disp(' For t=0+')
11 VR=60;
12 i0=VR/R
13 T=R*C
14 t=1.2*10^-3
15 disp(' The value of current is i(t)=i0*exp(-t/T) ')
16 ival=i0*exp(-t/T)
17 printf(" Value of resistor current at 1.2ms=%3.2 f mA
```

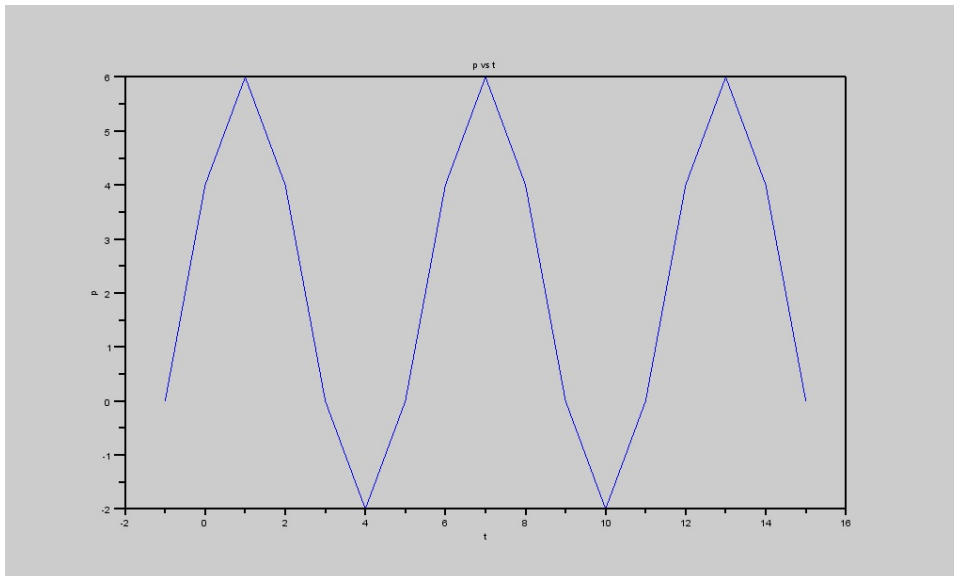


Figure 11.1: Average Power

```

    \n",ival*10^3)
18 //Let PR be the power absorbed by the resistor
19 PR=ival^2*R
20 printf("Value of resistive power at 1.2ms=%3.2f W \n
    ",PR)
21 //Out of the 100V available at t>0 the voltage
    across the capacitor is
22 disp('vC(t)=100-60*exp(-t/T)')
23 vCval=100-60*exp(-t/T)
24 printf("Value of capacitor voltage at 1.2ms=%3.2f V
    \n",vCval)
25 //Let PC be the power absorbed by the capacitor
26 PC=ival*vCval
27 printf("Value of capacitive power at 1.2ms=%3.2f W \
    n",PC)

```

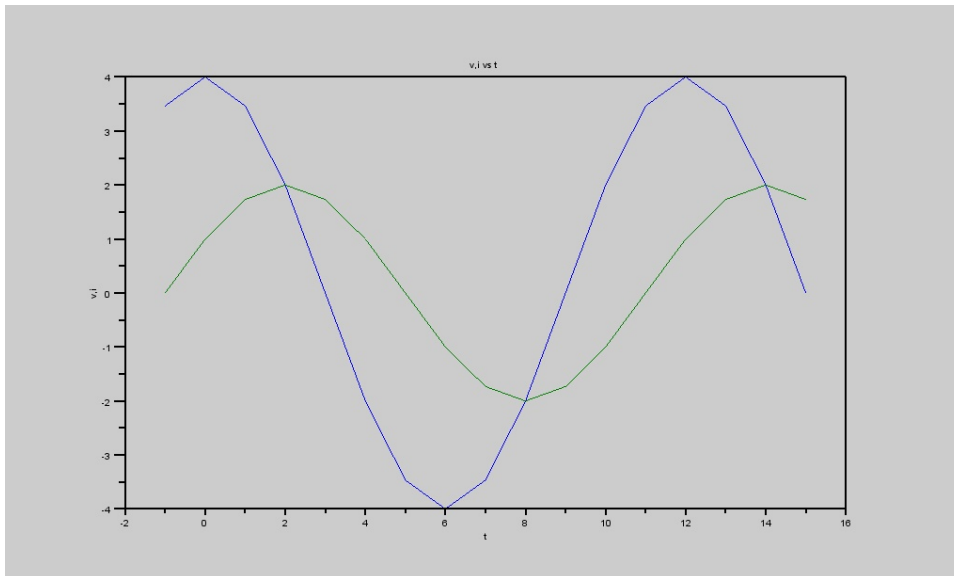


Figure 11.2: Average Power

Scilab code Exa 11.2 Average Power

```

1  clc
2  //Example 11.2
3  //Calculate the average power
4  printf(" Given")
5  disp('v=4*cos(%pi/6*t), V=4(0 deg), Z=2(60 deg)')
6  Vamp=4; Vang=0; Zamp=2; Zang=60;
7  //Let I be the phasor current
8  Iamp=Vamp/Zamp
9  Iang=Vang-Zang
10 P=0.5*Vamp*Zamp*cos((Zang*%pi)/180)
11 printf("P=%d W \n", P);
12 t=-1:1:15

```

```

13 t1=-3:1:12
14 v=Vamp*cos(%pi/6*t)
15 //i=2*cos((%pi/6)*t-(%pi/3))
16 i=Iamp*cos(%pi/6*t+((Iang*%pi)/180))
17 figure
18 a= gca ();
19 plot (t,v,t,i)
20 xtitle ('v,i vs t' , 't' , 'v,i');
21 a. thickness = 2;
22 //Instantaneous power p=v*i
23 //On solving
24 p=2+4*cos(%pi/3*t+((Iang*%pi)/180))
25 figure
26 a= gca ();
27 plot (t,p)
28 xtitle ('p vs t' , 't' , 'p');
29 a. thickness = 2;

```

Scilab code Exa 11.3 Average Power

```

1 clc
2 //Example 11.3
3 //Calculate the Average Power
4 printf(" Given")
5 disp('ZL=8-i*11 ohm, I=5(20 deg)A')
6 R=8;Iamp=5;
7 //We need to calculate the average power
8 //In the calculation of average power the resistance
   part of impedace only occurs
9 //Let P be the average power
10 P=0.5*Iamp^2*R
11 printf(" Average Power=%d W \n" ,P)

```

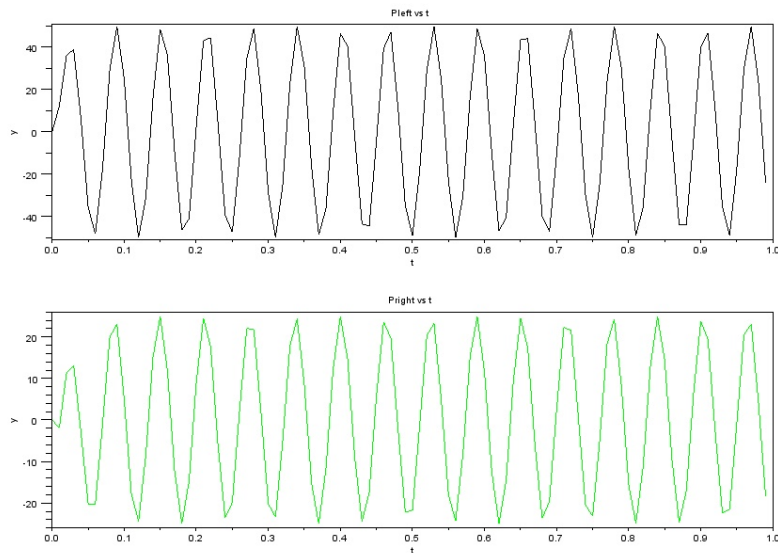


Figure 11.3: Average Power

Scilab code Exa 11.4 Average Power

```

1  clc
2  //Example 11.4
3  //Calculate the Average power absorbed and average
   power supplied by source
4  //From figure 11.6
5  //By applying mesh analysis
6  I1mag=11.18; I1ang=-63.43; I2mag=7.071; I2ang=-45; R=2;
   Vleft=20; Vright=10;
7  //Current through 2 ohm resistor
8  printf("I1-I2=%d(%d ang) A \n",5,-90)
9  //Average power absorbed by resistor
10 PR=0.5*5^2*R

```

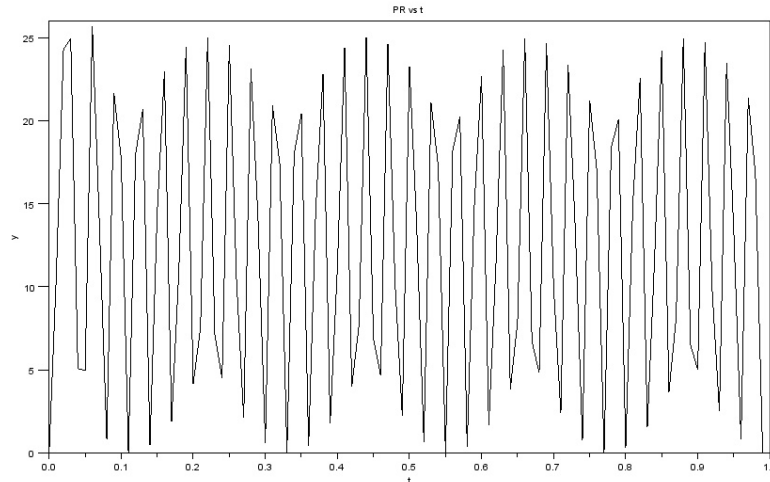



Figure 11.4: Average Power

```

11 printf("Average power absorbed by resistor=%d W \n",
    PR)
12 //Power supplied by left source
13 Pleft=0.5*Vleft*I1mag*cos(0-I1ang*pi/180)
14 //Power supplied by right source
15 Pright=0.5*Vright*I2mag*cos(0+I2ang*pi/180)
16 printf("Power supplied by sources \t Pleft=%d W \t
    Pright=%3.1 f W",Pleft,Pright);

```

Scilab code Exa 11.6 Average Power for Non periodic Functions

```

1 clc
2 //Example 11.6
3 //Calculate the Average power
4 printf("Given")
5 disp('Resistor value is 4 ohm, i1=2*cos(10t)-3*cos
    (20t) A')

```

```

6 R=4;im1=2;im2=-3;
7 //Let P be the average power delievered
8 P=0.5*im1^2*R+0.5*im2^2*R
9 printf("Average power=%d W",P)

```

Scilab code Exa 11.7 Average Power for Non periodic Functions

```

1 clc
2 //Example 11.7
3 //Calculate the Average power
4 printf("Given")
5 disp('Resistor value is 4 ohm, i2=2*cos(10t)-3*cos
      (10t) A')
6 disp('On solving we get i2=-cos(10t)')
7 R=4;im=-1
8 //Let P be the average power delievered
9 P=0.5*im^2*R
10 printf("Average power=%d W",P)

```

Scilab code Exa 11.8 Apparent Power and Power factor

```

1 clc
2 //Example 11.8
3 //Calculate average power, power supplied by source
  and the power factor
4 printf("Given")
5 disp('Voltage source is 60 V,Load values are 2-i ohm
      and 1+5i ohm')
6 Vamp=60;Vang=0;
7 //Let Z be the cobined resistance
8 Z=2-%i+1+5*%i
9 [Zmag Zph]=polar(Z)
10 Isamp=Vamp/Zmag;

```

```

11 Isang=Vang-Zph;
12 printf(" Ieff=%3.0f A rms and angle of Is is %3.2f
    degree\n",Isamp,(Isang*180)/%pi);
13 //Let Pupper be the power delivered to the upper
    load
14 Rtop=2;
15 Pupper=Isamp^2*Rtop
16 printf(" Average Power delivered to the top load=%3
    .0f W \n",Pupper)
17 //Let Plower be the power delivered to the lower
    load
18 Rright=1;
19 Plower=Isamp^2*Rright
20 printf(" Average Power delivered to the right load=
    %3.0f W \n",Plower)
21 //Let Papp be the apparent power
22 Papp=Vamp*Isamp
23 printf(" Apparent Power =%3.0f VA \n",Papp)
24 //Let pf be the power factor
25 pf=(Pupper+Plower)/Papp
26 printf(" power factor=%3.1f lag \n",pf)

```

Scilab code Exa 11.9 Complex Power

```

1 clc
2 //Example 11.9
3 printf(" Given")
4 disp('Power of induction motor=50kW ,power factor is
    0.8 lag ,Source voltage is 230V')
5 disp('The wish of the consumer is to raise the power
    factor to 0.95 lag')
6 //Let S1 be the complex power supplied to the
    induction motor
7 V=230;Pmag=50*10^3;pf=0.8;
8 Pang=(acos(pf)*180)/%pi

```

```

 9 S1mag=Pmag/pf
10 S1ph=Pang
11 x=S1mag * cos (( Pang * %pi ) /180) ;
12 y=S1mag * sin (( Pang * %pi ) /180) ;
13 z= complex (x,y)
14 disp(z , 'S1=')
15 //To achieve a power factor of 0.95
16 pf1=0.95
17 //Now the total complex power be S
18 P1ang=(acos(pf1)*180)/%pi
19 Smag=Pmag/pf1
20 Sph=P1ang
21 a=Smag * cos (( P1ang * %pi ) /180) ;
22 b=Smag * sin (( P1ang * %pi ) /180) ;
23 c= complex (a,b)
24 disp(c, 'S=')
25 //Let S2 be the complex power drawn by the
    corrective load
26 S2=c-z
27 disp(S2, 'S2=')
28 disp('Let a phase angle of voltage source selected
    be 0 degree')
29 //Let I2 be the current
30 I2=-S2/V
31 //Let Z2 be the impedance of corrective load
32 Z2=V/I2
33 disp(Z2, 'Z2=')

```

Chapter 12

Polyphase Circuits

This code can be downloaded from the website www.scilab.in

Scilab code Exa 12.2 Three phase Wye connection

```
1 clc
2 //Example 12.2
3 //Calculate total power dissipated
4 disp('Given ')
5 disp('Van=200 with angle 0 degree and Zp=100with
      angle 60 degree ')
6 Zpamp=100;Zpang=60
7 //Since one of the phase voltage is given , we need
      to find other phase voltages
8 Vanamp=200;Vbnamp=200 ; Vcnamp=200;
9 Vanang=0;Vbnang=-120;Vcnang=-240;
10 disp('The phase voltages are ')
11 printf("Van=%d /_%d deg V\tVbn=%d /_%d deg V\tVcn=%d
      /_%d deg V\t",Vanamp ,Vanang ,Vbnamp ,Vbnang ,Vcnamp
      ,Vcnang)
```

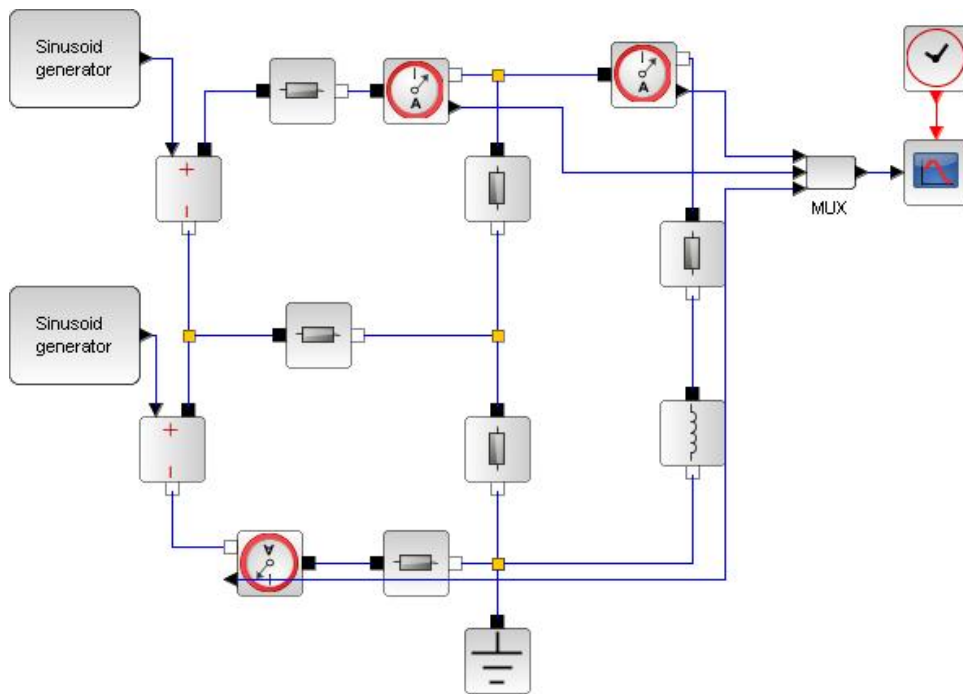


Figure 12.1: Single phase three wire systems

```

12
13 //Now we will find line voltages
14 //Let line voltage be Vline
15 Vline=200*sqrt(3)
16 //By constructing a phasor diagram
17 disp('The line voltages are')
18 printf("\n Vab=%d /_%d deg V\tVbc=%d /_%d deg V\tVca
        =%d /_%d deg V\t",Vline,30,Vline,-90,Vline,-210)
19
20 //Let the line current be IaA
21 IaAamp=Vanamp/Zpamp
22 IaAang=Vanang-Zpang
23 //Since the given system is a balanced three phase
    system
24 //From phasor diagram as shown in figure 12.16
25 disp('The line currents are')
26 printf("\n IaA=%d /_%d deg V\tIbB=%d /_%d deg V\tIcC
        =%d /_%d deg V\t",IaAamp,IaAang,IaAamp,IaAang
        -120,IaAamp,IaAang-240)
27 //Let power absorbeed by phase A is PAN
28 PAN=Vanamp*IaAamp*cos(((Vanang+IaAang)*%pi)/180)
29 printf("\n Total average power = %d W",3*PAN)

```

Scilab code Exa 12.3 Three phase Wye connection

```

1 clc
2 //Example 12.3
3 //Calculate the line current and phase impedance
4 disp('Given')
5 disp('Line voltage = 300V, Power factor=0.8(lead),
    Phase power = 1200W')
6 Vline=300;pf=0.8;PW=1200;
7 Vp=Vline/sqrt(3)
8 PerPhpower=PW/3;
9 //Line current can be found as

```

```

10 IL=PerPhpower/(pf*Vp)
11 printf("Line current= %3.2 f A \n",IL)
12 //Let Zp be the phase impedance
13 Zpmag=Vp/IL
14 //Sice power factor is 'leading '
15 Zpang=-(acos(0.8)*180)/%pi
16 printf("Phase impedance = %d/_%3.2 f deg ohm",Zpmag,
        Zpang);

```

Scilab code Exa 12.4 Three phase Wye connection

```

1  clc
2  //Example 12.4
3  //Calculate the line current
4  //Continuing from example 12.3
5  Vp=300/sqrt(3);
6  IL=2.89;pf=0.8
7  disp('A balanced 600W lighting load is added in
        parallel with the existing load')
8  disp('600W if balanced then 200W will be consumed by
        each phase')
9  Vpadd=200;
10 //From figure 12.17
11 I1=Vpadd/Vp
12 disp('Load current is unchanged')
13 I2mag=IL
14 I2ph=(acos(pf)*180)/%pi
15 x=I2mag * cos (( I2ph * %pi ) /180) ;
16 y=I2mag * sin (( I2ph * %pi ) /180) ;
17 z= complex (x,y)
18 disp(z)
19 ILnew=I1+z
20 [ILmag ILph]=polar(ILnew)
21 printf("Line current=%3.2 f /_%3.2 f deg A \n ",ILmag,
        ILph*(180/%pi));

```

Scilab code Exa 12.5 The Delta connection

```
1 clc
2 //Example 12.5
3 //Calculate amplitude of line current
4 disp('Given')
5 disp('Line voltage = 300V, Power factor=0.8(lag),
      Phase power = 1200W')
6 Vline=300;pf=0.8;PW=1200;
7 disp('1200W will be consumed as 400W in each phase')
8 Vp=400
9 //Phase current be Ip
10 Ip=Vp/(Vline*pf)
11 //Let amplitude of line current be IL
12 IL=Ip*sqrt(3)
13 printf("Line current=%3.2 f A \n",IL)
14 //Let Zp be the phase impedance
15 Zpmag=Vline/Ip
16 //Since power factor is 'lagging'
17 Zpang=(acos(0.8)*180)/%pi
18 printf("Phase impedance = %d(%3.2 f deg)ohm",Zpmag,
      Zpang);
```

Scilab code Exa 12.6 The Delta connection

```
1 clc
2 //Example 12.6
3 //Calculate amplitude of line current
4 disp('Given')
5 disp('Line voltage = 300V, Power factor=0.8(lag),
      Phase power = 1200W')
```

```

6 Vline=300;pf=0.8;PW=1200;
7 Vph=Vline/sqrt(3)
8 disp('1200W will be consumed as 400W in each phase')
9 Vp=400
10 //Let phase current be Ip
11 Ip=Vp/(Vph*pf)
12 printf("Phase current=%3.2f A \n",Ip)
13 //Let Zp be the phase impedance
14 Zpmag=Vph/Ip
15 //Since power factor is 'lagging'
16 Zpang=(acos(0.8)*180)/%pi
17 printf("Phase impedance = %d(%3.2f deg)ohm\n",Zpmag,
        Zpang);
18 //PW=sqrt(3)*VL*IL*pf
19 IL=PW/(sqrt(3)*Vline*pf)
20 printf("Line current=%3.2f A \n",IL)

```

Scilab code Exa 12.7 Power measurement in three phase systems

```

1 clc
2 //Example 12.7
3 //Determine wattmeter reading and total power drawn
  by the load
4 disp('Given')
5 disp('Vab=230(0 deg)V')
6 Vline=230
7 //Since positive phase sequence is used
8 disp('The line voltages are')
9 printf("\n Vab=%d (%d deg)V\tVbc=%d (%d deg) V\tVca=
        %d (%d deg)V\t",Vline,0,Vline,-120,Vline,120)
10 Vacamp=Vline;
11 Vacang=-60;
12 Vbcamp=Vline;
13 Vbcang=-120;
14 //Now we will evaluate phase current

```

```

15 //Let IaA be the phase current
16 Vanamp=Vline/sqrt(3)
17 Vanph=-30
18 //From figure 12.28
19 Zph=4+%i*15
20 [Zphmag Zphang]=polar(Zph)
21 IaAamp=Vanamp/Zphmag
22 IaAang=Vanph-(Zphang*180)/%pi
23 IbBang=IaAang+240
24 printf("\nIaA=%3.2 f (%3.2 f deg)A\n",IaAamp,IaAang);
25 //Power rating of each wattmeter is now calculated
26 //Power measured by wattmeter #1
27 P1=Vline*IaAamp*cos(((Vacang-IaAang)*%pi)/180)
28 printf("P1=%d W \n",P1)
29 //Power measured by wattmeter #2
30 P2=Vline*IaAamp*cos(((Vbcang-IbBang)*%pi)/180)
31 printf("P2=%3.2 f W \n",P2)
32 //Net power be P
33 P=P1+P2
34 printf("P=%3.2 f W \n",P)

```

Chapter 13

Magnetically coupled circuits

Scilab code Exa 13.2 Mutual Inductance

```
1 clc
2 //Example 13.2
3 disp('Given')
4 disp('Input voltage is 10V')
5 Viamp=10
6 //From figure 13.7
7 //Writing the left mesh equations
8 disp('(1+10i)*I1-90i*I2=10')
9 //Writing the right mesh equations
10 disp('(400+1000i)*I2-90i*I1=0')
11 i=%i
12 A=[1+10*i -90*i;-90*i 400+1000*i]
13 i2mat=[1+10*i 10; -90*i 0]
14 //Find i2
15 i2=det(i2mat)/det(A)
16 [mag Theta]=polar(i2)
17 Theta=(Theta*180)/%pi
18 //The value of resistor is 400 ohm
19 R=400;
20 //Let V=V2/V1
21 Vamp=R*mag/Viamp
```

```

22 printf("Ratio of output voltage to input is %3.2f
    with angle %3.2f degrees",Vamp,Theta);

```

Scilab code Exa 13.4 Energy considerations

```

1  clc
2  //Example 13.4
3  disp('Given')
4  disp('L1=0.4H L2=2.5H k=0.6 i1=4i2=20*cos(500t-20)mA
    ')
5  L1=0.4;L2=2.5;k=0.6;
6  disp('a')
7  t=0;
8  i2=5*cos(500*t-(20*%pi)/180)
9  printf("i2(0)=%3.2f mA \n",i2)
10 disp('b')
11 M=k*sqrt(L1*L2)
12 //v1(t)=L1*d/dt(i1)+M*d/dt(i2)
13 v1=-L1*20*500*10^-3*sin(500*t-(20*%pi)/180)-M
    *5*500*10^-3*sin(500*t-(20*%pi)/180)
14 printf("v1(0)=%3.2f V \n",v1)
15 disp('c')
16 //The total energy can be found as
17 w=(L1*(4*i2)^2)/2+(L2*(i2)^2)/2+M*(4*i2)*(i2)
18 printf("w=%3.2f uJ \n",w)

```

Scilab code Exa 13.5 T and PI equivalent networks

```

1  clc
2  //Example 13.5
3  printf("Given")
4  disp('L1=30 mH L2=60 mH M=40 mH')
5  L1=30*10^-3; L2=60*10^-3; M=40*10^-3;

```

```

6 //The equivalent T network is
7 UL=L1-M
8 UR=L2-M
9 CS=M
10 printf("The T network has \n")
11 printf("%d mH in the upper left arm\n",UL*10^3)
12 printf("%3.0f mH in the upper right arm\n",UR*10^3)
13 printf("%d mH in the center stem\n",CS*10^3)

```

Scilab code Exa 13.6 T and PI equivalent networks

```

1 clc
2 //Example 13.6
3 printf(" Given")
4 disp('L1=30 mH L2=60 mH M=40 mH')
5 L1=30*10^-3; L2=60*10^-3; M=40*10^-3;
6 //Let X=L1*L2-M^2
7 X=L1*L2-M^2
8 //The equivalent PI network is
9 LA=X/(L2-M)
10 LB=X/M
11 LC=X/(L1-M)
12 printf("The PI network has \n")
13 printf("LA=%3.0f mH\n",LA*10^3)
14 printf("LB=%3.0f mH \n",LB*10^3)
15 printf("LC=%3.0f mH\n",LC*10^3)

```

This code can be downloaded from the website www.scilab.in

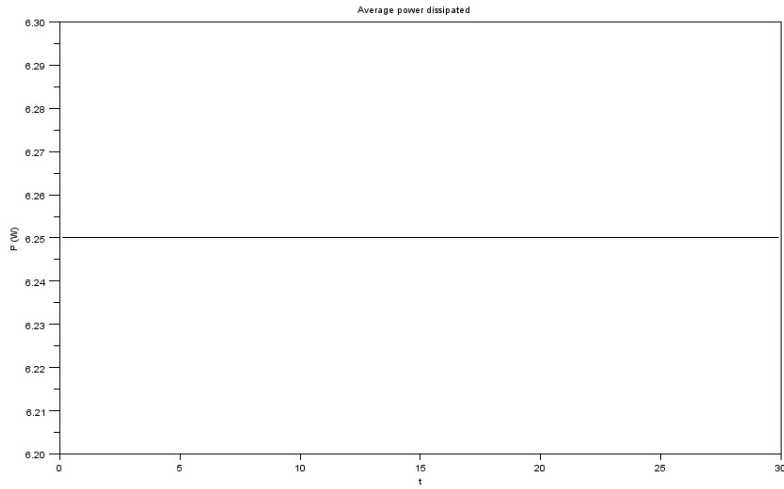


Figure 13.1: The Ideal Transformer

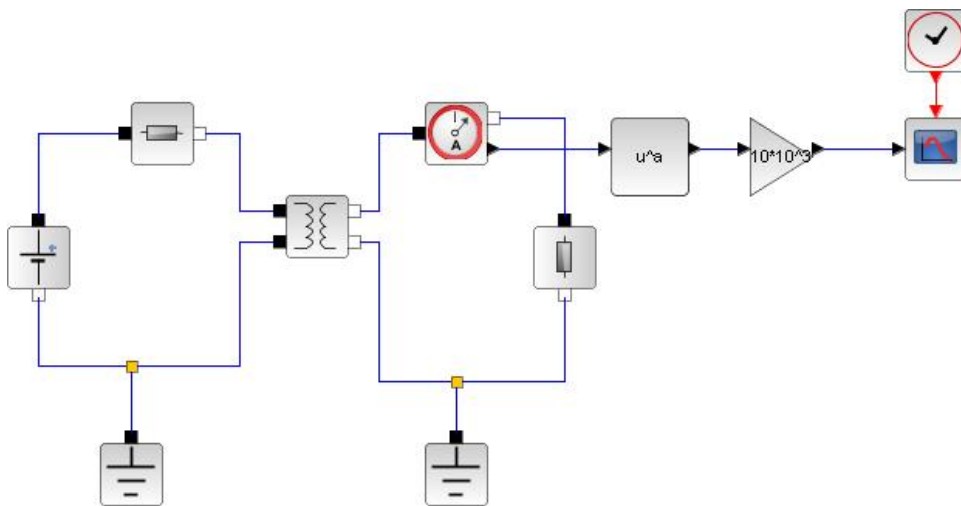


Figure 13.2: The Ideal Transformer

Scilab code Exa 13.8 Equivalent Circuits

```
1  clc
2  //Example 13.8
3  disp('Given ')
4  disp('Vin=50V Zg=100 ohm ')
5  Vin=50;Zg=100;
6  //From figure 13.32
7  disp('When the secondary circuit and ideal
      transformer is replaced by a Thevenin equivalent
      then the primary circuit sees a 100 ohm impedance
      ')
8  //The turns ratio is a
9  a=10;
10 disp('We place the secondary circuit and ideal
      transformer by a Thevenin equivalent circuit ')
11 Vth=-a*Vin
12 Zth=(-a)^2*Zg
13 printf("The secondary circuit has voltage source %d
      V rms with %d kohm resistance in series with it
      along with %d kohm load resistance",Vth,Zth
      *10^-3,10)
```

Chapter 14

Complex frequency and the Laplace Transform

Scilab code Exa 14.2 Definition of the Laplace Transform

```
1 //Example 14.2
2 //Install Symbolic toolbox
3 //Find the Laplace transform
4 syms t s
5 clc
6 z=integ(2*exp(-s*t),t,3,%inf)
7 //The second term will result in zero
8 disp(z, 'F(s)=')
```

Scilab code Exa 14.3 Inverse Transform Techniques

```
1 clc
2 //Example 14.3
3 //Install Symbolic toolbox
4 //Find the Inverse Laplace transform
5 syms s
```

```
6 a=7/s
7 b=31/(s+17)
8 x=ilaplace(a)
9 y=ilaplace(b)
10 g=x-y
11 disp(g, 'g(t)=')
```

Scilab code Exa 14.4 Inverse Transform Techniques

```
1 clc
2 //Example 14.4
3 //Install Symbolic toolbox
4 //Find the Inverse Laplace transform
5 syms s t
6 a=2
7 b=4/s
8 x=ilaplace(b)
9 //Inverse laplace transform of a constant is
10 disp('inverse laplace(2)=2*delta(t)')
11 disp('Answer is ')
12 disp(x+'2*delta(t)')
```

Scilab code Exa 14.5 Inverse Transform Techniques

```
1 clc
2 //Example 14.5
3 //Install Symbolic toolbox
4 //Find the Inverse Laplace transform
5 syms s
6 s=%s;
7 P =(7*s+5)/(s^2+s);
8 Pp=pfss (P)
9 p1=ilaplace (Pp(1))
```

```
10 p2=ilaplace (Pp(2))
11 p=p1+p2
12 disp(p, 'p(t)=');
```

Scilab code Exa 14.6 Inverse Transform Techniques

```
1 clc
2 //Example 14.6
3 //Install Symbolic toolbox
4 //Find the Inverse Laplace transform
5 syms s
6 s=%s;
7 V =2/(s^3+12*s^2+36*s);
8 Vp=pfss (V)
9 v1=ilaplace (Vp(1))
10 v2=ilaplace (Vp(2))
11 v=v1+v2
12 disp(v, 'v(t)=');
```

Scilab code Exa 14.7 Basic Theorems for the Laplace Transform

```
1 clc
2 //Example 14.7
3 //Install Symbolic toolbox
4 //Find the current through 5 ohm resistor
5 syms s
6 s=%s
7 //From figure 14.3
8 //Writing the KVL equation and taking the Laplace
  transform
9 I=1.5/(s*(s+2))+5/(s+2)
10 I1=1.5/(s*(s+2))
11 I2=5/(s+2)
```

```

12 I1p=pfss(I1)
13 i1=ilaplace(I1p(1))
14 i2=ilaplace(I1p(2)+I2)
15 i=i1+i2
16 disp(i, 'i(t)=')

```

Scilab code Exa 14.8 Basic Theorems for the Laplace Transform

```

1 clc
2 //Example 14.8
3 //Install Symbolic toolbox
4 //Find the current for t>0
5 syms s
6 s=%s
7 //From figure 14.5
8 //Writing the KVL equation and taking the Laplace
  transform
9 I=-2/(s+4)
10 i=ilaplace(I)
11 disp(i, 'i(t)=')

```

Scilab code Exa 14.9 Basic Theorems for the Laplace Transform

```

1 clc
2 //Example 14.9
3 //Install Symbolic toolbox
4 //Find the voltage v(t)
5 syms s
6 s=%s
7 //From figure 14.6
8 //Writing the KCL equation and taking the Laplace
  transform
9 V=4/(s*(s+4))+9/(s+4)

```

```

10 V1=4/(s*(s+4))
11 V2=9/(s+4)
12 V1p=pfss(V1)
13 v1=ilaplace(V1p(1))
14 v2=ilaplace(V1p(2)+V2)
15 v=v1+v2
16 disp(v, 'v(t)=')

```

Scilab code Exa 14.10 The time shift theorem

```

1 clc
2 //Example 14.10
3 //Install Symbolic toolbox
4 //Determine the transform of rectangular pulse
5 syms t s
6 v=integ(exp(-s*t),t,2,%inf)-integ(exp(-s*t),t,5,%inf
    )
7 disp(v, 'V(s)=')

```

Scilab code Exa 14.11 The Initial and Final value theorems

```

1 clc
2 //Example 14.11
3 //Install Symbolic toolbox
4 //Calculate f(inf)
5 syms s t ;
6 disp('Given function is f(t)=1-exp(-a*t)')
7 u=laplace(1)
8 v=laplace(exp(-2*t))
9 F=u-v
10 x=s*F
11 //From final value theorem
12 y=limit(x,s,0)

```

13 `disp(y, 'f(inf)=')`

Chapter 15

Circuit Analysis in the s domain

Scilab code Exa 15.1 Modeling Inductors in the s domain

```
1  clc
2  //Example 15.1
3  //Install Symbolic toolbox
4  //Calculate the voltage
5  //From figure 15.3
6  //Writing the KVL equation for the voltage and
   taking the Laplace transform
7  syms s
8  s=%s
9  disp('V=(2*s*(s+9.5)/((s+8)*(s+0.5)))-2')
10 //On solving
11 V=(2*s-8)/((s+8)*(s+0.5))
12 Vp=pfss (V)
13 Vp1=ilaplace(Vp(1))
14 Vp2=ilaplace(Vp(2))
15 v=Vp1+Vp2
16 disp(v, 'v(t)=')
```

Scilab code Exa 15.2 Modeling capacitors in the s domain

```
1  clc
2  //Example 15.2
3  //Install Symbolic toolbox
4  //Calculate the voltage
5  //Selecting the current based model
6  //From figure 15.6(b)
7  //Writing the KCL equation for the voltage and
   taking the Laplace transform
8  syms s
9  s=%s
10 Vc=-2*(s-3)/(s*(s+2/3))
11 Vcp=pfss (Vc)
12 Vcp1=ilaplace(Vcp(1))
13 Vcp2=ilaplace(Vcp(2))
14 vc=Vcp1+Vcp2
15 disp(vc, 'vc=')
```

Scilab code Exa 15.4 Nodal and Mesh analysis in s domain

```
1  clc
2  //Example 15.4
3  //Install Symbolic toolbox
4  //Calculate the voltage
5  //From figure 15.9
6  //Applying nodal equation and solving for vx
7  syms s
8  s=%s
9  Vx=(10*s^2+4)/(s*(2*s^2+4*s+1))
10 Vxp=pfss (Vx)
11 Vxp1= ilaplace (Vxp(1))
```



```
12 Vxp2= ilaplace (Vxp(2))
13 vx=Vxp1+Vxp2
14 disp(vx, 'vx=')
```

Scilab code Exa 15.6 Additional circuit analysis techniques

```
1 clc
2 //Example 15.6
3 //Install Symbolic toolbox
4 //Calculate the voltage
5 //Performing source transformation on the s-domain
  circuit
6 //Solving for V(s)
7 syms s
8 s=%s
9 V=(180*s^4)/((s^2+9)*(90*s^3+18*s^2+40*s+4))
10 Vp=pfss (V)
11 Vp1=ilaplace(Vp(1))
12 Vp2=ilaplace(Vp(2))
13 Vp3=ilaplace(Vp(3))
14 v=Vp1+Vp2+Vp3
15 disp(v, 'v(t)=')
```

Scilab code Exa 15.9 Convolution and Laplace Transform

```
1 clc
2 //Example 15.9
3 //Install Symbolic toolbox
4 //Find the inverse Laplace transform
5 syms s
6 s=%s
7 //Let a=1 and b=3
8 a=1;b=3;
```

```

9 V=1/((s+a)*(s+b))
10 Vp=pfss (V)
11 Vp1=ilaplace(Vp(1))
12 Vp2=ilaplace(Vp(2))
13 v=Vp1+Vp2
14 disp(v, 'v(t)=')

```

Scilab code Exa 15.10 Convolution and Laplace Transform

```

1 clc
2 //Example 15.10
3 //Since the input function is given the Laplace
  transform is found
4 syms s t
5 s=%s
6 vin=6*exp(-t)
7 Vin=laplace(vin)
8 //Connecting the impulse voltage pulse to the
  circuit and converting to s-domain
9 //If vin=delta(t)..the impulse source
10 V0=2/((2/s)+2)
11 //As source voltage is 1V
12 H=V0
13 V=Vin*H
14 Vp=pfss ((6*s)/(s+1)^2)
15 Vp1=ilaplace(Vp(1))
16 v0=Vp1
17 disp(v0, 'v0(t)=')

```

Chapter 16

Frequency Response

Scilab code Exa 16.1 Parallel Resonance

```
1 clc
2 //Example 16.1
3 disp('Given ')
4 disp('L=2.5mH Q0=5 C=0.01uF ')
5 L=2.5*10^-3; Q0=5; C=0.01*10^-6;
6 w0=1/sqrt(L*C)
7 printf("w0= %3.1 f krad/s \n",w0*10^-3);
8 f0=w0/(2*pi)
9 alpha=w0/(2*Q0)
10 printf("alpha= %3.1 f Np/s \n",alpha);
11 wd=sqrt(w0^2-alpha^2)
12 printf("wd= %3.1 f krad/s \n",wd*10^-3);
13 R=Q0/(w0*C)
14 printf("R= %3.2 f ohm \n",R*10^-3);
```

Scilab code Exa 16.2 Bandwidth and high Q circuits

```
1 clc
```

```

2 //Example 16.2
3 disp('Given')
4 disp('R=40Kohm L=1H C=1/64 uF w=8.2krad/s')
5 R=40*10^3; L=1; C=1/64 *10^-6; w=8.2*10^3;
6 //The value of Q0 must be at least 5
7 Q0=5;
8 w0=1/sqrt(L*C)
9 printf("w0= %3.1f krad/s \n",w0*10^-3);
10 f0=w0/(2*pi)
11 B=w0/Q0
12 printf("Bandwidth= %3.1f krad/s \n",B*10^-3);
13 //Number of half bandwidths be N
14 N=2*(w-w0)/B
15 disp(N)
16 //Admittance Y(s)=(1+i*N)/R
17 //Finding the magnitude and angle
18 magY=sqrt(1+N^2)/R
19 angY=atan(N)*(180/pi)
20 disp(angY,'angY=')
21 printf("admittance value=%3.2f uS",magY*10^6)

```

Scilab code Exa 16.3 Series Resonance

```

1 clc
2 //Example 16.3
3 disp('Given')
4 disp('R=10 ohm L=2mH C=200 nF w=48 krad/s vs=100*cos
      (wt) mV')
5 R=10; L=2*10^-3; C=200*10^-9; w=48*10^3;
6 vsamp=100;
7 w0=1/sqrt(L*C)
8 printf("w0= %3.1f krad/s \n",w0*10^-3);
9 Q0=w0*L/R
10 printf("Q0=%d \n",Q0)
11 B=w0/Q0

```

```

12 printf("Bandwidth= %3.1 f krad/s \n",B*10^-3);
13 //Number of half bandwidths be N
14 N=2*(w-w0)/B
15 disp(N)
16 //Impedance Z(s)=(1+i*N)*R
17 //Finding the magnitude and angle
18 magZ=sqrt(1+N^2)*R
19 angZ=atan(N)*(180/%pi)
20 disp(angZ, 'angZ=')
21 printf("Equivalent impedance value=%3.2 f ohm \n",
        magZ)
22 //Approx current magnitude is
23 Iamp=vsamp/magZ
24 printf("\n Approx current magnitude= %3.2 f mA \n",
        Iamp);

```

Scilab code Exa 16.4 Other resonant forms

```

1 clc
2 //Example 16.4
3 disp(' Given ')
4 disp(' R1=2 ohm R2=3 ohm L=1H C=125mF')
5 R1=2;R2=3 ; L=1;C=125*10^-3;
6 w0=sqrt(1/(L*C)-(R1/L)^2)
7 printf("w0=%d rad/s \n",w0)
8 //Input admittance is 1/R2+i*w*C+1/(R+I*w*L)
9 Y=1/3+%i/4+1/(2+%i*2)
10 printf("Y= %3.4 f S \n",Y)
11 //Now input impedance at resonance
12 Z=1/Y
13 printf("Z= %3.4 f ohm \n",Z)
14 //Resonant frequency f=1/sqrt(L*C)
15 f=1/sqrt(L*C)
16 printf(" f=%3.2 f rad/s \n",f);

```

Scilab code Exa 16.5 Equivalent Series and parallel combination

```
1  clc
2  //Example 16.5
3  disp('Given ')
4  disp('R=5 ohm L=100mH w=100 rad/s ')
5  Rs=5; Ls=100*10^-3 ;w=100;
6  //Let Xs be the capacitive and inductive reactance
7  Xs=w*Ls
8  Q=Xs/Rs
9  //As Q is greater than 5 we can approximate as
10 Rp=Q^2*Rs
11 Lp=Ls
12 printf("The parallel equivalent is \n");
13 printf("Rp= %d ohm \t Lp=%d mH" ,Rp ,Lp*10^3);
```

Scilab code Exa 16.6 Scaling

```
1  clc
2  //Example 16.6
3  disp('Given ')
4  disp('Km=20 Kf=50 ')
5  Km=20; Kf=50;
6  s=poly(0, 's')
7  //From figure 16.20(a)
8  C=0.05; L=0.5;
9  //Performing magnitude as well as frequency scaling
   simultaneously
10 Cscaled =C/(Km*Kf)
11 Lscaled = L*Km/Kf
12 printf("Scaled values are \n")
```

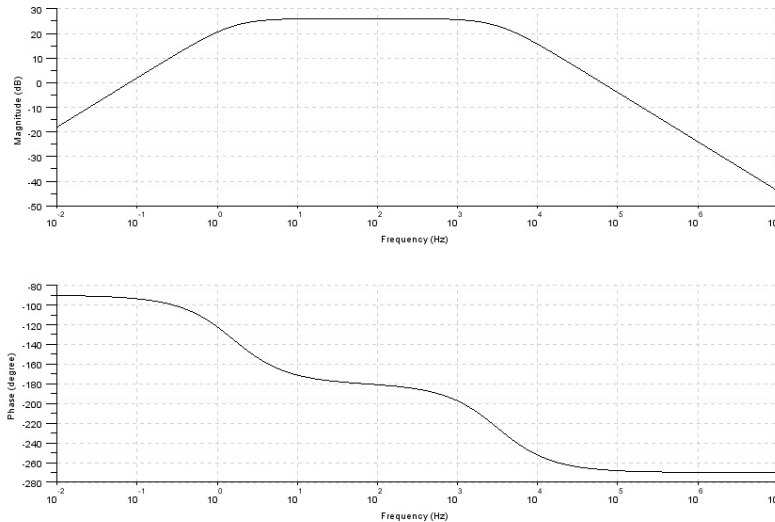


Figure 16.1: Bode diagrams

```

13 printf("Cscaled =%d uF \t Lscaled =%d mH \n",Cscaled
    *10^6,Lscaled*10^3)
14 //Converting the Laplace transform of the circuit
15 //From figure 16.20(c)
16 disp('Vin=V1+0.5s*(1-0.2*V1)')
17 disp('V1=20/s')
18 //On substituting V1 in equation of Vin
19
20 Zin=(s^2-4*s+40)/(2*s)
21 disp(Zin,'Zin=')
22 //Now we need to scale Zin
23 //We will multiply Zin by Km and replace s by s/Kf
24 Zinscaled=horner(Km*Zin,s/Kf)
25 disp(Zinscaled,'Zinscaled')

```

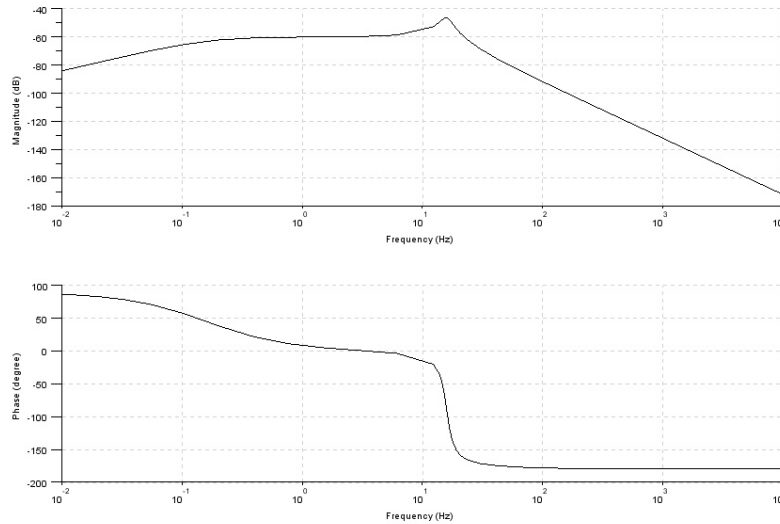


Figure 16.2: Bode diagrams

Scilab code Exa 16.8 Bode diagrams

```

1  clc
2  //Example 16.8
3  //From figure 16.26
4  disp('Writing the expression for voltage gain')
5  disp('Vout/Vin=4000*(-1/200)*(5000*10^8/s)')
6  disp(' /((5000+10^8/s)*(5000+10^6/20s))')
7  //On simplification
8  s=poly(0, 's')
9  h=syslin('c', (-2*s)/((1+s/10)*(1+s/20000)))
10 disp(h)
11 fmin=0.01
12 fmax=10^7
13 scf(1);clf;
14 bode(h, fmin, fmax)

```

Scilab code Exa 16.10 Bode diagrams

```
1  clc
2  //Example 16.10
3  s=poly(0, 's')
4  h=syslin('c', (10*s)/((1+s)*(s^2+20*s+10000)))
5  disp(h)
6  fmin=0.01
7  fmax=10^4
8  scf(1);clf;
9  //Calculate Bode plot
10 bode(h, fmin, fmax)
```

Scilab code Exa 16.11 Filters

```
1  clc
2  //Example 16.11
3  disp('Given')
4  disp('A high pass filter with cutoff frequency of 3k
      Hz')
5  //Cutoff frequency(wc)=1/(R*C)
6  //Let us select some standard value of resistor
7  disp('Let R=4.7k ohm')
8  fc=3*10^3;R=4.7*10^3;
9  wc=2*pi*fc
10 C=1/(R*wc)
11 printf("\n C=%3.2 f nF ",C*10^9);
12 s=poly(0, 's')
13 h=syslin('c', (R*C*s)/((1+s*R*C)))
14 disp(h)
15 HW = frmag(h,512);
16 w=0: %pi /511: %pi ;
```

17 `plot(w,HW)`

Scilab code Exa 16.12 Filters

```
1 clc
2 //Example 16.12
3 disp('Given')
4 disp('Bandwidth = 1M Hz and high frequency cutoff =
   1.1M Hz')
5 B=10^6;fH=1.1*10^6
6 //B=fH-fL
7 fL=fH-B
8 printf("Low frequency cutoff fL= %d kHz \n",fL
   *10^-3);
9 wL=2*pi*fL
10 printf("wL= %3.2 f krad/s \n",wL*10^-3);
11 wH=2*pi*fH
12 printf("wH= %3.3 f Mrad/s \n",wH*10^-6);
13 //Now we need to find values for R,L and C
14 //Let X=1/LC
15 B=2*pi*(fH-fL)
16 X=(wH-B/2)^2-(B^2/4)
17 disp(X)
18 disp('Let L=1H')
19 L=1;
20 C=1/(L*X)
21 disp(C, 'C=')
22 //B=R/L
23 R=L*B
24 printf("R= %3.3 f Mohm \n",R*10^-6);
```

Scilab code Exa 16.13 Filters

```

1  clc
2  //Example 16.13
3  disp('Given')
4  disp('Voltage gain = 40dB and cutoff frequency = 10k
      Hz')
5  Av_dB=40
6  Av=10^(Av_dB/20)
7  f=10*10^3
8  B=2*%pi*f
9  //From figure 16.41(a)
10 disp('1+Rf/R1=100(Gain)')
11 //From figure 16.41(b)
12 //The transfer function is
13 disp('V+= Vi*(1/sC)/(1+1/sC)')
14 //Combining two transfer functions
15 disp('V0 = Vi*(1/sC)/(1+1/sC)*(1+Rf/R1)')
16 //The maximum value of the combined transfer
      function is
17 disp('Maximum value is V0 = Vi*(1+Rf/R1)')
18 disp('Let R1=1k ohm')
19 R1=10^3
20 Rf=(Av-1)*R1
21 printf("Rf= %d kohm \n",Rf*10^-3);
22 disp('C=1 uF')
23 C=10^-6
24 //B=1/(R2*C)
25 R2=1/(C*B)
26 printf("R2= %3.2 f ohm \n",R2);

```

Chapter 17

Two Port Networks

Scilab code Exa 17.1 One port networks

```
1 //Example 17.1
2 clc
3 //From figure 17.3
4 disp('The mesh equations are')
5 disp('V1=10*I1-10*I2')
6 disp('0=-10*I1+17*I2-2*I3-5*I4')
7 disp('0=-2*I2+7*I3-I4')
8 disp('0=-5*I2-I3+26*I4')
9 //We need to find input impedance
10 disp('Zin=delz/del11')
11 //In matrix form
12 A=[10 -10 0 0 ; -10 17 -2 -5; 0 -2 7 -1; 0 -5 -1 26]
13 delz=det(A)
14 printf("\n delz=%f ohm^4",delz);
15 //Eliminating first row and first column to find
    del11
16 B=[17 -2 -5; -2 7 -1; -5 -1 26]
17 del11=det(B)
18 printf("\n del11=%f ohm^3",del11);
19 Zin=delz/del11
20 printf("\n Zin=%f ohm",Zin);
```

Scilab code Exa 17.2 One port networks

```
1 //Example 17.2
2 clc
3 //From figure 17.5
4 disp('The mesh equations are')
5 disp('V1=10*I1-10*I2')
6 disp('0=-10*I1+17*I2-2*I3-5*I4')
7 disp('0=-2*I2+7*I3-I4')
8 disp('0=-0.5*I3+1.5*I4')
9 //We need to find input impedance
10 disp('Zin=delz/del11')
11 //In matrix form
12 A=[10 -10 0 0 ; -10 17 -2 -5; 0 -2 7 -1;0 0 -0.5 1.5]
13 delz=det(A)
14 printf("\n delz=%f ohm^3",delz);
15 //Eliminating first row and first column to find
    del11
16 B=[17 -2 -5;-2 7 -1;0 -0.5 1.5]
17 del11=det(B)
18 printf("\n del11=%f ohm^2",del11);
19 Zin=delz/del11
20 printf("\n Zin=%f ohm",Zin);
```

Scilab code Exa 17.3 One port networks

```
1 //Example 17.3
2 clc
3 //From figure 17.7
4 disp('The nodal equations are')
5 disp('I1=0.35*V1-0.2*V2-0.05*V3')
```

```

6 disp('I2=-0.2*V1+1.7*V2-1*V3')
7 disp('I3=-0.05*V1-1*V2+1.3*I3')
8 //We need to find input impedance
9 disp('Yin=dely/del11')
10 disp('Zin=1/Yin')
11 //In matrix form
12 A=[0.35 -0.2 -0.05;-0.2 1.7 -1;-0.05 -1 1.3]
13 dely=det(A)
14 printf("\n dely=%f S^3",dely);
15 //Eliminating first row and first column to find
    del11
16 B=[1.7 -1;-1 1.3]
17 del11=det(B)
18 printf("\n del11=%f S^2",del11);
19 Yin=dely/del11
20 printf("\n Yin=%f S",Yin);
21 Zin=1/Yin
22 printf("\n Zin=%f ohm",Zin);

```

This code can be downloaded from the website www.scilab.in

Scilab code Exa 17.7 Some equivalent networks

```

1 clc
2 //Example 17.7
3 //From figure 17.16
4 disp('Given a linear model of a transistor we need
    not explicitly find the admittance parameters ')
5 disp('-y12 corresponds to admittance of 2k ohm
    resistor ')

```

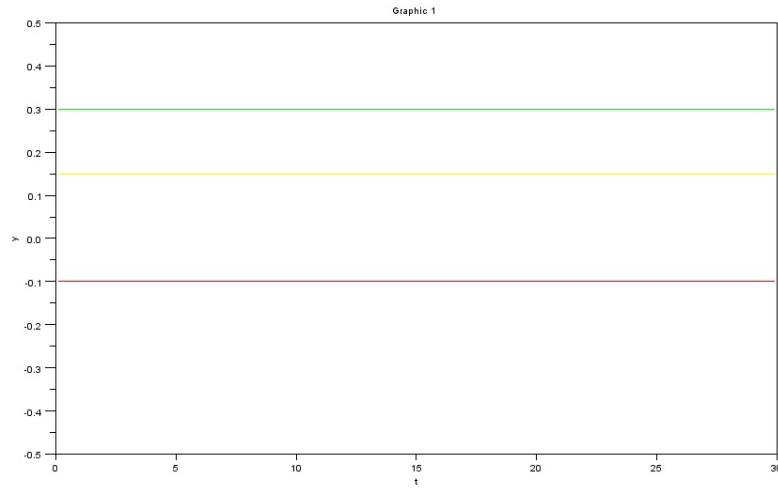


Figure 17.1: Admittance parameters

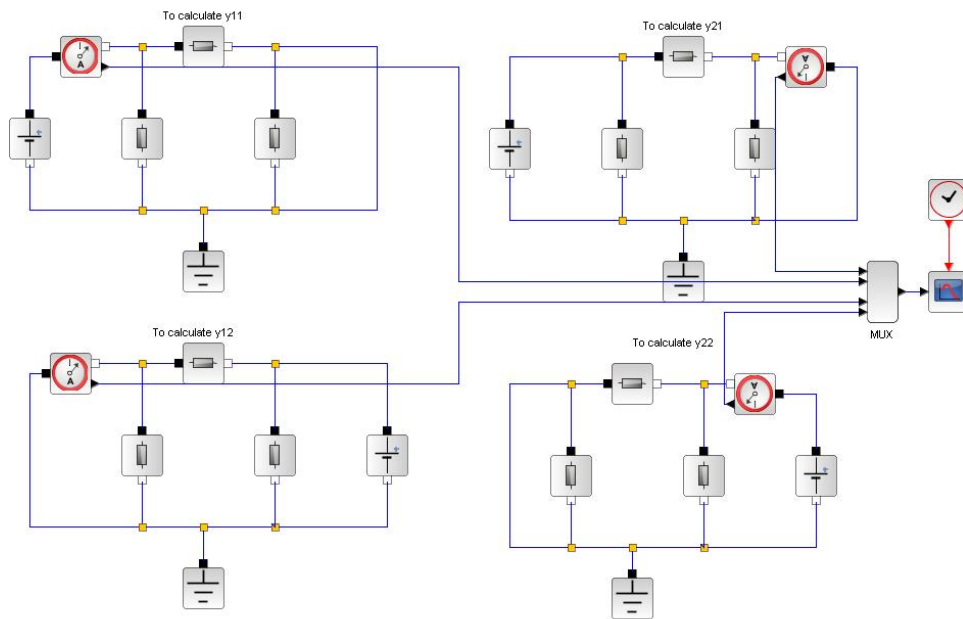


Figure 17.2: Admittance parameters

```

6 disp('y11+y12 corresponds to admittance of 500 ohm
      resistor')
7 disp('y21-y12 correponds to gain of dependent
      voltage source')
8 disp('y22+y12 corresponds to admittance of 10k ohm
      resistor')
9 //Writing down in equation form
10 y12=-1/2000
11 y11=1/500-y12
12 y21=0.0395+y12
13 y22=1/10000-y12
14 printf("\n y11= %3.2 f mS \n y12= %3.2 f mS \n y21= %3
      .2 f mS \n y22= %3.2 f mS",y11*10^3,y12*10^3,y21
      *10^3,y22*10^3);

```

Scilab code Exa 17.8 Impedance parameters

```

1 clc
2 //Example 17.8
3 disp('Given')
4 disp('Z=[10^3 10;-10^6 10^4 ]')
5 z11=10^3 ; z12=10;z21=-10^6;z22=10^4
6 //Using the given matrix we can write the mesh
      equations as
7 disp('V1=10^3*I1+10*I2')
8 disp('V2=-10^6*I1+10^4*I2')
9 //The input to an two port network is an ideal
      sinusoidal voltage source in series with 500 ohm
10 //Mathematically
11 disp('The characterizing equations are')
12 disp('Vs=500*I1+V1')
13 //The output to an two port network is a 10k ohm
      resistor
14 //Mathematically
15 disp('V2=-10^4*I2')

```



```

16 Zg=500;
17 // Expressing V1,V2,I1,I2 in terms of Vs
18 V1=0.75*Vs
19 I1=Vs/2000
20 V2=-250*Vs
21 I2=Vs/40
22 disp('Voltage gain Gv=V2/V1')
23 Gv=V2/V1
24 disp(Gv,'Gv=')
25 disp('Current gain Gi=I2/I1')
26 Gi=I2/I1
27 disp(Gi,'Gi=')
28 disp('Power gain Gp=Real[-0.5*V2*I2*]/Real[0.5*V1*
      I1*]')
29 Gp=(-0.5*V2*I2)/(0.5*V1*I1)
30 disp(Gp,'Gp=')
31 disp('Input impedance is Zin=V1/I1')
32 Zin=V1/I1
33 printf("\n Zin= %d ohm",Zin)
34 disp('Output impedance is Zout=z22-((z12*z21)/(z11+
      Zg))')
35 Zout=z22-((z12*z21)/(z11+Zg))
36 printf("\n Zout= %3.2 f kohm",Zout*10^-3)

```

Scilab code Exa 17.9 Hybrid parameters

```

1 clc
2 //Example 17.9
3 //From figure 17.27
4 //Writing the mesh equations
5 disp('V1=5*I1+4*I2')
6 disp('V2=4*I1+10*I2')
7 //Arranging in the standard form
8 //V1=h11*I1+h12*I2
9 //I2=h21*I1+h22*I2

```

```

10 //Therefore h parameters are
11 h11=3.4;h12=0.4;h21=-0.4;h22=0.1;
12 h=[h11 h12;h21 h22]
13 disp(h)

```

Scilab code Exa 17.10 Transmission parameters

```

1  clc
2  //Example 17.10
3  //From figure 17.32
4  disp('Consider Network A')
5  //Writing the mesh equations
6  disp('V1=12*I1+10*I2 ')
7  disp('V2=10*I1+14*I2 ')
8  //Arranging in the standard form
9  //V1=t11*V2-t12*I2
10 //I1=t21*V2-t22*I2
11 //Therefore t parameters of Network A is
12 t11A=1.2;t12A=6.8;t21A=0.1;t22A=1.4;
13 disp('Consider Network B')
14 //Writing the mesh equations
15 disp('V1=24*I1+20*I2 ')
16 disp('V2=20*I1+28*I2 ')
17 //Arranging in the standard form
18 //V1=t11*V2-t12*I2
19 //I1=t21*V2-t22*I2
20 //Therefore t parameters of Network B is
21 t11B=1.2;t12B=13.6;t21B=0.05;t22B=1.4;
22 tA=[1.2 6.8;0.1 1.4]
23 tB=[1.2 13.6;0.05 1.4]
24 disp('t parameters of cascaded network is t=tA*tB')
25 t=tA*tB
26 disp(t)

```

Chapter 18

Fourier Circuit Analysis

Scilab code Exa 18.1 Trigonometric form of the Fourier Series

```
1 clear
2 close
3 clc
4 //Example 18.1
5 //From the figure 18.2
6 disp('The equation of v(t) considering one period
      can be written as')
7 disp('v(t)=Vm*cos(5*%pi*t) for -0.1<=t<=0.1')
8 disp('v(t)=0 for 0.1<=t<=0.3')
9 //Assuming the value of Vm is 1
10 Vm=1;
11 //Evaluating the constants an and bn
12 //bn=0 for all n
13 //an=(2*Vm*cos(n*%pi/2))/(%pi*(1-n^2))
14 //a0=Vm/%pi
15 t=-1:0.02:1
16 v0t=Vm/%pi
17 v1t=(1/2)*(Vm*cos(5*%pi*t))
18 v0t_v1t=v0t+v1t
```

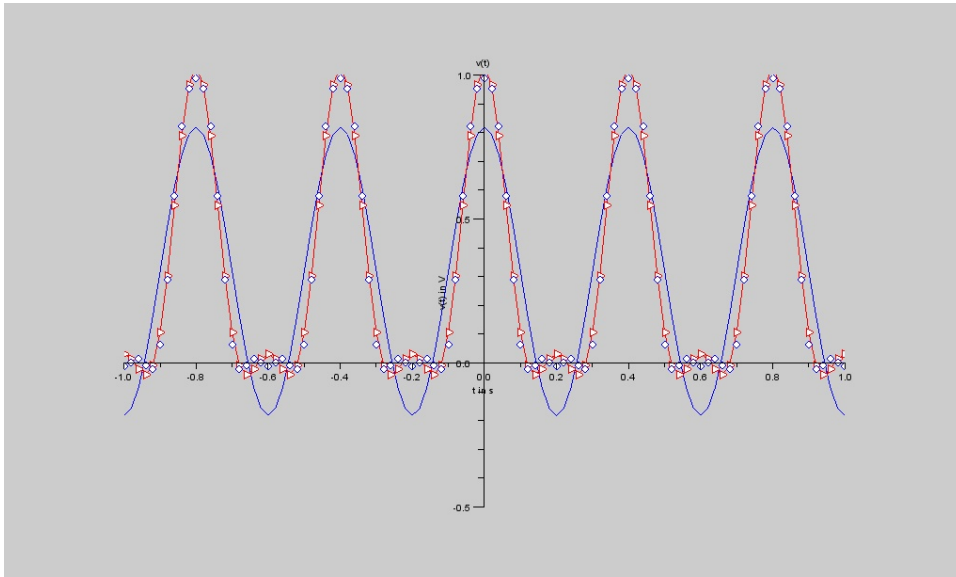


Figure 18.1: Trigonometric form of the Fourier Series

```

19 v2t=(2/(3*pi))*(Vm*cos(10*pi*t))
20 v0t_v1t_v2t=v0t+v1t+v2t
21 v3t=(2/(15*pi))*(Vm*cos(20*pi*t))
22 v0t_v1t_v2t_v3t=v0t+v1t+v2t-v3t
23 figure
24 a = gca ();
25 a. y_location = "origin";
26 a. x_location = "origin";
27 a. data_bounds =[-1,0;1 0.5];
28 plot (t,v0t)
29 xtitle('v0t vs t','t in s','v0t')
30 figure
31 a = gca ();
32 a. y_location = "origin";
33 a. x_location = "origin";
34 a. data_bounds =[-1,-0.5;1 0.5];
35 plot (t,v0t_v1t)
36 a. y_location = "origin";
37 a. x_location = "origin";

```

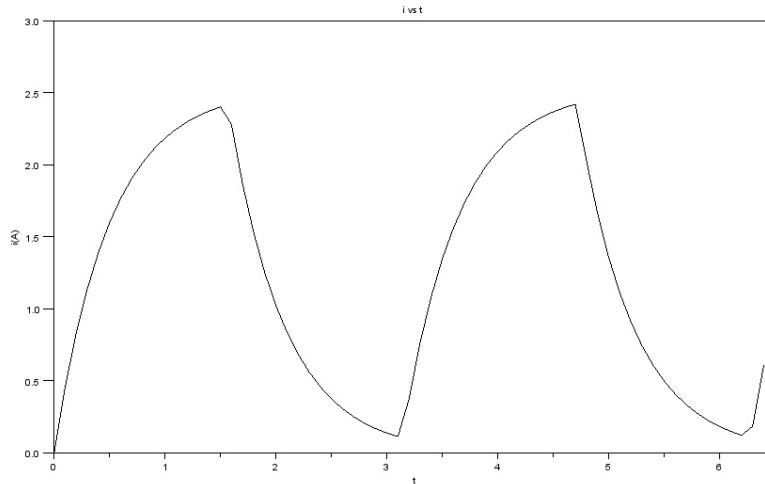


Figure 18.2: Complete Response to periodic Forcing Functions

```

38 a. data_bounds = [ -1, -0.5; 1 0.5];
39 plot (t, v0t_v1t_v2t, 'r.->')
40 a. y_location = "origin";
41 a. x_location = "origin";
42 a. data_bounds = [ -1, -0.5; 1 0.5];
43 plot (t, v0t_v1t_v2t_v3t, 'd')
44 xtitle('v(t)', 't in s', 'v(t) in V')

```

This code can be downloaded from the website www.scilab.in

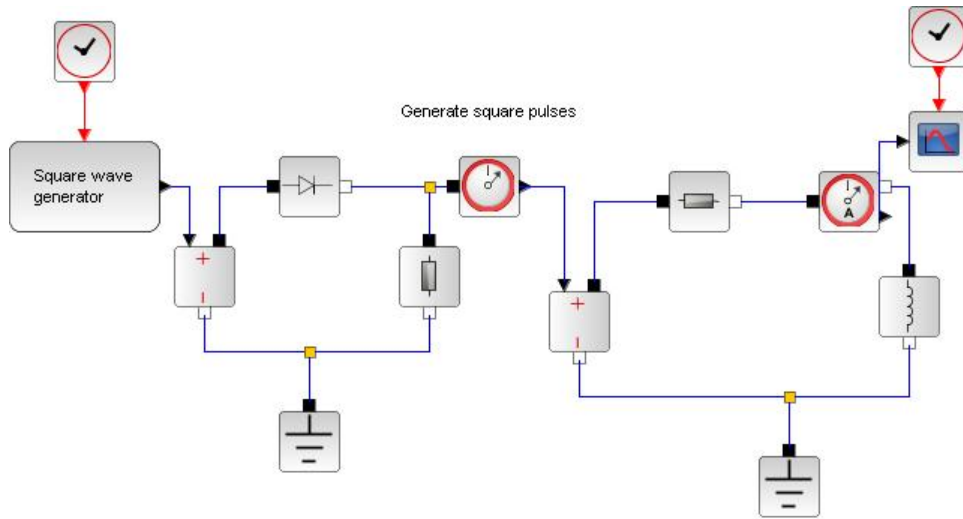


Figure 18.3: Complete Response to periodic Forcing Functions

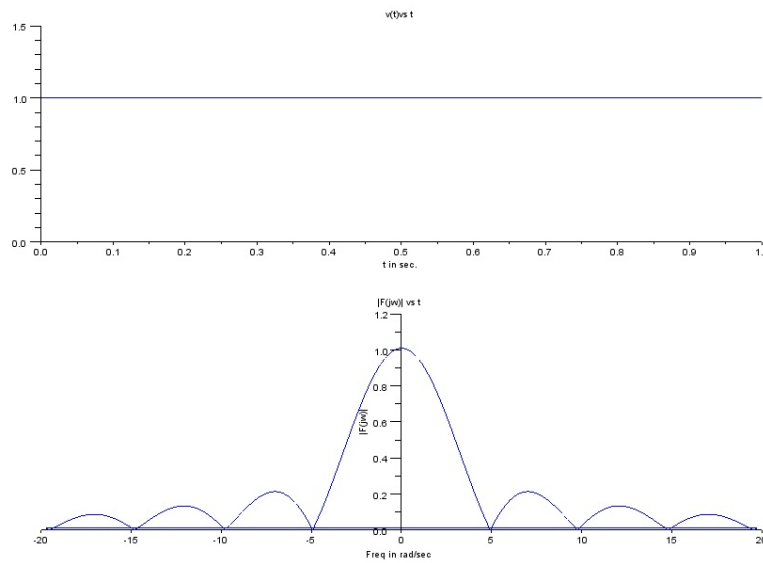


Figure 18.4: Definition of the Fourier Transform

Scilab code Exa 18.5 Definition of the Fourier Transform

```
1  clc ;
2  //Example 18.5
3  //Let amplitude be 1
4  A=1;
5  Dt=0.01;
6  T1=4;
7  t=0:Dt:T1/4;
8  for i=1:length(t)
9      xt(i)=A
10 end
11 //Calculate Fourier Transform
12 Wmax=2*%pi*1;
13 K=4;
14 k=-(2*K):(K/1000):(2*K);
15 W=k*Wmax/K;
16 xt=xt';
17 XW=xt*exp(-sqrt(-1)*t'*W)*Dt;
18 XW_Mag=real(XW);
19 W=[-mtlb_fliplr(W),W(2:1001)];
20 XW_Mag=[mtlb_fliplr(XW_Mag),XW_Mag(2:1001)];
21 subplot(2,1,1);
22 a=gca();
23 a.data_bounds=[0,0;1,1.5];
24 a.y_location="origin";
25 plot(t,xt);
26 xlabel('t in sec. ');
27 title('v(t) vs t');
28 subplot(2,1,2);
29 a=gca();
30 a.y_location="origin";
31 plot(W*%pi/2,abs(XW_Mag));
32 xlabel('Freq in rad/sec ');
33 ylabel('|F(jw)| ');
34 title('|F(jw)| vs t');
```

Scilab code Exa 18.6 Physical significance of Fourier Transform

```
1  clc
2  syms s t
3  printf(" Given")
4  disp('v(t)=4*exp(-3*t)*u(t)')
5  v=4*exp(-3*t)
6
7  F=4*(integ(exp(-(3+%i*1)*s),s,0,%inf))
8  //The second term tends to zero
9  disp(F, 'F=')
10 //Let W be the total 1 ohm energy in the input
    signal
11 W=integ(v^2,t,0,%inf)
12 disp(W, 'W=')
13 //Let Wo be the total energy
14 //As the frequency range is given as 1 Hz<|f|<2 Hz
15 //Considering symmetry
16 Wo=(1/%pi)*integ((16/(9+s^2)),s,2*%pi,4*%pi)
17 disp(Wo, 'Wo=')
```

This code can be downloaded from the website www.scilab.in

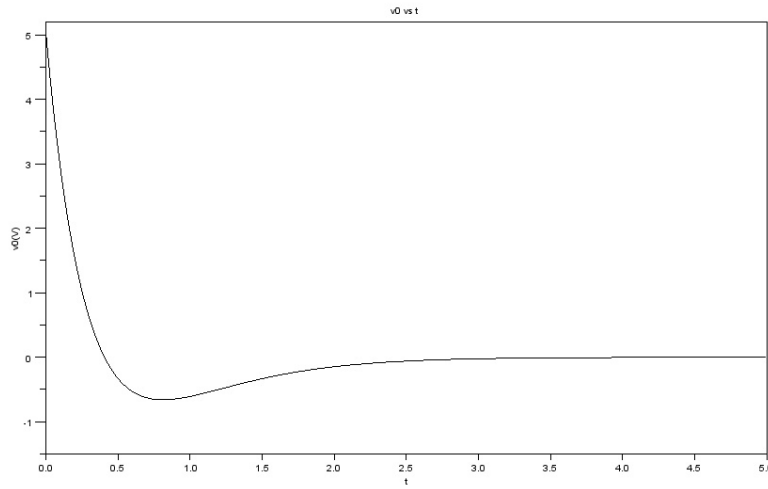


Figure 18.5: The physical significance of system function

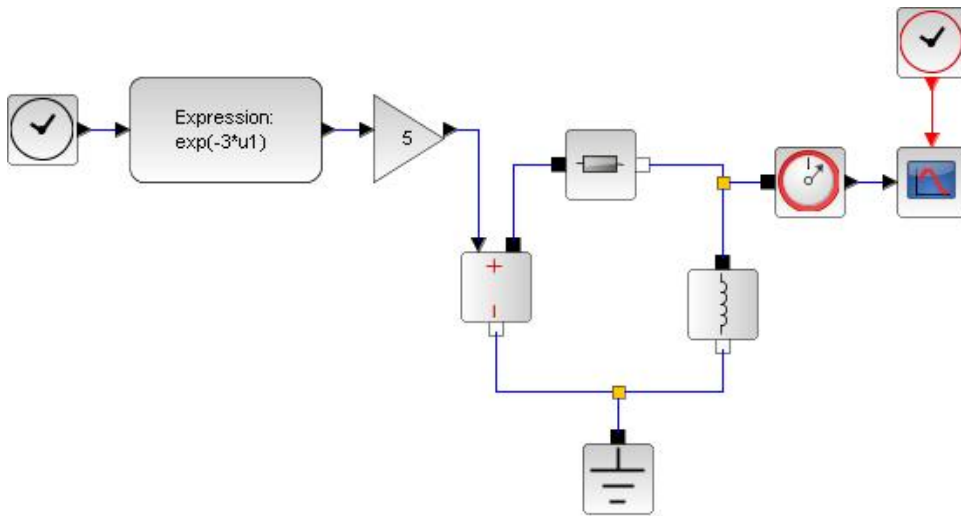


Figure 18.6: The physical significance of system function