

Scilab Textbook Companion for  
Electronic Devices And Circuits  
by D. A. Bell<sup>1</sup>

Created by  
Vaibhav Singh  
B.Tech(pursuing)  
Electronics Engineering  
NIT kurukshetra  
College Teacher  
Karan Sharma  
Cross-Checked by  
Prashant Dave

July 14, 2017

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Electronic Devices And Circuits

**Author:** D. A. Bell

**Publisher:** Oxford University Press

**Edition:** 5

**Year:** 2008

**ISBN:** 0-19-569340

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

|   |            |
|---|------------|
| <b>List of Scilab Codes</b>   | <b>4</b>   |
| <b>1 Basic Semiconductor and pn - Junction Theory</b>               | <b>5</b>   |
| <b>2 Semiconductor Diodes</b>                                       | <b>9</b>   |
| <b>3 Diode applications</b>   | <b>16</b>  |
| <b>4 Bipolar Junction Transistors</b>                               | <b>30</b>  |
| <b>5 BJT biasing</b>  | <b>33</b>  |
| <b>6 AC Analysis of BJT Circuits</b>                                | <b>45</b>  |
| <b>8 BJT specifications and performance</b>                         | <b>53</b>  |
| <b>10 FET biasing</b>   | <b>59</b>  |
| <b>11 AC Analysis of FET circuits</b>                               | <b>66</b>  |
| <b>12 Small signal Amplifiers</b>                                   | <b>70</b>  |
| <b>13 Amplifier with negative feedback</b>                          | <b>85</b>  |
| <b>14 IC operational Amplifier and basic Op amp circuits</b>        | <b>93</b>  |
| <b>15 Operational amplifier frequency Response and compensation</b> | <b>100</b> |
| <b>16 Signal generators</b>   | <b>104</b> |

|   |            |
|---|------------|
| <b>17 Active filters</b>                          | <b>111</b> |
| <b>18 Linear and switching voltage regulators</b> | <b>118</b> |
| <b>19 Power amplifiers</b>                        | <b>127</b> |
| <b>20 Thyristors</b>                              | <b>142</b> |
| <b>21 Optoelectronic Devices</b>                  | <b>147</b> |

# List of Scilab Codes

|          |  |    |
|----------|--|----|
| Exa 1.1  | Charge densities of free electrons and holes . . . . .   | 5  |
| Exa 1.2  | Drift current velocities for electrons and holes . . . . .   | 6  |
| Exa 1.3  | Conductivity and Resistance of a given material . . . . .  | 6  |
| Exa 1.4  | Levels of reverse saturation current at different temperatures . . . . .                                       | 7  |
| Exa 1.5  | Junction Current of silicon pn-junction . . . . .  | 7  |
| Exa 1.6  | Forward bias voltage of a silicon pn - Junction . . . . .  | 8  |
| Exa 1.1  | Forward and reverse resistances of a silicon diode . . . . .   | 9  |
| Exa 2.1  | Dynamic resistance of a diode . . . . .  | 9  |
| Exa 2.3  | Diode current . . . . .  | 10 |
| Exa 2.5  | Forward current of a diode . . . . .   | 10 |
| Exa 2.6  | DC load line for forward biased diode . . . . .  | 11 |
| Exa 2.8  | Calculating supply voltage from given Q - point . . . . .  | 11 |
| Exa 2.9  | Maximum forward current of a diode at a given temperature . . . . .  | 12 |
| Exa 2.10 | Forward voltage drop and junction dynamic resistance of a diode . . . . .                                      | 12 |
| Exa 2.11 | Diffusion capacitance of a Si diode . . . . .  | 13 |
| Exa 2.12 | Minimum fall times for 1N915 and 1N917 diodes . . . . .  | 13 |
| Exa 2.14 | Plotting Diode charecterstics . . . . .  | 14 |
| Exa 2.15 | Maximum current through the Zener diode . . . . .  | 14 |
| Exa 2.16 | Maximum diode current and power dissipation of 1N755   | 15 |
| Exa 2.17 | Upper and Lower limits of Zener voltage( $V_z$ ) . . . . .   | 15 |
| Exa 3.1  | Peak output voltage( $V_{po}$ ), Peak load current( $I_p$ ) and peak reverse voltage( $PIV$ ) of HWR . . . . . | 16 |
| Exa 3.2  | Peak output voltage and current of a Bridge rectifier . . . . .  | 16 |
| Exa 3.3  | Peak to Peak ripple voltage of HWR . . . . .   | 17 |
| Exa 3.4  | Required reservoir capacitance of a HWR . . . . .  | 17 |

|          |  |    |
|----------|--|----|
| Exa 3.5  | Charging and Discharging time of Half -Wave Rectifier(HWR) . . . . .                                   | 18 |
| Exa 3.6  | Surge limiting resistance of HWR . . . . .   | 18 |
| Exa 3.7  | RMS voltage(Vrms), RMS current(Irms) and Transformer primary current for half wave rectifier . . . . . | 19 |
| Exa 3.8  | Required reservoir capacitance value for full- wave rectifier . . . . .                                | 19 |
| Exa 3.9  | Reservoir capacitor value for full - wave rectifier . . . . .  | 20 |
| Exa 3.10 | Surge limiting resistance of bridge rectifier . . . . .  | 20 |
| Exa 3.11 | Transformer selection for a full-wave bridge rectifier . . . . .                                       | 21 |
| Exa 3.12 | DC output voltage and peak to peak voltage of given ripple waveform . . . . .                          | 21 |
| Exa 3.13 | Suitable capacitor and inductor values of LC pi filter . . . . .                                       | 22 |
| Exa 3.14 | Peak output voltage, value of inductor (L1)and capacitor(C1) of L-input filter . . . . .               | 22 |
| Exa 3.15 | Load regulation,Source effect, line regulation of FWR . . . . .  | 23 |
| Exa 3.16 | Parameters of Zener diode as voltage regulator . . . . .   | 23 |
| Exa 3.17 | Maximum load current of Load regulator circuit . . . . .   | 23 |
| Exa 3.18 | Line regulation, load regulation and ripple rejection ratio of Voltage regulator . . . . .             | 24 |
| Exa 3.19 | Load resistance (R1), forward and reverse currents of Voltage regulator circuit . . . . .              | 25 |
| Exa 3.20 | Forward and reverse currents for diode as Negative shunt clipper . . . . .                             | 25 |
| Exa 3.21 | Suitable resistor for biased shunt clipper . . . . .   | 26 |
| Exa 3.22 | Zener diode as shunt clipper . . . . .   | 26 |
| Exa 3.23 | Tilt on the output waveform of a diode clamping circuit . . . . .                                      | 26 |
| Exa 3.24 | Component determination of negative voltage clamping circuit . . . . .                                 | 27 |
| Exa 3.25 | Upper and lower voltages for biased clamping circuits . . . . .  | 27 |
| Exa 3.26 | Capacitor (C1, C2) values for voltage doubling circuit . . . . .                                       | 28 |
| Exa 3.27 | Diode forward current for AND logic circuit . . . . .  | 28 |
| Exa 4.1  | Determine the emitter (Ie) and base (Ib) currents of a transistor . . . . .                            | 30 |
| Exa 4.2  | Common base current gain (Adc), Common-emitter current gain (Bdc) of npn transistor . . . . .          | 30 |
| Exa 4.3  | DC collector voltage and circuit voltage gain of CE amplifier . . . . .                                | 31 |

|          |  |    |
|----------|--|----|
| Exa 4.4  | Collector current ( $I_c$ ), Base current ( $I_b$ ) and hFE of BJT as switch . . . . .       | 31 |
| Exa 4.6  | Base current ( $I_b$ ) and collector current ( $I_c$ ) from output characteristics . . . . . | 32 |
| Exa 5.1  | DC load line . . . . .   | 33 |
| Exa 5.2  | DC Bias point (Q-Point) . . . . .  | 33 |
| Exa 5.3  | DC analysis of common-base amplifier . . . . .   | 34 |
| Exa 5.4  | Maximum and Minimum levels of $I_c$ and $V_{ce}$ for base bias circuit . . . . .             | 34 |
| Exa 5.5  | DC analysis of collector-base bias circuit . . . . .   | 35 |
| Exa 5.7  | DC analysis of voltage -divider bias circuit . . . . .                                       | 35 |
| Exa 5.8  | Precise circuit analysis of voltage-divider bias circuit . . . . .                           | 36 |
| Exa 5.9  | Accurate analysis of voltage-divider bias circuit for minimum hFE of 50 . . . . .            | 36 |
| Exa 5.10 | Analyze voltage divider bias circuit for a maximum hFE of 200 . . . . .                      | 37 |
| Exa 5.11 | Base bias circuit design . . . . .   | 37 |
| Exa 5.12 | Collector to base bias circuit design . . . . .  | 38 |
| Exa 5.13 | Voltage divider bias circuit design . . . . .  | 38 |
| Exa 5.14 | Design voltage divider bias circuit with given bias parameters . . . . .                     | 39 |
| Exa 5.15 | Design voltage divider bias circuit to operate from 18V supply . . . . .                     | 39 |
| Exa 5.16 | Design voltage divider bias circuit to operate from 9V supply . . . . .                      | 40 |
| Exa 5.17 | Stability factors for three bias circuit . . . . .   | 41 |
| Exa 5.18 | Change in collector current ( $I_c$ ) when temperature increases . . . . .                   | 41 |
| Exa 5.19 | Effect of base-emitter voltage ( $V_{be}$ ) changes on collector current ( $I_c$ ) . . . . . | 42 |
| Exa 5.20 | DC analysis of BJT biased as switching circuit . . . . .                                     | 42 |
| Exa 5.21 | Minimum hFE of a transistor biased in saturation region . . . . .                            | 43 |
| Exa 5.22 | Suitable resistances for capacitor coupled switching circuit . . . . .                       | 43 |
| Exa 5.23 | Base and collector resistors for capacitor coupled switching . . . . .                       | 44 |
| Exa 6.1  | DC analysis of voltage divider circuit . . . . .   | 45 |
| Exa 6.2  | DC and AC load line for transistor circuit . . . . .   | 45 |

|           |   |    |
|-----------|---|----|
| Exa 6.3   | h-parameters of CE transistors . . . . .  | 46 |
| Exa 6.4   | CE h-parameters . . . . .   | 47 |
| Exa 6.5   | Estimate the CE input resistance and determine the h-parameters . . . . .           | 47 |
| Exa 6.6   | Input and Output impedances and voltage gain of CE circuit . . . . .                | 48 |
| Exa 6.7   | Calculate $r_e$ and voltage gain of CE circuit . . . . .                            | 48 |
| Exa 6.8   | Input and output impedance and voltage gain of CE circuit . . . . .                 | 49 |
| Exa 6.9   | h-parameter of CC circuit with and without load resistor ( $R_L$ ) . . . . .        | 49 |
| Exa 6.10  | Input and output impedance and voltage gain of transistor in CB circuit . . . . .   | 50 |
| Exa 6.11  | Input impedance and voltage gain of CB circuit without coupling capacitor . . . . . | 50 |
| Exa 6.12  | Output voltage ( $V_o$ ) for CE, CB transistor circuits . . . . .                   | 51 |
| Exa 6.13  | DC analysis of Eber-Moll's BJT model . . . . .                                      | 52 |
| Exa 8.2   | Output power change of an amplifier in dB . . . . .                                 | 53 |
| Exa 8.3   | Output power change of voltage amplifier in dB . . . . .                            | 53 |
| Exa 8.4   | Miller capacitance of CE amplifier . . . . .  | 54 |
| Exa 8.5   | Input capacitance effect on CE and CB circuits . . . . .                            | 54 |
| Exa 8.6   | Input capacitance effects on Emitter follower circuit . . . . .                     | 55 |
| Exa 8.8   | Transistor switching times . . . . .  | 55 |
| Exa 8.9   | Noise output voltage for an amplifier . . . . .                                     | 56 |
| Exa 8.10  | Noise and output voltage of transistor circuit . . . . .                            | 56 |
| Exa 8.11  | Transistor Power dissipation . . . . .  | 57 |
| Exa 8.13  | Maximum power dissipation of 2N3055 . . . . .                                       | 57 |
| Exa 8.14  | Thermal resistance for heat sink . . . . .  | 58 |
| Exa 10.1  | DC load line using FET characteristics . . . . .                                    | 59 |
| Exa 10.4  | DC circuit analysis . . . . .   | 59 |
| Exa 10.6  | DC Analysis of Voltage Divider Bias FET circuit . . . . .                           | 60 |
| Exa 10.7  | Transfer characteristics of gate bias circuit . . . . .                             | 60 |
| Exa 10.8  | Designing a self bias circuit . . . . .   | 61 |
| Exa 10.9  | Designing a voltage divider bias circuit . . . . .                                  | 61 |
| Exa 10.11 | Designing a constant current bias circuit . . . . .                                 | 62 |
| Exa 10.12 | Transfer characteristics of JFET . . . . .  | 62 |
| Exa 10.13 | FET universal transfer characteristics . . . . .                                    | 63 |
| Exa 10.14 | Transfer characteristics of MOSFET . . . . .  | 64 |

|           |  |    |
|-----------|--|----|
| Exa 10.16 | Biasing JFET switching circuit . . . . .   | 64 |
| Exa 10.17 | Transfer characteristics of MOSFET in switching bias . . . . .                       | 64 |
| Exa 11.2  | CS circuit performance parameters . . . . .  | 66 |
| Exa 11.3  | Performance parameters of CS circuit with Unbypassed source resistor . . . . .       | 66 |
| Exa 11.4  | Common Drain circuit analysis . . . . .  | 67 |
| Exa 11.5  | Common Gate circuit analysis . . . . .   | 67 |
| Exa 11.6  | AC output voltage with and without bypassed source resistor . . . . .                | 68 |
| Exa 11.7  | Input capacitance limited cutoff frequency for a CS circuit . . . . .                | 69 |
| Exa 12.1  | Required capacitance and voltage gain at different frequencies . . . . .             | 70 |
| Exa 12.2  | Suitable resistor values for common emitter amplifier . . . . .                      | 70 |
| Exa 12.3  | Suitable capacitor for CE amplifier circuit . . . . .                                | 71 |
| Exa 12.4  | Suitable resistor for common source circuit . . . . .                                | 72 |
| Exa 12.5  | Suitable resistor for common source amplifier . . . . .                              | 72 |
| Exa 12.7  | Analysis of two stage amplifier . . . . .  | 72 |
| Exa 12.8  | Analysis of direct coupled two stage amplifier . . . . .                             | 73 |
| Exa 12.9  | capacitor for two stage direct coupled amplifier . . . . .                           | 74 |
| Exa 12.10 | Minimum overall voltage gain for direct coupled CE amplifier . . . . .               | 74 |
| Exa 12.11 | CE input and CC output two stage amplifier analysis . . . . .                        | 75 |
| Exa 12.12 | Suitable capacitor for circuit . . . . .   | 76 |
| Exa 12.13 | analyze two stage amplifier and determine minimum voltage gain . . . . .             | 76 |
| Exa 12.14 | Dc feedback pair with an emitter follower output . . . . .                           | 77 |
| Exa 12.15 | suitable resistor for BIBET amplifier . . . . .                                      | 78 |
| Exa 12.16 | suitable capacitor For BIFET direct coupled amplifier . . . . .                      | 79 |
| Exa 12.17 | determine minimum overall voltage gain . . . . .                                     | 79 |
| Exa 12.18 | suitable resistor for differential amplifier . . . . .                               | 80 |
| Exa 12.19 | suitable capacitor value for amplifier and voltage gain . . . . .                    | 80 |
| Exa 12.20 | suitable resistor for cascode amplifier . . . . .                                    | 81 |
| Exa 12.21 | suitable capacitor for cascode circuit . . . . .                                     | 81 |
| Exa 12.22 | resonance frequency, voltage gain, bandwidth of amplifier . . . . .                  | 82 |
| Exa 12.23 | Determination of resonance frequency, voltage gain, bandwidth of amplifier . . . . . | 83 |

|           |  |     |
|-----------|--|-----|
| Exa 12.24 | capacitor required to resonate the secondary and overall voltage gain . . . . .      | 83  |
| Exa 13.1  | closed loop gain for negative feedback amplifier . . . . .                           | 85  |
| Exa 13.2  | input impedance with negative feedback . . . . .                                     | 85  |
| Exa 13.3  | input and output impedance when negative feedback . .                                | 86  |
| Exa 13.4  | circuit input and output impedance and voltage gain without feedback . . . . .       | 86  |
| Exa 13.5  | two stage coupled BJT use as voltage feedback . . . .                                | 87  |
| Exa 13.6  | modify direct coupled amplifier to use as series voltage negative feedback . . . . . | 87  |
| Exa 13.7  | calculate resistor value . . . . .   | 88  |
| Exa 13.8  | calculate Acm, Zin and Zout . . . . .  | 88  |
| Exa 13.9  | calculate output impedance for circuit modification . .                              | 89  |
| Exa 13.10 | calculate precise value of circuit voltage gain . . . . .                            | 89  |
| Exa 13.11 | modify CE amplifier to use emitter current feedback to give Av 70 . . . . .          | 90  |
| Exa 13.12 | suitable emitter resistor value . . . . .  | 90  |
| Exa 13.13 | suitable capacitor for two stage circuit . . . . .                                   | 91  |
| Exa 13.14 | determine current gain and input impedance . . . . .                                 | 91  |
| Exa 13.15 | calculate total harmonic . . . . .   | 92  |
| Exa 14.1  | calculate maximum resistance . . . . .   | 93  |
| Exa 14.2  | suitable resistor for BIFET op amp is used . . . . .                                 | 93  |
| Exa 14.3  | typical difference between input and out voltage and Zin and Zout . . . . .          | 94  |
| Exa 14.4  | capacitor coupled voltage follower usin 741 op amp . .                               | 94  |
| Exa 14.5  | direct coupled non inverting amplifier . . . . .                                     | 95  |
| Exa 14.6  | typical input and output impedances for non inverting                                | 95  |
| Exa 14.7  | voltage gain and lower cutoff frequency . . . . .                                    | 96  |
| Exa 14.8  | direct coupled inverting amplifier . . . . .   | 96  |
| Exa 14.9  | design three input summing amplifier . . . . .                                       | 96  |
| Exa 14.10 | suitable resistor for 741 op amp . . . . .   | 97  |
| Exa 14.11 | overall voltage gain for instrumentation amplifier . .                               | 97  |
| Exa 14.12 | typical output voltage swingand calculate rise time . .                              | 98  |
| Exa 14.13 | calculate resistor for schmitt trigger circuit . . . . .                             | 99  |
| Exa 14.14 | upper and lower trigger for non inverting schmitt trigger                            | 99  |
| Exa 15.2  | determine suitable component . . . . .   | 100 |
| Exa 15.3  | miller effect capacitor . . . . .  | 100 |
| Exa 15.5  | cutoff frequencies using gain bandwidth . . . . .                                    | 101 |

|           |   |     |
|-----------|---|-----|
| Exa 15.6  | full power bandwidth for AD843 op amp circuit . . . . .             | 101 |
| Exa 15.7  | input terminal stray capacitor . . . . .                            | 102 |
| Exa 15.8  | load capacitance . . . . .  | 102 |
| Exa 16.1  | phase shift oscillator . . . . .                                    | 104 |
| Exa 16.2  | colpitts oscillator . . . . .                                       | 104 |
| Exa 16.3  | hartley oscillator . . . . .  | 105 |
| Exa 16.4  | wein bridge oscillator . . . . .                                    | 106 |
| Exa 16.5  | design a phase shift oscillator . . . . .                           | 107 |
| Exa 16.6  | amplitude stabilization circuit . . . . .                           | 107 |
| Exa 16.7  | square wave generator . . . . .                                     | 108 |
| Exa 16.8  | calculate t1 t2 and pulse frequency . . . . .                       | 108 |
| Exa 16.10 | triangular wave generator . . . . .                                 | 109 |
| Exa 16.11 | design a wein bridge oscillator . . . . .                           | 109 |
| Exa 16.12 | pierce oscillator and peak power dissipated . . . . .               | 110 |
| Exa 17.1  | calculate attenuation . . . . .                                     | 111 |
| Exa 17.2  | first order active low pass filter . . . . .                        | 111 |
| Exa 17.3  | first order high pass filter and filter bandwidth . . . . .         | 112 |
| Exa 17.4  | butterworth second order low pass filter . . . . .                  | 112 |
| Exa 17.5  | using BIFET op amp design butterworth second order filter . . . . . | 113 |
| Exa 17.6  | third order low pass filter . . . . .                               | 113 |
| Exa 17.7  | third order high pass filter . . . . .                              | 114 |
| Exa 17.8  | single stage band pass filter . . . . .                             | 115 |
| Exa 17.9  | calculate Q factor for wide band filter . . . . .                   | 115 |
| Exa 17.10 | center frequency and bandwidth . . . . .                            | 116 |
| Exa 17.12 | state variable band pass filter . . . . .                           | 116 |
| Exa 17.13 | required resistance to operate one half of an MF10 . . . . .        | 117 |
| Exa 18.1  | load and source effects and load and line regulation . . . . .      | 118 |
| Exa 18.2  | voltage regulator circuit . . . . .                                 | 119 |
| Exa 18.3  | modify voltage regulator . . . . .                                  | 119 |
| Exa 18.4  | voltage regulator to change the load current . . . . .              | 120 |
| Exa 18.5  | suitable component for preregulator circuit . . . . .               | 120 |
| Exa 18.6  | differential amplifier . . . . .                                    | 121 |
| Exa 18.7  | fold back current limiting circuit for voltage regulator . . . . .  | 122 |
| Exa 18.8  | adjustable voltage regulator circuit . . . . .                      | 122 |
| Exa 18.9  | input voltage and maximum load current . . . . .                    | 123 |
| Exa 18.10 | calculate regulator power dissipation . . . . .                     | 124 |
| Exa 18.11 | efficiencies of linear regulator and switching regulator . . . . .  | 124 |

|           |   |     |
|-----------|---|-----|
| Exa 18.12 | step down switching regulator . . . . .   | 125 |
| Exa 18.13 | determine suitable value for R1 R2 Rsc and Ct . . . . .                                 | 125 |
| Exa 19.1  | Dc and Ac load line transistor common emitter characteristics . . . . .                 | 127 |
| Exa 19.2  | maximum efficiency of class A amplifier . . . . .                                       | 127 |
| Exa 19.4  | power deliver to load in class AB amplifier . . . . .                                   | 128 |
| Exa 19.5  | output transformer and transistor of class B circuit . .                                | 129 |
| Exa 19.6  | determine required supply voltage for class AB amplifier                                | 129 |
| Exa 19.7  | output transistors . . . . .  | 130 |
| Exa 19.8  | capacitor value for Ce and Co . . . . .   | 130 |
| Exa 19.9  | determine the value of Vcc Rc and Rb for class AB amplifier . . . . .                   | 131 |
| Exa 19.10 | design Vbe multiplier . . . . .   | 131 |
| Exa 19.11 | required supply voltage and specify output transistors                                  | 132 |
| Exa 19.12 | suitable resistor for output and intermediate stage . .                                 | 133 |
| Exa 19.13 | calculate required supply voltage and suitable DC voltage drop . . . . .                | 133 |
| Exa 19.14 | determine resistor value for MOSFET amplifier . . . . .                                 | 134 |
| Exa 19.15 | bootstrap capacitor terminal voltage and peak output voltage . . . . .                  | 135 |
| Exa 19.16 | use BIFET to determine supply voltage and resistor value                                | 135 |
| Exa 19.17 | capacitor value . . . . .   | 136 |
| Exa 19.18 | MOSFET gate source voltage for complementry common source amplifier . . . . .           | 136 |
| Exa 19.19 | calculate Vgsmmax and Vgsmmin . . . . .   | 137 |
| Exa 19.20 | maximum peak output voltage minimum supply voltage at op amp terminal . . . . .         | 137 |
| Exa 19.21 | op amp minimum supply voltage and MOSFET maximum gate source voltage . . . . .          | 138 |
| Exa 19.22 | determine Po Acl f1 and f2 . . . . .  | 138 |
| Exa 19.23 | maximum output power voltage gain and low cutoff frequency . . . . .                    | 139 |
| Exa 19.24 | determine the load power dissipation . . . . .  | 139 |
| Exa 19.25 | calculate ac output power dc input power conduction angle and efficiency . . . . .      | 140 |
| Exa 19.26 | for class C amplifier determine tank circuit component value and peak current . . . . . | 140 |

|           |  |     |
|-----------|--|-----|
| Exa 19.27 | for class C amplifier determine Ql Qp and Pl and band-width and efficiency . . . . . | 141 |
| Exa 20.1  | calculate instantaneous supply voltage . . . . .                                     | 142 |
| Exa 20.2  | determine suitable resistance . . . . .  | 142 |
| Exa 20.3  | determine SCR anode cathode voltage . . . . .  | 143 |
| Exa 20.4  | specify the SCR and suitable components for D1 and R1                                | 144 |
| Exa 20.5  | smallest conduction angle . . . . .  | 144 |
| Exa 20.6  | determine capacitor charging time . . . . .  | 145 |
| Exa 20.7  | calculate maximum Vb1b2 be used at temperature 100C                                  | 145 |
| Exa 20.8  | maximum and minimum triggering voltage . . . . .                                     | 146 |
| Exa 20.9  | calculate Re for relaxation oscillator and oscillating frequency . . . . .           | 146 |
| Exa 21.1  | total luminous flux . . . . .  | 147 |
| Exa 21.3  | suitable resistor . . . . .  | 147 |
| Exa 21.4  | total power supplied to digit LED . . . . .  | 148 |
| Exa 21.5  | required series resistance and dark current . . . . .                                | 148 |
| Exa 21.6  | minimum light level when transistor is turn off . . . . .                            | 149 |

# Chapter 1

## Basic Semiconductor and pn - Junction Theory

Scilab code Exa 1.1 Charge densities of free electrons and holes

```
1 //chapter 1
2 //example 1.1
3 //page 15
4 printf("\n")
5 printf("given")
6 Nd=3*10^14;Na=.5*10^14; // all in atom/cm^3
7 ni=1.5*10^10;
8 disp("resultant densities of free electrons and hole
      ")
9 ne=(-(Na-Nd)+sqrt(((Na-Nd)^2)+4*ni^2))/2;
10 disp(ne)//electron densities in electron/cm^3
11 Nd>Na;
12 n=Nd-Na;
13 disp(n)
14 p=(ni^2)/n
15 printf("densities of hole is %dhole/cm3\n",p)
```

---

### Scilab code Exa 1.2 Drift current velocities for electrons and holes

```
1 //chapter 1
2 //example 1.2
3 //page 18
4 printf("\n")
5 printf(" given")
6 l=1*10^-3;E=10;
7 un=1500*10^-4;up=500*10^-4;
8 Vn=-(un*E)/l;
9 printf(" drift current is %dm/s\n",Vn)
10 disp(" drift current of hole")
11 Vp=(up*E)/l;
12 printf(" drift current is %dm/s\n",Vp)
```

---

### Scilab code Exa 1.3 Conductivity and Resistance of a given material

```
1 //chapter 1
2 //example 1.3
3 //page 19
4 printf("\n")
5 printf(" given")
6 l=1*10^-3;a=.1*10^-4;
7 ni=1.5*10^10;p=1.5*10^10;
8 disp("a")
9 un=1500;up=500; //in cm3/V.s
10 q=1.6*10^-19;
11 m=q*((ni*un)+(p*up))*10^6;
12 printf(" mobility is %3.2fmicro/ohmcm\n",m)
13 R=l/(m*a);
14 printf(" resistance is %3.2fMohm\n",R)
15 disp("b")
16 //for doped material
17 n=8*10^13;
18 p=(ni^2)/n
```

```
19 m=q*((n*un)+(p*up));
20 printf(" mobility is %3.4f/ohmcm\n",m)
21 R=1/(m*a);
22 printf(" resistance is %dohm\n",R)
```

---

### Scilab code Exa 1.4 Levels of reverse saturation current at different temperatures

```
1 //chapter 1
2 // eaxample 1.4
3 //page 26
4 printf("\n")
5 printf(" given")
6 T1=25;T2=35;T3=45;
7 I0=30//nA
8 disp("I0(35)=I0*2^(T2-T1)/10")
9 //on solving
10 I0(35)=I0*2^((T2-T1)/10);
11 printf(" current at 35c is %dnA\n",I0(35))
12 disp("I0(45)=I0*2^(T3-T1)/10")
13 //on solving
14 I0(45)=30*2^2;
15 printf(" current at 45c is %dnA\n",I0(45))
```

---

### Scilab code Exa 1.5 Junction Current of silicon pn-junction

```
1 //chapter 1
2 //example 1.5
3 //page 28
4 printf("\n")
5 printf(" given")
6 I0=30;Vd=.7;n=2;Vt=26*10^-3;
7 k=Vd/(n*Vt);
8 disp(" junction current")
```

```

9 Id=I0*((2.7^k)-1)*10^-6
10 printf(" forward bias current is %dmA\n",Id)
11 disp("b")
12 Vd=-10 // reverse bias
13 k=Vd/(n*Vt);
14 Id=I0*((2.7^k)-1)
15 printf(" forward bias current is %dnA\n",Id)

```

---

### Scilab code Exa 1.6 Forward bias voltage of a silicon pn - Junction

```

1 //chapter 1
2 //example 1.6
3 //page 29
4 printf("\n")
5 printf("given")
6
7 Id=.1*10^-3;n=2;
8 Vt=26*10^-3;
9 I0=30*10^-9;
10 disp("a")
11 Vd=(n*Vt)*log(Id/I0)*10^3;
12 printf(" forward bias current is %dmV\n",Vd)
13 disp("b")
14 Id=10*10^-3
15 Vd=(n*Vt)*log(Id/I0)*10^3;
16 printf(" forward bias current is %dmV\n",Vd)

```

---

# Chapter 2

## Semiconductor Diodes

Scilab code Exa 1.1 Forward and reverse resistances of a silicon diode

```
1 //chapter 2
2 //example 2.1
3 //page 37
4 printf("\n")
5 printf("given")
6 disp("a")
7 If=100*10^-3;Vf=.75; //given
8 disp("forward resistance")
9 Rf=Vf/If;
10 printf("forward resistnace is %3.1fohm\n",Rf)
11 disp("b")
12 Vr=50;Ir=100*10^-9;
13 Rr=(Vr/Ir);
14 printf("reverse resistnace is %3.0fohm\n",Rr)
```

---

Scilab code Exa 2.1 Dynamic resistance of a diode

```
1 //chapter 2
```

```
2 //example 2.2
3 //page 39
4 printf("\n")
5 printf(" given")
6 If=70*10^-3;
7 rd=(26*10^-3)/If;
8 printf(" dynamic resistance is %3.2f ohm\n",rd)
9 disp("a")
10 If=60*10^-3;Vf=.025;
11 rd=Vf/If;
12 printf(" dynamic resistance is %3.2f ohm\n",rd)
```

---

### Scilab code Exa 2.3 Diode current

```
1 //chapter 2
2 //example 2.3
3 //page 40
4 printf("\n")
5 printf(" given")
6 R1=4.7*10^3;E=15;Vf=.7;
7 disp(" diode current is E=If *R1+Vf")
8 If=((E-Vf)/R1)*10^3;
9 printf(" diode current is %3.2fmA\n",If)
```

---

### Scilab code Exa 2.5 Forward current of a diode

```
1 //chapter 2
2 //example 2.5
3 //page 41
4 printf("\n")
5 printf(" given")
6 E=1.5;Vf=.7;R1=10;rd=.25;
7 disp("a")
```

```
8 If=(E-Vf)/R1;
9 printf(" forward current is %3.3fmA\n",If)
10 disp("b")
11 If=(E-Vf)/(R1+rd);
12 printf(" forward current is %3.3fmA\n",If)
```

---

**Scilab code Exa 2.6 DC load line for forward biased diode**

```
1 //chapter 2
2 //example 2.6
3 //page 43
4 printf("\n")
5 printf("given")
6 If=0;Vf=5;R1=100;
7 E=(If*R1)+Vf
8 disp("E")
9 disp("B")
10 Vf=0;E=5;R1=100;
11 If=(E/R1)*1000;
12 printf(" resistance is %dmA\n",If)
```

---

**Scilab code Exa 2.8 Calculating supply voltage from given Q - point**

```
1 //chapter 2
2 //example 2.8
3 //page 45
4 printf("\n")
5 printf("given")
6 If=50*10^-3;Vf=1.1;R1=100;
7 Vf1=If*R1;
8 disp("Vf1")
9 E=Vf1+Vf
10 printf(" new supply voltage is %3.1fV\n",E)
```

---

**Scilab code Exa 2.9 Maximum forward current of a diode at a given temperature**

```
1 //chapter 2
2 //example 2.9
3 //page 48
4 printf("\n")
5 printf("given")
6 P1=700*10^-3; Vf=.7;
7 //at 25C
8 If=P1/Vf;
9 disp("If")
10 //at 65C
11 D=5*10^-3; T=65-25;
12 P2=P1-D*T
13 If=P2/Vf;
14 printf("maximum forward current at 65C is %3.3fA\n"
, If)
```

---

**Scilab code Exa 2.10 Forward voltage drop and junction dynamic resistance of a diode**

```
1 //chapter 2
2 //example 2.10
3 //page 49
4 printf("\n")
5 printf("given")
6 Vf1=.7; Vf=-1.8*10^-3; If=26*10^-3;
7 T=100-25;
8 Vf2=Vf1+(T*Vf);
9 printf(" voltage at 100C is %3.3fV\n", Vf2)
10 disp("At 25C")
11 T1=25;
```

```
12 rd=(26*10^-3/If)*((T1+273)/298);  
13 printf(" resistance at 25 C is %dohm\n",rd)  
14 disp(" At 100C")  
15 T2=100;  
16 rd=(26*10^-3/If)*((T2+273)/298);  
17 printf(" resistance at 100 C is %3.2f ohm\n",rd)
```

---

### Scilab code Exa 2.11 Diffusion capacitance of a Si diode

```
1 //chapter 2  
2 //example 2.11  
3 //page 51  
4 printf("\n")  
5 printf("given")  
6 If=10*10^-3; Vf=.7; t=70*10^-9;  
7 Cd=((t*If)/Vf)*10^9;  
8 printf(" diffusion capacitance is %dnF\n",Cd)
```

---

### Scilab code Exa 2.12 Minimum fall times for 1N915 and 1N917 diodes

```
1 //chapter 2  
2 //example 2.12  
3 //page 53  
4 printf("\n")  
5 printf("given")  
6 disp("A")  
7 trr=10*10^-9;  
8 tf=10*trr*10^9  
9 printf("minimum fall times is %dns\n",tf)  
10 disp("B")  
11 trr=3;  
12 tf=10*trr;  
13 printf("minimum fall times is %dns\n",tf)
```

---

### Scilab code Exa 2.14 Plotting Diode characteristics

```
1 //chapter 2
2 //example 2.14
3 //page 58
4 printf("\n")
5 printf("given")
6 Io=75*10^-3;
7 //vertical scale of 5mA/cm
8 If=Io/5*10^-3
9 R1=15/(75*10^-3)
10 P=((Io)^2)*R1
```

---

### Scilab code Exa 2.15 Maximum current through the Zener diode

```
1 //chapter 2
2 //example 2.15
3 //page 63
4 printf("\n")
5 printf("given")
6 Vz=7.5; Pd=400*10^-3; D=3.2*10^-3;
7 Izm=Pd/Vz
8 printf("current at 50C is %3.3fA\n", Izm)
9 disp("At 100C")
10 P2=Pd-((100-50)*D)
11 printf(" power at 100C is %3.3fW\n", P2)
12 Izm=P2/Vz;
13 printf(" current at 100C is %3.3fA\n", Izm)
```

---

**Scilab code Exa 2.16 Maximum diode current and power dissipation of 1N755**

```
1 //chapter 2
2 //example 2.16
3 //page 64
4 printf("\n")
5 printf("given")
6 E=20; R1=620; Vz=7.5;
7 Vr1=E-Vz
8 Iz=Vr1/R1;
9 printf(" diode current is %3.5fA\n", Iz)
10 Pd=Vz*Iz;
11 printf(" power dissipation is %3.3fW\n", Pd)
```

---

**Scilab code Exa 2.17 Upper and Lower limits of Zener voltage(Vz)**

```
1 //chapter 2
2 //example 2.17
3 //page 64
4 printf("\n")
5 printf("given")
6 Vz=4.3; Zz=22; Iz=20*10^-3;
7 Iz1=5*10^-3; //change in current
8 Vz1=Iz1*Zz;
9 Vzmax=Vz+Vz1;
10 printf(" maximum voltage is %3.3fV\n", Vzmax)
11 Vzmin=Vz-Vz1;
12 printf(" minimum voltage is %3.3fV\n", Vzmin)
```

---

# Chapter 3

## Diode applications

Scilab code Exa 3.1 Peak output voltage( $V_{po}$ ), Peak load current( $I_p$ ) and peak reverse voltage( $PIV$ )

```
1 //chapter 3
2 //example 3.1
3 //page 73
4 printf("\n")
5 printf("given")
6 Vf=.7; Rl=500; Vi=22;
7 Vpi=1.414*Vi;
8 disp("Vpi")
9 Vpo=Vpi-Vf;
10 printf(" peak voutput voltage is %3.2fV\n",Vpo)
11 Ip=Vpo/Rl;
12 printf("peak load current is %3.4fA\n",Ip)
13 PIV=Vpi;
14 printf("diode peak reverse voltage %3.2fV\n",PIV)
```

---

Scilab code Exa 3.2 Peak output voltage and current of a Bridge rectifier

```
1 //chapter 3
```

```
2 //example 3.2
3 //page 779
4 printf("\n")
5 printf(" given")
6 Vi=30;Rl=300;Vf=.7;
7 Vpi=1.414*Vi;
8 Vpo=Vpi-2*Vf;
9 printf(" peak output voltage %dV\n",Vpo)
10 Ip=Vpo/Rl;
11 printf(" current bridge is %3.3fA\n",Ip)
```

---

### Scilab code Exa 3.3 Peak to Peak ripple voltage of HWR

```
1 //chapter 3
2 //example 3.3
3 //page 83
4 printf("\n")
5 printf(" given")
6 C1=680*10^-6;Eo=28;Rl=200;f=60;
7 I1=Eo/Rl;
8 T=1/f;
9 t1=T;
10 Vr=(I1*t1)/C1;
11 printf("peak to peak ripple voltage is %3.2fV\n",Vr)
```

---

### Scilab code Exa 3.4 Required reservoir capacitance of a HWR

```
1 //chapter 3
2 //example 3.4
3 //page 84
4 printf("\n")
5 printf(" given")
6 Eo=20;Rl=500;f=60;
```

```

7 Vr=(10*Eo)/100 //10% of Eo
8 I1=Eo/Rl
9 T=1/f;
10 t1=T
11 C1=((I1*t1)/Vr)*10^6;
12 printf("reservoir capacitance is %duF\n",C1)

```

---

### Scilab code Exa 3.5 Charging and Discharging time of Half -Wave Rectifier(HWR)

```

1 //chapter 3
2 //example 3.5
3 //page 85
4 printf("\n")
5 printf("given")
6 Eo=20; f=60; Rl=500;
7 I1=Eo/Rl;
8 Vr=(10*Eo)/100;
9 printf("10 percent of Eo is %dV\n",Vr)
10 Eomin=Eo-.5*Vr
11 Eomax=Eo+.5*Vr
12 Q1=sin(inv(Eomin/Eomax));
13 Q1=65
14 Q2=90-Q1
15 T=1/f;
16 t2=(Q2*T)/360;
17 printf(" charging time is %3.4 fs\n",t2)
18 t1=T-t2
19 printf("discharging time is %3.4 fs\n",t1)
20 C1=((I1*t1)/Vr)*10^6;
21 printf("reservoir capacitance is %duF\n",C1)

```

---

### Scilab code Exa 3.6 Surge limiting resistance of HWR

```

1 //chapter 3
2 //example 3.6
3 //page 88
4 printf("\n")
5 printf("given")
6 Eo=21; Vf=.7;
7 t1=1.16*10^-3; t2=15.54*10^-3;
8 Vp=Eo+Vf
9 Vr=2*Vp
10 I1=40*10^-4;
11 Ifrm=(I1*(t1+t2))/t2;
12 Ifsm=30;
13 Rs=Vp/Ifsm
14 printf(" surge limiting resistance is %3.2f ohm\n",Rs
)

```

---

**Scilab code Exa 3.7 RMS voltage(Vrms), RMS current(Irms) and Transformer primary c**

```

1 //chapter 3
2 //example 3.7
3 //page 89
4 printf("\n")
5 printf("given")
6 Vf=.7; Eo=21; I1=40*10^-3; Vp=115;
7 Vs=.707*(Vf+Eo);
8 printf(" Vrms voltage is %3.3f V\n",Vs)
9 Is=3.6*I1;
10 printf(" rms current is %3.3f A\n",Is)
11 Ip=(Vs*Is)/Vp;
12 printf(" primary current is %3.3f A\n",Ip)

```

---

**Scilab code Exa 3.8 Required reservoir capacitance value for full- wave rectifier**

```
1 //chapter 3
2 //example 3.8
3 //page 92
4 printf("\n")
5 printf("given")
6 Vr=2;T=16.7*10^-3;t2=1.16*10^-3;I1=40*10^-3; //from
    example 3.5
7 t1=(T/2)-t2
8 C1=(I1*t1)/Vr;
9 printf(" reservoir capacitor is %3.6 fF\n",C1)
```

---

**Scilab code Exa 3.9 Reservoir capacitor value for full - wave rectifier**

```
1 //chapter 3
2 //example 3.9
3 //page 93
4 printf("\n")
5 printf("given")
6 Vr=2;T=16.7*10^-3;I1=40*10^-3;
7 t1=T/2
8 C1=(I1*t1)/Vr;
9 printf(" reservoir capacitance is %3.6 fF\n",C1)
```

---

**Scilab code Exa 3.10 Surge limiting resistance of bridge rectifier**

```
1 //chapter 3
2 //example 3.10
3 //page 93
4 printf("\n")
5 printf("given")
6 Eo=21;Vf=.7;I1=40*10^-3;t1=7.19*10^-3;t2=1.16*10^-3;
7 Vp=Eo+(2*Vf)
8 Vr=Vp
```

```

9 If=I1/2
10 Ifrm=I1*(t1+t2)/t2
11 Ifsm=30;
12 Rs=Vp/Ifsm
13 printf("surge limiting resistance is %3.3f ohm\n",Rs)

```

---

**Scilab code Exa 3.11 Transformer selection for a full-wave bridge rectifier**

```

1 //chapter 3
2 //example 3.11
3 //page 73
4 printf("\n")
5 printf("given")
6 Eo=21; Vf=.7; I1=40*10^-3; Vp=115;
7 Vs=.707*(Eo+2*Vf)
8 Is=1.6*I1
9 Ip=(Vs*Is)/Vp;
10 printf(" supply current is %3.3f A\n",Ip)

```

---

**Scilab code Exa 3.12 DC output voltage and peak to peak voltage of given ripple wa**

```

1 //chapter 3
2 //example 3.12
3 //page 97
4 printf("\n")
5 printf("given")
6 Eo=20; I1=40*10^-3; R1=22; Vr=2; C1=150*10^-6; C2=C1; fr
    =120;
7 Vo=Eo-I1*R1;
8 vi=Vr/3.14
9 Xc2=1/(2*3.14*fr*C2)
10 vo=(vi*Xc2)/sqrt((R1^2) + (Xc2^2))
11 printf(" dc output voltage is %3.3f V\n",vo)

```

```
12 Vpp=2*vo;
13 printf(" peak to peak voltage is %3.3fV\n",Vpp)
```

---

**Scilab code Exa 3.13 Suitable capacitor and inductor values of LC pi filter**

```
1 //chapter 3
2 //example 3.13
3 //page 98
4 printf("\n")
5 printf(" given")
6 C1=150*10^-6;C2=C1;vi=4;vo=1;f=120;
7 Xc2=8.84; //FROM EXAMPLE 3.12
8 Xl=Xc2*((vi/vo)+1)
9 L1=Xl/(2*3.14*f);
10 printf(" suitable value of L1 is %3.3fH\n",L1)
```

---

**Scilab code Exa 3.14 Peak output voltage, value of inductor (L1)and capacitor(C1)**

```
1 //chapter 3
2 //example 3.14
3 //page 101
4 printf("\n")
5 printf(" given")
6 Edc=20;vo=.24;Vo=20;Il=40*10^-3;fr=120;
7 Eomax=(3.14*Edc)/2
8 Epeak=(4*Eomax)/(3*3.14)
9 vi=Epeak;
10 Rl=Vo/Il
11 Xlc=(2*Rl)/3
12 Lc=Xlc/(2*3.14*fr)
13 L=1.25*Lc;
14 Xl=2*3.14*fr*L
15 Xc=Xl/((vi/vo)+1)
```

```
16 C1=1/(2*3.14*fr*Xc)
```

---

**Scilab code Exa 3.15** Load regulation, Source effect, line regulation of FWR

```
1 //chapter 3
2 //example 3.15
3 //page 105
4 printf("\n")
5 printf("given")
6 Eo=20
7 E0=20-19.7 //load effect
8 loadregulation =(E0*100)/Eo //percentage
9 sourceeffect=20.2-20
10 lineregulation =(sourceeffect*100)/Eo
```

---

**Scilab code Exa 3.16** Parameters of Zener diode as voltage regulator

```
1 //chapter 3
2 //example 3.16
3 //page 108
4 printf("\n")
5 printf("given")
6 Vz=9.1; Izt=20*10^-3; Es=30;
7 R1=(Es-Vz)/Izt
8 Pr1=(Izt^2)*R1
9 Es=27;
10 Iz=(Es-Vz)/R1
```

---

**Scilab code Exa 3.17** Maximum load current of Load regulator circuit

```

1 //chapter 3
2 //example 3.17
3 //page 110
4 printf("\n")
5 printf("given")
6 Vz=6.2; Pd=400*10^-3; Es=16;
7 Izm=Pd/Vz
8 R1=(Es-Vz)/Izm
9 Pr1=(Izm^2)*R1
10 Izmin=5*10^-3;
11 Izmax=Izm-Izmin;
12 printf("maximum current is %3.4fA\n", Izmax)

```

---

**Scilab code Exa 3.18** Line regulation, load regulation and ripple rejection ratio of a voltage source

```

1 //chapter 3
2 //example 3.18
3 //page 112
4 printf("\n")
5 printf("given")
6 Zz=7; Es=16; Vo=6.2; Il=59.5*10^-3;
7 es=(10*Es)/100 //10% os Es
8 Rl=Vo/Il;
9 disp("es*Zz || Rl/R1+Zz || Rl")
10 V0=es*((Zz*Rl)/(Zz+Rl))/(Rl+((Zz*Rl)/(Zz+Rl)))
11 lineregulation=(V0*100)/Vo;
12 printf("line regulation voltage is %3.3f percentage\n"
      ,lineregulation)
13 V0=Il*((Zz*Rl)/(Zz+Rl))
14 loadregulation=(V0*100)/Vo;
15 printf("loadregulation voltage is %3.3f percentage\n"
      ,loadregulation)
16 Rr=((Zz*Rl)/(Zz+Rl))/(Rl+((Zz*Rl)/(Zz+Rl)));
17 printf("ripple rejection is %3.3f\n", Rr)

```

---

### Scilab code Exa 3.19 Load resistance ( $R_1$ ), forward and reverse currents of Voltage

```
1 //chapter 3
2 //example 3.19
3 //page 114
4 printf("\n")
5 printf("given")
6 E=9; Vf=.7; If=1*10^-3;
7 Vo=E-Vf
8 R1=Vo/If
9 Vr=E;
10 printf("diode forward voltage is %3.2f ohm\n",Vr)
11 printf("diode forward current is %3.3f A\n",If)
```

---

### Scilab code Exa 3.20 Forward and reverse currents for diode as Negative shunt clip

```
1 //chapter 3
2 //example 3.20
3 //page 117
4 printf("\n")
5 printf("given")
6 E=5; Vo=4.5; I1=2*10^-3; Vf=0.7;
7 R1=(E-Vo)/I1;
8 printf(" suitable resistance is %d ohm\n",R1)
9 Vr=E
10 disp("when diode is forward biased")
11 If=(E-Vf)/R1;
12 printf(" diode forward current is %3.3f A\n",If)
```

---

**Scilab code Exa 3.21 Suitable resistor for biased shunt clipper**

```
1 //chapter 3
2 //example 3.21
3 //page 119
4 printf("\n")
5 printf("given")
6 Vo=2.7; Vf=.7; E=9; If=1*10^-3; Il=If;
7 Vb=Vo-Vf;
8 R1=(E-Vo)/(Il+If);
9 printf("resistance is %3.3fOhm\n",R1)
```

---

**Scilab code Exa 3.22 Zener diode as shunt clipper**

```
1 //chapter 3
2 //example 3.22
3 //page 120
4 printf("\n")
5 printf("given")
6 Vo=5; Vf=.7; Iz=5*10^-3; Il=1*10^-3; E=20;
7 Vz=Vo-Vf
8 R1=(E-Vo)/(Il+Iz);
9 printf("zener diode resistance si %dohm\n",R1)
```

---

**Scilab code Exa 2.23 Tilt on the output waveform of a diode clamping circuit**

```
1 //chapter 3
2 //example 3.21
3 //page 119
4 printf("\n")
5 printf("given")
6 E=10; R1=56*10^3; f=1000; C1=1*10^-6;
7 Vo=2*E
```

```
8 Ic=Vo/R1
9 t=1/(2*f);
10 Vc=(Ic*t)/C1;
11 printf(" tilt output voltage is %3.3fV\n",Vc)
```

---

**Scilab code Exa 3.24** Component determination of negative voltage clamping circuit

```
1 //chapter 3
2 //example 3.24
3 //page 124
4 printf("\n")
5 printf("given")
6 f=500;Rs=600;E=8;
7 t=1/(2*f)
8 PW=t;
9 C1=PW/Rs
10 Vo=2*E
11 Vc=(1*Vo)/100;//1% of the Vo
12 Ic=(Vc*C1)/t
13 R1=(2*E)/Ic;
14 printf("suitable value of R1 is %dohm\n",R1)
```

---

**Scilab code Exa 3.25** Upper and lower voltages for biased clamping circuits

```
1 //chapter 3
2 //example 3.25
3 //page 125
4 printf("\n")
5 printf("given\n")
6 Vf=.7;E=6;Vb1=3;
7 Vc=Vb1-Vf-(-E)
8 Vo=Vb1-Vf
9 disp("when input is +E")
```

---

```

10 Vo=E+Vc
11 Vc=E-Vb1-Vf
12 Vo=Vb1+Vf
13 disp("when input is -E")
14 Vo=-E+(-Vc)

```

---

### Scilab code Exa 3.26 Capacitor (C1, C2) values for voltage doubling circuit

```

1 //chapter 3
2 //example 3.26
3 //page 130
4 printf("\n")
5 printf("given")
6 E=12;Vf=.7;Rl=47*10^3;f=5000;
7 Vo=2*(E-Vf)
8 I1=Vo/Rl
9 disp(" capacitor discharge time")
10 t=1/(2*f)
11 disp(" for 1% ripple allow .5% due to discharge of
      C2 ,.5%due to discharge of C1")
12 Vc=(.5*Vo)/100
13 C2=((I1*t)/Vc)*10^6;
14 printf(" value of capacitor C2 is %3.2fuF\n",C2)
15 C1=2*C2;
16 printf(" value of capacitor C1 is %3.2fuF\n",C1)

```

---

### Scilab code Exa 3.27 Diode forward current for AND logic circuit

```

1 //chapter 3
2 //example 3.21
3 //page 119
4 printf("\n")
5 printf("given")

```

```
6 Vcc=5;Vf=.7;R1=3.3*10^3;
7 disp("A")
8 Ir1=(Vcc-Vf)/R1;
9 printf(" diode forward current when all input are low
    is %3.4fA\n",Ir1)
10 disp(" for each diode")
11 If=Ir1/3
12 disp("B")
13 If2=Ir1/2
14 If3=If2;
15 printf(" forward current when input A is high is %3
    .5fA\n",If3)
16 disp("C")
17 If3=Ir1;
18 printf(" forward current when input A and B are high
    and C is low %3.5fA\n",If3)
```

---

# Chapter 4

## Bipolar Junction Transistors

**Scilab code Exa 4.1** Determine the emitter ( $I_e$ ) and base ( $I_b$ ) currents of a transis

```
1 //chapter 4
2 //example 4.1
3 //page 153
4 printf("\n")
5 printf("given")
6 Adc=.98; Ib=100*10^-6;
7 Ic=(Adc*Ib)/(1-Adc);
8 printf("value of Ic is %3.3fA\n",Ic)
9 Ie=Ic/Adc;
10 printf(" value of Ie is %3.3fA\n",Ie)
11 Bdc=Adc/(1-Adc);
12 disp(Bdc)
```

---

**Scilab code Exa 4.2** Common base current gain ( $A_{dc}$ ), Common-emitter current gain ( $B$ )

```
1 //chapter 4
2 //example 4.2
3 //page 153
```

```
4 printf("\n")
5 printf("given")
6 Ic=1*10^-3; Ib=25*10^-6;
7 Bdc=Ic/Ib
8 Ie=Ic+Ib
9 Adc=Ic/Ie
10 Ib=Ic/Bdc
```

---

**Scilab code Exa 4.3 DC collector voltage and circuit voltage gain of CE amplifier**

```
1 //chapter 4
2 //example 4.1
3 //page 153
4 printf("\n")
5 printf("given")
6 Bdc=80; Bac=Bdc; Vcc=18; R1=10*10^3;
7 Ib=15*10^-6; //for Vb=.7
8 Ic=Bdc*Ib;
9 Vc=Vcc-(Ic*R1);
10 printf("dc collector voltage is %dV\n",Vc)
11 disp(" when vi=50mV")
12 Ib=3*10^-6; Vi=50*10^-3;
13 Ic=Bdc*Ib
14 Vo=Ic*R1
15 Av=Vo/Vi
```

---

**Scilab code Exa 4.4 Collector current (Ic), Base current (Ib) and hFE of BJT as sw**

```
1 //chapter 4
2 //example 4.4
3 //page 160
4 printf("\n")
5 printf("given")
```

```
6 Vcc=5;Vce=.2;R2=4.7*10^3;Vi=2;Vbe=.7;R1=12*10^3;
7 Ic=(Vcc-Vce)/R2
8 Ib=(Vi-Vbe)/R1
9 hFE=Ic/Ib
```

---

Scilab code Exa 4.6 Base current (Ib) and collector current (Ic) from output characteristics

```
1 //chapter 4
2 //example 4.6
3 //page 169
4 printf("\n")
5 printf("given")
6 Vbe=.7;Vce=-6;
7 Ib=20*10^-6
8 Ic=2.5*10^-3 //from output characteristics
9 Bdc=Ic/Ib
```

---

# Chapter 5

## BJT biasing

Scilab code Exa 5.1 DC load line

```
1 //chapter 5
2 //example 5.1
3 //page 182
4 printf("\n")
5 printf("given")
6 Rc=12*10^3; Vcc=20;
7 disp(" When Ic=0")
8 Ic=0;
9 Vce=Vcc-Ic*Rc
10 disp(" At point A Ic=0 nad Vce=20")
11 disp("When Vce=0")
12 Vce=0;
13 Ic=Vcc/Rc
14 disp(" At point B Ic=1.7mA and Vce=0")
```

---

Scilab code Exa 5.2 DC Bias point (Q-Point)

```
1 //chapter 5
```

```
2 //example 5.2
3 //page 186
4 printf("\n")
5 printf(" given")
6 Vcc=18;Rc=2.2*10^3;Ib=40*10^-6;
7 disp("when Ic=0")
8 Ic=0;
9 Vce=Vcc-Ic*Rc
10 disp("At point A Ic=0 and Vce=18")
11 disp("when Vce=0")
12 Ic=Vcc/Rc
13 disp(" at point B Ic=8.2mA and Vce=0")
```

---

#### Scilab code Exa 5.3 DC analysis of common-base amplifier

```
1 //chapter 5
2 //example 5.1
3 //page 182
4 printf("\n")
5 printf(" given")
6 Rb=470*10^3;Rc=2.2*10^3;Vcc=18;hfe=100;
7 Vee=.7;
8 Ib=(Vcc-Vee)/Rb
9 Ic=hfe*Ib
10 Vce=Vcc-Ic*Rc
```

---

#### Scilab code Exa 5.4 Maximum and Minimum levels of Ic and Vce for base bias circuit

```
1 //chapter 5
2 //example 5.4
3 //page 189
4 printf("\n")
5 printf(" given")
```

```
6  Rc=12.0*10^3;
7  hFEmin=50; hFEmax=200; Vcc=18; Vbe=.7; Rb=470*10^3;
8  Ib=(Vcc-Vbe)/Rb
9  Ic=hFEmin*Ib
10 Vce=Vcc-Ic*Rc
11 Ic=hFEmax*Ib
12 Vce=Vcc-Ic*Rc
```

---

#### Scilab code Exa 5.5 DC analysis of collector-base bias circuit

```
1 //chapter 5
2 //example 5.5
3 //page 193
4 printf("\n")
5 printf("given")
6 Rb=270*10^3; Rc=2.2*10^3; Vcc=18;
7 hFE=100; Vbe=.7;
8 Ib=(Vcc-Vbe)/(Rb+Rc*(hFE+1))
9 Ic=hFE*Ib
10 Vce=Vcc-Rc*(Ic+Ib)
```

---

#### Scilab code Exa 5.7 DC analysis of voltage -divider bias circuit

```
1 //chapter 5
2 //example 5.7
3 //page 197
4 printf("\n")
5 printf("given")
6 R1=33*10^3; R2=12*10^3; Rc=1.2*10^3; Re=1*10^3;
7 Vcc=18; Vbe=.7;
8 Vb=(Vcc*R2)/(R1+R2)
9 Ve=Vb-Vbe
10 Ie=(Vb-Vbe)/Re
```

```
11 Ic=Ie;
12 Vc=Vcc-(Ic*Rc)
13 Vce=Vc-Ve
```

---

### Scilab code Exa 5.8 Precise circuit analysis of voltage-divider bias circuit

```
1 //chapter 5
2 //example 5.8
3 //page 199
4 printf("\n")
5 printf("given")
6 Vcc=18; Vbe=.7; hfe=100;
7 R1=33*10^3; R2=12*10^3; Re=1*10^3; Rc=1.2*10^3;
8 Vt=(Vcc*R2)/(R1+R2)
9 Rt=(R1*R2)/(R1+R2)
10 Ib=(Vt-Vbe)/(Rt+Re*(1+hfe))
11 Ic=hfe*Ib
12 Ie=Ib+Ic
13 Ve=Ie*Re
14 Vc=Vcc-(Ic*Rc)
15 Vce=Vc-Ve
```

---

### Scilab code Exa 5.9 Accurate analysis of voltage-divider bias circuit for minimum

```
1 //chapter 5
2 //example 5.9
3 //page 200
4 printf("\n")
5 printf("given")
6 Vcc=18.0;
7 Rc=1.2*10^3;
8 hfe=50; Vt=4.8; Rt=8.8*10^3; //from example 5.7
9 Re=1*10^3; Vbe=.7;
```

```
10 Ib=(Vt-Vbe)/(Rt+Re*(1+hfe))
11 Ic=hfe*Ib
12 Ie=Ib+Ic
13 Ve=Ie*Re
14 Vc=Vcc-(Ic*Rc)
15 Vce=Vc-Ve
```

---

### Scilab code Exa 5.10 Analyze voltage divider bias circuit for a maximum hFE of 200

```
1 //chapter 5
2 //example 5.10
3 //page 201
4 printf("\n")
5 printf("given")
6 Vcc=18.0;
7 Rc = 1.2*10^3;
8 Vt=4.8; Rt=8.8*10^3; //from example 5.8
9 Re=1*10^3; Vbe=.7; hfe=200;
10 Ib=(Vt-Vbe)/(Rt+Re*(1+hfe))
11 Ic=hfe*Ib
12 Ie=Ib+Ic
13 Ve=Ie*Re
14 Vc=Vcc-(Ic*Rc)
15 Vce=Vc-Ve
```

---

### Scilab code Exa 5.11 Base bias circuit design

```
1 //chapter 5
2 //example 5.11
3 //page 208
4 printf("\n")
5 printf("given")
6 Vce=5; Ic=5*10^-3; Vcc=15; hfe=100; Vbe=0.7;
```

```
7 Rc=(Vcc-Vce)/Ic
8 Ib=Ic/hfe
9 Rb=(Vcc-Vbe)/Ib
```

---

#### Scilab code Exa 5.12 Collector to base bias circuit design

```
1 //chapter 5
2 //example 5.12
3 //page 209
4 printf("\n")
5 printf("given")
6 Vce=5; Ic=5*10^-3; Vcc=15; hfe=100; Vbe = 0.7;
7 Ib=Ic/hfe
8 Rc=(Vcc-Vce)/(Ic+Ib)
9 Rb=(Vce-Vbe)/Ib
```

---

#### Scilab code Exa 5.13 Voltage divider bias circuit design

```
1 //chapter 5
2 //example 5.13
3 //page 211
4 printf("\n")
5 printf("given")
6 Vce=5; Ve=Vce; Ic=5*10^-3; hFE=100; Vcc=15; Vbe=.7;
7 Ie=Ic;
8 Re=Ve/Ie
9 Rc=(Vcc-Vce-Ve)/Ic
10 I2=Ic/10
11 Vb=Ve+Vbe
12 R2=Vb/I2
13 R1=(Vcc-Vb)/I2
```

---

**Scilab code Exa 5.14** Design voltage divider bias circuit with given bias parameter

```
1 //chapter 5
2 //example 5.14
3 //page 212
4 printf("\n")
5 printf("given")
6 Vce=3; Ve=5; Ic=1*10^-3; Vcc=12; Vbe=0.7;
7 Ie=Ic;
8 R4=Ve/Ie
9 disp(" with Ic=1mA and R4=4.7Kohm")
10 R4=4.7*10^3;
11 Ve=Ic*R4
12 Vc=Ve+Vce
13 Vr3=Vcc-Vc
14 R3=Vr3/Ic
15 Vb=Ve+Vbe
16 I2=Ic/10
17 R2=Vb/I2
18 disp(" with R2=56Kohm and Vb=5.4V")
19 R2=56*10^3;
20 I2=Vb/R2
21 R1=(Vcc-Vb)/I2
```

---

**Scilab code Exa 5.15** Design voltage divider bias circuit to operate from 18V suppl

```
1 //chapter 5
2 //example 5.15
3 //page 214
4 printf("\n")
5 printf("given")
6 Vce=9; Ve=4; Ic=4*10^-3; Vcc=18; Vbe = 0.7;
```

```

7 Ie=Ic;
8 R4=Ve/Ie
9 Vb=Ve+Vbe
10 I2=Ic/10
11 R2=Vb/I2
12 disp(" with R2=12Kohm standard")
13 R2=12*10^3;
14 I2=Vb/R2
15 R1=(Vce+Ve-Vb)/I2
16 disp(" with R1=22kohm standard")
17 R1=22*10^3;
18 Vr3=Vcc-Vce-Ve
19 R3=Vr3/(Ic+I2)

```

---

### Scilab code Exa 5.16 Design voltage divider bias circuit to operate from 9V supply

```

1 //chapter 5
2 //example 5.16
3 //page 216
4 printf("\n")
5 printf("given")
6 Vc=5; Ic=1*10^-3; hFE=70; Vbe=.7; Vee=9; Vcc=Vee; Re
    =8.2*10^3;
7 Ve=Vee-Vbe
8 Ie=Ic;
9 R3=Ve/Ie
10 disp(" with R3=8.2kohm standard value")
11 R3=8.2*10^3;
12 Ie=Ve/R3
13 Vr2=Vcc-Vc
14 R2=Vr2/Ic
15 Ib=Ic/hFE
16 Vr1=Vbe/10
17 R1=Vr1/Ib
18 disp(" use 4.7Kohm as standard")

```

```

19 //the transistor emitter terminal is .7 below ground
    and voltage across Re is
20 Ve=Vee-Vbe
21 Ie=Ve/Re
22 Vc=Vcc-(Ie*3.9*10^3)

```

---

### Scilab code Exa 5.17 Stability factors for three bias circuit

```

1 //chapter 5
2 //example 5.17
3 //page 220
4 printf("\n")
5 printf("given")
6 hFE=100;
7 Rc=2.2*10^3; Rb=270*10^3; Re=1*10^3; R1=33*10^3; R2
    =12*10^3;
8 S=1+hFE
9 disp("for collector to base bias")
10 S=(1+hFE)/(1+(hFE*Rc)/(Rc+Rb))
11 disp(" for voltage divider bias")
12 disp("S=(1+hFE)/(1+hFE*Re(Re+R1 || R2))")
13 S=(1+hFE)/(1+(hFE*Re)/(Re+(R1*R2)/(R1+R2)))

```

---

### Scilab code Exa 5.18 Change in collector current (Ic) when temperature increases

```

1 //chapter 5
2 //example 5.18
3 //page 221
4 printf("\n")
5 printf("given")
6 Icbo1=15*10^-9; // at 25C
7 S=101;
8 disp("chnage in temp")

```

```
9 T=105-25
10 disp(" n=T in 10 step")
11 n=T/10
12 Icbo2=Icbo1*2^n
13 Icbo=Icbo2-Icbo1
14 disp(" for base bias")
15 Ic=S*Icbo
16 disp(" for collector to base bias")
17 S=56;
18 Ic=S*Icbo
19 disp(" for voltage divider bias")
20 S=8.2;
21 Ic=S*Icbo
```

---

#### Scilab code Exa 5.19 Effect of base-emitter voltage (Vbe) changes on collector cur-

```
1 //chapter 5
2 //example 5.19
3 //page 223
4 printf("\n")
5 printf("given")
6 Re=4.7*10^3;
7 T=125-25
8 Vbe=T*(1.8*10^-3)
9 Ie=Vbe/Re
```

---

#### Scilab code Exa 5.20 DC analysis of BJT biased as switching circuit

```
1 //chapter 5
2 //example 5.20
3 //page 2
4 printf("\n")
5 printf("given")
```

```

6 Vcc=10;Rc=1*10^3;Rb=6.8*10^3;Vs=5;
7 T=125-25
8
9 Vbe=T*(1.8*10^-3)
10 disp(" hFE calculation")
11 Ic=Vcc/Rc
12 Ib=(Vs-Vbe)/Rb
13 hFE=Ic/Ib
14 disp(" when hFE=10")
15 hFE=10
16 Ic=hFE*Ib
17 Vce=Vcc-(Ic*Rc)

```

---

**Scilab code Exa 5.21** Minimum hFE of a transistor biased in saturation region

```

1 //chapter 5
2 //example 5.21
3 //page 227
4 printf("\n")
5 printf("given")
6 Vcc=15;Rc=3.3*10^3;Vbe=.7;Rb=56*10^3;
7 Ic=Vcc/Rc
8 Ib=(Vcc-Vbe)/Rb
9 hFE=Ic/Ib;
10 printf(" minimum hFE is %3.2f\n",hFE)

```

---

**Scilab code Exa 5.22** Suitable resistances for capacitor coupled switching circuit

```

1 //chapter 5
2 //example 5.22
3 //page 229
4 printf("\n")
5 printf("given")

```

```
6 Vcc=12; Ic=1.5*10^-3; Vs=5; hFE=10; Vbe=.7;  
7 Rc=Vcc/Ic  
8 Ib=Ic/hFE  
9 Rb=(Vs-Vbe)/Ib
```

---

Scilab code Exa 5.23 Base and collector resistors for capacitor coupled switching

```
1 //chapter 5  
2 //example 5.23  
3 //page 229  
4 printf("\n")  
5 printf("given")  
6 Vcc=9; Ic=2*10^-3; hFE=10; Vbe=.7;  
7 Rc=Vcc/Ic  
8 Ib=Ic/hFE  
9 Rb=(Vcc-Vbe)/Ib
```

---

# Chapter 6

## AC Analysis of BJT Circuits

Scilab code Exa 6.1 DC analysis of voltage divider circuit

```
1 //chapter 6
2 //example 6.1
3 //page 240
4 printf("\n")
5 printf("given")
6 Vcc=12; R2=15*10^3; R1=33*10^3; rs=600;
7 disp("with no signal source")
8 Vb=(Vcc*R2)/(R1+R2);
9 printf(" base bias voltage when no signal source is
       present %3.2fV\n",Vb)
10 disp(" signal source directly connected")
11 Vb=(Vcc*((rs*R2)/(rs+R2))/(R1+((rs*R2)/(rs+R2))));
```

---

Scilab code Exa 6.2 DC and AC load line for transistor circuit

```
1 //chapter 6
2 //example 6.2
```

```

3 // page 244
4 printf("\n")
5 printf(" given")
6 Rc=2.2*10^3; Re=2.7*10^3; R1=18*10^3; R2=8.2*10^3; Vbe
   = .7
7 disp(" drawing dc load line")
8 Rldc=Rc+Re
9 disp(" for Vce")
10 Ic=0; Vcc=20;
11 Vce=Vcc-Ic*(Rc+Re)
12 disp(" plot point A at")
13 Ic=Vcc/(Rc+Re)
14 disp(" plot point B Ic=4.08mA and Vce=0")
15 disp(" draw dc laod line through point A nad B")
16 Vb=(Vcc*R2)/(R1+R2)
17 Ve=Vb-Vbe
18 Ic=Ve/Re
19 Ie=Ic
20 disp(" drawing the ac load line")
21 Rlac=Rc //when there is no external Rl
22 Vce=Ic*Rc

```

---

### Scilab code Exa 6.3 h-parameters of CE transistors

```

1 //chapter 6
2 //example 6.2
3 //page 251
4 printf("\n")
5 printf(" given")
6 Vce=4.5; Ib=40*10^-6;
7 disp(" from current characteristic at Vce=4.5V and Ib
      =40uA")
8 Ic=4*10^-3; Ib=30*10^-6;
9 hFE=Ic/Ib;
10 printf(" the value of hFE is %d\n", hFE)

```

```
11 disp("from output characteristic at Vce=4.5 and Ib  
=40uA")  
12 Ic=400*10^-3; Vce=6;  
13 hoe=(Ic/Vce)*10^6;  
14 printf("the value of hoe is %3.2f uS\n",hoe)
```

---

### Scilab code Exa 6.4 CE h-parameters

```
1 //chapter 6  
2 //example 6.4  
3 //page 253  
4 printf("\n")  
5 printf("given")  
6 hfe=133; hoe=33.3*10^-6;  
7 hfc=1+hfe  
8 hob=hoe/(1+hfe)  
9 A=hfe/(1+hfe)
```

---

### Scilab code Exa 6.5 Estimate the CE input resistance and determine the h-parameter

```
1 //chapter 6  
2 //example 6.5  
3 //page 253  
4 printf("\n")  
5 printf("given")  
6 Ib=20*10^-6; Ic=1*10^-3;  
7 Ie=Ic;  
8 re=(26*10^-3)/Ie  
9 hfe=Ic/Ib  
10 hie=(1+hfe)*re  
11 r=hie  
12 B=hfe
```

---

### Scilab code Exa 6.6 Input and Output impedances and voltage gain of CE circuit

```
1 //chapter 6
2 //example 6.6
3 //page 258
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3; hfe=75; hoe=1*10^-6; R1=68*10^3; R2
    =56*10^3; Rc=3.9*10^3; Rl=82*10^3;
7 disp(" input impedance Zi=R1||R2||hie")
8 Zi=((R1*R2*hie)/(R1+R2+hie))*10^-3;
9 printf(" input impedance is %3.2fKohm\n",Zi)
10 disp("output impedance is Zo=Rc||(1/hoe)")
11 Zo=((Rc*(1/hoe))/(Rc+(1/hoe)))*10^-3;
12 printf(" output impedance is %f3.2fKohm\n",Zo)
13 Av=-(hfe*((Rc*Rl)/(Rc+Rl)))/hie;
14 printf(" voltage gain is %d\n",Av)
```

---

### Scilab code Exa 6.7 Calculate re and voltage gain of CE circuit

```
1 //chapter 6
2 //example 6.7
3 //page 259
4 printf("\n")
5 printf("given")
6 Ic=1.5*10^-3; Rc=4.7*10^3; Rl=56*10^3;
7 Ie=Ic;
8 re=(26*10^-3)/Ie
9 Av=-(((Rc*Rl)/(Rc+Rl))/re);
10 printf(" voltage gain is %d\n",Av)
```

---

**Scilab code Exa 6.8** Input and output impedance and voltage gain of CE circuit

```
1 //chapter 6
2 //example 6.8
3 //page 262
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3; hfe=75; hoe=1*10^-6; Re=4.7*10^3; R1
    =68*10^3; R2=56*10^3; Rc=3.9*10^3; Rl=82*10^3;
7 Zb=hie+Re*(1+hfe)
8 disp(" input impedance is Zi=R1 || R2 || Zb")
9 Zi=((R1*R2*Zb)/(R1+R2+Zb));
10 printf(" input circuit resistance is %3.3fKohm\n",Zi
    )
11 Zo=Rc
12
13 Av=-hfe*((Rc*Rl)/(Rc+Rl))/(hie+Re*(1+hfe));
14 printf(" voltage gain is %3.3f\n",Av)
```

---

**Scilab code Exa 6.9** h-parameter of CC circuit with and without load resistor (Rl)

```
1 //chapter 6
2 //example 6.9
3 //page 267
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3; hfe=75; R1=10*10^3; R2=10*10^3; Re
    =4.7*10^3; Rl=12*10^3; rs=1*10^3;
7 disp(" Rl is not connected")
8 hic=hie
9 hfc=1+hfe
10 Zb=hic+hfc*(Re)
```

```

11 Zi=(R1*R2*Zb)/(R1+R2+Zb)
12 Ze=(hic+(R1*R2*rs)/(R1+R2+rs))/hfc
13 Z0=(Ze*Re)/(Ze+Re)
14 disp(" when Rl is connected")
15 Zb=hic+hfc*((Re*Rl)/(Re+Rl))
16 Zi=(R1*R2*Zb)/(R1+R2+Zb)
17 hib=hie/(1+hfe)
18 Av=((Re*Rl)/(Re+Rl))/(hib+((Re*Rl)/(Re+Rl)))

```

---

**Scilab code Exa 6.10** Input and output impedance and voltage gain of transistor in

```

1 //chapter 6
2 //example 6.10
3 //page 273
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3; hfe=75; Re=4.7*10^3; Rc=3.9*10^3; Rl
    =82*10^3;
7 hib=hie/(1+hfe)
8 hfb=hfe/(1+hfe)
9 Zi=(hib*Re)/(Re+hib);
10 printf("input impedance is %3.2f ohm\n",Zi)
11 Zo=Rc;
12 printf(" output impedance is %3.2f ohm\n",Zo)
13 Av=(hfb*((Rc*Rl)/(Rc+Rl)))/hib;
14 printf(" voltage gain is %3.2f\n",Av)

```

---

**Scilab code Exa 6.11** Input impedance and voltage gain of CB circuit without coupling

```

1 //chapter 6
2 //example 6.11
3 //page 273
4 printf("\n")

```

```

5 printf("given")
6 hib=27.6; hfb=.987; R1=68*10^3; R2=56*10^3; Re=4.7*10^3;
    Rc=3.9*10^3; Rl=82*10^3;
7 Rb=(R1*R2)/(R1+R2);
8 Ze=hib+Rb*(1-hfb)
9 Zi=(Ze*Re)/(Ze+Re)
10 Av=(hfb*((Rc*R1)/(Rc+Rl)))/(hib+Rb*(1-hfb))

```

---

### Scilab code Exa 6.12 Output voltage (Vo) for CE, CB transistor circuits

```

1 //chapter 6
2 //example 6.12
3 //page 277
4 printf("\n")
5 printf("given")
6 Rc=5.6*10^3; Rl=33*10^3; rs=600; R1=68.0*10^3;
7 R2=56.0*10^3; Re=4.7*10^3;
8 hfe=100; hie=1.5*10^3; vs=50*10^-3;
9 disp("CE circuit operation with vs at transistor
       base and Re bypassed")
10 Av=(hfe*((Rc*R1)/(Rc+Rl)))/hie
11 Zb=hie
12 Rb=(R1*R2)/(R1+R2);
13 Zi=(Rb*Zb)/(Rb+Zb)
14 vi=(vs*Zi)/(rs+Zi)
15 vo=Av*vi
16 disp("Cb circuit operation with vs at emitter and
       the base resistor bypassed")
17 Av=(hfe*((Rc*R1)/(Rc+Rl)))/hie
18 Ze=hie/(1+hfe)
19 Zi=(Ze*Re)/(Ze+Re)
20 vi=(vs*Zi)/(rs+Zi)
21 vo=Av*vi

```

---

**Scilab code Exa 6.13 DC analysis of Eber-Moll's BJT model**

```
1 //chapter 6
2 //example 6.13
3 //page 279
4 printf("\n")
5 printf("given")
6 Io=50*10^-9; Vbe=.7; Vbc=-10; Af=.995; Ar=.5; Vt
    =26*10^-3; n=2; Vd=-10;
7 x=Vd/(n*Vt);
8 Idc=(Io*((2.73^x)-1))*10^9;
9 Idc=Io*(-1)
10 y=Vbe/(n*Vt);
11 Ide=Io*((2.73^y)-1)
12 I1=Af*Ide
13 I2=Ar*Idc
14 Ic=I1-Idc
15 Ie=Ide-I2
16 Ib=Ie-Ic
```

---

# Chapter 8

## BJT specifications and performance

Scilab code Exa 8.2 Output power change of an amplifier in dB

```
1 //chapter 8
2 //example 8.2
3 //page 313
4 printf("\n")
5 printf("given")
6 P2=25*10^-3; //when frequency increase to 20KHz
7 P1=50*10^-3; //when signal frequency is 5KHz
8 Po=10*log10(P2/P1);
9 printf(" output power change in decibels is %dB\n",
Po)
```

---

Scilab code Exa 8.3 Output power change of voltage amplifier in dB

```
1 //chapter 8
2 //example 8.3
3 //page 314
```

```

4 printf("\n")
5 printf("given")
6 v1=1; // output voltage measured at 5KHz
7 v2=.707; // output voltage measure at 20kHz
8 Po=20*log10(v2/v1);
9 printf(" output power change is %dB\n",Po)

```

---

### Scilab code Exa 8.4 Miller capacitance of CE amplifier

```

1 //chapter 8
2 //example 8.4
3 //page 317
4 printf("\n")
5 printf("given")
6 Ic=1*10^-3; hfe=50; hie=1.3*10^3; fT=250*10^6; Cbc
    =5*10^-12; Rc=8.2*10^3; Rl=100*10^3;
7 Ie=Ic;
8 Av=(hfe*((Rc*Rl)/(Rc+Rl)))/hie
9 Cbe=(6.1*Ie)/fT;
10 Cin=(Cbe+(1+Av)*Cbc)*10^9;
11 printf(" input capacitance when the circuit operated
        as CE is %3.3fnF\n",Cin)

```

---

### Scilab code Exa 8.5 Input capacitance effect on CE and CB circuits

```

1 //chapter 8
2 //example 8.5
3 //page 319
4 printf("\n")
5 printf("given")
6 R1=100*10^3; R2=47*10^3; Re=4.7*10^3;
7 Cbc=5*10^-12; Cbe=24.4*10^-12; hfe=50; hie=1.3*10^3; hib
    =24.5; rs=hib; rs=600;

```

```

8 disp(" common emitter circuit")
9 Rb=(R1*R2)/(R1+R2);
10 Zi=(Rb*hie)/(Rb+hie)
11 Cin=1.48*10^-9;
12 f2=1/(2*3.14*Cin*((rs*Zi)/(rs+Zi)));
13 printf("input-capacitance upper cutoff frequency is
    %dHz\n",f2)
14 disp("common base circuit")
15 Zi=(Re*hib)/(Re+hib)
16 Cin=(Cbe+Cbc)
17 f2=(1/(2*3.14*Cin*((rs*Zi)/(rs+Zi))))*10^-6;
18 printf(" input capacitance upper cutoff when
        operating as CB circuit with base bypassed to
        ground is %dMHz\n",f2)

```

---

### Scilab code Exa 8.6 Input capacitance effects on Emitter follower circuit

```

1 //chapter 8
2 //example 8.6
3 //page 322
4 printf("\n")
5 printf(" given")
6 fT=50*10^6; hfe=50; f2o=60*10^3; Rc=10*10^3;
7 fae=fT/hfe
8 C4=(1/(2*3.14*f2o*Rc))*10^12;
9 printf(" capacitance required for C4 to give 60kHz
    upper cutoff frequency is %dpF\n",C4)

```

---

### Scilab code Exa 8.8 Transistor switching times

```

1 //chapter 8
2 //example 8.8
3 //page 326

```

```

4 printf("\n")
5 printf("given")
6 ton=100*10^-9;Rs=600;Rb=4.7*10^3;
7 C1=(ton/Rs)*10^12;
8 printf(" suitable speed up capacitor is %dpF\n",C1)
9 C1=160*10^-12;//standard value
10 PWmin=(5*Rs*C1);
11 SWmin=5*Rb*C1;
12 fmax=1/(PWmin+SWmin);
13 printf("maximum signal frequency is %dHz\n",fmax)

```

---

### Scilab code Exa 8.9 Noise output voltage for an amplifier

```

1 //chapter 8
2 //example 8.9
3 //page 330
4 printf("\n")
5 printf("given")
6 R1=30*10^3;R2=30*10^3;rs=30*10^3;f2=40*10^3;f1=100;k
    =1.37*10^-23;R=10*10^3;Av=600;Ri=3*10^3;
7 Rb=(R1*R2)/(R1+R2);
8 Rg=(rs*Rb)/(rs+Rb);
9 T=(273+25)
10 B=f2-f1;
11 en=sqrt(4*k*T*B*R)
12 eni=en*((Ri/(Ri+Rg)))
13 eno=(Av*eni)*10^6;
14 printf(" noise output voltage is %duV\n",eno)

```

---

### Scilab code Exa 8.10 Noise and output voltage of transistor circuit

```

1 //chapter 8
2 //example 8.10

```

```
3 // page 331
4 printf("\n")
5 printf(" given")
6 Ic=30*10^-6; Vce=5; eno=354*10^-6;
7 NF=10;
8 F=2.51; //F=antilog(NF/10)
9 Vn=((sqrt(F))*eno)*10^6;
10 printf(" total noise output voltage for amplifier is
%duV\n", Vn)
```

---

### Scilab code Exa 8.11 Transistor Power dissipation

```
1 //chapter 8
2 //example 8.11
3 //page 333
4 printf("\n")
5 printf(" given")
6 Pd25=625*10^-3; D=5*10^-3; Vce=10;
7 T2=55;
8 Pdt2=Pd25-D*(T2-25)
9 Pd=Pdt2;
10 Ic=Pd/Vce;
11 printf(" maximum Ic level is %3.5fA\n", Ic)
```

---

### Scilab code Exa 8.13 Maximum power dissipation of 2N3055

```
1 //chapter 8
2 //example 8.13
3 //page 335
4 printf("\n")
5 printf(" given")
6 Pd=80;
7 Vce=60;
```

```
8 Ic=Pd/Vce
9 disp(" point 1 Vce=60 and Ic=1.3A")
10 Vce=40;
11 Ic=Pd/Vce
12 disp(" point 2 Vce=40 and Ic=2A")
13 Vce=20;
14 Ic=Pd/Vce
15 disp(" point 3 Vce=20 and Ic=4A")
16 Vce=10;
17 Ic=Pd/Vce
18 disp(" point 4 Vce=10 and Ic=8A")
```

---

### Scilab code Exa 8.14 Thermal resistance for heat sink

```
1 //chapter 8
2 //example 8.14
3 //page 339
4 printf("\n")
5 printf("given")
6 Vce=20; Ic=1; T2=90; T1=25;
7 Q=Vce*Ic;
8 Qcs=.4; Qjc=1; //from table
9 Qsa=((T2-T1)/Q)-(Qjc+Qcs)
```

---

# Chapter 10

## FET biasing

Scilab code Exa 10.1 DC load line using FET charecterstics

```
1 //chapter 10
2 //example 10.1
3 //page 381
4 printf("\n")
5 printf("given")
6 Vdd=22; Rd=2*10^3;
7 disp("when Id=0")
8 Id=0;
9 Vds=Vdd-Id*Rd
10 disp(" at point A Id=0 nad Vds=22")
11 Vds=0;
12 Id=Vdd/Rd
13 disp(" at point B Id=11mA and Vds=0")
```

---

Scilab code Exa 10.4 DC circuit analysis

```
1 //chapter 10
2 //example 10.4
```

```

3 // page 387
4 printf("\n")
5 printf(" given")
6 Idss=8*10^-3; Vpmax=6; Vgs=2.3; Vgsmax=6;
7 Id=Idss*(1-(Vgs/Vgsmax))^2
8 Idss=4*10^-3; Vp=3;
9 Idmin=Idss*(1-(Vgs/Vp))^2

```

---

### Scilab code Exa 10.6 DC Analysis of Voltage Divider Bias FET circuit

```

1 //chapter 10
2 //example 10.6
3 //page 393
4 printf("\n")
5 printf(" given")
6 Vdd=25; R2=1*10^6; R1=3.8*10^6; Rs=2.5*10^3; Rd
    =2.5*10^3;
7 Vg=(Vdd*R2)/(R1+R2)
8 disp(" when Id=0")
9 Id=0;
10 Vgs=Vg-Id*Rs
11 disp(" plot point A at Id=0 and Vgs=5.2")
12 Vgs=0;
13 Id=Vg/Rs
14 disp(" plot point B at Id=2.08mA and Vgs=0")
15 disp(" where the base line intersect the transfer
        characteristics")
16 Idmax=3*10^-3; Idmin=2.3*10^-3;
17 Vdsmin=Vdd-Idmax*(Rd+Rs)
18 Vdsmax=Vdd-Idmin*(Rd+Rs)

```

---

### Scilab code Exa 10.7 Transfer charecterstics of gate bais circuit

```
1 //chapter 10
2 //example 10.7
3 //page 401
4 printf("\n")
5 printf("given")
6 Id=3*10^-3; Vgs=-2.3; Vdsmin=10; Vdd=25; Vgsoff=-6; Idss
    =8*10^-3;
7 Vgs=Vgsoff*(1-sqrt(Id/Idss))
8 Rd=(Vdd-Vdsmin)/Id
```

---

#### Scilab code Exa 10.8 Designing a self bais circuit

```
1 //chapter 10
2 //example 10.8
3 //page 403
4 printf("\n")
5 printf("given")
6 Id=3*10^-3; Vds=10; Vdd=25; Vgs=2.3;
7 Rs=Vgs/Id
8 Rd=((Vdd-Vds)/Id)-Rs
```

---

#### Scilab code Exa 10.9 Designing a voltage divider bais circuit

```
1 //chapter 10
2 //example 10.9
3 //page 405
4 printf("\n")
5 printf("given")
6 Id=3*10^-3; Vds=10; Vdd=25; Vg=5.2; Vgsoff=-6; Idss
    =8*10^-3; R2=1*10^6;
7 R=(Vdd-Vds)/Id //R=(Rs+Rd)/2
8 Rd=R/2
9 Rs=Rd
```

---

```

10 Vgs=Id*Rs
11 Vgs=Vgsoff*(1-sqrt(Id/Idss))
12 Vs=Id*Rs
13 Vg=Vs-(-Vgs)
14 R1=((Vdd-Vg)*R2)/Vg

```

---

### Scilab code Exa 10.11 Designing a constant current bias circuit

```

1 //chapter 10
2 //example 10.11
3 //page 412
4 printf("\n")
5 printf("given")
6 Vee=20; Id=3*10^-3; Vds=9; Vbe=.7; Vb=0;
7 Ve=Vee-Vbe
8 Re=Ve/Id
9 Re=6.8*10^3; //satnadarad value
10 Id=Ve/Re;
11 Idss=16*10^-3; Vgsoff=-8;
12 Vgs=Vgsoff*(1-sqrt(Id/Idss))
13 Vs=Vb-Vgs
14 Vrd=Vee-Vds-Vs
15 Rd=Vrd/Id

```

---

### Scilab code Exa 10.12 Transfer characteristics of JFET

```

1 //chapter 10
2 //example 10.12
3 //page 415
4 printf("\n")
5 printf("given")
6 Idss=5*10^-3; Vgsoff=6; Rs=3.3*10^3; Vdd=20; Rd=Rs;
7 disp("when Id=0, Vgs=Vs=0")

```

```

8 Id=0; Vgs=0; Vs=0;
9 disp(" at point A universal transfer characteristic
      Id/Idss and Vgs/Vgsoff=0")
10 Id=1.5*10^-3;
11 Vgs=Id*Rs
12 y=Id/Idss;
13 x=Vgs/Vgsoff;
14 disp(" point B the universal transfer characteristic
      x=.825 and y=.3")
15 Id=.2*Idss
16 Vds=Vdd-Id*(Rd+Rs)

```

---

### Scilab code Exa 10.13 FET universal transfer characteristics

```

1 //chapter 10
2 //example 10.13
3 //page 416
4 printf("\n")
5 printf("given")
6 Idss=9*10^-3; Vgsoff=7; Vdd=22; R1=4.7*10^6; R2=1*10^6;
   Rs=2.7*10^3; Rd=Rs;
7 Vg=(Vdd*R2)/(R1+R2)
8 disp("when Vgs=0, Vgs/Vgsoff=0")
9 Id=Vg/Rs
10 disp("when Vgs/Vgsoff=.5")
11 Vgs=.5*(-Vgsoff)
12 Id=(Vg-Vgs)/Rs
13 x=Id/Idss
14 disp(" point Y on universal characteristic x=.3 and
      Vgs/Vgsoff=.5")
15 disp("draw voltage divider bias line through X nad Y
      where bisa line intersect transfer curve")
16 Id=.29*Idss
17 Vds=Vdd-Id*(Rd+Rs)

```

---

### Scilab code Exa 10.14 Transfer characteristics of MOSFET

```
1 //chapter 10
2 //example 10.14
3 //page 419
4 printf("\n")
5 printf("given")
6 Vdd=40;R2=1*10^6;R1=5.6*10^6;Rd=4.7;
7 Vg=(Vdd*R2)/(R1+R2)
8 disp("from the point where the bias line intersect
      the transfer curve")
9 Id=6.2
10 Vds=Vdd-Id*Rd
```

---

### Scilab code Exa 10.16 Biasing JFET switching circuit

```
1 //chapter 10
2 //example 10.16
3 //page 422
4 printf("\n")
5 printf("given")
6 rDS=25;Vgsoff=10;Vds=200*10^-3;Vdd=12;
7 Id=Vds/rDS
8 Rd=Vdd/Id
9 Vi=-(Vgsoff+1)
```

---

### Scilab code Exa 10.17 Transfer characteristics of MOSFET in switching bias

```
1 //chapter 10
```

```
2 //example 10.17
3 //page 424
4 printf("\n")
5 printf("given")
6 Vdd=50; Rd=10; R2=1*10^6; rDS=.25;
7 Id=Vdd/Rd
8 disp(" from transfer curve at Id=5 and Vgs=5.7")
9 Vgs=5.7;
10 R1=((Vdd-Vgs)*R2)/Vgs //use 6.8Mohm to make Vgs>5.7V
    to ensure that the FET is biased on
11 Vds=Id*rDS
```

---

# Chapter 11

## AC Analysis of FET circuits

Scilab code Exa 11.2 CS circuit performance parameters

```
1 //chapter 11
2 //example 11.2
3 //page 443
4 printf("\n")
5 printf("given")
6 Yos=10*10^-6; Yfs=3000*10^-6; R1=1*10^6; R2=5.6*10^6; Rd
    =2.7*10^3; Rl=Rd;
7 rd=1/Yos
8 Zi=((R1*R2)/(R1+R2))*10^-3;
9 printf("input impedance is %dKohm\n", Zi)
10 Zo=(Rd*rd)/(Rd+rd);
11 printf(" output impedance is %dohm\n", Zo)
12 Av=-Yfs*((Rl*rd)/(Rl+rd))
```

---

Scilab code Exa 11.3 Performance parameters of CS circuit with Unbypassed source r

```
1 //chapter 11
2 //example 11.3
```

```

3 //page 447
4 printf("\n")
5 printf("given")
6 Yos=10*10^-6; Yfs=4000*10^-6; Ig=1*10^-9; Vgs=15; Rs
    =3.3*10^3; Rg=1*10^6; Rd=4.7*10^3; Rl=33*10^3;
7 rd=1/Yos
8 Rgs=(Vgs/Ig)
9 Zg=(Rgs*(1+Yfs*Rs))
10 Zi=Rg;
11 Zd=rd+Rs+(Yfs*Rs*rd)
12 Zo=(Rd*Zd)/(Rd+Zd)
13 Av=-(Yfs*((Rd*Rl)/(Rd+Rl)))/(1+Yfs*Rs)
14 Av=-((Rd*Rl)/(Rd+Rl))/Rs

```

---

#### Scilab code Exa 11.4 Common Drain circuit analysis

```

1 //chapter 11
2 //example 11.4
3 //page 451
4 printf("\n")
5 printf("given")
6 Yfs=3000*10^-6; Rgs=100*10^6; rd=50*10^3; Rs=5.6*10^3;
    Rl=12*10^3; R1=1.5*10^6; R2=1*10^6;
7 Zg=Rgs*(1+Yfs*((Rs*Rl)/(Rs+Rl)))
8 Zi=(R1*R2)/(R1+R2)
9 Zs=((1/Yfs)*rd)/((1/Yfs)+rd)
10 Zo=(Rs*Rl*(1/Yfs))/(Rs*Rl+Rs*(1/Yfs)+Rl*(1/Yfs))
11 Av=-(Yfs*((Rs*Rl)/(Rs+Rl)))/(1+Yfs*((Rs*Rl)/(Rs+Rl)))
    )

```

---

#### Scilab code Exa 11.5 Common Gate circuit analysis

```
1 //chapter 11
```

```

2 //example 11.5
3 //page 456
4 printf("\n")
5 printf(" given")
6 Yfs=3000*10^-6; rd=50*10^3; Rs=3.3*10^3; Rd=4.7*10^3; Rl
    =50*10^3; rs=600;
7 Zs=1/Yfs
8 Zi=((1/Yfs)*Rs)/((1/Yfs)+Rs)
9 Zd=rd
10 Zo=(Rd*rd)/(Rd+rd)
11 Av=Yfs*((Rd*Rl)/(Rd+Rl))
12 disp(" overall volatge gain")
13 Av=(Yfs*((Rd*Rl)/(Rd+Rl))*Zi)/(rs+Zi)

```

---

**Scilab code Exa 11.6 AC output voltage with and without bypassed source resistor**

```

1 //chapter 11
2 //example 11.6
3 //page 459
4 printf("\n")
5 printf(" given")
6 Yfs=6000*10^-6; R1=100*10^3; R2=47*10^3; vs=50*10^-3; Rd
    =2.7*10^3; Rl=33*10^3; vs=50*10^-3; rs=600; Rs=Rd;
7 disp(" CS circuit")
8 Av=-Yfs*((Rd*Rl)/(Rd+Rl))
9 Zi=(R1*R2)/(R1+R2)
10 vi=(vs*Zi)/(rs+Zi)
11 vo=Av*vi
12 disp("CG circuit")
13 Av=Yfs*((Rd*Rl)/(Rd+Rl))
14 Zi=((1/Yfs)*Rs)/((1/Yfs)+Rs)
15 vi=(vs*Zi)/(rs+Zi)
16 vo=Av*vi

```

---

**Scilab code Exa 11.7** Input capacitance limited cutoff frequency for a CS circuit

```
1 //chapter 11
2 //example 11.7
3 //page 462
4 printf("\n")
5 printf("given")
6 Crss=1*10^-12; Ciss=5*10^-12; Yfs=2500*10^-6; Yos
    =75*10^-6; Rd=5.6*10^3; Rl=100*10^3; R1=3.3*10^6; R2
    =1*10^6; rs=600;
7 Cgd=Crss;
8 Cgs=Ciss-Crss
9 Av=Yfs*(((1/Yos)*Rd*Rl))/((Rd*Rl+(1/Yos)*Rd+(1/Yos)*
    Rl))
10 Cin=Cgs+(1+Av)*Cgd
11 Zi=(R1*R2)/(R1+R2)
12 f2=1/(2*3.14*Cin*((rs*Zi)/(rs+Zi)))
```

---

# Chapter 12

## Small signal Amplifiers

Scilab code Exa 12.1 Required capacitance and voltage gain at different frequencies

```
1 //chapter 12
2 //example 12.1
3 //page 474
4 printf("\n")
5 printf("given")
6 hfe=50; hie=1*10^3; hib=20; f1=100; Rc=3.3*10^3; Re=Rc;
7 disp(" required capacitance")
8 Xc2=hib;
9 C2=1/(2*3.14*f1*Xc2)
10 disp(" voltage gain with emitter terminal completely
      bypassed to ground")
11 Av=-(hfe*Rc)/hie
12 disp(" voltage gain when f=100")
13 Av=-(hfe*Rc)/sqrt(((hie^2)+((1+hfe)*Xc2)^2))
14 disp(" voltage gain when C2 is incorrectly selected
      as Xc2=Re/10")
15 Avx=-(hfe*Rc)/sqrt(((hie^2)+((1+hfe)*(Re/10))^2))
```

---

Scilab code Exa 12.2 Suitable resistor values for common emitter amplifier

```

1 //chapter 12
2 //example 12.2
3 //page 477
4 printf("\n")
5 printf("given")
6 Vcc=24; Ve=5; Vce=3; Rl=120*10^3; Vbe=.7
7 Rc=Rl/10
8 Vrc=Vcc-Vce-Ve
9 Ic=Vrc/Rc
10 Re=Ve/Ic//use 3.9Kohm standard value to make Ic
    littel less than design level
11 Re=3.9*10^3;
12 R2=10*Re
13 I2=(Ve+Vbe)/R2
14 R1=(Vcc-Ve-Vbe)/I2

```

---

### Scilab code Exa 12.3 Suitable capacitor for CE amplifier circuit

```

1 //chapter 12
2 //example 12.3
3 //page 477
4 printf("\n")
5 printf("given")
6 hfe=100; Ie=1.3*10^-3; f1=100; R1=120*10^3; R2=39*10^3;
    rs=600; Rl=R1;
7 re=(26*10^-3)/Ie
8 Xc2=re;
9 C2=1/(2*3.14*f1*Xc2)
10 hie=(1+hfe)*re
11 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
12 C1=1/((2*3.14*f1*((Zi+rs)/10)))
13 C3=1/(2*3.14*f1*((Rc+Rl)/10))

```

---

**Scilab code Exa 12.4 Suitable resistor for common source circuit**

```
1 //chapter 12
2 //example 12.5
3 //page 485
4 printf("\n")
5 printf("given")
6 rs=600; f1=100; Yfs=6000*10^-6; R1=4.7*10^6; R2=1*10^6;
   Rd=6.8*10^3; Rl=120*10^3;
7 Xc2=1/Yfs
8 C2=1/(2*3.14*f1*Xc2)
9 Zi=(R1*R2)/(R1+R2)
10 C1=1/(2*3.14*f1*(Zi+rs)/10)
11 C3=1/(2*3.14*f1*(Rd+Rl)/10)
```

---

**Scilab code Exa 12.5 Suitable resistor for common source amplifier**

```
1 //chapter 12
2 //example 12.5
3 //page 485
4 printf("\n")
5 printf("given")
6 rs=600; f1=100; Yfs=6000*10^-6; R1=4.7*10^6; R2=1*10^6;
   Rd=6.8*10^3; Rl=120*10^3;
7 Xc2=1/Yfs
8 C2=1/(2*3.14*f1*Xc2)
9 Zi=(R1*R2)/(R1+R2)
10 C1=1/(2*3.14*f1*(Zi+rs)/10)
11 C3=1/(2*3.14*f1*(Rd+Rl)/10)
```

---

**Scilab code Exa 12.7 Analysis of two stage amplifier**

```
1 //chapter 12
```

```

2 //example 12.7
3 //page 489
4 printf("\n")
5 printf(" given")
6 R1=120*10^3;R2=39*10^3;hie=2*10^3;R7=12*10^3;Zo=R7;
    R5=R1;R6=R2;hfe=100;R3=R7;Zl=R1;
7 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
8 Zi2=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
9 Av1=-(hfe*((R3*Zi2)/(R3+Zi2)))/hie
10 Av2=-(hfe*((R7*Zl)/(R7+Zl)))/hie
11 Av=Av1*Av2

```

---

### Scilab code Exa 12.8 Analysis of direct coupled two stage amplifier

```

1 //chapter 12
2 //example 12.8
3 //page 491
4 printf("\n")
5 printf(" given")
6 Ve1=5;Vce1=3;Vce2=3;Vbe=.7;Vcc=14;Rl=40*10^3;
7 Vb2=Ve1+Vce1
8 Vc1=Vb2;
9 Ve2=Vb2-Vbe
10 Vr5=Vcc-Ve2-Vce2
11 R5=Rl/10 //use 3.9Kohm satandard value
12 R5=3.9*10^3;
13 Ic2=Vr5/R5
14 R6=Ve2/Ic2 //use 8.2Kohm as standard and recalculate
15 R6=8.2*10^3;
16 Ic2=Ve2/R6
17 Vr3=Vcc-Vc1
18 disp(" Ic1>>Ib2 , select Ic1=1mA")
19 Ic1=1*10^-3;
20 R3=Vr3/Ic1 //use standard value as 5.6Kohm and
    recalculate Ic1 in order ti keep Vb2=8V

```

```
21 R3=5.6*10^3;
22 Ic1=Vr3/R3
23 R4=Ve1/Ic1
24 Vr2=Ve1+Vbe
25 Vr1=Vcc-Ve1-Vbe
26 R2=10*R4
27 I2=(Ve1+Vbe)/R2
28 R1=(Vr1*R2)/Vr2
```

---

Scilab code Exa 12.9 capacitor for two stage direct coupled amplifier

```
1 //chapter 12
2 //example 12.9
3 //page 493
4 printf("\n")
5 printf("given")
6 hfe=50; re=26; R1=68*10^3; R2=47*10^3; rs=600; f1=75; R5
    =3.9*10^3; Rl=40*10^3;
7 hie=(1+hfe)*re
8 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
9 Xc1=(Zi+rs)/10
10 C1=1/(2*3.14*f1*Xc1)
11 Xc2=.65*re
12 Xc3=Xc2;
13 C2=1/(2*3.14*f1*Xc2)
14 C3=C2;
15 Xc4=(R5+Rl)/10
16 C4=1/(2*3.14*f1*Xc4)
```

---

Scilab code Exa 12.10 Minimum overall voltage gain for direct coupled CE amplifier

```
1 //chapter 12
2 //example 12.10
```

```

3 //page 494
4 printf("\n")
5 printf(" given")
6 hfe=50; hie=1.3*10^3; R3=5.6*10^3; R5=3.9*10^3; Rl
    =40*10^3;
7 Av1=-(hfe*((R3*hie)/(R3+hie)))/hie
8 Av2=-(hfe*((R5*Rl)/(R5+Rl)))/hie
9 disp(" overall voltage gain is Av=Av1*Av2")
10 Av=Av1*Av2

```

---

### Scilab code Exa 12.11 CE input and CC output two stage amplifier analysis

```

1 //chapter 12
2 //example 12.11
3 //page 497
4 printf("\n")
5 printf(" given")
6 Vp=100*10^-3; Rl=100; Vbe=.7; Vcc=20;
7 ip=Vp/Rl
8 disp(" select Ie2>ip")
9 Ie2=2*10^-3;
10 Ve1=5; Vce1=3;
11 Vb2=Ve1+Vce1
12 Vc1=Vb2;
13 Ve2=Vb2-Vbe;
14 Vr2=Ve1+Vbe;
15 R5=Ve2/Ie2 //use 3.3Kohm standard value
16 R5=3.3*10^3;
17 Ic1=1*10^-3;
18 Vr3=Vcc-Vb2
19 R3=Vr3/Ic1
20 R4=Ve1/Ic1 //use 4.7Kohm standard value
21 R4=4.7*10^3;
22 Vb1=Ic1*R4+Vbe
23 R2=10*R4

```

24  $R_1 = ((V_{CC} - V_{b1}) * R_2) / V_{r2}$

---

### Scilab code Exa 12.12 Suitable capacitor for circuit

```
1 //chapter 12
2 //example 12.11
3 //page 498
4 printf("\n")
5 printf("given")
6 rs=600; Ie1=1*10^-3; hfe=50; R1=120*10^3; R2=47*10^3; f1
    =150; Ie2=2*10^-3; R5=3.3*10^3; R3=12*10^3; Rl=100;
7 re=26*10^-3/Ie1
8 hie=(1+hfe)*re
9 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
10 Xc1=(Zi+rs)/10
11 C1=1/(2*3.14*f1*Xc1) //use 6*10^-6 as standard value
12 Xc2=.65*re
13 C2=1/(2*3.14*f1*Xc2)
14 re2=26*10^-3/Ie2
15 Zo=(R5*(re2+R3/hfe))/(R5+(re2+R3/hfe))
16 Xc3=.65*(Rl+Zo)
17 C3=1/(2*3.14*f1*Xc3)
```

---

### Scilab code Exa 12.13 analyze two stage amplifier and determine minimum voltage ga

```
1 //chapter 12
2 //example 12.13
3 //page 499
4 printf("\n")
5 printf("given")
6 Ie2=2*10^-3; hfe=50; R5=3.3*10^3; Rl=100; hfc2=51; R3
    =12*10^3;
7 re=26*10^-3/Ie2
```

```

8 hic=hfe*re;
9 hie=2*(1+hfe)*re
10 Zi2=hic+hfc2*((Rl*R5)/(Rl+R5))
11 Av1=-(hfe*((R3*Zi2)/(R3+Zi2)))/hie
12 Av2=1
13 disp(" overall voltage gain is Av=Av1*Av2")
14 Av=Av1*Av2

```

---

### Scilab code Exa 12.14 Dc feedback pair with an emitter follower output

```

1 //chapter 12
2 //example 12.14
3 //page 503
4 printf("\n")
5 printf("given")
6 vp=50*10^-3; R1=50; Ve2=5; Vcc=12; Vbe=.7; hFE=70; hfe
    =100; R2=120*10^3; f1=150; R3=150*10^3; R1=5.6*10^3;
    R4=2.2*10^3;
7 ip=vp/R1
8 disp(" select Ie2>ip")
9 Ie2=2*10^-3;
10 R4=Ve2/Ie2//use standard 2.2Kohm
11 R4=2.2*10^3;
12 Ie2=Ve2/R4
13 Ic1=1*10^-3;
14 Vr1=Vcc-(Vbe+Ve2)
15 R1=Vr1/Ic1//use 5.6kohm and recalculate
16 R1=5.6*10^3;
17 Ic1=Vr1/R1
18 Ib1=Ic1/hFE
19 hie=hfe*(26*10^-3/Ic1)
20 hie2=hfe*((26*10^-3)/(2.27*10^-3))
21 Zi1=(R2*hie)/(R2+hie)
22 Xc1=Zi1/10
23 C1=1/(2*3.14*f1*Xc1)

```

```
24 Xc2=R3/100
25 C2=1/(2*3.14*f1*Xc2)
26 Zo=((hie2+R1)/hfe)*R4)/(((hie2+R1)/hfe)+R4)
27 Xc3=R1+Zo
28 C3=1/(2*3.14*f1*Xc3)
```

---

### Scilab code Exa 12.15 suitable resistor for BIBET amplifier

```
1 //chapter 12
2 //example 12.15
3 //page 407
4 printf("\n")
5 printf("given")
6 Vgsoff=-6; Idss=20*10^-3; Yfs=4000*10^-6; Id=2*10^-3;
    Vcc=20; Zi=500*10^3; R2=560*10^3; Rl=80*10^3; Vbe=.7;
    Vce=3;
7 Vgs=Vgsoff*(1-sqrt(Id/Idss))
8 Vds=(-Vgsoff)+1-(-Vgs)
9 Vr3=(Vcc-Vds)/2
10 Vr4=Vr3;
11 R3=Vr4/Id//use 3.9kohm as standard and recalculate
    Vr3 and Vr4
12 R4=R3;
13 R4=3.9*10^3;
14 Vr3=Id*R4
15 Vr4=Vr3;
16 Vr2=Vr4-(-Vgs)
17 Vr1=Vcc-Vr2
18 R1=(Vr1*R2)/Vr2
19 R6=R1/10
20 Vr5=Vr3-Vbe
21 Vr6=Vcc-Vr5-Vce
22 Ic2=Vr6/R6
23 R5=Vr5/Ic2
```

---

### Scilab code Exa 12.16 suitable capacitor For BIFET direct coupled amplifier

```
1 //chapter 12
2 //example 12.16
3 //page 508
4 printf("\n")
5 printf("given")
6 R1=2.7*10^6;R2=560*10^3;f1=150;Yfs=8000*10^-6;Ie
    =1.2*10^-3;Rl=80*10^3;R6=8.2*10^3;
7 Zi=(R1*R2)/(R1+R2)
8 Xc1=Zi/10
9 C1=1/(2*3.14*f1*Xc1)
10 Xc2=.65/Yfs
11 C2=1/(2*3.14*f1*Xc2) //use 15pF as standard value
12 re=26*10^-3/Ie
13 Xc3=.65*re
14 C3=1/(2*3.14*f1*Xc3)
15 Xc4=(R6+R1)/10
16 C4=1/(2*3.14*f1*Xc4)
```

---

### Scilab code Exa 12.17 determine minimum overall voltage gain

```
1 //chapter 12
2 //example 12.17
3 //page 509
4 printf("\n")
5 printf("given")
6 re=22;hfe=100;R3=3.9*10^3;Yfs=4000*10^-6;R6
    =8.2*10^3;Rl=80*10^3;
7 Zi2=hfe*re
8 Av1=-Yfs*((R3*Zi2)/(R3+Zi2))
9 Av2=-(hfe*((R6*Rl)/(R6+Rl)))/Zi2
```

```
10 disp(" overall voltage is Av=Av1*Av2")
11 Av=Av1*Av2
```

---

### Scilab code Exa 12.18 suitable resistor for differential amplifier

```
1 //chapter 12
2 //example 12.18
3 //page 516
4 printf("\n")
5 printf("given")
6 hFE=60; hfe=60; hie=1.4*10^3; Rl=70*10^3; Vce=3; Vbe=.7;
    Vcc=10;
7 Rc2=Rl/10 //use 6.8Kohm as standard value
8 Vrc2=Vcc+Vbe-Vce
9 Ic=Vrc2/Rc2
10 Ie=Ic;
11 Re=(Vcc-Vbe)/(2*Ie) //use 4.7 as standard value
12 Re=4.7*10^3;
13 Rb=Vbe/(10*(Ic/hFE))
14 Rb1=Rb;
```

---

### Scilab code Exa 12.19 suitable capacitor value for amplifier and voltage gain

```
1 //chapter 12
2 //example 12.19
3 //page 517
4 printf("\n")
5 printf("given")
6 f1=60; Ie=1.13*10^-3; hfe=60; Rb=3.9*10^3; Rl=70*10^3; Rc
    =6.8*10^3;
7 re=26*10^-3/Ie //use 20 as standard value
8 re=20;
9 hie=hfe*re
```

```
10 Zb=2*hie
11 Zi=(Rb*Zb)/(Rb+Zb)
12 C1=1/(2*3.14*f1*Zi)
13 C2=1/(2*3.14*f1*(Rl/10))
14 Av=(hfe*((Rc*Rl)/(Rc+Rl)))/(2*hie)
```

---

### Scilab code Exa 12.20 suitable resistor for cascode amplifier

```
1 //chapter 12
2 //example 12.20
3 //page 521
4 printf("\n")
5 printf("given")
6 Vcc=20; Rl=90*10^3; hfe=50; hie=1.2*10^3; hib=24; Vce=3;
    Vce1=Vce; Ve=5; Vbe=.7;
7 Rc=Rl/10 //use 8.2kohm as standard value
8 Rc=8.2*10^3;
9 Vrc=Vcc-Vce-Vce1-Ve
10 Ic=Vrc/Rc
11 Re=Ve/Ic
12 Re=4.7*10^3; //use 4.7 as standard value
13 R3=10*Re
14 Vb1=Ve+Vbe
15 I3=Vb1/R3
16 Vb2=Ve+Vce+Vbe
17 Vr2=Vb2-Vb1
18 R2=Vr2/I3
19 R1=(Vcc-Vb2)/I3
```

---

### Scilab code Exa 12.21 suitable capacitor for cascode circuit

```
1 //chapter 12
2 //example 12.21
```

```

3 //page 522
4 printf("\n")
5 printf("given")
6 f1=25; R2=24.7*10^3; R3=47*10^3; hie=1.2*10^3; hib=24; Rc
=9*10^3; Rl=90*10^3;
7 Zi=(R2*R3*hie)/(R2*R3+R2*hie+R3*hie)
8 C1=1/(2*3.14*f1*(Zi/10))
9 C2=1/(2*3.14*f1*(hie/10))
10 C3=1/(2*3.14*f1*hib)
11 C4=1/(2*3.14*f1*((Rc+Rl)/10))

```

---

**Scilab code Exa 12.22 resonance frequency, voltage gain, bandwidth of amplifier**

```

1 //chapter 12
2 //example 12.22
3 //page 525
4 printf("\n")
5 printf("given")
6 hie=1*10^3; hfe=50; hoe=10*10^-6; Cc=5*10^-12; Cp
=330*10^-12; Lp=75*10^-6; Rw=1; Rl=5*10^3; hfb=50; fo
=1*10^6;
7 fo=1/(2*3.14*sqrt(Lp*(Cp+Cc)))
8 printf("resonance frequency is %3fHz\n", fo)
9 Zp=Lp/((Cp+Cc)*Rw)
10 Rc=1/hoe
11 RL=(Zp*Rc*Rl)/(Rl*Rc+Rc*Zp+Rl*Zp);
12 RL=4.7*10^3; //as standard value
13 Av=(hfb*RL)/hie;
14 printf("voltage gain is %d\n", Av)
15 Qp=((Rc*Rl)/(Rc+Rl))/(2*3.14*fo*Lp)
16 QL=(2*3.14*fo*Lp)/Rw
17 disp("since QL>Qp")
18 B=fo/Qp;
19 printf("bandwidth is %dHz\n", B)

```

---

### Scilab code Exa 12.23 Determination of resonance frequency, voltage gain, bandwidth

```
1 //chapter 12
2 //example 12.23
3 //page 528
4 printf("\n")
5 printf("given")
6 hie=1*10^3; hfe=50; hoe=10*10^-6; Cc=5*10^-12; Cp
    =330*10^-12; Lp=75*10^-6; Rw=1; Rl=5*10^3; fo=1*10^6;
    K=.015; Ls=50*10^-6;
7 Zp=Lp/((Cp+Cc)*Rw);
8 Rc=(1.0/hoe)/1000;
9 RL=(Zp*Rc)/(Rc+Zp)
10 disp("voltage gain from the input to the primary
        memory winding")
11 Avp=(hfe*RL)/hie
12 Vsp=K*sqrt(Ls/Lp)
13 disp("overall voltage gain from the input to the
        secondary winding")
14 Av=Avp*Vsp
15 Qp=Rc/(2*3.14*fo*Lp)
16 Ql=471;
17 Q=(Ql*Qp)/(Ql+Qp)
18 B=fo/Q;
19 printf("bandwidth is %dHz\n",B)
```

---

### Scilab code Exa 12.24 capacitor required to resonate the secondary and overall vol

```
1 //chapter 12
2 //example 12.24
3 //page 530
4 printf("\n")
```

```

5 printf("given")
6 f=1*10^6;L2=50*10^-6;K=.015;L1=75*10^-6;rs=5;Rw=1;Lp
    =100*10^-6;Cp=330*10^-12;Cc=5*10^-12;Rc=100*10^3;
    hfe=50;hie=1*10^3;
7 C2=1/(((2*3.14*f)^2)*L2)
8 M=K*sqrt(L1*L2)
9 Rs=((2*3.14*f)^2)*(M)^2/rs
10 Rp=Rs+Rw
11 Zp=Lp/((Cp+Cc)*Rp)
12 Rl=(Zp*Rc)/(Zp+Rc)
13 disp("voltage gain from the input to primary winding
      ")
14 Avp=(hfe*Rl)/hie
15 Vsp=12.2*10^-3;
16 Vos=((2*3.14*f)*L2)/rs
17 disp("overall voltage gain from the input to
      secondary winding ")
18 Av=Avp*Vos*Vsp

```

---

# Chapter 13

## Amplifier with negative feedback

Scilab code Exa 13.1 closed loop gain for negative feedback amplifier

```
1 //chapter 13
2 //example 13.1
3 //page 547
4 printf("\n")
5 printf("given")
6 Av=100000;B=1/100;
7 disp("when Av=100000")
8 Acl=Av/(1+Av*B)
9 disp("when Av is 150000")
10 Av=150000;
11 Acl=Av/(1+Av*B)
12 disp("when Av is 50000")
13 Av=50000;
14 Acl=Av/(1+Av*B)
```

---

Scilab code Exa 13.2 input impedance with negative feedback

```

1 //chapter 13
2 //example 13.2
3 //page 549
4 printf("\n")
5 printf("given")
6 Rf2=560; Rf1=56*10^3; Av=100000; Zb=1*10^3; R1=68*10^3;
    R2=33*10^3;
7 B=Rf2/(Rf2+Rf1)
8 Zi=(1+Av*B)*Zb
9 Zin=(Zi*R1*R2)/(R1*R2+R1*Zi+R2*Zi);
10 printf("input impedance with negative feedback is
    %dohm\n", Zin)

```

---

**Scilab code Exa 13.3** input and output impedance when negative feedback

```

1 //chapter 13
2 //example 13.3
3 //page 552
4 printf("\n")
5 printf("given")
6 Zb=1*10^3; B=1/100; Av=5562; R1=68*10^3; R2=47*10^3; hoe
    =1/(50*10^3); Rc=3.9*10^3;
7 Zi=(1+Av*B)*Zb
8 Zin=(R1*R2*Zi)/(R1*R2+R2*Zi+R1*Zi)
9 Zo=(1/hoe)/(1+Av*B)
10 Zout=(Rc*Zo)/(Rc+Zo);
11 printf(" circuit output impedance is %dohm\n", Zout)

```

---

**Scilab code Exa 13.4** circuit input and output impedance and voltage gain without f

```

1 //chapter 13
2 //example 13.4
3 //page 554

```

```
4 printf("\n")
5 printf("given")
6 Zb=1*10^3; hoe=1/(85*10^3); Av=58000; Rf2=220; Rf1
    =16.2*10^3; R1=120*10^3; R2=39*10^3; R7=12*10^3;
7 B=Rf2/(Rf2+Rf1)
8 disp(" voltage gain")
9 Acl=Av/(1+Av*B)
10 Zi=Zb*(1+Av*B)
11 Zin=(Zi*R1*R2)/(Zi*R1+R2*R1+R2*Zi)
12 Zo=(1/hoe)/(1+Av*B)
13 Zout=(R7*Zo)/(R7+Zo)
14 printf("output impedance is %dohm\n", Zout)
```

---

**Scilab code Exa 13.5 two stage coupled BJT use as voltage feedback**

```
1 //chapter 13
2 //example 13.5
3 //page 558
4 printf("\n")
5 printf("given")
6 Rf2=220; R4=3.9*10^3; Acl=75; f=100;
7 Rf1=(Acl-1)*Rf2
8 Xc2=Rf2;
9 C2=1/(2*3.14*f*Rf2)
10 Xcf1=Rf1/100;
11 Cf1=1/(2*3.14*f*Xcf1)
```

---

**Scilab code Exa 13.6 modify direct coupled amplifier to use as series voltage nega**

```
1 //chapter 13
2 //example 13.6
3 //page 560
4 printf("\n")
```

```
5 printf("given")
6 Acl=300;Rf2=220;R4=4.7*10^3;f=100;
7 Rf1=(Acl-1)*Rf2
8 xc2=Rf2;
9 C2=1/(2*3.14*f*Rf2)
```

---

### Scilab code Exa 13.7 calculate resistor value

```
1 //chapter 13
2 //example 13.7
3 //page 565
4 printf("\n")
5 printf("given")
6 hfe=100;Vbe=.7;Ic1=1*10^-3;Ic2=Ic1;Ic3=Ic2;Ic4=Ic3;
    Vee=10;Vce=3;Acl=33;
7 disp("different resistor value of circuit")
8 R1=Vbe/((10*Ic1)/hfe)
9 R3=(Vee-Vbe)/(Ic1+Ic2)
10 Vr2=Vee+Vbe-Vce
11 R4=Vr2/Ic1
12 R2=R4;
13 R7=(Vr2-Vbe)/(Ic3+Ic4)
14 R8=Vee/Ic3
15 R6=6.8*10^3;
16 R5=(Acl-1)*R6
```

---

### Scilab code Exa 13.8 calculate Acm, Zin and Zout

```
1 //chapter 13
2 //example 13.8
3 //page 566
4 printf("\n")
5 printf("given")
```

```

6 Av=25000;hie=2*10^3;hib=25;hoe=1/(100*10^3);R6
    =6.8*10^3;R5=220*10^3;R1=R6;R8=10*10^3;
7 B=R6/(R5+R6)
8 Acl=Av/(1+Av*B)
9 Zi=2*hie*(1+Av*B)
10 Zin=(Zi*R1)/(Zi+R1)
11 Zo=(1/hoe)/(1+Av*B)
12 Zout=(R8*Zo)/(R8+Zo);
13 printf("output impedance is %dohm\n",Zout)

```

---

**Scilab code Exa 13.9 calculate output impedance for circuit modification**

```

1 //chapter 13
2 //example 13.9
3 //page 568
4 printf("\n")
5 printf("given")
6 hic=2*10^3;hie=hic;hfe=100;hfc=100;Av=25000;B
    =1/33.4;R8=10*10^3;R5=R8;
7 Ze=(hic+R8)/hfc
8 Zo=Ze/(1+Av*B)
9 Zout=(R5*Zo)/(R5+Zo);
10 printf("output impedance is %3.2f ohm\n",Zout)

```

---

**Scilab code Exa 13.10 calculate precise value of circuit voltage gain**

```

1 //chapter 13
2 //example 13.10
3 //page 570
4 printf("\n")
5 printf("given")
6 hfemin=100;hfemax=400;hiemin=2*10^3;hiemax=5*10^3;Rc
    =12*10^3;R1=120*10^3;Re1=150

```

```

7 disp(" voltage gain at extreme value ")
8 Avmax=(hfemax*((Rc*Rl)/(Rc+Rl)))/(hiemax+Re1*(1+
    hfemax))
9 Avmin=(hfemin*((Rc*Rl)/(Rc+Rl)))/(hiemin+Re1*(1+
    hfemin))
10 disp("approximate voltage gain")
11 Av=((Rc*Rl)/(Rc+Rl))/Re1

```

---

**Scilab code Exa 13.11** modify CE amplifier to use emitter current feedback to give

```

1 //chapter 13
2 //example 13.11
3 //page 571
4 printf("\n")
5 printf("given")
6 Av=70;f=100;rs=600;Rc=12*10^3;Rl=120*10^3;Re2
    =3.9*10^3;hie=2*10^3;hfe=100;R1=Rl;R2=39*10^3;Re1
    =150;
7 Zb=hie+Re1*(1+hfe)
8 Zin=(R1*R2*Zb)/(R1*R2+R1*Zb+R2*Zb)
9 C1=1/(2*3.14*f*((Zin+rs)/10))
10 C2=1/(2*3.14*f*Re1)

```

---

**Scilab code Exa 13.12** suitable emitter resistor value

```

1 //chapter 13
2 //example 13.12
3 //page 573
4 printf("\n")
5 printf("given")
6 Av=1000;f=100;hie=2*10^3;hfe=100;R8=12*10^3;Rl
    =120*10^3;R10=3.9*10^3;R6=R1;R7=39*10^3;R3=R8;
7 Av1=sqrt(Av)

```

```
8 Av2=Av1;
9 R9=((R8*R1)/(R8+R1))/Av2
10 R9=330; //use standard value
11 Av2=((R8*R1)/(R8+R1))/R9
12 Av1=Av/Av2
13 Zb=hie+R9*(1+hfe)
14 Zin=(R6*R7*Zb)/(R6*R7+R6*Zb+R7*Zb)
15 R4=((R3*Zin)/(R3+Zin))/Av1
16 R5=R10-R4
```

---

### Scilab code Exa 13.13 suitable capacitor for two stage circuit

```
1 //chapter 13
2 //example 13.13
3 //page 574
4 printf("\n")
5 printf("given")
6 f=100; hie=2*10^3; hfe=100; R8=12*10^3; R1=120*10^3; R10
    =3.9*10^3; R6=R1; R7=39*10^3; R3=R8; R4=220; rs=600;
    Zin2=16*10^3; R9=330; R1=R1
7 R2=39.0*10^3;
8 Zb=hie+R4*(1+hfe)
9 Zin=(R1*R2*Zb)/(R1*R2+R1*Zb+R2*Zb)
10 C1=1/(2*3.14*f*((Zin+rs)/10))
11 Xc2=.65*R4;
12 C2=1/(2*3.14*f*Xc2)
13 C3=1/(2*3.14*f*((Zin2+R3)/10))
14 C4=1/(2*3.14*f*.65*R9)
15 C5=1/(2*3.14*f*((R8+R1)/10))
```

---

### Scilab code Exa 13.14 determine current gain and input impedance

```
1 //chapter 13
```

```
2 //example 13.14
3 //page 580
4 printf("\n")
5 printf(" given")
6 hfe=100;hie=2*10^3;R4=100;R1=5.6*10^3;R6=2.2*10^3;
7 Zi=hie+(1+hfe)*R4
8 disp("open loop current gain")
9 Ai=(hfe*hfe*R1)/(R1+Zi)
10 B=R4/(R4+R6)
11 disp("closed loop gain")
12 Acl=Ai/(1+Ai*B)
13 Zi=hie/(1+Ai*B)
```

---

### Scilab code Exa 13.15 calculate total harmonic

```
1 //chapter 13
2 //example 13.15
3 //page 585
4 printf("\n")
5 printf(" given")
6 Av=60000;Acl=300;f1=15*10^3;B=1/300;
7 f2=(Av*f1)/Acl
8 disp("% distortion with NFB")
9 NFB=(.1/(1+Av*B))*100;
10 printf(" percenatge distortion with NFB is %3.3f\n"
, NFB)
```

---

# Chapter 14

## IC operational Amplifier and basic Op amp circuits

Scilab code Exa 14.1 calculate maximum resistance

```
1 //chapter 14
2 //example 14.1
3 //page 597
4 printf("\n")
5 printf("given")
6 Vbe=.7; Ib=500*10^-9;
7 R1=Vbe/(10*Ib);
8 R1=120*10^3 //use standard value
9 R2=R1;
10 I2=100*Ib
11 Vr1=15; Vr2=Vr1;
12 R1=Vr1/I2
13 R1=270*10^3; //use satndard value
14 R2=R1;
15 R3=(R1*R2)/(R1+R2)
```

---

**Scilab code Exa 14.2** suitable resistor for BIFET op amp is used

```
1 //chapter 14
2 //example 14.2
3 //page 599
4 printf("\n")
5 printf("given")
6 R2=1*10^6; Vb=3; Vo=3; Vee=9;
7 Vr2=Vb-(-Vee)
8 Vr1=Vee-Vb
9 I2=Vr2/R2
10 R1=Vr1/I2
11 R3=0
```

---

**Scilab code Exa 14.3** typical difference between input and out voltage and  $Z_{in}$  and

```
1 //chapter 14
2 //example 14.3
3 //page 601
4 printf("\n")
5 printf("given")
6 Av=200000; ri=2*10^6; ro=75; Vo=1; B=1;
7 Vd=Vo/Av
8 Zi=(1+Av*B)*ri
9 Zo=ro/(1+Av*B)
```

---

**Scilab code Exa 14.4** capacitor coupled voltage follower usin 741 op amp

```
1 //chapter 14
2 //example 14.4
3 //page 603
4 printf("\n")
5 printf("given")
```

```
6 f=70;R1=4*10^3; Ib=500*10^-9; Vbe=.7;
7 R1=Vbe/(10*Ib)
8 R1=120*10^3; //use standard value
9 R2=R1;
10 disp(" desire value of capacitor is C=1/2*3.14*f*R")
11 C2=1/(2*3.14*f*R1)
12 C1=1/(2*3.14*f*(R1/10))
```

---

### Scilab code Exa 14.5 direct coupled non inverting amplifier

```
1 //chapter 14
2 //example 14.5
3 //page 605
4 printf("\n")
5 printf(" given")
6 Ib=500*10^-9; Vi=50*10^-3; Vo=2;
7 I2=100*Ib;
8 R3=Vi/I2
9 R2=(Vo/I2)-R3
10 R1=(R2*R3)/(R2+R3)
```

---

### Scilab code Exa 14.6 typical input and output impedances for non inverting

```
1 //chapter 14
2 //example 14.6
3 //page 606
4 printf("\n")
5 printf(" given")
6 Av=200000; ri=2*10^6; ro=75; R3=1*10^3; R2=39*10^3;
7 B=R3/(R2+R3)
8 Zi=(1+Av*B)*ri
9 printf(" typical input impedance for non-inverting
        amplifier is %dohm\n", Zi)
```

```
10 Zo=r0/(1+Av*B)
```

---

### Scilab code Exa 14.7 voltage gain and lower cutoff frequency

```
1 //chapter 14
2 //example 14.7
3 //page 607
4 printf("\n")
5 printf("given")
6 R2=50*10^3;R3=2.2*10^3;C2=8.2*10^-6;Rl=600;
7 disp("voltage gain")
8 Acl=(R3+R2)/R3
9 disp("lower cutoff frequency")
10 f=1/(2*3.14*C2*Rl)
```

---

### Scilab code Exa 14.8 direct coupled inverting amplifier

```
1 //chapter 14
2 //example 14.8
3 //page 610
4 printf("\n")
5 printf("given")
6 Acl=144;Vi=20*10^-3;Ib=500*10^-9;
7 I1=100*Ib
8 R1=Vi/I1
9 R1=390;//use standard value
10 R2=Acl*R1
11 R3=(R1*R2)/(R1+R2)
```

---

### Scilab code Exa 14.9 design three input summing amplifier

```
1 //chapter 14
2 //example 14.9
3 //page 612
4 printf("\n")
5 printf("given")
6 Acl=3;R4=1*10^6;Vi=1;
7 R1=R4/Acl
8 R1=330*10^3; //use standard value
9 R2=R1;R3=R1;
10 I1=Vi/R1
11 I2=I1;I3=I1;
12 I4=I1+I2+I3
13 Vo=-I4*R4
```

---

**Scilab code Exa 14.10 suitable resistor for 741 op amp**

```
1 //chapter 14
2 //example 14.10
3 //page 615
4 printf("\n")
5 printf("given")
6 Ib=500*10^-9;Vi=1;Acl=10;
7 I1=100*Ib
8 R1=Vi/I1
9 R1=18*10^3; //use standard value
10 R2=Acl*R1
11 R4=R1
12 R3=R1/Acl
```

---

**Scilab code Exa 14.11 overall voltage gain for instrumentation amplifier**

```
1 //chapter 14
2 //example 14.11
```

```

3 // page 619
4 printf("\n")
5 printf(" given")
6 Vi=10*10^-3; Vn=1; R1=33*10^3; R2=300; R5=15*10^3; R4
    =15*10^3; Vi2=-10*10^-3; R3=R1; R6=15*10^3; R7=R6;
7 Acl=((2*R1+R2)/R2)*(R5/R4)
8 disp(" at junction of R1 and R2")
9 Vb=Vi+Vn
10 disp(" at junction of R2 and R3")
11 Vc=Vi2+Vn
12 disp(" current through R2")
13 I2=(Vb-Vc)/R2
14 disp(" at the output of A1")
15 Va=Vb+(I2*R1)
16 disp(" at output of A2")
17 Vd=Vc-(I2*R3)
18 disp(" at junction of R6 and R7")
19 Vf=Vd*(R7/(R6+R7))
20 disp(" at junction of R4 and R5")
21 Ve=Vf
22 disp(" current through R4")
23 I4=(Va-Ve)/R4
24 disp(" at output of A3")
25 Vg=Ve-(I4*R5)

```

---

Scilab code Exa 14.12 typical output voltage swing and calculate rise time

```

1 // chapter 14
2 //example 14.12
3 //page 623
4 printf("\n")
5 printf(" given")
6 Vcc=15; Vee=-15; Av=200000; SR=.5/10^-6; Vo=14;
7 V=(Vcc-1)-(Vee+1)
8 Vi=Vo/Av

```

```
9 disp("rise time of output is ")
10 t=(V/SR)*10^6;
11 printf("rise time of output is %dus\n",t)
```

---

**Scilab code Exa 14.13** calculate resistor for schmitt trigger circuit

```
1 //chapter 14
2 //example 14.13
3 //page 627
4 printf("\n")
5 printf("given")
6 Ib=500*10^-9; UTP=5; Vcc=15;
7 I1=100*Ib
8 R2=UTP/I1
9 R1=((Vcc-1)-5)/I1
```

---

**Scilab code Exa 14.14** upper and lower trigger for non inverting schmitt trigger

```
1 //chapter 14
2 //example 14.14
3 //page 630
4 printf("\n")
5 printf("given")
6 Vcc=15; Vsat=Vcc; R2=150*10^3; Vf=.7; R1=27*10^3; R3
    =120*10^3;
7 I2=(Vsat-Vf)/R2
8 UTP=I2*R1
9 disp(" LTP calculation including Vf")
10 I3=(Vsat-Vf)/R3
11 LTP=-I3*R1
```

---

# Chapter 15

## Operational amplifier frequency Response and compensation

Scilab code Exa 15.2 determine suitable component

```
1 //chapter 15
2 //example 15.2
3 //page 648
4 printf("\n")
5 printf("given")
6 R2=1*10^6; Acl=4.5;
7 R1=R2/Acl
8 R1=220*10^3; //use standard value
9 R3=(R1*R2)/(R1+R2)
10 Cf=((R1*30*10^-12)/(R1+R2))*10^12;
11 printf(" suitable value of capacitor is %3.2fpF\n",
Cf)
```

---

Scilab code Exa 15.3 miller effect capacitor

```
1 //chapter 15
```

```
2 //example 15.3
3 //page 649
4 printf("\n")
5 printf("given")
6 f=35*10^3;Rf=68*10^3;
7 Cf=(1/(2*3.14*f*Rf))*10^12;
8 printf(" suitable miller effect capacitor is %dpF\n"
    ,Cf)
```

---

Scilab code Exa 15.5 cutoff frequencies using gain bandwidth

```
1 //chapter 15
2 //example 15.5
3 //page 652
4 printf("\n")
5 printf("given")
6 Acl=100;Av=10;
7 disp(" for Cf=30pF")
8 GBW=800*10^3;
9 F2=GBW/Acl
10 disp(" for Cf=3pF")
11 GBW=(800*10^3)*Av;
12 f2=GBW/Acl
```

---

Scilab code Exa 15.6 full power bandwidth for AD843 op amp circuit

```
1 //chapter 15
2 //example 15.6
3 //page 654
4 printf("\n")
5 printf("given")
6 Vip=1;R2=39*10^3;R3=4.7*10^3;SR=250/10^-6;f
    =100*10^3;
```

```

7 disp(" for the AD843")
8 Vop=((R2+R3)/R3)*Vip
9 fp=SR/(2*3.14*Vop);
10 printf(" full power bandwidth is %dHz\n",fp)
11 disp(" for a 741")
12 SR=.5/10^-6;
13 Vp=SR/(2*3.14*f);
14 printf(" maximum peak output voltage is %3.2fV\n",Vp
    )

```

---

### Scilab code Exa 15.7 input terminal stray capacitor

```

1 //chapter 15
2 //example 15.7
3 //page 656
4 printf("\n")
5 printf("given")
6 rs=600;R1=1*10^3;R2=10*10^3;f=800*10^3;
7 disp(" stray capacitance")
8 Cs=1/(2*3.14*f*10*((rs+R1)*R2)/(rs+R1+R2)))
9 disp("compensation capacitor")
10 C2=((Cs*(rs+R1))/R2)*10^12;
11 printf("compensation capacitor is %3.2fpF\n",C2)

```

---

### Scilab code Exa 15.8 load capacitance

```

1 //chapter 15
2 //example 15.8
3 //page 659
4 printf("\n")
5 printf("given")
6 ro=25;f=2*10^6;R2=10*10^3;Rx=25;
7 C1=(1/(2*3.14*f*(10*ro)))*10^+12;

```

```
8 printf(" load capacitance is %3.2fpF\n",C1)
9 C1=.1*10^-6;
10 C2=((C1*(r0+Rx))/R2)*10^12;
11 printf(" compensation capacitance is %dpF\n",C2)
```

---

# Chapter 16

## Signal generators

Scilab code Exa 16.1 phase shift oscillator

```
1 //chapter 16
2 //example 16.1
3 //page 6568
4 printf("\n")
5 printf("given")
6 Vcc=10; Ib=500*10^-9; Acl=29; f=1*10^3;
7 disp(" phase shift oscillator")
8 I1=100*Ib
9 vo=Vcc-1
10 vi=vo/Acl
11 R1=vi/I1
12 R1=5.6*10^3; //use standard value 5.6Kohm
13 R2=Acl*R1
14 R2=180*10^3; //use satndard value 180Kohm to give Acl
15 >180
15 R3=R2; R=R1;
16 C=1/(2*3.14*R*f*sqrt(6))
```

---

Scilab code Exa 16.2 colpitts oscillator

```

1 //chapter 16
2 //example 16.2
3 //page 672
4 printf("\n")
5 printf("given")
6 f=40*10^3;L=100*10^-3;vp=8;
7 disp("colpitts oscillator")
8 Ct=1/(4*3.14*3.14*(f^2)*L)
9 C1=10*Ct
10 C2=1/((1/Ct)-(1/C1))
11 C2=180*10^-12; //use standard value
12 Xc2=1/(2*3.14*f*C2)
13 Xc1=1/(2*3.14*f*C1)
14 R1=10*Xc1
15 R1=27*10^3; //use standard value
16 Acl=C1/C2
17 R2=Acl*R1
18 R2=270*10^3; //use standard value
19 R3=(R1*R2)/(R1+R2)
20 f2=Acl*f
21 SR=2*3.14*f*vp

```

---

### Scilab code Exa 16.3 hartley oscillator

```

1 //chapter 16
2 //example 16.3
3 //page 678
4 printf("\n")
5 printf("given")
6 vo=8;f=100*10^3;
7 disp(" hartley oscillator")
8 Vcc=vo+1
9 Xl2=1*10^3;
10 L2=Xl2/(2*3.14*f)
11 L2=1.5*10^-3; //use standard value

```

```

12 L1=L2/10
13 Lt=L1+L2 // (assuming M=0)
14 C1=1/(4*(3.14^2)*(f^2)*Lt)
15 C1=1500*10^-12; //use 1500pF with aadditional
    parallel capacitance if necessary
16 //C1>>stray capacitance
17 Xl1=2*3.14*f*L1 //R1>>Xl1
18 R1=1*10^3;
19 Acl=L2/L1
20 R2=Acl*R1
21 R3=(R1*R2)/(R1+R2)
22 disp(" full power bandwidth ")
23 f2=Acl*f
24 SR=2*3.14*f*vo

```

---

#### Scilab code Exa 16.4 wein bridge oscillator

```

1 //chapter 16
2 //example 16.4
3 //page 680
4 printf("\n")
5 printf("given")
6 f=100*10^3; Vo=9; Acl=3;
7 disp(" design of wein bridge oscillator")
8 Vcc=Vo+1
9 C1=1000*10^-12; //standard value
10 C2=C1;
11 R1=1/(2*3.14*f*C1)
12 R2=R1; R4=R2;
13 R3=2*R4;
14 R3=3.3*10^3; //use standard value
15 disp(" minimum full power bandwidth")
16 f2=Acl*f
17 SR=2*3.14*f*Vo

```

---

### Scilab code Exa 16.5 design a phase shift oscillator

```
1 //chapter 16
2 //example 16.5
3 //page 683
4 printf("\n")
5 printf("given")
6 f=5*10^3; vo=5; I1=1*10^-3; Vf=.7;
7 disp("phase shift oscillator")
8 R1=(vo/29)/I1
9 R1=150; //use standard value
10 R2=29*R1
11 R4=(2*Vf)/I1
12 R4=1.5*10^3; //use 1.5kohm standard value
13 R5=R2-R4
14 R6=.4*R5
15 R7=.8*R5
16 R=R1;
17 C=1/(2*3.14*R*f*sqrt(6))
```

---

### Scilab code Exa 16.6 amplitude stabilization circuit

```
1 //chapter 16
2 //example 16.6
3 //page 686
4 printf("\n")
5 printf("given")
6 rds=600; Vgs=1; Vd1=.7; f=100*10^3;
7 disp("wien bridge oscillator")
8 R4=560;
9 R3=2*((R4*rds)/(R4+rds))
10 I5=200*10^-6; Vo=6;
```

```
11 R6=Vgs/I5
12 R5=(Vo-(Vgs+Vd1))/I5
13 disp(" C4 discharge voltage ")
14 Vc=.1*Vgs
15 disp("C4 discharge time")
16 T=1/f
17 Ic=I5;
18 C4=(Ic*T)/Vc
19 Xc3=rds/10 // at oscillating frequency
20 C3=1/(2*3.14*f*Xc3)
```

---

### Scilab code Exa 16.7 square wave generator

```
1 //chapter 16
2 //example 16.7
3 //page 689
4 printf("\n")
5 printf("given")
6 Vo=14; Vr3=.5; Ib=500*10^-9; f=1*10^3;
7 disp("square wave generator")
8 Vcc=Vo+1
9 UTP=Vr3; LTP=UTP;
10 I2=100*Ib;
11 R3=Vr3/I2
12 R2=(Vo-Vr3)/I2
13 t=1/(2*f)
14 V=UTP-(-LTP)
15 C1=.1*10^-6;
16 I1=(C1*V)/t
17 R1=Vo/I1
```

---

### Scilab code Exa 16.8 calculate t1 t2 and pulse frequency

```
1 //chapter 16
2 //example 16.8
3 //page 694
4 printf("\n")
5 printf("given")
6 R1=2.2*10^3;R2=2.7*10^3;C2=.5*10^-6;Vcc=15;
7 t1=.693*C2*(R1+R2)
8 t2=.693*C2*R2
9 T=t1+t2
10 f=1/T
11 Ic1=(Vcc/3)/(R1+R2)
```

---

#### Scilab code Exa 16.10 triangular wave generator

```
1 //chapter 16
2 //example 16.10
3 //page 699
4 printf("\n")
5 printf("given")
6 Vcc=9;Vo=3;I1=1*10^-3;f=500;UTP=3;
7 disp("design the triangular wave")
8 Vi=Vcc-1
9 V=Vo-(-Vo)
10 disp(" I1>>Ibmax for op-amp")
11 R1=Vi/I1
12 t=1/(2*f)
13 C1=(I1*t)/V
14 disp(" schmitt design")
15 I2=1*10^-3;
16 R2=UTP/I2
17 R3=(Vcc-1)/I2
```

---

#### Scilab code Exa 16.11 design a wein bridge oscillator

```
1 //chapter 16
2 //example 16.11
3 //page 705
4 printf("\n")
5 printf("given")
6 f=100*10^3;Rs=1.5*10^3;
7 R1=2*Rs
8 R1=2.7*10^3; //use standard value
9 R2=R1+Rs
10 C1=1/(2*3.14*f*R2)
11 R4=R2;
12 R3=2*R4
```

---

### Scilab code Exa 16.12 pierce oscillator and peak power dissipated

```
1 //chapter 16
2 //example 16.12
3 //page 705
4 printf("\n")
5 printf("given")
6 fs=1*10^6;Rs=700;C1=1000*10^-12;C2=100*10^-12;R1
    =1*10^6;R2=10*10^3;Rs=700;Vdd=5;
7 Ct=(C1*C2)/(C1+C2)
8 disp(" at resonance Xl=Xct      2*pi*f*L=1/2*pi*f*Ct")
9 L=1/(((2*3.14*fs)^2)*Ct)
10 ip=Vdd/(R1+R2+Rs)
11 Pd=((.707*ip)^2)*Rs)*10^9;
12 printf(" peak power dissipated is %3.3fnW\n",Pd)
```

---

# Chapter 17

## Active filters

Scilab code Exa 17.1 calculate attenuation

```
1 //chapter 17
2 //example 17.1
3 //page 716
4 printf("\n")
5 printf("given")
6 rs=600; R1=12*10^3; Rl=100*10^3; C1=.013*10^-6;
7 disp("when Rl is not connected")
8 fc=1/(2*3.14*R1*C1)
9 disp(" when Rl is connected")
10 fc=1/(2*3.14*((R1*Rl)/(R1+Rl))*C1)
11 Attn=3 //at fc attenuation is =3dB
12 falloffrate=6
13 disp("attenuation at 2fc")
14 Attn=3+6;
15 printf("attenuation at 2fc is %dB\n",Attn)
16 Attn=3+6+6;
17 printf(" attenuation at 4fc is %dB\n",Attn)
```

---

Scilab code Exa 17.2 first order active low pass filter

```
1 //chapter 17
2 //example 17.2
3 //page 718
4 printf("\n")
5 printf("given")
6 Ib=500*10^-9; f=1*10^3;
7 R1=(70*10^-3)/Ib
8 R1=140*10^3; //use standard value
9 R2=R1;
10 C1=(1/(2*3.14*R1*f))*10^12;
11 printf(" capacitor used is of %dpF\n",C1)
```

---

**Scilab code Exa 17.3 first order high pass filter and filter bandwidth**

```
1 //chapter 17
2 //example 17.3
3 //page 719
4 printf("\n")
5 printf("given")
6 disp("first order high pass active filter")
7 f=5*10^3; C1=1000*10^-12; fu=1*10^6;
8 R1=1/(2*3.14*f*C1)
9 BW=fu-f;
10 printf(" bandwidth is %dHz\n",BW)
```

---

**Scilab code Exa 17.4 butterworth second order low pass filter**

```
1 //chapter 17
2 //example 17.4
3 //page 724
4 printf("\n")
5 printf("given")
6 f=1*10^3; Ib=500*10^-9;
```

```

7 disp("butterworth second order filter")
8 R=(70*10^-3)/Ib
9 R1=R/2
10 R1=68.1*10^3; //use standard value
11 R2=R1;
12 R3=2*R1
13 Xc1=sqrt(2)*R2
14 C1=1/(2*3.14*f*sqr(2)*R2)
15 C2=2*C1
16 fc=1/(2*3.14*(sqrt(R1*R2*C1*C2)));
17 printf("actual cutoff frequency is %dHz\n",fc)

```

---

**Scilab code Exa 17.5 using BIFET op amp design butterworth second order filter**

```

1 //chapter 17
2 //example 17.5
3 //page 7
4 printf("\n")
5 printf("given")
6 f=12*10^3;C1=1000*10^-12;
7 disp("butterworth second order filter")
8 C2=C1;
9 R2=(sqrt(2))/(2*3.14*f*C1)
10 R1=.5*R2
11 R3=R2;
12 fc=1/(2*3.14*(sqrt(R1*R2*C1*C2)));
13 printf("actual cutoff frequency is %dHz\n",fc)

```

---

**Scilab code Exa 17.6 third order low pass filter**

```

1 //chapter 17
2 //example 17.6
3 //page 729

```

```

4 printf("\n")
5 printf("given")
6 f=30*10^3; C1=1000*10^-12;
7 disp(" third order low pass filter")
8 disp("-20 dB per decade stage")
9 fc1=f/.65;
10 R1=1/(2*3.14*fc1*C1)
11 R2=R1;
12 disp("-40dB per decade stage")
13 C3=1000*10^-12;
14 C2=2*C3
15 fc2=f/.8
16 R4=1/(2*3.14*fc2*C3*(sqrt(2)))
17 R3=R4;
18 R5=R3+R4

```

---

### Scilab code Exa 17.7 third order high pass filter

```

1 //chapter 17
2 //example 17.7
3 //page 730
4 printf("\n")
5 printf("given")
6 f=20*10^3;
7 disp("3rd order high pass filter")
8 disp("-20dB per decade stage")
9 R1=121*10^3;
10 fc1=.65*f
11 C1=1/(2*3.14*fc1*R1)
12 //this is so small it might be effected by stray
   capacitor.redesign , first choosing a suitable
   capacitance C1
13 C1=100*10^-12;
14 R1=1/(2*3.14*f*C1)
15 R2=R1;

```

```
16 disp("-40dB per decade stage")
17 C3=1000*10^-12;
18 R4=(sqrt(2))/(2*3.14*.8*f*C3)
19 C2=C3;
20 R3=.5*R4
21 R5=R4
```

---

### Scilab code Exa 17.8 single stage band pass filter

```
1 //chapter 17
2 //example 17.8
3 //page 734
4 printf("\n")
5 printf("given")
6 f1=300;f2=30*10^3;
7 disp(" single stage band pass filter")
8 C2=1000*10^-12;
9 R2=1/(2*3.14*f2*C2)
10 R1=R2;
11 Xc1=R1;//at voltage gain Av=1
12 C1=1/(2*3.14*f1*R1)
13 R3=R2
```

---

### Scilab code Exa 17.9 calculate Q factor for wide band filter

```
1 //chapter 17
2 //example 17.9
3 //page 736
4 printf("\n")
5 printf("given")
6 f1=300;f2=30*10^3;
7 fo=sqrt(f1*f2)
8 BW=f2-f1
```

9 Q=f<sub>o</sub>/BW

---

### Scilab code Exa 17.10 center frequency and bandwidth

```
1 //chapter 17
2 //example 17.10
3 //page 737
4 printf("\n")
5 printf("given")
6 R1=60.4*10^3;R4=1.21*10^3;C=.012*10^-6;R2=121*10^3;
7 Q=sqrt((R1+R4)/(2*R4))
8 fo=Q/(3.14*C*R2);
9 printf(" center frequency is %3.2fHz\n",fo)
10 BW=fo/Q;
11 printf(" bandwidth is %3.1fHz\n",BW)
```

---

### Scilab code Exa 17.12 state variable band pass filter

```
1 //chapter 17
2 //example 17.12
3 //page 744
4 printf("\n")
5 printf("given")
6 f1=10.3*10^3;f2=10.9*10^3;
7 C1=1000*10^-12;C2=C1;
8 fo=sqrt(f1*f2)
9 R5=1/(2*3.14*fo*C1)
10 R1=R5;
11 Q=fo/(f2-f1)
12 R2=R1*(2*Q-1)
```

---

Scilab code Exa 17.13 required resistance to operate one half of an MF10

```
1 //chapter 17
2 //example 17.13
3 //page 750
4 printf("\n")
5 printf("given")
6 f1=10.3*10^3;f2=10.9*10^3;Hobp=34;
7 fo = sqrt(f1*f2);
8 sqrt(f1*f2)
9 Q=fo/(f2-f1)
10 R3=120*10^3;
11 R2=R3/Q
12 R1=R3/Hobp
13 fck=50*fo
```

---

# Chapter 18

## Linear and switching voltage regulators

Scilab code Exa 18.1 load and source effects and load and line regulation

```
1 //chapter 18
2 //example 18.1
3 //page 761
4 printf("\n")
5 printf("given")
6 Vs=21; Vo=12; Av=100;
7 vo=(Vs*.1)/Av; //source effect is 10% of the Vs
8 printf(" source effect is %3.3fV\n",vo)
9 vo=(21-20)/100;
10 printf(" laod effect is %3.3fV\n",vo)
11 LR=(21*10^-3 *100)/12;
12 printf("line regulation is %3.3fpercentage\n",LR)
13 LR=(10*10^-3*100)/12;
14 printf(" load effect is %3.3fpercentage \n",LR)
15 RJ=20*log10(1/Av);
16 printf("ripple rejection is %ddB\n",RJ)
```

---

### Scilab code Exa 18.2 voltage regulator circuit

```
1 //chapter 18
2 //example 18.2
3 //page 762
4 printf("\n")
5 printf("given")
6 Vo=12; I1=40*10^-3; Vs=20; Vbe=.7;
7 Vz=.75*Vo
8 disp(" for minimum D1 current select")
9 Ir2=10*10^-3;
10 R2=(Vo-Vz)/Ir2
11 Ie1=I1+Ir2
12 disp(" specification for Q")
13 Vce1=20; Vs=Vce1;
14 Ic1=50*10^-3;
15 Pd=(Vs-Vo)*Ie1
16 hfe=50;
17 Ib1=Ie1/hfe
18 Ic2=5*10^-3;
19 R1=(Vs-(Vo+.7))/(Ic2+Ib1)
20 Iz=Ie2+Ir2
21 I4=1*10^-3;
22 R4=(Vz+Vbe)/I4
23 R3=(Vo-(Vz+Vbe))/I4
```

---

### Scilab code Exa 18.3 modify voltage regulator

```
1 //chapter 18
2 //example 18.3
3 //page 765
4 printf("\n")
5 printf("given")
6 I4=1*10^-3; Vb2=9.8;
7 disp(" for Vo=11V moving contact at top of R5")
```

```

8 Vo=11;
9 R3=(Vo-Vb2)/I4
10 R=Vb2/I4 //R=R4+R5
11 disp(" for Vo=13V moving contact at bottom of R5")
12 Vo=13;
13 I4=Vo/(R3+R)
14 R4=Vb2/I4
15 R5=R-R4

```

---

**Scilab code Exa 18.4** voltage regulator to change the load current

```

1 //chapter 18
2 //example 18.4
3 //page 766
4 printf("\n")
5 printf("given")
6 hFE3=50; hFE1=20; Ie1=200*10^-3+10*10^-3; Ic2=1*01^-3;
      Vs=20; Vb3=13.4; Vo=12; Vbe=.7;
7 Ib1=Ie1/hFE1
8 Ib3=Ib1/hFE3
9 R1=(Vs-Vb3)/(Ic2+Ib3)
10 disp(" select I6=.5*10^-3")
11 I6=.5*10^-3;
12 R6=(Vo+Vbe)/I6
13 Pd=(Vs-Vo)*Ie1

```

---

**Scilab code Exa 18.5** suitable component for preregulator circuit

```

1 //chapter 18
2 //example 18.5
3 //page 769
4 printf("\n")
5 printf("given")

```

```

6 Vo=12.0;
7 Vr1=3; Ic2=1*10^-3; Ib3=.21*10^-3; Vbe1=.7; Vbe3=Vbe1; Vs
   =20;
8 R1=Vr1/(Ic2+Ib3)
9 Vz2=Vo+Vbe1+Vbe3+Vr1
10 Ir7=5*10^-3;
11 R2=(Vs-Vz2)/Ir7

```

---

### Scilab code Exa 18.6 differential amplifier

```

1 //chapter 18
2 //example 18.6
3 //page 770
4 printf("\n")
5 printf("given")
6 Vc5=9.8; Vb2=Vc5; Vce5=3; Vbe=.7; Vo=12;
7 Vr9=Vc5-Vce5
8 Vz2=Vr9+Vbe
9 Ic5=1*10^-3;
10 R8=(Vo-Vc5)/Ic5
11 Ir9=2*Ic5
12 R9=Vr9/Ir9
13 disp(" Iz2>>Ib5 and Iz2 >(Izk for the zener diode )")
14 Iz2=10*10^-3;
15 R7=(Vo-Vz2)/Iz2
16 I4=1*10^-3;
17 Vb6=7.5; Vz2=Vb6;
18 disp(" when Vo=11V(moving contact at top of R5 )")
19 Vo=11;
20 R3=(Vo-Vb6)/I4
21 R3=3.3*10^3; //use standard value
22 I4=(Vo-Vb6)/R3
23 R=Vb6/I4 //R=R4+R5
24 disp(" when Vo=13V(moving contact at bottom of R5 )")
25 Vo=13; Vb6=7.5;

```

```
26 I4=Vo/(R3+R)
27 R4=Vb6/I4
28 R5=R-R4
```

---

### Scilab code Exa 18.7 fold back current limiting circuit for voltage regulator

```
1 //chapter 18
2 //example 18.7
3 //page 7
4 printf("\n")
5 printf("given")
6 Isc=100*10^-3; Vr10=.5; Vo=12;
7 R10=Vr10/Isc
8 R10=4.7; //use standard value
9 I1=200*10^-3;
10 Vr10=I1*R10
11 Vr11=Vr10-.5
12 I11=1*10^-3;
13 R11=Vr11/I11
14 R12=(Vo+Vr10-Vr11)/I11
```

---

### Scilab code Exa 18.8 adjustable voltage regulator circuit

```
1 //chapter 18
2 //example 18.8
3 //page 778
4 printf("\n")
5 printf("given")
6 Vo=12; hFE1=20; hFE2=50; I1=250*10^-3;
7 Vz=.75*Vo
8 Vz=9.1; //use standard value for 1N757 diode
9 Iz1=10*10^-3;
10 R1=(Vo-Vz)/Iz1
```

```

11 I3=1*10^-3;
12 disp(" when Vo=12V( moving contact at top of R5") )
13 R3=(Vo-Vz)/I3
14 R=Vz/I3
15 disp(" when Vo=15V moving contact at bottom of R5")
16 Vo=15;
17 I3=Vo/(R+R3)
18 R4=Vz/I3
19 R5=R-R4
20 Ir6=.5*10^-3;
21 R6=Vo/Ir6
22 disp(" op-amp output current")
23 Ib2=I1/(hFE1*hFE2)

```

---

### Scilab code Exa 18.9 input voltage and maximum load current

```

1 //chapter 18
2 //example 18.9
3 //page 782
4 printf("\n")
5 printf("given")
6 I2=1*10^-3; Vr2=7.15; Vref=Vr2; Vo=10; Pdmax=1000*10^-3;
7 R2=Vref/I2
8 R2=6.8*10^3; //use standard value and recalculate the
    I2
9 I2=Vref/R2
10 R1=(Vo-Vref)/I2
11 Vs=Vo+5 //for satisfactory operation of series pass
    transistor
12 Iint=25*10^-3; //internal circuit current
13 Pi=Vs*Iint
14 disp("maximum power dissipated in series pass
    transistor")
15 Pd=Pdmax-Pi
16 disp("maximum load current is ")

```

17  $I_1 = P_d / (V_s - V_o)$

---

### Scilab code Exa 18.10 calculate regulator power dissipation

```
1 //chapter 18
2 //example 18.10
3 //page 785
4 printf("\n")
5 printf(" given")
6 I1=1*10^-3; Vref=1.25; Vo=6; Vs=15; Il=200*10^-3;
7 R1=Vref/I1
8 R2=(Vo-Vref)/Il
9 Pd=(Vs-Vo)*Il;
10 printf(" regulated power dissipation is %3.2fW\n",Pd)
```

---

### Scilab code Exa 18.11 efficiencies of linear regulator and switching regulator

```
1 //chapter 18
2 //example 18.11
3 //page 788
4 printf("\n")
5 printf(" given")
6 Vo=10; Io=1; Vce=7; Vf=1;
7 Po=Vo*Io
8 disp(" linear regulator")
9 Pi=Po+(Vce*Io)
10 n=(Po*100)/Pi //efficiency
11 disp(" switching regulator")
12 Vce=1;
13 Pi=Po+Io*(Vce+Vf)
14 n=(Po*100)/Pi //efficiency
```

---

### Scilab code Exa 18.12 step down switching regulator

```
1 //chapter 18
2 //example 18.12
3 //page 792
4 printf("\n")
5 printf("given")
6 f=50*10^3; Vo=12; Vf=.7; Vi=30; Vsat=1; Io=500*10^-3; Vr
    =100*10^-3;
7 T=1/f
8 t=(Vo+Vf)/(Vi-Vsat-Vo)
9 toff=T/1.75
10 ton=T-toff
11 Ip=2*Io
12 L1=((Vi-Vsat-Vo)*ton)/Ip
13 C1=Ip/(8*f*Vr)
```

---

### Scilab code Exa 18.13 determine suitable value for R1 R2 Rsc and Ct

```
1 //chapter 18
2 //example 18.13
3 //page 799
4 printf("\n")
5 printf("given")
6 disp(" an MC34063 controller is for step down
        transformer")
7 Ib=-400*10^-3; I1=1*10^-3; Vref=1.25; V0=12; Ip=1; ton
        =8.6*10^-6;
8 R1=Vref/I1
9 R1=1.2*10^3; //use standard value
10 I1=Vref/R1
11 R2=(Vo-Vref)/I1
```

12 Rsc=.33/Ip  
13 Ct=4.8\*10^-5 \*ton

---

# Chapter 19

## Power amplifiers

Scilab code Exa 19.1 Dc and Ac load line transistor common emitter characteristics

```
1 //chapter 19
2 //example 19.1
3 //page 810
4 printf("\n")
5 printf("given")
6 Rpy=40; N1=74; N2=14; R2=3.7*10^3; R1=4.7*10^3; Vbe=.7; Re
    =1*10^3; Vcc=13; Rl=56;
7 disp("Q-point")
8 Vb=Vcc*(R2/(R1+R2))
9 Ic=(Vb-Vbe)/Re
10 Ie=Ic;
11 Vce=Vcc-Ic*(Rpy+Re)
12 rl=(N1/N2)^2 *Rl
13 rl=rl+Rpy
14 Ic=5*10^-3;
15 Vce=Ic*rl
```

---

Scilab code Exa 19.2 maximum efficiency of class A amplifier

```

1 //chapter 19
2 //example 19.2
3 //page 814
4 printf("\n")
5 printf(" given")
6 Vcc=13; Icq=5*10^-3; Vceq=8; Vp=Vceq; Ip=Icq; nt=.8;
7 Pi=Vcc*Icq
8 Po=.5*Vp*Ip
9 P0=nt*Po
10 n=(P0/Pi)*100;
11 printf(" maximum efficiency is %3.2f percentage\n",n
)

```

---

**Scilab code Exa 19.4 power deliver to load in class AB amplifier**

```

1 //chapter 19
2 //example 19.4
3 //page 821
4 printf("\n")
5 printf(" given")
6 N1=60; N2=10; Rl=16; Rpy=0; R6=56; Vcc=27; Vce=.5; n=.79;
7 disp(" Referred laod")
8 rl=(N1/N2)^2 *Rl
9 disp(" tatol ac load line in series with each of Q2
       and Q3")
10 Rl=rl+R6+Rpy
11 disp(" peak primary current")
12 Ip=(Vcc-Vce)/Rl
13 disp(" peak primary voltage")
14 Vp=Vcc-Vce-(Ip*R6)
15 disp(" power delivered to primary")
16 Po=.5*Vp*Ip
17 disp(" power delivered to the load")
18 Po=Po*n//n is power efficiency

```

---

**Scilab code Exa 19.5 output transformer and transistor of class B circuit**

```
1 //chapter 19
2 //example 19.5
3 //page 824
4 printf("\n")
5 printf("given")
6 Po=4; nt=.8; Vcc=30; Vp=Vcc; Rl=16;
7 P0=Po/nt
8 rl=(Vp)^2 /(2*P0)
9 rl=4*rl
10 disp("transformer specification Po=4 ,Rl=16 rl=360")
11 Vce=2*Vcc
12 Ip=(2*P0)/Vp
13 Pi=Vcc*.636*Ip
14 Pt=.5*(Pi-P0)
15 disp(" transistor specification is Py=.68W Vce=60
    Ip=333mA")
```

---

**Scilab code Exa 19.6 determine required supply voltage for class AB amplifier**

```
1 //chapter 19
2 //example 19.6
3 //page 830
4 printf("\n")
5 printf("given")
6 Rl=50; Po=1; hFE=50; Vbe=.7; Vrc=4; Vre=1; Vd1=.7; Vd2=Vd1;
7 Vp=sqrt(2*Rl*Po)
8 Ip=Vp/Rl
9 Re3=.1*Rl;
10 Re2=4.7; //use standard value
11 Re2=Re3;
```

```
12 Icq=.1*Ip
13 Vb=Vbe+Icq*(Re2+Re3)+Vbe
14 Vc1=Vrc;
15 Ib2=Ip/hFE
16 Irc=Ib2+1*10^-3
17 Rc=Vrc/Irc
18 Rc=680; //use standard value
19 Vcc=2*(Vp+Vre+Vbe+Vrc)
20 Vcc=32; //use standard value
21 Vrcdc=.5*(Vcc-Vb)
22 Ic1=Vrcdc/Rc
23 Rb=(Vb-Vd1-Vd2)/Ic1
```

---

### Scilab code Exa 19.7 output transistors

```
1 //chapter 19
2 //example 19.7
3 //page 832
4 printf("\n")
5 printf("given")
6 Vcc=32; Vce=32; Ip=200*10^-3; Po=1;
7 Ic=1.1*Ip
8 Pi=.35*Vcc*Ip
9 Pt=.5*(Pi-Po)
```

---

### Scilab code Exa 19.8 capacitor value for Ce and Co

```
1 //chapter 19
2 //example 19.8
3 //page 832
4 printf("\n")
5 printf("given")
6 f=50; hib=2; Rl=50;
```

```
7 Ce=1/(2*3.14*f*hib)
8 Co=1/(2*3.14*50*.1*R1)
```

---

**Scilab code Exa 19.9** determine the value of Vcc Rc and Rb for class AB amplifier

```
1 //chapter 19
2 //example 19.9
3 //page 834
4 printf("\n")
5 printf("given")
6 hFE=2000; Vbe=1.4; Vp=10; Ip=200*10^-3; Icq2=20*10^-3;
    Re3=4.7; Re2=4.7; Vd=.7;
7 Icq=20.0*10^-3;
8 Ve1=3; Vc1=15.2; Vrc=Vc1;
9 Vb=Vbe+Icq*(Re2+Re3)+Vbe
10 Vcc=Vrc+Vc1+Vb
11 Ib2=Ip/hFE
12 Irc=1*10^-3;
13 Vrcac=4;
14 Rc=Vrcac/Irc
15 Ic1=Vrc/Rc
16 Rb=(Vb-(4*Vd))/Ic1
```

---

**Scilab code Exa 19.10** design Vbe multiplier

```
1 //chapter 19
2 //example 19.10
3 //page 838
4 printf("\n")
5 printf("given")
6 Vb=3.2; Ic1=5*10^-3; Vce=3.2; Vbe=.7;
7 Vbmin=Vb-.5
8 Vbmax=Vb+.5
```

```

9 I10=.1*Ic1
10 R10=(Vce-Vbe)/I10
11 R10=4.7*10^3; //use standard value
12 disp(" for Vce=3.7")
13 Vce=3.7;
14 I10max=(Vce-Vbe)/R10
15 disp("Vce=2.7V")
16 Vce=2.7;
17 I10min=(Vce-Vbe)/R10
18 R=Vbe/I10min
19 R11=Vbe/I10max
20 R12=R-R11

```

---

**Scilab code Exa 19.11 required supply voltage and specify output transistors**

```

1 //chapter 19
2 //example 19.11
3 //page 843
4 printf("\n")
5 printf(" given")
6 Rl=16; Po=6; Vbe=.7;
7 Vp=sqrt(2*Rl*Po)
8 Vr14=.1*Vp; Vr15=Vr14;
9 R14=.1*Rl; R15=R14;
10 Vce3=1; Vce4=Vce3;
11 Vr9=3; Vr11=Vr9;
12 Vcc=(Vp+Vr14+Vbe+Vce3+Vr9)
13 Vee=-Vcc;
14 Ip=Vp/Rl
15 disp(" DC power input from supply line")
16 Pi=(Vcc-Vee)*.35*Ip
17 disp(" output transistor specification")
18 Pt=.5*(Pi-Po)
19 Vce=2*Vcc
20 Ic=1.1*Ip

```

---

**Scilab code Exa 19.12** suitable resistor for output and intermediate stage

```
1 //chapter 19
2 //example 19.12
3 //page 844
4 printf("\n")
5 printf("given")
6 hFE7=20; Icbo=50*10^-6; hFE5=70; Vr9=3; Ip=869*10^-3; R15
    =1.5; R8=15*10^3; Vbe=.7; Vr11=3; Vee=20;
7 R12=.01/Icbo
8 R12=220; //use standard value
9 R13=R12;
10 Ib5=Ip/(hFE7*hFE5)
11 Ic3=2*10^-3;
12 R9=Vr9/Ic3
13 R11=R9;
14 Iq78=.1*Ip
15 Vr14=Iq78*R15
16 Vr15=Vr14;
17 Vr10=(Vr14+Vr15)+(Vr14+Vr15)/2
18 R10=Vr10/Ic3
19 Ir8=(Vr11+Vbe)/R8
20 R7=(Vee-(Vr11+Vbe))/Ir8
```

---

**Scilab code Exa 19.13** calculate required supply voltage and suitable DC voltage dr

```
1 //chapter 19
2 //example 19.13
3 //page 848
4 printf("\n")
5 printf("given")
```

```

6 Rl=20; Po=2.5; Rd=4; Vr6=1; Vr9=Vr6; Vth=1; gFS=250*10^-3;
7 Vbe=.7;
8 Vp=sqrt(2*Rl*Po)
9 Ip=Vp/Rl
10 Vcc=(Vp+Ip*Rd)
11 vr6=Ip/gFS
12 Vr2=vr6+1
13 Vce=Vr2;
14 Vce3=1;
15 Vr2=Vcc-Vce
16 Vee=Vcc;
17 Vr3=Vee-Vbe
18 Vr7=Vr2-Vr6
19 Vr8=Vcc-(-Vee)-Vr6-Vr7-Vr9

```

---

Scilab code Exa 19.14 determine resistor value for MOSFET amplifier

```

1 //chapter 19
2 //example 19.14
3 //page 849
4 printf("\n")
5 printf("given")
6 R6=100*10^3; R9=R6; Vth=1; Vr7=8; Vr8=14; Vr3=11.3; Vpout
    =10; Vpin=800*10^-3;
7 I6=Vth/R6
8 R7=Vr7/I6
9 R8=Vr8/I6
10 Ic1=1*10^-4; Ic2=Ic1; Vr2=9;
11 R2=Vr2/Ic1
12 R3=Vr3/(Ic1+Ic2)
13 R5=4.7*10^3;
14 Acl=Vpout/Vpin
15 R4=R5/(Acl-1)

```

---

**Scilab code Exa 19.15** bootstrap capacitor terminal voltage and peak output voltage

```
1 //chapter 19
2 //example 19.15
3 //page 854
4 printf("\n")
5 printf("given")
6 Vce=1.5;Vcc=17;Vd1=.7;R8=1.5*10^3;R9=R8;Rl=100;R6
    =8.2;
7 I4=(Vcc-Vd1)/(R8+R9)
8 Vc3=Vcc-(I4*R8);
9 printf(" bootstrap capacitance terminal voltage is
    %3.1fV\n",Vc3)
10 V=Vcc-Vce //V=Vp+Vr6
11 Ip=V/(Rl+R6)
12 Vp=Ip*Rl;
13 printf(" peak output voltage is %3.1fV\n",Vp)
14 Po=(Vp)^2 /(2*Rl);
15 printf(" peak output power is %dW\n",Po)
```

---

**Scilab code Exa 19.16** use BIFET to determine supply voltage and resistor value

```
1 //chapter 19
2 //example 19.16
3 //page 856
4 printf("\n")
5 printf("given")
6 Rl=8;Po=6;vs=.1;hFE=1000;Vce=2;f=50*10^3;Vd1=.7;
7 Vp=sqrt(2*Rl*Po)
8 Ip=Vp/Rl
9 R6=.1*Rl
10 R7=R6;
```

```

11 Vcc=Vp+Ip*R6+Vce
12 Ib=Ip/hFE
13 I4=2*10^-3;
14 R4=(Vcc-Vd1-Vd1)/I4
15 R8=.5*R4
16 Acl=Vp/vs
17 R3=100*10^3;
18 R2=R3/(Acl-1)
19 SR=(2*3.14*f*Vp)*10^-6;
20 printf(" slew rate is %3.2fV/us\n",SR)

```

---

### Scilab code Exa 19.17 capacitor value

```

1 //chapter 19
2 //example 19.17
3 //page 858
4 printf("\n")
5 printf("given")
6 f=50; R1=100*10^3; R2=1*10^3; R8=2.7*10^3; R9=R8;
7 C1=1/(2*3.14*f*.1*R1)
8 C2=1/(2*3.14*f*R2)
9 Xc3=.1*((R8*R9)/(R8+R9))
10 C3=1/(2*3.14*f*Xc3)
11 C4=C3

```

---

### Scilab code Exa 19.18 MOSFET gate source voltage for complementary common source am

```

1 //chapter 19
2 //example 19.18
3 //page 860
4 printf("\n")
5 printf("given")

```

```

6 Ismin=1.8*10^-3; Ismax=3.4*10^-3; R7=820; R5=390; R6
 =18*10^3; Vi=100*10^-3; Rl=10;
7 Vgsmin=Ismin*R7
8 Vgsmax=Ismax*R7
9 Acl=(R5+R6)/R5
10 Vp=Acl*Vi
11 Ip=Vp/Rl;
12 printf("peak output current is %3.3fA\n", Ip)
13 Po=(Vp*Ip)/2;
14 printf("peak output power is %3.2fW\n", Po)

```

---

**Scilab code Exa 19.19** calculate Vgsmax and Vgsmin

```

1 //chapter 19
2 //example 19.19
3 //page 862
4 printf("\n")
5 printf("given")
6 Vbe=.7; R2=560; R3min=0; R3max=1*10^3; Is=2*10^-3;
7 Ic2max=Vbe/(R2+R3min)
8 Ic2min=Vbe/(R2+R3max)
9 Vgsmin=(Is+Ic2min)*820
10 Vgsmax=(Is+Ic2max)*820

```

---

**Scilab code Exa 19.20** maximum peak output voltage minimum supply voltage at op amp

```

1 //chapter 19
2 //example 19.20
3 //page 865
4 printf("\n")
5 printf("given")
6 Vcc=12; Rl=10; R9 = 100; Rd=.5; gfs=2.5; R7=820; V9
 =1*10^3; R10=R9; Is=2.0*10^-3;

```

```

7 Vp=(Vcc*R1)/(Rd+R1)
8 Ip=Vp/R1
9 Vgs=Ip/gfs
10 Vr7=Is*R7
11 Vs=Vcc-Vr7-Vgs
12 disp(" op-amp peak output voltage is")
13 Vr9=(Vp*R9)/(R9+R10)

```

---

**Scilab code Exa 19.21** op amp minimum supply voltage and MOSFET maximum gate source

```

1 //chapter 19
2 //example 19.21
3 //page 867
4 printf("\n")
5 printf("given")
6 Vbe=.7; R2=470; R3=1*10^3; Is=.5*10^-3; R7=1.5*10^3; Vcc
=15;
7 Ic2max=Vbe/R2
8 Ic2min=Vbe/(R2+R3)
9 Vgs=(Is+Ic2max)*R7;
10 printf(" MOSFET maximum gate source voltage is %3.1
fV\n",Vgs)
11 Vs=Vcc-Vgs;
12 printf(" op-amp minimum supply is %3.2fV\n",Vs)

```

---

**Scilab code Exa 19.22** determine Po Acl f1 and f2

```

1 //chapter 19
2 //example 19.22
3 //page 868
4 printf("\n")
5 printf("given")

```

```

6 Vcc=15;R1=15;Rd=.3;R5=2.2*10^3;R6=33*10^3;C2
 =3.9*10^-6;C4=100*10^-12;
7 disp(" power output")
8 Vp=(Vcc*R1)/(Rd+R1)
9 Ip=Vp/R1
10 Po=(Vp*Ip)/2
11 disp(" voltage gain")
12 Av=(R5+R6)/R5
13 disp(" cutoff frequency")
14 f1=1/(2*3.14*C2*R5)
15 f2=1/(2*3.14*C4*R6)

```

---

**Scilab code Exa 19.23** maximum output power voltage gain and low cutoff frequency

```

1 //chapter 19
2 //example 19.23
3 //page 871
4 printf("\n")
5 printf("given")
6 Vcc=23;R1=8;Rf2=100*10^3;Rf1=5.6*10^3;Cf=1*10^-6;
7 Vp=Vcc-5
8 Po=(Vp)^2 /(2*R1);
9 printf("maximum output power is %3.2fW\n",Po)
10 Acl=(Rf1+Rf2)/Rf1;
11 printf(" voltage gain %3.1f\n",Acl)
12 f=1/(2*3.14*Cf*Rf1);
13 printf("lower cutoff frequency is %dHz\n",f)

```

---

**Scilab code Exa 19.24** determine the load power dissipation

```

1 //chapter 19
2 //example 19.24
3 //page 875

```

```

4 printf("\n")
5 printf("given")
6 Rf=15*10^3; R1=5.6*10^3; vs=.5; Vp=2.7; Rl=8.0;
7 Acl=(2*Rf)/R1
8 Vo=Acl*vs
9 Po=(Vp)^2 /(2*Rl);
10 printf("load power dissipation is %3.2fW\n",Po)

```

---

**Scilab code Exa 19.25** calculate ac output power dc input power conduction angle and efficiency

```

1 //chapter 19
2 //example 19.25
3 //page 880
4 printf("\n")
5 printf("given")
6 Vcc=10; Rl=1*10^3; f=3*10^6; Ip=25*10^-3; Vce=.3;
7 Vp=Vcc-Vce
8 Po=(Vp)^2 /(2*Rl)
9 T=1/f
10 t=(Po*T)/(Ip*Vp)
11 angle=(t/T)*360;
12 printf(" conduction angle is %3.1f degree\n",angle)
13 Idc=Po/Vp
14 Pi=Vcc*Idc;
15 printf( "dc input power is %3.4fW\n",Pi)
16 n=(Po/Pi)*100 //efficiency

```

---

**Scilab code Exa 19.26** for class C amplifier determine tank circuit component values

```

1 //chapter 19
2 //example 19.26
3 //page 882
4 printf("\n")

```

```

5 printf("given")
6 f=1*10^6; Xc=120; Vce=.5; Vcc=30; Rl=1.2*10^3; O=100;
7 Cp=1/(2*3.14*f*Xc)
8 Cp=1300*10^-12; //use standard value
9 Lp=1/(((2*3.14*f)^2)*Cp)
10 Vp=Vcc-Vce
11 Po=((Vp)^2) /(2*Rl)
12 Idc=Po/Vp
13 T=1/f
14 t=(O*T)/360
15 Ip=(Idc*T)/t

```

---

Scilab code Exa 19.27 for class C amplifier determine Ql Qp and P1 and bandwidth a

```

1 //chapter 19
2 //example 19.27
3 //page 883
4 printf("\n")
5 printf("given")
6 Rw=.1; f=1*10^6; Lp=19.5*10^-6; Rl=1.2*10^3; Vcc=30; Idc
    =12.3*10^-3; Vce=0.5;
7 Vp=Vcc-Vce;
8 Po=((Vp)^2) /(2*Rl);
9 QL=(2*3.14*f*Lp)/Rw
10 Qp=Rl/(2*3.14*f*Lp)
11 B=f/Qp
12 I1=(.707*Vp)/(2*3.14*f*Lp)
13 P1=(I1)^2 *Rw
14 Pi=(Vcc*Idc)+P1
15 n=(Po/Pi)*100

```

---

# Chapter 20

## Thyristors

Scilab code Exa 20.1 calculate instantaneous supply voltage

```
1 //chapter 20
2 //example 20.1
3 //page 902
4 printf("\n")
5 printf("given")
6 Vs=25; Vtm=1.7; Rl=25; Ih=5*10^-3;
7 Vspk=1.414*Vs
8 Ilpk=(Vs-Vtm)/Rl
9 disp(" for half wave rectifier sinusodial waveform")
10 Ilrms=.5*Ilpk
11 disp(" switch-off voltage")
12 es=Vtm+(Ih*Rl)
```

---

Scilab code Exa 20.2 determine suitable resistance

```
1 //chapter 20
2 //example 20.2
3 //page 905
```

```

4 printf("\n")
5 printf("given")
6 Vs=30; Vd1=.7; Vg=.8; Ig=200*10^-6;
7 Vspk=1.414*Vs
8 disp(" at 5 degree")
9 es=Vspk*.087 // sin5=.087
10 disp(" at 90 degree")
11 es=Vspk
12 Vt=Vd1+Vg
13 disp(" to trigger at es=3.7V the R2 moving contact
      is at the top")
14 es=3.7;
15 Vr1=es-Vt
16 I1=1*10^-3;
17 R1=Vr1/I1
18 R=Vt/I1 //R=R2+R3
19 disp(" to trigger at es =42.4 the R2 moving contact
      at the bottom")
20 es=42.4;
21 Vr3=Vt;
22 I1=es/(R+R1)
23 R3=Vt/I1
24 R2=R-R3

```

---

### Scilab code Exa 20.3 determine SCR anode cathode voltage

```

1 //chapter 20
2 //example 20.3
3 //page 906
4 printf("\n")
5 printf("given")
6 R1=2.2*10^3; R2=1.5*10^3; R3=120; Vt=1.5;
7 disp(" with R2 contact at center")
8 Vak=Vt*((R1+R2+R3)/(R3+.5*R2))
9 disp(" with R2 contact at zero")

```

```
10 Vak=Vt*((R1+R2+R3)/R3)
```

---

**Scilab code Exa 20.4** specify the SCR and suitable components for D1 and R1

```
1 //chapter 20
2 //example 20.4
3 //page 911
4 printf("\n")
5 printf("given")
6 Vs=5; Ilmax=300*10^-3; Vl=7; Vg=.8;
7 Vz=Vl-Vg
8 disp(" for D1, select a 1N753 with Vz=6.2")
9 Izmin=1*10^-3;
10 R1=Vg/Izmin
```

---

**Scilab code Exa 20.5** smallest conduction angle

```
1 //chapter 20
2 //example 20.5
3 //page 9
4 printf("\n")
5 printf("given")
6 R1=25*10^3; R2=2.7*10^3; C1=3*10^-6; Vg=.8; Vd1=8; Vs
    =115; f=60;
7 Vc1=Vd1+Vg
8 //assume the average charging voltage is
9 Vac=1.414*Vs
10 E=.636*Vac
11 //average charging
12 Ic=E/(R1+R2)
13 //charging time
14 t=(C1*Vc1)/Ic
15 T=1/f
```

```
16 q=(t*360)/T
17 disp(" concudtion angle")
18 a=180-q
```

---

### Scilab code Exa 20.6 determine capacitor charging time

```
1 //chapter 20
2 //example 20.6
3 //page 925
4 printf("\n")
5 printf("given")
6 Vs=10; Vf=1.7; Is=500*10^-6; Ih=1.5*10^-3; E=30; R
    =27*10^3; C=.5*10^-6;
7 R1max=(E-Vs)/Is
8 R1min=(E-Vf)/Ih
9 t=C*R*log((E-Vf)/(E-Vs));
10 printf(" capacitor charging time is %3.4 fs\n",t)
```

---

### Scilab code Exa 20.7 calculate maximum Vb1b2 be used at temperature 100C

```
1 //chapter 20
2 //example 20.7
3 //page 931
4 printf("\n")
5 printf("given")
6 Rbb=4*10^3; Pd25=360*10^-3; D=2.4*10^-3; T2=100;
7 Pd=Pd25-D*(T2-25)
8 Vb1b1=sqrt(Rbb*Pd);
9 printf(" maximum Vb1b1 that should be used at a temp
    100 is %3.1 fV\n",Vb1b1)
```

---

**Scilab code Exa 20.8 maximum and minimum triggering voltage**

```
1 //chapter 20
2 //example 20.8
3 //page 931
4 printf("\n")
5 printf("given")
6 Vb1b1=25; nmax=.86; nmin=.74; Vd=.7;
7 Vpmax=Vd+(nmax*Vb1b1)
8 Vpmin=Vd+(nmin*Vb1b1)
```

---

**Scilab code Exa 20.9 calculate Re for relaxation oscillator and oscillating freque**

```
1 //chapter 20
2 //example 20.9
3 //page 933
4 printf("\n")
5 printf("given")
6 Ip=.6*10^-6; Iv=2*10^-3; Veb1=2.5; Vpmin=19.2; Vpmax
    =22.2; Vbb=25; C=1*10^-6; R=18*10^3; Vp=20;
7 Vpmin=(Vbb-Vpmax)/Ip
8 Remax=(Vbb-Veb1)/Iv
9 t=C*R*log((Vbb-Veb1)/(Vbb-Vp))
10 f=1/t
```

---

# Chapter 21

## Optoelectronic Devices

Scilab code Exa 21.1 total luminous flux

```
1 //chapter 21
2 //example 21.1
3 //page 947
4 printf("\n")
5 printf("given")
6 r=3;Os=25;area=.25;
7 Ea=Os/(4*3.14*(r)^2)
8 Tf=Ea*area;
9 printf(" total flux is %3.3fW\n",Tf)
```

---

Scilab code Exa 21.3 suitable resistor

```
1 //chapter 21
2 //example 21.3
3 //page 951
4 printf("\n")
5 printf("given")
6 Vcc=9;Vf=1.6;Vb=7;hFE=100;Vce=.2;Ic=10*10^-3;Vbe=.7;
```

```
7 R2=(Vcc-Vf-Vce)/Ic
8 R2=680; //use standard value
9 Ic=(Vcc-Vf-Vce)/R2
10 Ib=Ic/hFE
11 Rb=(Vb-Vbe)/Ib
```

---

**Scilab code Exa 21.4 total power supplied to digit LED**

```
1 //chapter 21
2 //example 21.4
3 //page 952
4 printf("\n")
5 printf("given")
6 Vcc=5;
7 N=(3*7)+(1*2)
8 It=N*10*10^-3
9 P=It*Vcc
```

---

**Scilab code Exa 21.5 required series resistance and dark current**

```
1 //chapter 21
2 //example 21.5
3 //page 957
4 printf("\n")
5 printf("given")
6 Rc=1*10^3; I=10*10^-3; E=30;
7 R1=E/I -Rc
8 R1=1.8*10^3; //use standard value
9 disp(" when dark Rc=100Kohm")
10 Rc=100*10^3;
11 I=E/(R1+Rc)
```

---

**Scilab code Exa 21.6 minimum light level when transitor is turn off**

```
1 //chapter 21
2 //example 21.6
3 //page 958
4 printf("\n")
5 printf("given")
6 Vee=6; Vbe=.7; Ib=200*10^-6; Vb=.7; Vcc=6;
7 disp("when cell is dark Rc=100Kohm")
8 Rc=100*10^3;
9 Vrc=Vee+Vbe
10 Irc=Vrc/Rc
11 Ir1=Irc+Ib
12 Vr1=Vcc-Vb
13 R1=Vr1/Ir1
14 R1=18*10^3; //use standard value
15 disp(" when Q1 is off")
16 Vr1=6; Vrc=6;
17 Ir1=Vr1/R1
18 Rc=Vrc/Ir1
```

---