

Scilab Textbook Companion for  
Electronic Devices And Circuits  
by D. A. Bell<sup>1</sup>

Created by  
Vaibhav Singh  
B.Tech(pursuing)  
Electronics Engineering  
NIT kurukshetra  
College Teacher  
Karan Sharma  
Cross-Checked by  
Prashant Dave

May 8, 2014

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electronic Devices And Circuits

**Author:** D. A. Bell

**Publisher:** Oxford University Press

**Edition:** 5

**Year:** 2008

**ISBN:** 0-19-569340

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	5
1 basic semiconductor and pn junction theory	13
2 semiconductor diodes	17
3 Diode applications	24
4 Bipolar junction transistors	38
5 BJT biasing	41
6 Ac analysis of BJT circuits	53
8 BJT specifications and performance	61
10 FET biasing	67
11 Ac analysis of FET circuits	74
12 Small signal Amplifiers	78
13 Amplifier with negative feedback	93
14 Ic operational Amplifier and basic Op amp circuits	101
15 Operational amplifier frequency Response and compensation	109
16 Signal generators	113

17 Active filters	120
18 Linear and switching voltage regulators	127
19 Power amplifiers	136
20 Thyristors	151
21 Optoelectronic Devices	156

# List of Scilab Codes

Exa 1.1	resultant densities . . . . .	13
Exa 1.2	drift current velocity . . . . .	14
Exa 1.3	conductivity and resistance . . . . .	14
Exa 1.4	reverse saturation current . . . . .	15
Exa 1.5	junction current . . . . .	15
Exa 1.6	junction forward voltage . . . . .	16
Exa 1.1	forward and reverse resistance . . . . .	17
Exa 2.1	dynamic resistance . . . . .	17
Exa 2.3	diode current . . . . .	18
Exa 2.5	forward current . . . . .	18
Exa 2.6	dc load line . . . . .	19
Exa 2.8	new supply voltage . . . . .	19
Exa 2.9	maximum forward current . . . . .	20
Exa 2.10	diode Vf and junction dynamic resistance . . . . .	20
Exa 2.11	diffusion capacitance . . . . .	21
Exa 2.12	minimum fall times . . . . .	21
Exa 2.14	resistor for R1 and appropriate scale . . . . .	22
Exa 2.15	maximum current . . . . .	22
Exa 2.16	diode current and power dissipation . . . . .	23
Exa 2.17	upper and lower limit of Vz . . . . .	23
Exa 3.1	peak output volatge laod current peak reverse voltage	24
Exa 3.2	peak output voltage and current . . . . .	24
Exa 3.3	peak to peak voltage . . . . .	25
Exa 3.4	required reservoir capacitance . . . . .	25
Exa 3.5	charging and discharging time . . . . .	26
Exa 3.6	required surge limiting resistance . . . . .	26
Exa 3.7	transformer for half wave rectifier . . . . .	27
Exa 3.8	required reservoir capacitance . . . . .	27

Exa 3.9	required reservoir capacitance . . . . .	28
Exa 3.10	calculate surge limiting resistance . . . . .	28
Exa 3.11	specify transformer for full wave rectifier . . . . .	29
Exa 3.12	dc output voltage and outpur ripple amplitude . . . . .	29
Exa 3.13	suitable value of L1 and C1 . . . . .	30
Exa 3.14	peak output voltage and value of L1 and C1 . . . . .	30
Exa 3.15	load and source effects and load and line regulation . .	31
Exa 3.16	circuit current . . . . .	31
Exa 3.17	maximum load current . . . . .	31
Exa 3.18	line regulation laod regulation and ripple rejection ratio	32
Exa 3.19	resistance R1 and forward and reverse current . . . . .	33
Exa 3.20	resistance R1 and forward current and reverse voltage	33
Exa 3.21	resistor for R1 . . . . .	34
Exa 3.22	zener diode and R1 . . . . .	34
Exa 2.23	tilt on output waveform . . . . .	34
Exa 3.24	suitable value of R1 and C1 . . . . .	35
Exa 3.25	capacitor voltage . . . . .	35
Exa 3.26	determine C1 and C2 . . . . .	36
Exa 3.27	diode forward current . . . . .	36
Exa 4.1	calculate Ic and Ie . . . . .	38
Exa 4.2	new base current . . . . .	38
Exa 4.3	dc collector voltage and circuit voltage gain . . . . .	39
Exa 4.4	calculate Ic Ib and hFE . . . . .	39
Exa 4.6	determine Ib and Ic . . . . .	40
Exa 5.1	new dc load line . . . . .	41
Exa 5.2	circuit Q point . . . . .	41
Exa 5.3	determine Ib Ic and Vce . . . . .	42
Exa 5.4	maximum and minimum level of Ic and Vce . . . . .	42
Exa 5.5	determine Ib Ic and Vce . . . . .	43
Exa 5.7	emitter voltage collector voltage and collector and emit- ter voltage . . . . .	43
Exa 5.8	determine Ic Ve Vc vce . . . . .	44
Exa 5.9	analyze voltage divider bais circuit for hFE 50 . . . . .	44
Exa 5.10	analyze voltage divider bais circuit for hFE is 200 . . . .	45
Exa 5.11	design base bias circuit . . . . .	45
Exa 5.12	collector to base bais circuit . . . . .	46
Exa 5.13	design voltage divider bais circuit . . . . .	46
Exa 5.14	design voltage divider bais circuit . . . . .	46

Exa 5.15	design bias circuit operate from 18V supply . . . . .	47
Exa 5.16	design bias circuit operate from 9V supply . . . . .	48
Exa 5.17	stability factors for three bias circuit . . . . .	49
Exa 5.18	determine $I_c$ change when temperature increases . . . . .	49
Exa 5.19	change in $I_c$ by effect of change in $V_{be}$ . . . . .	50
Exa 5.20	calculate minimum hFE and transistor $V_{ce}$ . . . . .	50
Exa 5.21	calculate minimum hFE for transistor . . . . .	51
Exa 5.22	determine suitable resistance for $R_b$ and $R_c$ . . . . .	51
Exa 5.23	suitable resistor for capacitor coupled switching . . . . .	52
Exa 6.1	calculate base bias voltage . . . . .	53
Exa 6.2	Dc and Ac load line . . . . .	53
Exa 6.3	determine hfe and hoe . . . . .	54
Exa 6.4	calculate hfc hob and alfa . . . . .	55
Exa 6.5	estimate the CE input resistance . . . . .	55
Exa 6.6	circuit input and output impedance voltage gain . . . . .	56
Exa 6.7	estimate $r_e$ and circuit voltage gain . . . . .	56
Exa 6.8	circuit input and output impedance and voltage gain . . . . .	57
Exa 6.9	circuit input and output impedance with $R_l$ not connected . . . . .	57
Exa 6.10	circuit input and output impedance and voltage gain . . . . .	58
Exa 6.11	input impedance and voltage gain when $C_1$ is disconnected . . . . .	58
Exa 6.12	calculate $v_o$ . . . . .	59
Exa 6.13	calculate $I_c$ $I_e$ and $I_b$ . . . . .	60
Exa 8.2	output power change . . . . .	61
Exa 8.3	output power change . . . . .	61
Exa 8.4	input capacitance . . . . .	62
Exa 8.5	input capacitance limited upper cutoff frequency . . . . .	62
Exa 8.6	upper 3db frequency . . . . .	63
Exa 8.8	calculate suitable speed up capacitor . . . . .	63
Exa 8.9	noise output voltage . . . . .	64
Exa 8.10	total noise output voltage for amplifier . . . . .	64
Exa 8.11	calculate maximum $I_c$ . . . . .	65
Exa 8.13	maximum power dissipation . . . . .	65
Exa 8.14	thermal resistance . . . . .	66
Exa 10.1	Dc load line . . . . .	67
Exa 10.4	determine $I_{dmax}$ and $I_{dmin}$ . . . . .	67
Exa 10.6	$I_d$ max $I_{dmin}$ and $V_{ds}$ . . . . .	68



Exa 10.7	gate bias circuit . . . . .	68
Exa 10.8	self bias circuit . . . . .	69
Exa 10.9	design voltage divider bias circuit . . . . .	69
Exa 10.11	constant current bias circuit . . . . .	70
Exa 10.12	determine $I_d$ and $V_{ds}$ . . . . .	70
Exa 10.13	determine $I_{dmax}$ and $V_{dsmin}$ . . . . .	71
Exa 10.14	determine $I_d$ and $V_{ds}$ . . . . .	72
Exa 10.16	design JFET switching . . . . .	72
Exa 10.17	determine suitable resistance and calculate $V_{ds}$ . . . . .	72
Exa 11.2	circuit input and output impedance and voltage gain . . . . .	74
Exa 11.3	gate input and source output impedance and voltage gain . . . . .	74
Exa 11.4	circuit input and output impedance and voltage gain . . . . .	75
Exa 11.5	circuit and device input and output impedance and voltage gain . . . . .	75
Exa 11.6	output voltage . . . . .	76
Exa 11.7	input capacitance limited cutoff frequency . . . . .	77
Exa 12.1	required capacitance and voltage gain at different frequency . . . . .	78
Exa 12.2	suitable resistor for common emitter amplifier . . . . .	79
Exa 12.3	suitable capacitor for CE . . . . .	79
Exa 12.4	suitable resistor for common source circuit . . . . .	80
Exa 12.5	suitable resistor for common source amplifier . . . . .	80
Exa 12.7	analyze two stage amplifier . . . . .	81
Exa 12.8	resistor for two stage direct coupled amplifier . . . . .	81
Exa 12.9	capacitor for two stage direct coupled amplifier . . . . .	82
Exa 12.10	minimum overall voltage gain . . . . .	82
Exa 12.11	resistor for two stage amplifier . . . . .	83
Exa 12.12	suitable capacitor for circuit . . . . .	84
Exa 12.13	analyze two stage amplifier and determine minimum voltage gain . . . . .	84
Exa 12.14	Dc feedback pair with an emitter follower output . . . . .	85
Exa 12.15	suitable resistor for BIFET amplifier . . . . .	86
Exa 12.16	suitable capacitor For BIFET direct coupled amplifier . . . . .	87
Exa 12.17	determine minimum overall voltage gain . . . . .	87
Exa 12.18	suitable resistor for differential amplifier . . . . .	88
Exa 12.19	suitable capacitor value for amplifier and voltage gain . . . . .	88
Exa 12.20	suitable resistor for cascode amplifier . . . . .	89
Exa 12.21	suitable capacitor for cascode circuit . . . . .	89

Exa 12.22	resonance frequency voltage gainbandwidth of amplifier	90
Exa 12.23	resonance frequency voltage gainbandwidth of amplifier	91
Exa 12.24	capacitor to resonate secondry and overall voltage gain	91
Exa 13.1	closed loop gain for negative feedback amplifier . . . . .	93
Exa 13.2	input impedance with negative feedback . . . . .	93
Exa 13.3	input and output impedance when negative feedback .	94
Exa 13.4	circuit input and output impedance and voltage gain without feedback . . . . .	94
Exa 13.5	two stage coupled BJT use as voltage feedback . . . . .	95
Exa 13.6	modify direct coupled amplifier to use as series voltage negative feedback . . . . .	95
Exa 13.7	calculate resistor value . . . . .	96
Exa 13.8	calculate Acl Zin and Zout . . . . .	96
Exa 13.9	calculate output impedance for circuit modification . .	97
Exa 13.10	calculate precise value of circuit voltage gain . . . . .	97
Exa 13.11	modify Ce amplifier to use emitter current feedback to give Av 70 . . . . .	98
Exa 13.12	suitable emitter resistor value . . . . .	98
Exa 13.13	suitable capacitor for two stage circuit . . . . .	99
Exa 13.14	determine current gain and input impedance . . . . .	100
Exa 13.15	calculate total harmonic . . . . .	100
Exa 14.1	calculate maximum resistance . . . . .	101
Exa 14.2	suitable resistor for BIFET op amp is used . . . . .	101
Exa 14.3	typical difference between input and out voltage and Zin and Zout . . . . .	102
Exa 14.4	capacitor coupled voltage follower usin 741 op amp . .	102
Exa 14.5	direct coupled non inverting amplifier . . . . .	103
Exa 14.6	typical input and output impedances for non inverting	103
Exa 14.7	voltage gain and lower cutoff frequency . . . . .	104
Exa 14.8	direct coupled inverting amplifier . . . . .	104
Exa 14.9	design three input summing amplifier . . . . .	105
Exa 14.10	suitable resistor for 741 op amp . . . . .	105
Exa 14.11	overall voltage gain for instrumentation amplifier . . .	105
Exa 14.12	typical output voltage swingand calculate rise time . .	106
Exa 14.13	calculate resistor for schmitt trigger circuit . . . . .	107
Exa 14.14	upper and lower trigger for non inverting schmitt trigger	107
Exa 15.2	determine suitable component . . . . .	109
Exa 15.3	miller effect capacitor . . . . .	109

Exa 15.5	cutoff frequencies using gain bandwidth . . . . .	110
Exa 15.6	full power bandwidth for AD843 op amp circuit . . . . .	110
Exa 15.7	input terminal stray capacitor . . . . .	111
Exa 15.8	load capacitance . . . . .	111
Exa 16.1	phase shift oscillator . . . . .	113
Exa 16.2	colpitts oscillator . . . . .	113
Exa 16.3	hartley oscillator . . . . .	114
Exa 16.4	wein bridge oscillator . . . . .	115
Exa 16.5	phase shift oscillator . . . . .	116
Exa 16.6	amplitude stabilization circuit . . . . .	116
Exa 16.7	square wave generator . . . . .	117
Exa 16.8	calculate t1 t2 and pulse frequency . . . . .	117
Exa 16.10	triangular wave generator . . . . .	118
Exa 16.11	wein bridge oscillator . . . . .	118
Exa 16.12	pierce oscillator and peak power dissipated . . . . .	119
Exa 17.1	calculate attenuation . . . . .	120
Exa 17.2	first order active low pass filter . . . . .	120
Exa 17.3	first order high pass filter and filter bandwidth . . . . .	121
Exa 17.4	butterworth second order low pass filter . . . . .	121
Exa 17.5	using BIFET op amp design butterworth second order filter . . . . .	122
Exa 17.6	third order low pass filter . . . . .	122
Exa 17.7	third order high pass filter . . . . .	123
Exa 17.8	single stage band pass filter . . . . .	124
Exa 17.9	calculate Q factor for wide band filter . . . . .	124
Exa 17.10	center frequency and bandwidth . . . . .	125
Exa 17.12	state variable band pass filter . . . . .	125
Exa 17.13	required resistance to operate one half of an MF10 . . . . .	126
Exa 18.1	load and source effects and load and line regulation . . . . .	127
Exa 18.2	voltage regulator circuit . . . . .	128
Exa 18.3	modify voltage regulator . . . . .	128
Exa 18.4	voltage regulator to change the load current . . . . .	129
Exa 18.5	suitable component for preregulator circuit . . . . .	129
Exa 18.6	differential amplifier . . . . .	130
Exa 18.7	fold back current limiting circuit for voltage regulator . . . . .	131
Exa 18.8	adjustable voltage regulator circuit . . . . .	131
Exa 18.9	input voltage and maximum load current . . . . .	132
Exa 18.10	calculate regulator power dissipation . . . . .	133

Exa 18.11	efficiencies of linear regulator and switching regulator .	133
Exa 18.12	step down switching regulator . . . . .	134
Exa 18.13	determine suitable value for R1 R2 Rsc and Ct . . . .	134
Exa 19.1	Dc and Ac load line transistor common emitter characteristics . . . . .	136
Exa 19.2	maximum efficiency of class A amplifier . . . . .	136
Exa 19.4	power deliver to load in class AB amplifier . . . . .	137
Exa 19.5	output transformer and transistor of class B circuit . .	138
Exa 19.6	determine required supply voltage for class AB amplifier	138
Exa 19.7	output transistors . . . . .	139
Exa 19.8	capacitor value for Ce and Co . . . . .	139
Exa 19.9	determine the value of Vcc Rc and Rb for class AB amplifier . . . . .	140
Exa 19.10	design Vbe multiplier . . . . .	140
Exa 19.11	required supply voltage and specify output transistors	141
Exa 19.12	suitable resistor for output and intermediate stage . .	142
Exa 19.13	calculate required supply voltage and suitable DC voltage drop . . . . .	142
Exa 19.14	determine resistor value for MOSFET amplifier . . . .	143
Exa 19.15	bootstrap capacitor terminal voltage and peak output voltage . . . . .	144
Exa 19.16	use BIFET to determine supply voltage and resistor value	144
Exa 19.17	capacitor value . . . . .	145
Exa 19.18	MOSFET gate source voltage for complementary common source amplifier . . . . .	145
Exa 19.19	calculate Vgsmax and Vgsmin . . . . .	146
Exa 19.20	maximum peak output voltage minimum supply voltage at op amp terminal . . . . .	146
Exa 19.21	op amp minimum supply voltage and MOSFET maximum gate source voltage . . . . .	147
Exa 19.22	determine Po Acl f1 and f2 . . . . .	147
Exa 19.23	maximum output power voltage gain and low cutoff frequency . . . . .	148
Exa 19.24	determine the load power dissipation . . . . .	148
Exa 19.25	calculate ac output power dc input power conduction angle and efficiency . . . . .	149
Exa 19.26	for class C amplifier determine tank circuit component value and peak current . . . . .	149

Exa 19.27	for class C amplifier determine $Q_l$ $Q_p$ and $P_l$ and bandwidth and efficiency . . . . .	150
Exa 20.1	calculate instantaneous supply voltage . . . . .	151
Exa 20.2	determine suitable resistance . . . . .	151
Exa 20.3	determine SCR anode cathode voltage . . . . .	152
Exa 20.4	specify the SCR and suitable components for D1 and R1	153
Exa 20.5	smallest conduction angle . . . . .	153
Exa 20.6	determine capacitor charging time . . . . .	154
Exa 20.7	calculate maximum $V_{b1b2}$ be used at temperature 100C	154
Exa 20.8	maximum and minimum triggering voltage . . . . .	155
Exa 20.9	calculate $R_e$ for relaxation oscillator and oscillating frequency . . . . .	155
Exa 21.1	total luminous flux . . . . .	156
Exa 21.3	suitable resistor . . . . .	156
Exa 21.4	total power supplied to digit LED . . . . .	157
Exa 21.5	required series resistance and dark current . . . . .	157
Exa 21.6	minimum light level when transistor is turn off . . . . .	158

# Chapter 1

## basic semiconductor and pn junction theory

Scilab code Exa 1.1 resultant densities

```
1 //chapter 1
2 //example 1.1
3 //page 15
4 printf("\n")
5 printf("given")
6 Nd=3*10^14;Na=.5*10^14;//all in atom/cm^3
7 ni=1.5*10^10;
8 disp("resultant densities of free electrons and hole
    ")
9 ne=(-(Na-Nd)+(sqrt(((Na-Nd)^2)+4*ni^2)))/2;
10 disp(ne)//electron densities in electron/cm^3
11 Nd>Na;
12 n=Nd-Na;
13 disp(n)
14 p=(ni^2)/n
15 printf("densities of hole is %dhole/cm3\n",p)
```

---

### Scilab code Exa 1.2 drift current velocity

```
1 //chapter 1
2 //example 1.2
3 //page 18
4 printf("\n")
5 printf(" given ")
6 l=1*10^-3;E=10;
7 un=1500*10^-4;up=500*10^-4;
8 Vn=-(un*E)/l;
9 printf(" drift current is %dm/s\n",Vn)
10 disp(" drift current of hole")
11 Vp=(up*E)/l;
12 printf(" drift current is %dm/s\n",Vp)
```

---

### Scilab code Exa 1.3 conductivity and resistance

```
1 //chapter 1
2 //example 1.3
3 //page 19
4 printf("\n")
5 printf(" given ")
6 l=1*10^-3;a=.1*10^-4;
7 ni=1.5*10^10;p=1.5*10^10;
8 disp(" a")
9 un=1500;up=500;//in cm3/V.s
10 q=1.6*10^-19;
11 m=q*((ni*un)+(p*up))*10^6;
12 printf(" mobility is %3.2fmicro/ohmcm\n",m)
13 R=1/(m*a);
14 printf(" resistance is %3.2fMohm\n",R)
15 disp(" b")
16 //for doped material
17 n=8*10^13;
18 p=(ni^2)/n
```

```
19 m=q*((n*un)+(p*up));
20 printf("mobility is %3.4f/ohmcm\n",m)
21 R=1/(m*a);
22 printf(" resistance is %dohm\n",R)
```

---

#### Scilab code Exa 1.4 reverse saturation current

```
1 //chapter 1
2 // example 1.4
3 //page 26
4 printf("\n")
5 printf(" given")
6 T1=25;T2=35;T3=45;
7 I0=30//nA
8 disp(" I0 (35)=I0*2^((T2-T1)/10)")
9 //on solving
10 I0(35)=I0*2^((T2-T1)/10);
11 printf(" current at 35c is %dnA\n",I0(35))
12 disp(" I0 (45)=I0*2^((T3-T1)/10)")
13 //on solving
14 I0(45)=30*2^2;
15 printf(" current at 45c is %dnA\n",I0(45))
```

---

#### Scilab code Exa 1.5 junction current

```
1 //chapter 1
2 //example 1.5
3 //page 28
4 printf("\n")
5 printf(" given")
6 I0=30;Vd=.7;n=2;Vt=26*10^-3;
7 k=Vd/(n*Vt);
8 disp(" junction current")
```



```

9 Id=I0*((2.7^k)-1)*10^-6
10 printf(" forward bais current is %dmA\n",Id)
11 disp("b)")
12 Vd=-10// reverse bais
13 k=Vd/(n*Vt);
14 Id=I0*((2.7^k)-1)
15 printf(" forward bais current is %dnA\n",Id)

```

---

### Scilab code Exa 1.6 junction forward voltage

```

1 //chapter 1
2 //example 1.6
3 //page 29
4 printf("\n")
5 printf(" given")
6 Id=.1*10^-3;n=2;vt=26*10^-3;
7 I0=30*10^-9;
8 disp(" a)")
9 Vd=(n*Vt)*log(Id/I0)*10^3;
10 printf(" forward bais current is %dmV\n",Vd)
11 disp(" b)")
12 Id=10*10^-3
13 Vd=(n*Vt)*log(Id/I0)*10^3;
14 printf(" forward bais current is %dmV\n",Vd)

```

---

# Chapter 2

## semiconductor diodes

Scilab code Exa 1.1 forward and reverse resistance

```
1 //chapter 2
2 //example 2.1
3 //page 37
4 printf("\n")
5 printf("given")
6 disp("a")
7 If=100*10^-3; Vf=.75; //given
8 disp("forward resistance")
9 Rf=Vf/If;
10 printf("forward resistnace is %3.1fohm\n",Rf)
11 disp("b")
12 Vr=50; Ir=100*10^-9;
13 Rr=(Vr/Ir);
14 printf("reverse resistnace is %3.0fohm\n",Rr)
```

---

Scilab code Exa 2.1 dynamic resistance

```
1 //chapter 2
```

```

2 //example 2.2
3 //page 39
4 printf("\n")
5 printf("given")
6 If=70*10^-3;
7 rd=(26*10^-3)/If;
8 printf("dynamic resistance is %3.2fohm\n",rd)
9 disp("a)")
10 If=60*10^-3;Vf=.025;
11 rd=Vf/If;
12 printf("dynamic resistance is %3.2fohm\n",rd)

```

---

#### Scilab code Exa 2.3 diode current

```

1 //chapter 2
2 //example 2.3
3 //page 40
4 printf("\n")
5 printf("given")
6 R1=4.7*10^3;E=15;Vf=.7;
7 disp("diode current is E=If*R1+Vf")
8 If=((E-Vf)/R1)*10^3;
9 printf(" diode current is %3.2fmA\n",If)

```

---

#### Scilab code Exa 2.5 forward current

```

1 //chapter 2
2 //example 2.5
3 //page 41
4 printf("\n")
5 printf("given")
6 E=1.5;Vf=.7;R1=10;rd=.25;
7 disp("a)")

```

```

8 If=(E-Vf)/R1;
9 printf(" forward current is %3.3fmA\n",If)
10 disp("b")
11 If=(E-Vf)/(R1+rd);
12 printf(" forward current is %3.3fmA\n",If)

```

---

### Scilab code Exa 2.6 dc load line

```

1 //chapter 2
2 //example 2.6
3 //page 43
4 printf("\n")
5 printf(" given")
6 If=0;Vf=5;R1=100;
7 E=(If*R1)+Vf
8 disp("E")
9 disp("B")
10 Vf=0;E=5;R1=100;
11 If=(E/R1)*1000;
12 printf(" resistance is %dmA\n",If)

```

---

### Scilab code Exa 2.8 new supply voltage

```

1 //chapter 2
2 //example 2.8
3 //page 45
4 printf("\n")
5 printf(" given")
6 If=50*10^-3;Vf=1.1;R1=100;
7 Vf1=If*R1;
8 disp(" Vf1")
9 E=Vf1+Vf
10 printf(" new supply voltage is %3.1fV\n",E)

```

---

**Scilab code Exa 2.9** maximum forward current

```
1 //chapter 2
2 //example 2.9
3 //page 48
4 printf("\n")
5 printf("given")
6 P1=700*10^-3; Vf=.7;
7 //at 25C
8 If=P1/Vf;
9 disp("If")
10 //at 65C
11 D=5*10^-3; T=65-25;
12 P2=P1-D*T
13 If=P2/Vf;
14 printf("maximum forward current at 65C is %3.3fA\n",
        ,If)
```

---

**Scilab code Exa 2.10** diode Vf and junction dynamic resistance

```
1 //chapter 2
2 //example 2.10
3 //page 49
4 printf("\n")
5 printf("given")
6 Vf1=.7; Vf=-1.8*10^-3; If=26*10^-3;
7 T=100-25;
8 Vf2=Vf1+(T*Vf);
9 printf("voltage at 100C is %3.3fV\n", Vf2)
10 disp("At 25C")
11 T1=25;
```

```

12 rd=(26*10^-3/If)*((T1+273)/298);
13 printf(" resistance at 25 C is %dohm\n",rd)
14 disp(" At 100C")
15 T2=100;
16 rd=(26*10^-3/If)*((T2+273)/298);
17 printf(" resistance at 100 C is %3.2fohm\n",rd)

```

---

### Scilab code Exa 2.11 diffusion capacitance

```

1 //chapter 2
2 //example 2.11
3 //page 51
4 printf("\n")
5 printf(" given")
6 If=10*10^-3;Vf=.7;t=70*10^-9;
7 Cd=((t*If)/Vf)*10^9;
8 printf(" diffusion capacitance is %dnF\n",Cd)

```

---

### Scilab code Exa 2.12 minimum fall times

```

1 //chapter 2
2 //example 2.12
3 //page 53
4 printf("\n")
5 printf(" given")
6 disp("A")
7 trr=10*10^-9;
8 tf=10*trr*10^9
9 printf("minimum fall times is %dns\n",tf)
10 disp("B")
11 trr=3;
12 tf=10*trr;
13 printf("minimum fall times is %dns\n",tf)

```

---

**Scilab code Exa 2.14** resistor for R1 and appropriate scale

```
1 //chapter 2
2 //example 2.14
3 //page 58
4 printf("\n")
5 printf("given")
6 Io=75*10^-3;
7 //vertical scale of 5mA/cm
8 If=Io/5*10^-3
9 R1=15/(75*10^-3)
10 P=((Io)^2)*R1
```

---

**Scilab code Exa 2.15** maximum current

```
1 //chapter 2
2 //example 2.15
3 //page 63
4 printf("\n")
5 printf("given")
6 Vz=7.5;Pd=400*10^-3;D=3.2*10^-3;
7 Izm=Pd/Vz
8 printf("current at 50C is %3.3fA\n",Izm)
9 disp("At 100C")
10 P2=Pd-((100-50)*D)
11 printf("power at 100C is %3.3fW\n",P2)
12 Izm=P2/Vz;
13 printf("current at 100C is %3.3fA\n",Izm)
```

---

**Scilab code Exa 2.16** diode current and power dissipation

```
1 //chapter 2
2 //example 2.16
3 //page 64
4 printf("\n")
5 printf(" given")
6 E=20;R1=620;Vz=7.5;
7 Vr1=E-Vz
8 Iz=Vr1/R1;
9 printf(" diode current is %3.5fA\n",Iz)
10 Pd=Vz*Iz;
11 printf(" power dissipation is %3.3fW\n",Pd)
```

---

**Scilab code Exa 2.17** upper and lower limit of Vz

```
1 //chapter 2
2 //example 2.17
3 //page 64
4 printf("\n")
5 printf(" given")
6 Vz=4.3;Zz=22;Iz=20*10^-3;
7 Iz1=5*10^-3;//change in current
8 Vz1=Iz1*Zz;
9 Vzmax=Vz+Vz1;
10 printf(" maximum voltage is %3.3fV\n",Vzmax)
11 Vzmin=Vz-Vz1;
12 printf(" minimum voltage is %3.3fV\n",Vzmin)
```

---



# Chapter 3

## Diode applications

**Scilab code Exa 3.1** peak output voltage load current peak reverse voltage

```
1 //chapter 3
2 //example 3.1
3 //page 73
4 printf("\n")
5 printf("given")
6 Vf=.7;Rl=500;Vi=22;
7 Vpi=1.414*Vi;
8 disp("Vpi")
9 Vpo=Vpi-Vf;
10 printf(" peak voutput voltage is %3.2fV\n",Vpo)
11 Ip=Vpo/Rl;
12 printf("peak load current is %3.4fA\n",Ip)
13 PIV=Vpi;
14 printf("diode peak reverse voltage %3.2fV\n",PIV)
```

---

**Scilab code Exa 3.2** peak output voltage and current

```
1 //chapter 3
```

```

2 //example 3.2
3 //page 779
4 printf("\n")
5 printf("given")
6 Vi=30;Rl=300;Vf=.7;
7 Vpi=1.414*Vi;
8 Vpo=Vpi-2*Vf;
9 printf(" peak output voltage %dV\n",Vpo)
10 Ip=Vpo/Rl;
11 printf(" current bridge is %3.3fA\n",Ip)

```

---

**Scilab code Exa 3.3** peak to peak voltage

```

1 //chapter 3
2 //example 3.3
3 //page 83
4 printf("\n")
5 printf("given")
6 C1=680*10^-6;Eo=28;Rl=200;f=60;
7 Il=Eo/Rl;
8 T=1/f;
9 t1=T;
10 Vr=(Il*t1)/C1;
11 printf("peak to peak ripple voltage is %3.2fV\n",Vr)

```

---

**Scilab code Exa 3.4** required reservoir capacitance

```

1 //chapter 3
2 //example 3.4
3 //page 84
4 printf("\n")
5 printf("given")
6 Eo=20;Rl=500;f=60;

```

```

7 Vr=(10*Eo)/100 //10% of Eo
8 I1=Eo/R1
9 T=1/f;
10 t1=T
11 C1=((I1*t1)/Vr)*10^6;
12 printf("reservior capacitance is %duF\n",C1)

```

---

**Scilab code Exa 3.5** charging and discharging time

```

1 //chapter 3
2 //example 3.5
3 //page 85
4 printf("\n")
5 printf("given")
6 Eo=20;f=60;R1=500;
7 I1=Eo/R1;
8 Vr=(10*Eo)/100;
9 printf("10percent of Eo is %dV\n",Vr)
10 Eomin=Eo-.5*Vr
11 Eomax=Eo+.5*Vr
12 Q1=sin(inv(Eomin/Eomax));
13 Q1=65
14 Q2=90-Q1
15 T=1/f;
16 t2=(Q2*T)/360;
17 printf(" charging time is %3.4 fs\n",t2)
18 t1=T-t2
19 printf("discharging time is %3.4 fs\n",t1)
20 C1=((I1*t1)/Vr)*10^6;
21 printf("reservior capacitance is %duF\n",C1)

```

---

**Scilab code Exa 3.6** required surge limiting resistance

```

1 //chapter 3
2 //example 3.6
3 //page 88
4 printf("\n")
5 printf(" given")
6 Eo=21; Vf=.7;
7 t1=1.16*10^-3; t2=15.54*10^-3;
8 Vp=Eo+Vf
9 Vr=2*Vp
10 I1=40*10^-4;
11 Ifrm=(I1*(t1+t2))/t2;
12 Ifsm=30;
13 Rs=Vp/Ifsm
14 printf(" surge limiting resistance is %3.2fohm\n",Rs
    )

```

---

**Scilab code Exa 3.7** transformer for half wave rectifier

```

1 //chapter 3
2 //example 3.7
3 //page 89
4 printf("\n")
5 printf(" given")
6 Vf=.7; Eo=21; I1=40*10^-3; Vp=115;
7 Vs=.707*(Vf+Eo);
8 printf(" Vrms voltage is %3.3fV\n",Vs)
9 Is=3.6*I1;
10 printf(" rms current is %3.3fA\n",Is)
11 Ip=(Vs*Is)/Vp;
12 printf(" primary current is %3.3fA\n",Ip)

```

---

**Scilab code Exa 3.8** required reservoir capacitance

```

1 //chapter 3
2 //example 3.8
3 //page 92
4 printf("\n")
5 printf(" given")
6 Vr=2;T=16.7*10^-3;t2=1.16*10^-3;I1=40*10^-3; //from
   example 3.5
7 t1=(T/2)-t2
8 C1=(I1*t1)/Vr;
9 printf(" resrvior capacitor is %3.6 fF\n",C1)

```

---

**Scilab code Exa 3.9** required reservoir capacitance

```

1 //chapter 3
2 //example 3.9
3 //page 93
4 printf("\n")
5 printf(" given")
6 Vr=2;T=16.7*10^-3;I1=40*10^-3;
7 t1=T/2
8 C1=(I1*t1)/Vr;
9 printf(" reservoir capacitance is %3.6 fF\n",C1)

```

---

**Scilab code Exa 3.10** calculate surge limiting resistance

```

1 //chapter 3
2 //example 3.10
3 //page 93
4 printf("\n")
5 printf(" given")
6 Eo=21;Vf=.7;I1=40*10^-3;t1=7.19*10^-3;t2=1.16*10^-3;
7 Vp=Eo+(2*Vf)
8 Vr=Vp

```

```

9 If=I1/2
10 Ifrm=I1*(t1+t2)/t2
11 Ifsm=30;
12 Rs=Vp/Ifsm
13 printf("surge limiting resistance is %3.3fohm\n",Rs)

```

---

**Scilab code Exa 3.11** specify transformer for full wave rectifier

```

1 //chapter 3
2 //example 3.11
3 //page 73
4 printf("\n")
5 printf("given")
6 Eo=21; Vf=.7; I1=40*10^-3; Vp=115;
7 Vs=.707*(Eo+2*Vf)
8 Is=1.6*I1
9 Ip=(Vs*Is)/Vp;
10 printf(" supply current is %3.3fA\n",Ip)

```

---

**Scilab code Exa 3.12** dc output voltage and outpur ripple amplitude

```

1 //chapter 3
2 //example 3.12
3 //page 97
4 printf("\n")
5 printf("given")
6 Eo=20; I1=40*10^-3; R1=22; Vr=2; C1=150*10^-6; C2=C1; fr
   =120;
7 Vo=Eo-I1*R1;
8 vi=Vr/3.14
9 Xc2=1/(2*3.14*fr*C2)
10 vo=(vi*Xc2)/sqrt((R1^2) + (Xc2^2))
11 printf(" dc output voltage is %3.3fV\n",vo)

```

```
12 Vpp=2*vo;
13 printf(" peak to peak voltage is %3.3fV\n",Vpp)
```

---

**Scilab code Exa 3.13** suitable value of L1 and C1

```
1 //chapter 3
2 //example 3.13
3 //page 98
4 printf("\n")
5 printf(" given")
6 C1=150*10^-6;C2=C1;vi=4;vo=1;f=120;
7 Xc2=8.84; //FROM EXAMPLE 3.12
8 Xl=Xc2*((vi/vo)+1)
9 L1=Xl/(2*3.14*f);
10 printf(" suitable value of L1 is %3.3fH\n",L1)
```

---

**Scilab code Exa 3.14** peak output voltage and value of L1 and C1

```
1 //chapter 3
2 //example 3.14
3 //page 101
4 printf("\n")
5 printf(" given")
6 Edc=20;vo=.24;Vo=20;I1=40*10^-3;fr=120;
7 Eomax=(3.14*Edc)/2
8 Epeak=(4*Eomax)/(3*3.14)
9 vi=Epeak;
10 Rl=Vo/I1
11 Xlc=(2*Rl)/3
12 Lc=Xlc/(2*3.14*fr)
13 L=1.25*Lc;
14 Xl=2*3.14*fr*L
15 Xc=Xl/((vi/vo)+1)
```

16  $C1=1/(2*3.14*fr*Xc)$

---

**Scilab code Exa 3.15** load and source effects and load and line regulation

```
1 //chapter 3
2 //example 3.15
3 //page 105
4 printf("\n")
5 printf("given")
6 Eo=20
7 E0=20-19.7//load effect
8 loadregulation =(E0*100)/Eo//percentage
9 sourceeffect=20.2-20
10 lineregulation =(sourceeffect*100)/Eo
```

---

**Scilab code Exa 3.16** circuit current

```
1 //chapter 3
2 //example 3.16
3 //page 108
4 printf("\n")
5 printf("given")
6 Vz=9.1; Izt=20*10^-3; Es=30;
7 R1=(Es-Vz)/Izt
8 Pr1=(Izt^2)*R1
9 Es=27;
10 Iz=(Es-Vz)/R1
```

---

**Scilab code Exa 3.17** maximum load current



```

1 //chapter 3
2 //example 3.17
3 //page 110
4 printf("\n")
5 printf(" given ")
6 Vz=6.2;Pd=400*10^-3;Es=16;
7 Izm=Pd/Vz
8 R1=(Es-Vz)/Izm
9 Pr1=(Izm^2)*R1
10 Izmin=5*10^-3;
11 Izmax=Izm-Izmin;
12 printf("maximum current is %3.4fA\n",Izmax)

```

---

**Scilab code Exa 3.18** line regulation load regulation and ripple rejection ratio

```

1 //chapter 3
2 //example 3.18
3 //page 112
4 printf("\n")
5 printf(" given ")
6 Zz=7;Es=16;Vo=6.2;I1=59.5*10^-3;
7 es=(10*Es)/100//10% os Es
8 R1=Vo/I1
9 disp(" es*Zz || R1/R1+Zz || R1")
10 V0=es*((Zz*R1)/(Zz+R1))/(R1+((Zz*R1)/(Zz+R1)))
11 lineregulation=(V0*100)/Vo;
12 printf("line regulation voltage is %3.3fpercentage\n",lineregulation)
13 V0=I1*((Zz*R1)/(Zz+R1))
14 loadregulation=(V0*100)/Vo;
15 printf("loadregulation voltage is %3.3fpercentage\n",loadregulation)
16 Rr=((Zz*R1)/(Zz+R1))/(R1+(Zz*R1)/(Zz+R1));
17 printf("ripple rejection is %3.3f\n",Rr)

```

---

**Scilab code Exa 3.19** resistance R1 and forward and reverse current

```
1 //chapter 3
2 //example 3.19
3 //page 114
4 printf("\n")
5 printf("given")
6 E=9; Vf=.7; If=1*10^-3;
7 Vo=E-Vf
8 R1=Vo/If
9 Vr=E;
10 printf("diode forward voltage is %3.2fohm\n",Vr)
11 printf("diode forward current is %3.3fA\n",If)
```

---

**Scilab code Exa 3.20** resistance R1 and forward current and reverse voltage

```
1 //chapter 3
2 //example 3.20
3 //page 117
4 printf("\n")
5 printf("given")
6 E=5; Vo=4.5; I1=2*10^-3;
7 R1=(E-Vo)/I1;
8 printf(" suitable resistance is %dohm\n",R1)
9 Vr=E
10 disp("when diode is forward baised")
11 If=(E-Vf)/R1;
12 printf(" diode forward current is %3.3fA\n",If)
```

---

**Scilab code Exa 3.21** resistor for R1

```
1 //chapter 3
2 //example 3.21
3 //page 119
4 printf("\n")
5 printf("given")
6 Vo=2.7;Vf=.7;E=9;If=1*10^-3;I1=If;
7 Vb=Vo-Vf;
8 R1=(E-Vo)/(I1+If);
9 printf("resistance is %3.3fOhm\n",R1)
```

---

**Scilab code Exa 3.22** zener diode and R1

```
1 //chapter 3
2 //example 3.22
3 //page 120
4 printf("\n")
5 printf("given")
6 Vo=5;Vf=.7;Iz=5*10^-3;I1=1*10^-3;E=20;
7 Vz=Vo-Vf
8 R1=(E-Vo)/(I1+Iz);
9 printf("zener diode resistance si %dohm\n",R1)
```

---

**Scilab code Exa 2.23** tilt on output waveform

```
1 //chapter 3
2 //example 3.21
3 //page 119
4 printf("\n")
5 printf("given")
6 E=10;R1=56*10^3;f=1000;C1=1*10^-6;
7 Vo=2*E
```

```

8 Ic=Vo/R1
9 t=1/(2*f);
10 Vc=(Ic*t)/C1;
11 printf(" tilt output voltage is %3.3fV\n",Vc)

```

---

**Scilab code Exa 3.24** suitable value of R1 and C1

```

1 //chapter 3
2 //example 3.24
3 //page 124
4 printf("\n")
5 printf(" given")
6 f=500;Rs=600;E=8;
7 t=1/(2*f)
8 PW=t;
9 C1=PW/Rs
10 Vo=2*E
11 Vc=(1*Vo)/100;//1% of the Vo
12 Ic=(Vc*C1)/t
13 R1=(2*E)/Ic;
14 printf(" suitable value of R1 is %dohm\n",R1)

```

---

**Scilab code Exa 3.25** capacitor voltage

```

1 //chapter 3
2 //example 3.25
3 //page 125
4 printf("\n")
5 printf(" given\n")
6 Vf=.7;E=6;Vb1=3;
7 Vc=Vb1-Vf-(-E)
8 Vo=Vb1-Vf
9 disp(" when input is +E")

```

```

10 Vo=E+Vc
11 Vc=E-Vb1-Vf
12 Vo=Vb1+Vf
13 disp("when input is -E")
14 Vo=-E+(-Vc)

```

---

**Scilab code Exa 3.26** determine C1 and C2

```

1 //chapter 3
2 //example 3.26
3 //page 130
4 printf("\n")
5 printf("given")
6 E=12; Vf=.7; R1=47*10^3; f=5000;
7 Vo=2*(E-Vf)
8 I1=Vo/R1
9 disp(" capacitor discharge time")
10 t=1/(2*f)
11 disp(" for 1% ripple allow .5% due to discharge of
      C2 ,.5%due to discharge of C1")
12 Vc=(.5*Vo)/100
13 C2=((I1*t)/Vc)*10^6;
14 printf(" value of capacitor C2 is %3.2fuF\n",C2)
15 C1=2*C2;
16 printf("value of capacitor C1 is %3.2fuF\n",C1)

```

---

**Scilab code Exa 3.27** diode forward current

```

1 //chapter 3
2 //example 3.21
3 //page 119
4 printf("\n")
5 printf("given")

```

```
6 Vcc=5;Vf=.7;R1=3.3*10^3;
7 disp("A")
8 Ir1=(Vcc-Vf)/R1;
9 printf("diode forward current when all input are low
      is %3.4fA\n",Ir1)
10 disp("for each diode")
11 If=Ir1/3
12 disp("B")
13 If2=Ir1/2
14 If3=If2;
15 printf(" forward current when input A is high is %3
      .5fA\n",If3)
16 disp("C")
17 If3=Ir1;
18 printf(" forward current when input A and B are high
      and C is low %3.5fA\n",If3)
```

---

# Chapter 4

## Bipolar junction transistors

Scilab code Exa 4.1 calculate  $I_c$  and  $I_e$

```
1 //chapter 4
2 //example 4.1
3 //page 153
4 printf("\n")
5 printf("given")
6 Adc=.98;Ib=100*10^-6;
7 Ic=(Adc*Ib)/(1-Adc);
8 printf("value of Ic is %3.3fA\n",Ic)
9 Ie=Ic/Adc;
10 printf(" value of Ie is %3.3fA\n",Ie)
11 Bdc=Adc/(1-Adc);
12 disp(Bdc)
```

---

Scilab code Exa 4.2 new base current

```
1 //chapter 4
2 //example 4.2
3 //page 153
```

```

4 printf("\n")
5 printf(" given")
6 Ic=1*10^-3; Ib=25*10^-6;
7 Bdc=Ic/Ib
8 Ie=Ic+Ib
9 Adc=Ic/Ie
10 Ib=Ic/Bdc

```

---

**Scilab code Exa 4.3** dc collector voltage and circuit voltage gain

```

1 //chapter 4
2 //example 4.1
3 //page 153
4 printf("\n")
5 printf(" given")
6 Bdc=80; Bac=Bdc; Vcc=18; R1=10*10^3;
7 Ib=15*10^-6; //for Vb=.7
8 Ic=Bdc*Ib;
9 Vc=Vcc-(Ic*R1);
10 printf("dc collector voltage is %dV\n",Vc)
11 disp(" when vi=50mV")
12 Ib=3*10^-6; Vi=50*10^-3;
13 Ic=Bdc*Ib
14 Vo=Ic*R1
15 Av=Vo/Vi

```

---

**Scilab code Exa 4.4** calculate Ic Ib and hFE

```

1 //chapter 4
2 //example 4.4
3 //page 160
4 printf("\n")
5 printf(" given")

```



```
6 Vcc=5;Vce=.2;R2=4.7*10^3;Vi=2;Vbe=.7;R1=12*10^3;
7 Ic=(Vcc-Vce)/R2
8 Ib=(Vi-Vbe)/R1
9 hFE=Ic/Ib
```

---

**Scilab code Exa 4.6** determine Ib and Ic

```
1 //chapter 4
2 //example 4.6
3 //page 169
4 printf("\n")
5 printf("given")
6 Vbe=.7;Vce=-6;
7 Ib=20*10^-6
8 Ic=2.5*10^-3//from output characteristics
9 Bdc=Ic/Ib
```

---

# Chapter 5

## BJT biasing

Scilab code Exa 5.1 new dc load line

```
1 //chapter 5
2 //example 5.1
3 //page 182
4 printf("\n")
5 printf("given")
6 Rc=12*10^3;Vcc=20;
7 disp(" When Ic=0")
8 Ic=0;
9 Vce=Vcc-Ic*Rc
10 disp(" At point A Ic=0 nad Vce=20")
11 disp("When Vce=0")
12 Vce=0;
13 Ic=Vcc/Rc
14 disp(" At point B Ic=1.7mA and Vce=0")
```

---

Scilab code Exa 5.2 circuit Q point

```
1 //chapter 5
```

```

2 //example 5.2
3 //page 186
4 printf("\n")
5 printf("given")
6 Vcc=18;Rc=2.2*10^3;Ib=40*10^-6;
7 disp("when Ic=0")
8 Ic=0;
9 Vce=Vcc-Ic*Rc
10 disp("At point A Ic=0 and Vce=18")
11 disp("when Vce=0")
12 Ic=Vcc/Rc
13 disp(" at point B Ic=8.2mA and Vce=0")

```

---

**Scilab code Exa 5.3** determine Ib Ic and Vce

```

1 //chapter 5
2 //example 5.1
3 //page 182
4 printf("\n")
5 printf("given")
6 Rb=470*10^3;Rc=2.2*10^3;Vcc=18;hfe=100;
7 Vee=.7;
8 Ib=(Vcc-Vee)/Rb
9 Ic=hfe*Ib
10 Vce=Vcc-Ic*Rc

```

---

**Scilab code Exa 5.4** maximum and minimum level of Ic and Vce

```

1 //chapter 5
2 //example 5.4
3 //page 189
4 printf("\n")
5 printf("given")

```

```

6 hFEmin=50; hFEmax=200; Vcc=18; Vbe=.7; Rb=470*10^3;
7 Ib=(Vcc-Vbe)/Rb
8 Ic=hFEmin*Ib
9 Vce=Vcc-Ic*Rc
10 Ic=hFEmax*Ib
11 Vce=Vcc-Ic*Rc

```

---

**Scilab code Exa 5.5** determine Ib Ic and Vce

```

1 //chapter 5
2 //example 5.5
3 //page 193
4 printf("\n")
5 printf("given")
6 Rb=270*10^3; Rc=2.2*10^3; Vcc=18;
7 hFE=100; Vbe=.7;
8 Ib=(Vcc-Vbe)/(Rb+Rc*(hFE+1))
9 Ic=hFE*Ib
10 Vce=Vcc-Rc*(Ic+Ib)

```

---

**Scilab code Exa 5.7** emitter voltage collector voltage and collector and emitter voltage

```

1 //chapter 5
2 //example 5.7
3 //page 197
4 printf("\n")
5 printf("given")
6 R1=33*10^3; R2=12*10^3; Rc=1.2*10^3; Re=1*10^3;
7 Vcc=18; Vbe=.7;
8 Vb=(Vcc*R2)/(R1+R2)
9 Ve=Vb-Vbe
10 Ie=(Vb-Vbe)/Re

```

```
11 Ic=Ie;
12 Vc=Vcc-(Ic*Rc)
13 Vce=Vc-Ve
```

---

**Scilab code Exa 5.8** determine Ic Ve Vc vce

```
1 //chapter 5
2 //example 5.8
3 //page 199
4 printf("\n")
5 printf("given")
6 Vcc=18;Vbe=.7;hfe=100;
7 R1=33*10^3;R2=12*10^3;Re=1*10^3;
8 Vt=(Vcc*R2)/(R1+R2)
9 Rt=(R1*R2)/(R1+R2)
10 Ib=(Vt-Vbe)/(Rt+Re*(1+hfe))
11 Ic=hfe*Ib
12 Ie=Ib+Ic
13 Ve=Ie*Re
14 Vc=Vcc-(Ic*Rc)
15 Vce=Vc-Ve
```

---

**Scilab code Exa 5.9** analyze voltage divider bias circuit for hFE 50

```
1 //chapter 5
2 //example 5.9
3 //page 200
4 printf("\n")
5 printf("given")
6 hfe=50;Vt=4.8;Rt=8.8*10^3;//from example 5.7
7 Re=1*10^3;Vbe=.7;
8 Ib=(Vt-Vbe)/(Rt+Re*(1+hfe))
9 Ic=hfe*Ib
```

```
10 Ie=Ib+Ic
11 Ve=Ie*Re
12 Vc=Vcc-(Ic*Rc)
13 Vce=Vc-Ve
```

---

**Scilab code Exa 5.10** analyze voltage divider bias circuit for hFE is 200

```
1 //chapter 5
2 //example 5.10
3 //page 201
4 printf("\n")
5 printf("given")
6 Vt=4.8;Rt=8.8*10^3;//from example 5.8
7 Re=1*10^3;Vbe=.7;hfe=200;
8 Ib=(Vt-Vbe)/(Rt+Re*(1+hfe))
9 Ic=hfe*Ib
10 Ie=Ib+Ic
11 Ve=Ie*Re
12 Vc=Vcc-(Ic*Rc)
13 Vce=Vc-Ve
```

---

**Scilab code Exa 5.11** design base bias circuit

```
1 //chapter 5
2 //example 5.11
3 //page 208
4 printf("\n")
5 printf("given")
6 Vce=5;Ic=5*10^-3;Vcc=15;hfe=100;
7 Rc=(Vcc-Vce)/Ic
8 Ib=Ic/hfe
9 Rb=(Vcc-Vbe)/Ib
```

---

**Scilab code Exa 5.12** collector to base bias circuit

```
1 //chapter 5
2 //example 5.12
3 //page 209
4 printf("\n")
5 printf("given")
6 Vce=5;Ic=5*10^-3;Vcc=15;hfe=100;
7 Ib=Ic/hfe
8 Rc=(Vcc-Vce)/(Ic+Ib)
9 Rb=(Vce-Vbe)/Ib
```

---

**Scilab code Exa 5.13** design voltage divider bias circuit

```
1 //chapter 5
2 //example 5.13
3 //page 211
4 printf("\n")
5 printf("given")
6 Vce=5;Ve=Vce;Ic=5*10^-3;hFE=100;Vcc=15;Vbe=.7;
7 Ie=Ic;
8 Re=Ve/Ie
9 Rc=(Vcc-Vce-Ve)/Ic
10 I2=Ic/10
11 Vb=Ve+Vbe
12 R2=Vb/I2
13 R1=(Vcc-Vb)/I2
```

---

**Scilab code Exa 5.14** design voltage divider bias circuit

```

1 //chapter 5
2 //example 5.14
3 //page 212
4 printf("\n")
5 printf(" given ")
6 Vce=3;Ve=5;Ic=1*10^-3;Vcc=12;
7 Ie=Ic;
8 R4=Ve/Ie
9 disp(" with Ic=1mA and R4=4.7Kohm")
10 R4=4.7*10^3;
11 Ve=Ic*R4
12 Vc=Ve+Vce
13 Vr3=Vcc-Vc
14 R3=Vr3/Ic
15 Vb=Ve+Vbe
16 I2=Ic/10
17 R2=Vb/I2
18 disp(" with R2=56Kohm and Vb=5.4V")
19 R2=56*10^3;
20 I2=Vb/R2
21 R1=(Vcc-Vb)/I2

```

---

**Scilab code Exa 5.15** design bais circuit operate from 18V supply

```

1 //chapter 5
2 //example 5.15
3 //page 214
4 printf("\n")
5 printf(" given ")
6 Vce=9;Ve=4;Ic=4*10^-3;Vcc=18;
7 Ie=Ic;
8 R4=Ve/Ie
9 Vb=Ve+Vbe
10 I2=Ic/10
11 R2=Vb/I2

```



```

12 disp(" with R2=12Kohm standard")
13 R2=12*10^3;
14 I2=Vb/R2
15 R1=(Vce+Ve-Vb)/I2
16 disp(" with R1=22kohm standard")
17 R1=22*10^3;
18 Vr3=Vcc-Vce-Ve
19 R3=Vr3/(Ic+I2)

```

---

**Scilab code Exa 5.16** design bais circuit operate from 9V supply

```

1 //chapter 5
2 //example 5.16
3 //page 216
4 printf("\n")
5 printf(" given")
6 Vc=5;Ic=1*10^-3;hFE=70;Vbe=.7;Vee=9;Vcc=Vee;Re
   =8.2*10^3;
7 Ve=Vee-Vbe
8 Ie=Ic;
9 R3=Ve/Ie
10 disp(" with R3=8.2kohm standard value")
11 R3=8.2*10^3;
12 Ie=Ve/R3
13 Vr2=Vcc-Vc
14 R2=Vr2/Ic
15 Ib=Ic/hFE
16 Vr1=Vbe/10
17 R1=Vr1/Ib
18 disp(" use 4.7Kohm as standard")
19 //the transistor emitter terminal is .7 below ground
   and voltage across Re is
20 Ve=Vee-Vbe
21 Ie=Ve/Re
22 Vc=Vcc-(Ie*3.9*10^3)

```

---

**Scilab code Exa 5.17** stability factors for three bias circuit

```
1 //chapter 5
2 //example 5.17
3 //page 220
4 printf("\n")
5 printf("given")
6 hFE=100;
7 Rc=2.2*10^3;Rb=270*10^3;Re=1*10^3;R1=33*10^3;R2
   =12*10^3;
8 S=1+hFE
9 disp("for collector to base bias")
10 S=(1+hFE)/(1+(hFE*Rc)/(Rc+Rb))
11 disp(" for voltage divider bias")
12 disp("S=(1+hFE)/(1+hFE*Re/(Re+R1||R2))")
13 S=(1+hFE)/(1+(hFE*Re)/(Re+(R1*R2)/(R1+R2)))
```

---

**Scilab code Exa 5.18** determine  $I_c$  change when temperture increases

```
1 //chapter 5
2 //example 5.18
3 //page 221
4 printf("\n")
5 printf("given")
6 Icbo1=15*10^-9; // at 25C
7 S=101;
8 disp("chnage in temp")
9 T=105-25
10 disp(" n=T/10")
11 n=T/10
12 Icbo2=Icbo1*2^n
```

```

13 Icbo=Icbo2-Icbo1
14 disp(" for base bais")
15 Ic=S*Icbo
16 disp(" for collector to base bais")
17 S=56;
18 Ic=S*Icbo
19 disp(" for voltage divider bais")
20 S=8.2;
21 Ic=S*Icbo

```

---

**Scilab code Exa 5.19** change in  $I_c$  by effect of change in  $V_{be}$

```

1 //chapter 5
2 //example 5.19
3 //page 223
4 printf("\n")
5 printf(" given")
6 Re=4.7*10^3;
7 T=125-25
8 Vbe=T*(1.8*10^-3)
9 Ie=Vbe/Re

```

---

**Scilab code Exa 5.20** calculate minimum  $h_{FE}$  and transistor  $V_{ce}$

```

1 //chapter 5
2 //example 5.20
3 //page 2
4 printf("\n")
5 printf(" given")
6 Vcc=10;Rc=1*10^3;Rb=6.8*10^3;Vs=5;
7 disp(" hFE calculation")
8 Ic=Vcc/Rc
9 Ib=(Vs-Vbe)/Rb

```

```

10 hFE=Ic/Ib
11 disp(" when hFE=10")
12 hFE=10
13 Ic=hFE*Ib
14 Vce=Vcc-(Ic*Rc)

```

---

**Scilab code Exa 5.21** calculate minimum hFE for transistor

```

1 //chapter 5
2 //example 5.21
3 //page 227
4 printf("\n")
5 printf(" given")
6 Vcc=15;Rc=3.3*10^3;Vbe=.7;Rb=56*10^3;
7 Ic=Vcc/Rc
8 Ib=(Vcc-Vbe)/Rb
9 hFE=Ic/Ib;
10 printf(" minimum hFE is %3.2 f\n",hFE)

```

---

**Scilab code Exa 5.22** determine suitable resistance for Rb and Rc

```

1 //chapter 5
2 //example 5.22
3 //page 229
4 printf("\n")
5 printf(" given")
6 Vcc=12;Ic=1.5*10^-3;Vs=5;hFE=10;Vbe=.7;
7 Rc=Vcc/Ic
8 Ib=Ic/hFE
9 Rb=(Vs-Vbe)/Ib

```

---

**Scilab code Exa 5.23** suitable resistor for capacitor coupled switching

```
1 //chapter 5
2 //example 5.23
3 //page 229
4 printf("\n")
5 printf("given")
6 Vcc=9; Ic=2*10^-3; hFE=10; Vbe=.7;
7 Rc=Vcc/Ic
8 Ib=Ic/hFE
9 Rb=(Vcc-Vbe)/Ib
```

---

# Chapter 6

## Ac analysis of BJT circuits

Scilab code Exa 6.1 calculate base bias voltage

```
1 //chapter 6
2 //example 6.1
3 //page 240
4 printf("\n")
5 printf("given")
6 Vcc=12;R2=15*10^3;R1=33*10^3;rs=600;
7 disp("with no signal source")
8 Vb=(Vcc*R2)/(R1+R2);
9 printf(" base bias voltage when no signal source is
   present %3.2fV\n",Vb)
10 disp(" signal source directly connected")
11 Vb=(Vcc*((rs*R2)/(rs+R2))/(R1+((rs*R2)/(rs+R2))));
12 printf("base bias voltage is %3.2fV\n",Vb)
```

---

Scilab code Exa 6.2 Dc and Ac load line

```
1 //chapter 6
2 //example 6.2
```

```

3 //page 244
4 printf("\n")
5 printf("given")
6 Rc=2.2*10^3;Re=2.7*10^3;R1=18*10^3;R2=8.2*10^3;Vbe
   =.7
7 disp("drawing dc load line")
8 Rldc=Rc+Re
9 disp(" for Vce")
10 Ic=0;Vcc=20;
11 Vce=Vcc-Ic*(Rc+Re)
12 disp("plot point A at")
13 Ic=Vcc/(Rc+Re)
14 disp("plot point B Ic=4.08mA and Vce=0")
15 disp(" draw dc laod line through point A nad B")
16 Vb=(Vcc*R2)/(R1+R2)
17 Ve=Vb-Vbe
18 Ic=Ve/Re
19 Ie=Ic
20 disp("drawing the ac load line")
21 Rlac=Rc//when there is no external Rl
22 Vce=Ic*Rc

```

---

**Scilab code Exa 6.3** determine hfe and hoe

```

1 //chapter 6
2 //example 6.2
3 //page 251
4 printf("\n")
5 printf("given")
6 Vce=4.5;Ib=40*10^-6;
7 disp("from current characteristic at Vce=4.5V and Ib
   =40uA")
8 Ic=4*10^-3;Ib=30*10^-6;
9 hFE=Ic/Ib;
10 printf(" the value of hFE is %d\n",hFE)

```

```

11 disp("from output characteristic at Vce=4.5 and Ib
      =40uA")
12 Ic=400*10^-3;Vce=6;
13 hoe=(Ic/Vce)*10^6;
14 printf("tye value of hoe is %3.2 fuS\n",hoe)

```

---

**Scilab code Exa 6.4** calculate hfc hob and alfa

```

1 //chapter 6
2 //example 6.4
3 //page 253
4 printf("\n")
5 printf("given")
6 hfe=133;hoe=33.3*10^-6;
7 hfc=1+hfe
8 hob=hoe/(1+hfe)
9 A=hfe/(1+hfe)

```

---

**Scilab code Exa 6.5** estimate the CE input resistance

```

1 //chapter 6
2 //example 6.5
3 //page 253
4 printf("\n")
5 printf("given")
6 Ib=20*10^-6;Ic=1*10^-3;
7 Ie=Ic;
8 re=(26*10^-3)/Ie
9 hfe=Ic/Ib
10 hie=(1+hfe)*re
11 r=hie
12 B=hfe

```

---



**Scilab code Exa 6.6** circuit input and output impedance voltage gain

```
1 //chapter 6
2 //example 6.6
3 //page 258
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3;hfe=75;hoe=1*10^-6;R1=68*10^3;R2
   =56*10^3;Rc=3.9*10^3;Rl=82*10^3;
7 disp(" input impedance Zi=R1||R2|| hie")
8 Zi=((R1*R2*hie)/(R1+R2+hie))*10^-3;
9 printf(" input impedance is %3.2fKohm\n",Zi)
10 disp(" output impedance is Zo=Rc||(1/hoe)")
11 Zo=((Rc*(1/hoe))/(Rc+(1/hoe)))*10^-3;
12 printf(" output impedance is %f3.2fKohm\n",Zo)
13 Av=-((hfe*((Rc*Rl)/(Rc+Rl)))/hie);
14 printf(" voltage gain is %d\n",Av)
```

---

**Scilab code Exa 6.7** estimate re and circuit voltage gain

```
1 //chapter 6
2 //example 6.7
3 //page 259
4 printf("\n")
5 printf("given")
6 Ic=1.5*10^-3;Rc=4.7*10^3;Rl=56*10^3;
7 Ie=Ic;
8 re=(26*10^-3)/Ie
9 Av=-(((Rc*Rl)/(Rc+Rl))/re);
10 printf(" voltage gain is %d\n",Av)
```

---

**Scilab code Exa 6.8** circuit input and output impedance and voltage gain

```
1 //chapter 6
2 //example 6.8
3 //page 262
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3;hfe=75;hoe=1*10^-6;Re=4.7*10^3;R1
   =68*10^3;R2=56*10^3;Rc=3.9*10^3;Rl=82*10^3;
7 Zb=hie+Re*(1+hfe)
8 disp(" input impedance is Zi=R1||R2||Zb")
9 Zi=((R1*R2*Zb)/(R1+R2+Zb));
10 printf(" input circuit resistance is %3.3fKohm\n",Zi
   )
11 Zo=Rc
12
13 Av=-hfe*((Rc*Rl)/(Rc+Rl))/(hie+Re*(1+hfe));
14 printf("voltage gain is %3.3f\n",Av)
```

---

**Scilab code Exa 6.9** circuit input and output impedance with Rl not connected

```
1 //chapter 6
2 //example 6.9
3 //page 267
4 printf("\n")
5 printf("given")
6 hie=2.1*10^3;hfe=75;R1=10*10^3;R2=10*10^3;Re
   =4.7*10^3;Rl=12*10^3;rs=1*10^3;
7 disp(" Rl is not connected")
8 hic=hie
9 hfc=1+hfe
```

```

10 Zb=hic+hfc*(Re)
11 Zi=(R1*R2*Zb)/(R1+R2+Zb)
12 Ze=(hic+(R1*R2*rs)/(R1+R2+rs))/hfc
13 ZO=(Ze*Re)/(Ze+Re)
14 disp(" when Rl is connected")
15 Zb=hic+hfc*((Re*Rl)/(Re+Rl))
16 Zi=(R1*R2*Zb)/(R1+R2+Zb)
17 hib=hie/(1+hfe)
18 Av=((Re*Rl)/(Re+Rl))/(hib+((Re*Rl)/(Re+Rl)))

```

---

**Scilab code Exa 6.10** circuit input and output impedance and voltage gain

```

1 //chapter 6
2 //example 6.10
3 //page 273
4 printf("\n")
5 printf(" given")
6 hie=2.1*10^3;hfe=75;Re=4.7*10^3;Rc=3.9*10^3;Rl
   =82*10^3;
7 hib=hie/(1+hfe)
8 hfb=hfe/(1+hfe)
9 Zi=(hib*Re)/(Re+hib);
10 printf("input impedance is %3.2fohm\n",Zi)
11 Zo=Rc;
12 printf(" output impedance is %3.2fohm\n",Zo)
13 Av=(hfb*((Rc*Rl)/(Rc+Rl)))/hib;
14 printf(" voltage gain is %3.2f\n",Av)

```

---

**Scilab code Exa 6.11** input impedance and voltage gain when C1 is disconnected

```

1 //chapter 6
2 //example 6.11

```

```

3 //page 273
4 printf("\n")
5 printf(" given")
6 hib=27.6;hfb=.987;R1=68*10^3;R2=56*10^3;Re=4.7*10^3;
   Rc=3.9*10^3;Rl=82*10^3;
7 Rb=(R1*R2)/(R1+R2);
8 Ze=hib+Rb*(1-hfb)
9 Zi=(Ze*Re)/(Ze+Re)
10 Av=(hfb*((Rc*Rl)/(Rc+Rl)))/(hib+Rb*(1-hfb))

```

---

**Scilab code Exa 6.12** calculate vo

```

1 //chapter 6
2 //example 6.12
3 //page 277
4 printf("\n")
5 printf(" given")
6 Rc=5.6*10^3;Rl=33*10^3;rs=600;
7 hfe=100;hie=1.5*10^3;vs=50*10^-3;
8 disp(" CE circuit operation with vs at transistor
   base and Re bypassed")
9 Av=(hfe*((Rc*Rl)/(Rc+Rl)))/hie
10 Zb=hie
11 Rb=(R1*R2)/(R1+R2);
12 Zi=(Rb*Zb)/(Rb+Zb)
13 vi=(vs*Zi)/(rs+Zi)
14 vo=Av*vi
15 disp("Cb circuit operation with vs at emitter and
   the base resistor bypassed")
16 Av=(hfe*((Rc*Rl)/(Rc+Rl)))/hie
17 Ze=hie/(1+hfe)
18 Zi=(Ze*Re)/(Ze+Re)
19 vi=(vs*Zi)/(rs+Zi)
20 vo=Av*vi

```

---

**Scilab code Exa 6.13** calculate  $I_c$   $I_e$  and  $I_b$

```
1 //chapter 6
2 //example 6.13
3 //page 279
4 printf("\n")
5 printf("given")
6 Io=50*10^-9; Vbe=.7; Vbc=-10; Af=.995; Ar=.5; Vt
   =26*10^-3; n=2; Vd=-10;
7 x=Vd/(n*Vt);
8 Idc=(Io*((2.73^-x)-1))*10^9;
9 Idc=Io*(-1)
10 y=Vbe/(n*Vt);
11 Ide=Io*((2.73^y)-1)
12 I1=Af*Ide
13 I2=Ar*Idc
14 Ic=I1-Idc
15 Ie=Ide-I2
16 Ib=Ie-Ic
```

---

# Chapter 8

## BJT specifications and performance

Scilab code Exa 8.2 output power change

```
1 //chapter 8
2 //example 8.2
3 //page 313
4 printf("\n")
5 printf(" given")
6 P2=25*10^-3;//when frequency increase to 20KHz
7 P1=50*10^-3;//when signal frequency is 5KHz
8 Po=10*log10(P2/P1);
9 printf(" output power change in decibels is %ddB\n",
    Po)
```

---

Scilab code Exa 8.3 output power change

```
1 //chapter 8
2 //example 8.3
3 //page 314
```

```

4 printf("\n")
5 printf(" given")
6 v1=1; // output voltage measured at 5KHz
7 v2=.707; // output voltage measure at 20kHz
8 Po=20*log10(v2/v1);
9 printf(" output power change is %ddB\n",Po)

```

---

#### Scilab code Exa 8.4 input capacitance

```

1 //chapter 8
2 //example 8.4
3 //page 317
4 printf("\n")
5 printf(" given")
6 Ic=1*10^-3; hfe=50; hie=1.3*10^3; fT=250*10^6; Cbc
   =5*10^-12; Rc=8.2*10^3; Rl=100*10^3;
7 Ie=Ic;
8 Av=(hfe*((Rc*Rl)/(Rc+Rl)))/hie
9 Cbe=(6.1*Ie)/fT;
10 Cin=(Cbe+(1+Av)*Cbc)*10^9;
11 printf(" input capacitance when the circuit operated
   as CE is %3.3fnF\n",Cin)

```

---

#### Scilab code Exa 8.5 input capacitance limited upper cutoff frequency

```

1 //chapter 8
2 //example 8.5
3 //page 319
4 printf("\n")
5 printf(" given")
6 R1=100*10^3; R2=47*10^3; Re=4.7*10^3;
7 Cbc=5*10^-12; Cbe=24.4*10^-12; hfe=50; hie=1.3*10^3; hib
   =24.5; rs=hib; rs=600;

```

```

8 disp(" common emitter circuit")
9 Rb=(R1*R2)/(R1+R2);
10 Zi=(Rb*hie)/(Rb+hie)
11 Cin=1.48*10^-9;
12 f2=1/(2*3.14*Cin*((rs*Zi)/(rs+Zi)));
13 printf("input-capacitance upper cutoff frequency is
    %dHz\n",f2)
14 disp("common base circuit")
15 Zi=(Re*hib)/(Re+hib)
16 Cin=(Cbe+Cbc)
17 f2=(1/(2*3.14*Cin*((rs*Zi)/(rs+Zi))))*10^-6;
18 printf(" input capacitance upper cutoff when
    operating as CB circuit with base bypassed to
    ground is %dMHz\n",f2)

```

---

**Scilab code Exa 8.6** upper 3db frequency

```

1 //chapter 8
2 //example 8.6
3 //page 322
4 printf("\n")
5 printf(" given")
6 fT=50*10^6;hfe=50;f2o=60*10^3;Rc=10*10^3;
7 fae=fT/hfe
8 C4=(1/(2*3.14*f2o*Rc))*10^12;
9 printf("capacitance required for C4 to give 60kHz
    upper cutoff frequency is %dpF\n",C4)

```

---

**Scilab code Exa 8.8** calculate suitable speed up capacitor

```

1 //chapter 8
2 //example 8.8
3 //page 326

```



```

4 printf("\n")
5 printf(" given")
6 ton=100*10^-9;Rs=600;Rb=4.7*10^3;
7 C1=(ton/Rs)*10^12;
8 printf(" suitable speed up capacitor is %dpF\n",C1)
9 C1=160*10^-12;//standard value
10 PWmin=(5*Rs*C1);
11 SWmin=5*Rb*C1;
12 fmax=1/(PWmin+SWmin);
13 printf("maximum signal frequency is %dHz\n",fmax)

```

---

#### Scilab code Exa 8.9 noise output voltage

```

1 //chapter 8
2 //example 8.9
3 //page 330
4 printf("\n")
5 printf(" given")
6 R1=30*10^3;R2=30*10^3;rs=30*10^3;f2=40*10^3;f1=100;k
   =1.37*10^-23;R=10*10^3;Av=600;Ri=3*10^3;
7 Rb=(R1*R2)/(R1+R2);
8 Rg=(rs*Rb)/(rs+Rb);
9 T=(273+25)
10 B=f2-f1;
11 en=sqrt(4*k*T*B*R)
12 eni=en*((Ri/(Ri+Rg)))
13 eno=(Av*eni)*10^6;
14 printf(" noise output voltage is %duV\n",eno)

```

---

#### Scilab code Exa 8.10 total noise output voltage for amlifier

```

1 //chapter 8
2 //example 8.10

```

```

3 //page 331
4 printf("\n")
5 printf(" given")
6 Ic=30*10^-6;Vce=5;eno=354*10^-6;
7 NF=10;
8 F=2.51;//F=antilog(NF/10)
9 Vn=((sqrt(F))*eno)*10^6;
10 printf("total noise output volateg for amplifier is
    %duV\n",Vn)

```

---

**Scilab code Exa 8.11** calculate maximum Ic

```

1 //chapter 8
2 //example 8.11
3 //page 333
4 printf("\n")
5 printf(" given")
6 Pd25=625*10^-3;D=5*10^-3;Vce=10;
7 T2=55;
8 Pdt2=Pd25-D*(T2-25)
9 Pd=Pdt2;
10 Ic=Pd/Vce;
11 printf(" maximum Ic level is %3.5fA\n",Ic)

```

---

**Scilab code Exa 8.13** maximum power dissipation

```

1 //chapter 8
2 //example 8.13
3 //page 335
4 printf("\n")
5 printf(" given")
6 Pd=80;
7 Vce=60;

```

```
8 Ic=Pd/Vce
9 disp(" point 1 Vce=60 and Ic=1.3A")
10 Vce=40;
11 Ic=Pd/Vce
12 disp(" point 2 Vce=40 and Ic=2A")
13 Vce=20;
14 Ic=Pd/Vce
15 disp(" point 3 Vce=20 and Ic=4A")
16 Vce=10;
17 Ic=Pd/Vce
18 disp(" point 4 Vce=10 and Ic=8A")
```

---

**Scilab code Exa 8.14** thermal resistance

```
1 //chapter 8
2 //example 8.14
3 //page 339
4 printf("\n")
5 printf(" given")
6 Vce=20;Ic=1;T2=90;T1=25;
7 Q=Vce*Ic;
8 Qcs=.4;Qjc=1;//from table
9 Qsa=((T2-T1)/Q)-(Qjc+Qcs)
```

---

# Chapter 10

## FET biasing

Scilab code Exa 10.1 Dc load line

```
1 //chapter 10
2 //example 10.1
3 //page 381
4 printf("\n")
5 printf("given")
6 Vdd=22;Rd=2*10^3;
7 disp("when Id=0")
8 Id=0;
9 Vds=Vdd-Id*Rd
10 disp(" at point A Id=0 nad Vds=22")
11 Vds=0;
12 Id=Vdd/Rd
13 disp(" at point B Id=11mA and Vds=0")
```

---

Scilab code Exa 10.4 determine Idmax and Idmin

```
1 //chapter 10
2 //example 10.4
```

```

3 //page 387
4 printf("\n")
5 printf(" given")
6 Idss=8*10^-3;Vpmax=6;Vgs=2.3;Vgsmax=6;
7 Id=Idss*(1-(Vgs/Vgsmax))^2
8 Idss=4*10^-3;Vp=3;
9 Idmin=Idss*(1-(Vgs/Vp))^2

```

---

### Scilab code Exa 10.6 Id max Idmin and Vds

```

1 //chapter 10
2 //example 10.6
3 //page 393
4 printf("\n")
5 printf(" given")
6 Vdd=25;R2=1*10^6;R1=3.8*10^6;Rs=2.5*10^3;Rd
   =2.5*10^3;
7 Vg=(Vdd*R2)/(R1+R2)
8 disp(" when Id=0")
9 Id=0;
10 Vgs=Vg-Id*Rs
11 disp(" plot point A at Id=0 and Vgs=5.2")
12 Vgs=0;
13 Id=Vg/Rs
14 disp(" plot point B at Id=2.08mA and Vgs=0")
15 disp(" where the base line intersect the transfer
   characteristics ")
16 Idmax=3*10^-3;Idmin=2.3*10^-3;
17 Vdsmin=Vdd-Idmax*(Rd+Rs)
18 Vdsmax=Vdd-Idmin*(Rd+Rs)

```

---

### Scilab code Exa 10.7 gate bias circuit

```

1 //chapter 10
2 //example 10.7
3 //page 401
4 printf("\n")
5 printf(" given")
6 Id=3*10^-3;Vgs=-2.3;Vdsmin=10;Vdd=25;Vgsoff=-6;Idss
   =8*10^-3;
7 Vgs=Vgsoff*(1-sqrt(Id/Idss))
8 Rd=(Vdd-Vdsmin)/Id

```

---

**Scilab code Exa 10.8** self bais circuit

```

1 //chapter 10
2 //example 10.8
3 //page 403
4 printf("\n")
5 printf(" given")
6 Id=3*10^-3;Vds=10;Vdd=25;Vgs=2.3;
7 Rs=Vgs/Id
8 Rd=((Vdd-Vds)/Id)-Rs

```

---

**Scilab code Exa 10.9** design voltage divider bais circuit

```

1 //chapter 10
2 //example 10.9
3 //page 405
4 printf("\n")
5 printf(" given")
6 Id=3*10^-3;Vds=10;Vdd=25;Vg=5.2;Vgsoff=-6;Idss
   =8*10^-3;R2=1*10^6;
7 R=(Vdd-Vds)/Id//R=(Rs+Rd)/2
8 Rd=R/2
9 Rs=Rd

```

```

10 Vgs=Id*Rs
11 Vgs=Vgsoff*(1-sqrt(Id/Idss))
12 Vs=Id*Rs
13 Vg=Vs-(-Vgs)
14 R1=((Vdd-Vg)*R2)/Vg

```

---

**Scilab code Exa 10.11** constant current bias circuit

```

1 //chapter 10
2 //example 10.11
3 //page 412
4 printf("\n")
5 printf("given")
6 Vee=20; Id=3*10^-3; Vds=9; Vbe=.7; Vb=0;
7 Ve=Vee-Vbe
8 Re=Ve/Id
9 Re=6.8*10^3; //satnadard value
10 Id=Ve/Re;
11 Idss=16*10^-3; Vgsoff=-8;
12 Vgs=Vgsoff*(1-sqrt(Id/Idss))
13 Vs=Vb-Vgs
14 Vrd=Vee-Vds-Vs
15 Rd=Vrd/Id

```

---

**Scilab code Exa 10.12** determine Id and Vds

```

1 //chapter 10
2 //example 10.12
3 //page 415
4 printf("\n")
5 printf("given")
6 Idss=5*10^-3; Vgsoff=6; Rs=3.3*10^3; Vdd=20; Rd=Rs;
7 disp("when Id=0, Vgs=Vs=0")

```

```

8 Id=0;Vgs=0;Vs=0;
9 disp(" at point A universal transfer characteristic
      Id/Idss and Vgs/Vgsoff=0")
10 Id=1.5*10^-3;
11 Vgs=Id*Rs
12 y=Id/Idss;
13 x=Vgs/Vgsoff;
14 disp(" point B the universal transfer characteristic
      x=.825 and y=.3")
15 Id=.2*Idss
16 Vds=Vdd-Id*(Rd+Rs)

```

---

**Scilab code Exa 10.13** determine Idmax and Vdsmin

```

1 //chapter 10
2 //example 10.13
3 //page 416
4 printf("\n")
5 printf("given")
6 Idss=9*10^-3;Vgsoff=7;Vdd=22;R1=4.7*10^6;R2=1*10^6;
   Rs=2.7*10^3;Rd=Rs;
7 Vg=(Vdd*R2)/(R1+R2)
8 disp(" when Vgs=0, Vgs/Vgsoff=0")
9 Id=Vg/Rs
10 disp(" when Vgs/Vgsoff=.5")
11 Vgs=.5*(-Vgsoff)
12 Id=(Vg-Vgs)/Rs
13 x=Id/Idss
14 disp(" point Y on universal characteristic x=.3 and
      Vgs/Vgsoff=.5")
15 disp("draw voltage divider bias line through X nad Y
      where bisa line intersect transfer curve")
16 Id=.29*Idss
17 Vds=Vdd-Id*(Rd+Rs)

```

---



**Scilab code Exa 10.14** determine Id and Vds

```
1 //chapter 10
2 //example 10.14
3 //page 419
4 printf("\n")
5 printf(" given ")
6 Vdd=40;R2=1*10^6;R1=5.6*10^6;Rd=4.7;
7 Vg=(Vdd*R2)/(R1+R2)
8 disp("from the point where the bias line intersect
      the transfer curve")
9 Id=6.2
10 Vds=Vdd-Id*Rd
```

---

**Scilab code Exa 10.16** design JFET switching

```
1 //chapter 10
2 //example 10.16
3 //page 422
4 printf("\n")
5 printf(" given ")
6 rDS=25;Vgsoff=10;Vds=200*10^-3;Vdd=12;
7 Id=Vds/rDS
8 Rd=Vdd/Id
9 Vi=-(Vgsoff+1)
```

---

**Scilab code Exa 10.17** determine suitable resistance and calculate Vds

```
1 //chapter 10
```

```
2 //example 10.17
3 //page 424
4 printf("\n")
5 printf("given")
6 Vdd=50;Rd=10;R2=1*10^6;rDS=.25;
7 Id=Vdd/Rd
8 disp(" from transfer curve at Id=5 and Vgs=5.7")
9 Vgs=5.7;
10 R1=((Vdd-Vgs)*R2)/Vgs//use 6.8Mohm to make Vgs>5.7V
    to ensure that the FET is biased on
11 Vds=Id*rDS
```

---

# Chapter 11

## Ac analysis of FET circuits

**Scilab code Exa 11.2** circuit input and output impedance and voltage gain

```
1 //chapter 11
2 //example 11.2
3 //page 443
4 printf("\n")
5 printf("given")
6 Yos=10*10^-6;Yfs=3000*10^-6;R1=1*10^6;R2=5.6*10^6;Rd
   =2.7*10^3;Rl=Rd;
7 rd=1/Yos
8 Zi=((R1*R2)/(R1+R2))*10^-3;
9 printf("input impedance is %dKohm\n",Zi)
10 Zo=(Rd*rd)/(Rd+rd);
11 printf(" output inpedance is %dohm\n",Zo)
12 Av=-Yfs*((Rl*rd)/(Rl+rd))
```

---

**Scilab code Exa 11.3** gate input and source output impedance and voltage gain

```
1 //chapter 11
```

```

2 //example 11.3
3 //page 447
4 printf("\n")
5 printf("given")
6 Yos=10*10^-6; Yfs=4000*10^-6; Ig=1*10^-9; Vgs=15; Rs
   =3.3*10^3; Rg=1*10^6; Rd=4.7*10^3; Rl=33*10^3;
7 rd=1/Yos
8 Rgs=(Vgs/Ig)
9 Zg=(Rgs*(1+Yfs*Rs))
10 Zi=Rg;
11 Zd=rd+Rs+(Yfs*Rs*rd)
12 Zo=(Rd*Rl)/(Rd+Rl)
13 Av=-((Yfs*((Rd*Rl)/(Rd+Rl)))/(1+Yfs*Rs))
14 Av=-((Rd*Rl)/(Rd+Rl))/Rs

```

---

**Scilab code Exa 11.4** circuit input and output impedance and voltage gain

```

1 //chapter 11
2 //example 11.4
3 //page 451
4 printf("\n")
5 printf("given")
6 Yfs=3000*10^-6; Rgs=100*10^6; rd=50*10^3; Rs=5.6*10^3;
   Rl=12*10^3; R1=1.5*10^6; R2=1*10^6;
7 Zg=Rgs*(1+Yfs*((Rs*Rl)/(Rs+Rl)))
8 Zi=(R1*R2)/(R1+R2)
9 Zs=((1/Yfs)*rd)/((1/Yfs)+rd)
10 Zo=(Rs*Rl*(1/Yfs))/(Rs*Rl+Rs*(1/Yfs)+Rl*(1/Yfs))
11 Av=-((Yfs*((Rs*Rl)/(Rs+Rl)))/(1+Yfs*((Rs*Rl)/(Rs+Rl)))
   )

```

---

**Scilab code Exa 11.5** circuit and device input and output impedance and voltage gain

```

1 //chapter 11
2 //example 11.5
3 //page 456
4 printf("\n")
5 printf("given")
6 Yfs=3000*10^-6;rd=50*10^3;Rs=3.3*10^3;Rd=4.7*10^3;Rl
    =50*10^3;rs=600;
7 Zs=1/Yfs
8 Zi=((1/Yfs)*Rs)/((1/Yfs)+Rs)
9 Zd=rd
10 Zo=(Rd*rd)/(Rd+rd)
11 Av=Yfs*((Rd*Rl)/(Rd+Rl))
12 disp("overall volateg gain")
13 Av=(Yfs*((Rd*Rl)/(Rd+Rl))*Zi)/(rs+Zi)

```

---

#### Scilab code Exa 11.6 output voltage

```

1 //chapter 11
2 //example 11.6
3 //page 459
4 printf("\n")
5 printf("given")
6 Yfs=6000*10^-6;R1=100*10^3;R2=47*10^3;vs=50*10^-3;Rd
    =2.7*10^3;Rl=33*10^3;vs=50*10^-3;rs=600;Rs=Rd;
7 disp("CS circuit")
8 Av=-Yfs*((Rd*Rl)/(Rd+Rl))
9 Zi=(R1*R2)/(R1+R2)
10 vi=(vs*Zi)/(rs+Zi)
11 vo=Av*vi
12 disp("CG circuit")
13 Av=Yfs*((Rd*Rl)/(Rd+Rl))
14 Zi=((1/Yfs)*Rs)/((1/Yfs)+Rs)
15 vi=(vs*Zi)/(rs+Zi)
16 vo=Av*vi

```

---

Scilab code Exa 11.7 input capacitance limited cutoff frequency

```
1 //chapter 11
2 //example 11.7
3 //page 462
4 printf("\n")
5 printf("given")
6 Crss=1*10^-12; Ciss=5*10^-12; Yfs=2500*10^-6; Yos
   =75*10^-6; Rd=5.6*10^3; Rl=100*10^3; R1=3.3*10^6; R2
   =1*10^6; rs=600;
7 Cgd=Crss;
8 Cgs=Ciss-Crss
9 Av=Yfs*(((1/Yos)*Rd*Rl))/((Rd*Rl+(1/Yos)*Rd+(1/Yos)*
   Rl))
10 Cin=Cgs+(1+Av)*Cgd
11 Zi=(R1*R2)/(R1+R2)
12 f2=1/(2*3.14*Cin*((rs*Zi)/(rs+Zi)))
```

---

# Chapter 12

## Small signal Amplifiers

Scilab code Exa 12.1 required capacitance and voltage gain at different frequency

```
1 //chapter 12
2 //example 12.1
3 //page 474
4 printf("\n")
5 printf("given")
6 hfe=50;hie=1*10^3;hib=20;f1=100;Rc=3.3*10^3;Re=Rc;
7 disp(" required capacitance")
8 Xc2=hib;
9 C2=1/(2*3.14*f1*Xc2)
10 disp(" voltage gain with emitter terminal completely
      bypassed to ground")
11 Av=-(hfe*Rc)/hie
12 disp(" voltage gain when f=100")
13 Av=-(hfe*Rc)/sqrt(((hie^2)+((1+hfe)*Xc2)^2))
14 disp(" voltage gain when C2 is incorrectly selected
      as Xc2=Re/10")
15 Avx=-(hfe*Rc)/sqrt(((hie^2)+((1+hfe)*(Re/10))^2))
```

---

**Scilab code Exa 12.2** suitable resistor for common emitter amplifier

```
1 //chapter 12
2 //example 12.2
3 //page 477
4 printf("\n")
5 printf(" given")
6 Vcc=24;Ve=5;Vce=3;R1=120*10^3;Vbe=.7
7 Rc=R1/10
8 Vrc=Vcc-Vce-Ve
9 Ic=Vrc/Rc
10 Re=Ve/Ic//use 3.9Kohm standard value to make Ic
    littel less than design level
11 Re=3.9*10^3;
12 R2=10*Re
13 I2=(Ve+Vbe)/R2
14 R1=(Vcc-Ve-Vbe)/I2
```

---

**Scilab code Exa 12.3** suitable capacitor for CE

```
1 //chapter 12
2 //example 12.3
3 //page 477
4 printf("\n")
5 printf(" given")
6 hfe=100;Ie=1.3*10^-3;f1=100;R1=120*10^3;R2=39*10^3;
    rs=600;Rl=R1;
7 re=(26*10^-3)/Ie
8 Xc2=re;
9 C2=1/(2*3.14*f1*Xc2)
10 hie=(1+hfe)*re
11 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
12 C1=1/((2*3.14*f1*((Zi+rs)/10)))
13 C3=1/(2*3.14*f1*((Rc+Rl)/10))
```

---



**Scilab code Exa 12.4** suitable resistor for common source circuit

```
1 //chapter 12
2 //example 12.5
3 //page 485
4 printf("\n")
5 printf(" given ")
6 rs=600;f1=100;Yfs=6000*10^-6;R1=4.7*10^6;R2=1*10^6;
   Rd=6.8*10^3;Rl=120*10^3;
7 Xc2=1/Yfs
8 C2=1/(2*3.14*f1*Xc2)
9 Zi=(R1*R2)/(R1+R2)
10 C1=1/(2*3.14*f1*(Zi+rs)/10)
11 C3=1/(2*3.14*f1*(Rd+Rl)/10)
```

---

**Scilab code Exa 12.5** suitable resistor for common source amplifier

```
1 //chapter 12
2 //example 12.5
3 //page 485
4 printf("\n")
5 printf(" given ")
6 rs=600;f1=100;Yfs=6000*10^-6;R1=4.7*10^6;R2=1*10^6;
   Rd=6.8*10^3;Rl=120*10^3;
7 Xc2=1/Yfs
8 C2=1/(2*3.14*f1*Xc2)
9 Zi=(R1*R2)/(R1+R2)
10 C1=1/(2*3.14*f1*(Zi+rs)/10)
11 C3=1/(2*3.14*f1*(Rd+Rl)/10)
```

---

**Scilab code Exa 12.7** analyze two stage amplifier

```
1 //chapter 12
2 //example 12.7
3 //page 489
4 printf("\n")
5 printf(" given ")
6 R1=120*10^3;R2=39*10^3;hie=2*10^3;R7=12*10^3;Zo=R7;
   R5=R1;R6=R2;hfe=100;R3=R7;Zl=R1;
7 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
8 Zi2=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
9 Av1=-(hfe*((R3*Zi2)/(R3+Zi2)))/hie
10 Av2=-(hfe*((R7*Zl)/(R7+Zl)))/hie
11 Av=Av1*Av2
```

---

**Scilab code Exa 12.8** resistor for two stage direct coupled amplifier

```
1 //chapter 12
2 //example 12.8
3 //page 491
4 printf("\n")
5 printf(" given ")
6 Ve1=5;Vce1=3;Vce2=3;Vbe=.7;Vcc=14;R1=40*10^3;
7 Vb2=Ve1+Vce1
8 Vc1=Vb2;
9 Ve2=Vb2-Vbe
10 Vr5=Vcc-Ve2-Vce2
11 R5=R1/10//use 3.9Kohm satandard value
12 R5=3.9*10^3;
13 Ic2=Vr5/R5
14 R6=Ve2/Ic2//use 8.2Kohm as standard and recalculate
15 R6=8.2*10^3;
16 Ic2=Ve2/R6
17 Vr3=Vcc-Vc1
18 disp(" Ic1>>Ib2 ,select Ic1=1mA")
```

```

19 Ic1=1*10^-3;
20 R3=Vr3/Ic1//use standard value as 5.6Kohm and
    recalculate Ic1 in order ti keep Vb2=8V
21 R3=5.6*10^3;
22 Ic1=Vr3/R3
23 R4=Ve1/Ic1
24 Vr2=Ve1+Vbe
25 Vr1=Vcc-Ve1-Vbe
26 R2=10*R4
27 I2=(Ve1+Vbe)/R2
28 R1=(Vr1*R2)/Vr2

```

---

**Scilab code Exa 12.9** capacitor for two stage direct coupled amplifier

```

1 //chapter 12
2 //example 12.9
3 //page 493
4 printf("\n")
5 printf("given")
6 hfe=50;re=26;R1=68*10^3;R2=47*10^3;rs=600;f1=75;R5
    =3.9*10^3;Rl=40*10^3;
7 hie=(1+hfe)*re
8 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
9 Xc1=(Zi+rs)/10
10 C1=1/(2*3.14*f1*Xc1)
11 Xc2=.65*re
12 Xc3=Xc2;
13 C2=1/(2*3.14*f1*Xc2)
14 C3=C2;
15 Xc4=(R5+Rl)/10
16 C4=1/(2*3.14*f1*Xc4)

```

---

**Scilab code Exa 12.10** minimum overall voltage gain

```

1 //chapter 12
2 //example 12.10
3 //page 494
4 printf("\n")
5 printf(" given")
6 hfe=50;hie=1.3*10^3;R3=5.6*10^3;R5=3.9*10^3;R1
   =40*10^3;
7 Av1=-((hfe*((R3*hie)/(R3+hie)))/hie
8 Av2=-((hfe*((R5*R1)/(R5+R1)))/hie
9 disp(" overall voltage gain is Av=Av1*Av2")
10 Av=Av1*Av2

```

---

**Scilab code Exa 12.11** resistor for two stage amplifier

```

1 //chapter 12
2 //example 12.11
3 //page 497
4 printf("\n")
5 printf(" given")
6 Vp=100*10^-3;R1=100;Vbe=.7;Vcc=20;
7 ip=Vp/R1
8 disp(" select Ie2>ip")
9 Ie2=2*10^-3;
10 Ve1=5;Vce1=3;
11 Vb2=Ve1+Vce1
12 Vc1=Vb2;
13 Ve2=Vb2-Vbe
14 R5=Ve2/Ie2//use 3.3Kohm standard value
15 R5=3.3*10^3;
16 Ic1=1*10^-3;
17 Vr3=Vcc-Vb2
18 R3=Vr3/Ic1
19 R4=Ve1/Ic1//use 4.7Kohm standard value
20 R4=4.7*10^3;
21 Vb1=Ic1*R4+Vbe

```

```
22 R2=10*R4
23 R1=((Vcc-Vb1)*R2)/Vr2
```

---

**Scilab code Exa 12.12** suitable capacitor for circuit

```
1 //chapter 12
2 //example 12.11
3 //page 498
4 printf("\n")
5 printf("given")
6 rs=600;Ie1=1*10^-3;hfe=50;R1=120*10^3;R2=47*10^3;f1
   =150;Ie2=2*10^-3;R5=3.3*10^3;R3=12*10^3;Rl=100;
7 re=26*10^-3/Ie1
8 hie=(1+hfe)*re
9 Zi=(R1*R2*hie)/(R1*R2+R1*hie+R2*hie)
10 Xc1=(Zi+rs)/10
11 C1=1/(2*3.14*f1*Xc1) //use 6*10^-6 as standard value
12 Xc2=.65*re
13 C2=1/(2*3.14*f1*Xc2)
14 re2=26*10^-3/Ie2
15 Zo=(R5*(re2+R3/hfe))/(R5+(re2+R3/hfe))
16 Xc3=.65*(Rl+Zo)
17 C3=1/(2*3.14*f1*Xc3)
```

---

**Scilab code Exa 12.13** analyze two stage amplifier and determine minimum voltage gain

```
1 //chapter 12
2 //example 12.13
3 //page 499
4 printf("\n")
5 printf("given")
```

```

6  Ie2=2*10^-3;hfe=50;R5=3.3*10^3;R1=100;hfc2=51;R3
    =12*10^3;
7  re=26*10^-3/Ie2
8  hic=hfe*re
9  Zi2=hic+hfc2*((R1*R5)/(R1+R5))
10 Av1=-((hfe*((R3*Zi2)/(R3+Zi2)))/hie)
11 Av2=1
12 disp("overall voltage gain is Av=Av1*Av2")
13 Av=Av1*Av2

```

---

**Scilab code Exa 12.14** Dc feedback pair with an emitter follower output

```

1  //chapter 12
2  //example 12.14
3  //page 503
4  printf("\n")
5  printf("given")
6  vp=50*10^-3;R1=50;Ve2=5;Vcc=12;Vbe=.7;hFE=70;hfe
    =100;R2=120*10^3;f1=150;R3=150*10^3;R1=5.6*10^3;
    R4=2.2*10^3;
7  ip=vp/R1
8  disp("select Ie2>ip")
9  Ie2=2*10^-3;
10 R4=Ve2/Ie2//use standard 2.2Kohm
11 R4=2.2*10^3;
12 Ie2=Ve2/R4
13 Ic1=1*10^-3;
14 Vr1=Vcc-(Vbe+Ve2)
15 R1=Vr1/Ic1//use 5.6kohm and recalculate
16 R1=5.6*10^3;
17 Ic1=Vr1/R1
18 Ib1=Ic1/hFE
19 hie=hfe*(26*10^-3/Ic1)
20 hie2=hfe*((26*10^-3)/(2.27*10^-3))
21 Zi1=(R2*hie)/(R2+hie)

```

```

22 Xc1=Zi1/10
23 C1=1/(2*3.14*f1*Xc1)
24 Xc2=R3/100
25 C2=1/(2*3.14*f1*Xc2)
26 Zo=((hie2+R1)/hfe)*R4/(((hie2+R1)/hfe)+R4)
27 Xc3=R1+Zo
28 C3=1/(2*3.14*f1*Xc3)

```

---

**Scilab code Exa 12.15** suitable resistor for BIBET amplifier

```

1 //chapter 12
2 //example 12.15
3 //page 407
4 printf("\n")
5 printf(" given")
6 Vgsoff=-6; Idss=20*10^-3; Yfs=4000*10^-6; Id=2*10^-3;
   Vcc=20; Zi=500*10^3; R2=560*10^3; R1=80*10^3; Vbe=.7;
   Vce=3;
7 Vgs=Vgsoff*(1-sqrt(Id/Idss))
8 Vds=(-Vgsoff)+1-(-Vgs)
9 Vr3=(Vcc-Vds)/2
10 Vr4=Vr3;
11 R3=Vr4/Id//use 3.9kohm as standard and recalculate
   Vr3 and Vr4
12 R4=R3;
13 R4=3.9*10^3;
14 Vr3=Id*R4
15 Vr4=Vr3;
16 Vr2=Vr4-(-Vgs)
17 Vr1=Vcc-Vr2
18 R1=(Vr1*R2)/Vr2
19 R6=R1/10
20 Vr5=Vr3-Vbe
21 Vr6=Vcc-Vr5-Vce
22 Ic2=Vr6/R6

```

23  $R_5 = V_{r5} / I_{c2}$

---

**Scilab code Exa 12.16** suitable capacitor For BIFET direct coupled amplifier

```
1 //chapter 12
2 //example 12.16
3 //page 508
4 printf("\n")
5 printf("given")
6 R1=2.7*10^6;R2=560*10^3;f1=150;Yfs=8000*10^-6;Ie
   =1.2*10^-3;Rl=80*10^3;R6=8.2*10^3;
7 Zi=(R1*R2)/(R1+R2)
8 Xc1=Zi/10
9 C1=1/(2*3.14*f1*Xc1)
10 Xc2=.65/Yfs
11 C2=1/(2*3.14*f1*Xc2)//use 15pF as standard value
12 re=26*10^-3/Ie
13 Xc3=.65*re
14 C3=1/(2*3.14*f1*Xc3)
15 Xc4=(R6+Rl)/10
16 C4=1/(2*3.14*f1*Xc4)
```

---

**Scilab code Exa 12.17** determine minimum overall voltage gain

```
1 //chapter 12
2 //example 12.17
3 //page 509
4 printf("\n")
5 printf("given")
6 re=22;hfe=100;R3=3.9*10^3;Yfs=4000*10^-6;R6
   =8.2*10^3;Rl=80*10^3;
7 Zi2=hfe*re
```



```

8 Av1=-Yfs*((R3*Zi2)/(R3+Zi2))
9 Av2=-(hfe*((R6*R1)/(R6+R1)))/Zi2
10 disp("overall voltage is Av=Av1*Av2")
11 Av=Av1*Av2

```

---

**Scilab code Exa 12.18** suitable resistor for differential amplifier

```

1 //chapter 12
2 //example 12.18
3 //page 516
4 printf("\n")
5 printf("given")
6 hFE=60;hfe=60;hie=1.4*10^3;R1=70*10^3;Vce=3;Vbe=.7;
   Vcc=10;
7 Rc2=R1/10//use 6.8Kohm as standard value
8 Vrc2=Vcc+Vbe-Vce
9 Ic=Vrc2/Rc2
10 Ie=Ic;
11 Re=(Vcc-Vbe)/(2*Ie)//use 4.7 as standard value
12 Re=4.7*10^3;
13 Rb=Vbe/(10*(Ic/hFE))
14 Rb1=Rb;

```

---

**Scilab code Exa 12.19** suitable capacitor value for amplifier and voltage gain

```

1 //chapter 12
2 //example 12.19
3 //page 517
4 printf("\n")
5 printf("given")
6 f1=60;Ie=1.13*10^-3;hfe=60;Rb=3.9*10^3;R1=70*10^3;Rc
   =6.8*10^3;

```

```

7 re=26*10^-3/Ie//use 20 as standard value
8 re=20;
9 hie=hfe*re
10 Zb=2*hie
11 Zi=(Rb*Zb)/(Rb+Zb)
12 C1=1/(2*3.14*f1*Zi)
13 C2=1/(2*3.14*f1*(R1/10))
14 Av=(hfe*((Rc*R1)/(Rc+R1)))/(2*hie)

```

---

**Scilab code Exa 12.20** suitable resistor for cascode amplifier

```

1 //chapter 12
2 //example 12.20
3 //page 521
4 printf("\n")
5 printf("given")
6 Vcc=20;R1=90*10^3;hfe=50;hie=1.2*10^3;hib=24;Vce=3;
   Vce1=Vce;Ve=5;Vbe=.7;
7 Rc=R1/10//use 8.2kohm as standard value
8 Rc=8.2*10^3;
9 Vrc=Vcc-Vce-Vce1-Ve
10 Ic=Vrc/Rc
11 Re=Ve/Ic
12 Re=4.7*10^3;//use 4.7 as standard value
13 R3=10*Re
14 Vb1=Ve+Vbe
15 I3=Vb1/R3
16 Vb2=Ve+Vce+Vbe
17 Vr2=Vb2-Vb1
18 R2=Vr2/I3
19 R1=(Vcc-Vb2)/I3

```

---

**Scilab code Exa 12.21** suitable capacitor for cascode circuit

```

1 //chapter 12
2 //example 12.21
3 //page 522
4 printf("\n")
5 printf(" given")
6 f1=25;R2=24.7*10^3;R3=47*10^3;hie=1.2*10^3;hib=24;Rc
   =9*10^3;Rl=90*10^3;
7 Zi=(R2*R3*hie)/(R2*R3+R2*hie+R3*hie)
8 C1=1/(2*3.14*f1*(Zi/10))
9 C2=1/(2*3.14*f1*(hie/10))
10 C3=1/(2*3.14*f1*hib)
11 C4=1/(2*3.14*f1*((Rc+Rl)/10))

```

---

**Scilab code Exa 12.22** resonance frequency voltage gainbandwidth of amplifier

```

1 //chapter 12
2 //example 12.22
3 //page 525
4 printf("\n")
5 printf(" given")
6 hie=1*10^3;hfe=50;hoe=10*10^-6;Cc=5*10^-12;Cp
   =330*10^-12;Lp=75*10^-6;Rw=1;Rl=5*10^3;hfb=50;fo
   =1*10^6;
7 fo=1/(2*3.14*sqrt(Lp*(Cp+Cc)))
8 printf("resonance frequency is %3fHz\n",fo)
9 Zp=Lp/((Cp+Cc)*Rw)
10 Rc=1/hoe
11 RL=(Zp*Rc*Rl)/(Rl*Rc+Rc*Zp+Rl*Zp);
12 RL=4.7*10^3;//as standard value
13 Av=(hfb*RL)/hie;
14 printf(" voltage gain is %d\n",Av)
15 Qp=((Rc*Rl)/(Rc+Rl))/(2*3.14*fo*Lp)
16 QL=(2*3.14*fo*Lp)/Rw
17 disp(" since QL>Qp")

```

```
18 B=fo/Qp;
19 printf("bandwidth is %dHz\n",B)
```

---

**Scilab code Exa 12.23** resonance frequency voltage gainbandwidth of amplifier

```
1 //chapter 12
2 //example 12.23
3 //page 528
4 printf("\n")
5 printf("given")
6 hie=1*10^3;hfe=50;hoe=10*10^-6;Cc=5*10^-12;Cp
   =330*10^-12;Lp=75*10^-6;Rw=1;Rl=5*10^3;fo=1*10^6;
   zP=224*10^3;rC=100*10^3;K=.015;Ls=50*10^-6;
7 RL=(Zp*Rc)/(Rc+Zp)
8 disp("voltage gain from the input to the primary
   memory winding")
9 Avp=(hfe*RL)/hie
10 Vsp=K*sqrt(Ls/Lp)
11 disp("overall voltage gain from the input to teh
   secondary winding")
12 Av=Avp*Vsp
13 Qp=Rc/(2*3.14*fo*Lp)
14 Ql=471;
15 Q=(Ql*Qp)/(Ql+Qp)
16 B=fo/Q;
17 printf("bandwidth is %dHz\n",B)
```

---

**Scilab code Exa 12.24** capacitor to resonate secondry and overall voltage gain

```
1 //chapter 12
2 //example 12.24
```

```

3 //page 530
4 printf("\n")
5 printf(" given")
6 f=1*10^6;L2=50*10^-6;K=.015;L1=75*10^-6;rs=5;Rw=1;Lp
    =100*10^-6;Cp=330*10^-12;Cc=5*10^-12;Rc=100*10^3;
    hfe=50;hie=1*10^3;
7 C2=1/(((2*3.14*f)^2)*L2)
8 M=K*sqrt(L1*L2)
9 Rs=(((2*3.14*f)^2)*(M)^2)/rs
10 Rp=Rs+Rw
11 Zp=Lp/((Cp+Cc)*Rp)
12 Rl=(Zp*Rc)/(Zp+Rc)
13 disp("voltage gain from the input to primary winding
    ")
14 Avp=(hfe*Rl)/hie
15 Vsp=12.2*10^-3;
16 Vos=(((2*3.14*f)*L2)/rs)
17 disp("overall voltage gain from the input to
    secondary winding ")
18 Av=Avp*Vos*Vsp

```

---

# Chapter 13

## Amplifier with negative feedback

Scilab code Exa 13.1 closed loop gain for negative feedback amplifier

```
1 //chapter 13
2 //example 13.1
3 //page 547
4 printf("\n")
5 printf(" given ")
6 Av=100000; B=1/100;
7 disp(" when Av=100000")
8 Acl=Av/(1+Av*B)
9 disp(" when Av is 150000")
10 Av=150000;
11 Acl=Av/(1+Av*B)
12 disp(" when Av is 50000")
13 Av=50000;
14 Acl=Av/(1+Av*B)
```

---

Scilab code Exa 13.2 input impedance with negative feedback

```

1 //chapter 13
2 //example 13.2
3 //page 549
4 printf("\n")
5 printf("given")
6 Rf2=560;Rf1=56*10^3;Av=100000;Zb=1*10^3;R1=68*10^3;
   R2=33*10^3;
7 B=Rf2/(Rf2+Rf1)
8 Zi=(1+Av*B)*Zb
9 Zin=(Zi*R1*R2)/(R1*R2+R1*Zi+R2*Zi);
10 printf("input impedance with negative feedback is
   %dohm\n",Zin)

```

---

**Scilab code Exa 13.3** input and output impedance when negative feedback

```

1 //chapter 13
2 //example 13.3
3 //page 552
4 printf("\n")
5 printf("given")
6 Zb=1*10^3;B=1/100;Av=5562;R1=68*10^3;R2=47*10^3;hoe
   =1/(50*10^3);Rc=3.9*10^3;
7 Zi=(1+Av*B)*Zb
8 Zin=(R1*R2*Zi)/(R1*R2+R2*Zi+R1*Zi)
9 Zo=(1/hoe)/(1+Av*B)
10 Zout=(Rc*Zo)/(Rc+Zo);
11 printf(" circuit output impedance is %dohm\n",Zout)

```

---

**Scilab code Exa 13.4** circuit input and output impedance and voltage gain without feedback

```

1 //chapter 13

```

```

2 //example 13.4
3 //page 554
4 printf("\n")
5 printf("given")
6 Zb=1*10^3; hoe=1/(85*10^3); Av=58000; Rf2=220; Rf1
    =16.2*10^3; R1=120*10^3; R2=39*10^3; R7=12*10^3;
7 B=Rf2/(Rf2+Rf1)
8 disp("voltage gain")
9 Acl=Av/(1+Av*B)
10 Zi=Zb*(1+Av*B)
11 Zin=(Zi*R1*R2)/(Zi*R1+R2*R1+R2*Zi)
12 Zo=(1/hoe)/(1+Av*B)
13 Zout=(R7*Zo)/(R7+Zo)
14 printf("output impedance is %dohm\n",Zout)

```

---

**Scilab code Exa 13.5** two stage coupled BJT use as voltage feedback

```

1 //chapter 13
2 //example 13.5
3 //page 558
4 printf("\n")
5 printf("given")
6 Rf2=220; R4=3.9*10^3; Acl=75; f=100;
7 Rf1=(Acl-1)*Rf2
8 Xc2=Rf2;
9 C2=1/(2*3.14*f*Rf2)
10 Xcf1=Rf1/100;
11 Cf1=1/(2*3.14*f*Xcf1)

```

---

**Scilab code Exa 13.6** modify direct coupled amplifier to use as series voltage negative feedback

```

1 //chapter 13

```



```

2 //example 13.6
3 //page 560
4 printf("\n")
5 printf("given")
6 Ac1=300;Rf2=220;R4=4.7*10^3;f=100;
7 Rf1=(Ac1-1)*Rf2
8 xc2=Rf2;
9 C2=1/(2*3.14*f*Rf2)

```

---

**Scilab code Exa 13.7** calculate resistor value

```

1 //chapter 13
2 //example 13.7
3 //page 565
4 printf("\n")
5 printf("given")
6 hfe=100;Vbe=.7;Ic1=1*10^-3;Ic2=Ic1;Ic3=Ic2;Ic4=Ic3;
   Vee=10;Vce=3;Ac1=33;
7 disp("different resistor value of circuit")
8 R1=Vbe/((10*Ic1)/hfe)
9 R3=(Vee-Vbe)/(Ic1+Ic2)
10 Vr2=Vee+Vbe-Vce
11 R4=Vr2/Ic1
12 R2=R4;
13 R7=(Vr2-Vbe)/(Ic3+Ic4)
14 R8=Vee/Ic3
15 R6=6.8*10^3;
16 R5=(Ac1-1)*R6

```

---

**Scilab code Exa 13.8** calculate  $A_{cl}$   $Z_{in}$  and  $Z_{out}$

```

1 //chapter 13
2 //example 13.8

```

```

3 //page 566
4 printf("\n")
5 printf(" given")
6 Av=25000;hie=2*10^3;hib=25;hoe=1/(100*10^3);R6
    =6.8*10^3;R5=220*10^3;R1=R6;R8=10*10^3;
7 B=R6/(R5+R6)
8 Acl=Av/(1+Av*B)
9 Zi=2*hie*(1+Av*B)
10 Zin=(Zi*R1)/(Zi+R1)
11 Zo=(1/hoe)/(1+Av*B)
12 Zout=(R8*Zo)/(R8+Zo);
13 printf(" output impedance is %dohm\n",Zout)

```

---

**Scilab code Exa 13.9** calculate output impedance for circuit modification

```

1 //chapter 13
2 //example 13.9
3 //page 568
4 printf("\n")
5 printf(" given")
6 hic=2*10^3;hie=hic;hfe=100;hfc=100;Av=25000;B
    =1/33.4;R8=10*10^3;R5=R8;
7 Ze=(hic+R8)/hfc
8 Zo=Ze/(1+Av*B)
9 Zout=(R5*Zo)/(R5+Zo);
10 printf(" output impedance is %3.2fohm\n",Zout)

```

---

**Scilab code Exa 13.10** calculate precise value of circuit voltage gain

```

1 //chapter 13
2 //example 13.10
3 //page 570
4 printf("\n")

```

```

5 printf(" given ")
6 hfemin=100;hfemax=400;hiemin=2*10^3;hiemax=5*10^3;Rc
  =12*10^3;Rl=120*10^3;Re1=150
7 disp(" voltage gain at extreme value ")
8 Avmax=(hfemax*((Rc*Rl)/(Rc+Rl)))/(hiemax+Re1*(1+
  hfemax))
9 Avmin=(hfemin*((Rc*Rl)/(Rc+Rl)))/(hiemin+Re1*(1+
  hfemin))
10 disp(" approximate voltage gain ")
11 Av=((Rc*Rl)/(Rc+Rl))/Re1

```

---

**Scilab code Exa 13.11** modify Ce amplifier to use emitter current feedback to give  $A_v = 70$

```

1 //chapter 13
2 //example 13.11
3 //page 571
4 printf("\n")
5 printf(" given ")
6 Av=70;f=100;rs=600;Rc=12*10^3;Rl=120*10^3;Re2
  =3.9*10^3;hie=2*10^3;hfe=100;R1=Rl;R2=39*10^3;Re1
  =150;
7 Zb=hie+Re1*(1+hfe)
8 Zin=(R1*R2*Zb)/(R1*R2+R1*Zb+R2*Zb)
9 C1=1/(2*3.14*f*((Zin+rs)/10))
10 C2=1/(2*3.14*f*Re1)

```

---

**Scilab code Exa 13.12** suitable emitter resistor value

```

1 //chapter 13
2 //example 13.12
3 //page 573
4 printf("\n")

```

```

5 printf(" given ")
6 Av=1000;f=100;hie=2*10^3;hfe=100;R8=12*10^3;R1
    =120*10^3;R10=3.9*10^3;R6=R1;R7=39*10^3;R3=R8;
7 Av1=sqrt(Av)
8 Av2=Av1;
9 R9=((R8*R1)/(R8+R1))/Av2
10 R9=330; //use standard value
11 Av2=((R8*R1)/(R8+R1))/R9
12 Av1=Av/Av2
13 Zb=hie+R9*(1+hfe)
14 Zin=(R6*R7*Zb)/(R6*R7+R6*Zb+R7*Zb)
15 R4=((R3*Zin)/(R3+Zin))/Av1
16 R5=R10-R4

```

---

**Scilab code Exa 13.13** suitable capacitor for two stage circuit

```

1 //chapter 13
2 //example 13.13
3 //page 574
4 printf("\n")
5 printf(" given ")
6 f=100;hie=2*10^3;hfe=100;R8=12*10^3;R1=120*10^3;R10
    =3.9*10^3;R6=R1;R7=39*10^3;R3=R8;R4=220;rs=600;
    Zin2=16*10^3;R9=330;
7 Zb=hie+R4*(1+hfe)
8 Zin=(R1*R2*Zb)/(R1*R2+R1*Zb+R2*Zb)
9 C1=1/(2*3.14*f*((Zin+rs)/10))
10 Xc2=.65*R4;
11 C2=1/(2*3.14*f*Xc2)
12 C3=1/(2*3.14*f*((Zin2+R3)/10))
13 C4=1/(2*3.14*f*.65*R9)
14 C5=1/(2*3.14*f*((R8+R1)/10))

```

---

**Scilab code Exa 13.14** determine current gain and input impedance

```
1 //chapter 13
2 //example 13.14
3 //page 580
4 printf("\n")
5 printf("given")
6 hfe=100;hie=2*10^3;R4=100;R1=5.6*10^3;R6=2.2*10^3;
7 Zi=hie+(1+hfe)*R4
8 disp("open loop current gain")
9 Ai=(hfe*hfe*R1)/(R1+Zi)
10 B=R4/(R4+R6)
11 disp("closed loop gain")
12 Acl=Ai/(1+Ai*B)
13 Zi=hie/(1+Ai*B)
```

---

**Scilab code Exa 13.15** calculate total harmonic

```
1 //chapter 13
2 //example 13.15
3 //page 585
4 printf("\n")
5 printf("given")
6 Av=60000;Acl=300;f1=15*10^3;B=1/300;
7 f2=(Av*f1)/Acl
8 disp("% distortion with NFB")
9 NFB=(.1/(1+Av*B))*100;
10 printf(" percentatge distortion with NFB is %3.3f\n",NFB)
```

---

# Chapter 14

## Ic operational Amplifier and basic Op amp circuits

Scilab code Exa 14.1 calculate maximum resistance

```
1 //chapter 14
2 //example 14.1
3 //page 597
4 printf("\n")
5 printf(" given")
6 Vbe=.7; Ib=500*10^-9;
7 R1=Vbe/(10*Ib);
8 R1=120*10^3//use standard value
9 R2=R1;
10 I2=100*Ib
11 Vr1=15; Vr2=Vr1;
12 R1=Vr1/I2
13 R1=270*10^3; //use standard value
14 R2=R1;
15 R3=(R1*R2)/(R1+R2)
```

---

**Scilab code Exa 14.2** suitable resistor for BIFET op amp is used

```
1 //chapter 14
2 //example 14.2
3 //page 599
4 printf("\n")
5 printf(" given ")
6 R2=1*10^6; Vb=3; Vo=3; Vee=9;
7 Vr2=Vb-(-Vee)
8 Vr1=Vee-Vb
9 I2=Vr2/R2
10 R1=Vr1/I2
11 R3=0
```

---

**Scilab code Exa 14.3** typical difference between input and out voltage and Zin and Zout

```
1 //chapter 14
2 //example 14.3
3 //page 601
4 printf("\n")
5 printf(" given ")
6 Av=200000; ri=2*10^6; ro=75; Vo=1; B=1;
7 Vd=Vo/Av
8 Zi=(1+Av*B)*ri
9 Zo=ro/(1+Av*B)
```

---

**Scilab code Exa 14.4** capacitor coupled voltage follower usin 741 op amp

```
1 //chapter 14
2 //example 14.4
3 //page 603
4 printf("\n")
```

```

5 printf(" given")
6 f=70;R1=4*10^3;Ib=500*10^-9;Vbe=.7;
7 R1=Vbe/(10*Ib)
8 R1=120*10^3;//use standard value
9 R2=R1;
10 disp(" desire value of capacitor is C=1/2*3.14*f*R")
11 C2=1/(2*3.14*f*R1)
12 C1=1/(2*3.14*f*(R1/10))

```

---

**Scilab code Exa 14.5** direct coupled non inverting amplifier

```

1 //chapter 14
2 //example 14.5
3 //page 605
4 printf("\n")
5 printf(" given")
6 Ib=500*10^-9;Vi=50*10^-3;Vo=2;
7 I2=100*Ib;
8 R3=Vi/I2
9 R2=(Vo/I2)-R3
10 R1=(R2*R3)/(R2+R3)

```

---

**Scilab code Exa 14.6** typical input and output impedances for non inverting

```

1 //chapter 14
2 //example 14.6
3 //page 606
4 printf("\n")
5 printf(" given")
6 Av=200000;ri=2*10^6;ro=75;R3=1*10^3;R2=39*10^3;
7 B=R3/(R2+R3)
8 Zi=(1+Av*B)*ri

```



```
9 printf(" typical input impedance for non-inverting
    amplifier is %dohm\n", Zi)
10 Zo=ro/(1+Av*B)
```

---

**Scilab code Exa 14.7** voltage gain and lower cutoff frequency

```
1 //chapter 14
2 //example 14.7
3 //page 607
4 printf("\n")
5 printf(" given ")
6 R2=50*10^3; R3=2.2*10^3; C2=8.2*10^-6; R1=600;
7 disp(" voltage gain ")
8 Ac1=(R3+R2)/R3
9 disp(" lower cutoff frequency ")
10 f=1/(2*3.14*C2*R1)
```

---

**Scilab code Exa 14.8** direct coupled inverting amplifier

```
1 //chapter 14
2 //example 14.8
3 //page 610
4 printf("\n")
5 printf(" given ")
6 Ac1=144; Vi=20*10^-3; Ib=500*10^-9;
7 I1=100*Ib
8 R1=Vi/I1
9 R1=390; //use standard value
10 R2=Ac1*R1
11 R3=(R1*R2)/(R1+R2)
```

---

**Scilab code Exa 14.9** design three input summing amplifier

```
1 //chapter 14
2 //example 14.9
3 //page 612
4 printf("\n")
5 printf(" given")
6 Ac1=3;R4=1*10^6;Vi=1;
7 R1=R4/Ac1
8 R1=330*10^3;//use standard value
9 R2=R1;R3=R1;
10 I1=Vi/R1
11 I2=I1;I3=I1;
12 I4=I1+I2+I3
13 Vo=-I4*R4
```

---

**Scilab code Exa 14.10** suitable resistor for 741 op amp

```
1 //chapter 14
2 //example 14.10
3 //page 615
4 printf("\n")
5 printf(" given")
6 Ib=500*10^-9;Vi=1;Ac1=10;
7 I1=100*Ib
8 R1=Vi/I1
9 R1=18*10^3;//use standard value
10 R2=Ac1*R1
11 R4=R1
12 R3=R1/Ac1
```

---

**Scilab code Exa 14.11** overall voltage gain for instrumentation amplifier

```

1 //chapter 14
2 //example 14.11
3 //page 619
4 printf("\n")
5 printf("given")
6 Vi=10*10^-3; Vn=1; R1=33*10^3; R2=300; R5=15*10^3; R4
    =15*10^3; Vi2=-10*10^-3; R3=R1; R6=15*10^3; R7=R6;
7 Ac1=((2*R1+R2)/R2)*(R5/R4)
8 disp("at junction of R1 and R2")
9 Vb=Vi+Vn
10 disp("at junction of R2 and R3")
11 Vc=Vi2+Vn
12 disp(" current through R2")
13 I2=(Vb-Vc)/R2
14 disp("at the output of A1")
15 Va=Vb+(I2*R1)
16 disp("at output of A2")
17 Vd=Vc-(I2*R3)
18 disp("at junction of R6 and R7")
19 Vf=Vd*(R7/(R6+R7))
20 disp("at junction of R4 and R5")
21 Ve=Vf
22 disp("current through R4")
23 I4=(Va-Ve)/R4
24 disp("at output of A3")
25 Vg=Ve-(I4*R5)

```

---

**Scilab code Exa 14.12** typical output voltage swing and calculate rise time

```

1 //chapter 14
2 //example 14.12
3 //page 623
4 printf("\n")
5 printf("given")
6 Vcc=15; Vee=-15; Av=200000; SR=.5/10^-6; Vo=14;

```

```

7 V=(Vcc-1)-(Vee+1)
8 Vi=Vo/Av
9 disp("rise time of output is ")
10 t=(V/SR)*10^6;
11 printf("rise time of output is %dus\n",t)

```

---

**Scilab code Exa 14.13** calculate resistor for schmitt trigger circuit

```

1 //chapter 14
2 //example 14.13
3 //page 627
4 printf("\n")
5 printf("given")
6 Ib=500*10^-9;UTP=5;Vcc=15;
7 I1=100*Ib
8 R2=UTP/I1
9 R1=((Vcc-1)-5)/I1

```

---

**Scilab code Exa 14.14** upper and lower trigger for non inverting schmitt trigger

```

1 //chapter 14
2 //example 14.14
3 //page 630
4 printf("\n")
5 printf("given")
6 Vcc=15;Vsat=Vcc;R2=150*10^3;Vf=.7;R1=27*10^3;R3
  =120*10^3;
7 I2=(Vsat-Vf)/R2
8 UTP=I2*R1
9 disp(" LTP calculation including Vf")
10 I3=(Vsat-Vf)/R3
11 LTP=-I3*R1

```



# Chapter 15

## Operational amplifier frequency Response and compensation

Scilab code Exa 15.2 determine suitable component

```
1 //chapter 15
2 //example 15.2
3 //page 648
4 printf("\n")
5 printf(" given ")
6 R2=1*10^6; Ac1=4.5;
7 R1=R2/Ac1
8 R1=220*10^3; //use standard value
9 R3=(R1*R2)/(R1+R2)
10 Cf=((R1*30*10^-12)/(R1+R2))*10^12;
11 printf(" suitable value of capacitor is %3.2fpF\n",
        Cf)
```

---

Scilab code Exa 15.3 miller effect capacitor

```
1 //chapter 15
```

```

2 //example 15.3
3 //page 649
4 printf("\n")
5 printf("given")
6 f=35*10^3;Rf=68*10^3;
7 Cf=(1/(2*3.14*f*Rf))*10^12;
8 printf(" suitable miller effect capacitor is %dpF\n"
    ,Cf)

```

---

**Scilab code Exa 15.5** cutoff frequencies using gain bandwidth

```

1 //chapter 15
2 //example 15.5
3 //page 652
4 printf("\n")
5 printf("given")
6 Acl=100;Av=10;
7 disp(" for Cf=30pF")
8 GBW=800*10^3;
9 F2=GBW/Acl
10 disp(" for Cf=3pF")
11 GBW=(800*10^3)*Av;
12 f2=GBW/Acl

```

---

**Scilab code Exa 15.6** full power bandwidth for AD843 op amp circuit

```

1 //chapter 15
2 //example 15.6
3 //page 654
4 printf("\n")
5 printf("given")
6 Vip=1;R2=39*10^3;R3=4.7*10^3;SR=250/10^-6;f
    =100*10^3;

```

```

7 disp(" for the AD843")
8 Vop=((R2+R3)/R3)*Vip
9 fp=SR/(2*3.14*Vop);
10 printf("full power bandwidth is %dHz\n",fp)
11 disp(" for a 741")
12 SR=.5/10^-6;
13 Vp=SR/(2*3.14*f);
14 printf(" maximum peak output voltage is %3.2fV\n",Vp
)

```

---

#### Scilab code Exa 15.7 input terminal stray capacitor

```

1 //chapter 15
2 //example 15.7
3 //page 656
4 printf("\n")
5 printf(" given")
6 rs=600;R1=1*10^3;R2=10*10^3;f=800*10^3;
7 disp(" stray capacitance")
8 Cs=1/(2*3.14*f*10*((rs+R1)*R2)/(rs+R1+R2))
9 disp(" compensation capacitor")
10 C2=((Cs*(rs+R1))/R2)*10^12;
11 printf(" compensation capacitor is %3.2fpF\n",C2)

```

---

#### Scilab code Exa 15.8 load capacitance

```

1 //chapter 15
2 //example 15.8
3 //page 659
4 printf("\n")
5 printf(" given")
6 ro=25;f=2*10^6;R2=10*10^3;Rx=25;
7 C1=(1/(2*3.14*f*(10*ro)))*10^+12;

```



```
8 printf(" load capacitance is %3.2fpF\n",C1)
9 C1=.1*10^-6;
10 C2=((C1*(ro+Rx))/R2)*10^12;
11 printf(" compensation capacitance is %dpF\n",C2)
```

---

# Chapter 16

## Signal generators

Scilab code Exa 16.1 phase shift oscillator

```
1 //chapter 16
2 //example 16.1
3 //page 6568
4 printf("\n")
5 printf("given")
6 Vcc=10; Ib=500*10^-9; Acl=29; f=1*10^3;
7 disp(" phase shift oscillator")
8 I1=100*Ib
9 vo=Vcc-1
10 vi=vo/Acl
11 R1=vi/I1
12 R1=5.6*10^3; //use standard value 5.6Kohm
13 R2=Acl*R1
14 R2=180*10^3; //use standard value 180Kohm to give Acl
    >180
15 R3=R2; R=R1;
16 C=1/(2*3.14*R*f*sqrt(6))
```

---

Scilab code Exa 16.2 colpitts oscillator

```

1 //chapter 16
2 //example 16.2
3 //page 672
4 printf("\n")
5 printf(" given")
6 f=40*10^3;L=100*10^-3;vp=8;
7 disp(" colpitts oscillator")
8 Ct=1/(4*3.14*3.14*(f^2)*L)
9 C1=10*Ct
10 C2=1/((1/Ct)-(1/C1))
11 C2=180*10^-12; //use standard value
12 Xc2=1/(2*3.14*f*C2)
13 Xc1=1/(2*3.14*f*C1)
14 R1=10*Xc1
15 R1=27*10^3; //use standard value
16 Ac1=C1/C2
17 R2=Ac1*R1
18 R2=270*10^3; //use standard value
19 R3=(R1*R2)/(R1+R2)
20 f2=Ac1*f
21 SR=2*3.14*f*vp

```

---

### Scilab code Exa 16.3 hartley oscillator

```

1 //chapter 16
2 //example 16.3
3 //page 678
4 printf("\n")
5 printf(" given")
6 vo=8;f=100*10^3;
7 disp(" hartley oscillator")
8 Vcc=vo+1
9 Xl2=1*10^3;
10 L2=Xl2/(2*3.14*f)
11 L2=1.5*10^-3; //use standard value

```

```

12 L1=L2/10
13 Lt=L1+L2//(assuming M=0)
14 C1=1/(4*(3.14^2)*(f^2)*Lt)
15 C1=1500*10^-12;//use 1500pF with aadditional
    parallel capacitance if necessary
16 //C1>>stray capacitance
17 Xl1=2*3.14*f*L1//R1>>Xl1
18 R1=1*10^3;
19 Acl=L2/L1
20 R2=Acl*R1
21 R3=(R1*R2)/(R1+R2)
22 disp(" full power bandwidth ")
23 f2=Acl*f
24 SR=2*3.14*f*vo

```

---

#### Scilab code Exa 16.4 wein bridge oscillator

```

1 //chapter 16
2 //example 16.4
3 //page 680
4 printf("\n")
5 printf(" given ")
6 f=100*10^3;Vo=9;Acl=3;
7 disp(" design of wein bridge oscillator")
8 Vcc=Vo+1
9 C1=1000*10^-12;//standard value
10 C2=C1;
11 R1=1/(2*3.14*f*C1)
12 R2=R1;R4=R2;
13 R3=2*R4;
14 R3=3.3*10^3;//use standard value
15 disp(" minimum full power bandwidth")
16 f2=Acl*f
17 SR=2*3.14*f*Vo

```

---

### Scilab code Exa 16.5 phase shift oscillator

```
1 //chapter 16
2 //example 16.5
3 //page 683
4 printf("\n")
5 printf("given")
6 f=5*10^3;vo=5;I1=1*10^-3;Vf=.7;
7 disp("phase shift oscillator")
8 R1=(vo/29)/I1
9 R1=150;//use standard value
10 R2=29*R1
11 R4=(2*Vf)/I1
12 R4=1.5*10^3;//use 1.5kohm standard value
13 R5=R2-R4
14 R6=.4*R5
15 R7=.8*R5
16 R=R1;
17 C=1/(2*3.14*R*f*sqrt(6))
```

---

### Scilab code Exa 16.6 amplitude stabilization circuit

```
1 //chapter 16
2 //example 16.6
3 //page 686
4 printf("\n")
5 printf("given")
6 rds=600;Vgs=1;Vd1=.7;f=100*10^3;
7 disp("wien bridge ocillator")
8 R4=560;
9 R3=2*((R4*rds)/(R4+rds))
10 I5=200*10^-6;Vo=6;
```

```

11 R6=Vgs/I5
12 R5=(Vo-(Vgs+Vd1))/I5
13 disp(" C4 discharge voltage ")
14 Vc=.1*Vgs
15 disp("C4 discharge time")
16 T=1/f
17 Ic=I5;
18 C4=(Ic*T)/Vc
19 Xc3=rds/10//at oscillating frequency
20 C3=1/(2*3.14*f*Xc3)

```

---

**Scilab code Exa 16.7** square wave generator

```

1 //chapter 16
2 //example 16.7
3 //page 689
4 printf("\n")
5 printf("given")
6 Vo=14;Vr3=.5;Ib=500*10^-9;f=1*10^3;
7 disp("square wave generator")
8 Vcc=Vo+1
9 UTP=Vr3;LTP=UTP;
10 I2=100*Ib;
11 R3=Vr3/I2
12 R2=(Vo-Vr3)/I2
13 t=1/(2*f)
14 V=UTP-(-LTP)
15 C1=.1*10^-6;
16 I1=(C1*V)/t
17 R1=Vo/I1

```

---

**Scilab code Exa 16.8** calculate t1 t2 and pulse frequency

```

1 //chapter 16
2 //example 16.8
3 //page 694
4 printf("\n")
5 printf("given")
6 R1=2.2*10^3;R2=2.7*10^3;C2=.5*10^-6;Vcc=15;
7 t1=.693*C2*(R1+R2)
8 t2=.693*C2*R2
9 T=t1+t2
10 f=1/T
11 Ic1=(Vcc/3)/(R1+R2)

```

---

**Scilab code Exa 16.10** triangular wave generator

```

1 //chapter 16
2 //example 16.10
3 //page 699
4 printf("\n")
5 printf("given")
6 Vcc=9;Vo=3;I1=1*10^-3;f=500;UTP=3;
7 disp("design the triangular wave")
8 Vi=Vcc-1
9 V=Vo-(-Vo)
10 disp(" I1>>Ibmax for op-amp")
11 R1=Vi/I1
12 t=1/(2*f)
13 C1=(I1*t)/V
14 disp("schmitt design")
15 I2=1*10^-3;
16 R2=UTP/I2
17 R3=(Vcc-1)/I2

```

---

**Scilab code Exa 16.11** wein bridge oscillator

```

1 //chapter 16
2 //example 16.11
3 //page 705
4 printf("\n")
5 printf("given")
6 f=100*10^3;Rs=1.5*10^3;
7 R1=2*Rs
8 R1=2.7*10^3;//use standard value
9 R2=R1+Rs
10 C1=1/(2*3.14*f*R2)
11 R4=R2;
12 R3=2*R4

```

---

**Scilab code Exa 16.12** pierce oscillator and peak power dissipated

```

1 //chapter 16
2 //example 16.12
3 //page 705
4 printf("\n")
5 printf("given")
6 fs=1*10^6;Rs=700;C1=1000*10^-12;C2=100*10^-12;R1
   =1*10^6;R2=10*10^3;Rs=700;Vdd=5;
7 Ct=(C1*C2)/(C1+C2)
8 disp(" at resonance  $Xl=Xct$   $2*pi*f*L=1/2*pi*f*Ct$ ")
9 L=1/(((2*3.14*f)^2)*Ct)
10 ip=Vdd/(R1+R2+Rs)
11 Pd((((0.707*ip)^2)*Rs)*10^9;
12 printf(" peak power dissipated is %3.3fnW\n",Pd)

```

---



# Chapter 17

## Active filters

Scilab code Exa 17.1 calculate attenuation

```
1 //chapter 17
2 //example 17.1
3 //page 716
4 printf("\n")
5 printf("given")
6 rs=600;R1=12*10^3;Rl=100*10^3;C1=.013*10^-6;
7 disp("when Rl is not connected")
8 fc=1/(2*3.14*R1*C1)
9 disp(" when Rl is connected")
10 fc=1/(2*3.14*((R1*Rl)/(R1+Rl))*C1)
11 Attn=3//at fc attenuation is =3dB
12 falloffrate=6
13 disp("attenuation at 2fc")
14 Attn=3+6;
15 printf("attenuation at 2fc is %ddB\n",Attn)
16 Attn=3+6+6;
17 printf(" attenuation at 4fc is %ddB\n",Attn)
```

---

Scilab code Exa 17.2 first order active low pass filter

```

1 //chapter 17
2 //example 17.2
3 //page 718
4 printf("\n")
5 printf(" given")
6 Ib=500*10^-9;f=1*10^3;
7 R1=(70*10^-3)/Ib
8 R1=140*10^3;//use standard value
9 R2=R1;
10 C1=(1/(2*3.14*R1*f))*10^12;
11 printf(" capacitor used is of %dpF\n",C1)

```

---

**Scilab code Exa 17.3** first order high pass filter and filter bandwidth

```

1 //chapter 17
2 //example 17.3
3 //page 719
4 printf("\n")
5 printf(" given")
6 disp(" first order high pass active filter")
7 f=5*10^3;C1=1000*10^-12;fu=1*10^6;
8 R1=1/(2*3.14*f*C1)
9 BW=fu-f;
10 printf(" bandwidth is %dHz\n",BW)

```

---

**Scilab code Exa 17.4** butterworth second order low pass filter

```

1 //chapter 17
2 //example 17.4
3 //page 724
4 printf("\n")
5 printf(" given")
6 f=1*10^3;Ib=500*10^-9;

```

```

7 disp("butterworth second order filter")
8 R=(70*10^-3)/Ib
9 R1=R/2
10 R1=68.1*10^3;//use standard value
11 R2=R1;
12 R3=2*R1
13 Xc1=sqrt(2)*R2
14 C1=1/(2*3.14*f*sqrt(2)*R2)
15 C2=2*C1
16 fc=1/(2*3.14*(sqrt(R1*R2*C1*C2)));
17 printf("actual cutoff frequency is %dHz\n",fc)

```

---

**Scilab code Exa 17.5** using BIFET op amp design butterworth second order filter

```

1 //chapter 17
2 //example 17.5
3 //page 7
4 printf("\n")
5 printf("given")
6 f=12*10^3;C1=1000*10^-12;
7 disp("butterworth second order filter")
8 C2=C1;
9 R2=(sqrt(2))/(2*3.14*f*C1)
10 R1=.5*R2
11 R3=R2;
12 fc=1/(2*3.14*(sqrt(R1*R2*C1*C2)));
13 printf("actual cutoff frequency is %dHz\n",fc)

```

---

**Scilab code Exa 17.6** third order low pass filter

```

1 //chapter 17
2 //example 17.6

```

```

3 //page 729
4 printf("\n")
5 printf("given")
6 f=30*10^3;C1=1000*10^-12;
7 disp(" third order low pass filter")
8 disp("-20 dB per decade stage")
9 fc1=f/.65;
10 R1=1/(2*3.14*fc1*C1)
11 R2=R1;
12 disp("-40dB per decade stage")
13 C3=1000*10^-12;
14 C2=2*C3
15 fc2=f/.8
16 R4=1/(2*3.14*fc2*C3*(sqrt(2)))
17 R3=R4;
18 R5=R3+R4

```

---

#### Scilab code Exa 17.7 third order high pass filter

```

1 //chapter 17
2 //example 17.7
3 //page 730
4 printf("\n")
5 printf("given")
6 f=20*10^3;
7 disp("3rd order high pass filter")
8 disp("-20dB per decade stage")
9 R1=121*10^3;
10 fc1=.65*f
11 C1=1/(2*3.14*fc1*R1)
12 //this is so small it might be effected by stray
    capacitor.redesign ,first choosing a suitable
    capacitance C1
13 C1=100*10^-12;
14 R1=1/(2*3.14*f*C1)

```

```

15 R2=R1;
16 disp("−40dB per decade stage")
17 C3=1000*10−12;
18 R4=(sqrt(2))/(2*3.14*.8*f*C3)
19 C2=C3;
20 R3=.5*R4
21 R5=R4

```

---

**Scilab code Exa 17.8** single stage band pass filter

```

1 //chapter 17
2 //example 17.8
3 //page 734
4 printf("\n")
5 printf("given")
6 f1=300;f2=30*103;
7 disp(" single stage band pass filter")
8 C2=1000*10−12;
9 R2=1/(2*3.14*f2*C2)
10 R1=R2;
11 Xc1=R1;//at voltage gain Av=1
12 C1=1/(2*3.14*f1*R1)
13 R3=R2

```

---

**Scilab code Exa 17.9** calculate Q factor for wide band filter

```

1 //chapter 17
2 //example 17.9
3 //page 736
4 printf("\n")
5 printf("given")
6 f1=300;f2=30*103;
7 fo=sqrt(f1*f2)

```

```
8 BW=f2-f1
9 Q=f0/BW
```

---

### Scilab code Exa 17.10 center frequency and bandwidth

```
1 //chapter 17
2 //example 17.10
3 //page 737
4 printf("\n")
5 printf("given")
6 R1=60.4*10^3;R4=1.21*10^3;C=.012*10^-6;R2=121*10^3;
7 Q=sqrt((R1+R4)/(2*R4))
8 f0=Q/(3.14*C*R2);
9 printf(" center frequency is %3.2 fHz\n",f0)
10 BW=f0/Q;
11 printf(" bandwidth is %3.1 fHz\n",BW)
```

---

### Scilab code Exa 17.12 state variable band pass filter

```
1 //chapter 17
2 //example 17.12
3 //page 744
4 printf("\n")
5 printf("given")
6 f1=10.3*10^3;f2=10.9*10^3;
7 C1=1000*10^-12;C2=C1;
8 f0=sqrt(f1*f2)
9 R5=1/(2*3.14*f0*C1)
10 R1=R5;
11 Q=f0/(f2-f1)
12 R2=R1*(2*Q-1)
```

---

**Scilab code Exa 17.13** required resistance to operate one half of an MF10

```
1 //chapter 17
2 //example 17.13
3 //page 750
4 printf("\n")
5 printf(" given")
6 f1=10.3*10^3;f2=10.9*10^3;Hobp=34;
7 sqrt(f1*f2)
8 Q=fo/(f2-f1)
9 R3=120*10^3;
10 R2=R3/Q
11 R1=R3/Hobp
12 fck=50*fo
```

---

# Chapter 18

## Linear and switching voltage regulators

Scilab code Exa 18.1 load and source effects and load and line regulation

```
1 //chapter 18
2 //example 18.1
3 //page 761
4 printf("\n")
5 printf(" given")
6 Vs=21;Vo=12;Av=100;
7 vo=(Vs*.1)/Av;//source effect is 10% of the Vs
8 printf(" source effect is %3.3fV\n",vo)
9 vo=(21-20)/100;
10 printf(" laod effect is %3.3fV\n",vo)
11 LR=(21*10^-3 *100)/12;
12 printf(" line regulation is %3.3 fpercentage\n",LR)
13 LR=(10*10^-3*100)/12;
14 printf(" load effect is %3.3 fpercentage \n",LR)
15 RJ=20*log10(1/Av);
16 printf(" ripple rejection is %ddb\n",RJ)
```

---



### Scilab code Exa 18.2 voltage regulator circuit

```
1 //chapter 18
2 //example 18.2
3 //page 762
4 printf("\n")
5 printf("given")
6 Vo=12; I1=40*10^-3; Vs=20; Vbe=.7;
7 Vz=.75*Vo
8 disp("for minimum D1 current select")
9 Ir2=10*10^-3;
10 R2=(Vo-Vz)/Ir2
11 Ie1=I1+Ir2
12 disp("specification for Q")
13 Vce1=20; Vs=Vce1;
14 Ic1=50*10^-3;
15 Pd=(Vs-Vo)*Ie1
16 hfe=50;
17 Ib1=Ie1/hfe
18 Ic2=5*10^-3;
19 R1=(Vs-(Vo+.7))/(Ic2+Ib1)
20 Iz=Ie2+Ir2
21 I4=1*10^-3;
22 R4=(Vz+Vbe)/I4
23 R3=(Vo-(Vz+Vbe))/I4
```

---

### Scilab code Exa 18.3 modify voltage regulator

```
1 //chapter 18
2 //example 18.3
3 //page 765
4 printf("\n")
5 printf("given")
6 I4=1*10^-3; Vb2=9.8;
7 disp(" for Vo=11V moving contact at top of R5")
```

```

8 Vo=11;
9 R3=(Vo-Vb2)/I4
10 R=Vb2/I4//R=R4+R5
11 disp(" for Vo=13V moving contact at bottom of R5")
12 Vo=13;
13 I4=Vo/(R3+R)
14 R4=Vb2/I4
15 R5=R-R4

```

---

**Scilab code Exa 18.4** voltage regulator to change the load current

```

1 //chapter 18
2 //example 18.4
3 //page 766
4 printf("\n")
5 printf(" given ")
6 hFE3=50; hFE1=20; Ie1=200*10^-3+10*10^-3; Ic2=1*01^-3;
   Vs=20; Vb3=13.4; Vo=12; Vbe=.7;
7 Ib1=Ie1/hFE1
8 Ib3=Ib1/hFE3
9 R1=(Vs-Vb3)/(Ic2+Ib3)
10 disp(" select I6=.5*10^-3")
11 I6=.5*10^-3;
12 R6=(Vo+Vbe)/I6
13 Pd=(Vs-Vo)*Ie1

```

---

**Scilab code Exa 18.5** suitable component for preregulator circuit

```

1 //chapter 18
2 //example 18.5
3 //page 769
4 printf("\n")
5 printf(" given ")

```

```

6 Vr1=3; Ic2=1*10^-3; Ib3=.21*10^-3; Vbe1=.7; Vbe3=Vbe1; Vs
  =20;
7 R1=Vr1/(Ic2+Ib3)
8 Vz2=Vo+Vbe1+Vbe3+Vr1
9 Ir7=5*10^-3;
10 R2=(Vs-Vz2)/Ir7

```

---

### Scilab code Exa 18.6 differential amplifier

```

1 //chapter 18
2 //example 18.6
3 //page 770
4 printf("\n")
5 printf("given")
6 Vc5=9.8; Vb2=Vc5; Vce5=3; Vbe=.7; Vo=12;
7 Vr9=Vc5-Vce5
8 Vz2=Vr9+Vbe
9 Ic5=1*10^-3;
10 R8=(Vo-Vc5)/Ic5
11 Ir9=2*Ic5
12 R9=Vr9/Ir9
13 disp(" Iz2>>Ib5 and Iz2>(Izk for the zener diode)")
14 Iz2=10*10^-3;
15 R7=(Vo-Vz2)/Iz2
16 I4=1*10^-3;
17 Vb6=7.5; Vz2=Vb6;
18 disp(" when Vo=11V(moving contact at top of R5)")
19 Vo=11;
20 R3=(Vo-Vb6)/I4
21 R3=3.3*10^3; //use standard value
22 I4=(Vo-Vb6)/R3
23 R=Vb6/I4 //R=R4+R5
24 disp(" when Vo=13V(moving contact at bottom of R5)")
25 Vo=13; Vb6=7.5;
26 I4=Vo/(R3+R)

```

```
27 R4=Vb6/I4
28 R5=R-R4
```

---

**Scilab code Exa 18.7** fold back current limiting circuit for voltage regulator

```
1 //chapter 18
2 //example 18.7
3 //page 7
4 printf("\n")
5 printf("given")
6 Isc=100*10^-3; Vr10=.5; Vo=12;
7 R10=Vr10/Isc
8 R10=4.7; //use standard value
9 I1=200*10^-3;
10 Vr10=I1*R10
11 Vr11=Vr10-.5
12 I11=1*10^-3;
13 R11=Vr11/I11
14 R12=(Vo+Vr10-Vr11)/I11
```

---

**Scilab code Exa 18.8** adjustable voltage regulator circuit

```
1 //chapter 18
2 //example 18.8
3 //page 778
4 printf("\n")
5 printf("given")
6 Vo=12; hFE1=20; hFE2=50; I1=250*10^-3;
7 Vz=.75*Vo
8 Vz=9.1; //use standard value for 1N757 diode
9 Iz1=10*10^-3;
10 R1=(Vo-Vz)/Iz1
```

```

11 I3=1*10^-3;
12 disp(" when V0=12V(moving contact at top of R5)")
13 R3=(Vo-Vz)/I3
14 R=Vz/I3
15 disp(" when Vo=15V moving contact at bottom of R5")
16 Vo=15;
17 I3=Vo/(R+R3)
18 R4=Vz/I3
19 R5=R-R4
20 Ir6=.5*10^-3;
21 R6=Vo/Ir6
22 disp(" op-amp output current")
23 Ib2=I1/(hFE1*hFE2)

```

---

**Scilab code Exa 18.9** input voltage and maximum load current

```

1 //chapter 18
2 //example 18.9
3 //page 782
4 printf("\n")
5 printf(" given")
6 I2=1*10^-3;Vr2=7.15;Vref=Vr2;Vo=10;Pdmax=1000*10^-3;
7 R2=Vref/I2
8 R2=6.8*10^3;//use standard value and recalculate the
   I2
9 I2=Vref/R2
10 R1=(Vo-Vref)/I2
11 Vs=Vo+5//for satisfactory operation of series pass
   transistor
12 Iint=25*10^-3;//internal circuit current
13 Pi=Vs*Iint
14 disp("maximum power dissipated in series pass
   transistor")
15 Pd=Pdmax-Pi
16 disp("maximum load current is ")

```

17  $I_1 = P_d / (V_s - V_o)$

---

**Scilab code Exa 18.10** calculate regulator power dissipation

```
1 //chapter 18
2 //example 18.10
3 //page 785
4 printf("\n")
5 printf("given")
6 I1=1*10^-3;Vref=1.25;Vo=6;Vs=15;I1=200*10^-3;
7 R1=Vref/I1
8 R2=(Vo-Vref)/I1
9 Pd=(Vs-Vo)*I1;
10 printf("regulated power dissipation is %3.2fW\n",Pd)
```

---

**Scilab code Exa 18.11** efficiencies of linear regulator and switching regulator

```
1 //chapter 18
2 //example 18.11
3 //page 788
4 printf("\n")
5 printf("given")
6 Vo=10;Io=1;Vce=7;Vf=1;
7 Po=Vo*Io
8 disp(" linear regulator")
9 Pi=Po+(Vce*Io)
10 n=(Po*100)/Pi//efficiency
11 disp(" switching regulator")
12 Vce=1;
13 Pi=Po+Io*(Vce+Vf)
14 n=(Po*100)/Pi//efficiency
```

---

**Scilab code Exa 18.12** step down switching regulator

```
1 //chapter 18
2 //example 18.12
3 //page 792
4 printf("\n")
5 printf("given")
6 f=50*103;Vo=12;Vf=.7;Vi=30;Vsat=1;Io=500*10-3;Vr
   =100*10-3;
7 T=1/f
8 t=(Vo+Vf)/(Vi-Vsat-Vo)
9 toff=T/1.75
10 ton=T-toff
11 Ip=2*Io
12 L1=((Vi-Vsat-Vo)*ton)/Ip
13 C1=Ip/(8*f*Vr)
```

---

**Scilab code Exa 18.13** determine suitable value for R1 R2 Rsc and Ct

```
1 //chapter 18
2 //example 18.13
3 //page 799
4 printf("\n")
5 printf("given")
6 disp(" an MC34063 controller is for step down
   transformer")
7 Ib=-400*10-3;I1=1*10-3;Vref=1.25;V0=12;Ip=1;ton
   =8.6*10-6;
8 R1=Vref/I1
9 R1=1.2*103; //use standard value
10 I1=Vref/R1
11 R2=(Vo-Vref)/I1
```

12  $R_{sc} = .33 / I_p$

13  $C_t = 4.8 * 10^{-5} * t_{on}$

---



# Chapter 19

## Power amplifiers

**Scilab code Exa 19.1** Dc and Ac load line transistor common emitter characteristics

```
1 //chapter 19
2 //example 19.1
3 //page 810
4 printf("\n")
5 printf("given")
6 Rpy=40; N1=74; N2=14; R2=3.7*10^3; R1=4.7*10^3; Vbe=.7; Re
   =1*10^3; Vcc=13; Rl=56;
7 disp("Q-point")
8 Vb=Vcc*(R2/(R1+R2))
9 Ic=(Vb-Vbe)/Re
10 Ie=Ic;
11 Vce=Vcc-Ic*(Rpy+Re)
12 rl=(N1/N2)^2 *Rl
13 rl=rl+Rpy
14 Ic=5*10^-3;
15 Vce=Ic*rl
```

---

**Scilab code Exa 19.2** maximum efficiency of class A amplifier

```

1 //chapter 19
2 //example 19.2
3 //page 814
4 printf("\n")
5 printf(" given")
6 Vcc=13;Icq=5*10^-3;Vceq=8;Vp=Vceq;Ip=Icq;nt=.8;
7 Pi=Vcc*Icq
8 Po=.5*Vp*Ip
9 P0=nt*Po
10 n=(P0/Pi)*100;
11 printf(" maximum efficiency is %3.2f percentage\n",n
    )

```

---

**Scilab code Exa 19.4** power deliver to load in class AB amplifier

```

1 //chapter 19
2 //example 19.4
3 //page 821
4 printf("\n")
5 printf(" given")
6 N1=60;N2=10;R1=16;Rpy=0;R6=56;Vcc=27;Vce=.5;n=.79;
7 disp(" Referred laod")
8 r1=(N1/N2)^2 *R1
9 disp(" tatol ac load line in series with each of Q2
    and Q3")
10 Rl=r1+R6+Rpy
11 disp(" peak primary current")
12 Ip=(Vcc-Vce)/Rl
13 disp(" peak primary voltage")
14 Vp=Vcc-Vce-(Ip*R6)
15 disp(" power delivered to primary")
16 Po=.5*Vp*Ip
17 disp(" power delivered to the load")
18 Po=Po*n//n is power efficiency

```

---

**Scilab code Exa 19.5** output transformer and transistor of class B circuit

```
1 //chapter 19
2 //example 19.5
3 //page 824
4 printf("\n")
5 printf("given")
6 Po=4; nt=.8; Vcc=30; Vp=Vcc; Rl=16;
7 P0=Po/nt
8 rl=(Vp)^2 / (2*P0)
9 rl=4*rl
10 disp("transformer specification Po=4 ,Rl=16 rl=360")
11 Vce=2*Vcc
12 Ip=(2*P0)/Vp
13 Pi=Vcc*.636*Ip
14 Pt=.5*(Pi-P0)
15 disp(" transistor specification is Py=.68W Vce=60
      Ip=333mA")
```

---

**Scilab code Exa 19.6** determine required supply voltage for class AB amplifier

```
1 //chapter 19
2 //example 19.6
3 //page 830
4 printf("\n")
5 printf("given")
6 Rl=50; Po=1; hFE=50; Vbe=.7; Vrc=4; Vre=1; Vd1=.7; Vd2=Vd1;
7 Vp=sqrt(2*Rl*Po)
8 Ip=Vp/Rl
9 Re3=.1*Rl;
10 Re2=4.7; //use standard value
```

```

11 Re2=Re3;
12 Icq=.1*Ip
13 Vb=Vbe+Icq*(Re2+Re3)+Vbe
14 Vc1=Vrc;
15 Ib2=Ip/hFE
16 Irc=Ib2+1*10^-3
17 Rc=Vrc/Irc
18 Rc=680; //use standard value
19 Vcc=2*(Vp+Vre+Vbe+Vrc)
20 Vcc=32; //use standard value
21 Vrcdc=.5*(Vcc-Vb)
22 Ic1=Vrcdc/Rc
23 Rb=(Vb-Vd1-Vd2)/Ic1

```

---

#### Scilab code Exa 19.7 output transistors

```

1 //chapter 19
2 //example 19.7
3 //page 832
4 printf("\n")
5 printf("given")
6 Vcc=32;Vce=32;Ip=200*10^-3;Po=1;
7 Ic=1.1*Ip
8 Pi=.35*Vcc*Ip
9 Pt=.5*(Pi-Po)

```

---

#### Scilab code Exa 19.8 capacitor value for Ce and Co

```

1 //chapter 19
2 //example 19.8
3 //page 832
4 printf("\n")
5 printf("given")

```

```

6 f=50;hib=2;Rl=50;
7 Ce=1/(2*3.14*f*hib)
8 Co=1/(2*3.14*50*.1*Rl)

```

---

**Scilab code Exa 19.9** determine the value of  $V_{cc}$   $R_c$  and  $R_b$  for class AB amplifier

```

1 //chapter 19
2 //example 19.9
3 //page 834
4 printf("\n")
5 printf(" given")
6 hFE=2000;Vbe=1.4;Vp=10;Ip=200*10^-3;Icq2=20*10^-3;
   Re3=4.7;Re2=4.7;Vd=.7;
7 Ve1=3;Vc1=15.2;Vrc=Vc1;
8 Vb=Vbe+Icq*(Re2+Re3)+Vbe
9 Vcc=Vrc+Vc1+Vb
10 Ib2=Ip/hFE
11 Irc=1*10^-3;
12 Vrcac=4;
13 Rc=Vrcac/Irc
14 Ic1=Vrc/Rc
15 Rb=(Vb-(4*Vd))/Ic1

```

---

**Scilab code Exa 19.10** design  $V_{be}$  multiplier

```

1 //chapter 19
2 //example 19.10
3 //page 838
4 printf("\n")
5 printf(" given")
6 Vb=3.2;Ic1=5*10^-3;Vce=3.2;Vbe=.7;
7 Vbmin=Vb-.5

```

```

8 Vbmax=Vb+.5
9 I10=.1*Ic1
10 R10=(Vce-Vbe)/I10
11 R10=4.7*10^3; //use standard value
12 disp(" for Vce=3.7")
13 Vce=3.7;
14 I10max=(Vce-Vbe)/R10
15 disp(" Vce=2.7V")
16 Vce=2.7;
17 I10min=(Vce-Vbe)/R10
18 R=Vbe/I10min
19 R11=Vbe/I10max
20 R12=R-R11

```

---

**Scilab code Exa 19.11** required supply voltage and specify output transistors

```

1 //chapter 19
2 //example 19.11
3 //page 843
4 printf("\n")
5 printf(" given")
6 R1=16;Po=6;Vbe=.7;
7 Vp=sqrt(2*R1*Po)
8 Vr14=.1*Vp;Vr15=Vr14;
9 R14=.1*R1;R15=R14;
10 Vce3=1;Vce4=Vce3;
11 Vr9=3;Vr11=Vr9;
12 Vcc=(Vp+Vr14+Vbe+Vce3+Vr9)
13 Vee=-Vcc;
14 Ip=Vp/R1
15 disp(" DC power input from supply line")
16 Pi=(Vcc-Vee)*.35*Ip
17 disp(" output transistor specification")
18 Pt=.5*(Pi-Po)

```

```
19 Vce=2*Vcc
20 Ic=1.1*Ip
```

---

**Scilab code Exa 19.12** suitable resistor for output and intermediate stage

```
1 //chapter 19
2 //example 19.12
3 //page 844
4 printf("\n")
5 printf("given")
6 hFE7=20;Icbo=50*10^-6;hFE5=70;Vr9=3;Ip=869*10^-3;R15
   =1.5;R8=15*10^3;Vbe=.7;Vr11=3;Vee=20;
7 R12=.01/Icbo
8 R12=220;//use standard value
9 R13=R12;
10 Ib5=Ip/(hFE7*hFE5)
11 Ic3=2*10^-3;
12 R9=Vr9/Ic3
13 R11=R9;
14 Iq78=.1*Ip
15 Vr14=Iq78*R15
16 Vr15=Vr14;
17 Vr10=(Vr14+Vr15)+(Vr14+Vr15)/2
18 R10=Vr10/Ic3
19 Ir8=(Vr11+Vbe)/R8
20 R7=(Vee-(Vr11+Vbe))/Ir8
```

---

**Scilab code Exa 19.13** calculate required supply voltage and suitable DC voltage drop

```
1 //chapter 19
2 //example 19.13
3 //page 848
```

```

4 printf("\n")
5 printf(" given")
6 R1=20; Po=2.5; Rd=4; Vr6=1; Vr9=Vr6; Vth=1; gFS=250*10^-3;
   Vbe=.7;
7 Vp=sqrt(2*R1*Po)
8 Ip=Vp/R1
9 Vcc=(Vp+Ip*Rd)
10 vr6=Ip/gFS
11 Vr2=vr6+1
12 Vce=Vr2;
13 Vce3=1;
14 Vr2=Vcc-Vce
15 Vee=Vcc;
16 Vr3=Vee-Vbe
17 Vr7=Vr2-Vr6
18 Vr8=Vcc-(-Vee)-Vr6-Vr7-Vr9

```

---

**Scilab code Exa 19.14** determine resistor value for MOSFET amplifier

```

1 //chapter 19
2 //example 19.14
3 //page 849
4 printf("\n")
5 printf(" given")
6 R6=100*10^3; R9=R6; Vth=1; Vr7=8; Vr8=14; Vr3=11.3; Vpout
   =10; Vpin=800*10^-3;
7 I6=Vth/R6
8 R7=Vr7/I6
9 R8=Vr8/I6
10 Ic1=1*10^-4; Ic2=Ic1; Vr2=9;
11 R2=Vr2/Ic1
12 R3=Vr3/(Ic1+Ic2)
13 R5=4.7*10^3;
14 Ac1=Vpout/Vpin
15 R4=R5/(Ac1-1)

```



---

**Scilab code Exa 19.15** bootstrap capacitor terminal voltage and peak output voltage

```
1 //chapter 19
2 //example 19.15
3 //page 854
4 printf("\n")
5 printf("given")
6 Vce=1.5;Vcc=17;Vd1=.7;R8=1.5*10^3;R9=R8;R1=100;R6
   =8.2;
7 I4=(Vcc-Vd1)/(R8+R9)
8 Vc3=Vcc-(I4*R8);
9 printf(" bootstrap capacitance terminal voltage is
   %3.1fV\n",Vc3)
10 V=Vcc-Vce//V=Vp+Vr6
11 Ip=V/(R1+R6)
12 Vp=Ip*R1;
13 printf(" peak output voltage is %3.1fV\n",Vp)
14 Po=(Vp)^2/(2*R1);
15 printf(" peak output power is %dW\n",Po)
```

---

**Scilab code Exa 19.16** use BIFET to determine supply voltage and resistor value

```
1 //chapter 19
2 //example 19.16
3 //page 856
4 printf("\n")
5 printf("given")
6 R1=8;Po=6;vs=.1;hFE=1000;Vce=2;f=50*10^3;Vd1=.7;
7 Vp=sqrt(2*R1*Po)
```

```

8 Ip=Vp/R1
9 R6=.1*R1
10 R7=R6;
11 Vcc=Vp+Ip*R6+Vce
12 Ib=Ip/hFE
13 I4=2*10^-3;
14 R4=(Vcc-Vd1-Vd1)/I4
15 R8=.5*R4
16 Ac1=Vp/vs
17 R3=100*10^3;
18 R2=R3/(Ac1-1)
19 SR=(2*3.14*f*Vp)*10^-6;
20 printf(" slew rate is %3.2fV/us\n",SR)

```

---

#### Scilab code Exa 19.17 capacitor value

```

1 //chapter 19
2 //example 19.17
3 //page 858
4 printf("\n")
5 printf(" given")
6 f=50;R1=100*10^3;R2=1*10^3;R8=2.7*10^3;R9=R8;
7 C1=1/(2*3.14*f*.1*R1)
8 C2=1/(2*3.14*f*R2)
9 Xc3=.1*((R8*R9)/(R8+R9))
10 C3=1/(2*3.14*f*Xc3)
11 C4=C3

```

---

#### Scilab code Exa 19.18 MOSFET gate source voltage for complementary common source amplifier

```

1 //chapter 19
2 //example 19.18

```

```

3 //page 860
4 printf("\n")
5 printf(" given")
6 Ismin=1.8*10^-3; Ismax=3.4*10^-3; R7=820; R5=390; R6
   =18*10^3; Vi=100*10^-3; R1=10;
7 Vgsmin=Ismin*R7
8 Vgsmax=Ismax*R7
9 Acl=(R5+R6)/R5
10 Vp=Acl*Vi
11 Ip=Vp/R1;
12 printf(" peak output current is %3.3fA\n",Ip)
13 Po=(Vp*Ip)/2;
14 printf(" peak output power is %3.2fW\n",Po)

```

---

**Scilab code Exa 19.19** calculate Vgsmax and Vgsmin

```

1 //chapter 19
2 //example 19.19
3 //page 862
4 printf("\n")
5 printf(" given")
6 Vbe=.7; R2=560; R3min=0; R3max=1*10^3; Is=2*10^-3;
7 Ic2max=Vbe/(R2+R3min)
8 Ic2min=Vbe/(R2+R3max)
9 Vgsmin=(Is+Ic2min)*820
10 Vgsmax=(Is+Ic2max)*820

```

---

**Scilab code Exa 19.20** maximum peak output voltage minimum supply voltage at op amp terminal

```

1 //chapter 19
2 //example 19.20
3 //page 865

```

```

4 printf("\n")
5 printf(" given")
6 Vcc=12;R1=10;Rd=.5;gfs=2.5;R7=820;V9=1*10^3;R10=R9;
7 Vp=(Vcc*R1)/(Rd+R1)
8 Ip=Vp/R1
9 Vgs=Ip/gfs
10 Vr7=Is*R7
11 Vs=Vcc-Vr7-Vgs
12 disp(" op-amp peak output voltage is")
13 Vr9=(Vp*R9)/(R9+R10)

```

---

**Scilab code Exa 19.21** op amp minimum supply voltage and MOSFET maximum gate source voltage

```

1 //chapter 19
2 //example 19.21
3 //page 867
4 printf("\n")
5 printf(" given")
6 Vbe=.7;R2=470;R3=1*10^3;Is=.5*10^-3;R7=1.5*10^3;Vcc
   =15;
7 Ic2max=Vbe/R2
8 Ic2min=Vbe/(R2+R3)
9 Vgs=(Is+Ic2max)*R7;
10 printf(" MOSFET maximum gate source voltage is %3.1
   fV\n",Vgs)
11 Vs=Vcc-Vgs;
12 printf(" op-amp minimum supply is %3.2fV\n",Vs)

```

---

**Scilab code Exa 19.22** determine  $P_o$   $A_{cl}$   $f_1$  and  $f_2$

```

1 //chapter 19
2 //example 19.22

```

```

3 //page 868
4 printf("\n")
5 printf(" given")
6 Vcc=15;R1=15;Rd=.3;R5=2.2*10^3;R6=33*10^3;C2
   =3.9*10^-6;C4=100*10^-12;
7 disp(" power output")
8 Vp=(Vcc*R1)/(Rd+R1)
9 Ip=Vp/R1
10 Po=(Vp*Ip)/2
11 disp(" voltage gain")
12 Av=(R5+R6)/R5
13 disp(" cutoff frequency")
14 f1=1/(2*3.14*C2*R5)
15 f2=1/(2*3.14*C4*R6)

```

---

**Scilab code Exa 19.23** maximum output power voltage gain and low cut-off frequency

```

1 //chapter 19
2 //example 19.23
3 //page 871
4 printf("\n")
5 printf(" given")
6 Vcc=23;R1=8;Rf2=100*10^3;Rf1=5.6*10^3;Cf=1*10^-6;
7 Vp=Vcc-5
8 Po=(Vp)^2/(2*R1);
9 printf("maximum output power is %3.2fW\n",Po)
10 Acl=(Rf1+Rf2)/Rf1;
11 printf(" voltage gain %3.1f\n",Acl)
12 f=1/(2*3.14*Cf*Rf1);
13 printf("lower cutoff frequency is %dHz\n",f)

```

---

**Scilab code Exa 19.24** determine the load power dissipation

```

1 //chapter 19
2 //example 19.24
3 //page 875
4 printf("\n")
5 printf("given")
6 Rf=15*10^3;R1=5.6*10^3;vs=.5;Vp=2.7;
7 Acl=(2*Rf)/R1
8 Vo=Acl*vs
9 Po=(Vp)^2/(2*R1);
10 printf("load power dissipation is %3.2fW\n",Po)

```

---

**Scilab code Exa 19.25** calculate ac output power dc input power conduction angle and efficiency

```

1 //chapter 19
2 //example 19.25
3 //page 880
4 printf("\n")
5 printf("given")
6 Vcc=10;R1=1*10^3;f=3*10^6;Ip=25*10^-3;Vce=.3;
7 Vp=Vcc-Vce
8 Po=(Vp)^2/(2*R1)
9 T=1/f
10 t=(Po*T)/(Ip*Vp)
11 angle=(t/T)*360;
12 printf("conduction angle is %3.1fdegree\n",angle)
13 Idc=Po/Vp
14 Pi=Vcc*Idc;
15 printf("dc input power is %3.4fW\n",Pi)
16 n=(Po/Pi)*100//efficiency

```

---

**Scilab code Exa 19.26** for class C amplifier determine tank circuit component value and peak current

```

1 //chapter 19
2 //example 19.26
3 //page 882
4 printf("\n")
5 printf(" given")
6 f=1*10^6; Xc=120; Vce=.5; Vcc=30; Rl=1.2*10^3; O=100;
7 Cp=1/(2*3.14*f*Xc)
8 Cp=1300*10^-12; //use standard value
9 Lp=1/(((2*3.14*f)^2)*Cp)
10 Vp=Vcc-Vce
11 Po=((Vp)^2)/(2*Rl)
12 Idc=Po/Vp
13 T=1/f
14 t=(O*T)/360
15 Ip=(Idc*T)/t

```

---

**Scilab code Exa 19.27** for class C amplifier determine  $Q_l$   $Q_p$  and  $P_l$  and bandwidth and efficiency

```

1 //chapter 19
2 //example 19.27
3 //page 883
4 printf("\n")
5 printf(" given")
6 Rw=.1; f=1*10^6; Lp=19.5*10^-6; Rl=1.2*10^3; Vcc=30; Idc
   =12.3*10^-3;
7 QL=(2*3.14*f*Lp)/Rw
8 Qp=Rl/(2*3.14*f*Lp)
9 B=f/Qp
10 Il=(.707*Vp)/(2*3.14*f*Lp)
11 Pl=(Il)^2 *Rw
12 Pi=(Vcc*Idc)+Pl
13 n=(Po/Pi)*100

```

---

# Chapter 20

## Thyristors

Scilab code Exa 20.1 calculate instantaneous supply voltage

```
1 //chapter 20
2 //example 20.1
3 //page 902
4 printf("\n")
5 printf("given")
6 Vs=25;Vtm=1.7;Rl=25;Ih=5*10^-3;
7 Vspk=1.414*Vs
8 Ilpk=(Vs-Vtm)/Rl
9 disp(" for half wave rectifier sinusodial waveform")
10 Ilrms=.5*Ilpk
11 disp(" switch-off voltage")
12 es=Vtm+(Ih*Rl)
```

---

Scilab code Exa 20.2 determine suitable resistance

```
1 //chapter 20
2 //example 20.2
3 //page 905
```



```

4 printf("\n")
5 printf(" given")
6 Vs=30;Vd1=.7;Vg=.8;Ig=200*10^-6;
7 Vspk=1.414*Vs
8 disp(" at 5 degree")
9 es=Vspk*.087// sin5=.087
10 disp(" at 90 degree")
11 es=Vspk
12 Vt=Vd1+Vg
13 disp(" to trigger at es=3.7V the R2 moving contact
      is at the top")
14 es=3.7;
15 Vr1=es-Vt
16 I1=1*10^-3;
17 R1=Vr1/I1
18 R=Vt/I1//R=R2+R3
19 disp(" to trigger at es =42.4 the R2 moving contact
      at the bottom")
20 es=42.4;
21 Vr3=Vt;
22 I1=es/(R+R1)
23 R3=Vt/I1
24 R2=R-R3

```

---

**Scilab code Exa 20.3** determine SCR anode cathode voltage

```

1 //chapter 20
2 //example 20.3
3 //page 906
4 printf("\n")
5 printf(" given")
6 R1=2.2*10^3;R2=1.5*10^3;R3=120;Vt=1.5;
7 disp(" with R2 contact at center")
8 Vak=Vt*((R1+R2+R3)/(R3+.5*R2))
9 disp(" with R2 contact at zero")

```

```
10 Vak=Vt*((R1+R2+R3)/R3)
```

---

**Scilab code Exa 20.4** specify the SCR and suitable components for D1 and R1

```
1 //chapter 20
2 //example 20.4
3 //page 911
4 printf("\n")
5 printf("given")
6 Vs=5; I1max=300*10^-3; V1=7; Vg=.8;
7 Vz=V1-Vg
8 disp(" for D1, select a 1N753 with Vz=6.2")
9 Izmin=1*10^-3;
10 R1=Vg/Izmin
```

---

**Scilab code Exa 20.5** smallest conduction angle

```
1 //chapter 20
2 //example 20.5
3 //page 9
4 printf("\n")
5 printf("given")
6 R1=25*10^3; R2=2.7*10^3; C1=3*10^-6; Vg=.8; Vd1=8; Vs
   =115; f=60;
7 Vc1=Vd1+Vg
8 //assume the average charging voltage is
9 Vac=1.414*Vs
10 E=.636*Vac
11 //average charging
12 Ic=E/(R1+R2)
13 //charging time
14 t=(C1*Vc1)/Ic
```

```

15 T=1/f
16 q=(t*360)/T
17 disp(" conduction angle")
18 a=180-q

```

---

**Scilab code Exa 20.6** determine capacitor charging time

```

1 //chapter 20
2 //example 20.6
3 //page 925
4 printf("\n")
5 printf(" given")
6 Vs=10; Vf=1.7; Is=500*10^-6; Ih=1.5*10^-3; E=30; R
   =27*10^3; C=.5*10^-6;
7 R1max=(E-Vs)/Is
8 R1min=(E-Vf)/Ih
9 t=C*R*log((E-Vf)/(E-Vs));
10 printf(" capacitor charging time is %3.4fs\n",t)

```

---

**Scilab code Exa 20.7** calculate maximum  $V_{b1b2}$  be used at temperature 100C

```

1 //chapter 20
2 //example 20.7
3 //page 931
4 printf("\n")
5 printf(" given")
6 Rbb=4*10^3; Pd25=360*10^-3; D=2.4*10^-3; T2=100;
7 Pd=Pd25-D*(T2-25)
8 Vb1b1=sqrt(Rbb*Pd);
9 printf(" maximum Vb1b1 that should be used at a temp
   100 is %3.1fV\n",Vb1b1)

```

---

**Scilab code Exa 20.8** maximum and minimum triggering voltage

```
1 //chapter 20
2 //example 20.8
3 //page 931
4 printf("\n")
5 printf("given")
6 Vb1b1=25;nmax=.86;nmin=.74;Vd=.7;
7 Vpmax=Vd+(nmax*Vb1b1)
8 Vpmin=Vd+(nmin*Vb1b1)
```

---

**Scilab code Exa 20.9** calculate Re for relaxation oscillator and oscillating frequency

```
1 //chapter 20
2 //example 20.9
3 //page 933
4 printf("\n")
5 printf("given")
6 Ip=.6*10^-6;Iv=2*10^-3;Veb1=2.5;Vpmin=19.2;Vpmax
   =22.2;Vbb=25;C=1*10^-6;R=18*10^3;Vp=20;
7 Vpmin=(Vbb-Vpmax)/Ip
8 Remax=(Vbb-Veb1)/Iv
9 t=C*R*log((Vbb-Veb1)/(Vbb-Vp))
10 f=1/t
```

---

# Chapter 21

## Optoelectronic Devices

Scilab code Exa 21.1 total luminous flux

```
1 //chapter 21
2 //example 21.1
3 //page 947
4 printf("\n")
5 printf(" given")
6 r=3;Os=25;area=.25;
7 Ea=Os/(4*3.14*(r)^2)
8 Tf=Ea*area;
9 printf(" total flux is %3.3fW\n",Tf)
```

---

Scilab code Exa 21.3 suitable resistor

```
1 //chapter 21
2 //example 21.3
3 //page 951
4 printf("\n")
5 printf(" given")
6 Vcc=9;Vf=1.6;Vb=7;hFE=100;Vce=.2;Ic=10*10^-3;Vbe=.7;
```

```

7 R2=(Vcc-Vf-Vce)/Ic
8 R2=680; //use standard value
9 Ic=(Vcc-Vf-Vce)/R2
10 Ib=Ic/hFE
11 Rb=(Vb-Vbe)/Ib

```

---

**Scilab code Exa 21.4** total power supplied to digit LED

```

1 //chapter 21
2 //example 21.4
3 //page 952
4 printf("\n")
5 printf("given")
6 Vcc=5;
7 N=(3*7)+(1*2)
8 It=N*10*10^-3
9 P=It*Vcc

```

---

**Scilab code Exa 21.5** required series resistance and dark current

```

1 //chapter 21
2 //example 21.5
3 //page 957
4 printf("\n")
5 printf("given")
6 Rc=1*10^3; I=10*10^-3; E=30;
7 R1=E/I -Rc
8 R1=1.8*10^3; //use standard value
9 disp(" when dark Rc=100Kohm")
10 Rc=100*10^3;
11 I=E/(R1+Rc)

```

---

**Scilab code Exa 21.6** minimum light level when transistor is turned off

```
1 //chapter 21
2 //example 21.6
3 //page 958
4 printf("\n")
5 printf("given")
6 Vee=6;Vbe=.7;Ib=200*10^-6;Vb=.7;Vcc=6;
7 disp("when cell is dark Rc=100Kohm")
8 Rc=100*10^3;
9 Vrc=Vee+Vbe
10 Irc=Vrc/Rc
11 Ir1=Irc+Ib
12 Vr1=Vcc-Vb
13 R1=Vr1/Ir1
14 R1=18*10^3;//use standard value
15 disp(" when Q1 is off")
16 Vr1=6;Vrc=6;
17 Ir1=Vr1/R1
18 Rc=Vrc/Ir1
```

---