

Scilab Textbook Companion for  
Worked Examples In Engineering In Si Units,  
Volume Iii, Electrical Engineering  
by M. Bates<sup>1</sup>

Created by  
Yeswanth Achari  
M.Tech Power Systems (5 Year Integrated)  
Electrical Engineering  
Sastra University  
College Teacher  
Prof. Nandhini Gayathri .m  
Cross-Checked by  
KVP Pradeep

June 19, 2014

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Worked Examples In Engineering In Si Units, Volume Iii, Electrical Engineering

**Author:** M. Bates

**Publisher:** George Allen & Unwin Ltd., London.

**Edition:** 1

**Year:** 1974

**ISBN:** 0046200061

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 circuit analysis	9
2 fields	23
3 d c machines	34
4 the single phase a c series circuit	52
5 the single phase ac parallel circuit	63
6 operational methods	74
7 power and power factor	81
8 three phase circuits	94
9 the single phase transformer	103
10 synchronous and asynchronous machines	114
11 electronics	122

# List of Scilab Codes

Exa 1.1	finding currents using superposition theorem . . . . .	9
Exa 1.2	finding thevinins equivalent circuit . . . . .	10
Exa 1.3	finding current in a branch using thevinins theorem . .	11
Exa 1.4	finding a current in a branch using thevinins theorem .	12
Exa 1.5	finding current in resistor using nortons theorem . . . .	13
Exa 1.6	finding current using nortons theorem . . . . .	14
Exa 1.7	finding current using nortons theorem . . . . .	16
Exa 1.8	delta to star conversion . . . . .	17
Exa 1.9	finding the currents in wheatstone bridge using delta to star conversion . . . . .	17
Exa 1.10	star to delta conversion and finding conductances . . . .	19
Exa 1.11	finding current using star to delta transform . . . . .	20
Exa 1.12	determining the maximum power transfered . . . . .	21
Exa 2.1	finding energy stored in magnetic field . . . . .	23
Exa 2.2	finding energy stored in magnetic field . . . . .	23
Exa 2.3	finding energy stored . . . . .	24
Exa 2.4	estimation of coupling factor . . . . .	25
Exa 2.5	finding the load that can be lifted by a magnet . . . . .	26
Exa 2.6	finding area of hysteresis loop and power loss . . . . .	27
Exa 2.7	finding the speed of a machine . . . . .	28
Exa 2.8	finding maximum permissible volume of transformer core	28
Exa 2.9	comparing energies stored in different fields . . . . .	29
Exa 2.10	finding energy stored in capacitor . . . . .	30
Exa 2.11	finding potential difference and different energies . . . .	31
Exa 2.12	finding equivalent resistance . . . . .	31
Exa 2.13	finding energy dissipated in a material . . . . .	32
Exa 3.1	determination of angular speed . . . . .	34
Exa 3.2	finding output of a machine in different cases . . . . .	35

Exa 3.3	finding induced emf . . . . .	36
Exa 3.4	determination of torque produced . . . . .	36
Exa 3.5	finding power output of the motor . . . . .	37
Exa 3.6	finding required torque . . . . .	38
Exa 3.7	finding required flux per pole . . . . .	38
Exa 3.8	finding terminal voltage of a shunt generator . . . . .	39
Exa 3.9	finding power developed in the armature . . . . .	40
Exa 3.10	finding different efficiencies . . . . .	40
Exa 3.11	finding output of series generator . . . . .	41
Exa 3.12	finding different efficiencies of a series generator . . . . .	42
Exa 3.13	finding velocity of shunt motor . . . . .	43
Exa 3.14	finding total torque produced . . . . .	43
Exa 3.15	finding overall efficiency of motor . . . . .	44
Exa 3.16	finding speed of armature of dc series motor . . . . .	45
Exa 3.17	finding required current . . . . .	46
Exa 3.18	finding total and shaft torque . . . . .	47
Exa 3.19	finding speed of the motor . . . . .	47
Exa 3.20	finding speed of the motor . . . . .	48
Exa 3.21	finding value of regulator resistance . . . . .	49
Exa 3.22	calculation of speed of motor . . . . .	50
Exa 4.1	finding the current taken by the coil . . . . .	52
Exa 4.2	finding the phase angle and magnitude of current . . . . .	53
Exa 4.3	finding required components of a coil . . . . .	53
Exa 4.4	finding the resistance and inductance of a coil . . . . .	54
Exa 4.5	calculation of required capacitance . . . . .	55
Exa 4.6	determination of current and voltage . . . . .	56
Exa 4.7	determination of voltage equation . . . . .	57
Exa 4.8	finding frequency and potential differences . . . . .	58
Exa 4.9	calculation of required capacitance . . . . .	58
Exa 4.10	calculations of required frequency and currents . . . . .	59
Exa 4.11	calculation of ratio between the pd and supply voltage . . . . .	60
Exa 4.12	determination of inductance and phase angle of the coil . . . . .	61
Exa 5.1	determining the current taken from the supply . . . . .	63
Exa 5.2	finding current and phase angle . . . . .	64
Exa 5.3	calculation of current taken from the supply . . . . .	65
Exa 5.4	calculation of reactance and inductance . . . . .	66
Exa 5.5	determination of total current and phase angle in rc parallel circuit . . . . .	66

Exa 5.6	calculation of current using admittance method . . . . .	67
Exa 5.7	finding current taken from the supply by an rlc parallel circuit . . . . .	68
Exa 5.8	calculation of total current and phase angle . . . . .	69
Exa 5.9	finding resonant frequency . . . . .	71
Exa 5.10	calculation of ratio between capacitor current and supply current . . . . .	71
Exa 5.11	calculation of resistance and inductance of load . . . . .	72
Exa 6.1	calculation of current taken from the supply and its phase angle . . . . .	74
Exa 6.2	calculation of supply current and voltages and phase angle . . . . .	75
Exa 6.3	calculation of total impedance and the current . . . . .	76
Exa 6.4	calculation of current taken by a combination . . . . .	76
Exa 6.5	calculation of current and phase angle . . . . .	77
Exa 6.6	finding magnitude and phase angle of the voltage . . . . .	78
Exa 6.7	calculating the components of equivalent series circuit . . . . .	78
Exa 6.8	finding the magnitude and phase angle of current . . . . .	80
Exa 7.1	finding the average and instantaneous power . . . . .	81
Exa 7.2	finding the time elapsed before maximum power . . . . .	82
Exa 7.3	calculation of apparent and reactive powers and the inductance of coil . . . . .	83
Exa 7.4	finding the total kVA loading and overall power factor . . . . .	83
Exa 7.5	finding total active power taken from the supply . . . . .	84
Exa 7.6	calculation of total power and current taken from the supply using admittance method . . . . .	85
Exa 7.7	finding required range of frequency . . . . .	86
Exa 7.8	calculation of required capacitance . . . . .	87
Exa 7.9	calculation of required capacitance . . . . .	88
Exa 7.10	calculation of pure resistive load for maximum power . . . . .	89
Exa 7.11	calculation of components of a fully variable load . . . . .	90
Exa 7.12	calculation of power dissipated by the inductor . . . . .	90
Exa 7.13	calculation of inductance resistance and the power loss . . . . .	91
Exa 7.14	finding the power for the load and whole circuit . . . . .	92
Exa 8.1	finding the phase voltage and line current . . . . .	94
Exa 8.2	finding the line current and the phase angle . . . . .	94
Exa 8.3	calculation of total line current and total phase angle . . . . .	95
Exa 8.4	illustration for neutral current is zero . . . . .	96
Exa 8.5	calculation of phase and line currents . . . . .	97

Exa 8.6	calculation of line current and phase angle . . . . .	98
Exa 8.7	determination of line currents and phase angle in two cases . . . . .	98
Exa 8.8	determination of line and motor phase currents . . . . .	100
Exa 8.9	calculation of capacitance per phase . . . . .	100
Exa 8.10	detrmining the wattmeter readings for given conditions	101
Exa 9.1	finding the number turns on secondary . . . . .	103
Exa 9.2	finding the secondary turns and the full load primary and secondary currents . . . . .	104
Exa 9.3	finding the mutual inductance between the windings .	104
Exa 9.4	finding magnetizing current and the no load loss . . . .	105
Exa 9.5	finding the flux density in the core . . . . .	106
Exa 9.6	determination of components of parallel circuit . . . . .	106
Exa 9.7	finding number of primary and secondary turns . . . . .	107
Exa 9.8	estimation of flux density magnetizing current and core loss . . . . .	108
Exa 9.9	calculation of different efficiencies and loading for maximum efficiency . . . . .	109
Exa 9.10	calculation of all day efficiency . . . . .	109
Exa 9.11	determination of equivalent circuit . . . . .	110
Exa 9.12	finding the primary input current secondary terminal voltage and the efficiency . . . . .	111
Exa 9.13	calculation of secondary terminal voltage . . . . .	113
Exa 10.1	determination of emf between ends of a coil . . . . .	114
Exa 10.2	finding the emf between the ends of the series connected coils . . . . .	115
Exa 10.3	calculation of phase and line voltages . . . . .	115
Exa 10.4	calculation of torque produced . . . . .	116
Exa 10.5	determination torque produced . . . . .	117
Exa 10.6	finding the slip speed and the slip . . . . .	118
Exa 10.7	finding the rotor speed and the frequency of rotor components . . . . .	118
Exa 10.8	calculation of slip rotor copper loss total torque and the efficiency . . . . .	119
Exa 10.9	calculation of rotor copper loss and the input and efficiency of the motor . . . . .	120
Exa 11.1	determination of anode slope resistance the mutual conductance and the amplification factor . . . . .	122



Exa 11.2	determination of the triode parameters . . . . .	123
Exa 11.3	finding the required anode voltage . . . . .	124
Exa 11.4	determination of operating points . . . . .	124
Exa 11.5	finding the voltage amplification . . . . .	126
Exa 11.6	determination of ac voltage across the load . . . . .	126
Exa 11.7	calculation of input resistances . . . . .	127
Exa 11.8	determination of output resistances . . . . .	128
Exa 11.9	finding the parameters of the operating points . . . . .	129
Exa 11.10	calculation of current gain . . . . .	130
Exa 11.11	determination of collector emitter voltage and current gain . . . . .	131
Exa 11.12	calculation of voltage and current gains . . . . .	131
Exa 11.13	calculation of voltage gain . . . . .	132
Exa 11.14	finding voltage gain when h parameters are given . . . . .	133
Exa 11.15	calculation of required load resistance . . . . .	133

# Chapter 1

## circuit analysis

Scilab code Exa 1.1 finding currents using superposition theorem

```
1  clc
2  clear
3
4  //input
5  r1=4; //resistance between point A and B in ohms
        which is in series with 10 volts d.c. supply.
6  r2=3; //resistance between points C and D in ohms
        which is in series with a d.c. supply of 8 volts.
7  r3=5; //resistance between points F and G in ohms
8  //arms AB,CD,FG are in parallel with each other.
9  v1=10; //d.c. supply voltage in the arm AB in volts
10 v2=8; //d.c. supply voltage in the arm CD in volts
11
12 //calculations
13 //using SUPER POSITION THEOREM
14 //voltage source of 8 volts is neglected and supply
        is 10 volts d.c
15 R1=r1+((r2*r3)/(r2+r3)); // total resistance in ohms
16 bIa1=v1/R1; //current in arm AB in amperes
17 cId1=v1*(r3/(R1*(r2+r3))); //current in arm CD in
        amperes
```

```

18 dIc1= -cId1;
19 fIg1=(v1/R1)-cId1;//current in arm FG in amperes
20 //voltage source of 10 volts is neglected and supply
    is 8 volts d.c
21 R2=r2+((r1*r3)/(r1+r3));//total resistance in ohms
22 dIc2=v2/R2;//current in arm CD in amperes
23 aIb2=v2*(r3/(R2*(r3+r1)));//current in arm AB in
    amperes
24 bIa2= -aIb2;
25 fIg2=(v2/R2)-aIb2;//current in arm FG in amperes
26 I1=bIa1+bIa2;//current in 10 V source in amperes
27 I2=dIc1+dIc2;//current in 8V source in amperes
28 I3=fIg1+fIg2;//current in arm FG in amperes
29
30 //output
31 mprintf('the currents in the circuit are %3.5f A %3
    .5f A %3.5f A',I1,I2,I3)

```

---

**Scilab code Exa 1.2** finding thevinins equivalent circuit

```

1 clc
2 clear
3
4 //input
5 v1=10;// d.c. voltage source in volts present in arm
    1 in series with a 2 ohm resistor
6 v2=15;//d.c. voltage source in volts present in arm
    2 in series with a 3 ohm resistor
7 r1=2; //resistance in arm 1 in ohms
8 r2=3; // resistance in arm 2 in ohms
9 r3=1.8; //resistance between node formed by arm 1 and
    2 and point A
10 R=3; //load resistance in ohms placed in arm AB
11 // point A and B are in open condition and arm 1 and
    2 are in parallel

```

```

12
13 //calculations
14 //thevenin equivalent circuit method
15 i1=(v2-v1)/(r1+r2);// current in the parallel
    circuit in amperes
16 e=v2-(i1*r2);// open circuit e.m.f in volts i.e.
    thevenin's voltage
17 r=r3+((r1*r2)/(r1+r2));// resistance to be
    considered between AandB in ohms i.e. thevenin's
    resistance
18 I=e/(r+R);//current through the load resistance in
    amperes
19
20 //output
21 mprintf(' the thevenin equivalent generator will
    have a constant e.m.f. of %3.0f V and internal
    resistance of %3.0f ohm. \n the current in 3 ohm
    resistor is %3.0f A',e,r,I)

```

---

**Scilab code Exa 1.3** finding current in a branch using thevenin's theorem

```

1 clc
2 clear
3
4 //input
5 r1=0.2;//resistance in arm 1 in ohms which is in
    series with 10 volts d.c. supply.
6 r2=0.2;//resistance in arm 2 in ohms which is in
    series with a d.c. supply of 12 volts.
7 r3=0.4;//resistance in arm 3 in ohms which is in
    series with 15 volts d.c. supply .
8 //arms 1,2 and 3 are in parallel with each other and
    are parallel with the arm AB.
9 v1=10;//d.c. supply voltage in the arm 1 in volts
10 v2=12;//d.c. supply voltage in the arm 2 in volts

```

```

11 v3=15; //d.c. supply voltage in the arm 3 in volts
12 R1=2.28; // resistance in arm AB in ohms in one case
13 R2=5.82; // resistance in arm AB in ohms in another
14
15 //calculations
16 //thevenin equivalent circuit method
17 e=((v3/r3)+(v2/r2)+(v1/r1))/((1/r1)+(1/r2)+(1/r3));
    // thevenin's voltage in volts
18 r=1/((1/r1)+(1/r2)+(1/r3)); //thevenin's resistance
    in ohms
19 I1=e/(r+R1); // current when resistance in AB arm is
    2.28 ohms
20 I2=e/(r+R2); // current when resistance in AB arm is
    5.82 ohms
21
22 //output
23 mprintf('the equivalent generator has a constant
    voltage of %3.1f V and an internal resistance of
    %3.2f ohms \n the load currents are %3.0f A and
    %3.0f A',e,r,I1,I2)

```

---

**Scilab code Exa 1.4** finding a current in a branch using thevenins theorem

```

1  clc
2  clear
3
4  //input
5  //AB,BC,CD,DA are arms of a wheatstone bridge
6  r1=4; //resistance in arm AB in ohms
7  r2=6; //resistance in arm BC in ohms
8  r3=5; //resistance in arm CD in ohms
9  r4=3; //resistance in arm DA in ohms
10 v=4; //d.c. supply given between points A and C in
    volt
11 R=10; //resistance of the detector placed between the

```

```

        points B and D in ohms
12
13 //calculations
14 aIb=v/(r1+r2); //current in arm AB in amperes
15 aId=v/(r3+r4); //current in arm DA in amperes
16 aVb=aIb*r1; //voltage drop along arm AB in volts
17 aVd=aId*r4; //voltage drop across arm AD in volts
18 dVb=aVb-aVd; //since D is positive with respect to B
19 e=dVb; // open circuit voltage in volts
20 r0=((r1*r2)/(r1+r2))+((r3*r4)/(r3+r4)); //equivalent
    resistance in ohms when the supply neglected
21 I=e/(r0+R); //current through the 10 ohms resistance
    in amperes
22
23 //output
24 mprintf('the current through the detector will be %3
    .5f A in the direction from D to B',I)

```

---

**Scilab code Exa 1.5** finding current in resistor using nortons theorem

```

1 clc
2 clear
3
4 //input
5 v1=21; //voltage of first battery in arm 1 in volts
6 v2=16; //voltage of second battery in arm 2 in volts
7 r1=3; //internal resistance of first battery in ohms
8 r2=2; //internal resistance of second battery in ohms
9 R=6; //resistance going to be introduced in arm AB in
    ohms
10 //arms 1,2 and AB are in parallel
11 //arm AB is a short circuit path
12
13 //calculations
14 //norton's equivalent circuit method

```

```

15 Isc=(v1/r1)+(v2/r2); //current through short circuit
    path in amperes
16 aRb=(r1*r2)/(r1+r2); //equivalent resistance in ohms
17 //now 6ohm resistor is placed in arm AB
18 aIb=Isc*((aRb)/(aRb+R)); //current through 6 ohm
    resistor in amperes
19
20 //output
21 mprintf('the constants for norton equivalent
    generator are %3.1f A and %3.1f ohm \n the
    current through the 6 ohm resistor is %3.1f A',
    Isc ,aRb ,aIb)

```

---

**Scilab code Exa 1.6** finding current using nortons theorem

```

1 clc
2 clear
3
4 //input
5 v1=5; //voltage of battery in arm 1 in volts
6 v2=10; //voltage of battery in arm 2 in volts
7 v3=20; //voltage of battery in arm 3 in volts
8 r1=3; //internal resistance of battery in arm 1 in
    ohms
9 r2=8; //internal resistance of battery in arm 2 in
    ohms
10 r3=24; //internal resistance of battery in arm 3 in
    ohms
11 //arms 1,2,3 and AB are in parallel with each other
    and AB are in open condition
12 r4=6; //resistance between node formed by arms 1,2
    and 3 and point A in ohms
13 R0=7; //load resistance to be connected in arm AB in
    ohms
14 //calculations

```

```

15 //norton's equivalent method
16 //batteries are neglected. so, only internal
    resistances remain in the arms
17 R=1/((1/r1)+(1/r2)+(1/r3)); //equivalent resistance
    in ohms
18 aRb=R+r4; // total resistance when looked into the
    circuit from arm AB in ohm
19 //applying superposition principle to determine the
    short circuit current
20 //battery in arm 1 alone is considered
21 R1=r1+(1/((1/r2)+(1/r3)+(1/r4))); //effective
    resistance in ohms
22 I1=v1/R1; //current in amperes
23 pd=I1*r1; //potential drop across the parallel
    combination in volts
24 aIb1=pd/r4; //current in amperes
25 //battery in the arm 2 alone is considered
26 R2=r2+(1/((1/r1)+(1/r3)+(1/r4))); // effective
    resistance in ohms
27 I2=v2/R2; //current in amperes
28 V1=I2/((1/r1)+(1/r3)+(1/r4)); //voltage in volts
29 aIb2=V1/r4; //current in amperes
30 //battery in the arm 3 alone is considered
31 R3=r3+(1/((1/r1)+(1/r2)+(1/r4))); //effective
    resistance in ohms
32 I3=v3/R3; //current in amperes
33 V2=I3/((1/r1)+(1/r2)+(1/r4)); //voltage in volts
34 aIb3=V2/r4; //current in amperes
35 Isc=aIb1+aIb2+aIb3; //short circuit current in
    amperes
36 I=Isc*(aRb/(aRb+R0)); //current through load resistor
    in amperes
37
38 //output
39 mprintf('Nortons equivalent generator will produce a
    constant current of %3.3f A and has a shunt
    resistance of %3.0f ohms \n the current through
    the external resistor will be %3.1f A',Isc,r2,I)

```



---

Scilab code Exa 1.7 finding current using nortons theorem

```
1  clc
2  clear
3
4  //input
5  //AB,BC,CD,DA are arms of a wheatstone bridge
6  r1=4; //resistance in arm AB in ohms
7  r2=6; //resistance in arm BC in ohms
8  r3=5; //resistance in arm CD in ohms
9  r4=3; //resistance in arm DA in ohms
10 v=4; //d.c. supply given between points A and C in
    volt
11 R0=10; //resistance of the detector placed between
    the points B and D in ohms
12 //a detector is placed between the point B and D
13
14 //calculations
15 // noerton's equivalent circuit method
16 R1=((r1*r2)/(r1+r2))+((r3*r4)/(r3+r4)); // equivalent
    resistance assuming short circuit between poin A
    and C in ohms
17 R2=((r1*r4)/(r1+r4))+((r2*r3)/(r2+r3)); //equivalent
    resistance assuming short circuit between points
    B and D in ohms
18 I1=v/R2; // total current in amperes
19 aIb=v*(r4/(R2*(r4+r1))); //current in arm AB in
    amperes
20 aVDb=v*aIb; //voltage drop in arm AB
21 bVDc=v-aVDb; //voltage drop in arm DC
22 bIc=bVDc/r2; //current in arm BC in amperes
23 dIb=bIc-aIb; //current in arm DB in amperes
24 Isc=dIb; //short circuit current in amperes
25 I=Isc*(R1/(R1+R0)); //current through the detector in
```

```

        amperes
26
27 //output
28 mprintf('nortons equivalent generator produces %3.5
        f A and has a shunt resistance of %3.3f ohms \n
        the current through the detector will be %3.3f A'
        ,Isc,R1,I)

```

---

**Scilab code Exa 1.8** delta to star conversion

```

1  clc
2  clear
3
4  //input
5  //arma AB,BC and CA forms delta connection
6  r1=2;//resistance in arm AB in ohms
7  r2=3;//resistance in arm BC in ohms
8  r3=5;//resistance in arm CA in ohms
9
10 //calculations
11 //conversion of given delta into star connection
12 //let N be the star point
13 R1=(r1*r2)/(r1+r2+r3);//resistance in arm AN in ohms
14 R2=(r2*r3)/(r1+r2+r3);//resistance in arm BN in ohms
15 R3=(r1*r3)/(r1+r2+r3);//resistance in arm CN in ohms
16
17 //output
18 mprintf('the respective star connected resistances
        are %3.1f ohm,%3.1f ohm and %3.1f ohm',R1,R2,R3 )

```

---

**Scilab code Exa 1.9** finding the currents in wheatstone bridge using delta to star conversion

```

1  clc
2  clear
3
4  //input
5  //AB,BC,CD,DA are arms of a wheatstone bridge
6  r1=5; //resistance in arm AB in ohms
7  r2=20; //resistance in arm BC in ohms
8  r3=15; //resistance in arm CD in ohms
9  r4=4; //resistance in arm DA in ohms
10 v=4; //d.c. supply given between points A and C in
    volt
11 r0=0.5; // internal resistances pf the d.c. supply in
    ohms
12 r5=15; //resistance in arm BD in ohms
13
14 //calculations
15 //BCD is replaced by equivalent star connection
16 //assume N as star piont after conversion
17 bRn=(r2*r3)/(r3+r2+r5); //resistance in arm BN in
    ohms
18 cRn=(r2*r5)/(r3+r2+r5); //resistance in arm CN in
    ohms
19 dRn=(r5*r3)/(r3+r2+r5); //resistance in arm DN in
    ohms
20 R=r0+cRn+(((r1+bRn)*(r4+dRn))/(r1+bRn+r4+dRn)); //
    total resistance in ohms after conversion
21 I=v/R; //totalcurrent supply in amperes
22 I1=(v/R)*((r4+dRn)/(r1+bRn+r4+dRn)); //current
    between points A and B in amperes
23 I2=I-I1; //current between points A and D in amperes
24 V1=I1*r1; //voltage drop across r1 in volts
25 V2=I2*r4; //voltage drop across r4 in volts
26 V3=V2-V1; //voltage drop across r5 in volts and B is
    positive to D
27 I3=V3/r5; //current between points B and D in amperes
28 I4=I1-I3; //current between points B and C in amperes
29 I5=I2+I3; //current between points D and C in amperes
30

```

```

31 //output
32 mprintf('the currents in each part of the circuit
    are \n It= %3.3f A \n aIb= %3.3f A \n aId= %3.3f
    A \n bId= %3.3f A \n bIc= %3.3f A \n dIc= %3.3f A
    ',I,I1,I2,I3,I4,I5)

```

---

**Scilab code Exa 1.10** star to delta conversion and finding conductances

```

1  clc
2  clear
3
4  //input
5  //AN,BN,CN are connected in star fashion where N is
    the neutral point
6  r1=5;//resistance in arm AN in ohms
7  r2=20;//resistance in arm BN in ohms
8  r3=10;//resistance in arm CN in ohms
9
10 //calculations
11 //star to delta conversion
12 Y1=1/r1;//conductance of arm AN in seimens
13 Y2=1/r2;//conductance of arm BN in seimens
14 Y3=1/r3;//conductance of arm CN in seimens
15 R1=1/((Y1*Y2)/(Y1+Y2+Y3));//resistance of arm AB in
    ohms
16 R2=1/((Y2*Y3)/(Y1+Y2+Y3));//resistance of arm BC in
    ohms
17 R3=1/((Y1*Y3)/(Y1+Y2+Y3));//resistance of arm CA in
    ohms
18
19 //ouput
20 mprintf('the equivalent resistances values for delta
    circuit are %3.0f ohms, %3.0f ohms and %3.1f
    ohms ',R1,R2,R3)

```

---

Scilab code Exa 1.11 finding current using star to delta transform

```
1  clc
2  clear
3
4  //input
5  //AB,BC,CD,DA forms an unbalanced wheatstone's
   bridge
6  r1=2; //resistance in arm AB in ohms
7  r2=5; //resistance in arm BC in ohms
8  r3=6; //resistance in arm CD in ohms
9  r4=2; //resistance in arm DA in ohms
10 r5=10; //resistance of detector placed between the
    points B and D
11 v=4; //battery supplying d.c. voltage in volts which
    is placed between points A and C
12 r0=0.2; // internal resistance of the battery in ohms
13
14 //calculations
15 //AB,BC and BD are considered to be in star
    connection with B as star point
16 Y1=1/r1; //conductance of r1 in seimens
17 Y2=1/r2; //conductance of r2 in seimens
18 Y3=1/r5; //conductance of r5 in seimens
19 //after delta conversion
20 R1=1/((Y1*Y2)/(Y1+Y2+Y3)); //resistance between
    points A and B in ohms
21 R2=1/((Y2*Y3)/(Y1+Y2+Y3)); //resistance between
    points C and D in ohms
22 R3=1/((Y1*Y3)/(Y1+Y2+Y3)); //resistance between
    points D and A in ohms
23 Rad=(r4*R3)/(r4+R3); //effective resistance of arm AD
    in ohms
24 Rdc=(r3*R2)/(r3+R2); //effective resistance of arm DC
```

```

        in ohms
25 Radc=(Rad+Rdc); //effective resistance if arms AD and
        DC in ohms
26 R=r0+((R1*Radc)/(R1+Radc)); // total resistance of
        hte circuit in ohms
27 I=v/R; //total current in the circuit in amperes
28 I1=I*(R1/(R1+Radc)); //current in arm AD in amperes
29 I2=I-I1; //current in arm AB in amperes
30 V1=I1*r4; //voltage across arm AD in volts
31 V2=I2*r1; //voltage across arm AB in volts
32 V3=V1-V2; //voltage across arm BD in volts and B is
        positive to D
33 I3=V3/r5; //current in arm BD in amperes
34
35 //output
36 mprintf('the current in the detector is %3.3f A',I3)

```

---

**Scilab code Exa 1.12** determining the maximum power transfered

```

1 clc
2 clear
3
4 //input
5 // a battery consists of 10 cells connected in series
6 v=1.5; //e.m.f. of each cell in volts
7 r=0.2; // internal resistance of each cell in ohms
8 n=10; //number of cells in the battery
9
10 //calculations
11 //for maximum power load resistance=internal
        resistance
12 R=n*r; //total internal resistance of hte battery in
        ohms
13 Rl=R; //load resistance in ohms
14 e=n*v; //total e.m.f. of battery in volts

```

```
15 I=e/(R+Rl); //current from battery in amperes
16 P=(I^2)*R; //heating loss in the battery in watts
17 V=e-(I*R); //terminal voltage in volts
18
19 //output
20 fprintf('The maximum value of power which the
    battery may transfer is %3.1f W and an equal
    quantity of power is dissipated in the battery. \
    n under these conditions the terminal p.d. is %3
    .1f V',P,V)
```

---

# Chapter 2

## fields

Scilab code Exa 2.1 finding energy stored in magnetic field

```
1  clc
2  clear
3  //input
4  r=5; //resistance of the coil in ohms
5  v=100; // d.c supply voltage to the coil in volts
6  l=100*(10^-3); // inductance of the coil in henry
7
8  //calculations
9  i=v/r; // value of the current in amperes
10 e=(1*(i^2))/2; // energy stored in the circuit in
    joules
11
12 //output
13 mprintf('the value of current is %3.2f amperes \n
    the energy stored in the magnetic field is %3.2f
    joules ',i,e)
```

---

Scilab code Exa 2.2 finding energy stored in magnetic field



```

1  clc
2  clear
3
4  //input
5  l=0.5; //length of an air cored cylinder in meters
6  d1=0.05; // diameter of an air cored cylinder in
    meters
7  n=400; //number of turns of copper wire wound around
    the cylinder
8  d2=0.001; //diameter of the copper wire wound in
    meters
9  v=14; //dc supply voltage in volts
10 r=1.71*(10^-8); // resistivity of copper in ohm
    meteres
11 u0=1.257*(10^-6); // permeabilty of free space
12 ur=1; //relative permeability
13
14 //calculations
15 L=(u0*ur*(n^2)*(%pi*(d1^2)))/(4*l); //inductance of
    the coil in henry
16 R=(r*n*(d1+d2)*%pi*4)/(%pi*(d2^2)); // resistance of
    the field in ohm
17 i=v/R; //current in the field in amperes
18 e=(L*(i^2))/2; // energy stored in the field in
    joules
19
20 //output
21 mprintf('the inductanec of the coil is %3.10f H \n
    the resistance of the field is %3.10f ohm \n the
    energy stored in the field is %3.10f J',L,R,e)

```

---

Scilab code Exa 2.3 finding energy stored

```

1  clc
2  clear

```

```

3
4 //input
5 mmf=1800; // magneto motive force in amperes
6 l1=0.8; // length of iron in meters
7 l2=0.002; //length of air gap in meters
8 a=9*(10^-4); // area of the air gap in square meters
9 ui=2000; // relative permeability of iron
10 ua=1; // relative permeability of air
11 u0=1.257*(10^-6); // absolute permeability of free
    space
12
13 //calculations
14 b=(mmf*u0)/((l1/ui)+(l2/ua)); // flux density in
    tesla
15 e=(b^2)/(2*u0*ui); //energy stored in joules/cubic
    meter
16 v=l1*a; // volume of the iron in cubic meters
17 E=v*e; // total energy stored in the iron in joules
18
19 // output
20 mprintf('flux density is %3.10f T \n energy stored
    is %3.10f J/cubic m \n volume of the iron is %3
    .10f cubic m \n total energy stored in the iron
    is %3.10f J',b,e,v,E)

```

---

**Scilab code Exa 2.4** estimation of coupling factor

```

1 clc
2 clear
3
4 //input
5 l1=0.4; //inductance of the first coil in henry
    which is in series with the second
6 l2=0.1; //inductance of the second coil in henry
7 i=5; // current through both the coils in amperes

```

```

8 e=2.25; // energy stored in magnetic field in joules
9
10 //calculations
11 L=(2*e)/(i^2); //total inductance in henry
12 M=(l1+l2-L)/2; // mutual inductance between the
    coils in henry
13 K=M/((l1*l2)^(0.5)); // coupling factor between the
    coils
14
15 //output
16 mprintf('total inductance is %3.10f H \n mutual
    inductance between the coils is %3.10f H \n the
    coupling factor is %3.10f',L,M,K)

```

---

**Scilab code Exa 2.5** finding the load that can be lifted by a magnet

```

1 clc
2 clear
3
4 //input
5 l1=0.5; //length of iron bar in meters which is bent
    into horse shoe lifting magnet
6 a=1*(10^-3); // cross sectional area in cubic meters
7 n=500; // number of turns wound
8 i=4; //current flowing in amperes
9 ui=1100; // relative permeability of iron
10 ua=1; //relative permeability of air gap
11 l2=0.001; //length of the air gap
12 k=1.1; //leakage coefficient
13 u0=1.257*(10^-6); //absolute permeability
14
15 //calculations
16 b=(n*i*u0)/(((k*l1)/ui)+((2*a)/ua)); //flux density
    in tesla
17 P=((b^2)*2*l2)/(2*u0*ua); //increase in stored

```

```

        energy due to movement of the load by magnet in
        joules
18 m=P/9.81; //mass lifted in kilo grams
19
20 //output
21 mprintf('fulx density is %3.10f T \n increase in
        stored energy is %3.2f J \n mass that can be
        lifted by the magnet is %3.2f Kg',b,P,m)

```

---

**Scilab code Exa 2.6** finding area of hysteresis loop and power loss

```

1  clc
2  clear
3
4  //input
5  h=500; //hysteresis losses of the rotor of a d.c.
        machine in joule/cubic meter/cycle
6  n=50; //number of cycles of magnetisation
7  d=0.0075; //density of the material in mg/cubic
        meter
8  H=10; //magnetising force in ampere/meter per mm
        when hysteresis loop is plotted on a graph
9  B=0.02; //flux density in tesla per mm when
        hysteresis loop is plotted on a graph
10
11 //calculations
12 e=B*H; //energy represented by 1square mm in joules
13 a=h/e; //area of loop in square mm
14 p=h*n; //power loss in watts per cubic meter
15 P=(p*(10^-6))/d; //power loss in watts per Kg
16
17 //output
18 mprintf('the area of hysteresis loop is %3.10f sq.mm
        \n the power loss is %3.10f W/Kg',a,P)

```

---

**Scilab code Exa 2.7** finding the speed of a machine

```
1  clc
2  clear
3
4  //input
5  p=6; //number of poles of a d.c. machine
6  v=0.01; // volume of iron in cubic meters
7  d=0.0079; //density of the iron in mg/square meter
8  hi=4; // hysteresis loss of iron in W/Kg
9  hl=619; //loss given by hysteresis loop in joule/
    cubic meter/cycle
10
11 //calculations
12 h=hi*d*v*(10^6); // total hysteresis losses in watts
13 f=h/(hl*v); // frequency in cycles/second
14 n=(f*60)/3; //rotor undergoes 3 cycles of
    magnetisation in each revolution and speed in rev
    /minute
15 a=(f*2*%pi)/3; // angular velocity if rotor in
    radian per second
16
17 //output
18 mprintf('the speed of the machine will be %3.10f rev
    /min or %3.10f rad/s',n,a)
```

---

**Scilab code Exa 2.8** finding maximum permissible volume of transformer core

```
1  clc
2  clear
3
```

```

4 //input
5 a=2500; //area of hysteresis loop in square
  millimeter
6 H=16; //magnetising force in ampere/meter per mm when
  hysteresis loop is plotted on a graph
7 B=0.02; //flux density in tesla per mm when
  hysteresis loop is plotted on a graph
8 hloss=24; //desired hysteresis loss
9 n=50; //cycles of magnetisation
10
11 //calculations
12 e=B*H; //energy represented by square millimeter
13 l=a*e; //loss/cubic meter/cycle
14 Vmax=hloss/(l*n); //maximum volume core in cubic
  meter
15
16 //output
17 mprintf('the permissible volume of the transformer
  core is %3.10f cubicmeter',Vmax)

```

---

**Scilab code Exa 2.9** comparing energies stored in different fields

```

1 clc
2 clear
3
4 //input
5 l=0.002; //length in meters
6 a=0.01; //area in square meters
7 pd=250000; //potential gradient in V/m
8 h=250000; //magnetic force in A/m
9 e0=8.85*(10^-12); //absolute permittivity
10 er=1; //relative permittivity of air
11 u0=1.257*(10^-6); //absolute permeability
12 ur=1; //relative permeability of air
13

```

```

14 //calculations
15 D=e0*er*pd;//electric flux density in C/sq.m
16 Ee=((D^2)*l*a)/(2*e0*er);//energy stored in electric
    field in joules
17 B=h*u0*ur;//magnetic flux density
18 Em=((B^2)*l*a)/(2*u0*ur);//energy stored in magnetic
    field
19 k=Ee/Em;//ratio of energy in electric field to
    magnetic field
20
21 //output
22 mprintf('the ratio of energies in electric to
    magnetic field is %3.10f :1',k)

```

---

**Scilab code Exa 2.10** finding energy stored in capacitor

```

1  clc
2  clear
3
4  //input
5  c1=2*(10^-6);// capacitance of first capacitor in
    farad which is connected in series with second
6  c2=6*(10^-6);// capacitance of second capacitor in
    farad which is connected in series with first
7  v=240;//d.c. voltage supply in volts
8
9  //calculations
10 ct=(c1*c2)/(c1+c2);//effective capacitance in farad
11 q=ct*v;//total charge in coulombs
12 e1=(q^2)/(2*c1);// energy stored in first capacitor
    in joules
13 e2=(q^2)/(2*c2);// energy stored in second capacitor
    in joules
14
15 //output

```

```
16 mprintf('the energy stored in first capacitor is %3
    .10f J \n the energy stored in second capacitor
    is %3.10f J',e1,e2)
```

---

**Scilab code Exa 2.11** finding potential difference and different energies

```
1 clc
2 clear
3
4 //input
5 c1=0.000005; //capacitance of first capacitor in
    farad
6 c2=0.000003; //capacitance of second capacitor in
    farad
7 v=200; //potential difference to which capacitor is
    charged in volts
8
9 //calculations
10 q1=c1*v; // charge given to first capacitor
11 ct=c1+c2; // total capacitance in farad
12 pd=q1/ct; // final potential difference across
    combination in volts
13 Eo=(c1*v*v)/2; //original energy in system in joules
14 Ef=(pd*pd*(c1+c2))/2; //final energy in system in
    joules
15
16 //output
17 mprintf('the initial energy stored in the capacitor
    is %3.10f J and final energy stored in the
    combination is %3.10f J',Eo,Ef)
```

---

**Scilab code Exa 2.12** finding equivalent resistance



```

1  clc
2  clear
3
4  //input
5  c=0.000002; // capacitance of a capacitor in farad
6  theta=0.12; // loss angle in radians
7  v=230; // a.c. voltage supply in volts
8  f=50; //supply frequency in hertz
9
10 //calculations
11 ic=v*2*%pi*f*c; // capacitor current in amperes
12 ir=ic*tan(theta); // current through shunt resistance
    in amperes
13 r=v/ir; // shunt resistance in ohm
14
15 //output
16 mprintf('the value of the equivalent shunt
    resistance is %3.10f ohm',r)

```

---

**Scilab code Exa 2.13** finding energy dissipated in a material

```

1  clc
2  clear
3
4  //input
5  s=1; //side of square piece of wood which is clamped
    between two mettalic plates in meters
6  t=0.005; //thickness of square piece of wood which is
    clamped between two mettalic plates in meters
7  pd=20; //applied potential difference in volts
8  f=25000000; //supply frequency in hertz
9  er=4; //relative permittivity of the wood
10 theta=0.2 // loss angle in radians
11 T=10; //time in minutes
12 e0=8.85*(10^-12); //absolute permittivity

```

```
13
14 //calculations
15 P=(pd*pd*2*%pi*f*e0*er*s*s*theta)/t;// power loss in
    watts
16 E=P*60*T;// energy dissipated in ten minutes in
    joules
17
18 //output
19 mprintf('the energy dissipated in the wood in 10 min
    is %3.10f J',E)
```

---

# Chapter 3

## d c machines

Scilab code Exa 3.1 determination of angular speed

```
1  clc
2  clear
3
4  //input
5  n1=420; //number of conductors in armature of a d.c.
    machine
6  phi=0.024; //flux produced by each pole in weber
7  e=250; //desired e.m.f in volts
8  n2=4; //number of poles of the d.c. machine
9
10 //calculations
11 N=n1/2; //number of conductors per path and there are
    two parallel paths
12 //e1= e.m.f induced per conductor=(4*0.024*w)/(2*%pi
    ) where w is the required angular velocity in rad
    /s
13 w=e/((n1*(48*10^-3))/(2*%pi)); //required angular
    velocity in rad/s
14
15 //output
16 printf('the armature of hte machine must have an
```

angular velocity of %3.0f rad/s',w)

---

**Scilab code Exa 3.2** finding output of a machine in different cases

```
1  clc
2  clear
3
4  //input
5  n1=200; //number of armature conductors
6  i=5; //current capability of each conductor in
    amperes
7  n2=4; //number of poles in the machine
8  e=1; //e.m.f. induced in each pole in volts
9
10 //calculations
11 //for a wave winding
12 n3=2; //number of parallel paths
13 n4=n1/n3; //number of conductors per path
14 e1=e*n4; //e.m.f of the machine in volts
15 i1=n3*i; //current capacity in amperes
16 op1=i1*e1; //output of the machine in watts
17 //for a lap winding
18 n5=n2; //number of parallel paths=number of poles
19 n6=n1/n5; //number of conductors per path
20 e2=n6*e; //e.m.f. of the machine in volts
21 i2=n5*i; //current capacity in amperes
22 op2=i2*e2; //output of the machine in watts
23
24 //output
25 mprintf('the output of the machine if armature is
    wave wound is %3.3f W and lap wound is %3.3f W',
    op1, op2)
```

---

### Scilab code Exa 3.3 finding induced emf

```
1  clc
2  clear
3
4  //input
5  n1=480; //number of conductors in the armature
6  n2=6; //number of poles in the machine
7  w=100; //angular velocity in rad/s
8  phi=0.03; // flux per pole in weber
9
10 //calculations
11 phi1=n2*phi; //flux cut by each conductor in weber
12 e1=(phi1*w)/(2*%pi); //e.m.f. induced/conductor in
    volts
13 n3=n2; //number of parallel paths
14 n4=n1/n3; //number of conductors per path
15 e2=e1*n4; //e.m.f. per path in volts
16
17 //output
18 mprintf('the e.m.f. induced in the armature is %3.0f
    V', e2)
```

---

### Scilab code Exa 3.4 determination of torque produced

```
1  clc
2  clear
3
4  //input
5  n1=16; //number of coils under the influence of the
    poles at any instant
6  phi=0.03; //flux produced by each coil in weber
7  a1=(200*300*(10^-6)); //area of a pole in square
    meter
8  n2=8; //number of turns in each coil
```

```

 9 d=0.25; //diameter of the armature in meters
10 i=12; // current in the armature conductors in
    amperes
11 l=0.3; //length of the pole in meters
12
13 //calculations
14 b=phi/a1; //flux density under poles in tesla
15 f1=b*i*l; //force acting on 1 conductor in newton
16 f2=n2*f1; //force per coil side in newton
17 t1=f2*(d/2); //toque per coil side in newton meter
18 t2=t1*2; //total torque per coil in newton meter
19 T=n1*t2; //total torque on armature in newton meter
20
21 //output
22 mprintf('the total exerted on the armature is %3.1f
    Nm',T)

```

---

**Scilab code Exa 3.5** finding power output of the motor

```

1  clc
2  clear
3
4  //input
5  d=0.25; //diameter of a pulley placed on the end of
    hte shaft of a d.c. motor in meter
6  m=60; //mass attached by a rope to the pulley in kg
7  w=50; //angular velocity of the pulley in rad/sec
8
9  //calculations
10 f=m*9.81; //force acting on the pulley in newton
    meter
11 W=f*%pi*d; //work done in one revolution
12 v=(d/2)*w;
13 p=(f*v)/1000; //power in kilo watts
14

```

```
15 //output
16 mprintf('the output of the motor is %3.2f kW',p)
```

---

**Scilab code Exa 3.6** finding required torque

```
1 clc
2 clear
3
4 //input
5 e=235; //e.m.f generated by an armature of a d.c.
   machine in volts
6 v=100; //velocity of armature of a d.c. machine in
   rad/s
7 i=16; //current in amperes
8
9 //calculations
10 p=e*i; //power of armature in watts
11 t=p/v; //required torque in newton meter
12
13 //output
14 mprintf('required torque is %3.1f Nm',t)
```

---

**Scilab code Exa 3.7** finding required flux per pole

```
1 clc
2 clear
3
4 //input
5 n1=4; //number of poles in a d.c. machine
6 n2=290; //number of conductors in the armature which
   are connected in lap winding
7 i=20; //armature current in amperes
8 t=50; //torque produced in newton meter
```

```

9
10 //calculations
11 phi=((t*(2*%pi))/(n2*i))*1000;//required flux per
    pole in milliweber
12
13 //output
14 mprintf('the required flux per pole is %3.1f mWb',
    phi)

```

---

**Scilab code Exa 3.8** finding terminal voltage of a shunt generator

```

1  clc
2  clear
3
4  //input
5  ra=0.05;//armature resistance of a d.c. shunt
    generator in ohms
6  rf=120;//feild resistance of a d.c. shunt generator
    in ohms
7  li=98;//load current in amperes
8  lv=240;//load voltage in volts
9  ia2=60;//reduced current in armature in amperes
10
11 //calculations
12 //generated e.m.f. remains constant
13 if=lv/rf;//feild current in amperes
14 ia1=li+if;//armature current in amperes
15 e=lv+(ia1*ra);//generated e.m.f. in volts
16 V=e-(ia2*ra);//final terminal voltage in amperes
17
18 //output
19 mprintf('for an armature of 60A the terminal p.d.
    will be %3.0f',V)

```

---



**Scilab code Exa 3.9** finding power developed in the armature

```
1  clc
2  clear
3
4  //input
5  ra=0.1; //armature resistance of a shunt generator in
      ohms
6  rf=250; //feild resistance of a shunt generator in
      ohms
7  p=7250; //load supplied by the shunt generator in
      watts
8  v=250; //voltage of shunt generator in volts
9
10 //calculations
11 il=p/v; //load current in amperes
12 if=v/rf; //feild current in amperes
13 ia=il+if; //armature current in amperes
14 e=v+(ia*ra); //generated e.m.f. in volts
15 P=(e*ia)/1000; //armature power in kW
16
17 //output
18 mprintf('the power developed in the armature will be
      %3.2 f kW',P)
```

---

**Scilab code Exa 3.10** finding different efficiencies

```
1  clc
2  clear
3
4  //input
5  v=230; //voltage of a shunt generator in volts
```

```

6 ra=0.2; //armature resistance of the shunt generator
  in ohms
7 rf=115; //feild resistance of the shunt generator in
  ohms
8 n=0.85; //overall effeciency in per units
9 il=37; //load current in amperes
10
11 //calculations
12 inp=(v*il)/n; //input in watts
13 inp1=inp/1000; //input power in kilo watts
14 fi=v/rf; //feild current in amperes
15 ai=il+fi; //armature current in amperes
16 e=v+(ai*ra); //generated e.m.f. in volts
17 ap=e*ai; //armature power in watts
18 ml=inp-ap; //mechanical losses in watts
19 nm=ap/inp; //mechanical effeciency in per units
20 Nm=nm*100;
21 ne=(v*il)/ap; //electrical effeciency in per units
22 Ne=ne*100;
23
24 //output
25 mprintf('the input power will be %3.0f kW and the
  mechanical losses are %3.0f W \n the mechanical
  and electrical effeciencies are %3.1f per cent and
  %3.1f per cent ',inp1,ml,Nm,Ne)

```

---

**Scilab code Exa 3.11** finding output of series generator

```

1 clc
2 clear
3
4 //input
5 ra=0.08; //armature resistance of a d.c. series
  generator in ohms
6 rf=0.1; //feild resistance of a d.c. series generator

```

```

        in ohms
7  il=50; //load current in amperes
8  e=250; //e.m.f. generated in volts
9
10 //calculations
11 R=ra+rf; //total resistance of machine in ohms
12 pd=e-(il*R); //terminal p.d. in volts
13 p=pd*il; //power output in watts
14 P=p/1000; //power output in kilo watts
15
16 //output
17 mprintf('the power output of the generator is %3.2f
        kW',P)

```

---

**Scilab code Exa 3.12** finding different efficiencies of a series generator

```

1  clc
2  clear
3
4  //input
5  v=240; //voltage of d.c. series generator in volts
6  ra=0.1; //armature resistance of d.c. series
        generator in ohms
7  rf=0.15; //field resistance of d.c. series generator
        in ohms
8  n=0.87; //overall efficiency in per units
9  lp=7200; //load power in watts
10
11 //calculations
12 il=lp/v; //load current in amperes
13 R=ra+rf; //total resistance in ohms
14 e=v+(il*R); //generated e.m.f. in volts
15 ap=e*il; //armature power in watts
16 ne=(lp/ap); //electrical efficiency in per units
17 ne1=ne*100;

```

```

18 nm=(n/ne)*100; //mechanical effeciency
19
20 //output
21 mprintf('the electrical and mechanical effeciencies
    are %3.0f per cent and %3.1f per cent',ne1,nm)

```

---

**Scilab code Exa 3.13** finding velocity of shunt motor

```

1  clc
2  clear
3
4  //input
5  v=250; //voltage of shunt motor in volts
6  ra=0.2; //armature resistance of shunt motor in ohms
7  rf=250; //feild resistance of shunt motor in ohms
8  w=75; //velocity of shunt motor in rad/sec
9  i1=21; //current taken by the motor in amperes
10 i2=60; //changed current in amperes
11
12 //calculations
13 fi=v/rf; //feild current in amperes
14 ai=i1-fi; //armature current in amperes
15 e1=v-(ai*ra); //induced e.m.f. in volts
16 e2=v-(i2*ra); //induced e.m.f. for changed current in
    volts
17 W=w*(e2/e1); //new speed in rad/sec
18
19 //ouput
20 mprintf('with an armature current of 60A the motor
    speed will be %3.1f rad/s ',W)

```

---

**Scilab code Exa 3.14** finding total torque produced

```

1  clc
2  clear
3
4  //input
5  v=240; //voltage of a d.c. shunt motor in volts
6  ra=0.4; //armature resistance of d.c. shunt motor in
      ohms
7  rf=120; //armature resistance of d.c. shunt motor in
      ohms
8  is=22; //supply current in amperes
9  w=600; //angular velocity of motor in rev/min
10 il=30; //load current in amperes
11
12 //calculations
13 //armature reaction is neglected
14 W=(w*(2*%pi))/60; //angular velocity in rad/s
15 fi=v/rf; //feild current in amperes
16 ai=is-fi; //armature current in amperes
17 e=v-(ai*ra); //e.m.f. in volts
18 t1=(e*ai)/W; //torque when current is 20A in newton
      meter
19 aI=il-fi; //changed armature current in amperes
20 t2=t1*(aI/is); //torque when current is 30A in newton
      meter
21
22 //output
23 mprintf('with a supply current of 30A the motor
      produces a total torque of %3.1f Nm',t2)

```

---

**Scilab code Exa 3.15** finding overall efficiency of motor

```

1  clc
2  clear
3
4  //input

```

```

5 v=250; //voltage of a d.c. shunt motor in volts
6 ra=0.4; //armature resistance of a d.c. shunt motor
  in ohms
7 rf=250; //field resistance of a d.c. shunt motor in
  ohms
8 t=80; //total torque in newton meter
9 w=75; //velocity in rad/s
10 ml=0.1; //mechanical losses in per units
11
12 //calculations
13 ap=t*w; //armature power in watts
14 //(ia^2)-625ia+15000=0 will be the equation obtained
  from the e.m.f. equation
15 //(-ia+25)(ia-600)=0 is simplified equation
16 ai=25; //armature current in amperes as 600A armature
  current is inadmissable
17 fi=v/rf; //field current in amperes
18 inpI=ai+fi; //input current in amperes
19 inpP=v*inpI; //power input in watts
20 outP=0.9*t*w; //output power in watts and 0.9 is used
  after considering the 10% mechanical losses
21 n=outP/inpP; //overall effeciency in p.u.
22
23 //output
24 mprintf('for the loading condition the overall
  efficiency is %3.3f p.u.',n )

```

---

**Scilab code Exa 3.16** finding speed of armature of dc series motor

```

1 clc
2 clear
3
4 //input
5 v=240; //voltage of a d.c. series motor in volts
6 rm=0.2; //resistance of the motor in ohms

```

```

7 w=80; // velocity of motor in rad/s
8 i1=20; //current in amperes
9 i2=30; //changed current in the armature in amperes
10
11 //calculations
12 //it is assumed that flux/pole is proportional to
    the field current
13 e1=v-(i1*rm); //e.m.f. induced in volts when the
    current is 20 A
14 e2=v-(i2*rm); //e.m.f. induced in volts when the
    current is 30 A
15 W=(e2/e1)*(i1/i2)*w; //final velocity in rad/s
16
17 //output
18 mprintf('with the increased current the motor will
    run with a velocity of %3.2f rad/s',W)

```

---

**Scilab code Exa 3.17** finding required current

```

1 clc
2 clear
3
4 //input
5 //for a series motor
6 i1=40; //current in amperes
7 t1=110; //torque in newton meter
8 t2=75; //torque in newton meter
9
10 //calculations
11 //it assumed that up to a current of 50A the
    magnetizing curve for the motor is linear
12 i2=((t2/t1)*(i1^2))^0.5; //required torque in newton
    meter
13
14 //ouput

```

```
15 mprintf('the current to produce a total torque of 75
    Nm is %3.0f A',i2)
```

---

**Scilab code Exa 3.18** finding total and shaft torque

```
1 clc
2 clear
3
4 //input
5 n1=4; //number of poles in a aeries motor
6 v=240; //voltage of the series motor in volts
7 n2=348; //number of conductors in the armature which
    is wave connected
8 r=0.8; //resistance in ohms
9 i=45; //current taken by the motor in amperes
10 phi=0.028; //flux/pole in weber
11 outP=8200; //output power in watts
12
13 //calculations
14 t=(phi*n2*2*i)/(2*pi); //since wave winding 2 is
    taken and the torque in newton meter
15 e=v-(i*r); //e.m.f. induced in volts
16 ap=e*i; //armature power in watts
17 w=(ap/t); //angular velocity in rad/s
18 st=outP/w; //shaft torque in newton meter
19
20 //output
21 mprintf('the total torque and the shaft torque
    produced by the motor are %3.0f Nm and %3.0f Nm',
    t,st)
```

---

**Scilab code Exa 3.19** finding speed of the motor



```

1  clc
2  clear
3
4  //input
5  v1=240; //voltage of a d.c. shunt motor in volts
6  ra=1; //armature current in ohms of a d.c. shunt
    motor
7  rf=240; //field current in ohms of a d.c. shunt motor
8  ifl=20; //full load current in amperes
9  w=200; //speed in rad/s
10 v2=200; //reduced voltage in volts
11
12 //calculations
13 //flux/pole is assumed to be proportional to the
    field current
14 //for a 240V supply
15 E1=v1-(ifl*ra); //induced e.m.f. in volts
16 i=ifl*(v1/v2); //new current in amperes
17 E2=v2-(i*ra); //induced e.m.f. for new current in
    volts
18 W=w*(E2/E1)*(i/ifl); //new speed in rad/s
19
20 //output
21 mprintf('with the reduced voltage the motor will run
    at %3.0f rad/s',W)

```

---

**Scilab code Exa 3.20** finding speed of the motor

```

1  clc
2  clear
3
4  //input
5  rm=0.5; //resistance of a series motor in ohms
6  w=100; //velocity in rad/sec
7  i=25; //current taken by the motor in amperes

```

```

8 v=250; //supply voltage in volts
9 r=2.5; //resistance connected in series with armature
    in ohms
10
11 //calculations
12 //armature current remains constant
13 E1=v-(i*rm); //e.m.f. induced under normal conditions
14 R=r+rm; //total resistance of circuit in ohms
15 E2=v-(i*R); //new induced e.m.f. in volts
16 W=(E2/E1)*w; //new speed for the same current in rad/
    s
17
18 //output
19 mprintf('with resistor in series with the armature
    the motor will run at %3.1f rad/s',W)

```

---

**Scilab code Exa 3.21** finding value of regulator resistance

```

1 clc
2 clear
3
4 //input
5 v=240; //voltage of a shunt motor in volts
6 ra=0.4; //armature resistance in ohms of the shunt
    motor
7 rf=160; //field resistance in ohms of the shunt motor
8 ia=30; //armature current in amperes
9 w=1250; //speed in rev/min
10
11 //calculations
12 //it is assumed that flux is proportoinal to the
    field current
13 E1=v-(ia*ra); //induced e.m.f. in volts
14 fi=v/rf; //field current in amperes
15 k=E1/(fi*w);

```

```

16 //if=k*(v/r2) where r2 is the resistance to be added
17 //ia1=(3*r2)/16 and E2=v-(ra*ia1)
18 //(E2/E1)=((24-0.4ia1)/228) and (E2/E1)=(192/r2)
19 //we get an equation for r2 as (r2^2)-(3200*r2)
    +583680=0
20 r21=((3200+(((3200*3200)-(4*1*583680))^0.5))/2);//
    one of two solution for r2 in ohms
21 r22=((3200-(((3200*3200)-(4*1*583680))^0.5))/2);//
    one of two solution for r2 in ohms
22 R=r22-rf;//final resistance to be added in ohms and
    r22 is considered as the other value is too large
    and impractical
23
24 //ouput
25 mprintf('resistance to be added is %3.0f ohms',R)

```

---

**Scilab code Exa 3.22** calculation of speed of motor

```

1 clc
2 clear
3
4 //input
5 v=250;//voltage of the series motor in volts
6 ra=0.25;//armature resistance of the series motor in
    ohms
7 rf=0.2;//field resistance of the series motor in
    ohms
8 i=60;//current taken by the motor in amperes
9 w=90;//speed of the motor in rad/s
10 r0=0.4;//resistance added in parallel with the field
    in ohms
11
12 //calculations
13 //it is assumed that flux is propertoinal to the
    field current and load is constant

```

```
14 E1=v-(i*(rf+ra));//motor e.m.f. in volts
15 I=i/((r0/(r0+rf))^0.5);//current in amperes
16 E2=v-(I*ra)-((I*rf)*(r0/(r0+rf)));//new motor e.m.f.
    in volts
17 W=(E2/E1)*(i/I)*((r0+rf)/r0)*w;//increased speed of
    the motor in rad/s
18
19 //output
20 mprintf('with resistor connected the speed of the
    motor will increase to %3.0f rad/s',W)
```

---

# Chapter 4

## the single phase a c series circuit

Scilab code Exa 4.1 finding the current taken by the coil

```
1  clc
2  clear
3
4  //input
5  r=10; //resistance of a coil in ohms
6  l=0.08; //inductance of the coil in henry
7  v=250; //a.c. supply voltage in volts
8  f=50; //supply frequency in hertz
9
10 //calculations
11 Xl=2*pi*f*l; //reactance of the coil in ohms
12 z=((r^2)+(Xl^2))^0.5; //impedance of the circuit
13 I=v/z; //current in amperes
14 phi=acos(r/z); // phase angle in radians
15 PHI=(phi*180)/%pi; //phase angle in degrees
16
17 //output
18 mprintf('the coil will take a current of %3.2f A
           lagging by %3.0f degree on the voltage ',I,PHI)
```

---

**Scilab code Exa 4.2** finding the phase angle and magnitude of current

```
1  clc
2  clear
3
4  //input
5  r=12; //resistance connected in series with a coil in
      ohms
6  rc=4; //resistance of the coil in ohms
7  l=0.02; //inductance of the coil in henry
8  v=230; //a.c. supply voltage in volts
9  f=50; //frequency of the supply in hertz
10
11 //calculations
12 R=r+rc; //total resistance of circuit in ohms
13 xl=2*pi*f*l; //reactance of the coil in ohms
14 z=((R^2)+(xl^2))^0.5; //impedance of the circuit in
      ohms
15 i=v/z; //current in amperes
16 phi=(acos(r/z))*(180/(2*pi)); //angle of phase
      difference in degrees
17 vr=i*r; //voltage drop across resistor in volts
18 vc=i*(((rc^2)+(xl^2))^0.5); //voltage drop across
      coil in volts
19
20 //output
21 mprintf('the current taken from the supply is %3.1f
      A lagging by %3.1f degree.\n the voltage drops
      across the resistor and the coil are %3.0f V and
      %3.0f V', i, phi, vr, vc)
```

---

**Scilab code Exa 4.3** finding required components of a coil

```

1  clc
2  clear
3
4  //input
5  r1=10; //resistance of first coil in ohms
6  l1=0.05; //inductance of first coil in henry
7  v1=150; //limit of voltage drop across of first coil
   in volts
8  v=240; //supply a.c. voltage in volts
9  f=50; //frequency of supply in hertz
10 a=40; //angle by which current lags the combined
    circuit after adding another coil to the first
    coil in series in degrees
11
12 //calculations
13 R=2*%pi*f*l1; //reactance of first coil in ohms
14 z=((r1^2)+(R^2))^0.5; //impedance of the first coil
    in ohms
15 i=v1/z; //maximum safe current in amperes
16 Z=v/i; //total impedance in ohms
17 Rt=Z*cos(a*(%pi/180)); //total resistance in ohms
18 r2=Rt-r1; //resistance of the second coil in ohms
19 xt=Z*sin(a*(%pi/180)); //total reactance in ohms
20 x2=xt-R; //reactance of the second coil in ohms
21 l2=x2/(2*%pi*f); //inductance of the second coil in
    henry
22 L=l2*1000; //inductance of the second coil in
    millihenry
23
24 //output
25 mprintf('the second coil must have a resistance of
    %3.1f ohm and an inductance of %3.1f mH',r2,L)

```

---

**Scilab code Exa 4.4** finding the resistance and inductance of a coil

```

1  clc
2  clear
3
4  //input
5  //given voltage and current equations are v=354*(
    sin(314*t)) volts , i=14.1*(sin((314*t)-0.5))
    amperes
6  vmax=354; //maximum voltage in volts
7  imax=14.1; //maximum current in amperes
8  phi=0.5; //phase angle in radians
9  f=50; //supply frequency in hertz
10
11 //calculations
12 V=0.707*vmax; //voltmeter reading placed in the
    circuit
13 I=0.707*imax; //ammeter reading placed in circuit
14 z=V/I; //impedance of the coil in ohms
15 R=z*cos(phi); //resistance in ohms
16 xl=z*sin(phi); //reactance of coil in ohms
17 l=(xl/(2*pi*f))*1000; //inductance of the coil in
    millihenry
18
19 //output
20 mprintf('the coil has a resistance of %3.0f ohm and
    an inductance of %3.0f mH \n the instrument
    readings will be %3.0f V and %3.0f A',R,l,V,I)

```

---

**Scilab code Exa 4.5** calculation of required capacitance

```

1  clc
2  clear
3
4  //input
5  i=0.5; //current taken by filament of an electric
    lamp in amperes

```



```

6 v1=110; //supply voltage in volts
7 v2=240; //changed supply in volts
8 f=50; //supply frequency in hertz
9
10 //calculations
11 z=v2/i; //impedance in ohms
12 r=v1/i; //resistance of the lamp
13 xc=((z^2)-(r^2))^0.5; //reactance of the capacitor
    added to the lamp in series in ohms
14 c=(10^6)/(2*pi*f*xc); //capacitance in microfarad
15 //this can also be solved using phasor diagram
16
17 //output
18 mprintf('the required value of the capacitance is %3
    .1f microfarad ',c)

```

---

**Scilab code Exa 4.6** determination of current and voltage

```

1 clc
2 clear
3
4 //input
5 r=10; //resistance of an inductor in ohms
6 l=0.08; //inductance in henry
7 c=200*(10^-6); //capacitance of the capacitor
    connected in series to the inductor in farad
8 v=240; //supply voltage in volts
9 f=50; //supply frequency in hertz
10
11 //calculations
12 xl=2*pi*f*l; //reactance of the inductor in ohms
13 xc=1/(2*pi*f*c); //reactance of the capacitor in
    ohms
14 R=xl-xc; //total reactance of the circuit in ohms
15 z=((r^2)+(R^2))^0.5; //impedance of the circuit in

```

```

    ohms
16 I=v/z;//current in ohms
17 phi=(180/%pi)*acos(r/z);//phase angle in degrees
18 pd=I*(((r^2)+(xl^2))^0.5);//p.d. across inductor in
    volts
19
20 //output
21 mprintf('the current taken from the supply is %3.1f
    A lagging on the voltage by %3.1f degrees and the
    voltage drop across the inductor is %3.0f V',I,
    phi,pd)

```

---

**Scilab code Exa 4.7** determination of voltage equation

```

1 clc
2 clear
3
4 //input
5 r0=15;//resistance added in series with an inductor
    and capacitor in ohms
6 r1=5;//resistance of the inductor in ohms
7 l=0.03;//inductance of the inductor in henry
8 c=250*(10^-6);//capacitance in farad
9 //i=14.5sin(314t) is the given current expression
10 w=314;//from the current expression
11 im=14.5;//from the current expression
12
13 //calculations
14 xl=w*l;//reactance of coil in ohms
15 xc=1/(w*c);//reactance of capacitor in ohms
16 r=r0+r1;//total resistance in ohms
17 R=xc-xl;//total reactance in ohms
18 z=(((r^2)+(R^2))^0.5);//impedance in ohms
19 vm=im*z;//maximum voltage in volts
20 phi=acos(r/z);//phase angle in radians

```

```

21
22 //output
23 mprintf('the supply voltage will be V= %3.0f sin((%3
    .0f t)- %3.3f)',vm,w,phi)

```

---

**Scilab code Exa 4.8** finding frequency and potential differences

```

1  clc
2  clear
3
4  //input
5  r=12;//resistance of the coil in ohms
6  l=0.08;//inductance of the coil in henry
7  c=150*(10^-6);//capacitance of capacitor connected
    in series in farad
8  v=240;//supply voltage in volts
9  i=20;//desired current in amperes
10
11 //calculations
12 z=v/i;//impedance in ohms
13 w=((1/(l*c))^0.5);//angular frequency in rad/sec
14 f=w/(2*pi);//frequency required in hertz
15 xl=w*l;//inductive reactance in ohms
16 pdc=xl*i;//p.d. across the capacitor in volts
17 pd=i*(((r^2)+(xl^2))^0.5);//p.d. across the coil
18
19 //ouput
20 mprintf('the frequency at which the current will be
    20A is %3.0f Hz and at this frequency the p.d.s
    across the coil and across the capacitor will be
    %3.0f V and %3.0f V respectively ',f,pd,pdc)

```

---

**Scilab code Exa 4.9** calculation of required capacitance

```

1  clc
2  clear
3
4  //input
5  f=100000; //frequency in hertz
6  r=5; //resistance of the coil in ohms
7  l=0.0016; //inductance of the coil in henry
8
9  //calculations
10 x1=2*%pi*f*l; //inductive reactance of the coil in
    ohms
11 c=(10^12)/(2*%pi*f*x1); //capacitance required for
    resonance in pico farad
12
13 //output
14 mprintf('the series capacitor must be turned to %3.0
    f pF to produce resonance at 100kHz',c)

```

---

**Scilab code Exa 4.10** calculations of required frequency and currents

```

1  clc
2  clear
3
4  //input
5  r=1; //resistance of the coil in ohms
6  l1=10*(10^-6); //inductance of coil in henry
7  c1=1*(10^-6); //capacitor which is connected in
    series with the coil in farad
8  l2=20*(10^-6); //changed inductance in henry
9  c2=0.5*(10^-6); //changed capacitance in farad
10 v=10; //supply volts in volts
11
12 //calculations
13 f0=1/(2*%pi*((l1*c1)^0.5)); //resonant frequency in
    hertz

```

```

14 F0=0.9*f0; //required resonant frequency in hertz
15 x11=2*%pi*F0*l1; //inductive reactance in ohms
16 xc1=1/(2*%pi*F0*c1); //capacitive reactance in ohms
17 X=xc1-x11; //effective reactance in ohms
18 z=((r^2)+(X^2))^0.5; //impedance in ohms
19 i=v/z; //current in ohms
20 x12=2*%pi*f0*l2; //new inductive reactance in ohms
21 xc2=x12; // at resonance
22 x13=0.9*x12; //inductive reactacne at lower frequency
    in ohms
23 xc3=xc2/0.9; //inductive capacitance at lower
    frequency in ohms
24 X1=xc3-x13; //effective reatance in ohms
25 I=v/X1; //current in amperes
26
27 //output
28 mprintf('the value of the current at 0.9*resonant
    frequency is %3.2f A and at lower frequency with
    change in values of inductance and capacitance is
    %3.0f A',i,I)

```

---

**Scilab code Exa 4.11** calculation of ratio between the pd and supply voltage

```

1 clc
2 clear
3
4 //input
5 c=200*(10^-12); //capacitance of a capacitor which is
    connected in series with a coil in farad
6 q=80; //Q factor
7 v=0.250; //supply voltage in volts
8 f=500000; //supply frequency in hertz
9
10 //calculations

```

```

11 pd=q*v;//p.d. across the capacitor in volts
12 ic=pd*2*%pi*f*c;//capacitor current in amperes
13 r=v/ic;//resistance of the coil in ohms
14 xl=q*r;//reactance of coil in ohms
15 l=(xl/(2*%pi*f))*(10^6);//inductance of the coil in
    ohms
16
17 //output
18 mprintf('the resistance and the inductance of the
    coil are %3.1f ohms and %3.0f microH respectively
    ',r,l)

```

---

**Scilab code Exa 4.12** determination of inductance and phase angle of the coil

```

1  clc
2  clear
3
4  //input
5  q=100;//Q factor of a coil
6  r=25;//resistance of the coil in ohms
7  //a capacitor is connected in sries with the coil
8  f=400000;//resonant frequency in hertz
9  i=0.125;//current at resonance in amperes
10
11 //calculations
12 p=i*i*r;//power dissipated in coil in watts
13 e=p/f;//energy dissipated per cycle in joules
14 im=(2*i)^0.5;//assumin sinusoidal current in maperes
15 l=(((q*p)/(2*%pi*f))*(2/(im^2)))*1000;//inductance
    in millihenry
16 phi=acos(1/q);//phase angle in radians
17 c=(10^12)/(2*%pi*f*r*q);//capacitance in picofarad
18
19 //output

```

```
20 mprintf('the inductance and the phase angle of the  
    coil are %3.1f mH and %3.2f radians and the  
    required capacitance for resonance is %3.0f pF',l  
    ,phi,c)
```

---

# Chapter 5

## the single phase ac parallel circuit

Scilab code Exa 5.1 determining the current taken from the supply

```
1  clc
2  clear
3
4  //input
5  r=20; //pure resistance connected in parallel with a
      pure inductance in ohms
6  l=0.08; //pure inductance in henry
7  v=240; //supply voltage in volts
8  f=50; //supply frequency in hertz
9
10 //calculations
11 i1=v/r; //current in resistive branch in amperes
12 i2=v/(2*%pi*f*l); //current in inductive branch in
      amperes
13 it=((i1*i1)+(i2*i2))^0.5; //total current in amperes
14 phi=(180/%pi)*acos(i1/it); //phase angle in degrees
15
16 //output
17 mprintf('the total current is %3.1f A lagging by %3
```



```
.1f degree',it,phi)
```

---

**Scilab code Exa 5.2** finding current and phase angle

```
1  clc
2  clear
3
4  //input
5  r=25;//resistance of a non inductive resistor in
      ohms
6  rl=10;//resistance of the inductor
7  l=0.06;//inductance of the inductor in henry
8  //non inductive resistor and resistive inductor are
      connected in parallel
9  v=230;//supply voltage in volts
10 f=50;//supply frequency in hertz
11
12 //calculations
13 i1=v/r;//current in resistive branch in amperes
14 i2=v/(((rl*rl)+((2*pi*f*l)^2))^0.5);//current is
      reactive-resistive branch in amperes
15 phi=acos(rl/(2*pi*f*l));//phase angle in radians
16 it=i1+(i2*cos(phi));//total in-phase component in
      amperes
17 iq=i2*sin(phi);//total quadrature component in
      amperes
18 I=(((it*it)+(iq*iq))^0.5);//resultant current in
      amperes
19 phit=(180/pi)*acos(it/I);//phase angle in degrees
20
21 //output
22 mprintf('the total current is %3.1f A lagging by %3
      .0f degrees',I,phit)
```

---

**Scilab code Exa 5.3** calculation of current taken from the supply

```
1  clc
2  clear
3
4  //input
5  //coils a and b in connected in parallel
6  v=240;//supply voltage in volts
7  f=50;//supply frequency in hertz
8  ra=10;//resistance of coil a in ohms
9  xla=25;//inductive reactance of coil a in ohms
10 rb=20;//resistance of coil b in ohms
11 xlb=12;//inductive reactance of coil b in ohms
12
13 //calculations
14 z1=((ra^2)+(xla^2))^0.5;//impedance of coil a in
    ohms
15 i1=v/z1;//current in coil a in amperes
16 cos1=ra/z1;//cosine of phase angle1
17 sin1=xla/z1;//sine of phase angle1
18 z2=((rb^2)+(xlb^2))^0.5;//impedance of coil b in
    ohms
19 i2=v/z2;//current in coil b in amperes
20 cos2=rb/z2;//cosine of phase angle2
21 sin2=xlb/z2;//sine of phase angle2
22 ii=(i1*cos1)+(i2*cos2);//total in phase component in
    amperes
23 iq=(i1*sin1)+(i2*sin2);//total quadrature component
    in amperes
24 I=((ii^2)+(iq^2))^0.5;//total current in amperes
25
26 //output
27 mprintf('the total current is %3.1f A',I)
```

---

**Scilab code Exa 5.4** calculation of reactance and inductance

```
1  clc
2  clear
3
4  //input
5  i=10; //total current taken by two-branch parallel
      circuit in amperes
6  a=37*(%pi/180); //phase angle by which current lags
      by on the voltage in degrees
7  v=100; //voltage supply in volts
8  f=50; //frequency of supply in hertz
9  g1=0.03; //conductance of first branch in siemens
10 b1=0.04; //inductive susceptance of first branch in
      siemens
11
12 //calculations
13 gt=(i*cos(a))/v; //total conductance in siemens
14 bt=(i*sin(a))/v; //total susceptance in siemens
15 g2=gt-g1; //conductance of second branch in siemens
16 b2=bt-b1; //susceptance of second branch in siemens
17 y2=((g2^2)+(b2^2))^0.5; //admittance of second branch
18 r2=g2/(y2^2); //resistance of second branch in ohms
19 x2=b2/(y2^2); //reactance of second coil in ohms
20 l2=(1000*x2)/(2*%pi*f); //inductance of second coil
      in millihenry
21
22 //output
23 mprintf('the resistance and inductance of second
      branch are %3.2f ohm and %3.2f mH',r2,l2)
```

---

**Scilab code Exa 5.5** determination of total current and phase angle in rc parallel circuit

```
1  clc
2  clear
3
4  //input
5  r=30; //resistance of a resistance in ohms which is
        connected in parallel with a bank of capacitors
6  c=80*(10^-6); //capacitance of bank of capacitors in
        farad
7  v=240; //supply voltage in volts
8  f=50; //supply frequency in hertz
9
10 //calculations
11 i1=v/r; //current in phase with the voltage in
        amperes
12 i2=v*2*%pi*f*c;; //current leading on voltage by 90
        degrees in amperes
13 i=((i1^2)+(i2^2))^0.5; //total current in amperes
14 phi=(180/%pi)*acos(i1/i); //phase angle in degrees
15
16 //output
17 mprintf('the total current is %3.0f A leading on the
        voltage by %3.0f degrees ',i,phi)
```

---

**Scilab code Exa 5.6** calculation of current using admittance method

```
1  clc
2  clear
3
4  //input
5  v=415; //supply voltage in volts
6  f=50; //supply frequency in hertz
7  r1=50; //resistance in branch 1 in ohms
```

```

8 r2=30; //resistance in branch 2 in ohms
9 c=50*(10^-6); //capacitance in branch 2 in farad
10 //branch 1 and 2 are in parallel
11
12 //calculations
13 g1=1/r1; //conductance of branch 1 in siemens
14 xc=1/(2*pi*f*c); //reactance of branch 2 in siemens
15 z=((r2^2)+(xc^2))^0.5; //impedance in ohms
16 g2=r2/(z^2); //conductance of branch 2 in siemens
17 b2=xc/(z^2); //susceptance of branch 2 in siemens
18 gt=g1+g2; //total conductance in siemens
19 bt=0+b2; //total susceptance in siemens
20 yt=((gt^2)+(bt^2))^0.5; //total admittance in mho
21 it=v*yt; //total current in amperes
22 R=gt/(yt^2); //resistance of the series equivalent
    circuit in ohms
23 Xc=bt/(yt^2); //capacitive reactance of the series
    circuit in ohms
24
25 //output
26 mprintf('the current taken from the supply will be
    %3.1f A and the resistance and capacitive
    reactance of the equivalent series circuit are %3
    .0fohm and %3.0fohms respectively ',it,R,Xc)

```

---

**Scilab code Exa 5.7** finding current taken from the supply by an rlc parallel circuit

```

1 clc
2 clear
3
4 //input
5 r=32; //resistance in branch 1 in ohms
6 l=0.08; //inductance in branch 2 in henry
7 c=200*(10^-6); //capacitance in branch 3 in farad

```

```

8 //braches 1,2 and 3 are in parallel
9 v=240;//supply voltage in volts
10 f=50;//supply frequency in hertz
11
12 //calculations
13 g1=1/r;//conductance of branch 1 in siemens
14 b2=-1/(2*%pi*f*1);//susceptance of branch 2 in
    siemens
15 b3=2*%pi*f*c;//susceptance of branch 3 in siemens
16 bt=b2+b3;//total susceptance in siemens
17 yt=((g1^2)+(bt^2))^0.5;//total admittance in mho
18 it=v*yt;//total current in amperes
19 phi=(180/%pi)*acos(g1/yt);//phase angle in degrees
20
21 //output
22 mprintf('the total current will be %3.2f A leading
    on the voltage by %3.1f degrees',it,phi)

```

---

**Scilab code Exa 5.8** calculation of total current and phase angle

```

1 clc
2 clear
3
4 //input
5 r1=100;//resistance in branch 1 in ohms
6 r2=10;//resistance in branch 2 in ohms
7 l2=0.07;//inductance in branch 2 in henry
8 r3=10;//resistance in branch 3 in ohms
9 c3=100*(10^-6);//capacitance in branch 3 in farad
10 //branches 1,2 and 3 are in parallel with each other
11 v=250;//supply voltage in volts
12 f=50;//supply frequency in hertz
13
14 //calculations
15 it=v/r1;//total current in branch 1 in amperes

```

```

16 ii1=it;//since resistive branch
17 iq1=0;//since resistive branch
18 z2=((r2^2)+((2*%pi*f*12)^2))^0.5;//impedance of
    branch 2 in ohms
19 i2=v/z2;//current in branch 2 in amperes
20 cos2=r2/z2;//cosine of phase angle
21 phi2=(180/%pi)*acos(cos2);//phase angle in degree
22 ii2=i2*cos2;//in phase component of branch2 in
    amperes
23 iq2=-i2*sin(acos(cos2));//quadrature component of
    branch 2 in amperes
24 z3=((r3^2)+((1/(2*%pi*f*c3))^2))^0.5;//impedance of
    branch 3 in ohms
25 i3=v/z3;//current in branch 3 in amperes
26 cos3=r3/z3;//cosine of the phase angle
27 phi3=(180/%pi)*acos(cos3);//phase angle in degrees
28 ii3=i3*cos3;//in phase component of branch 3 in
    amperes
29 iq3=i3*sin(acos(cos2));//quadrature component of
    branch 3 in amperes
30 ii=ii1+ii2+ii3;//total in phase component in amperes
31 iq=iq1+iq2+iq3;//total quadrature component in
    amperes
32 it=((ii^2)+(iq^2))^0.5;//total current in amperes
33 cost=ii/it;//cosine of total phase angle
34 phit=(180/%pi)*acos(cost);//phase angle in degrees
35 zs=v/it;//equivalent series impedance in ohms
36 rs=zs*cost;//equivalent series resistance in ohms
37 xs=zs*sin(acos(cost));//equivalent series reactance
    in ohms
38 l=(xs*1000)/(2*%pi*f);//inductance in millihenry
39
40 //output
41 mprintf('the total current is %3.2f A lagging by %3
    .0f degrees and the equivalent series circuit
    would be a resistive inductive circuit of %3.1f
    ohms and %3.0f mH',it,phit,rs,l )

```

---

**Scilab code Exa 5.9** finding resonant frequency

```
1  clc
2  clear
3
4  //input
5  r=10; //resistance of an inductor in ohms
6  l=0.08; //inductance of an inductor in henry
7  c=150*(10^-6); //capacitance by which the inductor is
   shunted in farad
8  v=240; //supply voltage in volts
9
10 //calculation
11 z1=1/c; //impedance in henry
12 f0=(1/(2*pi))*(((z1-(r^2))/(l^2))^0.5); //resonant
   frequency in hertz
13 z=((r^2)+((2*pi*f0*l)^2))^0.5; //impedance in ohms
14 it=(v*r)/(z^2); //total current in amperes
15
16 //output
17 mprintf('the circuit will be in current resonance at
   a frequency of %3.1f Hz and at this frequency
   the supply current will be %3.1f A',f0,it)
```

---

**Scilab code Exa 5.10** calculation of ratio between capacitor current and supply current

```
1  clc
2  clear
3
4  //input
5  r=2; //resistance of an inductor in ohms
```



```

6 l=0.07; //inductance of an inductor in henry which is
   in resonance with a capacitor
7 f=60; //resonant frequency in hertz
8
9 //calculations
10 tanphi=(2*%pi*f*l)/r; //ratio between capacitor
   current and supply current
11
12 //output
13 mprintf('the ratio of capacitor current to supply
   current is %3.1f : 1',tanphi)

```

---

**Scilab code Exa 5.11** calculation of resistance and inductance of load

```

1 clc
2 clear
3
4 //input
5 c=4*(10^-6); //capacitance of a capacitor by which a
   resistive-inductive load is shunted in farad
6 v=2; //supply voltage in volts
7 f=5000; //supply frequency in hertz
8 q=10; //Q factor of the circuit
9
10 //calculations
11 vwc=2*2*%pi*f*c; //capacitor current in amperes
12 it=vwc/q; //total current in amperes
13 i1=((vwc^2)+(it^2))^0.5; //load current in amperes
14 z1=v/i1; //load impedance in ohms
15 r1=z1*(it/i1); //resistance of load in ohms
16 x1=q*r1; //reactance of load in ohms
17 l=(x1*(10^6))/(2*%pi*f); //load inductance in
   microhenry
18
19 //output

```

```
20 mprintf('the load has a resistance of %3.3f ohms and  
    an inductance of %3.0f microhenry ',r1,l)
```

---

# Chapter 6

## operational methods

**Scilab code Exa 6.1** calculation of current taken from the supply and its phase angle

```
1  clc
2  clear
3
4  //input
5  z=7.5+(%i*10); //impedance connected to a supply in
    ohms
6  r=7.5; //resistance from impedance in ohms
7  x=10; //reactance from impedance in ohms
8  v=200; //supply voltage in volts
9
10 //calculations
11 i=v/z; //current taken from supply in amperes
12 I=(((real(i))^2)+((imag(i))^2))^0.5; //current
    magnitude in amperes
13 phi=(180/%pi)*atan(-x/r); //phase angle in degrees
14 PHI=-phi; //lag
15
16 //output
17 mprintf('the supply current is %3.0f A lagging on
    the voltage by %3.0f',I,PHI)
```

---

**Scilab code Exa 6.2** calculation of supply current and voltages and phase angle

```
1  clc
2  clear
3
4  //input
5  z1=5+(%i*5); //impedance 1 in ohms
6  z2=10-(%i*15); //impedance 2 in ohms
7  //impedances 1 and 2 are in series
8  v=240; //supply voltage in volts
9
10 //calculations
11 zt=z1+z2; //total impedance in ohms
12 i=v/zt; //current taken in amperes
13 v1=z1*i; //voltage 1 in volts
14 V1=(((real(v1))^2)+((imag(v1))^2))^0.5; //voltage
    magnitude in volts
15 phi1=(180/%pi)*atan((imag(v1))/(real(v1))); //phase
    angle 1 in degrees
16 v2=i*z2; //voltage 2 in volts
17 V2=(((real(v2))^2)+((imag(v2))^2))^0.5; //voltage
    magnitude in volts
18 phi2=(180/%pi)*atan(-(imag(v2))/(real(v2))); //phase
    angle 2 in degrees
19 I=(((real(i))^2)+((imag(i))^2))^0.5; //current
    magnitude in amperes
20
21 //output
22 mprintf('the supply current is%3.1f A and the two
    voltages are %3.0f V and %3.0f V leading by %3.1f
    degrees and lagging by %3.1f degrees
    respectively ',I,V1,V2,phi1,phi2)
```

---

**Scilab code Exa 6.3** calculation of total impedance and the current

```
1  clc
2  clear
3
4  //input
5  z1=12+(%pi*16); //impedance 1 in ohms
6  z2=10-(%i*10); //impedance 2 in ohms
7  //impedances 1 and 2 are in parallel
8  v=240; //supply voltage in volts
9
10 //calculations
11 zt=(z1*z2)/(z1+z2); //total impedance in ohms
12 Z=((real(zt))^2+((imag(zt))^2))^0.5; //current
    magnitude in amperes
13 i=v/zt; //supply current in amperes
14 I=((real(i))^2+((imag(i))^2))^0.5; //current
    magnitude in amperes
15
16 //output
17 mprintf('the magnitude of total impedance is %3.1f
    ohms and of the supply current is %3.1f A',Z,I)
```

---

**Scilab code Exa 6.4** caculation of current taken by a combination

```
1  clc
2  clear
3
4  //input
5  r1=10; //resistance of branch 1 in ohms
6  l1=0.08; //inductance of branch 1 in henry
7  r2=20; //resistance of branch 2 in ohms
```

```

8 c2=150*(10^-6); //capacitance of branch 2 in farad
9 //branch 1 and 2 are in parallel
10 v=240; //supply voltage in volts
11 f=50; //supply frequency in hertz
12
13 //calculations
14 x1=2*%pi*f*l1; //reactance of branch 1 in ohms
15 z1=r1+(%i*x1); //impedance of branch 1 in ohms
16 y1=1/z1; //admittance of branch 1 in mho
17 x2=1/(2*%pi*f*c2); //reactane of branch 2 in ohms
18 z2=r2-(%i*x2); //impedance of branch 2
19 y2=1/z2; //admittance of branch 2 in mho
20 yt=y1+y2; //total admittance in mho
21 it=v*yt; //supply current in amperes
22 I=((real(it))^2)+((imag(it))^2))^0.5; //current
    magnitude in amperes
23
24 //output
25 mprintf('the current taken from the supply is %3.2f
    A',I)

```

---

**Scilab code Exa 6.5** calculation of current and phase angle

```

1 clc
2 clear
3
4 //input
5 r=20; //resistance of an inductor in ohms
6 x=15; //reactance of an inductor in ohms
7 v=250; //supply voltage in volts
8
9 //calculations
10 z=((r^2)+(x^2))^0.5; //magnitude of impedance in ohms
11 phi=(180/%pi)*atan(x/r); //phase angle in degrees
12 i=v/z; //current magnitude in amperes

```

```

13
14 //output
15 mprintf('the current will be %3.0f A lagging by %3.0
    f degrees',i,phi)

```

---

**Scilab code Exa 6.6** finding magnitude and phase angle of the voltage

```

1  clc
2  clear
3
4  //input
5  i=8-(%i*6); //current flowing in amperes
6  z=10+(%i*10); //impedance in ohms
7
8  //calculations
9  I=(((real(i))^2)+((imag(i))^2))^0.5; //current
    magnitude in amperes
10 Z=(((real(z))^2)+((imag(z))^2))^0.5; //magnitude of
    impedance in ohms
11 phi1=(180/%pi)*atan(-(imag(i))/(real(i))); //phase
    angle of current in degrees
12 phi2=(180/%pi)*atan(-(imag(z))/(real(z))); //phase
    angle of impedance in degrees
13 phi=-(phi2+phi1);
14 v=I*Z; //voltage across coil in volts
15
16 //output
17 mprintf('the voltage across the coil is %3.0f V
    leading by %3.0f degrees',v,phi)

```

---

**Scilab code Exa 6.7** calculating the components of equivalent series circuit

```

1  clc
2  clear
3
4  //input
5  z1=10+(%i*15); //first impedance in ohms
6  z2=15-(%i*25); //second impedance in ohms
7  //impedances 1 and 2 are connected in parallel
8
9  //calculations
10 Z1=(((real(z1)^2)+(imag(z1)^2)))^0.5; //magnitude of
    impedance 1 in ohms
11 Z2=(((real(z2)^2)+(imag(z2)^2)))^0.5; //magnitude of
    impedance 2 in ohms
12 phi1=(180/%pi)*atan((imag(z1))/real(z1)); //phase
    angle 1 in degrees
13 phi2=(180/%pi)*atan((imag(z2))/real(z2)); //phase
    angle 1 in degrees
14 Z=z1+z2; //total impedance in ohms
15 Zt=(((real(Z)^2)+(imag(Z)^2)))^0.5; //magnitude of
    total impedance in ohms
16 PHIt=(180/%pi)*atan((imag(Z))/real(Z)); //total phase
    angle in degrees
17 ZT=(Z1*Z2)/Zt; //magnitude of equivalent impedance in
    ohms
18 PHIT=phi1+phi2-PHIt; //phase angle of equivalent
    impedance in degrees
19 p=(PHIT*%pi)/180; // phase angle in radians
20 Zs=(ZT*cos(p))+(%i*(ZT*sin(p))); //series impedance
    in ohms
21 R=real(Zs); //resistance of equivalent series circuit
    in ohms
22 X=imag(Zs); //reactance of equivalent series circuit
    in ohms
23
24 //output
25 fprintf('the resistance and inductive reactance of
    equivalent series circuit are %3.1f ohm and %3.2f
    ohm ',R,X)

```



---

**Scilab code Exa 6.8** finding the magnitude and phase angle of current

```
1  clc
2  clear
3
4  //input
5  y1=0.01-(%i*0.03); //first admittance in mho
6  y2=0.05+(%i*0); //second admittance in mho
7  y3=%i*0.05; //third admittance in mho
8  //three admittances are connected in parallel
9  v=250; //supply voltage in volts
10
11 //calculations
12 y=y1+y2+y3; //total admittance in mho
13 Y=(((real(y)^2)+(imag(y)^2))^0.5; //magnitude of
    total admittance in mho
14 phi=(180/%pi)*atan((imag(y))/(real(y))); //phase
    angle in degrees
15 i=v*Y; //current in amperes
16
17 //output
18 mprintf('the total current is %3.1f A leading on the
    voltage by %3.1f degrees',i,phi)
```

---

# Chapter 7

## power and power factor

Scilab code Exa 7.1 finding the average and instantaneous power

```
1  clc
2  clear
3
4  //input
5  r=20; //resistance of coil in ohms
6  l=0.04; //inductance of coil in henry
7  v=240; //supply voltage in volts
8  f=50; //frequency of supply in hertz
9
10 //calculations
11 x1=2*%pi*f*l; //reactance of coil in ohms
12 z=((r^2)+(x1^2))^0.5; //impedance of coil in ohms
13 i=v/z; //current in amperes
14 cosp=r/z; //cosine of phase angle
15 Pavg=v*i*cosp; //average power in watts
16 pmax=v*i*(cosp+1); //maximum instantaneous power in
    watts
17
18 //ouput
19 mprintf('the average power and the maximum
    instantaneous power in the coil are %3.0f W and
```

`%3.0f W respectively ',Pavg,pmax)`

---

**Scilab code Exa 7.2** finding the time elapsed before maximum power

```
1  clc
2  clear
3
4  //input
5  //given e.m.f. equation is e=340sin(314t)V and
   current equation is i=12sin(314t-0.7)A
6  t=0.0015; //time in seconds after which the e.m.f. is
   zero and increasing positively
7  vm=340; //maximum voltage in volts from voltage
   equation
8  im=12; //maximum current in amperes from current
   equation
9  phi=0.7 //phase angle from current equation
10 w=314; //from voltage and current equations
11
12 //calculations
13 //when t=0.0015 seconds
14 p=vm*sin(w*t)*im*sin((w*t)-phi); //power in watts
15 pmax=(vm*im*((cos(phi))+1))/2; //maximum power in
   watts
16 T=(((acos(((2*pmax)/(vm*im))-cos(phi))))+phi)
   *(1000))/(2*w); //time interval in milliseconds
17
18 //output
19 mprintf('at a time of 1.5mS after the specified
   instant the power was %3.0f W and the maximum
   power occured %3.1f mS after the same specified
   instant ',p,T)
```

---

**Scilab code Exa 7.3** calculation of apparent and reactive powers and the inductance of coil

```
1  clc
2  clear
3
4  //input
5  z1=20; //impedance of the inductor in ohms
6  pf=0.45; //lagging power factor
7  v=240; //supply voltage in volts
8  f=50; //supply frequency in hertz
9
10 //calculations
11 i=v/z1; //current taken by the inductor in amperes
12 p=v*i*pf; //true power in the circuit in watts
13 pa=v*i; //apparent power in VA
14 pr=v*i*sin(acos(pf)); //reactive power in var
15 r=p/(i*i); //resistance in ohms
16 x1=((z1^2)-(r^2))^0.5; //reactance in ohms
17 l=(x1*1000)/(2*pi*f); //inductance in millihenry
18
19 //output
20 mprintf('the wattmeter will read %3.0f W \n the
    apparent and the reactive powers are %3.0f VA and
    %3.0f var respectively \n the inductance of the
    inductor is %3.0f mH',p,pa,pr,l)
```

---

**Scilab code Exa 7.4** finding the total kVA loading and overall power factor

```
1  clc
2  clear
3
4  //input
5  d1=400; //load in kW at unity power factor
6  d2=1000; //load in kVA at a lagging power factor
```

```

7 d3=500; //load in kVA at a leading power factor
8 pf1=1; //unity power factor
9 pf2=0.71; //lagging power factor
10 pf3=0.8; //leading power factor
11
12 //calculations
13 pa=d1+(d2*pf2)+(d3*pf3); //total active power loading
    in watts
14 pr=(d2*pf2)-(d3*sin(acos(pf3))); //total reactive
    power in var
15 pk=(((pa^2)+(pr^2))^0.5)/1000; //total MVA loading
16 pf=pa/(pk*1000); //total power factor
17
18 //output
19 mprintf('the total load on the sub-station is %3.2f
    MVA at a lagging power factor of %3.3f ',pk,pf)

```

---

**Scilab code Exa 7.5** finding total active power taken from the supply

```

1 clc
2 clear
3
4 //input
5 r1=10; //resistance of an inductor in ohms
6 l=0.05; //inductance of an inductor in henry
7 rc=20; //resistance in series with a capacitor in
    ohms
8 c=150*(10^-6); //capacitance of a capacitor in farad
9 //inductor is in parallel with the series circuit
    containing a resistor and a capacitor
10 v=240; //supply voltage in volts
11 f=50; //supply frequency in hertz
12
13 //calculations
14 xl=2*pi*f*l; //inductive reactance in ohms

```

```

15 z1=((r1^2)+(x1^2))^0.5;//impedance of the inductor
    in ohms
16 i1=v/z1;//current in inductor in amperes
17 phi1=r1/z1;//power factor of inductor
18 xc=1/(2*%pi*f*c);//capacitive reactance in ohms
19 z2=((rc^2)+(xc^2))^0.5;//impedance of series circuit
    in ohms
20 i2=v/z2;//current in series circuit in amperes
21 phi2=rc/z2;//power factor of series circuit
22 i=(i1*phi1)+(i2*phi2);//total in phase component in
    amperes
23 P=(v*i);//total power in watts
24
25 //output
26 mprintf('the active power taken from the supply is
    %3.0f W',P)

```

---

**Scilab code Exa 7.6** calculation of total power and current taken from the supply using admittance method

```

1 clc
2 clear
3
4 //input
5 ra=5;//resistance of inductor in branch a in ohms
6 la=0.08;//inductance of the inductor in branch a in
    henry
7 rb=15;//resistance in branch 2 in ohms
8 cb=100*(10^-6);//capacitance in branch b in farad
9 v=240;//supply voltage in volts
10 f=50;//supply frequency in hertz
11
12 //calculations
13 //branches a and b are in parallel with supply
14 xa=2*%pi*f*la;//inductive reactance in ohms

```

```

15 za=((ra^2)+(xa^2))^0.5; //impedance in branch a in
    ohms
16 xc=1/(2*%pi*f*cb); //capacitive reactance in ohms
17 zb=((rb^2)+(xc^2))^0.5; //impedance in branch b in
    ohms
18 g=(ra/(za^2))+(rb/(zb^2)); //total conductance in
    siemens
19 b=(-xa/(za^2))+(xc/(zb^2)); //total susceptance in
    siemens
20 y=((g^2)+(b^2))^0.5; //total admittance in siemens
21 i=v*y; //total current in amperes
22 p=v*v*g; //total power taken from the supply in watts
23
24 //output
25 mprintf('the total current and power taken from the
    supply are %3.2f A and %3.0f W',i,p)

```

---

**Scilab code Exa 7.7** finding required range of frequency

```

1  clc
2  clear
3
4  //input
5  r=10; //resistance of an acceptor circuit in ohms
6  l=0.08; //inductance of an acceptor circuit in henry
7  c=1250*(10^-12); //capacitance of an acceptor circuit
    in faraf
8  v=1.5; //supply voltage in volts
9  //average power dissipated in not less than half of
    power at resonance
10
11 //calculations
12 i=v/r; //current in amperes
13 p=i*i*r; //power in watts
14 pmin=p*0.5; //minimum average power in watts

```

```

15 i1=pmin/r;//current in amperes
16 z1=v/i1;//impedance in ohms
17 x=((z1^2)-(r^2))^0.5;//effective reactance in ohms
18 //on equating xc and xl we get equation for
    frequency as  $-(502*(10^{-6}))(f^2)-10f+127.2(10^6)$ 
    =0
19 a= -502*(10^-6);//from the above equation
20 b= -10;//from the above equation
21 c=127.2*(10^6);//from the above equation
22 f2=((b-(((b^2)-(4*a*c))^0.5))/(2*a))/1000;//upper
    frequency in hertz
23 f1=(((-b)-(((b^2)-(4*a*c))^0.5))/(2*a))/1000;//
    lower frequency in hertz
24
25 //output
26 mprintf('the frequency range over which the average
    power doesnot fall below 0.5*the average power at
    resonance is %3.0f kHz and %3.0f kHz',f1,f2)

```

---

**Scilab code Exa 7.8** calculation of required capacitance

```

1 clc
2 clear
3
4 //input
5 d=125;//power taken by an industrial load in
    kilowatts
6 pf=0.6;//power factor
7 v=415;//supply voltage in volts
8 f=50;//supply frequency in hertz
9
10 //calculations
11 phii=acos(pf);//initial phase angle in radians
12 kVAo=d/pf;//original kVA
13 kvaro=d*tan(phii);//original kvar

```



```

14 //for 0.9 power factor
15 phif=acos(0.9); //phase angle in radians
16 kvarf=d*tan(phif); //final kvar
17 kvarc=kvaro-kvarf; //capacitor kvar
18 c1=(kvarc*(10^3)*(10^6))/(v*v*2*pi*f); //capacitance
    in microfarad
19 kVAf=d/0.9; //final kVA
20 kVAR=kVAo-kVAf; //reduction in kVA
21 //for unity power factor
22 kvarC=kvaro; //capacitor kvar
23 c2=(kvarC*(10^3)*(10^6))/(v*v*2*pi*f); //capacitance
    in microfarad
24 kVAF=d; //final kVA
25 kVAR=kVAo-kVAF; //reduction in kVA
26
27 //output
28 mprintf('the required values of capacitance are %3.0
    f uF and %3.0f uF and the respective savings in
    kVA are %3.1f kVA and %3.1f kVA',c1,c2,kVAR,kVAR
    )

```

---

**Scilab code Exa 7.9** calculation of required capacitance

```

1  clc
2  clear
3
4  //input
5  d=75; //load at lagging powerfactor in kW
6  pf=0.75; //lagging power factor
7  v=1100; //supply voltage in volts
8  f=50; //frequency in hertz
9  d0=10; //desired increment in load in kW
10
11 //calculations
12 kVAi=d/pf; //initial kVA

```

```

13 cos2=(d+d0)/kVAi;//final power factor
14 phi1=acos(pf);
15 phi2=acos(cos2);
16 kvarc=kVAi*(d0)*(sin(phi1)-sin(phi2));//capacitor
    kvar
17 c=(kvarc*(10^3)*(10^6))/(v*v*2*pi*f);//capacitance
    required in microfarad
18
19 //output
20 mprintf('the power factor has to be increased to %3
    .2f lag and the value of capacitance required is
    %3.0f uF',cos2,c)

```

---

**Scilab code Exa 7.10** calculation of pure resistive load for maximum power

```

1  clc
2  clear
3
4  //input
5  v=3.3;//voltage rating of an alternator in kV
6  ri=3;//internal resistance of alternator in ohms
7  xl=32;//series inductive reactance in ohms
8  rc=1;//resistance of a cable in ohms
9  xc=2;//effective reactance of the cable in ohms
10
11 //calculations
12 R=ri+rc;//resistance of line and alternator in ohms
13 X=xl+xc;//reactance of line and alternator in ohms
14 Z=((R^2)+(X^2))^0.5;//impedance of line and
    alternator in ohms
15 Rl=Z;//required load resistance in ohms
16 zt((((Z+R)^2)+(X^2))^0.5;//total impedance of the
    circuit in ohms
17 I=(v*1000)/zt;//current in amperes
18 pmax=(I*I*Rl)/1000;//maximum power in load in

```

```

        kilowatts
19
20 //output
21 mprintf('to give a maximum load power of %3.0f kW the
        load must have a resistance of %3.2f ohms', pmax,
        R1)

```

---

**Scilab code Exa 7.11** calculation of components of a fully variable load

```

1  clc
2  clear
3
4  //input
5  r=10; //resistance in source impedance in kilohms
6  l=0.005; //inductance in source impedance in henry
7  v=100; //supply voltage in volts
8  f=10000; //supply frequency in hertz
9
10 //calculations
11 xl=2*pi*f*l; //inductive reactance in ohms
12 c=((10^6)*(10^3))/(2*pi*f*xl); //capacitance in
        picofarad
13
14 //output
15 mprintf('for maximum power transfer the load must
        consist of %3.0f kilo ohms resistance in series
        with a capacitance of %3.0f pF', r, c)

```

---

**Scilab code Exa 7.12** calculation of power dissipated by the inductor

```

1  clc
2  clear
3

```

```

4 //input
5 r=20; //resistance of resistor connected in series
   with inductor in ohms
6 v=240; //supply voltage in volts
7 f=50; //supply frequency in hertz
8 pdr=130; //potential drop across resistor in volts
9 pdl=170; //potential drop across inductor in volts
10
11 //calculations
12 cosp=((v*v)-(pdr^2)-(pdl^2))/(2*pdr*pdl); //power
   factor
13 i=pdr/r; //current in amperes
14 p=pdl*i*cosp; //power in watts
15
16 //output
17 mprintf('the power dissipated by the inductor is %3
   .0 f W',p)

```

---

**Scilab code Exa 7.13** calculation of inductance resistance and the power loss

```

1 clc
2 clear
3
4 //input
5 r=32; //resistance connected in parallel with an
   inductor in ohms
6 v=240; //supply voltage in volts
7 f=50; //supply frequency in hertz
8 il=8; //current in inductor in amperes
9 it=14; //total current in amperes
10
11 //calculations
12 ir=v/r; //current in resistor in amperes
13 cosp=((it^2)-(ir^2)-(il^2))/(2*ir*il); //power factor

```

```

14 R=(v*cosp)/i1;//resistance of inductor in ohms
15 x1=(v*sin(acos(cosp)))/i1;//reactance in ohms
16 l=(x1*1000)/(2*pi*f);//inductance in millihenry
17 p=i1*i1*R;//power loss in inductor in watts
18
19 //output
20 mprintf('the resistance and the inductance of the
    inductor are %3.2f ohms and %3.0f mH respectively
    and the power loss is %3.0f W',R,l,p)

```

---

**Scilab code Exa 7.14** finding the power for the load and whole circuit

```

1  clc
2  clear
3
4  //input
5  i1=9;//current taken by a resistive inductive load
    form supply in amperes
6  v=250;//supply voltage in volts
7  f=50;//frequency in hertz
8  i2=12;//current taken when a resistor is placed in
    parallel with the load in amperes
9  r=50;//resistance of the resistor placed in parallel
10
11 //calculations
12 ir=v/r;//current through the resistor in amperes
13 cosp=((i2^2)-(ir^2)-(i1^2))/(2*i1*ir);//power factor
14 cosP=(ir+(i1*cosp))/i2;//power factor for whole
    circuit
15 pc=(v*i2*cosP)/1000;//power taken by whole circuit
    in kilowatts
16 pl=(v*i1*cosp);//power taken by load in watts
17
18 //output
19 mprintf('the values of power and power factor for

```

the whole circuit and the load are %3.1f kW:%3.2f  
(lag) and %3.0f W:%3.2f (lag) respectively ',pc,  
cosP ,pl ,cosp)

---

# Chapter 8

## three phase circuits

Scilab code Exa 8.1 finding the phase voltage and line current

```
1 clc
2 clear
3
4 //input
5 r=24; //resistance of each of three resistors
   connected in star in ohms
6 v=415; //3 phase supply in volts
7
8 //calculations
9 vp=v/(3^0.5); //phase voltage in volts
10 ip=vp/r; //phase current in amperes
11 il=ip; //for star connection
12
13 //output
14 mprintf('the phase voltage is %3.0f V and the
   current in each line is %3.0f A',vp,il)
```

---

Scilab code Exa 8.2 finding the line current and the phase angle

```

1  clc
2  clear
3
4  //input
5  r=15; //resistance of each of three coils connected
      in star in ohms
6  l=0.08; //inductance of each of three coils connected
      in star in in henry
7  v=415; //supply voltage in volts
8  f=50; //supply frequency in hertz
9
10 //calculations
11 zp=((r^2)+((2*pi*f*l)^2))^0.5; //impedance per phase
      in ohms
12 il=v/(zp*(3^0.5)); //line current in amperes
13 ip=il; //for star connection
14 phi=(180/pi)*acos(r/zp); //phase angle in degrees
15
16 //output
17 mprintf('the line current will be %3.1f A lagging on
      its corresponding phase voltage by %3.0f degrees
      ',il,phi)

```

---

**Scilab code Exa 8.3** calculation of total line current and total phase angle

```

1  clc
2  clear
3
4  //input
5  v=415; //3 phase supply voltage in volts
6  f=50; //supply frequency in hertz
7  //system is loaded with three star connected coils
      and three star connected resistors
8  ic=10; //current taken by each of the coils in
      amperes lagging by 60 degrees

```



```

9 ir=8;//current taken by each of the resistors in
  amperes
10 phi=(60*%pi)/180;//lagging phase angle in radians
11
12 //calculations
13 ii=ir+(ic*cos(phi));//sum of in phase components in
  amperes
14 iq=(ic*sin(phi));//sum of quadrature components in
  amperes
15 i=((ii^2)+(iq^2))^0.5;//total current in amperes
16 PHI=(180/%pi)*acos(ii/i);//phase angle in degrees
17
18 //ouput
19 mprintf('the total line current is %3.1f A lagging
  on the relative phase voltage by %3.1f degrees',i
  ,PHI)

```

---

**Scilab code Exa 8.4** illustration for neutral current is zero

```

1 clc
2 clear
3
4 //input
5 //three impedances of resistance and inductive
  reactance are connected in star
6 r=20;//resistance in ohms
7 x=15;//reactance in ohms
8 v=440;//three phase supply voltage in volts
9
10 //calculations
11 z=((r^2)+(x^2))^0.5;//each impedance in ohms
12 il=v/((3^0.5)*z);//line current in amperes
13 ip=il;//for star connections
14 cosp1=(180/%pi)*acos(r/z);//power factor1 in degrees
15 cosp2=120+cosp1;//each current is displaced by 120

```

```

degrees
16 cosp3=240+cosp1;//each current is displaced by 120
degrees
17 ii=il*((cos(acos(r/z)))+cos((120+cosp1)*(%pi/180))+
cos((240+cosp1)*(%pi/180)));//total in phase
component in amperes
18 iq=il*-((sin(acos(r/z)))+sin((120+cosp1)*(%pi/180))+
sin((240+cosp1)*(%pi/180)));//total quadrature
component in amperes
19
20 //output
21 mprintf('the the resultant in phase and quadrature
components are %3.5fA and %3.5fA respectively\
hence the sum of three balanced currents is zero
',ii,iq)

```

---

**Scilab code Exa 8.5** calculation of phase and line currents

```

1 clc
2 clear
3
4 //input
5 //three resistors are connected in delta
6 r=30;//resistance of each resistor in ohms
7 v=240;//supply voltage in volts
8 f=50;//supply frequency in hertz
9
10 //calculations
11 ip=v/r;//phase current in amperes
12 il=ip*(3^0.5);//line current in amperes
13
14 //output
15 mprintf('the phase and line currents are %3.0f A and
%3.1f A respectively ',ip,il)

```

---

**Scilab code Exa 8.6** calculation of line current and phase angle

```
1  clc
2  clear
3
4  //input
5  //three impedances are connected in delta each
   containing a resistor and a capacitor
6  r=15; //resistance in ohms
7  c=100*(10^-6); //capacitance in farad
8  v=415; //3phase supply voltage in volts
9  f=50; //frequency in hertz
10
11 //calculations
12 xc=1/(2*%pi*f*c); //capacitive reactance in ohms
13 zp=((r^2)+(xc^2))^0.5; //impedance per phase in ohms
14 ip=v/zp; //phase current in amperes
15 il=ip*(3^0.5); //line current in amperes
16 phi=(180/%pi)*acos(r/zp); //leading phase angle in
   degrees
17
18 //output
19 mprintf('the line current is %3.1f A and the phase
   angle is %3.1f lead',il,phi)
```

---

**Scilab code Exa 8.7** determination of line currents and phase angle in two cases

```
1  clc
2  clear
3
4  //input
```

```

5 //three impedances are connected in delta each
   containing a resistor and an inductor
6 r=25;//resistance in ohms
7 l=0.06;//inductance in henry
8 v=415;//3 phase supply voltage in volts
9 f=50;//supply frequency in hertz
10 //three capacitors are connected across the same
   supply in star
11 c=200*(10^-6);//the capacitance in farad
12
13 //calculations
14 //for delta connection
15 xl=2*%pi*f*l;//inductive reactance in ohms
16 zp=((r^2)+(xl^2))^0.5;//impedance per phase in ohms
17 ip=v/zp;//phase current in amperes
18 il=ip*(3^0.5);//line current in amperes
19 //il lags on ip by 30degrees.so the angle between
   the line current and ilne voltage is 30+phase
   angle in degrees
20 phi=30+((180/%pi)*acos(r/zp));//phase angle in
   degrees
21 cosp=(r/zp);//phase angle in radians
22 //for star connection
23 vp=v/(3^0.5);//phase voltage in volts
24 xc=1/(2*%pi*f*c);//capacitive reactance in ohms
25 ic=vp/xc;//current in amperes
26 //ic leads the line voltage by 60degrees
27 cosP=cos((60*%pi)/180);//phase angle in radians
28 ii=(il*cos((phi*%pi)/180))+(ic*(cosP));//in-phase
   components in amperes
29 iq=((-il*sin((phi*%pi)/180))+(ic*sin(acos(cosP))));
   //quadrature component in amperes
30 it=((ii^2)+(iq^2))^0.5;//total current in amperes
31 PHI=(180/%pi)*acos(ii/it);//phase angle in degrees
32
33 //output
34 mprintf('the original line current was %3.0f A
   lagging on the line voltage by %3.0f degrees and

```

the final current is %3.1f A lagging on the line voltage by %3.1f degrees',il,phi,it,PHI)

---

**Scilab code Exa 8.8** determination of line and motor phase currents

```
1  clc
2  clear
3
4  //input
5  p=50; //power rating of a delta connected 3 phase a.c
   . motor in kW
6  v=415; //voltage rating of a delta connected 3 phase
   a.c. motor in volts
7  n=0.85; //full load efficiency in per units
8  pf=0.87; //full load power factor
9
10 //calculations
11 inp=p/n; //full load input in kW
12 il=inp*(1000/((3^0.5)*v*pf)); //line current in
   amperes
13 ip=il/(3^0.5); //phase current in amperes
14
15 //output
16 mprintf('the line and motor phase currents are %3.0
   fA and %3.1fA respectively ',il,ip)
```

---

**Scilab code Exa 8.9** calculation of capacitance per phase

```
1  clc
2  clear
3
4  //input
```

```

5 p=27; //power rating of a delta connected 3 phase a.c
  . motor in kW
6 v=500; //voltage rating of a delta connected 3 phase
  a.c. motor in volts
7 n=0.9; //full load effeciency in per units
8 pf=0.7; //full load power factor
9 f=50; //general supply frequency in hertz
10
11 //calculations
12 il=(1000*p)/((3^0.5)*v*pf*n); //line current taken by
  motor in amperes
13 phi=acos(pf); //phase angle
14 //the line current will lag by phi radians on the
  line voltage
15 //to bring total current in phase with line voltage
  ic*sin60 must equal ilsin75.(information from
  phasor diagram)
16 ic=(il*sin(phi+0.524))/sin((60*%pi)/180); //capacitor
  current in amperes and 0.524 is 30degrees
  converted into radians and added in respect to
  above mentioned condition
17 c=(ic*1000000)/((3^0.5)*v*f*2*%pi); //capacitance per
  phase in micro farad
18
19 //output
20 mprintf('the required capacitance per phase is %3.0
  fuF ',c)

```

---

**Scilab code Exa 8.10** detmrining the wattmeter readings for given condi-  
tions

```

1 clc
2 clear
3
4 //input

```

```

5 v=415; // three phase supply voltage in volts
6 f=50; //supply frequency in hertz
7 //the power taken from this supply is taken by a
   delta connected load with each branch consisting
   a resistor and an inductance is measured by two
   wattmeters
8 r=20; //resistance in ohms
9 l=0.06; //inductance in henry
10
11 //calculations
12 xp=2*pi*f*l; //reactance per phase in ohms
13 zp=((r^2)+(xp^2))^0.5; //impedance per phase in ohms
14 ip=v/zp; //current per phase in amperes
15 il=ip*(3^0.5); //line current in amperes
16 phi=acos(r/zp); //phase angle in radians
17 phi1=(30*pi)/180; //30 degrees converted into radians
18 w1=(v*il*cos(phi+phi1))/1000; //reading of wattmeter
   1 and 30 degrees is added with correspondence to
   phasor diagram in kilowatts
19 w2=(v*il*cos(phi-phi1))/1000; //reading of wattmeter
   2 and 30 degrees is added with correspondence to
   phasor diagram in kilowatts
20
21 mprintf('the readings on the two wattmeters will be
   %3.3f kW and %3.2f kW',w1,w2)

```

---

# Chapter 9

## the single phase transformer

Scilab code Exa 9.1 finding the number turns on secondary

```
1  clc
2  clear
3
4  //input
5  t1=96;//number turns on the primary side of an ideal
    transformer
6  v=240;//supply voltage in volts
7  f=50;//supply frequency in hertz
8  v2=660;//secondary pd in volts
9
10 //calculations
11 vp=v/t1;//primary volts per turn
12 vs=vp;//secondary volts per turn
13 t2=v2/vs;//secondary turns
14
15 //output
16 mprintf('to produce a p.d. of 660V the secondary
    coil should have %3.0f turns ',t2)
```

---



**Scilab code Exa 9.2** finding the secondary turns and the full load primary and secondary currents

```
1  clc
2  clear
3
4  //input
5  vp=660; //primary voltage in volts
6  vs=1100; //secondary voltage in volts
7  f=50; //supply frequency in hertz
8  kva=10; //kVA rating of the transformer
9  t1=550; //number of primary turns
10
11 //calculations
12 pv=vp/t1; //primary volts per turn
13 t2=vs/pv; //number of secondary turns
14 inpi=(kva*1000)/vp; //input current in amperes
15 is=(kva*1000)/vs; //secondary current in amperes
16
17 //output
18 mprintf('the number of secondary turns is %3.0f and
    the respective primary and secondary currents are
    %3.1fA and %3.1fA ',t2,inpi,is)
```

---

**Scilab code Exa 9.3** finding the mutual inductance between the windings

```
1  clc
2  clear
3
4  //input
5  t1=120; //primary turns of an ideal transformer
6  ls1=0.24; //self inductance of primary in henry
7  v=240; //supply voltage in volts
8  t2=300; //secondary turns of the ideal transformer
9
```

```

10 //calculations
11 d=v/ls1; //rate of change of current in A/s
12 v2=v*(t2/t1); //secondary voltage in volts
13 M=v2/d; //mutual impedance in henry
14 ls2=ls1*((t2*t2)/(t1*t1)); //self inductance of the
    secondary in henry
15
16 //output
17 mprintf('the mutual impedance between the coils is
    %3.1fH and the self inductance of the secondary
    winding is %3.1fH',M,ls2)

```

---

**Scilab code Exa 9.4** finding magnetizing current and the no load loss

```

1 clc
2 clear
3
4 //input
5 i=0.4; //no load current in amperes
6 pf=0.25; //lagging power factor
7 v=250; //supply voltage in volts
8 f=50; //supply frequency in hertz
9
10 //calculations
11 ie=i*pf; //loss component of no load current in
    amperes
12 im=(i2-(ie2))0.5; //magnetizing component in
    amperes
13 p=v*ie; //no load power loss in watts
14
15 //output
16 mprintf('the magnetising current is %3.3fA and the
    no load loss is %3.0f W',im,p)

```

---

**Scilab code Exa 9.5** finding the flux density in the core

```
1  clc
2  clear
3
4  //input
5  v=240; //supply voltage in volts
6  f=50; //supply frequency in hertz
7  t1=500; //number of primary turns
8  i0=0.35; //no load current in amperes
9  p=44; //power loss in watts
10 l=0.4; //magnetic length of the core in meters
11 ur=2000; //relative permeability of core
12 u0=1.257*(10^-6); //absolute permeability
13
14 //calculations
15 cosp=p/(v*i0); //no load power factor
16 im=i0*sin(acos(cosp)); //magnetizing current in
    amperes
17 b=(u0*ur*im*t1)/l; //flux density in tesla
18
19 //output
20 mprintf('the flux density produced in the core will
    be %3.3f T',b)
```

---

**Scilab code Exa 9.6** determination of components of parallel circuit

```
1  clc
2  clear
3
4  //input
5  vp=440; //primary voltage in volts
```

```

6 vs=240;//secondary voltage in volts
7 f=50;//supply voltage in hertz
8 i0=0.5;//no load current in amperes
9 pf=0.3;//lagging power factor
10
11 //calculations
12 ii=i0*pf;//in phase component in amperes
13 r0=vp/(ii*1000);//resistance in ohms
14 iq=((i0^2)-(ii^2))^0.5;//quadrature component in
    amperes
15 x0=vp/iq;//reactance in ohms
16 l0=x0/(2*pi*f);//inductance in henry
17
18 //output
19 mprintf('the transformer on load may be represented
    by %3.2fkOhms resistance in parallel with a pure
    inductance of %3.2fH',r0,l0)

```

---

**Scilab code Exa 9.7** finding number of primary and secondary turns

```

1 clc
2 clear
3
4 //input
5 vp=1100;//voltage on the primary in volts
6 vs=240;//secondary voltage in volts
7 f=50;//supply frequency in hertz
8 b=1.4;//flux density in tesla
9 s=0.2;//side of the square core in meter
10
11 //calculations
12 ag=s*s;//gross area of core in square meters
13 am=0.9*ag;//magnetic area of core in square meters
14 np=vp/(4.44*b*am*f);//number of turns in primary
15 ns=np*(vs/vp);//number of turns in secondary

```

```

16
17 //output
18 mprintf('the number of turns in the primary and
    secondary winding would be %3.0f and %3.0f
    respectively ',np,ns)

```

---

**Scilab code Exa 9.8** estimation of flux density magnetizing current and core loss

```

1  clc
2  clear
3
4  //input
5  np=350; //number of turn in the primary
6  lm=0.8; //mean length of core in meters
7  am=0.006; //magnetic area in square meter
8  i0=0.8; //no load current in amperes
9  v=500; //supply voltage in volts
10 f=50; //frequency of supply in hertz
11 ur=2000; //relative permeability of the core
12 u0=1.257*(10^-6); //absolute permeability
13
14 //calculations
15 bm=v/(4.44*am*np*f); //maximum flux density in tesla
16 im=(bm*i0)/(u0*ur*np*(2^0.5)); //magnetizing current
    in amperes
17 sinp=im/i0; //sine of no load phase angle
18 p=v*lm*cos(asin(im/i0)); //power loss of core in
    watts
19
20 //output
21 mprintf('the maximum flux density in the core will
    be %3.3fT with a magnetizing current of %3.3fA
    and a core loss of %3.0fW',bm,im,p)

```

---

**Scilab code Exa 9.9** calculation of different efficiencies and loading for maximum efficiency

```
1  clc
2  clear
3
4  //input
5  kva=20000; //kVA rating of the transformer in VA
6  vp=1100; //primary voltage in volts
7  vs=240; //secondary voltage in volts
8  pi=500; //iron losses in watts
9  pc=600; //full load copper losses in watts
10 pf=0.8; //lagging power factor
11
12 //calculations
13 out=kva*pf; //full load output in watts
14 fl1=pi+pc; //full load losses in watts
15 n=out/(out+fl1); //efficiency in perunits
16 hf1=kva/2; //unity power factor
17 cp=pc*(1/(2*2)); //copper loss in watts
18 n1=(hf1/1000)/((hf1/1000)+0.5+(cp/1000)); //
    efficiency in per units
19 kvat=(kva*((pi/pc)^0.5))/1000; // total kVA
20
21 //output
22 mprintf('the efficiencies on full load ,at 0.8 lag
    and 0.5*full load ,at unity power factor are %3.3f
    p.u. and %3.2f p.u. respectively.\n the loading
    for maximum efficiency is %3.2f kVA',n,n1,kvat)
```

---

**Scilab code Exa 9.10** calculation of all day efficiency

```

1  clc
2  clear
3
4  //input
5  kva=10; //kVA rating of the transformer
6  vp=400; //voltage on primary side in volts
7  vs=230; //voltage on secondary side in volts
8  //short circuit test
9  ppd1=18; //primary p.d. in volts
10 ip1=25; //primary current in amperes
11 inp1=120; //power input in watts
12 //short circuit test
13 ppd2=400; //primary p.d. in volts
14 ip2=0.5; //primary current in amperes
15 inp2=70; //power input in watts
16
17 //calculations
18 zp=ppd1/ip1; //equivalent primary impedance in ohms
19 rp=inp1/(ip1^2); //equivalent resistance in ohms
20 xp=((zp^2)-(rp^2))^0.5; //equivalent leakage
    reactance in ohms
21 r0=(vp^2)/(1000*inp2); //resistance of parallel
    circuit
22 phi=sin(acos(inp2/(vp*ip2))); //sine of power factor
23 im=ip2*phi; //magnetizing current in amperes
24 x0=vp/im; //reactance in ohms
25
26 //output
27 mprintf('the equivalent circuit parameters are \n Rp
    =%3.3f ohms \n Xp=%3.3f ohms \n r0=%3.3f kilo
    ohms \n x0=%3.1f ohms ',rp,xp,r0,x0)

```

---

**Scilab code Exa 9.11** determination of equivalent circuit

```

1  clc

```

```

2 clear
3
4 //input
5 kva=10;//kVA rating of the transformer
6 vp=400;//voltage on primary side in volts
7 vs=230;//voltage on secondary side in volts
8 //short circuit test
9 ppd1=18;//primary p.d. in volts
10 ip1=25;//primary current in amperes
11 inp1=120;//power input in watts
12 //short circuit test
13 ppd2=400;//primary p.d. in volts
14 ip2=0.5;//primary current in amperes
15 inp2=70;//power input in watts
16
17 //calculations
18 zp=ppd1/ip1;//equivalent primary impedance in ohms
19 rp=inp1/(ip1^2);//equivalent resistance in ohms
20 xp=((zp^2)-(rp^2))^0.5;//equivalent leakage
    reactance in ohms
21 r0=(vp^2)/(1000*inp2);//resistance of parallel
    circuit
22 phi=sin(acos(inp2/(vp*ip2)));//sine of power factor
23 im=ip2*phi;//magnetizing current in amperes
24 x0=vp/im;//reactance in ohms
25
26 //output
27 mprintf('the equivalent circuit parameters are \n Rp
    =%3.3f ohms \n Xp=%3.3f ohms \n r0=%3.3f kilo
    ohms \n x0=%3.1f ohms ',rp,xp,r0,x0)

```

---

**Scilab code Exa 9.12** finding the primary input current secondary terminal voltage and the efficiency

```

1 clc

```



```

2 clear
3
4 //input
5 kva=5; //kVA rating of the transformer
6 pf=0.8; //power factor
7 vp=250; //voltage on primary side in volts
8 vs=500; //voltage on secondary side in volts
9 //from equivalent circuit
10 r0=750; //resistance in ohms
11 x0=325; //reactance in ohms
12 Rp=0.4; //equivalent resistance referred to primary
    side in ohms
13 Xp=0.75; //equivalent reactance referred to primary
    side in ohms
14
15 //calculations
16 is=(kva*1000)/vs; //full load secondary current in
    amperes
17 ip1=is*(vs/vp); //current in amperes
18 ep=vp-((ip1*pf)+(Xp*sin(acos(pf))))); //in volts
19 Vs=ep*(vs/vp); // in volts
20 i1=vp/(vs+vp); //component of Io in phase with Vs in
    amperes
21 i2=i1*pf; //component of Ie in phase with Ip
22 i3=i1*sin(acos(pf)); //component of Ie in quadrature
    with Ip
23 im=vp/x0; //magnetizing current in amperes
24 i4=im*sin(acos(pf)); //component of Im in phase with
    Ip
25 i5=im*pf; //component of Im in quadrature with Ip
26 Ip=(((ip1+i2+i4)^2)+((i5-i3)^2))^0.5; //total primary
    current in amperes
27 P=vp*Ip*pf; //power input in watts
28 pc=ip1*ip1*i4; //copper loss in watts
29 pi=vp*i1; //iron loss in watts
30 n=1-((pc+pi)/P); //efficiency in per units
31
32 //output

```

```
33 mprintf('the primary input current is %3.2f A : the
    secondary terminal voltage is %3.0f V and the
    efficiency of the transformer is %3.2f p.u. ',Ip,
    Vs,n)
```

---

**Scilab code Exa 9.13** calculation of secondary terminal voltage

```
1 clc
2 clear
3
4 //input
5 //all values refered to primary and from given
  equivalent circuit
6 v=240;//supply voltage in volts
7 r0=0.25;//resistance in ohms
8 x0=0.4;//reactance in ohms
9 r1=7.75;//load resistance in ohms
10 x1=5.6;//load reactance in ohms
11 n=5;//turns ratio of the transformer
12
13 //calculations
14 rt=r0+r1;//total resistance of the circuit in ohms
15 xt=x0+x1;//total reactance of the circuit in ohms
16 zt=((rt^2)+(xt^2))^0.5;//total impedance of
  transformer and the load in ohms
17 Ip=v/zt;//current in amperes
18 z1=((r1^2)+(x1^2))^0.5;//impedance of load in ohms
19 d=Ip*z1;//voltage drop across referred load
  impedance in volts
20 vs=n*d;//secondary terminal voltage in volts
21
22 //output
23 mprintf('the secondary terminal voltage is %3.0f V',
  vs)
```

---

# Chapter 10

## synchronous and asynchronous machines

Scilab code Exa 10.1 determination of emf between ends of a coil

```
1  clc
2  clear
3
4  //input
5  p=4; //number of poles of an alternator
6  w=50*pi; //angular velocity in rad/sec
7  b=0.015; //sinusoidal flux per pole in weber
8  phi=10*(pi/180); //pole pitch in radians
9  kf=1.11; //form factor
10
11 //calculations
12 f=(w*(p/2))/(2*pi); //frequency in hertz
13 e=2*kf*b*f; //e.m.f. per conductor in volts
14 E=2*e*cos(phi/2); //total e.m.f. in volts
15
16 //ouput
17 mprintf('the e.m.f. between the ends of the coil is
           %3.1f V',E)
```

---

**Scilab code Exa 10.2** finding the emf between the ends of the series connected coils

```
1  clc
2  clear
3
4  //input
5  p=4; //number of poles
6  n=48; //number of slots
7  b=0.02; //fulx per pole in weber
8  w=50*(%pi); //angular velocity in rad/sec
9
10 //calculations
11 f=(w*(p/2))/(2*%pi); //frequency in hertz
12 phim=360/n; //mechanical angle in degrees
13 phie=phim*(p/2); //electrical angle in degrees
14 phiE=phie*(%pi/180); //electrical angle in radians
15 kd=(sin(2*(phiE/2)))/(2*sin(phiE/2)); //distribution
    factor and 2 is taken as we are calculating for 2
    coils
16 e=(p/2)*kd*4.44; //total e.m.f. for two coils in
    series in volts
17
18 //output
19 mprintf('the total e.m.f. for two coils in series is
    %3.1f V',e)
```

---

**Scilab code Exa 10.3** calculation of phase and line voltages

```
1  clc
2  clear
3
```

```

4 //input
5 p=6;//number of poles
6 n=72;//number of slots
7 n1=10;//conductors per slot
8 b=0.01;//flux per pole in weber
9 f=50;//frequency in hertz
10 phi=170;//pitch of coil in electrical degrees
11 kf=1.11;//form factor for sinusoidal forms
12
13 //calculations
14 n2=n/p;//number of slots per pole
15 n3=n2/3;//number of slots per pole per phase for 3
    phase system
16 phim=360/n;//mechanical angle between slots in
    degrees
17 phie=phim*(p/2);//electrical angle in degrees
18 phiE=phie*(%pi/180);//electrical angle in radians
19 kd=(sin(n3*(phiE/2)))/(n3*sin(phiE/2));//
    distribution factor
20 phis=(180-phi)*(%pi/180);//coil spam factor in
    radians
21 kc=cos(phis);//pitch factor in radians
22 e=2*kd*kc*kf*f*b*((n*n1)/3);//e.m.f. per phase in
    volts
23 vl=(3^0.5)*e;//line voltage for star connection in
    volts
24
25 //output
26 mprintf('the phase and line voltages are %3.0f V and
    %3.0f V respectively ',e,vl)

```

---

Scilab code Exa 10.4 calculation of torque produced

```

1 clc
2 clear

```

```

3
4 //input
5 p=4;//number of poles
6 n1=3;//number of phases
7 f=50;//frequency in hertz
8 inp=60;//input to the motor in kW
9 l=0.06;//losses in per units
10
11 //calculations
12 w=2*%pi*(f/(p/2));//angular velocity in rad/sec
13 t=(inp*1000)/w;//total torque produced in newton
    meter
14 tu=t-(t*l);//useful torque in newton meter
15
16 //calculations
17 mprintf('the total torque and the useful torque of
    the machine are %3.0f Nm and %3.0f Nm
    respectively ',t,tu)

```

---

**Scilab code Exa 10.5** determination torque produced

```

1 clc
2 clear
3
4 //input
5 p=2;//number of poles
6 v=415;//3 phase supply voltage in volts
7 n=3;//number of phases
8 x=0.6;//reactance of phase in ohms
9 f=50;//supply frequency in hertz
10 e=0.08;//resultant e.m.f. is 0.08 of supply voltage
11
12 //calculations
13 e1=(e*v)/(3^0.5);//resultant e.m.f. per phase in
    volts

```

```

14 i=e1/x;//current per phase in current
15 il=i;//line current in amperes
16 phi=(180/%pi)*atan(e);//load angle in degrees
17 the=(180-phi)/p;
18 PHI=cos(atan(e));//power factor
19 inp=(3^0.5)*v*PHI*il;//power input in watts
20 t=inp/(2*%pi*(f/(p/2)));//torque in newton meter
21
22 //output
23 mprintf('the total torque produced is %3.0f Nm',t)

```

---

**Scilab code Exa 10.6** finding the slip speed and the slip

```

1 clc
2 clear
3
4 //input
5 n=3;//number of phases
6 f=50;//frequency in hertz
7 w=96*(%pi);//angular velocity in rad/sec
8
9 //calculations
10 ws=(2*%pi*f)-w;//slip speed in rad/sec
11 s=ws/(2*%pi*f);//slip in per units
12
13 //output
14 mprintf('the slip speed is %3.2f rad/s and the slip
    is %3.2f p.u. ',ws,s)

```

---

**Scilab code Exa 10.7** finding the rotor speed and the frequency of rotor components

```

1 clc

```

```

2 clear
3
4 //input
5 p=6;//number of poles
6 n=3;//number of phases
7 f=50;//frequency in hertz
8 s=0.03;//slip in per units
9
10 //calculations
11 w=(2*%pi*f*60)/(n*2*%pi);//synchronous speed in rev/
    min
12 ws=s*w;//slip speed in rev/min
13 wr=w-ws;//rotor speed in rev/min
14 fs=(ws*n)/60;//frequency of rotor currents in
    amperes
15
16 //output
17 mprintf('the rotor speed will be %3.0f rev/min and
    the frequency of rotor currents will be%3.1f Hz',
    wr,fs)

```

---

**Scilab code Exa 10.8** calculation of slip rotor copper loss total torque and the efficiency

```

1 clc
2 clear
3
4 //input
5 p=4;//number of poles
6 f=50;//supply frequency in hertz
7 n=3;//number of phases
8 w=1440;//speed in rev/min
9 sl=1.5;//stator losses in kW
10 fl=1.2;//friction losses in kW
11 inp=60;//input to motor in kW

```



```

12
13 //calculations
14 N=(inp*f)/(p/2); //synchronous speed in rev/min
15 ns=N-w; //slip speed in rev/min
16 s=ns/N; //slip in per units
17 rinp=inp-sl; //rotor input in kW
18 rc=s*rinp; //rotor copper losses in kW
19 tr=(rinp*1000)/((N*2*pi)/60); //rotor torque in
    newton meter
20 rout=rinp-rc; //rotor output in kW
21 mout=rout-fl; //motor output in kW
22 eff=mout/inp; //efficiency of rotor in per unit
23
24 //output
25 mprintf('the slip is %3.2f p.u.:the rotor copper
    loss is %3.2f kW: the total torque is %3.0f Nm
    and the efficiency is %3.3f p.u.',s,rc,tr,eff)

```

---

**Scilab code Exa 10.9** calculation of rotor copper loss and the input and efficiency of the motor

```

1  clc
2  clear
3
4  //input
5  p=6; //number of poles
6  f=50; //frequency in hertz
7  n=3; //number of phases
8  t=160; //total torque in newton meter
9  fs=120; //slip frequency in cycles/min
10 tf=12; //torque lost in friction
11 sl=750; //stator losses in watts
12
13 //calculations
14 s=fs/(60*f); //slip in per unit

```

```

15 w=(2*pi*f)/n;//speed of motor in rad/sec
16 wr=w*(1-s);//rotor speed in rad/sec
17 rinp=t*w;//rotor input in watts
18 rc=s*rinp;//rotor copper losses in watts
19 sinp=rinp+sl;//stator input in watts
20 Sinp=sinp/1000;//stator input in kilowatts
21 tout=t-tf;//output torque in newton meter
22 pout=tout*wr;//power output in watts
23 eff=pout/sinp;//efficiency in per unit
24
25 //output
26 mprintf('the rotor loss is %3.0fW, the input to the
           motor is %3.2f kW and the motor efficiency is %3
           .2f p.u.',rc,Sinp,eff)

```

---

# Chapter 11

## electronics

**Scilab code Exa 11.1** determination of anode slope resistance the mutual conductance and the amplification factor

```
1  clc
2  clear
3
4  //input
5  va=120; //anode voltage in volts
6  vg1=-1; //grid voltage in volts
7  vg2=-2; //grid voltage for which another curve is
           drawn in volts
8  //given scale is vertical scale: anode current lmm
           =0.00025A and horizontal scale : anode voltage 1
           mm=2.5V
9  //from VI characteristics
10 i=0.00025; //current in amperes
11 v=2.5; //voltage in volts
12 CD=4;
13 BD=9;
14 EF=34;
15 CE=14.5;
16 //calculations
17 ra=(CD*v)/(BD*i*1000); //anode slope resistance in
```

```

    kilo ohms
18 gm=(EF*i*1000)/(vg1-vg2); //mutual conductance in
    millisiemens
19 u=(CE*v)/(vg1-vg2); //amplification factor
20
21 //ouput
22 mprintf('at the operational point the parameters of
    the valve are %3.2f kohms,%3.1f mS and %3.2f.',ra
    ,gm,u)

```

---

**Scilab code Exa 11.2** determination of the triode parameters

```

1  clc
2  clear
3
4  //input
5  va1=125; //anode voltage in volts
6  va2=100; //anode voltage in volts for which another
    curve is obtained
7  vg1=0; //grid voltage in volts
8  vg2=-1; //grid voltage in volts
9  //given scale is vertical scale: anode current lmm
    =0.0002A and horizontal scale : anode voltage lmm
    =0.1V
10 v=0.1; //voltage in volts from scale
11 //from given data
12 //for vg1 and va2
13 ia11=4.8; //current in milli amperes
14 ia12=3.2; //current in milli amperes
15 //for vg2 and va1
16 ia21=6.625; //current in amperes
17 ia22=5.0; //current in amperes
18
19 //calculations
20 ra=(va1-va2)/(ia21-ia11); //anode slope resistance in

```

```

        kilo ohms
21 gm=(ia21-ia22)/(vg1-vg2); //mutual conductance in
    millisiemens
22 u=(va1-va2)/(v-vg2); //amplification factor
23
24 //ouput
25 mprintf('at the operational point the parameters of
    the valve are %3.1f kohms,%3.3f mS and %3.1f.',ra
    ,gm,u)

```

---

**Scilab code Exa 11.3** finding the required anode voltage

```

1  clc
2  clear
3
4  //input
5  ia=0.002; //anode current in amperes
6  r1=5000; //resistance in ohms
7  vht=100; //anode voltage in volts
8
9  //calculations
10 va=vht-(ia*r1); //next anode voltage in volts to plot
    the characteistic curve
11
12 //output
13 mprintf('the next required anode voltage for
    plotting characteristic curve is %3.0fV ',va)

```

---

**Scilab code Exa 11.4** determination of operating points

```

1  clc
2  clear
3

```

```

4 //input
5 vht=100;//higher threshold voltage in volts
6 r11=5;//resistance of load in kilohms
7 r12=10;//load resistance in kilohms
8
9 //calculations
10 //for r11
11 //when va=0
12 ia1=vht/r11;//anode current in milliamperes
13 //when va=100
14 ia2=0;//since va=vht
15 //for r12
16 //when va=0
17 ia3=vht/r12;//anode current in milliamperes
18 //when va=100
19 ia4=0;//since va=vht
20 //two load lines are drawn on VI graph which
    coincides the anode characteristic curve at four
    points
21 //using the data given
22 //point 1
23 vg1=0;//grid voltage in volts
24 va1=71;//anode voltage in volts
25 i1=5.9;//anode current in milliamperes
26 //point 2
27 vg2=-2;//grid voltage in volts
28 va2=79;//anode voltage in volts
29 i2=4.3;//anode current in milliamperes
30 //point 3
31 vg3=0;//grid voltage in volts
32 va3=57;//anode voltage in volts
33 i3=4.3;//anode current in amperes
34 //point 4
35 vg4=-2;//grid voltage in volts
36 va4=68;//anode voltage in volts
37 i4=3.2;//anode current in amperes
38
39 //output

```

```

40 mprintf('for a load of 5kiloohm ,the operating points
    are \n vg=%3.0fV: va=%3.0fV ia=%3.1fmA \n vg=%3
    .0fV: va=%3.0fV ia=%3.1fmA \n for a load of 10
    kiloohms ,the operating points are \n vg=%3.0fV:
    va=%3.0fV ia=%3.1fmA \n vg=%3.0fV: va=%3.0fV ia=
    %3.1fmA ',vg1 ,va1 ,i1 ,vg2 ,va2 ,i2 ,vg3 ,va3 ,i3 ,vg4 ,va4
    ,i4)

```

---

**Scilab code Exa 11.5** finding the voltage amplification

```

1 clc
2 clear
3
4 //input
5 g=4;//mutual conductance of a triode in millisiemens
6 u=25;//amplification factor
7 l=20;//load in kilo ohms
8
9 //calculations
10 ra=u/g;//slope resistance in kilo ohms
11 av=(u*l)/(ra+l);//voltage gain
12
13 //output
14 mprintf('with aload resistance of 20 kilo ohms this
    triode will give a voltage amplification of %3.2f
    ',av)

```

---

**Scilab code Exa 11.6** determination of ac voltage across the load

```

1 clc
2 clear
3
4 //input

```

```

5 rc=50;//resistance of the coil in ohms
6 lc=0.0005;//inductance of the coil in henry
7 //coil is connected in parallel with a capacitor
8 fr=0.5*(10^6);//resonance frequency in hertz
9 vl=1.5;//voltage across the load in volts
10 rs=50000;//slope resistance in ohms of the triode
11 u=25;//amplification factor of the triode
12
13 //calculations
14 c=(lc*(10^12))/((rc^2)+(2*%pi*fr*lc)^2);//
    capacitance in picofarad
15 rl=(lc*(10^9))/(rc*c);//resistance of load in
    kiloohms
16 a=(u*rl)/(rc+rl);//voltage amplification
17 e0=a*vl;//a.c. voltage across load in volts
18
19 //output
20 mprintf('at a frequency of 0.5MHz the a.c. voltage
    across the load will be %3.1fV in antiphase to
    the 1.5V in the grid circuit',e0)

```

---

**Scilab code Exa 11.7** calculation of input resistances

```

1 clc
2 clear
3
4 //input
5 ib1=-50;//base current in micro amperes
6 vce1=0;//emitter collector voltage in volts
7 ib2=-25;//base current in microamperes
8 vce2=6;//emitter collector voltage in volts
9 //locate a point at vce=0V and Ib=-50uA and draw
    tangent to it.
10 //from tangent co-ordinates
11 a1=150;

```



```

12 a2=87.5;
13 a3=75;
14 a4=25;
15 //locate a point at vce=6V and Ib=-25uA and draw a
    tangent to it.
16 //from the tangent co-ordinates
17 vbe1=200;//base emitter voltage in millivolts
18 vbe2=100;//base emitter voltage in millivolts
19 vbe3=50;//base emitter voltage in millivolts
20 vbe4=0;//base emitter voltage in millivolts
21
22 //calculations
23 ri=((a1-a2))/(a3-a4);//input resistance in kilo ohms
24 Ri=(vbe1-vbe2)/(vbe3-vbe4);//input resistance in
    kilo ohms
25
26 //output
27 mprintf('the input resistances for the specified
    conditions are %3.2f kilo ohms and %3.0f kilo
    ohms. ',ri,Ri)

```

---

**Scilab code Exa 11.8** determination of output resistances

```

1  clc
2  clear
3
4  //input
5  ib1=-100;//base current in micro amperes
6  vce1=10;//emitter collector voltage in volts
7  ib2=-50;//base current in microamperes
8  vce2=25;//emitter collector voltage in volts
9  //locate a point at vce=10V and Ib=-100uA and draw
    tangent to it.
10 //from tangent co-ordinates
11 a1=20;

```

```

12 a2=5;
13 a3=5.22;
14 a4=4.55;
15 //locate a point at vce=25V and Ib=-50uA and draw a
    tangent to it.
16 //from the tangent co-ordinates
17 vbe1=30;//base emitter voltage in millivolts
18 vbe2=20;//base emitter voltage in millivolts
19 vbe3=3.65;//base emitter voltage in millivolts
20 vbe4=2.9;//base emitter voltage in millivolts
21
22 //calculations
23 r0=((a1-a2))/(a3-a4);//input resistance in kilo ohms
24 R0=(vbe1-vbe2)/(vbe3-vbe4);//input resistance in
    kilo ohms
25
26 //output
27 mprintf('the output resistances for the specified
    conditions are %3.1f kilo ohms and %3.1f kilo
    ohms. ',r0,R0)

```

---

**Scilab code Exa 11.9** finding the parameters of the operating points

```

1  clc
2  clear
3
4  //input
5  ib=-10;//base current in microamperes
6  r1=6;//load resistance in kilo ohms
7  v=30;//supply voltage in volts
8
9  //calculations
10 //when vce=0V
11 ic=v/r1;//collector current in milliamperes
12 //when ic=0mA

```

```

13 vce=v; //collector emitter voltage in volts
14 //line AB where A(Vce=0V,Ic=5mA) and B(Vce=30V,Ic=0
    mA) cuts characteristic curve at point P
15 //from co-ordinates of P
16 Vce=16; //collector emitter voltage in volts
17 Ic=2.4; //collector current in milliamperes
18 ie=Ic+(-ib/1000); //emitter current in amperes
19
20 //output
21 mprintf('the parameters of the operating point under
    the conditions specified are Vce=%3.0fV,Ic=%3.1
    fmA and Ie=%3.2f mA ',Vce,Ic,ie)

```

---

**Scilab code Exa 11.10** calculation of current gain

```

1 clc
2 clear
3
4 //input
5 r1=10; //load resistance in kilohms
6 //for Ie= 0 ,0.8,2.0,2.8,4.0 Ic
    =0,0.78,1.95,2.73,3.9 respectively in mA
7 //taking any two set of values
8 ic1=3.9;
9 ic2=0;
10 ie1=4;
11 ie2=0;
12
13 //calculations
14 cg=(ic1-ic2)/(ie1-ie2); //current gain
15
16 //output
17 mprintf('the current gain is %3.3f',cg)

```

---

**Scilab code Exa 11.11** determination of collector emitter voltage and current gain

```
1  clc
2  clear
3
4  //input
5  //from the characteristics when Vce=15V
6  ic1=5; //collector current in milli amperes
7  ic2=2.8; //collector current in milli amperes
8  ib1=100; //base current in micro amperes
9  ib2=50; //base current in micro amperes
10
11 //calculations
12 b=((ic1-ic2)*1000)/(ib1-ib2); //current gain
13
14 //output
15 mprintf('when the collector-emitter voltage is 15V
    the current gain is %3.0f',b)
```

---

**Scilab code Exa 11.12** calculation of voltage and current gains

```
1  clc
2  clear
3
4  //input
5  rl=2.5; //resistance of load in kilo ohms
6  //from VI charecteristic curves
7  //for bias current of -10uA
8  vce1=21; //in volts
9  ic1=3.6; //in mA
10 ib1=-10; //in uA
```

```

11 //for bias current of -15uA
12 vce2=14.75;//in volts
13 ic2=6;//in mA
14 ib2=-15;//in uA
15 //from input characteristic curve
16 vbe1=0.75;
17 vbe2=0.45;
18 Ib1=40;
19 Ib2=0;
20
21 //calculations
22 b=((-ic2-(-ic1))*1000)/(ib2-ib1);//current gain
23 s=(vbe1-vbe2)/(Ib1-Ib2);//slope of curve
24 S=s*5;//for change in 5mV
25 v=(vce1-vce2)/S;
26
27 //output
28 mprintf('the voltage and current gains are %3.0f and
           %3.0f ',v,b)

```

---

**Scilab code Exa 11.13** calculation of voltage gain

```

1 clc
2 clear
3
4 //input
5 b=50;//current gain
6 rl=10;//load resistance in kilo ohms
7 rint=6.5;//internal resistance of an alternating
   source in kilo ohms
8 rinp=1;//input resistance in kilohms
9
10 //calculations
11 v=(rl*b)/(rint+rinp);//voltage gain
12

```

```
13 //output
14 mprintf('the voltage gain under given conditions
    will be %3.0f',v)
```

---

**Scilab code Exa 11.14** finding voltage gain when h parameters are given

```
1 clc
2 clear
3
4 //input
5 //given h-parameters of a junction transistor
6 hie=1000;//in ohms
7 hoe=100*(10^-6);//Sec
8 hre=0.0005;
9 hfe=50;
10 rl=10000;//load resistance in ohms
11
12 //calculations
13 Yt=hoe+(1/rl);
14 v=(1/((hie*(-Yt/hfe))+hre));//voltage gain and -
    signifies the 180 degree phase shift
15 vg=-v;
16 //output
17 mprintf('the voltage gain would be %3.0f',vg)
```

---

**Scilab code Exa 11.15** calculation of required load resistance

```
1 clc
2 clear
3
4 //input
5 //given h-parameters of a junction transistor
6 hie=1000;//in ohms
```

```
7 hoe=100*(10^-6); //Sec
8 hre=0.0005;
9 hfe=50;
10 cg=30; //current gain
11
12 //calculations
13 yl=(cg*hoe)/(hfe-cg); //load admittance in kilo mho
14 rl=1/(yl*1000); //load resistance in kilo ohms
15
16 //output
17 mprintf('to give a current gain of 30 the load would
    have to have a resistance of %3.2f kilo ohms',rl
    )
```

---