

Scilab Textbook Companion for
Op Amps and Linear Integrated Circuits
by J. M. Fiore¹

Created by
Sadhvi Sharma
Electronics and Communication
Electronics Engineering
Shri Mata Vaishno Devi University
College Teacher
None
Cross-Checked by
K. V. P. Pradeep

June 2, 2016

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Op Amps and Linear Integrated Circuits

Author: J. M. Fiore

Publisher: Cengage Learning, India

Edition: 1

Year: 2009

ISBN: 9788131512340

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introductory Concepts and Fundamentals	5
2 Operational Amplifier Internals	16
3 Negative Feedback	18
4 Basic Op Amp Circuits	21
5 Practical limitation of Op Amps circuits	30
6 Specialised Op Amps	40
7 Nonlinear circuits	45
8 Voltage regulation	55
9 Oscillators and Frequency Generators	62
10 Integrators and Differentiators	72
11 Active filters	81
12 Analog to Digital to Analog Conversion	89

List of Scilab Codes

Exa 1.1	Decibel power gain	5
Exa 1.2	Loss in dB	5
Exa 1.3	Ordinary power gain	6
Exa 1.4	Total dB gain	6
Exa 1.5	Gain	7
Exa 1.6	Output gain	7
Exa 1.7	Power in dBW	8
Exa 1.8	Output power in dBW and dBm	8
Exa 1.9	Output power in watts	9
Exa 1.10	Value in dBV	9
Exa 1.11	Output signal in dBV	10
Exa 1.12	The gain of amplifier in dB	10
Exa 1.13	Gain lost at 10 Hz	11
Exa 1.14	Phase Response	11
Exa 1.15	Gain and phase values at 1600000 Hz	12
Exa 1.16	The rise time for Lag network	12
Exa 1.17	Bode gain plot	13
Exa 1.18	Find current in the circuit	13
Exa 1.19	Find input output voltage gains	14
Exa 2.2	Square up circuit	16
Exa 3.1	Closed loop gain and break frequency	18
Exa 3.2	Design the amplifier	19
Exa 3.3	Input Output impedance	19
Exa 3.4	Amplifier current gain	20
Exa 4.1	Input Impedance and gain	21
Exa 4.2	Design an amplifier	21
Exa 4.3	Design a voltage follower	22
Exa 4.4	Input Impedance and Vout	22

Exa 4.5	Input Impedance and output voltage	23
Exa 4.6	Design an inverting amplifier	24
Exa 4.7	Minimum and maximum gain	24
Exa 4.8	Design the circuit	25
Exa 4.9	Load current	25
Exa 4.10	calculate R_i	25
Exa 4.11	Load Current	26
Exa 4.12	Design the amplifier	26
Exa 4.13	Output of summing amplifier	27
Exa 4.14	Determine the output of non inverting summer	28
Exa 4.15	Design the difference amplifier	29
Exa 5.1	Upper break frequency	30
Exa 5.2	Frequency response	30
Exa 5.3	Minimum acceptable funity	31
Exa 5.4	System gain and upper break frequency	31
Exa 5.5	System gain and upper break	33
Exa 5.6	Upper break requency	33
Exa 5.7	Does slewing occur	34
Exa 5.8	Minimum acceptable slew rate	35
Exa 5.9	Calculate new offset	35
Exa 5.10	Output voltage typically	36
Exa 5.11	Output drift	36
Exa 5.12	Output Voltage	37
Exa 5.13	Ripples in output	38
Exa 5.14	Output noise voltage	38
Exa 6.1	Output signal	40
Exa 6.2	Instrumentation amplifier	41
Exa 6.3	Power bandwidth	41
Exa 6.4	bandwidth required	42
Exa 6.5	Voltage controlled amplifier	42
Exa 6.6	Design an amplifier	43
Exa 6.7	Design a non inverting amplifier	44
Exa 7.1	Point at which led flashes	45
Exa 7.2	Capacitor voltage and time constant	45
Exa 7.3	Sketch V_{out}	46
Exa 7.4	Sketch the transfer curve	48
Exa 7.5	Draw the transfer curve	49
Exa 7.6	Temperature tranducer response characteristics	51

Exa 7.7	Sketch output waveform	52
Exa 7.8	Determine the Output voltage	53
Exa 7.9	Output Voltage	54
Exa 8.1	Output	55
Exa 8.2	The power dissipation	55
Exa 8.3	Value of R2	57
Exa 8.4	12 V Regulator	57
Exa 8.5	2V to 5V supply	58
Exa 8.6	Step down Voltage regulator	59
Exa 8.7	Heat sink rating	60
Exa 9.1	frequency of oscillation	62
Exa 9.2	Maximum and minimum frequency of oscillation	62
Exa 9.3	Frequency of oscillation	63
Exa 9.4	Value of Ri	64
Exa 9.5	Output frequency and amplitude	65
Exa 9.6	Square wave generator	65
Exa 9.7	Output frequency	66
Exa 9.8	Maximum and minimum frequency	66
Exa 9.9	Free running frequency	67
Exa 9.10	Timing resistor and capacitor	68
Exa 9.11	Square wave generator	69
Exa 9.12	range of output frequency	69
Exa 10.1	vout and lower frequency range	72
Exa 10.2	Output	72
Exa 10.3	Output of the circuit	73
Exa 10.4	Integrator connected to accelerometer	74
Exa 10.5	Range for differentiation	75
Exa 10.6	Output Waveform	76
Exa 10.7	Sketch the output wave form	77
Exa 10.8	LVDT	78
Exa 11.1	Butterworth low pass filter	81
Exa 11.2	Design second order bessel filter	82
Exa 11.3	Fifth order system	83
Exa 11.4	Crossover network	85
Exa 11.5	Band pass filter	86
Exa 11.6	Band pass filter with center frequency	87
Exa 11.7	Notch filter	87
Exa 12.1	determine the resolution	89

Exa 12.2	Determine the step size	90
Exa 12.3	sampling rates and no of bits	90

Chapter 1

Introductory Concepts and Fundamentals

Scilab code Exa 1.1 Decibel power gain

```
1 //Chapter 1
2 //Decibel Power gain
3 //page 14
4 //Example no 1-1
5 //Given
6 clc;
7 clear;
8 G=800;
9 G1=10*log10(G);
10 printf("\\n The decibel power gain ,G= %.2 f dB\\n",G1);
    // Result
```

Scilab code Exa 1.2 Loss in dB

```
1 // Chapter 1
2 //Loss expressed
```

```

3 //page 14
4 //Example no 1-2
5 //Given
6 clc;
7 G=1/10000;
8 G1=10*log10(G);
9 printf("\n The decibel power gain = %.0f dB\n",G1);
   // Result

```

Scilab code Exa 1.3 Ordinary power gain

```

1 // Chapter 1
2 //Ordinary power gain
3 //page 15
4 //Example no 1-3
5 //Given
6 clc;
7 G1=23;           //in dB
8 G=10^(G1/10);
9 printf("\n The ordinary power gain is %.4f \n",G);
   // Result
10 Pin=10^-3;      //in mW
11 Pout=Pin*G;
12 printf("\n The output power is %.4f mW \n",Pout);
   // Result

```

Scilab code Exa 1.4 Total dB gain

```

1 // Chapter 1
2 // Total gain
3 //page 15
4 //Example no 1-4
5 //Given

```

```

6  clc;
7  G1=10;      //in dB
8  G2=16;      //in dB
9  G3=14;      //in dB
10 Gt=G1+G2+G3; //total gain
11 printf("\n The ordinary power gain %.0f \n",Gt);
    // Result

```

Scilab code Exa 1.5 Gain

```

1  // Chapter 1
2  // Ordinary Gain
3  // page 16
4  // Example no 1-5
5  // Given
6  clc;
7  Ao=2;      //in Volt
8  Ai=50;     // in milliVolt
9  Ai1=0.05;  //input in Volt
10 Av=Ao/Ai1;
11 printf("\n The ordinary power gain %.0f \n ",Av); //
    Result
12 Av1=20*log10(Av);
13 printf("\n The power gain is %.2f dB\n",Av1);//
    Result

```

Scilab code Exa 1.6 Output gain

```

1  // Chapter 1
2  // Amplifier Gain
3  // page 17
4  // Example no 1-6
5  // Given

```

```

6  clc;
7  G1=26;      //in dB
8  Vin=0.01;   //in volt
9  G=10^(G1/20);
10 printf("\n The ordinary power gain %.2 f \n",G); //
    Result
11 Vout=Vin*G;
12 printf("\n The output voltage is %.4 f  V\n",Vout);
    // Result

```

Scilab code Exa 1.7 Power in dBW

```

1  // Chapter 1
2  //Power vin dBW
3  //page 17
4  //Example no 1-7
5  //Given
6  clc;
7  P=120;      //in Watt
8  P1=10*log10(P);
9  printf("\n The ordinary power gain %.1 f dBW \n",P1);
    //Result

```

Scilab code Exa 1.8 Output power in dBW and dBm

```

1  // Chapter 1
2  //Output power in dBW
3  //page 18
4  //Example no 1-8
5  //Given
6  clc;
7  clear;
8  P=0.200;    //in Watt

```

```

9 P1=10*log10(P/1);
10 printf("\n The ordinary power gain %.0 f dBW \n",P1);
    // Result
11 P=200;          //in mW
12 P1=10*log10(P/1);
13 printf("\n The ordinary power gain %.0 f dBm \n",P1);
    // Result

```

Scilab code Exa 1.9 Output power in watts

```

1 // Chapter 1
2 //Output power in Watt
3 //page 18
4 //Example no 1-9
5 //Given
6 clc;
7 P1=12;          // in dBw
8 Ref=1;         // in mW
9 P=10^(P1*Ref/10);
10 printf("\n The ordinary power gain %.1 f mW \n",P);
    // Result

```

Scilab code Exa 1.10 Value in dBV

```

1 // Chapter 1
2 //Output power
3 //page 18
4 //Example no 1-10
5 //Given
6 clc;
7 V=2;           // in V
8 Ref=1;         // in V
9 V1=20*log10(V/Ref);

```

```
10 printf("\n The value in dBV is %.2f dBV\n",v1);//  
    Result
```

Scilab code Exa 1.11 Output signal in dBV

```
1 // Chapter 1  
2 //Output signal  
3 //page 19  
4 //Example no 1-11  
5 //Given  
6 clc;  
7 clear;  
8 Vin=-42; // in dBV  
9 Av=35; //in dBV  
10 Vout=Vin+Av;  
11 printf("\n The output signal is %.0f dBV \n",Vout);  
    // Result
```

Scilab code Exa 1.12 The gain of amplifier in dB

```
1 // Chapter 1  
2 // Gain of the amplifier  
3 //page 19  
4 //Example no 1-12  
5 //Given  
6 clc;  
7 Pin1=20; //in dBm  
8 Pin=-10; //in dBW  
9 Pout=25; //in dBW  
10 G=Pout-Pin;  
11 printf("\n The gain of amplifer is %.0f dB",G);//  
    Result
```

Scilab code Exa 1.13 Gain lost at 10 Hz

```
1 // Chapter 1
2 //Gain lost
3 //page 23
4 //Example no 1-13
5 //Given
6 clc;
7 clear;
8 fc=40; //in Hz
9 f=10; //in Hz
10 Av=-10*log10(1+(fc^2)/(f^2));
11 printf("\n Gain lost is %.1f dB",Av);// Result
```

Scilab code Exa 1.14 Phase Response

```
1 // Chapter 1
2 //Phase response
3 //page 14
4 //Example no 1-14
5 //Given
6 clc;
7 fc=120; // in Hz
8 fc1=1200; // in Hz
9 fc2=12; // in Hz
10 w1=atan(fc/fc2);
11 printf("\n W1 = %.1f degrees one decade below fc\n ",
    w1*180/pi);// Result
12 w2=atan(fc/fc1);
13 printf("\n W2 = %.2f degrees one decade below fc\n",
    w2*180/pi);// Result
```

Scilab code Exa 1.15 Gain and phase values at 1600000 Hz

```
1 // Chapter 1
2 //page 15
3 //Example no 1-15
4 //Given
5 clc;
6 f=1.6*10^6;           //in Hz
7 fc=150*10^3;         //in Hz
8 Av=-10*log10(1+(f^2)/(fc^2));
9 printf("\n The Gain is %.1f dB \n ",Av); // Result
10 w=-(%pi/2)+atan(fc/f);
11 printf("\n Phase value is %.1f degree",w*180/%pi);
    // Result
```

Scilab code Exa 1.16 The rise time for Lag network

```
1 // Chapter 1
2 //Rise time
3 //page 29
4 //Example no 1-16
5 //Given
6 clc;
7 //f2=0.35/Tr;
8 f2=100*10^3;         //in kHz
9 Tr=0.35/f2;
10 printf("\n The rise time for 90 degree lag network
    is %.7f sec",Tr); // Result
```

Scilab code Exa 1.17 Bode gain plot

```
1 //Chapter 1
2 //page 30
3 //Example no 1-17
4 //figure 1.15
5 //Given
6 clc;
7 clear;
8 Avmidband=26;
9 f=(100:.5:40000+.5);
10
11 Av=[Avmidband*ones(200+.5:.5:10000-.5)];
12 for i=0:6/200:6
13 Av=[Avmidband-i Av]
14 end
15 for i=0:12/40000:12
16 Av=[Av Avmidband-i]
17 end
18 for i=0:6/20000:6
19 Av=[Av Avmidband-12-i]
20 end
21 x=ones(Av)
22 clf
23 gainplot(f,x)
24 plot(f,Av)
25 title('Gainplot for complete amplifier')
```

Scilab code Exa 1.18 Find current in the circuit

```
1 // Chapter 1
2 //page 34
3 //Example no 1-18
4 //figure 1.19
5 //tail current
```

```

6 //Given
7 clc;
8 Vcc=20;      //in Volt
9 Rc=3000;     //in Ohm
10 Rb=5000;    //in ohm
11 Rt=2000;    //in Ohm
12 Vee=10;     //in Volt
13 It=(Vee-0.7)/Rt;
14 printf("\n It =%.5 f Amp\n ",It); // Result
15 //Ie1=Ie2=It/2
16 Ic=It/2;
17 Vc=Vcc-Ic*Rc;
18 printf("\n Collector voltage is %.3 f V\n ",Vc); //
    Result
19 B=100;      //Assumption
20 Ib=Ic/B;
21 printf("\n Ib %.8 f Amp\n ",Ib); // Result
22 Vb=-Ib*Rb;
23 printf("\n Base Voltage %.5 f V\n ",Vb); // Result

```

Scilab code Exa 1.19 Find input output voltage gains

```

1 //Chapter 1
2 //page 40
3 //Example no 1-19
4 //Determine single ended output
5 //figure 1.20
6 //Given
7 clc;
8 Vcc=15;      //in Volt
9 Rc=8000;     //in Ohm
10 re=30;      //in ohm
11 Rt=10000;   //in Ohm
12 Vee=8;      //in Volt
13 It=(Vee-0.7)/Rt;

```

```
14 printf("\n It =%.5f Amp \n",It);// Result
15 Ie=It/2;
16 re1=(26*10^-3)/Ie;
17 printf("\n re1 =%.1f \n",re1);// Result
18 //for single ended output gain
19 Av=Rc/(2*(re1+re));
20 printf("\n Single output gain is %.1f \n",Av);//
    Result
21 printf("\n The diferential output gain is twice Av i
    .e. %.0f ",2*Av);// Result
```

Chapter 2

Operational Amplifier Internals

Scilab code Exa 2.2 Square up circuit

```
1 //chapter 2
2 //figure 2.13
3 //frequency counter
4
5 clc; clear;
6 t=(0:0.1:100)';
7
8 k = input('Enter the reference voltage between 0 to
          0.8= ');
9
10
11 f=0.1;
12 x3=1*sin(2*f*t);
13
14 x4=squarewave(2*f*t-k,50-10*k*%pi)
15 figure;
16
17 plot2d1(t,x3);
18 plot2d1(t,x4);
19 xlabel('time n—>');
20 ylabel('amplitude—>');
```

```
21 title('square wave at cutoff reference voltage');
```

Chapter 3

Negative Feedback

Scilab code Exa 3.1 Closed loop gain and break frequency

```
1 //Chapter 3
2 //Closed loop gain
3 //page 75
4 //Example no 3-1
5 //figure 3.4
6 clc;
7 clear;
8 Ao1=200;
9 f2_ol=10000; // in Hz
10 B=0.04;
11 Asp=Ao1/(1+B*Ao1);
12 printf("\n Asp %.2 f \n ",Asp); //Result
13 printf("\n Approximately Asp =1/B equal to %.0 f \n"
14 ,1/B); //result
14 S=Ao1/Asp;
15 printf("\n S =%.0 f \n",S);
16 f2_sp=f2_ol*S;
17 printf("\nf2_sp %.0 f Hz",f2_sp); //Result
```

Scilab code Exa 3.2 Design the amplifier

```
1 //Chapter 3
2 //page 76
3 //Example no 3-2
4 //figure 3.7
5 clear;
6 clc;
7 Asp=20
8 Asp=10^(Asp1/20);
9 printf("\n Asp =%.0f\n",Asp); //Result
10 //Rf/Ri=Asp-1;
11 printf("\n Rf/Ri=%.0f \n",Asp-1); //Result
12 printf("Rf must be 9 times larger than Ri. \n There
    are many possibilities "); //Result
```

Scilab code Exa 3.3 Input Output impedance

```
1 //Chapter 3
2 //page 82
3 //Example no 3-3
4 clc;
5 clear;
6 Zin_ol=300*10^3; //in Ohms
7 Zout=100; //in Ohms
8 Aol=50000;
9 Zout_ol=100;
10 Asp=100;
11 S=Aol/Asp;
12 printf("\n S = %.0f",S); //Result
13 Zin_sp=S*Zin_ol;
14 printf("\n Zin_sp = %.0f Ohm",Zin_sp); //Result
15 Zout_sp=Zout_ol/S;
16 printf("\n Zout_sp = %.1f Ohm",Zout_sp); //Result
```

Scilab code Exa 3.4 Amplifier current gain

```
1 //Chapter 3
2 //Output current of circuit
3 //page 88
4 //Example no 3-4
5 clc;
6 clear;
7 R1=9000;           // in Ohm
8 R2=1000;          //in Ohm
9 B=R2/(R1+R2);
10 printf("\\n B is %.2 f\\n",B); //Result
11 //Aps=1/B;
12 Aps=(R1+R2)/R2;
13 printf("\\n Aps = %.0 f \\n ",Aps); //Result
```

Chapter 4

Basic Op Amp Circuits

Scilab code Exa 4.1 Input Impedance and gain

```
1
2 clear;
3 clc;
4 close;
5 //page no 98
6 //figure 4.2
7 Rf=10*10^3;      ///In Ohms
8 Ri=1*10^3;      ///In Ohms
9 Av=1+(Rf/Ri);
10 disp(Av,"Gain of Circuit is")
```

Scilab code Exa 4.2 Design an amplifier

```
1 clc;
2 clear;
3 close;
4 //page no 98
5 //figure 4.3
```

```

6 Av1=26; //in dB
7 Av=20;
8 //Zi=47*10^3 //in ohms
9 Ri=1*10^3; //In Ohms
10 //we know Av=1+(Rf/Ri)
11 Rf=Ri*(Av-1);
12 disp(Rf," Value of Rf(ohm) when Ri is 1k");
13 Ri=2*10^3; //In Ohms
14 Rf=Ri*(Av-1);
15 disp(Rf," Value of Rf(ohm) when Ri is 1k")
16 Ri=5*10^2; //In Ohms
17 Rf=Ri*(Av-1);
18 disp(Rf," Value of Rf(ohm) when Ri is 1k")

```

Scilab code Exa 4.3 Design a voltage follower

```

1
2 clc;
3 clear;
4 close;
5 //pagec no 99
6 //figure 4.4
7 Av=1;
8 //Av=1+(Rf/Ri)
9 //Rf/Ri=Av-1=0
10 disp("Rf/Ri=0 ");
11 disp("Rf is replaced by short circuiting wire and Ri
      can have any theoretical value")
12 disp("When Ri is infinite it can be deleted from
      circuit");

```

Scilab code Exa 4.4 Input Impedance and Vout

```

1  clc;
2  clear;
3  close;
4  //pagec no 100
5  Rf=14*10^3; //in ohm
6  Ri=2*10^3; //in ohm
7  Av1=1+(Rf/Ri);
8  disp(Av1,"Av1 is");
9  Av3=20*log10(Av1);
10 disp(Av3,"Av1 in dB is");
11
12 Rf=18*10^3; //in ohm
13 Ri=2*10^3; //in ohm
14 Av2=1+(Rf/Ri);
15 disp(Av2,"Av2 is");
16 Av4=20*log10(Av2);
17 disp(Av4,"Av2 dB is ");
18 Avt=Av3+Av4;
19 disp(Avt,"Total Gain dB Av1+Av2 is");
20 vin=-30; //in dB
21 vout=Avt+vin;
22 disp(vout,"Vout in dB ");

```

Scilab code Exa 4.5 Input Impedance and output voltage

```

1  clc;
2  clear;
3  close;
4  //pagec no 102
5  Ri=5*10^3; // in ohm
6  Rf=20*10^3; // in ohm
7  vin=100*10^-3; //In volt
8  Av=-(Rf/Ri);
9  vout=vin*Av;
10 disp(" Volt",vout," Vout is ");

```

```
11 disp(" (i.e. negative sign means inverted)");
```

Scilab code Exa 4.6 Design an inverting amplifier

```
1 clc;
2 clear;
3 close;
4 //pagec no 103
5 Ri=15*10^3;
6 zin=Ri;
7 Av=-10; //inverting amplifier gain
8 //Av=-(Rf/Ri)
9 Rf=Ri*-Av;
10 disp("ohm" ,Rf , " Value for Rf ");
```

Scilab code Exa 4.7 Minimum and maximum gain

```
1 clc;
2 clear;
3 close;
4 //pagec no 103
5 //capacitors are used to remove higher frequencies
6 Rf=200*10^3; //In Ohm
7 Ri=15*10^3; //In Ohm
8 Av=-(Rf/Ri);
9 Av1=20*log10(-Av);
10 disp(Av,"Maximum gain is ");
11 disp(Av1,"Maximum gain in dB is ");
12 Av2=0; // divider action makes Ri infinite
13 disp(Av2,"Minimum gain in dB is ");
```

Scilab code Exa 4.8 Design the circuit

```
1 clc ;
2 clear ;
3 close ;
4 //pagec no 105
5 //Figure 4.6
6 Iin=50*10-6; //In Ampere
7 Vout=4; //In Volt
8 Rf=Vout/Iin;
9 disp("ohm",Rf," Transresistance of Circuit is");
```

Scilab code Exa 4.9 Load current

```
1 clc ;
2 clear ;
3 close ;
4 //pagec no 107
5 //Figure 4.13
6 Ri=20*103; //In Ohm
7 Vin=0.4; //In Volt
8 Rl=1*103; //In ohm
9 gm=1/Ri; //unit-micro*Siemens
10 Iload=gm*Vin;
11 disp("A",Iload," Load current is");
12 //maximum current is 20microAmp in Op Amp
13 Vout=(Ri+Rl)*Iload;
14 disp("V",Vout," V max ");
```

Scilab code Exa 4.10 calculate Ri

```
1 clc ;
2 clear ;
```

```

3 close;
4 //figure 4.15
5 //pagec no 107
6 //Figure 4.15
7 Iload=100*10-6; //In Amp
8 Vin=10; //In Volt
9 gm=Iload/Vin;
10 Ri=1/gm;
11 disp("ohm",Ri," Value of Ri")

```

Scilab code Exa 4.11 Load Current

```

1 clc;
2 clear;
3 close;
4 //pagec no 111
5 //Figure 4.17
6 Iin=5*10-6; //In Ampere
7 Ri=33*103; //In Ohm
8 Rf=1*103; //In Ohm
9 Rload=10*103; //In Ohm
10 Ai=1+(Ri/Rf); //for inverting current
    amplifier
11 Iout=Ai*Iin;
12 disp("A",Iout," I out ");
13 Vmax=Iout*Rload+Iin*Ri;
14 disp("V",Vmax,"Vmax is");
15 disp("(No problem)")

```

Scilab code Exa 4.12 Design the amplifier

```

1 clc;
2 clear;

```

```

3 close;
4 //pagec no 111
5 //Figure 4.18
6 Ai=50;
7 Rl=200*10^3;           //In Ohm
8 //Ai=1+(Ri/Rf)
9 Rf=1*10^3;           //In Ohm(Assumption)
10 Ri=Rf*(Ai-1);
11 disp("ohm",Ri,"Ri for Rf 1000ohm");
12 Rf=2*10^3;           //In Ohm(Assumption)
13 Ri=Rf*(Ai-1);
14 disp("ohm",Ri,"Ri for Rf 2000ohm");
15 Rf=0.5*10^3;        //In Ohm(Assumption)
16 Ri=Rf*(Ai-1);
17 disp("ohm",Ri,"Ri for Rf 500ohm");
18 Imax=13.5/Rl;
19 disp("A",Imax,"Resulting current");
20 disp("A",Imax/50,"Maximum allowable input current ")
    ;

```

Scilab code Exa 4.13 Output of summing amplifier

```

1 clc;
2 clear;
3 close;
4 //pagec no 113
5 //Figure 4.20
6 //Noninverting Amplifier
7 Rf=10*10^3;           //In Ohm(Assumption)
8 //Channel 1
9 Ri1=4*10^3;           //In Ohm(Assumption)
10 Vi1=1;               //In Volt
11 Av1=-Rf/Ri1;
12 Vo1=Av1*Vi1;
13 disp("V",Vo1,"Vout1");

```

```

14 //Channel 2
15 Ri2=2*10^3; //In Ohm(Assumption)
16 Vi2=-2; //In Volt
17 Av2=-Rf/Ri2;
18 Vo2=Av2*Vi2;
19 disp("V",Vo2,"Vout2");
20 //Channel 3
21 Ri3=1*10^3; //In Ohm(Assumption)
22 Vi3=0.5; //In Volt
23 Av3=-Rf/Ri3;
24 Vo3=Av3*Vi3;
25 disp("V",Vo3,"Vout1")
26 disp("V",Vo1+Vo2+Vo3,"Total output via summation is
")

```

Scilab code Exa 4.14 Determine the output of non inverting summer

```

1 clc;
2 clear;
3 close;
4 //pagec no 116
5 //Figure 4.22
6 //Noninverting Amplifier
7 V1=1; //In Volt
8 V2=-0.2; //In Volt
9 //to draw graph of V3
10 step=0.5;
11 t=0:step:10*%pi;
12
13 V3=2*sin(100*t); //In Volt
14 R1=20*10^3; //In ohm
15 R2=20*10^3; //In ohm
16 R3=20*10^3; //In ohm
17 Rf=20*10^3; //In ohm
18 Ri=5*10^3; //In ohm

```



```

19 //Vout=(1+(Rf/Ri))*(V1+V2+V3)/3;
20 Vout=(1+(Rf/Ri))*(V1+V2)/3;      //for DC componet in
    Vin
21 Voutac=(1+(Rf/Ri))*(V3)/3;      //for ac componet in
    Vin
22 disp("Output Voltage is 3.33 V peak sine wave riding
    on 1.33 V DC");
23 plot(Voutac+Vout);
24 xtitle("Output" ,"t" ,"V")

```

Scilab code Exa 4.15 Design the difference amplifier

```

1  clc;
2  clear;
3  close;
4  //pagec no 118
5  //Figure 4.27
6  Ri=10*10^3;      //In ohm
7  Av=26;          //In dB
8  Av1=10*log10(Av);
9  Rf1=Av1*Ri;
10 //Rf1=20*Ri1;
11 //Ri1+20*Ri1=Ri;
12 //Ri1=Ri-Rf1;
13 Ri1=Ri/21;
14 Rf1=20*Ri1;
15 disp("ohm" ,Rf1 ," Rf1 is ")

```

Chapter 5

Practical limitation of Op Amps circuits

Scilab code Exa 5.1 Upper break frequency

```
1 //Chapter 5
2 //page 135
3 //Example no 5-1
4 clc;
5 clear;
6 G=20;           //in dB
7 A=10^(G/20);   //Ordinary gain
8 GBW=1*10^6;    //in Hz (from datasheet)
9 f2=GBW/A;
10 printf("Uper break frequency %.0 f Hz",f2);
```

Scilab code Exa 5.2 Frequency response

```
1 //Chapter 5
2 //page 135
3 //Example no 5-2
```

```

4 //Given
5 clc;
6 clear;
7 Rf=10000;          //in Ohm
8 Ri=2000;          //in Ohm
9 Av=-Rf/Ri;
10 printf("\n Av  = %.0 f ",Av); //Result
11 Av1=20*log10(-Av);
12 printf("\n Av in %.0 f dB",Av1); //Result
13 //for noise gain
14 An=1+Rf/Ri;
15 printf("\n Anoise =%.0 f ",An); //Result

```

Scilab code Exa 5.3 Minimum acceptable funity

```

1 //clear//
2 //Example5.3:Finimum acceptable frequency
3 //Page 138
4 //figure 5.5
5 clear;
6 clc;
7 Rf=20000;          //in Ohms
8 Ri=500;           //in Ohms
9 f2=50*10^3;       //In Hz
10 Anoise=1+(Rf/Ri);
11 disp(Anoise," Anoise");
12 funity=Anoise*f2;
13 disp("Hz",funity," funity");
14
15 disp("For this application 741 would not be fast
      enough, therefore 411 would be fine");

```

Scilab code Exa 5.4 System gain and upper break frequency

```

1 // clear //
2 //Example5.4: System gain and upper break frequency
3 //Page 140
4 //figure 5.6
5 clear;
6 clc;
7 //STAGE 1
8 disp("Stage 1");
9 Rf1=14000; //in Ohms
10 Ri1=2000; //in Ohms
11 Av1=1+(Rf1/Ri1);
12 disp(Av1,"Av");
13 Anoise1=1+(Rf1/Ri1);
14 disp(Anoise1,"Anoise");
15 GBW=1*10^6; //in Hz (from Datasheet)
16 f1=GBW/Anoise1;
17 disp(f1,"f2");
18
19 //STAGE 2
20 disp("Stage 2");
21 Rf2=20000; //in Ohms
22 Ri2=10000; //in Ohms
23 Av2=-(Rf2/Ri2);
24 disp(Av2,"Av");
25 Anoise2=1+(Rf2/Ri2);
26 disp(Anoise2,"Anoise");
27 GBW=1*10^6; //in Hz (from Datasheet)
28 f2=GBW/Anoise2;
29 disp(f2,"f2");
30
31 //STAGE 3
32 disp("Stage 3");
33 Rf3=12000; //in Ohms
34 Ri3=4000; //in Ohms
35 Av3=1+(Rf3/Ri3);
36 disp(Av3,"Av");
37 Anoise3=1+(Rf3/Ri3);
38 disp(Anoise3,"Anoise");

```

```

39 GBW=1*10^6;           //in Hz (from Datasheet)
40 f3=GBW/Anoise3;
41 disp(f3,"f2");
42
43 //SYSTEM
44 Av=Av1*Av2*Av3;
45 disp(Av,"Av");
46
47 disp("Dominant break frequency here is 125kHz");
48 GBW=f1*64;
49 disp(GBW,"Gain bandwidth product is");

```

Scilab code Exa 5.5 System gain and upper break

```

1 //clear//
2 //Example5.5: System gain and upper break frequency
3 //Page 142
4 clear;
5 clc;
6 Anoise=10;
7 funity=4*10^6;           //in Hz
8 f2=funity/Anoise;
9 disp(f2,"f2");
10 n=3;
11 f2_system=f2*(2^(1/n)-1)^0.5;
12 disp(f2_system,"f2_system");

```

Scilab code Exa 5.6 Upper break requeryency

```

1 //clear//
2 //Example5.6: design a circuit with upper break
  frequency
3 //Page 142

```

```

4 clear;
5 clc;
6 Av1=26;      //in dB
7 Av=20;      //ordinary gain
8 f2=500*10^3; //in Hz
9
10 funity=f2*Av; // (Anoise=Av for non inverting
    terminal)
11 disp("Hz",funity,"funity")
12 //411 has funity =4MHZ ,therefore atleast 2 stages
    would be required
13 //Stage 1
14 f411=4*10^6; //in hz
15 Av1=f411/f2;
16 disp(Av1,"Av");
17 //To achive gain of 20 second stage should have gain
    of atleast Av2=2.5
18 Av2=2.5;
19 f2=f411/Av2;
20 disp("Hz",f2,"f2");

```

Scilab code Exa 5.7 Does slewing occur

```

1 //clear//
2 //Example5.7:" is 741's power bandwith atleast 3kHz""
3 //Page 148
4 //figure 5.6
5 clear;
6 clc;
7 slewrate=0.5/10^-6; // in V/S
8 Vp=12; //in Volts
9 fmax=slewrate/(2*%pi*Vp);
10 disp("Hz",fmax,"Fmax");
11 //Result

```

Scilab code Exa 5.8 Minimum acceptable slew rate

```
1 //clear//
2 //Example5.8:" minimum acceptable rate for 741""
3 //Page 149
4 //figure 5.6
5 clear;
6 clc;
7 fmax=20000; //in Hz
8 Vp=10; //in Volts
9 slewrate=fmax*(2*%pi*Vp);
10 disp("V/S",slewrate,"Slew rate ");
11 ///Result in V/S
```

Scilab code Exa 5.9 Calculate new offset

```
1 //clear//
2 //Example5.9:" Typical offset voltage""
3 //Page 157
4 //figure 5.9
5 clear;
6 clc;
7 Rf=10000; // in Ohm
8 Ri=1000; //in ohm
9 Roff=0; //in ohm
10 Anoise=1+Rf/Ri;
11 disp(Anoise," Anoise");
12 Vos=0.5*10^-3; //in Volt
13 Ios=10*10^-9; //in Amp
14 Ib=800*10^-9; //in Amp
15 Vout=(Vos*Anoise)+(Ib*Roff*Anoise+Ib*Rf);
16 disp("V",Vout," Vout");
```

```

17
18 Roff=Ri*Rf/(Rf+Ri);
19 Vout=(Vos*Anoise)+(Ios*Rf);
20 disp("V",Vout," Vout_offset");
21 //result

```

Scilab code Exa 5.10 Output voltage typically

```

1
2 //clear//
3 //Example5.10:" Output voltage"
4 //Page 158
5 //figure 5.24
6 clear;
7 clc;
8 Rf=20000; // in Ohm
9 Ri=5000; //in ohm
10 Av=-Rf/Ri;
11 Vin=3*10^-3; //in Volt
12 Vout=Av*Vin;
13 disp("V",Vout," Vout");
14
15 //411 typical apeecs
16 Vos=0.8*10^-3; //in Volt
17 Ios=25*10^-12; //in Amp
18 Ib=50*10^-12; //in Amp
19 Anoise=1+Rf/Ri;
20 Roff=0;
21 Vout=(Vos*Anoise)+(Ib*Roff*Anoise+Ib*Rf);
22 disp("V",Vout," Vout");
23 //Result

```

Scilab code Exa 5.11 Output drift


```

1
2 //clear//
3 //Example5.11:" Output Drift""
4 //Page 161
5 //figure 5.23
6 clear;
7 clc;
8 Roff=909;           //in Ohm
9 Rf=10000;          //in Ohm
10 Anoise=11;
11 DT=55;             //degree Celsius
12 DVbyDT=5*10^-6;   // V/C
13 DInoisebyDT=200*10^-12; // A/C
14 Vdrift=(DVbyDT*DT*Anoise)+(DInoisebyDT*DT*Rf);
15 disp("V",Vdrift," Vdrift");
16 Av=Anoise;
17 Vdriftin=Vdrift/Av;
18 disp("V",Vdriftin," Vdriftinput");

```

Scilab code Exa 5.12 Output Voltage

```

1 //Example5.12:" Output "
2 //Page 163
3 clear;
4 clc;
5 Av=20;             //in dB
6 Vin=-60;           //in dBV
7 CMRR=-90;          //in dB
8 //for differential input
9 Vout=Av+Vin;
10 disp("dBV",Vout," Vout for differential mode input");
11 //for common mode input
12 Vout1=Vout+CMRR;
13 disp("dBV",Vout1," Vout for common mode signal");
14 //This signal is so small that it is overshadowed by

```

Scilab code Exa 5.13 Ripples in output

```
1 //Example5.13:"How much Ripples is seen in output"
2 //Page 164
3 clear;
4 clc;
5 PSRR=86;           //in dB
6 Vripple=0.5;      //in Volt
7 Psrr=10^(PSRR/20);
8 disp(Psrr,"PSRR ordinary value");
9 Vout=Vripple/Psrr;
10 disp("Vpp",Vout,"Vout_ripple ");
11 //result//
```

Scilab code Exa 5.14 Output noise voltage

```
1 //Example5.14:"Output noise voltage"
2 //Page 167
3 //figure 5.29
4 clear;
5 clc;
6 Rf=99000;         // in Ohm
7 Ri=1000;          //in ohm
8 Rs=100;           //in ohm
9 Av=1+Rf/Ri;
10 disp(Av,"Av ordinary value");
11 disp(20*log10(Av),"Av dB value");
12 Anoise=Av;       //for non inverting amplifier
13 Rnoise=Rs+Rf*Ri/(Rf+Ri);
14 disp("Ohm",Rnoise,"Rnoise");
15
```

```

16 T=300;           //Given in degree cel.
17 K=1.38*10^-23;  //Boltzmann's constant
18 Vind=4*10^-9;   //In V/Hz
19 Iind=0.6*10^-12; //in A/Sqrtof Hz
20 eth=(4*K*T*Rnoise)^0.5; //sqared the
21 etot=((Vind^2)+(Iind*Rnoise)^2 +eth^2)^0.5;
22 disp("V/(Hz)^0.5",etot,"etotal");
23
24 funity=10*10^6; //in Hz
25 f2=funity/Anoise;
26 disp("Hz",f2,"f2");
27 BWnoise=f2*1.57;
28 disp("Hz",BWnoise,"BWnoise");
29
30 en=etot*(BWnoise)^0.5;
31 disp("V",en,"en");
32
33 en_out=en*Anoise;
34 disp("V",en_out,"en_out");
35
36 //for a nominal output signal of 1V RMS signal to
   noise ratio is
37 signal=1; //in V
38 Noise=en_out;
39 S_N=signal/Noise;
40
41 disp(S_N,"Signal to Noise ratio "); //
   answer in book is approxmately
42 disp(20*log10(S_N),"S/N in dB");
43 //Result

```

Chapter 6

Specialised Op Amps

Scilab code Exa 6.1 Output signal

```
1 //Example6.1:" Output signal""
2 //Page 176
3 //figure 6.4
4 clear;
5 clc;
6 R1=20000; //in Ohm
7 R2=400; //in Ohm
8 Vinp=0.006; //in V (Vinp=Vin+)
9 Vinm=-0.006; //in V Vinp=Vin-)
10 Vh=0.010; //in V
11 Vad=Vinm*(1+R1/R2)-Vinp*R1/R2; //-----1
    equation Va=0.606mV approx
12 disp("V",Vad,"Va");
13 //for common mode
14 Vac=Vh*(1+R1/R2)-Vh*R1/R2;
15 disp("V",Vac,"Va");
16 Rf=50000; //in Ohm
17 Ri=10000; //in Ohm
18 Av=Rf/Ri;
19 disp(Av,"Av");
20 Va=-0.606; //V
```

```

21 Vb=-Va;
22 Voutd=Av*(Vb-Va);
23 disp("V",Voutd," Desired differential input signal is
      Vb-Va=");
24 Vout=(Vinp-Vinm)*(Rf/Ri)*(1+2*(R1/R2));
25 disp("V",Vout," By using equation 6.1 given in book
      Vout =(Vinp-Vinm)*(Rf/Ri)*(1+2*(R1/R2))=");
26 CMRR=10^5;
27 Av=505;
28 Vincm=10*10^-3;
29 Voutcm=Vincm*Av/CMRR;
30 disp("V",Voutcm," Vout (cm)")

```

Scilab code Exa 6.2 Instrumentation amplifier

```

1 //Example6.2:" Designing the Circuit""
2 //Page 180
3 //figure 6.9
4 clear;
5 clc;
6 Av=10;
7 Rg=(49.4*10^3)/(Av-1);
8 disp("Ohm",Rg," Rg")

```

Scilab code Exa 6.3 Power bandwidth

```

1 //Example6.3:" Determine the Power Bandwidth""
2 //Page 183
3 //figure 6.14
4 clear;
5 clc;
6 Vp=10;           //in V
7 Vcc=15;         //in V

```

```

8 Rf=50000;           //in Ohm
9 Ri=2000;           //in Ohm
10 Rset=3*10^6;      //in Ohm
11 Iset=(Vcc-0.5)/Rset;
12 disp("A",Iset," Iset")
13 Anoise=1+Rf/Ri;
14 disp(Anoise," Anoise");
15 funity=200000;    //in Hz
16 f2=funity/Anoise;
17 disp("Hz",f2," f2");
18 SR=0.11/10^-6;   //in V/S
19 fmax=SR/(2*%pi*Vp);
20 disp("Hz",fmax," fmax");
21 //Result//

```

Scilab code Exa 6.4 bandwidth required

```

1 //Example6.4:" Determine the approx Bandwidth"
2 //Page 191
3 clear;
4 clc;
5 Refresh=60;
6 Height=1024;
7 Width=1024;
8 Pixelrate=Refresh*Height*Width;
9 disp(" pixels per second",Pixelrate," Pixelrate");
10 Tr=1/Pixelrate;
11 f2=0.35/(0.3*Tr);
12 disp("Hz",f2," f2");
13 //Result//

```

Scilab code Exa 6.5 Voltage controlled amplifier

```

1 //Example6.5:"OTA use"
2 //Page 191
3 //figure 6.22
4 clear;
5 clc;
6 Vp=5;           //in V
7 Vm=-Vp;
8 Rcontrol=22000; //In Ohm
9 Vd=0.7;        //in V
10 Iabc=(Vp-Vm-Vd)/Rcontrol;
11 disp("A",Iabc,"Iabc");
12 //Using voltage divider
13 Loss=470/(33000+470);
14 disp(Loss,"Loss");
15 Vpp=0.050;    //in V
16 Vinmax=Vpp/Loss;
17 disp("V",Vinmax,"Vinmax");
18 gm=0.010;    //in S
19 Iout=Vpp*gm;
20 disp("A",Iout,"Iout");
21 //maximum output
22 Rf=22000;    //in Ohm
23 Vout=Iout*Rf;
24 disp("V",Vout,"Vout");
25 //result//

```

Scilab code Exa 6.6 Design an amplifier

```

1 //Example6.6:" design an Amplifier "
2 //Page 197
3 //figure 6.27
4 clear;
5 clc;
6 Av=-20;
7 Ri=50000;     //in Ohm

```

```

8 fc=100;           //in Hz
9 //Av=-Rf/Ri
10 Rf=-Av*Ri;
11 disp("Ohm",Rf," Value of Rf");
12 Rb=2*Rf;
13 disp("Ohm",Rb," Value of Rb");
14 C=1/(2*%pi*Ri*fc);
15 disp("F",C," Value of C");
16 //Result//

```

Scilab code Exa 6.7 Design a non inverting amplifier

```

1 //Example6.7:" design a non-inverting amplifier "
2 //Page 205
3 clear;
4 clc;
5 Av=20;           //in dB
6 Av1=10^(Av/20); //ordinary gain
7 Rf=1500;        //in Ohm (Assumption)
8 //Av=1+Rf/R we know
9 R=Rf/(Av1-1);
10 disp("Ohm",R,"R");
11 //Result//

```

Chapter 7

Nonlinear circuits

Scilab code Exa 7.1 Point at which led flashes

```
1 // Chapter7
2 //Example-7.1
3 //Figure 7.11
4 //page 216
5 clear;
6 clc;
7 R=10*10^6;           //in Ohm
8 C=10*10^-9;         //in Farad
9 T=R*C;              //discharge Time
10 printf("\n T %.1 f S\n",T);
11 Vled=2.5;           //in V
12 Vsat=13;            //in V
13 Rl=500;             //in Ohm
14 Iled=(Vsat-Vled)/Rl;
15 printf("\n Iled %.3 f A\n",Iled);
16 //result//
```

Scilab code Exa 7.2 Capacitor voltage and time constant

```

1 // Chapter7
2 //Example-7.2
3 //Figure 7.24
4 //page 222
5 clear;
6 clc;
7 R2=1.5*10^3; //in Ohm
8 R1=10*10^3; //in Ohm
9 Vcc=15; //in V
10 Vpm=1; //in V (=Vp-)
11 C=10*10^-9; //in Farad
12
13 Vofst=Vcc*R2/(R1+R2);
14 printf("\n Voffset %0.2f V",Vofst);
15 Vc=Vofst+Vpm;
16 printf("\n Vc %0.2f V",Vc);
17 Rl=10*10^6; //in Ohm
18 T=Rl*C; //discharge Time
19 printf("\n T %0.2f S",T);
20 Vinp=1.96;
21 Vinm=5.96;
22 Vind=Vinp-Vinm;
23 printf("\n Vin_diff =%0.0f V \n ",Vind);
24 //Graph
25 t=(0:0.01:5)';
26 f=1; //1kHz
27 Vin=2*sin(f*pi*t);
28 Vin1=Vin^2-1;
29 Vout=Vin1+2.96;
30 clf;
31 plot(t,Vout,t,Vin1)
32 xtitle("Green Input signal & Blue Output signal",t
33 "","Vin");//result
33 xgrid;

```

Scilab code Exa 7.3 Sketch Vout

```
1 // Chapter7
2 // Page.No-226
3 // Example7_3
4 //page 226
5 // Output waveform of zener limits Diodes
6 // Given
7 clc;
8 clear;
9 Rf=20*10^3;           //in Ohm
10 Ri=10*10^3;          //in Ohm
11 Av=-Rf/Ri;
12 Vin=4;               //in V
13 Vout=Av*Vin;
14 printf("\n Vout = %0.0f V(peak)",Vout);
15 Vzener=5.1;         //in V
16
17 Vlimit=(Vzener+0.7);
18 printf("\n Vlimit +_%.1f V",Vlimit);
19 //graph
20
21 T0=4;
22 t=-5.99:0.01:6;
23 t_temp=0.01:0.01:T0/4;
24 s=length(t)/length(t_temp);
25 dx=[];
26 x=[];
27 for i=1:s
28     if modulo(i,2)==1 then
29         dx=[dx -ones(1,length(t_temp))];
30         x=[x .1*t_temp($:-1:1)];
31     else
32         dx=[dx ones(1,length(t_temp))];
33         x=[x .1*t_temp];
34     end
35 end
36 clf();
```

```

37 k=-(-80*2*x)-8; //function for output plot
38 x1=[] //function for clipped output
39 for c=1:length(x)
40     if k(c) < -5.8 then
41         x1(c)=-5.8;
42     else
43         if k(c)<5.8 then
44             x1(c)=k(c);
45         else
46             x1(c)=5.8
47         end
48     end
49 end
50 plot(t-1.5,-80*x+4,t-1.5,k,t-1.5,x1);
51 xtitle("Input (Blue) / Output (Green/Red for
        clipped ) waveform");
52
53 xgrid;

```

Scilab code Exa 7.4 Sketch the transfer curve

```

1 // Chapter7
2 // Page.No-229
3 // Example7_4
4 // Sketch the Transfer Curve
5 // Given
6 clc;
7 clear;
8 Vz=3.9; //in V
9 Rf=20000; //in Ohm
10 Ri=5000; //in Ohm
11 Ra=10000; //in Ohm
12 Vbreak=Vz+0.7;
13 printf("\n Vbreak +- %.2 f V",Vbreak);
14

```

```

15 Av=-Rf/Ri;
16 printf("\n Av %.2 f ",Av);
17
18 Av2=(-Rf*Ra/(Rf+Ra))/Ri;
19 printf("\n Av2 %.2 f ",Av2);
20 //Graph
21 t=-4:0.001:4;
22 L=length(t);
23 for i=1:L
24     if t(i)<-1.15
25         x1(i)=Av2*t(i)+3.0705;
26
27
28     elseif t(i)<1.15
29         x1(i)=Av*t(i) ;
30
31
32     elseif t(i)>1.15
33         x1(i)=Av2*t(i)-3.0705 ;
34     end ;
35 end;
36 clf;
37 plot2d1(t,x1);
38 xtitle('Transfer Characteristics ','Vin','Vout')
39 xgrid;

```

Scilab code Exa 7.5 Draw the transfer curve

```

1 // Chapter7
2 // Page.No-231
3 // Example_7_5
4 // Sketch the Transfer Curve
5 // Given
6 clc;
7 clear;

```

```

8 Vz1=1;           //in V
9 Vz2=2.2;        //in V
10 Rf=12000;      //in Ohm
11 Ri=10000;     //in Ohm
12 R2=15000;     //in Ohm
13 R1=20000;     //in Ohm
14 Vbreak1=Vz1+0.7;
15 printf("\n Vbreak1_in +- %.2f V",Vbreak1);
16 Vbreak2=Vz2+0.7;
17 printf("\n Vbreak2_in +- %.2f V",Vbreak2);
18
19 Av=-Rf/Ri;
20 printf("\n Av %.1f ",Av);
21 Av1=-Rf*(Ri+R1)/(R1*Ri);
22 printf("\n Av1 %.1f ",Av1);
23
24 Av2=-Rf*(Ri*R1+R1*R2+R2*Ri)/(R1*Ri*R2);
25 printf("\n Av2 %.1f ",Av2);
26 Vbreak1_out=Av*Vbreak1
27 Vbreak2_out=Vbreak1_out+Av2*(Vbreak2-Vbreak1);
28 printf("\n Vbreak1_out %.2f V ",Vbreak1_out);
29 printf("\n Vbreak2_out %.2f V",Vbreak2_out);
30 //graph
31 t=-5:0.01:5;
32 L=length(t);
33 for i=1:L
34     //if t(i)< then
35     //end
36     if t(i)<-2.9 then
37         x1(i)=Av2*t(i)-3;
38     elseif t(i)<-1.15 then
39         x1(i)=Av1*t(i)-0.67;
40     elseif t(i)<1.15 then
41         x1(i)=Av*t(i) ;
42     elseif t(i)<2.9 then
43         x1(i)=Av1*t(i)+0.67 ;
44     elseif t(i)>2.9 then
45         x1(i)=Av2*t(i)+3;

```

```

46     end;
47 end;
48 clf;
49 plot2d1(t,x1);
50 xtitle('Transfer Characteristics ','Vin','Vout')

```

Scilab code Exa 7.6 Temperature transducer response characteristics

```

1 // Chapter7
2 // Page.No-232
3 // Example_7_6
4 // Sketch the Transfer Curve
5 // Given
6 clc;
7 clear;
8 Vz1=1;           //in V
9 Vz2=2.2;        //in V
10 Rf=10000;       //in Ohm
11 Ri=10000;      //in Ohm
12
13 Vz1p=3-0.7;
14 printf("\n Vz+in  %.2 f V",Vz1p);
15 Vz1m=-(4-0.7);
16 printf("\n Vz-in  %.2 f V",Vz1m);
17 //Ra || Rf=8k
18 Ra=8000*Rf/(Rf-8000);
19 Av2=0.8;
20 Av1=1;
21 //graph
22 t=-50:0.001:50;
23 L=length(t);
24 for i=1:L
25     if t(i)<-40 then
26         x1(i)=0.8*t(i)-8;
27     elseif t(i)<30+0.01 then

```

```

28         x1(i)=1*t(i);
29
30     elseif t(i)>30 then
31         x1(i)=0.8*t(i)+5.5;
32     end;
33 end;
34 clf;
35 plot2d1(t,x1);
36 xtitle('Transfer Characteristics','Vin','Vout')

```

Scilab code Exa 7.7 Sketch output waveform

```

1 // Chapter7
2 // Page.No-241
3 // Example7_4
4 // Sketch the output waveform
5 // Given
6 clc;
7 clear;
8 Vi=5;           //in V
9 Vsat=13;        //in V
10 R2=2000;        //in Ohm
11 R1=20000;       //in Ohm
12 Vupper=Vsat*R2/R1;
13 Vlower=-Vsat*R2/R1;
14 printf("\n Vupperthreshold  %.1f V",Vupper);
15 printf("\n Vlowerthreshold  %.1f V",Vlower);
16 t=(0:0.1:20)';
17 f=0.1;
18 x3=1*sin(2*f*%pi*t);
19 A=asin(Vupper);
20 k=atan(imag(A),real(A))
21
22
23 x4=squarewave(2*f*%pi*t-2*f*%pi*k,50)

```



```

24
25 plot(t,x3,t,x4);
26 //plot2d1();
27 xlabel('time n—>');
28 ylabel('Vout—>');
29 title('Input(Blue) / Output(Green)');
30 xgrid(color("grey"));

```

Scilab code Exa 7.8 Determine the Output voltage

```

1 // Chapter7
2 // Page.No-250
3 // Example7-8
4 // Determine the output voltage
5 //Figure 7.56
6 // Given
7 clc;
8 clear;
9 Vin=1; //in V
10 T=300; //in Kelvin
11 Ri=50000; //in Ohm
12 Is=30*10^-9; //in Amp
13 //Vout=-0.0259*ln(Vin/RiIs)
14 Vout=-0.0259*log1p(Vin/(Ri*Is))
15 printf("\n Vout when Vin=1V %.4 f V\n",Vout);
16 //for Vin=0.5V
17 Vin1=0.5; //in V
18 Vout1=-0.0259*log1p(Vin1/(Ri*Is))
19 printf("\n Vout when Vin=0.5V %.4 f V\n",Vout1);
20 //for Vin=2V
21 Vin2=2; //in V
22 Vout2=-0.0259*log1p(Vin2/(Ri*Is))
23 printf("\n Vout when Vin=2V %.4 f V",Vout2);

```

Scilab code Exa 7.9 Output Voltage

```
1 // Chapter7
2 // Page.No-253
3 // Example_7_9
4 // Determine the output voltage
5 //Figure 7.62
6 // Given
7 clc;
8 clear;
9 K=0.1;
10 t=(0:0.01:0.5)';
11 Vin=2*sin(2*60*%pi*t);
12 Vout=K*Vin^2;
13
14 plot(t,Vout,t,Vin)
15 xtitle(" Input (Green) signal & Output (Blue) signal
    ", "t", "V"); //result
```

Chapter 8

Voltage regulation

Scilab code Exa 8.1 Output

```
1 // Chapter8
2 // Page.No-263
3 // Example8_1
4 // Figure 8.4
5 // Output of Voltage and Current
6 // Given
7 clear;clc;
8 R1=5000;           //In Ohm
9 R2=20000;         //In Ohm
10 R3=10000;        //In Ohm
11 Vz=3.9;          //In V
12 V1=Vz*(R2+R3)/R3;
13 printf("\n Output Load Voltage V1 is = %.2f V\n",V1)
   ; // Result
14 Iz=(V1-Vz)/R1;
15 printf("\n Output Zener Current Iz is = %.5f A \n",
   Iz); // Result
```

Scilab code Exa 8.2 The power dissipation

```

1 // Chapter8
2 // Page.No-264
3 // Example8_2
4 // Figure 8.4
5 // Power dissipation for Q1
6 // Page.No-264
7 // Example_8_2
8 // Figure 8.4
9 // Given
10 clear;clc;
11 V1=11.7; //in V
12 R1=20; //in Ohm
13 I1=V1/R1;
14 printf("\n Output Load Current I1 is = %.3f A \n",I1
); // Result
15 Vc=20; Ve=11.7; //in V
16 Vce=Vc-Ve;
17 printf("\n Output Load Voltage Vce is = %.2f V\n",
Vce); // Result
18 Pd=I1*Vce;
19 printf("\n Power dissipation Pd is = %.2f W \n",Pd);
// Result
20 Ib=0.020; //in Amp
21 B=I1/Ib;
22 printf("\n Beta is = %.2f \n",B); // Result
23 P1=I1*V1;
24 printf("\n Power dissipation across load ,P1 is = %.3
f W \n",P1); // Result
25 Vin=20; //in V
26 Pin=I1*Vin; //Iin=I1
27 printf("\n Input Power dissipation ,Pin is = %.2f W \
n",Pin); // Result
28 n=P1/Pin;
29 printf("\n Efficiency is = %.3f or %.1f percent \
n",n,n*100); // Result

```

Scilab code Exa 8.3 Value of R2

```
1 // Chapter8
2 // Value of R2
3 // Page.No-272
4 // Example8_3
5 // Given
6 clear;clc;
7 Vm=1.25; //in V
8 Vout=15; //in V
9 R1=240; //in Ohm
10 R2=R1*((Vout/Vm)-1);
11 printf("\n Value for R2 is = %.2 f Ohm\n",R2); //
    Result
```

Scilab code Exa 8.4 12 V Regulator

```
1 // Chapter8
2 // 12V Voltage Regulator
3 // Page.No-279
4 // Example8_4
5 //Figure 8.17
6 // Given
7 clear;clc;
8 Vref=7.15; //in V
9 Vout=12; //in V
10 Ilimit=0.050; //in Amp
11 R2=10000; //in Ohm
12 R1=Vout*R2/Vref-R2;
13 printf("\n Value of R1 is = %.f Ohm\n",R1); //
    Result
14 Vsense=0.65; //in V
```

```

15 Rsc=Vsense/Ilimit;
16 printf("\n Value of current sense resistor is = %.f
    Ohm\n",Rsc); // Result
17 R3=R1*R2/(R1+R2);
18 printf("\n Value of minimum drift resistor is = %.f
    Ohm\n",R3); // Result

```

Scilab code Exa 8.5 2V to 5V supply

```

1 // Chapter8
2 // Design a contineously adjusted supply b/w 2V to
  5 V
3 // Page.No-279
4 // Example8_5
5 //Figure 8.15.1
6 // Given
7 clear;clc;
8 Vref=7.15; //in V
9 Vout=5; //in V
10 // $(R1b+R2)/R2=Vref/Vout$ ;
11 printf("\n For maximum case  $(R1b+R2)/R2$  is = %.2 f \n
    ",Vref/Vout); // Result
12 R2=1; // In Ohm (Assumption)
13 R1b=Vref/Vout-1;
14 printf("\n For  $R2=1$  Ohm  $R1b:R2$  is = %.2 f:%.0 f \n",
    R1b,R2); // Result
15 Voutm=2; // in V
16 printf("\n For maximum case  $(R1a+R1b+R2)/R2$  is = %.3
    f \n",Vref/Voutm); // Result
17 R1a=Vref/Voutm-1-0.43;
18 printf("\n For  $R2=1$  Ohm  $R1b:R2$  is = %.3 f:%.0 f \n",
    R1a,R2); // Result
19 R1a=10000; //in Ohm (Assumption)
20 R2=R1a/2.145;
21 printf("\n Value of  $R2$  is = %.f Ohm\n",R2); //

```

```

    Result
22 // Similarly
23 R1b=R2*0.43;
24 printf("\n Value of R1b is = %.f Ohm\n",R1b); //
    Result
25 // Ilimit=Vsense/rsc;
26 Vsense=0.65; //in V
27 Ilimit=1; //in Amp
28 Rsc=Vsense/Ilimit;
29 printf("\n Value of current sense resistor is = %.f
    Ohm\n",Rsc); // Result
30 R1=6000; //in Ohm
31 R3=R1*R2/(R1+R2);
32 printf("\n Value of minimum drift resistor is = %.f
    Ohm\n",R3); // Result
33 Ic=1; //in Amp
34 Ib=0.150; //in Amp
35 B=Ic/Ib;
36 printf("\n Value of B minimum = %.2 f \n",B); //
    Result

```

Scilab code Exa 8.6 Step down Voltage regulator

```

1 // Chapter8
2 // Design a step down regulator
3 // Page.No-288
4 // Example8_6
5 // Figure 8.27
6 // Given
7 clear;clc;
8 Vout=12; //in V
9 R2=10000; //in Ohm (Assumption)
10 R1=R2*(Vout-1);
11 printf("\n Value of R1 is = %.f Ohm\n",R1); //
    Result

```

```

12 Isw=0.75;                                //in Amp
13 R3=0.11/Isw;
14 printf("\n Value of R3 is = %.2 f Ohm\n",R3); //
    Result
15 Iout=0.200;                               //in Amp
16 Df=0.2;
17 delI =2*Iout*Df;
18 printf("\n Value of del I is = %.3 f Amp\n",delI); //
    Result
19 F=50000;                                  //in Hz
20 Vin=20;                                   //in V
21 L1=Vout*(Vin-Vout)/(delI*Vin*F);
22 printf("\n Value of L1 is = %.4 f H\n",L1); // Result
23 Vripple=0.040;                            //in V
24 C2=Vout*(Vin-Vout)/(8*F^2*Vin*Vripple*L1);
25 printf("\n Value of C2 is = %.6 f F\n",C2); // Result
26 //C2 is ste a standard of 33microF or 47microF

```

Scilab code Exa 8.7 Heat sink rating

```

1 // Chapter8
2 // Determine appropriate heat sink rating
3 // Page.No-296
4 // Example8_7
5 //Figure 8.34
6 // Given
7 clear;clc;
8 Tj=150;                                    // in degree C
9 Ta=40;                                     // in degree C
10 Qjc=3.0;                                  // in C/W
11 Qcs=1.6;                                  // in C/W
12 PD=6;                                     //in W
13 Qsa=(Tj-Ta)/PD - Qjc-Qcs;
14 printf("\n Value of Qsa = %.2 f C/W\n",Qsa); //
    Result

```


Chapter 9

Oscillators and Frequency Generators

Scilab code Exa 9.1 frequency of oscillation

```
1 // Chapter9
2 // Frequency of oscillation
3 // Page.No-306
4 // Example9_1
5 // Figure 9.8
6 // Given
7 clear;clc;
8 R=50000; //in Ohm
9 C=0.01*10^-6; //in F
10 f=1/(2*pi*R*C);
11 printf("\n The frequency of oscillation = %.0f Hz\n
    ",f); // Result
```

Scilab code Exa 9.2 Maximum and minimum frequency of oscillation

```
1 // Chapter9
```

```

2 // Maximum and minimum Frequency of oscillation
3 // Page.No-307
4 // Example9_2
5 //Figure 9.9
6 // Given
7 clear;clc;
8 // for minimum frequency
9 R=11100; //in Ohm
10 C=0.1*10^-6; //in F
11 f=1/(2*pi*R*C);
12 printf("\n The minimum frequency of oscillation = %
    .1f Hz\n",f); // Result
13 // for maximum frequency
14 R=1100; //in Ohm
15 C=0.1*10^-6; //in F
16 fm=1/(2*pi*R*C);
17 printf("\n The maximum frequency of oscillation = %
    .0f Hz\n",fm); // Result
18 printf("\n For C=0.001microF, the range is from %.1f
    Hz to %.0f Hz\n ", f*10, fm*10); //Result
19 printf("\n For C=0.0001microF, the range is from %.1
    f Hz to %.0f Hz\n ", f*100, fm*100); //Result
20 Rf=10000+2700; //in ohm
21 Ri=5600; //in Ohm
22 Av=1+Rf/Ri;
23 printf("\n Gain ,Av is %.2f \n ", Av); //Result

```

Scilab code Exa 9.3 Frequency of oscillation

```

1 // Chapter9
2 // Frequency of oscillation
3 // Page.No-310
4 // Example_9_3
5 //Figure 9.12-9.14
6 // Given

```

```

7 clear;clc;
8 R=1000;           //in Ohm
9 C=0.1*10^-6;     //in F
10 f=1/(2*pi*1.732*R*C);
11 printf("\n The mimimum frequency of oscillation = %
    .0f Hz\n",f); // Result
12 //Vo=(R+Xc)*I1-R*I2
13 W=1/((6^0.5)*C*R);
14 printf("\n The frequency = %.0f Hz\n",W); // Result
15 //Vo/V3=1+(6*Xc/R)+(5*Xc/R^2)+(Xc/R)^3;
16 Vr=1-(5/((W*C*R)^2)); //Vr=Vo/V3
17 printf("\n The Vo/V3 is = %.0f \n",Vr); // Result
18 printf("\n The gain of ladder network is B= V3/Vo =
    1/%.0f \n",Vr); // Result

```

Scilab code Exa 9.4 Value of Ri

```

1 // Chapter9
2 // value of Rf
3 // Page.No-313
4 // Example9_4
5 //Figure 9.15
6 // Given
7 clear;clc;
8 C=0.1*10^-6;     //in F
9 R=1000;          //in Ohm
10 Av=-29;
11 Rf=-Av*R;
12 printf("\n The value for Rf is = %.0f Ohm\n",Rf); //
    Result
13 f=1/(2*pi*6^0.5*R*C);
14 printf("\n The frequency ,fo = %.0f Hz\n",f); //
    Result

```

Scilab code Exa 9.5 Output frequency and amplitude

```
1 // Chapter9
2 // Output Frequency and Amplitudes
3 // Page.No-318
4 // Example9_5
5 //Figure 9.21
6 // Given
7 clear;clc;
8 Vsat=13; //in V
9 R2=10000; //in ohm
10 R3=20000; //in ohm
11 R=33000; //in ohm
12 C=0.01*10^-6; //in Farad
13 Vup=Vsat*R2/R3;
14 printf("\n Value of Vupperthreshold is = %.1f V\n",
    Vup); // Result
15 //dv/dt=Vsat/RC=k
16 k=Vsat/R/C;
17 printf("\n dv/dt = %.0f V/S\n",k); // Result
18 T=Vsat/k;
19 printf("\n T = %.5f S\n",T); // Result
20
21 f=1/T/2;
22 printf("\nf = %.0f Hz\n",f); // Result
```

Scilab code Exa 9.6 Square wave generator

```
1 // Chapter 9
2 // 2kHz Square Wave generator
3 // Page.No-323
4 // Example9_6
```

```

5 //Figure 9.23
6 // Given
7 clear;clc;
8 R1=10000; //in Ohm
9 R2=R1/0.859; //in Ohm
10 fo=2000; //in Hz
11
12 printf("\n R2 is %.0f Ohm\n",R2); // Result
13 C=1/(2*R1*fo);
14 printf("\n C is %.9f F\n",C); // Result

```

Scilab code Exa 9.7 Output frequency

```

1 // Chapter 9
2 // determine Output frequency
3 // Page.No-327
4 // Example9_7
5 //Figure 9.28
6 // Given
7 clear;clc;
8 Vp=12; //in V
9 R1=4700; //in Ohm
10 R2=2000; //in Ohm
11 R3=20000; //in Ohm
12 C=1.1*10^-9; //in Farad
13 Vc=Vp*(R3/(R2+R3));
14 printf("\n The control Voltage is = %.2f V\n",Vc);
// Result
15 fo=2*(Vp-Vc)/(Vp*R1*C);
16 printf("\n Output frequency = %.0f Hz\n",fo); //
Result

```

Scilab code Exa 9.8 Maximum and minimum frequency

```

1 // Chapter 9
2 // determine Output frequency
3 // Page.No-328
4 // Example9_8
5 //Figure 9.29
6 // Given
7 clear;clc;
8 Vp=12;           //in V
9 R1=4700;         //in Ohm
10 R2=2000;        //in Ohm
11 R3=20000;       //in Ohm
12 C=1.1*10^-9;   //in Farad
13 Vc=Vp*(R3/(R2+R3));
14 //for minimum Vc
15 Vcmin=Vc-0.5;
16 printf("\n The control Voltage is = %.2f V\n",Vcmin
   ); // Result
17 fo=2*(Vp-Vcmin)/(Vp*R1*C);
18 printf("\n Output frequency = %.0f Hz\n",fo); //
   Result
19 //for maximum Vc
20 disp("For minimum frequency Use maximum Vc");
21 Vcmin1=Vc+0.5;
22 printf("\n The control Voltage is = %.2f V\n",
   Vcmin1); // Result
23 fo=2*(Vp-Vcmin1)/(Vp*R1*C);
24 printf("\n Output frequency = %.0f Hz\n",fo); //
   Result

```

Scilab code Exa 9.9 Free running frequency

```

1 // Chapter 9
2 // determine Output frequency
3 // Page.No-333
4 // Example9_9

```

```

5 //Figure 9.37
6 // Given
7 clear;clc;
8 Vp=6;           //in V
9 R1=4000;        //in Ohm
10 C=330*10^-12;  //in Farad
11 C2=270*10^-12; //in Farad
12 fo=0.3/(R1*C);
13 printf("\n Free runing frequency = %.0f Hz\n",fo);
    // Result
14 fl=8*fo/Vp;
15 printf("\n Lock Range = %.0f Hz\n",fl); // Result
16 fc=sqrt(2*%pi*fl/(3600*C2))/(2*%pi);
17 printf("\n Capture Range = %.0f Hz\n",fc); //
    Result

```

Scilab code Exa 9.10 Timing resistor and capacitor

```

1 // Chapter 9
2 // determine Output frequency
3 // Page.No-336
4 // Example9_10
5 //Figure 9.40
6 // Given
7 clear;clc;
8 R=10000;        //in Ohm
9 printf("\n Value of Assumed resistance is = %.0f
    Ohm\n",R); // Result
10
11 Tout=100*10^-6;
12 C=Tout/(1.1*R);
13 printf("\n Value of Capacitance is = %.11f F\n",C);
    // Result
14 printf("\n The nearst value would be 10nF");

```

Scilab code Exa 9.11 Square wave generator

```
1 // Chapter 9
2 // determine Output frequency
3 // Page.No-340
4 // Example9_11
5 // Given
6 clear;clc;
7 f=2000;          ///in Hz
8 DC=0.8;
9 T=1/f;
10 Thigh=DC*T;
11 printf("\n T high is = %.6f Sec\n",Thigh); //
    Result
12 Tlow=T-Thigh;
13 printf("\n T low is = %.6f Sec\n",Tlow); // Result
14 //assumption
15 Rb=10000;       //in Ohm
16 //Tlow=0.69RC
17 C1=Tlow/(0.69*Rb);
18 printf("\n Value of Capacitance C is = %.10f F\n",
    C1); // Result
19 //Thigh=0.69(Ra+Rb)
20 Ra=Thigh/(0.69*C1)-Rb;
21 printf("\n Value of resistance Ra is = %.0f Ohm\n",
    Ra); // Result
```

Scilab code Exa 9.12 range of output frequency

```
1 // Chapter 9
2 // determine Output frequency
3 // Page.No-344
```

```

4 // Example_9_12
5 //Figure 9.47
6 // Given
7 clear;clc;
8 R=110000; //in Ohm
9 C=0.1*10^-6; //in Farad
10 //
11 disp("When C=0.1microF")
12
13 fomin=0.15/(R*C);
14 printf("\n For low range with lowest frequency =
    %.1f Hz\n",fomin); // Result
15 //
16 R1=10000; //in Ohm
17 fomax=0.15/(R1*C);
18 printf("\n For low range with highest frequency =
    %.1f Hz\n",fomax); // Result
19 //
20 disp("When C=0.01microF")
21 R=110000; //in Ohm
22 C=0.01*10^-6; //in Farad
23 fomin=0.15/(R*C);
24 printf("\n For low range with lowest frequency =
    %.1f Hz\n",fomin); // Result
25 //
26 R1=10000; //in Ohm
27 fomax=0.15/(R1*C);
28 printf("\n For low range with highest frequency =
    %.1f Hz\n",fomax); // Result
29 //
30 disp("When C=0.001microF")
31 R=110000; //in Ohm
32 C=0.001*10^-6; //in Farad
33 fomin=0.15/(R*C);
34 printf("\n For low range with lowest frequency =
    %.1f Hz\n",fomin); // Result
35 //
36 R1=10000; //in Ohm

```

```
37 fmax=0.15/(R1*C);
38 printf("\n For low range with highest frequency =
    %.1f Hz\n",fmax); // Result
```

Chapter 10

Integrators and Differentiators

Scilab code Exa 10.1 vout and lower frequency range

```
1 //chapter 10
2 //Vout and lower frequency
3 //page no. 354
4 //Example10_1
5 //Figure 10.7
6 //Given
7 clc;
8 clear;
9 t=0;
10 Ri=10000; //in Ohm
11 C=10^-8; //in farad
12 Rf=100000; //in Ohm
13 //Vout(t)=-1/(Ri*C)*int(Vi(t))dt
14 Flow=1/(2*pi*Rf*C);
15 printf("\n Flow is %.0f Hz",Flow);
```

Scilab code Exa 10.2 Output

```

1 //chapter 10
2 //Vout
3 //page no. 356
4 //Example10_2
5 //Figure 10.7
6 //Given
7 clc;
8 clear;
9 step=0.1;
10 t=0:step:10;
11 disp("Answer is coming interm of t so solution is
      done by graph");
12 //x=1;
13 //f=5000;
14 x0=-1.6;x1=0:0.1:10;
15 Vin=sin(t);
16
17 xtitle('Sin(x)', 't')
18 X=integrate('sin(t)', 't', x0, x1);
19 Ri=10000;           //in Ohm
20 C=10^-8;           //in farad
21 Rf=100000;         //in Ohm
22 Vout=-0.318*X;
23 clf;
24 plot(t, Vin, t, Vout);
25 xtitle('Input (Blue) / Output (Green)', 't', 'V');

```

Scilab code Exa 10.3 Output of the circuit

```

1 //Chapter 10
2 //Sketch the output Waveform
3 //page no. 358
4 //Example10_3
5 //Figure 10.7
6 //Given

```

```

7  clc;
8  clear;
9  T0=4;
10 t=-5.99:0.01:6;
11 t_temp=0.01:0.01:T0/4;
12 s=length(t)/length(t_temp);
13 dx=[];
14 x=[];
15 for i=1:s
16     if modulo(i,2)==1 then
17         dx=[dx -ones(1,length(t_temp))];
18         x=[x .1*t_temp($:-1:1)];
19     else
20         dx=[dx ones(1,length(t_temp))];
21         x=[x .1*t_temp];
22     end
23 end
24 clf();
25 subplot(1,2,2)
26 plot(50*t,10*x-0.5,8)
27 xtitle("Output Waveform", "Microsecond", "V");
28 t=-30:0.01:30;
29 subplot(1,2,1);
30 plot('onn',10*t,[2*squarewave(2*t/(%pi),50)])
31 xtitle("Input Waveform", "Microsecond", "V");

```

Scilab code Exa 10.4 Integrator connected to accelerometer

```

1 //chapter 10
2 //Vout
3 //page no. 359
4 //Figure 10.11a
5 //Given
6 clc;
7 clear;

```

```

8 Rf=400000;           //in Ohm
9 C=20*10^-9;         //in farad
10 flow=1/(2*%pi*Rf*C);
11 printf("\n Flow = %.1 f Hz",flow);
12 Ri=15000;           //in Ohm
13 //integration
14 function Vin=f(t),Vin=.6, endfunction
15 exact=-2.5432596188;
16 I=intg(0,10^-3,f)
17
18 Vout=-1*I/Ri/C;
19 printf("\n Vout(t) = %.1 f V",Vout); // Result
20
21 //Graph
22 t=(0:0.001:6);
23 V=Vout*ones(1:0.001:4);
24
25 for i=0.001:0.001:1-.001
26     V=[Vout*(1-i) V Vout*(1-i)]
27 end
28
29 V=[V zeros(5.001:0.001:6)]
30 V=[2 V 0]
31 clf;
32 plot(t,V)
33 xgrid;
34 xtitle('Integrator output', '$t$', '$Voltage$')

```

Scilab code Exa 10.5 Range for differentiation

```

1 //Chapter 10
2 //range of Differentiation & Sketch the output
  Waveform
3 //page no. 365
4 //Example10_5

```

```

5 //Figure 10.19
6 //Given
7 clc;
8 clear;
9 Ri=100;           //in Ohm
10 Ci=10^-8;        //in farad
11 Rf=5000;         //in Ohm
12 Cf=10^-10;      //in farad
13 fhf=1/(2*pi*Rf*Cf);
14 fh_in=1/(2*pi*Ri*Ci);
15 printf("\n Fhigh(f dbk)=%.0f Hz",fhf);
16 printf("\n Fhigh(in)=%.0f Hz",fh_in);
17 //graph is drawn taking function sin(t)
18 t=[0:0.01:15];
19 Vi=sin(t);
20 plot(2*Vi);
21 plot(diff(-1.885*100*Vi));
22 xtitle("Partial Differentiator of sin(t)","t","V");
23
24 xgrid;

```

Scilab code Exa 10.6 Output Waveform

```

1 //Chapter 10
2 //Sketch the output Waveform
3 //page no. 368
4 //Example10_6
5 //Figure 10.19
6 //Given
7 clc;
8 clear;
9 Rf=5000;         //in Ohm
10 C=10^-8;        //in farad
11
12 f=4000;         //in KHz

```



```

13 T=1/f;
14 printf("\n T = %.6 f second",T);
15 S=6/(125*10^-6);
16 printf("\n Slope = %.0 f V/S",S);
17 //graph
18 step=1;
19 t=0:step:1;
20 Vin=S*t;
21 dy=diff(S*t/step); //approximate differentiation of
    sine function
22
23 Vout=-Rf*C*dy;
24 printf("\n Vou(t) = %.1 f V",Vout);
25
26 T0=4;
27 t=-5.99:0.01:6;
28 t_temp=0.01:0.01:T0/2;
29 s=length(t)/length(t_temp);
30 dx=[];
31 x=[];
32 for i=1:s
33     if modulo(i,2)==1 then
34         dx=[dx -ones(1,length(t_temp))];
35         x=[x .5*t_temp($:-1:1)];
36     else
37         dx=[dx ones(1,length(t_temp))];
38         x=[x .5*t_temp];
39     end
40 end
41 //figure
42
43 subplot (1,1,1)
44 plot(t,3-6*x,'b',t,2.4*dx,'r')
45 xtitle('Input(b) and Output(r)', 't', "V")

```

Scilab code Exa 10.7 Sketch the output wave form

```
1 //Chapter 10
2 //Sketch the output Waveform
3 //page no. 370
4 //Example10_7
5 //Figure 10.23
6 //Given
7 clc;
8 clear;
9 f=4; //in KHz
10 T=1/f;
11 S=5*10^6;
12 step=1;
13 t=0:step:1;
14 Vin=S*t;
15 printf("\n Vin(t) = %.0f*t",S);
16 Rf=5000; //in Ohm
17 C=10^-8; //in farad
18 dy=diff(S*t/step); //approximate differentiation of
    sine function
19 Vout=-Rf*C*dy;
20 printf("\n Vou(t) = %.0f V",Vout);
21 t=(0:0.1:5*pi)';
22 plot(t,3*squarewave(t));
23 xtitle("Output Wave form","t","V");
24 xtitle('Input(b) and Output(r)', 't');
```

Scilab code Exa 10.8 LVDT

```
1 //Chapter 10
2 //Sketch the output Waveform
3 //page no. 370
4 //Example10_8
5 //Figure 10.24a
```

```

6 //Given
7 clc;
8 clear;
9 Ri=250; //in Ohm
10 Ci=0.5*10^-6; //in farad
11 Rf=40000; //in Ohm
12 Cf=2*10^-9; //in farad
13 fhf=1/(2*%pi*Rf*Cf);
14 fh_in=1/(2*%pi*Ri*Ci);
15 printf("\n Fhigh(f dbk)=%.0f Hz",fhf);
16 printf("\n Fhigh(in)=%.0f Hz",fh_in);
17 //
18
19 S=10; //in V/S
20 step=1;
21 disp(S,"For slope")
22 t=0:step:1;
23 Vin=10*t;
24 dy=diff(S*t/step); //approximate differentiation of
    sine function
25 Vout=-Rf*Ci*dy;
26 printf("\n Vout(t) = %.1f V",Vout);
27 //
28 Slope=-4/0.2; //in V/S
29 step=1;
30 disp(Slope,"For slope")
31 t=0:step:1;
32 Vin=10*t;
33 dy=diff(Slope*t/step); //approximate differentiation
    of sine function
34 Vout2=-Rf*Ci*dy;
35 printf("\n Vout(t) = %.1f V",Vout2);
36 //graph
37 t=(0:0.0001:1.5);
38 V=Vout*ones(0:0.0001:.2);
39 V=[V zeros(.2+.0001:0.0001:.5-.0001)];
40 V=[V Vout2*ones(.5:0.0001:.7)];
41 V=[V zeros(.7+.0001:0.0001:1-.0001)];

```

```
42 V=[V Vout*ones(1:0.0001:1.2)];
43 V=[V zeros(1.2+.0001:.0001:1.5)]
44 clf;
45 plot(t,V)
46
47 xtitle('Differentiator output ','t$ ','$Voltage$')
```

Chapter 11

Active filters

Scilab code Exa 11.1 Butterworth low pass filter

```
1 // Chapter 11
2 // Design a low pass Butterworth filter
3 // Page.No-397
4 // Example11_1
5 // Figure 11.13 and 11.14
6 // Given
7 clear;clc;
8 L=1.414; //Alpha
9 Ri=1; //in Ohm
10 Rf=2-L;
11 printf("\n The value of Rf is = %.3f Ohm\n",Rf); //
    Result
12 Av=1+Rf/Ri;
13 printf("\n The pass band gain of = %.3f \n",Av); //
    Result
14 fc=1000; //in Hz
15 W=2*%pi*fc;
16 printf("\n The critical frequency is = %.0f radians
    per seconds\n",W); // Result
17 R=1/W;
18 printf("\n The Resistor required is = %.6f Ohm\n",R
```

```

    ); // Result
19 C1=2/L;
20 printf("\n The capacitor1 required is = %.3f F\n",
    C1); // Result
21 C2=L/2;
22 printf("\n The capacitor2 required is = %.3f F\n",
    C2); // Result

```

Scilab code Exa 11.2 Design second order bessel filter

```

1 // Chapter 11
2 // Design a second order high pass Bessel's filter
3 // Page.No-404
4 // Example11.2
5 //Figure 11.25
6 // Given
7 clear;clc;
8 L=1.732; // Aplha = DAMPING
9 Kf=1.274;
10 R1=L/2;
11 printf("\n The Resistor required is = %.3f Ohm\n",
    R1); // Result
12 R2=2/L;
13 printf("\n The Resistor required is = %.3f Ohm\n",
    R2); // Result
14 F3db=5000; //in Hz
15 Fc=F3db/Kf;
16 printf("\n The critical frequency is = %.0f Hz\n",Fc
    ); // Result
17 Wc=2*pi*Fc;
18 printf("\n The Wc is = %.0f radians per seconds\n",
    Wc); // Result
19 R1n=R1/Wc;
20 printf("\n The value of scaled Resistor R1 is = %.7
    f Ohm\n",R1n); // Result

```

```

21 R2n=R2/Wc;
22 printf("\n The value of scaled Resistor R2 is = %.7
    f Ohm\n",R2n); // Result

```

Scilab code Exa 11.3 Fifth order system

```

1 // Chapter 11
2 // Design a filter to remove subsonic tones
3 // Page.No-406
4 // Example11.2
5 //Figure 11.29
6 // Given
7 clear;clc;
8 f3db=20; //In Hz
9 W3db=2*%pi*f3db;
10 printf("\n The desired break frequency , W3db is = %
    .1f radians per second\n",W3db); // Result
11 disp(" Stage 1");
12 kf=1.557;
13 Wc=W3db/kf;
14 printf("\n The Wc is = %.1f radians per second\n",Wc
    ); // Result
15 Rscaled=1/80.7; //Rscaled value
16 R=1000*Rscaled; //Practical Value
17 printf("\n The scaled Resistor required is = %.3f
    Ohm\n",R); // Result
18 C=1*10^-6; //Assumed Value
19 printf("\n The assumed capacitor is = %.6f Farad\n
    ",C); // Result
20 disp(" Stage 2");
21 Alpha=1.775;
22 R1=Alpha/2;
23 printf("\n The Resistor R1 required is = %.4f Ohm\n
    ",R1); // Result
24 R2=2/Alpha;

```

```

25 printf("\n The Resistor R2 required is = %.3f Ohm\n
    ",R2); // Result
26 kf1=1.613;
27 Wc1=W3db/kf1;
28 printf("\n The required critical frequency ,Wc is =
    %.1f radians per second\n",Wc1); // Result
29 //we will scale the resistor
30 R1s=R1/Wc1;
31 R2s=R2/Wc1;
32 printf("\n The scaled resistor R1 is = %.4f Ohm\n",
    R1s); // Result
33 printf("\n The scaled resistor R2 is = %.4f Ohm\n",
    R2s); // Result
34 printf("\n The assumed capacitor is = %.6f Farad\n
    ",C); // Result
35 //for practical values of resistor and capacitor
    multiplying by 10^6
36 R1m=R1s*10^6;
37 R2m=R2s*10^6;
38 printf("\n The practical value of resistor R1 is =
    %.0f Ohm\n",R1m); // Result
39 printf("\n The practical value of resistor R2 is =
    %.0f Ohm\n",R2m); // Result
40 printf("\n The assumed capacitor is = %.6f Farad\n
    ",C); // Result
41
42 disp(" Stage 3");
43 Alpha=1.091;
44 R21=Alpha/2;
45 R22=2/Alpha;
46 kf2=1.819;
47 Wc2=W3db/kf2;
48 printf("\n The required critical frequency ,Wc is =
    %.1f radians per second\n",Wc2); // Result
49 //Scale resistor by Wc to achive tuning frequency
50 R21s=R21/Wc2;
51 R22s=R22/Wc2;
52 printf("\n The scaled resistor R1 is = %.5f Ohm\n",

```



```

    R21s); // Result
53 printf("\n The scaled resistor R2 is = %.4f Ohm\n",
    R22s); // Result
54 //for practical values of resistor and capacitor
    multiplying by 10^6
55 R21m=R21s*10^6;
56 R22m=R22s*10^6;
57 printf("\n The practical value of resistor R1 is =
    %.0f Ohm\n",R21m); // Result
58 printf("\n The practical value of resistor R2 is =
    %.0f Ohm\n",R22m); // Result
59 printf("\n The assumed capacitor is = %.6f Farad\n
    ",C); // Result

```

Scilab code Exa 11.4 Crossover network

```

1 // Chapter 11
2 // crossover network
3 // Page.No-412
4 // Example11.4
5 //Figure 11.32
6 // Given
7 clear;clc;
8 L=1.414; //Alpha
9 fc=800; //In Hz
10 Rf=2-L;
11 printf("\n The value of Rf is = %.3f Ohm\n",Rf); //
    Result
12 Wc=2*pi*fc;
13 printf("\n The critical frequency is = %.0f radians
    per seconds\n",Wc); // Result
14 R=1/Wc;
15 printf("\n The value of scaled Resistor R1 is = %.7
    f Ohm\n",R); // Result
16

```

```

17 printf("\n The value of scaled Resistor and
    capacitor is = %.0f Ohm and 10nF \n",R*10^8); //
    Result

```

Scilab code Exa 11.5 Band pass filter

```

1 // Chapter 11
2 // Band pass Filter
3 // Page.No-418
4 // Example11.5
5 // Given
6 clear;clc;
7 f2=1200; //in Hz
8 f1=800; //in Hz
9 BW=f2-f1;
10 printf("\n The Bandwidth is %.3f Hz\n",BW); //
    Result
11 fo=(f1*f2)^0.5;
12 printf("\n fo is %.0f Hz\n",fo); // Result
13 Q=fo/BW;
14 printf("\n Q is %.2f \n",Q); // Result
15 Av=-2*Q*Q;
16 printf("\n Av is %.0f \n",Av); // Result
17 fut=10*Av*fo;
18 printf("\n funity is %.0f Hz\n",fut); // Result
19 R2=2*Q;
20 printf("\n R2 is %.1f Ohm\n",R2); // Result
21 R1b=Q/(2*Q*Q-1);
22 printf("\n R1b is %.4f Ohm\n",R1b); // Result
23 W=2*pi*fo;
24 printf("\n The frequency is = %.0f radians per
    seconds\n",W); // Result
25 C=1/W;
26 printf("\n C is %.7f F\n",C); // Result
27 //practical component value

```

```
28 printf("\n R and C are %.0f Ohm and %.8f F\n",R2*10,  
    C/10); // Result
```

Scilab code Exa 11.6 Band pass filter with center frequency

```
1 // Chapter 11  
2 // Band pass Filter  
3 // Page.No-424  
4 // Example_11.6  
5 // Given  
6 clear;clc;  
7 Q=25;  
8 fo=4300; //in Hz  
9 Rd=3*Q-1; //R damping  
10 printf("\n Rdamping is %.1f Ohm\n",Rd); // Result  
11 W=2*pi*fo;  
12 printf("\n The frequency is = %.0f radians per  
    seconds\n",W); // Result  
13 C=1/W;  
14 printf("\n C is %.7f F\n",C); // Result  
15 //practical component value  
16 printf("\n Rdamping and C are %.0f Ohm and %.10f F\n  
    ",Rd*5000,C/5000); // Result  
17 //remaining other Resistor are of 5K Ohm
```

Scilab code Exa 11.7 Notch filter

```
1 // Chapter 11  
2 // Band pass Filter  
3 // Page.No-427  
4 // Example_11.7  
5 // Given  
6 clear;clc;
```

```
7 Q=30;
8 fo=60;           //in Hz
9 Rd=3*Q-1;       //R damping
10 printf("\n Rdamping is %.1f Ohm\n",Rd); // Result
11 W=2*pi*fo;
12 printf("\n The frequency is = %.0f radians per
    seconds\n",W); // Result
13 C=1/W;
14 printf("\n C is %.5f F\n",C); // Result
```

Chapter 12

Analog to Digital to Analog Conversion

Scilab code Exa 12.1 determine the resolution

```
1 // Chapter 12
2 // Resolution of System
3 // Page.No-445
4 // Example12_1
5 // Given
6 clear;clc;
7 V=2; //in V
8 Bits=12;
9 levels=2^Bits; //12 bit words
10 step=V/levels;
11 printf("\n The system can resolve = %.6f V\n",step);
12 // Result
12 Drange=20*log10(levels);
13 printf("\n The Dynamic Range is = %.0f dB\n",Drange)
14 ; // Result
14
15 DR=6*Bits;
16 printf("\n The Dynamic Range is approx (6dB * no.of
17 bits),i.e. = %.0f dB\n",DR); // Result
```

Scilab code Exa 12.2 Determine the step size

```
1 // Chapter 12
2 // Step size
3 // Page.No-446
4 // Example12_2
5 // Given
6 clear;clc;
7 Bits=16;
8 V=0.775;           //in V
9 Vp=1.550;         //in Vp-p
10 levels=2^Bits;    //12 bit words
11 DR=6*Bits;
12 printf("\n The Dynamic Range is = %.0 f dB\n",DR);
13 //
14 step=Vp/levels;
15 printf("\n The system can resolve = %.8 f V\n",step);
16 // Result
```

Scilab code Exa 12.3 sampling rates and no of bits

```
1 // Chapter 12
2 // Minimum acceptable frquency range
3 // Page.No-448
4 // Example_12_3
5 // Given
6 clear;clc;
7 DR=50;             //in dB
8 Bits=DR/6;
9 printf("\n The Bits required are = %.1 f \n",Bits);
10 // Result
```

```
10 //we cannot have fractional bit so,  
11 printf("\n we cannot have fractional bit so, Bits  
    required are = %.0f \n",Bits+1); // Result
```
