

Scilab Textbook Companion for
Analog Integrated Circuits
by R. S. Tomar¹

Created by
Saleem Ahmed
B.Tech
Electrical Engineering
Uttarakhand Technical University
College Teacher
None
Cross-Checked by
Chaya Ravindra

July 7, 2014

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Analog Integrated Circuits

Author: R. S. Tomar

Publisher: Umesh Publications, New Delhi

Edition: 2

Year: 2007

ISBN: 81-88114-72-3

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Constant Current Sources	8
2 Differentials Aplifiers	15
3 Operational Amlifiers and their Parameters	24
4 Opamps with negative feedback	28
5 Linear Applications of OPamps	36
6 Oscillators and waveform generators	46
7 The 555 timer	59
8 Frequency Synthesizers and PLL	64
9 Active Filters	67
10 Comparators	83
11 Non linear applications of opamp	87
12 Operational Transconductance Amplifier	91
13 Voltage Regulators	92

List of Scilab Codes

Exa 1.1	Design a current mirror circuit	8
Exa 1.2	Design a current mirror circuit	8
Exa 1.3	Design a current source	9
Exa 1.4	Design a current mirror circuit	9
Exa 1.5	Modified current mirror circuit	10
Exa 1.6	Find Iout	10
Exa 1.7	Design a widlar current source	11
Exa 1.8	Design a widlar current source	12
Exa 1.9	Calculate Current	12
Exa 1.10	Determine IC1 and IC2	13
Exa 2.1	Output Voltage	15
Exa 2.2	Output Voltage and percent error	15
Exa 2.3	Current Ad Ac CMRR	16
Exa 2.4	Gain and CMRR	17
Exa 2.5	Operating point Gain and Resistance	18
Exa 2.6	Gain and input resistance	19
Exa 2.7	Q point and voltage gain	19
Exa 2.8	RC RE Rid Rid	20
Exa 2.9	Operating point Gain and Resistance	21
Exa 2.10	Differential input resistance	22
Exa 2.11	Gain and input resistance	22
Exa 3.1	Open loop gain	24
Exa 3.2	Time taken	24
Exa 3.3	Maximum Voltage	25
Exa 3.4	Maximum Frequency	25
Exa 3.5	Slew rate	26
Exa 3.6	Close Loop Voltage Gain	26
Exa 3.7	Limiting Frequency	26

Exa 4.1	Bandwidth with feedback	28
Exa 4.2	Acl Rif Rof fodash	28
Exa 4.3	Impedence and gain	29
Exa 4.4	Input and output impedence	30
Exa 4.5	Non Inverting Amplifier	30
Exa 4.6	Close Loop Voltage Gain	31
Exa 4.7	Acl Rif Rof	31
Exa 4.8	Output Voltage	32
Exa 4.9	Variation in output Voltage	32
Exa 4.10	Gain and impedence	33
Exa 4.11	Gain and Bandwidth	34
Exa 4.12	Calculate Gain	34
Exa 4.13	Input and output impedence	35
Exa 5.1	Output Voltage	36
Exa 5.2	Resistor R1 and R2	36
Exa 5.3	Output Voltage	37
Exa 5.4	Output Voltage	37
Exa 5.5	Instrumentation Amplifier	38
Exa 5.6	Gain and Impedence	38
Exa 5.8	Output Voltage	39
Exa 5.9	Output Voltage	40
Exa 5.11	Resistor Ri and Rf	40
Exa 5.13	Output of opamp	41
Exa 5.14	Output Voltage	41
Exa 5.16	Design required circuit	42
Exa 5.17	Output of opamp	43
Exa 5.18	Design a differentiator	43
Exa 5.19	Design a differentiator	44
Exa 5.20	Rf Ri and Cf	45
Exa 6.1	Design a RC phase shift oscillator	46
Exa 6.3	Design a wein bridge oscillator	47
Exa 6.5	Design a wein bridge oscillator	48
Exa 6.6	Frequency of oscillation	48
Exa 6.7	Design a quadrature oscillator	49
Exa 6.8	Causes of distortion	49
Exa 6.9	Frequency of oscillation	50
Exa 6.10	Design a square wave generator	51
Exa 6.11	Find Rf and C	52

Exa 6.12	Frequency of output	52
Exa 6.13	Triangular wave generator	52
Exa 6.14	Peak output voltage	53
Exa 6.15	Triangular wave generator	54
Exa 6.16	Frequency of output	54
Exa 6.17	Series and parallel resonant frequencies	55
Exa 6.18	Design a function generator	56
Exa 6.19	V0 V7 I and fo	56
Exa 7.1	Monostable Multivibrator	59
Exa 7.2	Value of R	60
Exa 7.3	Astable Multivibrator	60
Exa 7.4	Design a square wave generator	61
Exa 7.5	Astable Multivibrator	61
Exa 7.6	Astable Multivibrator	62
Exa 7.7	Astable Multivibrator	63
Exa 8.1	Lock Capture and pullin range	64
Exa 8.2	Design a FM demodulator	65
Exa 8.3	Clock frequency and no of bits	65
Exa 9.2	First order low pass filter	67
Exa 9.3	Find Bandwidth	68
Exa 9.4	First order low pass filter	68
Exa 9.5	Convert Cutoff frequency	69
Exa 9.6	First order high pass filter	69
Exa 9.7	Retune the high pass filter	70
Exa 9.8	Second order Butterworth filter	71
Exa 9.9	Second order Butterworth filter	72
Exa 9.10	Second order low pass filter	73
Exa 9.11	Low pass bessel filter	74
Exa 9.12	Second order low pass filter	74
Exa 9.13	Second order low pass filter	75
Exa 9.14	Third order low pass butterworth filter	76
Exa 9.15	Design a band pass filter	77
Exa 9.16	Design a band pass filter	79
Exa 9.17	Design a band pass filter	80
Exa 9.18	Design a band pass filter	81
Exa 9.20	Second order notch filter	82
Exa 10.1	Output Voltage	83
Exa 10.2	Upper and Lower Trip points	83

Exa 10.3	Phase shift	84
Exa 10.4	Output Voltage	84
Exa 10.5	Threshold and hysteresis voltage	85
Exa 11.1	Output Voltage	87
Exa 11.3	Output Voltage	87
Exa 11.4	Output Voltage	88
Exa 11.7	Calculate Output	88
Exa 11.8	Calculate Output	89
Exa 12.1	f3dB frequency	91
Exa 13.1	Regulation	92
Exa 13.2	Load Regulation	92
Exa 13.3	Calculate Load Current	93
Exa 13.4	Determine the output	93
Exa 13.5	Design a regulator circuit	94
Exa 13.6	Calculate I_{ext}	94
Exa 13.7	Value of R1	95
Exa 13.8	Adjustable Voltage regulator	96
Exa 13.9	Regulated Power Supply	96
Exa 13.10	Regulated Power Supply	97

Chapter 1

Constant Current Sources

Scilab code Exa 1.1 Design a current mirror circuit

```
1 //Ex 1.1
2 clc;
3 clear;
4 close;
5 format('v',5);
6 Iout=8;//micro A
7 VBE=0.7;//V
8 Beta=80;//unitless
9 VCC=20;//V
10 IREF=Iout*(1+2/Beta);//micro A
11 R=(VCC-VBE)/IREF;//Mohm
12 disp(IREF,"Reference current (micro A)");
13 disp(R,"Resistance required (Mohm)");;
```

Scilab code Exa 1.2 Design a current mirror circuit

```
1 //Ex 1.2
2 clc;
```

```

3  clear;
4  close;
5  format('v',5);
6  Iout=1; //mA
7  VBE=0.7; //V
8  Beta=100; // unitless
9  VCC=30; //V
10 IREF=Iout*(1+2/Beta); //mA
11 R=(VCC-VBE)/IREF; //kohm
12 disp(IREF," Reference current (mA)");
13 disp(R," Resistance required (kohm)");;

```

Scilab code Exa 1.3 Design a current source

```

1  //Ex 1.3
2  clc;
3  clear;
4  close;
5  format('v',5);
6  Iout=0.5; //mA
7  Beta=50; // unitless
8  VEB=0.7; //V
9  VCC=5; //V
10 IREF=Iout*(1+2/Beta); //mA
11 R=(VCC-VEB)/IREF; //kohm
12 disp(IREF," Reference current (mA)");
13 disp(R," Resistance required (kohm)");;

```

Scilab code Exa 1.4 Design a current mirror circuit

```

1  //Ex 1.4
2  clc;
3  clear;

```

```

4 close;
5 format('v',5);
6 Iout=8; //micro A
7 Beta=100; // unitless
8 VBE=0.7; //V
9 VCC=20; //V
10 IREF=Iout/(1+2/Beta/(1+Beta)); //micro A
11 R=(VCC-2*VBE)/IREF; //Mohm
12 disp(IREF," Reference current (micro A)");
13 disp(R," Resistance required (Mohm)");;

```

Scilab code Exa 1.5 Modified current mirror circuit

```

1 //Ex 1.5
2 clc;
3 clear;
4 close;
5 format('v',7);
6 Iout=60; //micro A
7 VBE=0.7; //V
8 Beta=150; // unitless
9 VCC=30; //V
10 IREF=Iout*(1+2/Beta/(1+Beta)); //micro A
11 R=(VCC-2*VBE)/IREF; //Mohm
12 disp(IREF," Reference current (micro A)");
13 disp(R*1000," Resistance required (kohm)");;

```

Scilab code Exa 1.6 Find Iout

```

1 //Ex 1.6
2 clc;
3 clear;
4 close;

```

```

5 format('v',5);
6 VBE=0.7; //V
7 Beta=120; // unitless
8 VCC=10; //V
9 R=5.6; //kohm
10 //KCL at node x : IREF=IC1+I1; // as Beta>>1
11 //KCL at node y : I1=IC2+IB3; // as Beta>>1
12 IREF=(VCC-VBE)/R; //mA
13 // as IREF=2*IC+IB3=IC*(2+1/Beta)=2*IC; // as Beta>>1
14 IC=IREF/2; //mA
15 Iout=IC; //mA
16 disp(Iout,"Output current (mA)");

```

Scilab code Exa 1.7 Design a widlar current source

```

1 //Ex 1.7
2 clc;
3 clear;
4 close;
5 format('v',5);
6 Iout=6; //micro A
7 IREF=1.2; //mA
8 VBE2=0.7; //V
9 VT=26; //mV
10 Beta=120; // unitless
11 VCC=20; //V
12 R=(VCC-VBE2)/IREF; //kohm
13 disp(R,"Value of resistance R(kohm)");
14 IC1=Iout; //micro A
15 IC2=(IREF-IC1*10^-3/Beta)/(1+1/Beta); //mA
16 RS=1/(IC1*10^-6)*VT*10^-3*log(IC2*1000/IC1); //ohm
17 disp(RS/1000,"Value of resistance RS(kohm)");

```

Scilab code Exa 1.8 Design a widlar current source

```
1 //Ex 1.8
2 clc;
3 clear;
4 close;
5 format('v',6);
6 IREF=1; //mA
7 Io2=20; //micro A
8 Io3=40; //micro A
9 VBE1=0.7; //V
10 VT=26; //mV
11 VCC=10; //V
12 VEE=-10; //V
13 R=(VCC-VBE1-VEE)/IREF; //kohm
14 disp(R," Value of resistance R(kohm)");
15 RE2=VT/Io2*log(IREF*1000/Io2); //kohm
16 disp(RE2," Value of resistance RE2(kohm)");
17 RE3=VT/Io3*log(IREF*1000/Io3); //kohm
18 disp(RE3," Value of resistance RE3(kohm)");
19 VBE2=VBE1-RE2*Io2/1000; //V
20 disp(VBE2," Value of Base emitter voltage of
   transistor Q2(V)");
21 VBE3=VBE1-RE3*Io3/1000; //V
22 disp(VBE3," Value of Base emitter voltage of
   transistor Q3(V)");
```

Scilab code Exa 1.9 Calculate Current

```
1 //Ex 1.9
2 clc;
3 clear;
4 close;
5 format('v',5);
6 Beta=100; // unitless
```

```

7 VBE=0.715; //V
8 R=5.6; //kohm
9 RC=1; //kohm
10 VCC=10; //V
11 VCB1=0; //V(Q1 will act as diode)
12 IREF=(VCC-VBE)/R; //mA
13 //KCL at node x : IREF=IC1+2*IB;
14 //KCL at node y : I1=IC2+IB3; // as Beta>>1
15 IREF=(VCC-VBE)/R; //mA
16 // as IREF=2*IC1/Beta+IC1
17 IC1=IREF/(1+2/Beta); //mA
18 IC2=IC1; //mA
19 IC3=IC1; //mA
20 disp(IC1," Collector current in each transistor , IC1=
    IC2=IC3 in mA");
21 IRC=IC1+IC2+IC3; //mA
22 disp(IRC," Current through RC(mA)");

```

Scilab code Exa 1.10 Determine IC1 and IC2

```

1 //Ex 1.10
2 clc;
3 clear;
4 close;
5 format('v',5);
6 Vout=5; //V
7 Beta=180; // unitless
8 R=22; //kohm
9 VCC=10; //V
10 VBE=0.7; //V
11 IREF=(VCC-VBE)/R; //mA
12 IC=(IREF-VBE/R)/(1+2/Beta); //mA
13 RC=(VCC-Vout)/IC; //kohm
14 disp(IC,"IC1 & IC2 in mA are ");
15 disp(RC,"RC in kohm is ");

```

16 //Answer in the book is wrong.

Chapter 2

Differentials Aplifiers

Scilab code Exa 2.1 Output Voltage

```
1 //Ex 2.1
2 clc;
3 clear;
4 close;
5 format('v',5);
6 v1=7; //mV
7 v2=9; //mV
8 Ad=80; //dB
9 CMRR=90; //dB
10 vid=v2-v1; //mV
11 vcm=(v1+v2)/2; //mV
12 Ad=10^(Ad/20); // unitless
13 CMRR=10^(CMRR/20); // unitless
14 vout=Ad*(vid+vcm/CMRR)/1000; //V
15 disp(vout,"Output Voltage(V)");;
```

Scilab code Exa 2.2 Output Voltage and percent error


```

1  ////Ex 2.2
2  clc;
3  clear;
4  close;
5  format('v',7);
6  v1=50; //micro V
7  v2=55; //micro V
8  Ad=2*10^5; // unitless
9  CMRR=80; //dB
10 vid=v2-v1; //micro V
11 vcm=(v1+v2)/2; //mV
12 CMRR=10^(CMRR/20); // unitless
13 vout=Ad*(vid+vcm/CMRR)/10^6; //V
14 disp(vout,"Output Voltage(V)");
15 Verror=vout-Ad*vid/10^6; //V
16 disp(Verror,"Error Voltage(V)");
17 error_p=(Verror/vout)*100; // % error
18 disp(error_p,"Percentage error(%)");
19 //Percentage error answer is not correct in the book

```

Scilab code Exa 2.3 Current Ad Ac CMRR

```

1  ////Ex 2.3
2  clc;
3  clear;
4  close;
5  format('v',6);
6  IT=1; //mA
7  VCC=15; //V
8  RE=50; //kohm
9  RC=15; //kohm
10 Beta=120; // unitless
11 alfa=Beta/(Beta+1); // unitless
12 Vid=6; //mV

```

```

13 VT=26; //mV
14 //Part (a)
15 iC1=alfa*IT/(1+exp(-Vid/VT)); //mA
16 iC2=IT-iC1; //mA
17 disp(iC2,"dc Collector current through transistors(
    mA)");
18 //Part (b)
19 iC=IT/2; //mA(let iC1=iC2=iC)
20 re=VT/iC; //ohm(let re1=re2=re)
21 Ad=-RC*1000/re; // unitless
22 Acm=-RC*1000/(re+2*RE*1000); // unitless
23 Acm=abs(Acm); // unitless
24 CMRR=abs(Ad/Acm); // unitless
25 disp(Ad,"Ad");
26 disp(Acm,"Acm");
27 CMRR=20*log10(CMRR); //dB
28 disp(CMRR,"CMRR(dB)");

```

Scilab code Exa 2.4 Gain and CMRR

```

1 //Ex 2.4
2 clc;
3 clear;
4 close;
5 format('v',6);
6 RC=2; //kohm
7 RE=4.3; //kohm
8 VEE=5; //V
9 VBE=0.7; //V
10 IT=(VEE-VBE)/RE; //mA
11 VT=26; //mV
12 re=2*VT/IT; //ohm
13 Ad=-RC*1000/2/re; // unitless
14 disp(Ad,"Ad");
15 Acm=-RC*1000/(re+2*RE*1000); // unitless

```

```

16 disp(Acm,"Acm");
17 CMRR=abs(Ad/Acm);//// unitless
18 disp(CMRR,"CMRR");

```

Scilab code Exa 2.5 Operating point Gain and Resistance

```

1  ////Ex 2.5
2  clc;
3  clear;
4  close;
5  format('v',5);
6  Beta=100;//// unitless
7  VBE=0.715;VD1=0.715;////V
8  VZ=6.2;////V
9  VT=26;////mV
10 IZt=41;////mA
11 VCC=10;////V
12 VEE=10;////V
13 RE=2.7;////kohm
14 RC=4.7;////kohm
15 VB=-VEE+VZ+VD1;////V
16 VE=VB-VBE;////V
17 IE3=(VE-(-VEE))/(RE);////mA
18 IT=IE3;////mA
19 ICQ=IT/2;////mA(let ICQ1=ICQ2=ICQ)
20 VCEQ=VCC+VBE-ICQ*RC;////V
21 Q=[ICQ VCEQ];////[mA V](Q point)
22 disp(Q,"Q point (ICQ(mA), VCEQ(V)) is ");
23 re=2*VT/IT;////ohm
24 Ad=-RC*1000/re;//// unitless
25 Rid=2*Beta*re/1000;////kohm
26 disp(Ad,"Ad");
27 disp(Rid,"Rid(kohm)");

```

Scilab code Exa 2.6 Gain and input resistance

```
1  ////Ex 2.6
2  clc;
3  clear;
4  close;
5  format('v',6);
6  Beta=100; // unitless
7  VBE=0.7; //V
8  VCC=10; //V
9  VEE=10; //V
10 VT=26; //mV
11 RC=2.7; //kohm
12 R=2.2; //kohm
13 IExt=(VEE-VBE)/R; //mA
14 IC3=IExt; IT=IExt;; //mA
15 ICQ=IT/2; //mA
16 re=2*VT/IT; //ohm(let re1=re2=re)
17 Ad=-RC*1000/re; // unitless
18 Rid=2*Beta*re/1000; //kohm(let Rid1=Rid2=Rid)
19 disp(Ad,"Differntial moe gain , Ad");
20 disp(Rid,"Differntial input resistance , Rid(kohm)");
```

Scilab code Exa 2.7 Q point and voltage gain

```
1  ////Ex 2.7
2  clc;
3  clear;
4  close;
5  format('v',7);
6  Beta=100; // unitless
7  VBE=0.7; //V
```

```

8 VD1=0.7;VD2=0.7//V
9 VCC=15;//V
10 VEE=15;//V
11 VT=26;//mV
12 RE=560;//ohm
13 RC=6.8;//kohm
14 R=220;//ohm
15 VB=-VEE+VD1+VD2;//V
16 VE=VB-VBE;//V
17 IE3=(VE-(-VEE))/RE*1000;//mA
18 IT=IE3;//mA
19 ICQ=IT/2;//mA
20 VCEQ=VCC+VBE-ICQ*RC;//V
21 Q=[ICQ VCEQ];//[mA V](Q point)
22 disp(Q,"Q point (ICQ(mA), VCEQ(V)) is ");
23 re=2*VT/IT;//ohm
24 Ad=-RC*1000/re;//unitless
25 disp(Ad,"Differntial moe gain, Ad");
26 //Answer in the book is wrong for Q point.

```

Scilab code Exa 2.8 RC RE Rid Rid

```

1 ////Ex 2.8
2 clc;
3 clear;
4 close;
5 format('v',5);
6 ICQ=200;//micro A
7 Beta=1000;//unitless
8 Ad=180;//unitless
9 CMRR=80;//dB
10 VT=26;//mV
11 re=VT/(ICQ/1000);//ohm(Let re=re1=re2)
12 RC=Ad*re/1000;//kohm
13 CMRR=10^(CMRR/20);//untless

```

```

14 RE=(CMRR-1)*re/2/1000; //kohm
15 disp(RE,RC," Value of RC & RE(kohm)");
16 Rid=2*Beta*re/1000; //kohm(Let Rid=Rid1=Rid2)
17 disp(Rid," Differntial input resistance , Rid(kohm)");
18 Ric=(Beta+1)*(re+2*RE*1000)/10^6; //Mohm
19 disp(Ric,"Common mode input resistance , Ric(Mohm)");

```

Scilab code Exa 2.9 Operating point Gain and Resistance

```

1  ///Ex 2.9
2  clc;
3  clear;
4  close;
5  format('v',5);
6  Beta=110; // unitless
7  VBE=0.7; //V
8  VT=26; //mV
9  VCC=10; //V
10 VEE=10; //V
11 RC=1.8; //kohm
12 R=3.9; //kohm
13 IExt=(VCC-VBE-(-VEE))/R; //mA
14 IT=IExt; //mA
15 ICQ=IT/2; //mA
16 V1=0; V2=0; //V
17 VE=-2*VBE; //V
18 VC=VCC-ICQ*RC; //V
19 VCEQ=VC-VE; //V
20 Q=[ICQ VCEQ]; // [mA V](Q point)
21 disp(Q,"Q point (ICQ(mA), VCEQ(V)) is ");
22 re=2*VT/IT; //ohm(let re1=re2=re)
23 reD=2*re; //ohm
24 Ad=-RC*1000/reD; // unitless
25 disp(Ad," Differntial moe gain , Ad");
26 BetaD=Beta^2; // unitless

```

```

27 Rid=2*BetaD*reD/1000; //kohm(let Rid1=Rid2=Rid)
28 disp(Rid,"Differential input resistance , Rid(kohm)");
29 //Answer for Ad is wrong(+ve) in the book while it
    is negative.

```

Scilab code Exa 2.10 Differential input resistance

```

1  ////Ex 2.10
2  clc;
3  clear;
4  close;
5  format('v',9);
6  Beta=100; // unitless
7  VBE=0.7; //V
8  R=18.6; //kohm
9  VT=26; //mV
10 VCC=5; //V
11 VEE=5; //V
12 IExt=(VCC-VBE-(-VEE))/R; //mA
13 IT=IExt; //mA
14 re=2*VT/IT; //ohm(let re1=re2=re)
15 Rid=2*Beta*re/1000; //kohm(let Rid1=Rid2=Rid)
16 disp(Rid,"Differential input resistances , Rid1=Rid2(
    kohm)");

```

Scilab code Exa 2.11 Gain and input resistance

```

1  ////Ex 2.11
2  clc;
3  clear;
4  close;
5  format('v',6);
6  Beta=100; // unitless

```

```

7 VBE=0.7; //V
8 RC=2.7; //kohm
9 R=2.2; //kohm
10 VT=26; //mV
11 VCC=10; //V
12 VEE=10; //V
13 IExt=(VEE-VBE)/R; //mA
14 IT=IExt;; //mA
15 IE=IT/2; //mA(Let IE1=IE2=IE)
16 re=2*VT/IT; re1=re; re2=re; re3=re; re4=re //ohm
17 reD=re1+re2; //ohm
18 BetaD=Beta^2; // unitless
19 Ad=-RC*1000/reD; // unitless
20 disp(Ad," Differential voltage gain , Ad")
21 Rid=2*BetaD*reD/1000; //kohm(let Rid1=Rid2=Rid)
22 disp(Rid," Differntial input resistances , Rid1=Rid2(
    kohm)");
23 //Answer in the bok is not accurate.

```

Chapter 3

Operational Amplifiers and their Parameters

Scilab code Exa 3.1 Open loop gain

```
1 //Ex 3.1
2 clc;
3 clear;
4 close;
5 format('e',8);
6 fBW=4; //MHz
7 fo=10; //Hz
8 AOL=fBW*10^6/fo; // unitless
9 disp(AOL,"Open loop gain is");
```

Scilab code Exa 3.2 Time taken

```
1 //Ex 3.2
2 clc;
3 clear;
4 close;
```

```

5 format('v',5);
6 V1=-10; //V
7 V2=10; //V
8 SR=0.5; //V/micro second
9 delta_Vo=V2-V1; //V
10 delta_t=delta_Vo/SR; //micro second
11 disp(delta_t,"Time taken by op-amp is (micro second)");

```

Scilab code Exa 3.3 Maximum Voltage

```

1 //Ex 3.3
2 clc;
3 clear;
4 close;
5 format('v',6);
6 SR=0.6; //V/micro second
7 f=100; //kHz
8 Vm=(SR/10^-6)/(2*pi*f*1000); //V
9 disp(Vm,"Maximum voltage , Vm is (V)");

```

Scilab code Exa 3.4 Maximum Frequency

```

1 //Ex 3.4
2 clc;
3 clear;
4 close;
5 format('v',5);
6 SR=0.5; //V/micro second
7 Vm=10; //V
8 f=100; //kHz
9 fm=(SR/10^-6)/(2*pi*Vm); //Hz
10 disp(fm/1000,"Maximum frequency , fm is (kHz)");

```

Scilab code Exa 3.5 Slew rate

```
1 //Ex 3.5
2 clc;
3 clear;
4 close;
5 format('v',5);
6 delta_t=0.3/2; //micro second
7 V1=-3; //V
8 V2=3; //V
9 delta_Vo=V2-V1; //V
10 SR=delta_Vo/delta_t; //V/micro second
11 disp(SR,"Slew rate is (V/micro second)");
```

Scilab code Exa 3.6 Close Loop Voltage Gain

```
1 //Ex 3.6
2 clc;
3 clear;
4 close;
5 format('v',5);
6 SR=2; //V/micro second
7 delta_Vin=0.8; //V
8 delta_t=10; //micro second
9 Acl_max=SR/(delta_Vin/delta_t); //unitless
10 disp(Acl_max,"Maximum close loop voltage gain is");
```

Scilab code Exa 3.7 Limiting Frequency

```
1 //Ex 3.7
2 clc;
3 clear;
4 close;
5 format('v',5);
6 SR=6; //V/micro second
7 //Part (i)
8 Vm=1; //V
9 fm=(SR/10^-6)/(2*%pi*Vm); //Hz
10 disp(fm/1000,"part (i) Maximum frequency , fm is (kHz)
    ");
11 //Part (i)
12 Vm=10; //V
13 fm=(SR/10^-6)/(2*%pi*Vm); //Hz
14 disp(fm/1000,"part (ii) Maximum frequency , fm is (kHz
    )");
```

Chapter 4

Opamps with negative feedback

Scilab code Exa 4.1 Bandwidth with feedback

```
1  ////Ex 4.1
2  clc;
3  clear;
4  close;
5  format('v',9);
6  AOL=2*10^5; // unitless
7  fo=5; //Hz
8  ACL=100; // unitless
9  SF=AOL/ACL; // unitless
10 fodash=SF*fo; //Hz
11 disp(fodash/1000,"Bandwidth with feedback(kHz)");
```

Scilab code Exa 4.2 Acl Rif Rof fodash

```
1  ////Ex 4.2
2  clc;
3  clear;
4  close;
```

```

5  format('v',6);
6  AOL=2*10^5; // unitless
7  Ri=1.5; //kohm
8  Rf=12; //kohm
9  Rio=1; //Mohm
10 Ro=100; //ohm
11 fo=5; //Hz
12 Beta=Ri/(Ri+Rf); // unitless
13 SF=(1+AOL)*Beta; // unitless
14 ACL=AOL/SF; // unitless
15 disp(ACL," Value of ACL");
16 //In case of ideal opamp
17 ACL=1+Rf/Ri; // unitless
18 disp(ACL," In case of ideal opamp, Value of ACL");
19 Rif=Rio*SF; //kohm
20 disp(Rif," Value of Rif(Mohm)");
21 disp("This is a large value can be assumed as infity
      resistance.");
22 format('v',5);
23 Rof=Ro/SF; //mohm
24 disp(Rof*1000," Value of Rof(mohm)");
25 fodash=SF*fo; //Hz
26 disp(fodash/1000," Bandwidth with feedback , fo_dash(
      kHz)");
27 //Answer for Rif in the book has mistake of unit.

```

Scilab code Exa 4.3 Impedence and gain

```

1  ////Ex 4.3
2  clc;
3  clear;
4  close;
5  format('v',9);
6  AOL=%inf; // unitless
7  Rio=%inf; //ohm

```

```

8 Ri=1; //kohm
9 Rf=15; //kohm
10 SF=%inf; //unitless; // as SF=1+AOL*Beta
11 Beta=Ri/(Ri+Rf); //unitless
12 ACL=1/Beta; //unitless
13 disp(Rio,"Input impedance(ohm) for ideal opamp is ")
    ;
14 disp(ACL,"Gain of the circuit , ACL");

```

Scilab code Exa 4.4 Input and output impedance

```

1 ///Ex 4.4
2 clc;
3 clear;
4 close;
5 format('v',9);
6 AOL=400; //unitless
7 Rio=500; //kohm
8 Ro=75; //ohm
9 ACL=100; //unitless
10 SF=AOL/ACL; //unitless
11 Rif=Rio*SF; //kohm
12 disp(Rif/1000,"Input impedance , Rif(Mohm)");
13 Rof=Ro/SF; //ohm
14 disp(Rof,"Output impedance , Rof(ohm)");

```

Scilab code Exa 4.5 Non Inverting Amplifier

```

1 ///Ex 4.5
2 clc;
3 clear;
4 close;
5 format('v',5);

```

```

6 ACL=200; // unitless
7 AOL=2*10^5; // unitless
8 Rio=2; //Mohm
9 Ro=75; //ohm
10 Ri=1; //kohm(Assumed)
11 SF=AOL/ACL; // unitless
12 Beta=(SF-1)/AOL; // unitless
13 Rf=Ri*(1-Beta)/Beta; //kohm
14 disp(Ri,"Input impedance , Rif(kohm)");
15 disp(Rf,"Feedback impedance , Rf(kohm)");

```

Scilab code Exa 4.6 Close Loop Voltage Gain

```

1 ////Ex 4.6
2 clc;
3 clear;
4 close;
5 format('v',5);
6 AOL=50; // unitless
7 Beta=0.8; // unitless
8 deltaAOL=-20; //%(Change in open loop gain)
9 deltaBeta=15; //%(Change in feedback factor)
10 AOLnew=AOL+AOL*deltaAOL/100; //unitless(AOL after
    change)
11 Betanew=Beta+Beta*deltaBeta/100; // unitless(Beta
    after change)
12 ACL=AOLnew/(1+AOLnew*Betanew); // unitless
13 disp(ACL,"Close loop gain , ACL");

```

Scilab code Exa 4.7 Acl Rif Rof

```

1 ////Ex 4.7
2 clc;

```



```

3 clear;
4 close;
5 format('v',5);
6 AOL=500; // unitless
7 Rio=300; //kohm
8 Ro=100; //ohm
9 ACL=AOL/(1+AOL); // unitless
10 Rif=Rio*(1+AOL)/1000; //Mohm
11 Rof=Ro/(1+AOL); //ohm
12 disp(ACL," Close loop gain , ACL");
13 disp(Rif," Value of Rif(Mohm)");
14 disp(Rof," Value of Rof(ohm)");

```

Scilab code Exa 4.8 Output Voltage

```

1 ////Ex 4.8
2 clc;
3 clear;
4 close;
5 format('v',5);
6 Iin=1; //mA
7 Rf=1; //kohm
8 IB=0; //for ideal opamp
9 If=Iin-IB; //mA
10 Vout=-If*Rf; //V
11 disp(Vout," Output Voltage (V)");

```

Scilab code Exa 4.9 Variation in output Voltage

```

1 ////Ex 4.9
2 clc;
3 clear;
4 close;

```

```

5 format('v',5);
6 I2=1; //mA
7 Rf=4.7; //kohm
8 //Case 1st
9 I1=500; //micro A
10 Vout1=-I1*10^-6*Rf*10^3; //V
11 disp(Vout1,"For 500 micro A current , Output Voltage(
    V)");
12 //Case 2nd
13 I2=1; //mA
14 Vout2=-I2*10^-3*Rf*10^3; //V
15 disp(Vout2,"For 1 mA current , Output Voltage(V)");
16 deltaVout=Vout2-Vout1; //V
17 disp(deltaVout,"Variation in Output Voltage(V)");

```

Scilab code Exa 4.10 Gain and impedance

```

1 //Ex 4.10
2 clc;
3 clear;
4 close;
5 format('v',5);
6 AOL=2*10^5; //unitless
7 Rio=2; //Mohm
8 Ro=75; //ohm
9 Ri=1; //kohm
10 Rf=10; //kohm
11 ACL=-AOL*Rf/(Rf+Ri+AOL*Ri); //unitless (Exact)
12 disp(ACL,"Exact close loop voltage gain");
13 ACL=-Rf/Ri; //unitless (Approximate)
14 disp(ACL,"Approximate close loop voltage gain");
15 Beta=Ri/(Ri+Rf); //unitless
16 SF=1+AOL*Beta; //unitless
17 Rif=Rio*10^6/SF; //ohm
18 disp(Rif,"Input impedance after feedback(ohm)");

```

Scilab code Exa 4.11 Gain and Bandwidth

```
1  ///Ex 4.11
2  clc;
3  clear;
4  close;
5  format('v',5);
6  Ri=2; //kohm
7  Rf=200; //kohm
8  //For 741C
9  fo=5; //Hz
10 AOL=2*10^5; // unitless
11 UGB=1; //MHz
12 ACL=-AOL*Rf/(Rf+Ri+AOL*Ri); // unitless (Exact)
13 disp(ACL," Close loop voltage gain");
14 fodash=fo*AOL/-ACL; //Hz
15 disp(fodash/1000," Bandwidth , fo_dash (kHz)");
```

Scilab code Exa 4.12 Calculate Gain

```
1  ///Ex 4.12
2  clc;
3  clear;
4  close;
5  format('v',6);
6  Beta=0.06; //feedback factor
7  fo=100; //Hz
8  AOL=40000; //unitless(at dc)
9  SFdc=1+AOL*Beta; //sacrifice factor at dc
10 f=1; //kHz
11 f=f*10^3; //Hz
```

```

12 SF1=1+AOL*Beta/sqrt(1+f^2/fo^2);//sacrifice factor
    at 1 kHz
13 //(a)
14 ACL=AOL/SFdc;//(unitless)exact close loop gain at dc
15 disp(ACL,"Exact close loop gain at dc");
16 //(b)
17 ACL=1/Beta;//(unitless)approximate close loop gain
    at dc
18 disp(ACL,"Approximate close loop gain at dc");
19 //(c)
20 AOL=3980;//unitless(at dc)
21 ACL=AOL/SF1;//(unitless)exact close loop gain at 1
    kHz
22 disp(ACL,"Exact close loop gain at 1kHz");

```

Scilab code Exa 4.13 Input and output impedance

```

1  ////Ex 4.13
2  clc;
3  clear;
4  close;
5  format('v',5);
6  Beta=0.04;//feedback factor
7  AOL=5000;//unitless(at dc)
8  Rio=40;//kohm
9  Ro=1;//kohm
10 SF=1+AOL*Beta;//sacrifice factor at dc
11 Rif=Rio/SF*1000;//ohm
12 disp(Rif,"Input impedance(ohm)");
13 Rof=Ro*1000/SF;//ohm
14 disp(Rof,"Output impedance(ohm)");

```

Chapter 5

Linear Applications of OPamps

Scilab code Exa 5.1 Output Voltage

```
1 //Ex 5.1
2 clc;
3 clear;
4 close;
5 format('v',5);
6 V1=2;V2=3;V3=4;V4=5; //V
7 R1=10;R2=15;R3=22;R4=50; //kohm
8 Rf=10; //kohm
9 Vout=-Rf/R1*V1-Rf/R2*V2-Rf/R3*V3-Rf/R4*V4; //V
10 disp(Vout,"Output voltage of the circuit(V)");;
```

Scilab code Exa 5.2 Resistor R1 and R2

```
1 //Ex 5.1
2 clc;
3 clear;
4 close;
5 format('v',5);
```

```

6 Rf=240; //kohm
7 //Vout=-4*Vx+3*Vy;
8 // case 1st
9 Vy=0; //V(But Vx is not=0)
10 //Vox=-Rf/R1*Vx=-4*Vx
11 R1=Rf/4; //kohm
12 // case 2nd
13 Vx=0; //V(But Vy is not=0)
14 //Voy=(1+Rf/R1)*R2*Vy/(R1+R2)=3*Vy
15 R2=3/(1+Rf/R1)*R1/((1-3/(1+Rf/R1)))
16 disp(R1," Resistance R1(kohm)");
17 disp(R2," Resistance R2(kohm)");

```

Scilab code Exa 5.3 Output Voltage

```

1 //Ex 5.3
2 clc;
3 clear;
4 close;
5 format('v',5);
6 V1=-2;V2=3; //V
7 R1=50;R2=100; //kohm
8 Rf=250; //kohm
9 //I1+I2=If with IB=0 & Vx=0
10 Vout=-(V1/R1+V2/R2)*Rf; //V
11 disp(Vout," Output Voltage (V)");

```

Scilab code Exa 5.4 Output Voltage

```

1 //Ex 5.4
2 clc;
3 clear;
4 close;

```

```

5 format('v',5);
6 V1=-2;V2=3;//V
7 R1=12;R2=12;R3=10//kohm
8 Rf=12;Ri=12;//kohm
9 Rt=2;//kohm
10 Vyx=200*10^-6;//V
11 Vout=Rf/Ri*(1+2*R3/Rt)*Vyx;//V
12 disp(Vout*1000,"Output Voltage(mV)");

```

Scilab code Exa 5.5 Instrumentation Amplifier

```

1 //Ex 5.5
2 clc;
3 clear;
4 close;
5 format('v',4);
6 Ad=5:200;//Gain
7 R1max=50;//kohm(Potentiometer)
8 R4=10;R3=10;//kohm
9 //Case 1st : Ad=Admin &R1=R1max
10 R1=R1max;//kohm
11 R2=(min(Ad)-1)/2*R1max
12 //Case 2nd : Ad=Admax &R1=R1min
13 R1min=2*R2/(max(Ad)-1);//kohm
14 disp(R2,"Resistance R2(kohm)");
15 disp(R1min,"Minimum value of resistance R1(kohm)");

```

Scilab code Exa 5.6 Gain and Impedence

```

1 //Ex 5.6
2 clc;
3 clear;
4 close;

```

```

5  format('v',8);
6  R3=1; //kohm
7  Rt=5; //kohm
8  Ri=1.8;R1=1.8; //kohm
9  Rf=18;R2=18; //kohm
10 Vs=15; //V
11 AoL=2*10^5; //Gain( for 741C)
12 Rio=2 //Mohm
13 Ro=75 //Mohm
14 fo=5; //Hz
15 fBW=1; //MHz
16 Ad=Rf/Ri*(1+2*R3/Rt); //differential gain
17 disp(Ad," Differential gain");
18 Beta=(R3+Rt)/(2*R3+Rt); //unitless
19 Rix=Rio*10^6*(1+AoL*Beta); //ohm
20 disp(Rix," Input impedance , Rix(ohm)");
21 Rof=Ro/(1+AoL/Ad); //ohm
22 disp(Rof," Output impedance , Rof(ohm)");
23 //Answer in the book is wron for Rix.

```

Scilab code Exa 5.8 Output Voltage

```

1  //Ex 5.8
2  clc;
3  clear;
4  close;
5  format('v',8);
6  Ri=10; //kohm
7  Rf=15; //kohm
8  Vs=9; //V
9  //Part (a)
10 Ra=120;Rb=120;Rc=120;Rd=120; //ohm
11 Vx=0;Vy=0 //V(as Bridge is balanced)
12 Vout=(Vy-Vx)*Rf/Ri; //V
13 disp(Vout," (a) Output Voltage(V)");

```



```

14 //Part (b)
15 Ra=120;Rb=120;Rc=120;Rd=150; //ohm
16 Vx=Rb*Vs/(Ra+Rb); //V
17 Vy=Rc*Vs/(Rc+Rd) //V
18 Vyx=Vy-Vx; //V
19 Vout=(Vy-Vx)*Rf/Ri; //V
20 disp(Vout, "(b) Output Voltage(V)");

```

Scilab code Exa 5.9 Output Voltage

```

1 //Ex 5.9
2 clc;
3 clear;
4 close;
5 format('v',8);
6 Vin=2; //V
7 Rf=2*2/(2+2)+2; //kohm
8 R1=1; //kohm
9 Vout=-Rf/R1*Vin; //V
10 disp(Vout, "Output Voltage(V)");

```

Scilab code Exa 5.11 Resistor Ri and Rf

```

1 //Ex 5.11
2 clc;
3 clear;
4 close;
5 format('v',4);
6 G=20; //dB(Gain)
7 f3dB=2; //kHz
8 Cf=0.05; //micro F
9 Rf=1/(f3dB*1000*2*%pi*Cf/1000000)/1000; //kohm
10 G=10^(G/20); //Gain(unitless)

```

```

11 Ri=Rf*1000/G; //ohm
12 disp(Rf," Resistance Rf(kohm)");
13 disp(Ri," Resistance Ri(ohm)");

```

Scilab code Exa 5.13 Output of opamp

```

1 //Ex 5.13
2 clc;
3 clear;
4 close;
5 format('v',4);
6 t2=50; //ms(After open the switch)
7 R=40; //kohm
8 C=0.2; //micro F
9 V2=3; //V
10 Vin=5; //V
11 //For Ideal op-amp V1=V2
12 t1=0; //s
13 Vout1=V2; //V
14 V1=V2; //V
15 t2=t2*10^-3; //s
16 Vout2=-1/(R*10^3*C*10^-6)*integrate('Vin-V1','T',0,
    t2)+Vout1; //V
17 //Here we have t=0 switch closed Vout=3V
18 t=[t1*1000 t2*1000]; //ms
19 Vout=[Vout1 Vout2]; //V
20 plot(t,Vout);
21 title('Vout Vs time after switch is opened');
22 xlabel('t(ms)');
23 ylabel('Vout(V)');

```

Scilab code Exa 5.14 Output Voltage

```

1 //Ex 5.14
2 clc;
3 clear;
4 close;
5 format('v',4);
6 R1=1;//kohm
7 R2=1;//kohm
8 R3=1;//kohm
9 Rf=R2+R3;//kohm
10 Vin=1;//V
11 //Capacitor remains open circuited for steady state
    in both cases.
12 Vout=-Rf/R1*Vin;//V
13 disp(Vout,"Output Voltage(V)");

```

Scilab code Exa 5.16 Design required circuit

```

1 //Ex 5.16
2 clc;
3 clear;
4 close;
5 format('v',4);
6 //From the given equation  $V_{out} = -\int (5V_x + 2V_y + 4V_z) dt$  :
7 R1Cf=1/5;R2Cf=1/2;R3Cf=1/4;
8 disp("Various design parameters are : ");
9 Cf=10;//micro F////Chosen for the design
10 disp(Cf,"Capacitance(micro F)");
11 R1=R1Cf/(Cf*10^-6)/1000;//kohm
12 R2=R2Cf/(Cf*10^-6)/1000;//kohm
13 R3=R3Cf/(Cf*10^-6)/1000;//kohm
14 disp(R1,"Resistance R1(kohm)");
15 disp(R2,"Resistance R1(kohm)");
16 disp(R3,"Resistance R1(kohm)");

```

Scilab code Exa 5.17 Output of opamp

```
1 //Ex 5.17
2 clc;
3 clear;
4 close;
5 format('v',4);
6 f=10;//kHz
7 Rf=3.2;//kohm
8 Ci=0.001;//micro F
9 dt=5;//micro seconds
10 dVin=5-(-5);//V(When voltage changes from -5V to +5V
   )
11 Vout=-Rf*1000*Ci*10^-6*dVin/(dt*10^-6);//V
12 disp(Vout,"When voltage changes from -5V to +5V, The
   output Voltage(V)");
13 dVin=-5-(+5);//V(When voltage changes from +5V to -5
   V)
14 Vout=-Rf*1000*Ci*10^-6*dVin/(dt*10^-6);//V
15 disp(Vout,"When voltage changes from +5V to -5V, The
   output Voltage(V)");
```

Scilab code Exa 5.18 Design a differentiator

```
1 //Ex 5.18
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fmin=200;//Hz
7 fmax=1;//kHz
8 fa=fmax;//kHz
```

```

 9 disp(" Various design parameters are : ");
10 Ci=0.05; //micro F//// Chosen for the design
11 disp(Ci," Capacitance Ci(micro F)");
12 format('v',4);
13 fb=10*fa; //kHz
14 Rf=1/(2*%pi*fa*10^3*Ci*10^-6)/1000; //kohm
15 disp(Rf," Resistance Rf(kohm)");
16 Ri=1/(2*%pi*fb*10^3*Ci*10^-6); //ohm
17 disp(Ri," Resistance Ri(ohm)");
18 format('v',6);
19 Cf=Ri*Ci/(Rf*10^3); //micro F
20 disp(Cf," Capacitance Cf(micro F)");

```

Scilab code Exa 5.19 Design a differentiator

```

1 //Ex 5.19
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fmax=100; //Hz
7 fa=fmax; //Hz
8 disp(" Various design parameters are : ");
9 Ci=0.1; //micro F//// Chosen for the design
10 disp(Ci," Capacitance Ci(micro F)");
11 Rf=1/(2*%pi*fa*Ci*10^-6)/1000; //kohm
12 disp(Rf," Resistance Rf(kohm)");
13 disp(" Use f=15 kohm");
14 fb=15*fa; //kHz
15 Ri=1/(2*%pi*fb*Ci*10^-6)/1000; //kohm
16 disp(Ri," Resistance Ri(kohm)");
17 disp(" Use Ri=1 kohm");
18 format('v',6);
19 Cf=Ri*Ci/Rf; //micro F
20 disp(Cf," Capacitance Cf(micro F)");

```

21 //Answer in the book is not accurate for Cf.

Scilab code Exa 5.20 Rf Ri and Cf

```
1 //Ex 5.20
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f=50;//Hz
7 T=1/f;//s(Period)
8 Ci=0.05;//micro F
9 RiCi=0.01*T;//Given
10 Ri=RiCi/(Ci*10^-6)/1000;//kohm
11 disp(Ri,"Resistance Ri(kohm)");
12 //Vout=-.002*dVin/dt given
13 //On comparing with Vout=-Rf*Ci*dVin/dt
14 RfCi=0.002;//on comparing
15 Rf=RfCi/(Ci*10^-6)/1000;//kohm
16 disp(Rf,"Resistance Rf(kohm)");
17 Cf=Ri*Ci/Rf;//micro F
18 format('v',6);
19 disp(Cf,"Capacitance Cf(micro F)");
```

Chapter 6

Oscillators and waveform generators

Scilab code Exa 6.1 Design a RC phase shift oscillator

```
1 //Ex 6.1
2 clc;
3 clear;
4 close;
5 format('v',6);
6 f0=600;//Hz// Oscillating Frequency
7 disp("Various design parameters are :-");
8 C=0.05;//micro F//Chosen for the design
9 disp(C,"Capacitance(micro F)");
10 format('v',5);
11 R=1/(2*%pi*f0*sqrt(6)*C*10^-6);//ohm
12 R=R/1000;//kohm
13 disp(R,"Resistance R(kohm)");
14 disp("We can use R=2.2 kohm for design purpose.")
15 //To avoid loading effect
16 Ri=10*R;//kohm//Ri>=10*R
17 Ri=ceil(Ri);//kohm
18 disp(Ri,"Resistance Ri(kohm)");
19 Rf=29*Ri;//kohm//Rf>=29*Ri
```

```

20 disp(Rf," Resistance Rf(kohm)");
21 disp("We can use Rf=640 kohm for design purpose.")
22 Rf=640; //kohm
23 //Balancing the circuit
24 Rom=Rf*Ri/(Rf+Ri); //kohm
25 Rom=ceil(Rom); //kohm
26 format('v',6);
27 disp(Rom," Resistance Rom(kohm)");

```

Scilab code Exa 6.3 Design a wein bridge oscillator

```

1 //Ex 6.3
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=12; //kHz// Oscillating Frequency
7 disp(" Various design parameters are :-");
8 C=0.01; //micro F// Chosen for the design between 0.01
   & 1 micro F
9 disp(C," Capacitance(micro F)");
10 R=1/(2*%pi*f0*1000*C*10^-6); //ohm
11 R=R/1000; //kohm
12 disp(R," Resistance R(kohm)");
13 format('v',5);
14 Ri=3*R/2; //kohm// Ri >= 3*R/2
15 disp(Ri," Resistance Ri(kohm)");
16 disp("We can use Ri=2.2 kohm for design purpose.")
17 Ri=2.2; //kohm
18 Rf=2*Ri; //kohm
19 disp(Rf," Resistance Rf(kohm)");
20 disp("We should use Rf=4.7 kohm for design purpose."
   )

```

Scilab code Exa 6.5 Design a wein bridge oscillator

```
1 //Ex 6.5
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=2;//kHz// Oscillating Frequency
7 disp("Various design parameters are :-");
8 C=0.05;//micro F//Chosen for the design
9 disp(C,"Capacitance(micro F)");
10 R=1/(2*pi*f0*1000*C*10^-6);//ohm
11 R=R/1000;//kohm
12 disp(R,"Resistance R(kohm)");
13 format('v',5);
14 Ri=3*R/2;//kohm//Ri>=3*R/2
15 format('v',4);
16 disp(Ri,"Resistance Ri(kohm)");
17 disp("We can use Ri=2.2 kohm for design purpose.")
18 Rf=2*Ri;//kohm
19 disp(Rf,"Resistance Rf(kohm)");
20 disp("We should use 5k pot for Rf.")
```

Scilab code Exa 6.6 Frequency of oscillation

```
1 //Ex 6.6
2 clc;
3 clear;
4 close;
5 format('v',6);
6 //Data given
7 R1=1;//kohm
```

```

8 R2=1; //kohm
9 R=1; //kohm
10 C=4.7; //micro F
11 f0=1/(2*%pi*R*10^3*C*10^-6); //Hz// Oscillating
    Frequency
12 disp(f0," Oscillation frequency (Hz)");

```

Scilab code Exa 6.7 Design a quadrature oscillator

```

1 //Ex 6.7
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=200; //Hz// Oscillating Frequency
7 disp(" Various design parameters are :-");
8 C=0.05; //micro F// Chosen for the design
9 disp(C," Capacitance (micro F)");
10 R=0.159/(f0*C*10^-6); //ohm
11 R=R/1000; //kohm
12 disp(R," Resistance R(kohm)");
13 disp("We should use R=510 kohm for the design.");
14 R=510; //kohm
15 C1=C; C2=C; C3=C; //micro F
16 disp(C3,C2,C1," Capacitance C1, C2 & C3(micro F)");
17 R2=R; R3=R; //kohm
18 disp(R3,R2," Resistance R2, R3(kohm)");
19 disp("1000k pot can be used.")
20 //Answer for R is calculated wrong in the textbook.

```

Scilab code Exa 6.8 Causes of distortion

```

1 //Ex 6.8

```

```

2  clc;
3  clear;
4  close;
5  format('v',5);
6  Rf=570; //kohm
7  Ri=15; //kohm
8  A=Rf/Ri; //Gain of the circuit
9  Amin=29; //Minimum Gain requirement of RC phase shift
      oscillator
10 deltaA=(A-Amin)/Amin*100; //%(Exceeding Gain)
11 disp(deltaA,"Gain is exceeded by(%) ");
12 disp("It will cause distortion at output.");

```

Scilab code Exa 6.9 Frequency of oscillation

```

1  //Ex 6.9
2  clc;
3  clear;
4  close;
5  format('v',6);
6  disp("Part (a)");
7  L1=25; //micro H
8  L2=10; //micro H
9  Rf=22; //kohm
10 C=0.01; //micro F
11 LT=L1+L2; //micro H
12 fr=1/(2*%pi*sqrt(C*10^-6*LT*10^-6)); //Hz
13 fr=fr/1000; //kHz
14 f0=fr; //kHz
15 disp(f0," Oscillation frequency(kHz)");
16 Ri=Rf/(L1/L2); //kohm
17 disp(Ri," Resistance Ri(kohm)");
18 disp("Part (b)");
19 C1=220; //pF
20 C2=680; //pF

```

```

21 Rf=22; //kohm
22 L=1; //mH
23 CT=C1*C2/(C1+C2); //pF
24 fr=1/(2*%pi*sqrt(L*10^-3*CT*10^-12)); //Hz
25 fr=fr/1000; //kHz
26 f0=fr; ///kHz
27 f0=round(f0); //kHz
28 disp(f0," Oscillation frequency (kHz)");
29 Ri=Rf/(C1/C2); //kohm
30 disp(Ri," Resistance Ri (kohm)");

```

Scilab code Exa 6.10 Design a square wave generator

```

1 //Ex 6.10
2 clc;
3 clear;
4 close;
5 format('v',6);
6 f0=1; ///kHz
7 Vsat=14; //V
8 disp(" Various design parameters are :-");
9 C1=0.05; //micro F//Chosen for the design
10 disp(C1," Capacitance (micro F)");
11 Rf=1/(2*f0*10^3*C1*10^-6)/1000; //kohm
12 disp(Rf," Resistance Rf(kohm)");
13 //R2=0.86*R1 and Rf=R1||R2
14 R2byR1=0.86; //from R2=0.86*R1
15 R2=Rf*(1+R2byR1); //kohm
16 R1=R2/R2byR1; //kohm
17 disp(R1," Resistance R1(kohm)");
18 disp(" Use R1=22 kohm for the design.");
19 disp(R2," Resistance R2(kohm)");

```

Scilab code Exa 6.11 Find Rf and C

```
1 //Ex 6.11
2 clc;
3 clear;
4 close;
5 format('v',6);
6 T=10; //ms//(Time period)
7 f0=1/(T*10^-3); //Hz
8 C=0.05; //micro F//Chosen for the design
9 //Formula : f0=1/{2*Rf*C*log(1+2*R2/R1)}
10 Rf=1/(f0*2*C*10^-6*log(1+2))/1000; //kohm//By putting
    R1=R2 for this case
11 Rf=round(Rf); //kohm
12 disp(Rf,"Resistance Rf(kohm)");
13 disp(C,"Capacitance for the design(micro F)");
```

Scilab code Exa 6.12 Frequency of output

```
1 //Ex 6.12
2 clc;
3 clear;
4 close;
5 format('v',6);
6 R1=4.7; //kohm
7 R2=3.3; //kohm
8 Rf=2; //kohm
9 C=0.1; //micro F
10 f0=1/2/(Rf*1000)/(C*10^-6)/log(1+2*R2/R1)/1000; //kHz
11 disp(f0,"Frequency of output signal(kHz)");
```

Scilab code Exa 6.13 Triangular wave generator

```

1 //Ex 6.13
2 clc;
3 clear;
4 close;
5 format('v',6);
6 f0=1.5; //kHz
7 Vout=6; //V////peak to peak
8 Vsat=13.5; //V
9 disp("Various design parameters are : ");
10 R2=10; //kohm////chosen for the design
11 R1=R2*2*Vsat/Vout; //kohm
12 disp(R1,"R1(kohm)");
13 disp(R2,"R2(kohm)");
14 disp("Use R1=50 kohm for the design");
15 //Let Cf=0.05 micro F for the design
16 Cf=0.05; //micro F
17 disp(Cf,"Cf(micro F)");
18 Ri=R1*1000/(f0*1000)/4/(Cf*10^-6*R2*1000)/1000; //
    kohm
19 disp(Ri,"Ri(kohm)");

```

Scilab code Exa 6.14 Peak output voltage

```

1 //Ex 6.14
2 clc;
3 clear;
4 close;
5 format('v',4);
6 //Data given
7 R1=6.8; //kohm
8 Ri=100; //kohm
9 R2=1.5; //kohm
10 Cf=0.01; //micro F
11 Vsat=14; //V
12 Vo_pp=2*R2/R1*Vsat; //V////Peak to peak output of

```

```

    triangular wave
13 disp(Vo_pp,"Peak to peak output of triangular wave(V
    )");
14 format('v',5);
15 f0=R1*1000/(4*Ri*10^3*Cf*10^-6*R2*10^3)/1000; //kHz//
    Oscillating Frequency
16 disp(f0," Oscillation frequency (Hz)");

```

Scilab code Exa 6.15 Triangular wave generator

```

1 //Ex 6.15
2 clc;
3 clear;
4 close;
5 format('v',4);
6 //Data given
7 f0=1; //kHz
8 Vo_pp=7; //V
9 Vsat=14; //V
10 disp(" Various design parameters are :-");
11 //Let R2=10; //kohm for the design
12 R2=10; //kohm
13 R1=2*R2*Vsat/Vo_pp; //kohm
14 disp(R1," R1(kohm)");
15 disp(R2," R2(kohm)");
16 //Choose Cf=0.1 micro F for the design
17 Cf=0.1; //micro F
18 disp(Cf," Cf(micro F)");
19 Ri=R1*10^3/(4*f0*10^3*Cf*10^-6*R2*10^3)/1000; //kohm
20 disp(Ri," Ri(kohm)");

```

Scilab code Exa 6.16 Frequency of output

```

1 //Ex 6.16
2 clc;
3 clear;
4 close;
5 format('v',4);
6 //Data given
7 tau=1;//ms(time period)
8 R1byR2=1.8:0.2:9;//range of R1/R2
9 Beta_min=1/(1+min(R1byR2));//minimum value of Beta
10 Beta_max=1/(1+max(R1byR2));//maximum value of Beta
11 Tmax=2*tau*log((1+Beta_min)/(1-Beta_min));//ms////
    For minimum value of Beta
12 fmin=1/(Tmax*10^-3);//Hz
13 Tmin=2*tau*log((1+Beta_max)/(1-Beta_max));//ms////
    For maximum value of Beta
14 fmax=1/(Tmin*10^-3)/1000;//kHz
15 disp("Frequency range is "+string(fmin)+" Hz to "+
    string(fmax)+" kHz.");

```

Scilab code Exa 6.17 Series and parallel resonant frequencies

```

1 //Ex 6.17
2 clc;
3 clear;
4 close;
5 format('v',4);
6 //Data given
7 Ls=3;//H
8 Cs=0.05;//pF
9 Rs=2;//kohm
10 Cm=10;//pF
11 fS=1/2/%pi/sqrt(Ls*Cs*10^-12)/1000;//kHz
12 disp(fS,"Series resonant frequency (kHz)");
13 CT=Cm*Cs/(Cm+Cs);//pF////Equivalent capacitance
14 fP=1/2/%pi/sqrt(Ls*CT*10^-12)/1000;//kHz

```



```
15 disp(fP," Parallel resonant frequency (kHz)");
```

Scilab code Exa 6.18 Design a function generator

```
1 //Ex 6.18
2 clc;
3 clear;
4 close;
5 format('v',5);
6 //Data given
7 f0=5; //kHz
8 D=60; //%////duty cycle
9 VCC=12; //V
10 //As  $D=t1/(t1+t2)$ 
11  $t2BYt1=1/(D/100)-1$ ; //ratio of t1 & t2
12  $//RB/(2*RA-RB)=t2/t1$ 
13  $RAbyRB=(1/t2BYt1+1)/2$ ; //Ratio of RA & RB
14 disp(" Various design parameters are :");
15 //Let CT=0.05 micro F for this design choosing
    between 0.01 & 1 microo F
16 CT=0.05; //micro F
17 disp(CT,"CT(micro F)");
18  $RA=1/(f0*10^3)/(5/3)^2/(CT*10^-6)/1000$ ; //kohm
19 disp(RA,"RA(kohm)");
20  $RB=RA/RAbyRB$ ; //kohm
21 disp(RB,"RB(kohm)");
```

Scilab code Exa 6.19 V0 V7 I and fo

```
1 //Ex 6.19
2 clc;
3 clear;
4 close;
```

```

5  format('v',6);
6  //Data given
7  Rf=15; //kohm
8  RT1=4.7; //kohm
9  R1=56; //kohm
10 R2=6.8; //kohm
11 R3=10; //kohm
12 R4=1; //kohm
13 R5=1; //kohm
14 CB=1; //micro F
15 CT=0.05; //mic
16 VCC=15; //V
17 V1=-15; //V////Voltage given through the resistance(
    R1) 56 kohm
18 disp("Part (i)");
19 Vin=2; //V
20 Vo=Rf/R1*(-V1)-Rf/R2*Vin; //V
21 disp(Vo,"Voltage Vo(V)");
22 N_VCC=0; //V////-VCC////voltage given to the 12th pin
    of IC
23 V7=N_VCC+3; //V
24 disp(V7,"Voltage V7(V)");
25 I=(V7-Vo)/RT1; //mA
26 disp(I,"Current I(mA)");
27 Rmult=R4*R5/(R4+R5)+R3; //kohm////on pin 3
28 disp(Rmult,"Total resistance on pin 3, Rmult(kohm)");
    ;
29 format('v',4);
30 f0=0.32*I*10^-3/(CT*10^-6)/1000; //kHz
31 disp(f0,"Oscillation frequency(kHz)");
32 disp("Part (ii)");
33 format('v',4);
34 Vin=5; //V
35 Vo=Rf/R1*(-V1)-Rf/R2*Vin; //V
36 disp(Vo,"Voltage Vo(V)");
37 N_VCC=0; //V////-VCC////voltage given to the 12th pin
    of IC
38 V7=N_VCC+3; //V

```

```
39 disp(V7," Voltage V7(V)");
40 I=(V7-Vo)/RT1;//mA
41 format('v',6);
42 disp(I," Current I(mA)");
43 Rmult=R4*R5/(R4+R5)+R3;//kohm////on pin 3
44 disp(Rmult," Total resistance on pin 3, Rmult(kohm)")
    ;
45 f0=0.32*I*10^-3/(CT*10^-6)/1000;//kHz
46 disp(f0," Oscillation frequency(kHz)");
```

Chapter 7

The 555 timer

Scilab code Exa 7.1 Monostable Multivibrator

```
1  ///Ex 7.1
2  clc;
3  clear;
4  close;
5  format('v',9);
6  th=4; //ms
7  VCC=10; //V
8  C=0.05; //micro F(choosen between 0.01<=C<=1)
9  R=th*10^-3/(1.1*C*10^-6)/1000; //kohm
10 C1=0.01; //micro F(assumed)
11 C2=0.01; //micro F(choosen between 0.01<=C<=1)
12 R2=th*10^-3/(10*C2*10^-6)/1000; //kohm
13 C3=10; //micro F
14 disp("Design values are : ");
15 disp(C,"Capacitance C(micro F)");
16 disp(R,"Resistance R(kohm)");
17 disp(C1,"Capacitance C1(micro F)");
18 disp(C2,"Capacitance C2(micro F)");
19 disp(R2,"Resistance R2(kohm)");
20 disp(C3,"Capacitance C3(micro F)");
21 //Answer of R2 is wrong in the book.
```

Scilab code Exa 7.2 Value of R

```
1  ///Ex 7.2
2  clc;
3  clear;
4  close;
5  format('v',9);
6  ft=2; //kHz
7  C=0.01; //micro F
8  T=1/ft; //ms
9  n=3; //for divide-by-3 circuit
10 th=(0.2+(n-1))*T; //ms
11 R=th/(1.1*C); //kohm
12 disp(R,"Value of Resistance R(kohm)");
```

Scilab code Exa 7.3 Astable Multivibrator

```
1  ///Ex 7.3
2  clc;
3  clear;
4  close;
5  format('v',9);
6  fo=2; //kHz
7  D=70; //%(duty cycle)
8  T=1/fo; //ms
9  VCC=12; //V
10 tC=D*T/100; //ms
11 tD=T-tC; //ms
12 C=0.05; //micro F(choosen between 0.01<=C<=1)
13 RB=tD*10^-3/(0.69*C*10^-6)/1000; //kohm
14 RA=tC*10^-3/(0.69*C*10^-6)/1000-RB; //kohm
```

```

15 disp("Design values are : ");
16 disp(C,"Capacitance C(micro F)");
17 disp(RA,"Resistance RA(kohm)");
18 disp(RB,"Resistance RB(kohm)");

```

Scilab code Exa 7.4 Design a square wave generator

```

1  ////Ex 7.4
2  clc;
3  clear;
4  close;
5  format('v',9);
6  fo=2;//kHz
7  D=50;//%(duty cycle)
8  T=1/fo;//ms
9  VCC=10;//V
10 tC=D*T/100;//ms
11 tD=T-tC;//ms
12 C=0.1;//micro F(choosen between 0.01<=C<=1)
13 RB=tD*10^-3/(0.69*C*10^-6)/1000;//kohm
14 RA=T*10^-3*1.45/(C*10^-6)/1000-RB;//kohm
15 disp("Design values are : ");
16 disp(C,"Capacitance C(micro F)");
17 disp(RA,"Resistance RA(kohm)");
18 disp(RB,"Resistance RB(kohm)");
19 disp("RA & RB should be equal for 50% duty cycle.")

```

Scilab code Exa 7.5 Astable Multivibrator

```

1  ////Ex 7.5
2  clc;
3  clear;
4  close;

```

```

5 format('v',9);
6 fo=2; //kHz
7 D=40; //%(duty cycle)
8 T=1/fo; //ms
9 VCC=10; //V
10 tC=D*T/100; //ms
11 tD=T-tC; //ms
12 C=0.22; //micro F(choosen between 0.01<=C<=1)
13 RB=tD*10^-3/(0.69*C*10^-6)/1000; //kohm
14 RA=T*10^-3*1.45/(C*10^-6)/1000-RB; //kohm
15 disp("Design values are : ");
16 disp(C,"Capacitance C(micro F)");
17 disp(RA,"Resistance RA(kohm)");
18 disp(round(RB),"Resistance RB(kohm)");

```

Scilab code Exa 7.6 Astable Multivibrator

```

1 ///Ex 7.6
2 clc;
3 clear;
4 close;
5 format('v',9);
6 fo=700; //Hz
7 D=50; //%(duty cycle)
8 T=1/fo*1000; //ms
9 VCC=10; //V
10 tC=D*T/100; //ms
11 tD=T-tC; //ms
12 C=0.05; //micro F(choosen between 0.01<=C<=1)
13 RB=tD*10^-3/(0.69*C*10^-6)/1000; //kohm
14 RA=T*10^-3*1.45/(C*10^-6)/1000-RB; //kohm
15 disp("Design values are : ");
16 disp(C,"Capacitance C(micro F)");
17 disp(round(RA),"Resistance RA(kohm)");
18 disp(round(RB),"Resistance RB(kohm)");

```

Scilab code Exa 7.7 Astable Multivibrator

```
1  ///Ex 7.7
2  clc;
3  clear;
4  close;
5  format('v',9);
6  fo=800; //Hz
7  D=60; //%(duty cycle)
8  T=1/fo*1000; //ms
9  VCC=10; //V
10 tC=D*T/100; //ms
11 tD=T-tC; //ms
12 C=0.047; //micro F(choosen between 0.01<=C<=1)
13 RB=tD*10-3/(0.69*C*10-6)/1000; //kohm
14 RA=tC*10-3*1.45/(C*10-6)/1000-RB; //kohm
15 disp("Design values are : ");
16 disp(C,"Capacitance C(micro F)");
17 disp(round(RA),"Resistance RA(kohm)");
18 disp(round(RB),"Resistance RB(kohm)");
```

Chapter 8

Frequency Synthesizers and PLL

Scilab code Exa 8.1 Lock Capture and pullin range

```
1  ///Ex 8.1
2  clc;
3  clear;
4  close;
5  format('v',9);
6  VCC=6; //V
7  VEE=6; //V
8  RT=4; //kohm
9  CT=330; //pF
10 C=240; //pF
11 fo=0.3/(RT*1000*CT*10^-12)/1000; //kHz
12 disp(fo,"Free running frequency (kHz)");
13 Vplus=(VCC-(-VEE))/2; //V
14 deltafL=8*fo/Vplus; //kHz
15 disp(deltafL,"Lock Range(+ve & -ve in kHz)");
16 //For LM 565
17 R=3.6; //kohm
18 deltafC=sqrt(deltafL*1000/(2*%pi*R*1000*C*10^-12))
    /1000; //kHz
```

```

19  disp(deltafC," Capture Range(+ve & -ve in kHz)");
20  deltafP=2*deltafC/2; //kHz
21  disp(deltafP," Pull-in Range(kHz)");

```

Scilab code Exa 8.2 Design a FM demodulator

```

1  ///Ex 8.2
2  clc;
3  clear;
4  close;
5  format('v',9);
6  fo=450; //kHz
7  deltafL=240; //kHz(+ve & -ve)
8  deltafC=40; //kHz(+ve & -ve)
9  Vplus=8*fo/deltafL; //V
10 //Vplus=(VCC-(-VEE))/2 but |VCC|=|-VEE|
11 VCC=Vplus; //V
12 VEE=Vplus; //V
13 disp(VCC," For the design |VCC|=|-VEE| in Volt");
14 RT=4.7; //kohm(Assumed for design)
15 R=3.6; //kohm
16 CT=0.3/(RT*1000*fo*1000)*10^12; //pF
17 C=1/((deltafC*10^3)^2*(2*pi*R*10^3)/(deltafL*1000))
    *10^9; //nF
18 disp(RT," Value of RT(kohm)");
19 disp(CT," Value of CT(pF)");
20 disp(C," Value of C(nF)");
21 //Answer in the book is not accurate.

```

Scilab code Exa 8.3 Clock frequency and no of bits

```

1  ///Ex 8.3
2  clc;

```

```
3 clear;
4 close;
5 format('v',9);
6 fmax=160;//kHz
7 fr=4;//Hz(Resolution)
8 M=2.4;// unitless
9 fclk=M*fmax;//kHz
10 disp(fclk,"Clock frequency(kHz)");
11 N=log(fclk*1000/fr)/log(2);//no. of bits
12 disp(round(N),"No. of bits");
```

Chapter 9

Active Filters

Scilab code Exa 9.2 First order low pass filter

```
1 //Ex 9.2
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fH=1; //kHz
7 Ap=2; //Pass band gain
8 disp("Various design parameters are :-");
9 C=0.05; //micro F//Chosen for the design
10 disp(C,"Capacitance(micro F)");
11 format('v',4);
12 R=1/(2*%pi*fH*1000*C*10^-6)/1000; //kohm
13 disp(R,"Resistance R(kohm)");
14 //Ap=1+Rf/Ri
15 RfBYRi=Ap-1; //Rf=Ri here
16 //R=Rf||Ri
17 Ri=2*R; //kohm
18 Rf=Ri; //kohm
19 disp(Ri,"Resistance Ri(kohm)");
20 disp(Rf,"Resistance Rf(kohm)");
```

Scilab code Exa 9.3 Find Bandwidth

```
1 //Ex 9.3
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=800;//Hz
7 //For Butterworth filter : f0=fH=f_3dB
8 fH=f0;//Hz
9 f_3dB=f0;//Hz
10 BW=fH;//Hz
11 disp(BW,"Bandwidth (Hz)");
```

Scilab code Exa 9.4 First order low pass filter

```
1 //Ex 9.4
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fH=2;//kHz(Cutoff frequency)
7 Ap=1;//Pass band gain
8 disp("Various design parameters are :-");
9 C=0.05;//micro F//Chosen for the design between 0.01
   & 1 micro F
10 disp(C,"Capacitance(micro F)");
11 format('v',4);
12 R=1/(2*%pi*fH*1000*C*10^-6)/1000;//kohm
13 disp(R,"Resistance R(kohm)");
14 Rdash=R;//kohm(To eliminate the effect of offset)
15 disp(Rdash,"Resistance R*(kohm)");
```

Scilab code Exa 9.5 Convert Cutoff frequency

```
1 //Ex 9.5
2 clc;
3 clear;
4 close;
5 format('v',4);
6 f0=1;//kHz(Cutoff frequency)
7 f0dash=1.5;//kHz(Cutoff frequency)
8 disp("Various design parameters are :-");
9 //For Butterworth filter
10 fH=f0;//kHz
11 fHdash=f0dash;//kHz
12 K=f0/f0dash;//ratio
13 R=3.2;//kohm
14 Rdash=K*R;//kohm
15 disp(Rdash,"Resistance Rdash(kohm)");
16 disp("Use Rdash=2.2 kohm");
17 format('v',5);
18 C=0.05;//micro F//Chosen for the design
19 disp(C,"Capacitance(micro F)");
20 format('v',4);
21 fHdash=1/(2*pi*Rdash*1000*C*10^-6)/1000;//kHz
22 disp(fHdash,"Cutoff frequency(kHz)");
```

Scilab code Exa 9.6 First order high pass filter

```
1 //Ex 9.6
2 clc;
3 clear;
4 close;
```

```

5 format('v',5);
6 fL=400; //Hz
7 Ap=2; //Pass band gain
8 disp("Various design parameters are :-");
9 C=0.05; //micro F //Chosen for the design between 0.01
    & 1 micro F
10 disp(C,"Capacitance(micro F)");
11 R=1/(2*pi*fL*C*10^-6)/1000; //kohm
12 format('v',4);
13 disp(R,"Resistance R(kohm)");
14 disp("Use R=8.2 kohm");
15 //Ap=1+Rf/Ri
16 RfBYRi=Ap-1; //Rf=Ri here
17 //R=Rf||Ri
18 Ri=2*R; //kohm
19 Rf=Ri; //kohm
20 disp(Ri,"Resistance Ri(kohm)");
21 disp(Rf,"Resistance Rf(kohm)");

```

Scilab code Exa 9.7 Retune the high pass filter

```

1 //Ex 9.7
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fL=400; //Hz
7 fLdash=800; //Hz
8 K=fL/fLdash; //ratio
9 disp("Various parameters for retuning are :-");
10 R=8.2; //kohm
11 Rdash=K*R; //kohm
12 disp(Rdash,"Resistance Rdash(kohm)");
13 disp("Use Rdash=4.2 kohm");
14 Rf=2*Rdash; //kohm

```

```

15 Ri=2*Rdash; //kohm
16 disp(Ri," Resistance Ri(kohm)");
17 disp(Rf," Resistance Rf(kohm)");

```

Scilab code Exa 9.8 Second order Butterworth filter

```

1 //Ex 9.8
2 clc;
3 clear;
4 close;
5 format('v',6);
6 f0=3; //kHz(Critical frequency)
7 Ap=4; //Pass band gain
8 //For Butterworth filter using sallen key
9 alfa=1.414; klp=1; //constant
10 fH=f0; //kHz
11 f_3dB=f0; //kHz
12 disp(" Various design parameters are :-");
13 C1=0.01; //micro F//Chosen for the design
14 disp(C1," Capacitance C1(micro F)");
15 C2=alfa^2*C1/4; //micro F
16 disp(C2," Capacitance C2(micro F)");
17 disp(" Use C2=0.004 micro F");
18 C2=0.004; // micro F
19 R=1/(2*%pi*fH*10^3*sqrt(C1*10^-6*C2*10^-6))/1000; //
    kohm
20 format('v',4);
21 disp(R," Resistance R(kohm)");
22 disp(" Use R=8.2 kohm");
23 R=8.2; //kohm
24 //For offset minimization
25 Rdash=2*R; //kohm
26 disp(Rdash," Resistance R*(kohm)");
27 RfBYRi=Ap-1; //Rf=Ri here
28 //Ri=10 kohm chosen for design

```



```

29 Ri=10; //kohm
30 Rf=RfBYRi*Ri; //kohm
31 disp(Ri," Resistance Ri(kohm)");
32 disp(Rf," Resistance Rf(kohm)");

```

Scilab code Exa 9.9 Second order Butterworth filter

```

1 //Ex 9.9
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=2; //kHz(Critical frequency)
7 Ap=5; //dc gain
8 //For Butterworth filter using sallen key
9 alfa=1.414; klp=1; //constant
10 fH=f0; //kHz
11 f_3dB=f0; //kHz
12 Ap1=3-alfa; //gain
13 RfBYRi=Ap1-1; //ratio
14 disp(" Various design parameters are :-");
15 C=0.05; //micro F//Chosen for the design
16 disp(C," Capacitance C(micro F)");
17 R=klp/(2*pi*fH*10^3*C*10^-6)/1000; //kohm
18 disp(R," Resistance R(kohm)");
19 disp(" Use R=1.6 kohm");
20 //For offset minimization
21 //2*R=Rf || Ri=Rf/(RfBYRi+1)
22 Rf=2*R*(RfBYRi+1); //kohm
23 disp(Rf," Resistance Rf(kohm)");
24 Ri=Rf/RfBYRi; //kohm
25 format('v',4);
26 disp(Ri," Resistance Ri(kohm)");
27 //Ap=4; //dc gain in this case
28 Ap=4; //dc gain

```

```

29 Ap2=Ap/Ap1;//remaining gain after 2nd order
    butterworth filter
30 RfdashBYRidash=Ap2-1;//ratio
31 //Ridash=10;//kohm chosen for design
32 Ridash=10;//kohm
33 disp(Ridash,"Resistance Ridash(kohm)");
34 Rfdash=RfdashBYRidash*Ridash;//kohm
35 disp(Rfdash,"Resistance Rfdash(kohm)");

```

Scilab code Exa 9.10 Second order low pass filter

```

1 //Ex 9.10
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=2;//kHz(Critical frequency)
7 fH=f0;//kHz
8 f_3dB=f0;//kHz
9 //For Butterworth filter using sallen key
10 alfa=1.414;klp=1;//constant
11 Ap=3-alfa;// band pass gain
12 RfBYRi=Ap-1;//ratio
13 disp("Various design parameters are :-");
14 C=0.05;//micro F//Chosen for the design
15 disp(C,"Capacitance C(micro F)");
16 format('v',4);
17 R=1/(2*pi*fH*10^3*C*10^-6)/1000;//kohm
18 disp(R,"Resistance R(kohm)");
19 //For offset minimization
20 //2*R=Rf || Ri=Rf/(RfBYRi+1)
21 Rf=2*R*(RfBYRi+1);//kohm
22 disp(Rf,"Resistance Rf(kohm)");
23 Ri=Rf/RfBYRi;//kohm
24 disp(Ri,"Resistance Ri(kohm)");

```

25 //Answer in the book is not accurate. Some
calculation mistake is there while working for
offset minimization.

Scilab code Exa 9.11 Low pass bessel filter

```
1 //Ex 9.11
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=2;//kHz(Critical frequency)
7 fH=f0;//kHz
8 f_3dB=f0;//kHz
9 //For Bessel filter of 2nd order
10 alfa=1.73;klp=0.785;//constant
11 Ap=3-alfa;// band pass gain
12 RfBYRi=Ap-1;//ratio
13 disp("Various design parameters are :-");
14 C=0.05;//micro F//Chosen for the design
15 disp(C,"Capacitance C(micro F)");
16 format('v',4);
17 R=klp/(2*pi*fH*10^3*C*10^-6)/1000;//kohm
18 disp(R,"Resistance R(kohm)");
19 //For offset minimization
20 //2*R=Rf || Ri=Rf/(RfBYRi+1)
21 Rf=2*R*(RfBYRi+1);//kohm
22 disp(Rf,"Resistance Rf(kohm)");
23 Ri=Rf/RfBYRi;//kohm
24 disp(Ri,"Resistance Ri(kohm)");
```

Scilab code Exa 9.12 Second order low pass filter

```

1 //Ex 9.12
2 clc;
3 clear;
4 close;
5 format('v',5);
6 f0=.12;//kHz(Cutoff frequency)
7 fH=f0;//kHz
8 //For Butterworth filter of 2nd order
9 alfa=1.414;klp=1;//constant
10 Ap=3-alfa;// band pass gain
11 RfBYRi=Ap-1;//ratio
12 disp("Various design parameters are :-");
13 C=0.33;//micro F//Chosen for the design choosing
    between 0.01 & 1 micro F
14 disp(C,"Capacitance C(micro F)");
15 format('v',4);
16 R=klp/(2*pi*fH*10^3*C*10^-6)/1000;//kohm
17 disp(R,"Resistance R(kohm)");
18 disp("Use R=3.9 kohm");
19 //For offset minimization
20 //2*R=Rf||Ri=Rf/(RfBYRi+1)
21 Rf=2*R*(RfBYRi+1);//kohm
22 disp(Rf,"Resistance Rf(kohm)");
23 Ri=Rf/RfBYRi;//kohm
24 disp(Ri,"Resistance Ri(kohm)");

```

Scilab code Exa 9.13 Second order low pass filter

```

1 //Ex 9.13
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fL=20;//Hz(Cutoff frequency)
7 //For Butterworth filter of 2nd order

```

```

8  alfa=1.414;klp=1;//constant
9  Ap=3-alfa;// band pass gain
10 RfBYRi=Ap-1;//ratio
11 disp(" Various design parameters are :-");
12 C=0.22;//micro F//Chosen for the design choosing
    between 0.01 & 1 micro F
13 disp(C," Capacitance C(micro F)");
14 format('v',4);
15 R=klp/(2*pi*fL*C*10^-6)/1000;//kohm
16 disp(R," Resistance R(kohm)");
17 //For offset minimization
18 //R=Rf || Ri=Rf/(RfBYRi+1)
19 Rf=R*(RfBYRi+1);//kohm
20 disp(Rf," Resistance Rf(kohm)");
21 Ri=Rf/RfBYRi;//kohm
22 Ri=floor(Ri);//kohm
23 disp(Ri," Resistance Ri(kohm)");

```

Scilab code Exa 9.14 Third order low pass butterworth filter

```

1 //Ex 9.14
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fH=2;//kHz(Cutoff frequency)
7 Ap=4;//Pass band gain
8 disp(" Butterworth filter of 3rd order can be
    obtained by cascading of first and second order
    high pass filter.");
9 //Butterworth polynomial is (s+1)*(s^2+s+1)
10 alfa=1;//for sallen key
11 Ap2=3-alfa;//gain for 2nd order filter
12 Ap1=Ap/Ap2;//gain for 1st order filter
13 //Design parameters for 1st order filter :

```

```

14 disp(" Various design parameters for 1st order filter
      are :-");
15 C=0.01; //micro F//Chosen for the design
16 disp(C," Capacitance C(micro F)");
17 R=1/(2*%pi*fH*10^3*C*10^-6)/1000; //kohm
18 disp(R," Resistance R(kohm)");
19 disp(" Use R=8.2 kohm");
20 R=8.2; //kohm
21 //Ap1=Rf/Ri+1 ; with Ap1=2 we have Rf=Ri
22 Rf=2*R; //kohm
23 Ri=2*R; //kohm
24 disp(Ri,Rf," Resistance Rf & Ri(kohm)");
25 format('v',6);
26 //Design parameters for 2nd order filter :
27 kLp=1/alfa; //unitless
28 //Ap2=Rfdash/Ridash+1 ; with Ap2=2 we have Rfdash=
      Ridash
29 disp(" Various design parameters for 2nd order filter
      are :-");
30 C=0.033; //micro F//Chosen for the design
31 disp(C," Capacitance C(micro F)");
32 format('v',4);
33 R=kLp/(2*%pi*fH*10^3*C*10^-6)/1000; //kohm
34 disp(R," Resistance R(kohm)");
35 Rf=2*R; //kohm
36 Ri=2*R; //kohm
37 disp(Ri,Rf," Resistance Rfdash & Ridash(kohm)");

```

Scilab code Exa 9.15 Design a band pass filter

```

1 //Ex 9.15
2 clc;
3 clear;
4 close;
5 format('v',6);

```

```

6 fL=200; //Hz
7 fH=1; //kHz
8 Ap=4; //Pass band gain
9 fc=sqrt(fH*1000*fL); //Hz(Cutoff frequency)
10 BW=fH*1000-fL; //Hz
11 Q=fc/BW; //Quality Factor
12 disp(Q,"Quality factor is ");
13 disp("As Q<12, it is a wide band filter.");
14 Ap1=2; //Pass band gain for high pass section
15 disp("Various design parameters for high pass
    section are :-");
16 C=0.033; //micro F//Chosen for the design
17 disp(C,"Capacitance C(micro F)");
18 format('v',4);
19 R=1/(2*pi*fL*C*10^-6)/1000; //kohm
20 disp(R,"Resistance R(kohm)");
21 //Ap1=Rf/Ri+1 ; with Ap1=2 we have Rf=Ri
22 Rf=2*R; //kohm
23 Ri=2*R; //kohm
24 disp(Ri,Rf,"Resistance Rf & Ri(kohm)");
25 Ap2=2; //Pass band gain for low pass section
26 disp("Various design parameters for low pass section
    are :-");
27 format('v',6);
28 C=0.033; //micro F//Chosen for the design
29 disp(C,"Capacitance C(micro F)");
30 format('v',4);
31 K=fL/(fH*1000); // unitless
32 Rdash=K*R; //kohm
33 disp(Rdash,"Resistance Rdash(kohm)");
34 //Ap1=Rf/Ri+1 ; with Ap1=2 we have Rf=Ri
35 Rf=2*Rdash; //kohm
36 Ri=2*Rdash; //kohm
37 disp(Ri,Rf,"Resistance Rf & Ri(kohm)");
38 disp("Use Rf=Ri=10 kohm");

```

Scilab code Exa 9.16 Design a band pass filter

```
1 //Ex 9.16
2 clc;
3 clear;
4 close;
5 format('v',5);
6 disp("Part(a)");
7 fc=1.2; //kHz
8 Q=4; //Quality Factor
9 Ap=10; //Pass band gain
10 disp("Here  $2*Q^2=32 > AP=10$ , hence it can be designed
      using single op-amp.");
11 disp("Various design parameters are :-");
12 C=0.05; //micro F//Chosen for the design
13 disp(C,"Capacitance C(micro F)");
14 //fc/Q=1/(%pi*R2*C)
15 R2=Q/(fc*1000)/%pi/(C*10^-6)/1000; //kohm
16 disp(R2,"Resistance R2(kohm)");
17 disp("Use R2=22 kohm");
18 format('v',5);
19 R1=R2/(2*Ap); //kohm
20 disp(R1,"Resistance R1(kohm)");
21 R3=R1*1000/(4*%pi^2*R1*1000*R2*1000*(C*10^-6)^2*(fc
      *1000)^2-1); //ohm
22 disp(R3,"Resistance R3(ohm)");
23 disp("Use R3=460 ohm");
24 disp("Part(b)");
25 R3=460; //ohm
26 fc_new=1.5; //kHz
27 fc_old=1.2; //kHz
28 R3new=R3*(fc_old/fc_new)^2; //ohm
29 disp("Resistance R3 should be changed from "+string(
      R3)+" ohm to "+string(R3new)+" ohm");
```


30 `///Answer for R3 is wrong in the book`

Scilab code Exa 9.17 Design a band pass filter

```
1 ///Ex 9.17
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fL=3;///kHz
7 fH=3.6;///kHz
8 Ap=-6;///Pass band gain
9 fc=sqrt(fH*fL)*1000;///Hz
10 BW=(fH-fL)*1000;///Hz
11 Q=fc/BW;///Quality factor
12 disp(Q, "Quality factor is ");
13 disp("Here  $1 \leq Q \leq 12$  criteria fulfills , hence it can
       be designed using single op-amp.");
14 disp("Various design parameters are :-");
15 C=0.01;///micro F//Chosen for the design
16 disp(C, "Capacitance C(micro F)");
17 //fc/Q=1/(%pi*R2*C)
18 format('v',4);
19 R2=1/%pi/(BW)/(C*10^-6)/1000;///kohm
20 disp(R2, "Resistance R2(kohm)");
21 format('v',5);
22 R1=-R2/(2*Ap);///kohm
23 disp(R1, "Resistance R1(kohm)");
24 R3=R1*1000/(4*%pi^2*R1*1000*R2*1000*(C*10^-6)^2*(fc)
       ^2-1);///ohm
25 disp(R3, "Resistance R3(ohm)");
26 disp("Design Verification : ");
27 disp(2*Q^2>abs(Ap), "(i) Is  $2*Q^2 > |A_p|$  ?");
28 disp("For op-amp 741, GBW=1 MHz");
29 GBW=1;///MHz
```

```

30 disp(GBW*10^6>20*Q^2*fc," Is GBW*10^6>20*Q^2*fc ?");
31 disp("2nd criteria failed. The op-amp should have
    higher GBW product. Use LF411");

```

Scilab code Exa 9.18 Design a band pass filter

```

1 //Ex 9.18
2 clc;
3 clear;
4 close;
5 format('v',5);
6 Ap=-10;//Pass band gain
7 Q=22;//Quality factor
8 fc=50;//Hz
9 R=60;//dB/decade(Roll off rate)
10 disp("Roll off rate of single op-amp=20 dB/decade.
    No. of stages will be 3. Desired design can be
    obtained by cascading three stages.");
11 n=3;//no. of op-amps(as single op-amp has 20 dB/
    decade)
12 fc1=fc;//Hz
13 fc2=fc;//Hz
14 fc3=fc;//Hz
15 Q1=Q*sqrt(2^(1/n)-1);//Quality factor of each stage
16 Q2=Q1;//Quality factor
17 Q3=Q1;//Quality factor
18 Ap1=-(-Ap)^(1/n);//Band pass gain of each stage
19 Ap2=Ap1;//Band pass gain
20 Ap3=Ap1;//Band pass gain
21 //Design of a single op-amp
22 C=0.1;//micro F//Chosen for the design
23 disp("Various design parameters for a single stages
    are :");
24 disp(C,"Capacitance C(micro F)");
25 format('v',4);

```

```

26 R2=Q1/%pi/(fc)/(C*10^-6)/1000; //kohm
27 disp(R2," Resistance R2(kohm)");
28 format('v',5);
29 R1=-R2/(2*Ap1); //kohm
30 disp(R1," Resistance R1(kohm)");
31 format('v',4);
32 R3=R1/(4*%pi^2*R1*1000*R2*1000*(C*10^-6)^2*(fc)^2-1)
    ; //kohm
33 disp(R3," Resistance R3(ohm)");
34 //Answer for R2 is wrong in the book.

```

Scilab code Exa 9.20 Second order notch filter

```

1 //Ex 9.20
2 clc;
3 clear;
4 close;
5 format('v',5);
6 fN0=50; //Hz
7 Q=20; //Quality Factor
8 disp(" Various design parameters are :-");
9 C=1; //micro F//Chosen for the design
10 disp(C," Capacitance C(micro F)");
11 R=1/(2*%pi*fN0)/(C*10^-6)/1000; //kohm
12 disp(R," Resistance R(kohm)");
13 disp(" Use R=3.2 kohm");
14 //Q=(RA+RB)/4/RA
15 RA=1; //kohm(chosen for the design)
16 RB=Q*4*RA-RA; //kohm
17 disp(RA," Resistance RA(kohm)");
18 disp(RB," Resistance RB(kohm)");

```

Chapter 10

Comparators

Scilab code Exa 10.1 Output Voltage

```
1  ///Ex 10.1
2  clc;
3  clear;
4  close;
5  format('v',5);
6  t=0:0.01:5; //sec (Assumed)
7  Vin=5*sin(2*pi*t); //V
8  VCC=15; //V
9  R2=1; //kohm
10 R1=6.8; //kohm
11 VEE=-15; //V
12 Vsat=13; //V
13 Vref=R2*VCC/(R1+R2); //V
14 disp(Vref," Reference Voltage(V)")
15 disp(Vsat," If Vin>Vref , Vout (V):");
16 disp(-Vsat," If Vin<Vref , Vout (V):");
```

Scilab code Exa 10.2 Upper and Lower Trip points

```

1  ///Ex 10.2
2  clc;
3  clear;
4  close;
5  format('v',9);
6  Vsat=7; //V
7  R1=68; //kohm
8  R2=82; //kohm
9  VUTP=R2*Vsat/(R1+R2); //V
10 VLTP=R2*-Vsat/(R1+R2); //V
11 disp(VUTP,"Upper trip point (V)");
12 disp(VLTP,"Lower trip point (V)");

```

Scilab code Exa 10.3 Phase shift

```

1  ///Ex 10.3
2  clc;
3  clear;
4  close;
5  format('v',9);
6  //Vin=5*sin(omega*t)
7  Vm=5; //V
8  Vsat=7; //V
9  R1=68; //kohm
10 R2=82; //kohm
11 VUTP=R2*Vsat/(R1+R2); //V
12 fi=asind(VUTP/Vm); //degree
13 disp(fi,"Phase shift (degree)");

```

Scilab code Exa 10.4 Output Voltage

```

1  ///Ex 10.4
2  clc;

```

```

3  clear;
4  close;
5  format('v',5);
6  VZ1=4.7; //V
7  VZ2=4.7; //V
8  R1=68; //kohm
9  R2=15; //kohm
10 Vout=VZ1+0.7; //V(As one zener diode is always
    forward biased)
11 VR1=Vout; //V
12 IR1=VR1/R1*1000; //micro A
13 IR2=IR1; //micro A
14 VR2=IR2*10^-3*R2; //V
15 Vout=VR1+VR2; //V
16 VUTP=(R2/(R1+R2))*Vout; //V
17 VLTP=(R2/(R1+R2))*(-Vout); //V
18 disp(VUTP,"VUTP(V)");
19 disp(VLTP,"VLTP(V)");

```

Scilab code Exa 10.5 Threshold and hysteresis voltage

```

1  ////Ex 10.5
2  clc;
3  clear;
4  close;
5  format('v',9);
6  Vsat=12.5; //V
7  Vref=-12.5; //V
8  R1=80; //kohm
9  R2=20; //kohm
10 Beta=R2/(R1+R2); // unitless
11 UTP=Beta*Vsat+(1-Beta)*Vref; //V
12 LTP=-Beta*Vsat+(1-Beta)*Vref; //V
13 VH=UTP-LTP; //V
14 R3=R1*R2/(R1+R2); //kohm

```

```
15 disp(UTP,"UTP(V)");
16 disp(LTP,"LTP(V)");
17 disp(VH,"Hysteresis Voltage , VH(V)");
18 disp(R3,"Use R3(kohm)");
```

Chapter 11

Non linear applications of opamp

Scilab code Exa 11.1 Output Voltage

```
1  ///Ex 11.1
2  clc;
3  clear;
4  close;
5  format('v',5);
6  Vin=12.5;//V
7  Ri=10;//kohm
8  IS=10^-13;//A
9  T=27;//degree C
10 VT=26;//mV
11 Vref=Ri*IS*1000;//V
12 Vout=-VT*10^-3*log(Vin/Vref);//V
13 disp(Vout,"Output Voltage , Vout(V)");
```

Scilab code Exa 11.3 Output Voltage


```

1  ////Ex 11.2
2  clc;
3  clear;
4  close;
5  format('v',7);
6  R1=10; //kohm
7  k=1.38*10^-23; //J/K
8  T=298; //K
9  q=1.6*10^-19; //C
10 Kdash=k*T/q; //Kdash=k*T/q assumed for temporary
    calculation
11 disp("Output Voltage , Vout(V) is "+string(-Kdash)+"*
    log(Vin/10*10^3)");

```

Scilab code Exa 11.4 Output Voltage

```

1  ////Ex 11.4
2  clc;
3  clear;
4  close;
5  format('v',5);
6  R1=10; //kohm
7  R2=10; //kohm
8  k=1.38*10^-23; //J/K
9  T=298; //K
10 q=1.6*10^-19; //C
11 Kdash=k*T/q; //Kdash=k*T/q assumed for temporary
    calculation
12 disp("Output Voltage , Vout(V) is -R1*(log("+string
    (-1/Kdash)+"*Vin)^-1)");

```

Scilab code Exa 11.7 Calculate Output

```

1  ///Ex 11.7
2  clc;
3  clear;
4  close;
5  format('v',6);
6  k=1;//for the givn connection
7  //(a)
8  Vin=5;//V
9  Vout=-k*log10(Vin/0.1);//V
10 disp(Vout,"For 5V input , Output Voltage(V)");
11 //(b)
12 Vin=2;//V
13 Vout=-k*log10(Vin/0.1);//V
14 disp(Vout,"For 2V input , Output Voltage(V)");
15 //(c)
16 Vin=0.1;//V
17 Vout=-k*log10(Vin/0.1);//V
18 disp(Vout,"For 0.1V input , Output Voltage(V)");
19 //(d)
20 Vin=50;//mV
21 Vout=-k*log10(Vin/1000/0.1);//V
22 disp(Vout,"For 50mV input , Output Voltage(V)");
23 //(a)
24 Vin=5;//mV
25 Vout=-k*log10(Vin/1000/0.1);//V
26 disp(Vout,"For 5mV input , Output Voltage(V)");

```

Scilab code Exa 11.8 Calculate Output

```

1  ///Ex 11.8
2  clc;
3  clear;
4  close;
5  format('v',6);
6  k=1;//for the givn connection

```

```

7 //For 755N module
8 Rin=10;//kohm
9 Iref=10;//micro A
10 Vref=Rin*Iref/1000;//V
11 //(a)
12 Vin=5;//V
13 Vout1=-k*log10(Vin/0.1);//V
14 Vout=Vref*10^(-Vout1/k);//V
15 disp(Vout,"For 5V input to log amp, Antilog amp
    Output(V)");
16 //(b)
17 Vin=2;//V
18 Vout1=-k*log10(Vin/0.1);//V
19 Vout=Vref*10^(-Vout1/k);//V
20 disp(Vout,"For 2V input to log amp, Antilog amp
    Output(V)");
21 //(c)
22 Vin=0.1;//V
23 Vout1=-k*log10(Vin/0.1);//V
24 Vout=Vref*10^(-Vout1/k);//V
25 disp(Vout,"For 0.1V input to log amp, Antilog amp
    Output(V)");
26 //(d)
27 Vin=50;//mV
28 Vout1=-k*log10(Vin/1000/0.1);//V
29 Vout=Vref*10^(-Vout1/k);//V
30 disp(Vout*1000,"For 50mV input to log amp, Antilog
    amp Output(mV)");
31 //(e)
32 Vin=5;//mV
33 Vout1=-k*log10(Vin/1000/0.1);//V
34 Vout=Vref*10^(-Vout1/k);//V
35 disp(Vout*1000,"For 5mV input to log amp, Antilog
    amp Output(mV)");

```

Chapter 12

Operational Transconductance Amplifier

Scilab code Exa 12.1 f3dB frequency

```
1  ///Ex 12.1
2  clc;
3  clear;
4  close;
5  format('v',9);
6  gm=55; //micro U
7  C=8.75; //pF
8  f3dB=gm/(2*%pi*C); //MHz
9  disp(f3dB, "f-3dB frequency (MHz)")
```

Chapter 13

Voltage Regulators

Scilab code Exa 13.1 Regulation

```
1  ///Ex 13.1
2  clc;
3  clear;
4  close;
5  format('v',6);
6  deltaVin=4; //V
7  deltaVout=0.4; //V
8  Vout=20; //V
9  LR=(deltaVout/Vout)*100/deltaVin; //%/V( Line
   Regulation)
10 disp(LR," Line Regulation (%/V)");
```

Scilab code Exa 13.2 Load Regulation

```
1  ///Ex 13.2
2  clc;
3  clear;
4  close;
```

```

5 format('v',6);
6 VNL=18; //V
7 VFL=17.8; //V
8 IL=50; //mA
9 LR=(VNL-VFL)*100/VFL; //%(Line Regulation)
10 LdR=LR/IL; //%/mA(Load Regulation)
11 disp(LdR,"Load Regulation (%/mA)");

```

Scilab code Exa 13.3 Calculate Load Current

```

1 ////Ex 13.3
2 clc;
3 clear;
4 close;
5 format('v',6);
6 VBE=0.65; //V
7 RCL=1.2; //ohm
8 ILmax=VBE/RCL; //A
9 //For Vout=0, IL=ILmax
10 IL=ILmax; //A
11 disp(IL,"Load current (A)");

```

Scilab code Exa 13.4 Determine the output

```

1 ////Ex 13.4
2 clc;
3 clear;
4 close;
5 format('v',6);
6 R=20; //kohm
7 R1=20; //kohm
8 R2=10; //kohm
9 VZ=4.7; //V

```

```

10 Vref=VZ; //V
11 Vout=Vref*(1+R1/R2); //V
12 disp(Vout,"Output Voltage(V)");

```

Scilab code Exa 13.5 Design a regulator circuit

```

1  ////Ex 13.5
2  clc;
3  clear;
4  close;
5  format('v',6);
6  Vout=15; //V
7  Vin=20; //V
8  INL=2; //mA(INL=Iadj+Iref)
9  Iadj=60; //mA(Assumed)
10 Iref=INL-Iadj/1000; //mA
11 Vref=1.25; //V
12 R1=Vref/Iref*1000; //ohm
13 VR2=Vout-Vref; //V
14 R2=VR2/INL*1000; //ohm
15 disp("Design values are : ");
16 disp(R1,"Resistance , R1(ohm)");
17 disp(R2/1000,"Resistance , R2(kohm)");

```

Scilab code Exa 13.6 Calculate Iext

```

1  ////Ex 13.6
2  clc;
3  clear;
4  close;
5  format('v',6);
6  RL1=100; //ohm
7  RL2=1; //ohm

```

```

8 RCS=7; //ohm
9 VEB=0.7; //V
10 Beta=25; //unitless
11 //For 100 ohm Load
12 Vout=5; //V(as 7805 used)
13 IL=Vout/RL1; //A
14 VRCS=IL*RCS; //V(Voltage across RCS)
15 //VRCS<VEB, hence Q1 is off
16 Iout=IL; Iin=IL; //A
17 Iext=Iout-Iin; //A
18 disp(Iext,"For 100 ohm load , Output current Iext(A)"
    );
19 //For 1 ohm Load
20 Vout=5; //V(as 7805 used)
21 IL=Vout/RL2; //A
22 ILmax=IL; //A
23 VRCS=IL*RCS; //V(Voltage across RCS)
24 //VRCS>VEB, hence Q1 is on
25 Iout=(ILmax+Beta*VEB/RCS)/(Beta+1); //A
26 Iext=ILmax-Iout; //A
27 disp(Iext,"For 10 ohm load , Output current Iext(A)"
    );

```

Scilab code Exa 13.7 Value of R1

```

1 ////Ex 13.7
2 clc;
3 clear;
4 close;
5 format('v',6);
6 RL=1:10; //ohm
7 R1=5; //ohm
8 Vref=5; //V
9 IL=1; //A
10 IQ=0; //A

```



```

11 Iref=IL; //A
12 R1=Vref/Iref; //ohm
13 disp(R1," Value of resistor R1(ohm)");

```

Scilab code Exa 13.8 Adjustable Voltage regulator

```

1  ////Ex 13.8
2  clc;
3  clear;
4  close;
5  format('v',6);
6  Vout=15:20; //V
7  Vin=24; //V
8  VR1=12; //V
9  Vref=12; //V
10 I4=0; //A( Assumed)
11 Iout=1; //A( Assumed)
12 R1=VR1/Iout; //ohm
13 //Vout=VR1*(1+R2/R1)
14 R2min=R1*(min(Vout)/VR1-1); //Putting min Vout
15 R2max=R1*(max(Vout)/VR1-1); //Putting min Vout
16 disp(R1," Resistance R1(ohm)");
17 disp(R2max,R2min," Minimum & maximum value of R2(ohm)
    ");
18 disp("A pot of 10 ohm should be used.");

```

Scilab code Exa 13.9 Regulated Power Supply

```

1  ////Ex 13.9
2  clc;
3  clear;
4  close;
5  format('v',6);

```

```

6 Vout=6; //V
7 IL=100; //mA
8 Vref=7.15; //V(For LM 723)
9 Iref=1; //mA(Assumed)
10 R1=(Vref-Vout)/Iref; //kohm
11 R2=Vout/Iref; //kohm
12 disp("Design values are : ");
13 disp(R1,"R1 should be used 1.2kohm. Calculated R1(
    kohm) is");
14 disp(R2,"R2 should be used 6.2kohm. Calculated R2(
    kohm)");
15 R1=1.2;R2=6.2; //kohm
16 R3=R1*R2/(R1+R2); //kohm
17 disp(R3,"Resistance R3(kohm)");
18 RCL=0.65/(IL/1000); //kohm
19 disp(RCL,"Resistance RCL(kohm)");

```

Scilab code Exa 13.10 Regulated Power Supply

```

1 ///Ex 13.10
2 clc;
3 clear;
4 close;
5 format('v',6);
6 Vout=15; //V
7 IL=50; //mA
8 Vin=20; //V
9 PDmax=1; //W(For LM 723)
10 Iref=3; //mA(From datasheet)
11 PD=Vout*(IL+Iref); //mW
12 disp(PD/1000,"Required PD(W)");
13 disp(PDmax,"PDmax supplied by LM723(mW)");
14 disp("PD<PDmax, so we can use it.");
15 Vref=7.15; //V(For LM 723)
16 R3=1.5; //kohm(choosen)

```

```
17 R1BYR2=(Vout-Vref)/Vref;
18 R1=R3*(R1BYR2+1); //ohm
19 disp(R1," Resistance R1(kohm)");
20 R2=R1/R1BYR2; //ohm
21 disp(R2," Resistance R2(kohm)");
22 disp(R3," Resistance R3(kohm)");
23 RCL=0.65/(IL/1000); //ohm
24 disp(RCL," Resistance RCL(ohm)");
```
