

Scilab Textbook Companion for
Solid State Electronics
by J. P. Agrawal¹

Created by
Vijay Kant Kala
B.Tech
Electronics Engineering
Krishna Institute of Engineering and Technology
College Teacher
None
Cross-Checked by
Chaya Ravindra

June 2, 2016

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Solid State Electronics

Author: J. P. Agrawal

Publisher: Pragati Prakashan, Merrut

Edition: 1

Year: 2013

ISBN: 93-5006-947-4

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introduction to solid state electronics	5
2 Special Purpose Diodes	19
3 Bi Polar Junction Transistor	21
4 Small signal amplifiers	30
5 Power Amplifiers	43
6 Field Effect Transistors	48
9 Silicon Controlled Rectifier	53
10 The Unijunction Transistor	56

List of Scilab Codes

Exa 1.1	ne	5
Exa 1.2	resistivity	5
Exa 1.3	density	6
Exa 1.4	density	6
Exa 1.5	resistivity	7
Exa 1.6	conductivity	8
Exa 1.7	fremi level	9
Exa 1.8	density	9
Exa 1.9	current	10
Exa 1.10	hole concentration and conductivity	11
Exa 1.11	donor concentration	11
Exa 1.12	resistivity	12
Exa 1.13	current	12
Exa 1.14	diode current and voltage	13
Exa 1.15	voltage	14
Exa 1.16	voltage	14
Exa 1.17	resistance	15
Exa 1.18	resistance	15
Exa 1.19	resistance	16
Exa 1.20	capacitance	17
Exa 1.21	resistance	17
Exa 2.1	maximum current	19
Exa 2.2	resistance	19
Exa 2.3	current	20
Exa 3.1	varitation in alpha and value of beta	21
Exa 3.2	current amplification factor	21
Exa 3.3	base current	22
Exa 3.4	short circuit current gain	22

Exa 3.5	collector and base current	23
Exa 3.6	I_c I_b and I_{ce0}	23
Exa 3.7	change in collector current	24
Exa 3.8	emitter current	24
Exa 3.9	beta	25
Exa 3.10	error	25
Exa 3.11	change in base current	26
Exa 3.12	collector current base current and α	26
Exa 3.13	ac current gain	27
Exa 3.14	Beta I_{ce0} and collector current	27
Exa 3.15	collector current α and beta	28
Exa 3.16	collector current	29
Exa 4.1	voltage	30
Exa 4.2	vce	31
Exa 4.3	base resistance	31
Exa 4.4	operating point	32
Exa 4.5	resistor	32
Exa 4.6	operating point	33
Exa 4.7	operating point	33
Exa 4.8	operating point	34
Exa 4.9	maximum collector current	34
Exa 4.10	maximum collector current	35
Exa 4.11	gain	35
Exa 4.12	output voltage	36
Exa 4.13	gain and resistance	37
Exa 4.14	gain and voltage	37
Exa 4.15	voltage gain	38
Exa 4.16	small change in gain	39
Exa 4.17	input voltage	39
Exa 4.18	percentage of feedback	40
Exa 4.19	band width	40
Exa 4.20	percentage reduction	41
Exa 4.21	A_v and beta	41
Exa 5.1	efficiency	43
Exa 5.2	collector current	43
Exa 5.3	collector efficiency and power rating	44
Exa 5.4	power	44
Exa 5.5	power	45

Exa 5.6	harmonic distortions and change in power	45
Exa 5.7	power dissipated	46
Exa 6.1	drain resistance transconductance and amplification factor	48
Exa 6.2	mutual conductance	49
Exa 6.3	pinch off voltage	49
Exa 6.4	ID gm and gmo	50
Exa 6.5	Vgs	50
Exa 6.6	voltage amplification	51
Exa 6.7	output voltage	51
Exa 9.1	average voltage	53
Exa 9.2	dc load current rms load current amd power dissipated	53
Exa 9.3	firing angle conducting angle and average current	54
Exa 10.1	stand off and peak point voltage	56
Exa 10.2	time period	56
Exa 10.3	resistance	57

Chapter 1

Introduction to solid state electronics

Scilab code Exa 1.1 ne

```
1 //Example 1.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 ni=1.5*10^16; // in m^-3
7 nh=4.5*10^22; // in m^-3
8 ne=ni^2/nh;
9 format('e',8)
10 disp(ne," ne in the doped silicon is ,(m^-3) = ")
```

Scilab code Exa 1.2 resistivity

```
1 //Example 1.2:
2 clc;
3 clear;
```



```

4 close;
5 //given data :
6 ne=8*10^19; // in m^-3
7 nh=5*10^18; // in m^-3
8 mu_e=2.3; // in m^2/V-s
9 mu_h=.01; // in m^2/V-s
10 e=1.6*10^-19; // in V
11 p=1/(e*((ne*mu_e)+(nh*mu_h)));
12 format('e',8)
13 disp(p,"(b) the resistivity ,p(ohm-m)=")

```

Scilab code Exa 1.3 density

```

1 //Example 1.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 sigma=500; // in ohm^-1 m^-1
7 mu_e=.39; // m^2/V-s
8 e=1.6*10^-19; // in V
9 ne=sigma/(e*mu_e);
10 format('e',9)
11 disp(ne,"number density of donor ,ne(m^-3) = ")

```

Scilab code Exa 1.4 density

```

1 //Example 1.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10^-19; // in V

```

```

7 Pp=10^-2; // p-type silicon in ohm-m
8 Pn=10^-2; // n-type silicon in ohm-m
9 mu_p=0.048; // holes mobilities in m^2/V-s
10 mu_n=0.135; // electrons mobilities in m^2/V-s
11 Na=1/(e*mu_p*Pp);
12 Nd=1/(e*mu_n*Pn);
13 format('e',8)
14 disp(Na,"(i). the density of impurity,Na (m^-3) = ")
15 format('e',9)
16 disp(Nd,"(ii). the density of impurity,Nd (m^-3) = "
    )

```

Scilab code Exa 1.5 resistivity

```

1 //Example 1.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 e=1.6*10^-19; // in V
8 n=2.5*10^19; //m^3
9 p=n; //
10 ni=n; //
11 mu_p=0.17; // holes mobilities in m^2/V-s
12 mu_n=0.36; // electrons mobilities in m^2/V-s
13 sgint=e*(ni*(mu_p+mu_n)); //electrical conductivity
    in mho/metre
14 pint=1/sgint; //resistivity in ohm-meter
15 disp(sgint,"electrical conductivity is ,(mho/metre)=
    ")
16 disp(pint,"resistivity is ,(ohm-metre)=")

```

Scilab code Exa 1.6 conductivity

```
1 //Example 1.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('e',9)
7 e=1.6*10^-19; // in V
8 ni=1.5*10^16; //in m^3
9 mu_p=0.13; // holes mobilities in m^2/V-s
10 mu_n=0.05; // electrons mobilities in m^2/V-s
11 sgint=e*(ni*(mu_p+mu_n)); //electrical conductivity
    in mho/m
12 siat=10^8; //number of silicon atoms
13 ta=5*10^28; //silicon atoms in atoms/m^3
14 Nd=ta/siat; // in atoms/m^3
15 p= ni^2/Nd; //holes concentration in holes/m^3
16 n=Nd; //
17 mu_n=0.13; // electrons mobilities in m^2/V-s
18 sntype=e*n*mu_n; // in mho/m
19 disp(sgint,"(i) electrical conductivity is ,(mhos/m)
    =")
20 format('e',8)
21 disp(p,"(ii) holes concentration is , (holes/m^3)=")
22 format('v',5)
23 disp(sntype,"(ii) conductivity is ,(mho/m)=")
24 siat=10^8; //number of silicon atoms
25 ta=5*10^28; //silicon atoms in atoms/m^3
26 Na=ta/siat; // in atoms/m^3
27 n= ni^2/Na; //holes concentration in holes/m^3
28 p=Na; //
29 mu_p=0.05; //holes mobilities in m^2/V-s
30 sptype=e*p*mu_p; // in mho/m
31 format('e',8)
32 disp(n,"(iii) electron concentration is , (holes/m^3)
    =")
33 format('v',3)
```

34 `disp(sptype, "(iii) conductivity is ,(mho/m)=")`

Scilab code Exa 1.7 fremi level

```
1 //Example 1.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 //Nd1=Nc*exp-(Ec-Ef1)/kT ... Formula Used
8 Nc=1; //assume
9 kT=0.03; //eV
10 EcEf1=0.5; //position of Fermi level in V
11 Nd=1; //assume
12 Nd1=3*Nd; //After tripling the donor concentration
13 EcEf2=(EcEf1-(kT*(log(Nd1/Nd)))); //in eV
14 disp(EcEf2, "new position of Fermi-level is ,(eV)=")
```

Scilab code Exa 1.8 density

```
1 //Example 1.8:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10-19; // in V
7 Pp=10-1; // p-type silicon in ohm-m
8 Pn=10-1; // n-type silicon in ohm-m
9 mu_h=0.05; // holes mobilities in m2/V-s
10 mu_e=0.13; // electrons mobilities in m2/V-s
11 Na=1/(e*mu_h*Pp);
12 Nd=1/(e*mu_e*Pn);
```

```

13 format('e',9)
14 disp(Na,"(i). the density of impurity ,Na (m-3) = ")
15 format('e',8)
16 disp(Nd,"(ii). the density of impurity ,Nd (m-3) = "
    )

```

Scilab code Exa 1.9 current

```

1 //Example 1.9:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10-19; // in V
7 Pp=10-1; // p-type silicon in ohm-m
8 Pn=10-1; // n-type silicon in ohm-m
9 mu_hsi=0.048; // holes mobilities in m2/V-s
10 mu_esi=0.135; // electrons mobilities in m2/V-s
11 nisi=1.5*1016; //in m-3
12 nesi=nisi; //
13 nhsi=nisi; //
14 mu_hge=0.19; // holes mobilities in m2/V-s
15 mu_ege=0.39; // electrons mobilities in m2/V-s
16 A=1*10-4; //area in m2
17 nige=2.4*1019; //in m-3
18 V=2; //in V
19 l=0.1; //in m
20 Isi= e*A*(V/l)*((nesi*mu_esi)+(nhsi*mu_hsi)); //in A
21 format('e',8)
22 disp(Isi,"Total current for silicon is ,(A)=")
23 //Current for silicon is calculated wrong in the
    textbook
24 nege=nige; //
25 nhge=nige; //
26 Ige= e*A*(V/l)*((nege*mu_ege)+(nhge*mu_hge)); //in A

```

```
27 format('e',9)
28 disp(Ige,"Total current for germanium is ,(A)=")
```

Scilab code Exa 1.10 hole concentration and conductivity

```
1 //Example 1.10:
2 clc;
3 clear;
4 close;
5 //given data :
6 nh=2*10^21;// acceptor atoms in atoms/m^3
7 Na=nh;
8 format('e',8)
9 disp(Na,"(i). hole concentration ,Na(atoms/m^3) = ")
10 mu_h=0.17;// mobility of holes in m^2/V-s
11 e=1.6*10^-19;// in C
12 sigma=nh*mu_h*e;
13 format('v',6)
14 disp(sigma,"conductivity ,(ohm^-1-m^-1) = ")
15 //conductivity is calculated wrong in the book
```

Scilab code Exa 1.11 donor concentration

```
1 //Example 1.11:
2 clc;
3 clear;
4 close;
5 //given data :
6 p=0.15;// in ohm-m
7 mu_e=0.39;// mobility of electron in m^2/V-s
8 e=1.6*10^-19;// in C
9 Na=1/(e*mu_e*p);
10 format('e',9)
```

```
11 disp(Na,"The value of donor concentration ,Na(m-3) =
    ")
```

Scilab code Exa 1.12 resistivity

```
1 //Example 1.12:
2 clc;
3 clear;
4 close;
5 //given data :
6 mu_n=0.13; // in m2/V-s
7 mu_p=0.05; // in m2/V-s
8 ni=1.5*1016; // in m-3
9 e=1.6*10-19; // in C
10 p=1/((e*ni)*(mu_n+mu_p));
11 format('v',7)
12 disp(p,"The resistivity ,p(ohm-m) = ")
```

Scilab code Exa 1.13 current

```
1 //Example 1.13:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10-19; // electron charge in coulombs
7 k=1.38*10-23; //Boltzmann constant in m2-kg/s2-K
    ^-1
8 T=300; //in Kelvin
9 Vt=(k*T)/e; //in V
10 I=240; //in mA
11 eta=2; //
12 Ve=0.8; //in V
```

```

13 V=0.7; //in V
14 Id=I*exp((V-Ve)/(eta*Vt)); //in mA
15 format('v',5)
16 disp(round(Id),"(i) Current is ,(mA)=")
17 Ir=(I/((exp(Ve/(eta*Vt)))-1))*10^6; //
18 format('v',4)
19 disp(round(Ir),"(ii) reverse saturation current is
    ,(nA)=")
20 //reverse saturation current is calculated wrong in
    the textbook

```

Scilab code Exa 1.14 diode current and voltage

```

1 //Example 1.14:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10^-19; // electron charge in coulombs
7 k=1.38*10^-23; //Boltzmann constant in m^2-kg/s^2-K
    ^-1
8 T=300; //in Kelvin
9 Vt=(k*T)/e; //in V
10 Ir1=10^-10; //in A
11 Ir2=10^-12; //in A
12 V21=((Vt)*log10(Ir1/Ir2))*2.3026; //in V
13 V211=0.5; //in V
14 V2=(1/2)*(V21+V211); //in V
15 V1=(1/2)*(V211-V21); //in V
16 I1=Ir2*exp(V2/Vt)*10^6; //in micro-A
17 I2=I1; //
18 format('v',8)
19 disp(V2,"diode voltage V2 is ,(V)=")
20 disp(V1,"diode voltage V1 is ,(V)=")
21 format('v',7)

```



```
22 disp(I1,"diode current is ,(micro-A)=")
23 //diode current is calculated wrong in the textbook
```

Scilab code Exa 1.15 voltage

```
1 //Example 1.15:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10^-19;// electron charge in coulombs
7 k=1.38*10^-23;//Boltzmann constant in m^2-kg/s^2-K
   ^-1
8 T=300;//in Kelvin
9 Vt=(k*T)/e;//in V
10 Ir1=10^-12;//in A
11 Ir2=10^-10;//in A
12 I21=Ir2/Ir1;//
13 It=2;//mA
14 I1=It/(1+I21)*10^3;//in micro-A
15 I2=It*10^3-I1;//in micro-A
16 I1=I2/I21;//in micro-A
17 x=((I1*10^-6)/Ir1);//
18 V=Vt*log10(x)*2.3026;//in V
19 format('v',6)
20 disp(V,"diode voltage is ,(V)=")
```

Scilab code Exa 1.16 voltage

```
1 //Example 1.16:
2 clc;
3 clear;
4 close;
```

```

5 //given data :
6 format('v',5)
7 T=27; //degree Celsius
8 Tk=273+T; //in Kelvin
9 e=1.6*10^-19; // electron charge in coulombs
10 k=1.38*10^-23; //Boltzmann constant in m^2-kg/s^2-K
    ^-1
11 J=10^4; //in Amp/m^2
12 Jo=200; //in mA/m^2
13 x=(J/(Jo*10^-3)); //
14 Ve=((log(x))*k*Tk)/e; //in V
15 disp(Ve," voltage to be applied is ,(V)=")

```

Scilab code Exa 1.17 resistance

```

1 //Example 1.17:
2 clc;
3 clear;
4 close;
5 format('v',5)
6 V=3; //in V
7 I=55; //in mA
8 Rdc=V/(I*10^-3); //in ohm
9 V2=26; //in mV
10 Rac=V2/I; //in ohm
11 disp(Rdc," static resistance is ,(ohm)=")
12 disp(Rac," dynamic resistance is ,(ohm)=")

```

Scilab code Exa 1.18 resistance

```

1 //Example 1.18:
2 clc;
3 clear;

```

```

4 close;
5 //given data :
6 format('v',5)
7 k=1.38*10^-23; // constant
8 T=27+273; // in K
9 eta=2;
10 e=1.6*10^-19; // in C
11 Vt=(k*T/e); // in V
12 V=0.5; // in V
13 Ir=10^-6; // in A
14 I=(Ir*10^3*(exp(V/(eta*Vt))-1)); // in A
15 R_dc=V*10^3/I;
16 disp(R_dc,"static resistance ,R_dc(ohm) = ")
17 R_ac=(eta*k*T)/(e*I*10^-3);
18 format('v',5)
19 disp(R_ac,"Dynamic resistance ,R_ac(ohm) = ")
20 // answer is wrong in textbook

```

Scilab code Exa 1.19 resistance

```

1 //Example 1.19:
2 clc;
3 clear;
4 close;
5 //given data :
6 V=1.2; // in V
7 Vk=0.7; // in V
8 I_F=100; // in mA
9 R_B=(V-Vk)/(I_F*10^-3);
10 V_R=10; // in V
11 I_R=1; // in micro-A
12 R_R=V_R/I_R;
13 format('v',3)
14 disp(R_B,"the bulk resistance ,R_B(ohm) = ")
15 disp(R_R,"the reverse resistance ,R_R(M-ohm) = ")

```

```

16 eta=2;
17 I=5; // in mA
18 R_ac=eta*26/I;
19 format('v',5)
20 disp(R_ac,"ac resistance ,R_ac(ohm) = ")

```

Scilab code Exa 1.20 capacitance

```

1 //Example 1.20:
2 clc;
3 clear;
4 close;
5 //given data :
6 epsilon_0=8.85*10^-12; // in farada/m
7 K=12; // constant for silicon
8 epsilon=epsilon_0*K
9 A=1*10^-8; // in m^2
10 W=5*10^-7; // in m
11 Ct=epsilon*A*10^14/W;
12 format('v',6)
13 disp(Ct,"the transition capacitance ,Ct(PF) = ")

```

Scilab code Exa 1.21 resistance

```

1 //Example 1.21:
2 clc;
3 clear;
4 close;
5 //given data :
6 V=0.2; // in V
7 I=1; // in micro-A
8 R_dc=V*10^3/I;
9 R_ac=26/(I*10^3);

```

```
10 format('v',5)
11 disp(R_dc,"The static resistance ,R_ac(k-ohm) = ")
12 format('v',6)
13 disp(R_ac,"the dynamic resistance ,R_ac(ohm) = ")
```

Chapter 2

Special Purpose Diodes

Scilab code Exa 2.1 maximum current

```
1 //Example 2.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Pmax=364; //dissipation in milliwatt
7 Vz=9.1; //in V
8 Izmax=Pmax/Vz; //in mA
9 format('v',4)
10 disp(Izmax,"maximum current the diode can handle is
    ,(mA)=")
```

Scilab code Exa 2.2 resistance

```
1 //Example 2.2:
2 clc;
3 clear;
4 close;
```

```

5 //given data :
6 mip=15;//in volt
7 op=6.8;//output potential in volt
8 pd=mip-op;//potential difference across series
  resistor
9 I1=5;//load current in mA
10 nmip=20;//new maximum input voltage in volt
11 pd1=nmip-op;//new potential difference across series
  resistor
12 I11=20;//new load current in mA
13 R=((pd1-pd)/((I11-I1)*10^-3));//resistance in ohm
14 format('v',6)
15 disp(R,"value of series resistance is ,(ohm)=")

```

Scilab code Exa 2.3 current

```

1 //Example 2.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 V=120;//in V
7 Vz=50;//in V
8 vd5=V-Vz;//voltage drop across 5 ohm resistor
9 R=5;// in ohm
10 I5=vd5/R;//current through 5 ohm resistor
11 R1=10;// in k-ohm
12 I1=Vz/(R1*10^3);//current through load resistor
13 Iz=I5-I1;//in A
14 format('v',7)
15 disp(Iz,"current through zener diode is ,(A)=")

```

Chapter 3

Bi Polar Junction Transistor

Scilab code Exa 3.1 variation in alpha and value of beta

```
1 //Example 3.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Beta=50; //amplification factor
7 dbb=1; //percentage variation in degree celsius
8 daa=dbb/50; //variation in degree celsius
9 format('v',5)
10 disp(daa,"(i) variation in alpha for a silicon BJT
    is ,(%/degree-Celsius)=")
11 temp=325; //in K
12 t=25; //degree celsius
13 Beta1=dbb*t; //in %
14 nBeta=Beta+(Beta1/100)*t; //
15 format('v',6)
16 disp(nBeta,"new value of Beta is ,=")
```

Scilab code Exa 3.2 current amplification factor


```

1 //Example 3.2:
2 clc;
3 clear;
4 close;
5 format('v',4)
6 //given data :
7 del_Ic=1*10^-3;// in A
8 del_Ib=50*10^-6;// in A
9 Beta=del_Ic/del_Ib;
10 disp(Beta,"The current amplification factor ,Beta = "
      )

```

Scilab code Exa 3.3 base current

```

1 //Example 3.3:
2 clc;
3 clear;
4 close;
5 format('v',5)
6 //given data :
7 alfa=0.88;
8 Ie=1;// in mA
9 Ic=alfa*Ie;// in mA
10 I_B=Ie-Ic;
11 disp(I_B,"Base current ,(mA) = ")

```

Scilab code Exa 3.4 short circuit current gain

```

1 //Example 3.4:
2 clc;
3 clear;
4 close;
5 format('v',5)

```

```

6 //given data :
7 del_Ic=0.95*10^-3; // in A
8 del_Ie=1*10^-3; // in A
9 alfa=del_Ic/del_Ie;
10 disp(alfa,"the short circuit current gain, = ")

```

Scilab code Exa 3.5 collector and base current

```

1 //Example 3.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 Ie=5*10^-3; // in A
8 alfa=0.95;
9 I_co=10*10^-6; // in A
10 Ic=((alfa*Ie)+I_co)*10^3;
11 Ib=(Ie-(Ic*10^-3))*10^6;
12 disp(Ic,"Collector current ,(mA) = ")
13 disp(Ib,"Base current ,(micro-A) = ")

```

Scilab code Exa 3.6 Ic Ib and Ico

```

1 //Example 3.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ie=5; // in mA
7 alfa=0.99;
8 I_co=0.005; // in mA
9 Ic=((alfa*Ie)+I_co);

```

```

10 Ib=(Ie-Ic);
11 Beta=alfa/(1-alfa);
12 I_CEO=I_co/(1-alfa);
13 format('v',6)
14 disp(Ic,"Ic ,(mA) = ")
15 format('v',4)
16 disp(Ib*10^3,"Ib ,(micro-A) = ")
17 disp(Beta,"Beta = ")
18 format('v',6)
19 disp(I_CEO*10^3,"I_CEO(micro-A) = ")

```

Scilab code Exa 3.7 change in collector current

```

1 //Example 3.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 alfa=0.9;// constant
7 Beta=alfa/(1-alfa);
8 Del_Ib=4;// in mA
9 Del_Ic=Beta*Del_Ib;
10 format('v',4)
11 disp(Del_Ic,"the change in the collector current ,(mA
    ) = ")

```

Scilab code Exa 3.8 emitter current

```

1 //Example 3.8:
2 clc;
3 clear;
4 close;
5 //given data :

```

```

6 Beta=40;
7 Ib=25; // base current in micro-A
8 Ic=Beta*Ib;
9 Ie=(Ib+Ic)*10^-3;
10 format('v',6)
11 disp(Ie,"Ie ,(mA) = ")

```

Scilab code Exa 3.9 beta

```

1 //Example 3.9:
2 clc;
3 clear;
4 close;
5 //given data :
6 alfa=0.98; // constant
7 Beta=alfa/(1-alfa);
8 format('v',4)
9 disp(Beta,"Beta = ")

```

Scilab code Exa 3.10 error

```

1 //Example 3.10:
2 clc;
3 clear;
4 close;
5 //given data :
6 Beta=100; // constant
7 Ib=20*10^-6; // in A
8 I_co=500*10^-9; // in A
9 Ic1=((Beta*Ib)+(1+Beta)*I_co)*10^3;
10 Ic2=(Beta*Ib)*10^3;
11 Error=(Ic1-Ic2)*100/Ic1;
12 format('v',5)

```

```
13 disp(Error,"The error ,(%) = ")
14 //answer is wrong in the txtbook
```

Scilab code Exa 3.11 change in base current

```
1 //Example 3.11:
2 clc;
3 clear;
4 close;
5 //given data :
6 alfa=0.98; //
7 del_Ie=5; // in mA
8 del_Ic=alfa*del_Ie; // in mA
9 del_Ib=del_Ie-del_Ic;
10 format('v',4)
11 disp(del_Ib,"change in base current ,(mA) = ")
```

Scilab code Exa 3.12 collector current base current and alfa

```
1 //Example 3.12:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ie=8.4; // in mA
7 cr=0.8/100; // carriers recombine in base in %
8 Ib=cr*Ie;
9 format('v',6)
10 disp(Ib,"(a). The base current ,Ib(mA) = ")
11 Ic=Ie-Ib;
12 format('v',5)
13 disp(Ic,"(b). The collector current ,Ic(mA) = ")
14 alfa=Ic/Ie;
```

```
15 format('v',6)
16 disp(alfa,"(c). the value of alfa = ")
```

Scilab code Exa 3.13 ac current gain

```
1 //Example 3.13:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ie1=20; // in mA
7 Ie2=15; // in mA
8 Ib1=0.48; // in mA
9 Ib2=0.32; // in mA
10 del_Ie=(Ie1-Ie2)*10^-3; // in A
11 del_Ib=(Ib1-Ib2)*10^-3; // in A
12 del_Ic=del_Ie-del_Ib; // in A
13 alfa=del_Ic/del_Ie; //
14 Beta=del_Ic/del_Ib;
15 format('v',5)
16 disp(alfa,"ac current gain in common base
    arrangement, = ")
17 format('v',4)
18 disp(Beta,"ac current gain in common emitter
    arrangement, = ")
```

Scilab code Exa 3.14 Beta I_{ceo} and collector current

```
1 //Example 3.14:
2 clc;
3 clear;
4 close;
5 //given data :
```

```

6  alfa=0.992; // constant
7  Beta=alfa/(1-alfa);
8  format('v',5)
9  disp(Beta,"(a) Beta= ")
10 I_CB0=48*10^-9; // in A
11 I_CEO=(1+Beta)*I_CB0*10^6;
12 format('v',3)
13 disp(I_CEO,"(a) I_CEO (micro-A) = ")
14 Ib=30*10^-6; // in A
15 Ic=((Beta*Ib)+(1+Beta)*I_CB0)*10^3;
16 format('v',5)
17 disp(Ic,"(b) Collector current ,Ic(mA) = ")

```

Scilab code Exa 3.15 collector current alfa and beta

```

1  //Example 3.15:
2  clc;
3  clear;
4  close;
5  //given data :
6  format('v',5)
7  Ie=9.6; //emitter current in mA
8  Ib=0.08; //base current in mA
9  Ic=Ie-Ib; //
10 format('v',5)
11 disp(Ic,"(a). collector current ,Ic(mA) = ")
12 alfa=Ic/Ie;
13 format('v',5)
14 disp(alfa,"(b). alfa = ")
15 alfa=0.99; //
16 Beta=alfa/(1-alfa)
17 format('v',4)
18 disp(Beta,"(c). Beta = ")

```

Scilab code Exa 3.16 collector current

```
1 //Example 3.16:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ib=68*10^-6; // in A
7 Ie=30*10^-3; // in A
8 Beta=440; // constant
9 alfa=Beta/(1+Beta);
10 Ic=alfa*Ie*10^3;
11 format('v',6)
12 disp(Ic," Collector current ,Ic (mA) = ")
```

Chapter 4

Small signal amplifiers

Scilab code Exa 4.1 voltage

```
1 //Example 4.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 Rc=4.7; // in ohm
8 Vcc=24; // in V
9 Ic=1.5; //in mA
10 //this is given as 15 mA in textbook which is wrong
11 Vce=Vcc-(Ic*Rc*10^-3*10^3); //in V
12 disp(Vce,"(i) Collector to emitter voltage ,Vce(V) =
    ")
13 Ic1=0; //in A
14 Vce1=Vcc-Ic1*Rc; //in V
15 format('v',4)
16 disp(Vce1,"(ii) Collector to emitter voltage ,Vce(V)
    = ")
```

Scilab code Exa 4.2 vce

```
1 //Example 4.2:
2 clc;
3 clear;
4 close;
5 //given data :
6 Beta=100;
7 Rb=200*10^3; // in ohm
8 Rc=1*10^3; // in ohm
9 Vcc=10; // in V
10 Ib=Vcc/Rb; // in A
11 Ic=Beta*Ib; //in A
12 Vce=Vcc-(Ic*Rc);
13 format('v',4)
14 disp(Vce," Collector to emitter voltage ,Vce(V) = ")
```

Scilab code Exa 4.3 base resistance

```
1 //Example 4.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 Vcc=20; // in V
8 Vbe=0.7; // in V
9 Rc=2; //in kilo-ohm
10 Icsat= Vcc/Rc; //in mA
11 Beta=200; //
12 Ib=(Icsat/Beta)*10^3; //in micro-A
13 Rb=((Vcc-Vbe)/(Ib))*10^3; //in kilo-ohm
14 disp("Rb < "+string(Rb)+" kilo-ohm")
```

Scilab code Exa 4.4 operating point

```
1 //Example 4.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=15; // in V
7 Rb=200; // in k-ohm
8 Rc=2; // in k-ohm
9 Beta=50;
10 Ib=(Vcc/(Rb*10^3+(Beta*Rc*10^3)))*10^6; //in micro-A
11 Ic=Beta*Ib*10^-3; //in mA
12 Vce=Vcc-(Ic*10^-3*(Rc*10^3));
13 format('v',4)
14 disp(Ic," collector current ,Ic(mA) = ")
15 disp(Vce," Collector to emitter voltage ,Vce(V) = ")
```

Scilab code Exa 4.5 resistor

```
1 //Example 4.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=15; // in V
7 Vce=6; // in V
8 Rc=3*10^3; // in ohm
9 Beta=50;
10 Ic=(Vcc-Vce)/Rc;
11 Ib=Ic/Beta;
12 Rb=((Vcc/Ib)-(Beta*Rc))*10^-3;
```

```
13 format('v',5)
14 disp(Rb,"The value of resistoe ,Rb(k-ohm) = ")
```

Scilab code Exa 4.6 operating point

```
1 //Example 4.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=12; // in V
7 Rb1=70; // in k-ohm
8 Rb2=70; // in k-ohm
9 Beta=50;
10 Rc=2; // in k-ohm
11 Ib=Vcc/((Rb1+Rb2+(Beta*Rc))*10^3);
12 Ic=Beta*Ib*10^3;
13 Vce=Vcc-(Ic*Rc);
14 format('v',4)
15 disp(Ic," collector current ,Ic(mA) = ")
16 disp(Vce," Collector to emitter voltage ,Vce(V) = ")
```

Scilab code Exa 4.7 operating point

```
1 //Example 4.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=9; // in V
7 Rb=50; // in k-ohm
8 Rc=250; // in ohm
9 Re=500; // in ohm
```

```

10 Beta=80;
11 Ib=Vcc/(Rb*10^3+(Beta*Re));
12 Ic=Beta*Ib*10^3;
13 Vce=Vcc-(Ic*10^-3*(Rc+Re));
14 format('v',3)
15 disp(Ic," collector current ,Ic(mA) = ")
16 disp(Vce," Collector to emitter voltage ,Vce(V) = ")

```

Scilab code Exa 4.8 operating point

```

1 //Example 4.8:
2 clc;
3 clear;
4 close;
5 //given data :
6 R2=4; // in k-ohm
7 R1=40; // in k-ohm
8 Vcc=22; // in V
9 Rc=10; // in k-ohm
10 Re=1.5; // in k-ohm
11 Vbe=0.5; // in V
12 Voc=R2*10^3*Vcc/((R1+R2)*10^3);
13 Ic=(Voc-Vbe)/(Re*10^3);
14 Vce=Vcc-(Rc+Re)*Ic*10^3;
15 format('v',5)
16 disp(Vce," Collector to emitter voltage ,Vce(V) = ")

```

Scilab code Exa 4.9 maximum collector current

```

1 //Example 4.9:
2 clc;
3 clear;
4 close;

```

```

5 //given data :
6 Bv=12;//battery voltage in V
7 Cl=6;//collector load in k-ohm
8 CC=Bv/Cl;
9 format('v',4)
10 disp(CC,"Collector current ,(mA) = ")

```

Scilab code Exa 4.10 maximum collector current

```

1 //Example 4.10:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 Bv=12;//battery voltage in V
8 P=2;// power in Watt
9 Ic=(P/Bv)*10^3;
10 disp(Ic,"The maximum collector current ,Ic(mA) = ")

```

Scilab code Exa 4.11 gain

```

1 //Example 4.11:
2 clc;
3 clear;
4 close;
5 //given data :
6 del_ic=1;// in mA
7 del_ib=10;// in micro-A
8 del_Vbe=0.02;// in V
9 del_ib=10*10^-6;// in A
10 Rc=2;// in k-ohm
11 Rl=10;// in k-ohm

```

```

12 Beta=del_ic/(del_ib*10^3);//
13 format('v',5)
14 disp(Beta," Current gain ,Beta = ")
15 Ri=(del_Vbe/del_ib)*10^-3;
16 format('v',4)
17 disp(Ri," Input impedance ,Ri(k-ohm) = ")
18 Rac=Rc*Rl/(Rc+Rl);
19 format('v',5)
20 disp(Rac," Effective load ,Rac(k-ohm) = ")
21 Av=round(Beta*Rac/Ri);
22 format('v',4)
23 disp(Av," Voltage gain ,Av = ")
24 Ap=Beta*Av;
25 format('v',6)
26 disp(Ap," power gain ,Ap = ")

```

Scilab code Exa 4.12 output voltage

```

1 //Example 4.12:
2 clc;
3 clear;
4 close;
5 //given data :
6 Rc=10;// in k-ohm
7 Rl=10;// in k-ohm
8 Beta=100;
9 Ri=2.5;
10 Iv=2;// input voltage in mV
11 Rac=Rc*Rl/(Rc+Rl);
12 Av=round(Beta*Rac/Ri);
13 Ov=Av*Iv*10^-3;
14 format('v',4)
15 disp(Ov," Output voltage ,(V) = ")

```

Scilab code Exa 4.13 gain and resistance

```
1 //Example 4.13:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 I=1;
8 hfe=46;
9 hoe=80*10^-6; // in mho
10 hre=5.4*10^-4;
11 hie=800; // in ohm
12 RL=5*10^3; // in ohm
13 Aie=hfe/(I+(hoe*RL));
14 Zie=hie-(hre*RL*Aie);
15 Ave=(Aie*RL)/Zie;
16 Rg=500; // in ohm
17 Zoe=((hie+Rg)/(hoe*(hie+Rg)-(hfe*hre)))/10^3;
18 Ape=Aie*Ave;
19 disp(Aie,"Current gain ,Aie = ")
20 format('v',6)
21 disp(Zie,"Input resistance ,Zie(ohm) = ")
22 disp(Ave,"Voltage gain ,Ave = ")
23 format('v',5)
24 disp(Zoe,"Output resistance ,Zoe(k-ohm) = ")
25 format('v',7)
26 disp(Ape,"Power gain ,Ape = ")
27 //voltage gain and power gain are calculated wrong
    in the textbook
```

Scilab code Exa 4.14 gain and voltage


```

1 //Example 4.14:
2 clc;
3 clear;
4 close;
5 //given data :
6 A=100; //gain without feedback
7 Beta=1/25; //feed back ratio
8 Af=(A/(1+(Beta*A))); //gain with feedback
9 disp(Af,"(i) gain with feedback is ,=")
10 ff=Beta*A; //feedback factor
11 disp(ff,"feedback factor is ,=")
12 vi=50; //mV
13 Vo=Af*vi*10^-3; //in V
14 disp(Vo,"output voltage is ,(V)=")
15 fv=Beta*Vo; //in V
16 format('v',5)
17 disp(fv,"feedback voltage is ,(V)=")
18 vin=vi*(1+Beta*A); //mV
19 disp(vin,"new increased input voltage is ,(mV)=")

```

Scilab code Exa 4.15 voltage gain

```

1 //Example 4.15:
2 clc;
3 clear;
4 close;
5 //given data :
6 A=1000; //gain without feedback
7 fctr=0.40; //gain reduction factor
8 Af=A-fctr*A; //gain with feedback
9 Beta=((A/Af)-1)/A; //feed back ratio
10 A2=800 ; //reduced gain
11 Af2=((A2)/(1+(Beta*A2))); //
12 format('v',6)
13 disp(Af2,"(i) voltage gain is ,=")

```

```

14 prfb= ((A-A2)/A)*100; //percentage reduction without
    feedback
15 format('v',4)
16 disp(prfb,"(ii) percentage reduction without
    feedback is ,(%)=")
17 prwfb= ((Af-Af2)/Af)*100; //percentage reduction
    without feedback
18 format('v',6)
19 disp(prwfb,"percentage reduction with feedback is ,(%)
    )=")

```

Scilab code Exa 4.16 small change in gain

```

1 //Example 4.16:
2 clc;
3 clear;
4 close;
5 //given data :
6 A=200; //gain without feedback
7 Beta=0.25; //feed back ratio
8 gc=10; //percent gain change
9 dA=gc/100; //
10 dAf= ((1/(1+Beta*A)))*dA; //
11 format('v',7)
12 disp(dAf,"small change in gain is,=")

```

Scilab code Exa 4.17 input voltage

```

1 //Example 4.17:
2 clc;
3 clear;
4 close;
5 //given data :

```

```

6  format('v',5)
7  A=200; //gain without feedback
8  Beta=0.05; //feed back ratio
9  Af=(A/(1+(Beta*A))); //gain with feedback
10 disp(Af," gain with negative feedback is ,=")
11 Dn=10; //percentage distortion
12 format('v',6)
13 Dn1=(Dn/(1+A*Beta)); //percentage Distortion with
    negative feedback
14 ff=Beta*A; //feedback factor
15 vo=0.5; //initial output voltage
16 vi=A*vo; //in V
17 vin=vi/Af; //in V
18 disp(Dn1," percentage Distortion with negative
    feedback is ,(%)=")
19 disp(vin,"new input voltage is ,(V)=")
20 //gain and input voltage are calculated wrong in the
    textbook

```

Scilab code Exa 4.18 percentage of feedback

```

1  //Example 4.18:
2  clc;
3  clear;
4  close;
5  //given data :
6  format('v',5)
7  A=50; //gain without feedback
8  Af=10; //gain with feedback
9  Beta=((A/Af)-1)/A)*100; //feed back ratio
10 disp(Beta," percentage of feedback is ,(%)=")

```

Scilab code Exa 4.19 band width

```

1 //Example 4.19:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 Bw=200; //bandwidth in kHz
8 vg=40; //dB
9 fb=5; //percentage negative feedback
10 A=40; //gain without feedback
11 Beta=fb/100; //feed back ratio
12 Af=(A/(1+(Beta*A))); //gain with feedback
13 Bwf= (A*Bw)/Af; //Bandwidth with feedback
14 disp(Bwf," new band-width is ,(kHz)=")

```

Scilab code Exa 4.20 percentage reduction

```

1 //Example 4.20:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 A=50; //gain without feedback
8 Af=25; //gain with feedback
9 Beta=((A/Af)-1)/A; //feed back ratio
10 Ad=40; //new gain after ageing
11 Af1=(Ad/(1+(Beta*Ad))); //new gain with feedback
12 df=Af-Af1; // reduction in gain
13 pdf= (df/Af)*100; //percentage reduction in gain
14 disp(pdf," percentage reduction in gain is ,(%)=")

```

Scilab code Exa 4.21 Av and beta

```
1 //Example 4.21:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 Af=100;//gain with feedback
8 vi=50;//in mV
9 vi1=60;//in mV
10 AAf=vi1/vi;//
11 A=AAf*Af;//
12 Beta=(((A/Af)-1)/A);//feed back ratio
13 disp(A,"Av is ,=")
14 format('v',8)
15 disp(Beta," feedback factor is ,=")
```

Chapter 5

Power Amplifiers

Scilab code Exa 5.1 efficiency

```
1 //Example 5.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Pac=0.1; //in W
7 Vcc=20; //in V
8 Ic=20; //in mA
9 Pdc=Vcc*Ic*10^-3; //in W
10 eta=(Pac/Pdc)*100; //efficiency
11 format('v',4)
12 disp(eta," efficiency is ,(%)=")
```

Scilab code Exa 5.2 collector current

```
1 //Example 5.2:
2 clc;
3 clear;
```

```

4 close;
5 //given data :
6 Pac=2;//in W
7 Vcc=12;//in V
8 Ic=(Pac*sqrt(2)*sqrt(2))/Vcc;//in A
9 format('v',5)
10 disp(Ic,"maximum collector current is ,(A)=")

```

Scilab code Exa 5.3 collector efficiency and power rating

```

1 //Example 5.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 Pac=3;//in W
7 Pdc=10;//in W
8 eta=(Pac/Pdc)*100;//percentage efficiency
9 format('v',4)
10 disp(eta,"collector efficiency is ,(%)=")
11 disp(Pdc,"power rating of transistor is ,(W)=")

```

Scilab code Exa 5.4 power

```

1 //Example 5.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 dIc=100;//in mA
7 Rl=6;//in ohm
8 mv=dIc*Rl*10^-3;//in V
9 pd=mv*dIc;//in mW

```

```

10 disp(pd,"(i) power developed in loudspeaker is ,(mW)
    =")
11 dVc=10; //in V
12 oi=(dVc/dIc)*10^3; //in ohm
13 Rl=6; //in ohm
14 n=sqrt(oi/Rl); //turn ratio of transformer
15 tsv=dVc/n; //om V
16 Il=tsv/Rl; //in A
17 ptr= Il^2*Rl*10^3; //in mW
18 format('v',5)
19 disp(ptr,"(ii) power transferred to loudspeaker is
    ,(mw)=")
20 //in textbook in second case there is one point
    deviation in the answer.

```

Scilab code Exa 5.5 power

```

1 //Example 5.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 n=10; //turn ratio
7 Rl=10; //ohm
8 Rld=n^2*Rl; //in ohm
9 Ic=100; //in mA
10 Irms=Ic/(sqrt(2)); //in mA
11 P=Irms^2*Rld; //in W
12 format('v',3)
13 disp(P*10^-6,"maximum power output is ,(W)=")

```

Scilab code Exa 5.6 harmonic distortions and change in power


```

1 //Example 5.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 //ie=15*sin 400*t+1.5*sin 800*t + 1.2*sin 1200*t +
   0.5*sin 1600*t given equation
7 I2=1.5; //in A
8 I1=15; //in A
9 I3=1.2; //in A
10 I4=0.5; //in A
11 D2=(I2/I1)*100; //Second percentage harmonic
   distortion
12 D3=(I3/I1)*100; //Third percentage harmonic
   distortion
13 //in book I2 is mentioned wrongly in place of I1
14 D4=(I4/I1)*100; //Fourth percentage harmonic
   distortion
15 disp(" part (i)")
16 disp(D2,"Second percentage harmonic distortion (D2)
   is ,(%)=")
17 disp(D3,"Third percentage harmonic distortion (D3)
   is ,(%)=")
18 format('v',5)
19 disp(D4,"Fourth percentage harmonic distortion (D4)
   is ,(%)=")
20 disp(" part (ii)")
21 D=sqrt(D2^2+D3^2+D4^2)/100; //Distortion Factor
22 P1=1; //assume
23 P=(1+D^2)*P1; //in W
24 peri=((P-P1)/P1)*100; //percentage increase in power
   due to distortion
25 disp(peri,"percentage increase in power due to
   distortion is ,(%)=")

```

Scilab code Exa 5.7 power dissipated

```
1 //Example 5.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=15; //in V
7 Vpeak=24/2; //in V
8 Rl=100; //in ohm
9 Ipeak= Vpeak/Rl; //in A
10 Pdc=Vcc*(2/(%pi))*Ipeak; //in W
11 pad=(1/2)*(Vpeak^2)/Rl; //in W
12 pd=Pdc-pad; //in W
13 pde=pd/2; //in W
14 disp(pde*10^3,"power dissipated by each transistor
      is ,(mW)=")
```

Chapter 6

Field Effect Transistors

Scilab code Exa 6.1 drain resistance transconductance and amplification factor

```
1 //Example 6.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vgs= [0;0;0.3]; //in V
7 Vds=[5;10;10]; //in V
8 Id=[8;8.2;7.6]; //in mA
9 dVds=Vds(2)-Vds(1); //in V
10 dId=Id(2)-Id(1); //in mA
11 rd=(dVds/dId); //in kilo-ohm
12 format('v',4)
13 disp(rd,"(i) A.C. Drain resistance is ,(kilo-ohm)=")
14 dVgs=Vgs(3)-Vgs(2); //in V
15 dId1=Id(2)-Id(3); //in mA
16 gm=dId1/dVgs; //in mA/volt
17 format('v',3)
18 disp(gm,"(ii) Transconductance is ,(mS)=")
19 mu=gm*rd; //A/V
20 format('v',4)
```

```
21 disp(mu,"(iii) Amplification factor is ,=")
22 //Transconductance and Amplification factor are
    calculated wrong in the textbook
```

Scilab code Exa 6.2 mutual conductance

```
1 //Example 6.2:
2 clc;
3 clear;
4 close;
5 //given data :
6 I1=1; // in mA
7 I2=1.2; // in mA
8 del_ID=(I2-I1);
9 V1=-3; // in V
10 V2=-2.9; // in V
11 del_VGS=V2-V1; // in V
12 gm=del_ID/del_VGS;
13 format('v',4)
14 disp(gm,"mutual conductance ,gm(mS) = ")
```

Scilab code Exa 6.3 pinch off voltage

```
1 //Example 6.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',4)
7 a=5.6*10^-6/2; // channel width in m
8 epsilon0=8.86*10^-12; // in F/m
9 epsilon=12*epsilon0; // in F/m
10 Nd=10^21; // in m^-3
```

```

11 e=1.6*10^-19; // in V
12 Vp=e*Nd*a^2/(2*epsilon);
13 disp(Vp,"Pinch off voltage ,Vp(V) = ")

```

Scilab code Exa 6.4 ID gm and gmo

```

1 //Example 6.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 I_DES=8.7; // in mA
7 V1=-3; // in V
8 V_GS=-1; // in V
9 ID=I_DES*(1-(V_GS/V1))^2;
10 format('v',6)
11 disp(ID,"(i). ID(mA) = ")
12 gmo=-(2*I_DES/V1);
13 format('v',4)
14 disp(gmo,"(ii). gmo(mS) = ")
15 gm=gmo*(1-(V_GS/V1));
16 format('v',6)
17 disp(gm,"(iii). gm(mA) = ")

```

Scilab code Exa 6.5 Vgs

```

1 //Example 6.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',4)
7 ID=3; // in mA

```

```
8 I_DSS=9; // in mA
9 Vp=-4.5; // in V
10 Vgs=-Vp*(sqrt(ID/I_DSS)-1);
11 disp(Vgs,"Vgs(V) = ")
```

Scilab code Exa 6.6 voltage amplification

```
1 //Example 6.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 gm=3; //Transconductance in mS
7 rl=10; //load resistance in kilo-ohm
8 av=gm*rl; //
9 format('v',4)
10 disp(av,"the voltage amplification is ,=")
```

Scilab code Exa 6.7 output voltage

```
1 //Example 6.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 Rl=20; //in kilo-ohm
7 Rs=1; //in kilo-ohm
8 Rg=1; //in M-ohm
9 Cs=25; //in micro-F
10 mu=20; //amplification factor
11 rd=100; //in kilo-ohm
12 vi=2; //in V
13 f=1; //in kilo-Hz
```

```
14 Xc=((1/(2*pi*f*10^3*Cs*10^-6))); //in ohm
15 A=((mu*Rl*10^3)/((rd+Rl)*10^3)); //Voltage gain
16 Vo=A*vi; //in V
17 format('v',5)
18 disp(Vo," amplifier output signal voltage is ,(V)=")
```

Chapter 9

Silicon Controlled Rectifier

Scilab code Exa 9.1 average voltage

```
1 //Example 9.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vm=200;// in V
7 theta=30;//firing angle in degree
8 vdc=((Vm/%pi)*(1+cosd(theta)));//in V
9 format('v',5)
10 disp(round(vdc),"average value of voltage is ,(V)=")
```

Scilab code Exa 9.2 dc load current rms load current amd power dissipated

```
1 //Example 9.2:
2 clc;
3 clear;
4 close;
```



```

5 //given data :
6 Va=300; // in V
7 Vm=300*sqrt(2); //in V
8 Rl=50; //in ohm
9 theta1=90; //firing angle in degree
10 idc=((Vm/(2*%pi*Rl))*(1+cosd(theta1))); //in A
11 format('v',6)
12 disp(idc,"(i) the dc load current is ,(A)=")
13 irms=Va/(2*Rl); //in A
14 format('v',4)
15 disp(round(irms),"(ii) the rms load current is ,(A)=")
16 P=irms^2*Rl; //in W
17 format('v',5)
18 disp(round(P),"(iii) the power dissipated by the
    load is ,(W)=")

```

Scilab code Exa 9.3 firing angle conducting angle and average current

```

1 //Example 9.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ih=0; //in A
7 Vi=100; // in V
8 Vm=200; //in V
9 Rl=100; //in ohm
10 theta1=asind(Vi/Vm); //firing angle in degree
11 ca=180-theta1; //conducting angle in degree
12 format('v',4)
13 disp(theta1,"(i) firing angle is ,(degree)=")
14 format('v',5)
15 disp(ca,"(ii) conducting angle is ,(degree)=")
16 av=((Vm/(2*%pi))*(1+cosd(theta1))); //in V

```

```
17 ac=av/R1; //in A
18 format('v',7)
19 disp(ac,"(iii) average current is ,(A)=")
20 //average current is wrong in the textbook
```

Chapter 10

The Unijunction Transistor

Scilab code Exa 10.1 stand off and peak point voltage

```
1 //Example 10.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vbb=20; // in V
7 eta=0.6; // instrinsic stand off ratio
8 Vb=0.7; // in V
9 sov=eta*Vbb; // Stand off voltage
10 format('v',4)
11 disp(sov,"(i). Stand off voltage ,(V) = ")
12 Vp=(eta*Vbb)+Vb;
13 format('v',6)
14 disp(Vp,"(ii). Peak point voltage ,Vp(V) = ")
```

Scilab code Exa 10.2 time period

```
1 //Example 10.2:
```

```

2  clc;
3  clear;
4  close;
5  format('v',6)
6  //given data :
7  Vbb=20; // in V
8  C=100; //in micro-farad
9  R=100; //in kilo-ohms
10 Vp=10; // in V
11 eta=Vp/Vbb; // instrinsic stand off ratio
12 T= ((C*10^-12*R*10^3 *log(1/(1-eta))))*10^7; //in
    micro-seconds
13 format('v',6)
14 disp(T,"time period of the saw tooth waveform
    generated is ,(micro-seconds)=")

```

Scilab code Exa 10.3 resistance

```

1  //Example 10.3:
2  clc;
3  clear;
4  close;
5  //given data :
6  eta=0.6; // instrinsic stand off ratio
7  Rbb=10; // interbase resistance in k-ohm
8  Rb1=eta*Rbb;
9  Rb2=Rbb-Rb1;
10 format('v',4)
11 disp(Rb1," Resistance ,Rb1(k-ohm) = ")
12 disp(Rb2," Resistance ,Rb1(k-ohm) = ")

```
