

Scilab Textbook Companion for  
Solid State Electronics  
by J. P. Agrawal<sup>1</sup>

Created by  
Vijay Kant Kala  
B.Tech  
Electronics Engineering  
KIET  
College Teacher  
None  
Cross-Checked by  
Chaya Ravindra

October 22, 2014

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Solid State Electronics

**Author:** J. P. Agrawal

**Publisher:** Pragati Prakashan, Merrut

**Edition:** 1

**Year:** 2013

**ISBN:** 93-5006-947-4

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Introduction to solid state electronics	7
2 Special Purpose Diodes	21
3 Bi Polar Junction Transistor	23
4 Small signal amplifiers	32
5 Power Amplifiers	45
6 Field Effect Transistors	50
9 Silicon Controlled Rectifier	55
10 The Unijunction Transistor	58

# List of Scilab Codes

Exa 1.1	ne . . . . .	7
Exa 1.2	resistivity . . . . .	7
Exa 1.3	density . . . . .	8
Exa 1.4	density . . . . .	8
Exa 1.5	resistivity . . . . .	9
Exa 1.6	conductivity . . . . .	10
Exa 1.7	fremi level . . . . .	11
Exa 1.8	density . . . . .	11
Exa 1.9	current . . . . .	12
Exa 1.10	hole concentration and conductivity . . . . .	13
Exa 1.11	donor concentration . . . . .	13
Exa 1.12	resistivity . . . . .	14
Exa 1.13	current . . . . .	14
Exa 1.14	diode current and voltage . . . . .	15
Exa 1.15	voltage . . . . .	16
Exa 1.16	voltage . . . . .	16
Exa 1.17	resistance . . . . .	17
Exa 1.18	resistance . . . . .	17
Exa 1.19	resistance . . . . .	18
Exa 1.20	capacitance . . . . .	19
Exa 1.21	resistance . . . . .	19
Exa 2.1	maximum current . . . . .	21
Exa 2.2	resistance . . . . .	21
Exa 2.3	current . . . . .	22
Exa 3.1	varitation in alpha and value of beta . . . . .	23
Exa 3.2	current amplification factor . . . . .	23
Exa 3.3	base current . . . . .	24
Exa 3.4	short circuit current gain . . . . .	24

Exa 3.5	collector and base current . . . . .	25
Exa 3.6	$I_c$ $I_b$ and $I_{ce0}$ . . . . .	25
Exa 3.7	change in collector current . . . . .	26
Exa 3.8	emitter current . . . . .	26
Exa 3.9	beta . . . . .	27
Exa 3.10	error . . . . .	27
Exa 3.11	change in base current . . . . .	28
Exa 3.12	collector current base current and $\alpha$ . . . . .	28
Exa 3.13	ac current gain . . . . .	29
Exa 3.14	Beta $I_{ce0}$ and collector current . . . . .	29
Exa 3.15	collector current $\alpha$ and beta . . . . .	30
Exa 3.16	collector current . . . . .	31
Exa 4.1	voltage . . . . .	32
Exa 4.2	vce . . . . .	33
Exa 4.3	base resistance . . . . .	33
Exa 4.4	operating point . . . . .	34
Exa 4.5	resistor . . . . .	34
Exa 4.6	operating point . . . . .	35
Exa 4.7	operating point . . . . .	35
Exa 4.8	operating point . . . . .	36
Exa 4.9	maximum collector current . . . . .	36
Exa 4.10	maximum collector current . . . . .	37
Exa 4.11	gain . . . . .	37
Exa 4.12	output voltage . . . . .	38
Exa 4.13	gain and resistance . . . . .	39
Exa 4.14	gain and voltage . . . . .	39
Exa 4.15	voltage gain . . . . .	40
Exa 4.16	small change in gain . . . . .	41
Exa 4.17	input voltage . . . . .	41
Exa 4.18	percentage of feedback . . . . .	42
Exa 4.19	band width . . . . .	42
Exa 4.20	percentage reduction . . . . .	43
Exa 4.21	$A_v$ and beta . . . . .	43
Exa 5.1	efficiency . . . . .	45
Exa 5.2	collector current . . . . .	45
Exa 5.3	collector efficiency and power rating . . . . .	46
Exa 5.4	power . . . . .	46
Exa 5.5	power . . . . .	47

Exa 5.6	harmonic distortions and change in power . . . . .	47
Exa 5.7	power dissipated . . . . .	48
Exa 6.1	drain resistance transconductance and amplification factor . . . . .	50
Exa 6.2	mutual conductance . . . . .	51
Exa 6.3	pinch off voltage . . . . .	51
Exa 6.4	ID gm and gmo . . . . .	52
Exa 6.5	Vgs . . . . .	52
Exa 6.6	voltage amplification . . . . .	53
Exa 6.7	output voltage . . . . .	53
Exa 9.1	average voltage . . . . .	55
Exa 9.2	dc load current rms load current amd power dissipated . . . . .	55
Exa 9.3	firing angle conducting angle and average current . . . . .	56
Exa 10.1	stand off and peak point voltage . . . . .	58
Exa 10.2	time period . . . . .	58
Exa 10.3	resistance . . . . .	59

# Chapter 1

## Introduction to solid state electronics

Scilab code Exa 1.1 ne

```
1 //Example 1.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 ni=1.5*10^16; // in m^-3
7 nh=4.5*10^22; // in m^-3
8 ne=ni^2/nh;
9 format('e',8)
10 disp(ne," ne in the doped silicon is ,(m^-3) = ")
```

---

Scilab code Exa 1.2 resistivity

```
1 //Example 1.2:
2 clc;
3 clear;
```



```

4 close;
5 //given data :
6 ne=8*10^19; // in m^-3
7 nh=5*10^18; // in m^-3
8 mu_e=2.3; // in m^2/V-s
9 mu_h=.01; // in m^2/V-s
10 e=1.6*10^-19; // in V
11 p=1/(e*((ne*mu_e)+(nh*mu_h)));
12 format('e',8)
13 disp(p,"(b) the resistivity ,p(ohm-m)=")

```

---

#### Scilab code Exa 1.3 density

```

1 //Example 1.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 sigma=500; // in ohm^-1 m^-1
7 mu_e=.39; // m^2/V-s
8 e=1.6*10^-19; // in V
9 ne=sigma/(e*mu_e);
10 format('e',9)
11 disp(ne,"number density of donor ,ne(m^-3) = ")

```

---

#### Scilab code Exa 1.4 density

```

1 //Example 1.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10^-19; // in V

```

```

7 Pp=10^-2; // p-type silicon in ohm-m
8 Pn=10^-2; // n-type silicon in ohm-m
9 mu_p=0.048; // holes mobilities in m^2/V-s
10 mu_n=0.135; // electrons mobilities in m^2/V-s
11 Na=1/(e*mu_p*Pp);
12 Nd=1/(e*mu_n*Pn);
13 format('e',8)
14 disp(Na,"(i). the density of impurity,Na (m^-3) = ")
15 format('e',9)
16 disp(Nd,"(ii). the density of impurity,Nd (m^-3) = "
    )

```

---

#### Scilab code Exa 1.5 resistivity

```

1 //Example 1.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 e=1.6*10^-19; // in V
8 n=2.5*10^19; //m^3
9 p=n; //
10 ni=n; //
11 mu_p=0.17; // holes mobilities in m^2/V-s
12 mu_n=0.36; // electrons mobilities in m^2/V-s
13 sgint=e*(ni*(mu_p+mu_n)); //electrical conductivity
    in mho/metre
14 pint=1/sgint; //resistivity in ohm-meter
15 disp(sgint,"electrical conductivity is ,(mho/metre)="
    ")
16 disp(pint,"resistivity is ,(ohm-metre)=")

```

---

### Scilab code Exa 1.6 conductivity

```
1 //Example 1.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('e',9)
7 e=1.6*10^-19; // in V
8 ni=1.5*10^16; //in m^3
9 mu_p=0.13; // holes mobilities in m^2/V-s
10 mu_n=0.05; // electrons mobilities in m^2/V-s
11 sgint=e*(ni*(mu_p+mu_n)); //electrical conductivity
    in mho/m
12 siat=10^8; //number of silicon atoms
13 ta=5*10^28; //silicon atoms in atoms/m^3
14 Nd=ta/siat; // in atoms/m^3
15 p= ni^2/Nd; //holes concentration in holes/m^3
16 n=Nd; //
17 mu_n=0.13; // electrons mobilities in m^2/V-s
18 sntype=e*n*mu_n; // in mho/m
19 disp(sgint,"(i) electrical conductivity is ,(mhos/m)
    =")
20 format('e',8)
21 disp(p,"(ii) holes concentration is , (holes/m^3)=")
22 format('v',5)
23 disp(sntype,"(ii) conductivity is ,(mho/m)=")
24 siat=10^8; //number of silicon atoms
25 ta=5*10^28; //silicon atoms in atoms/m^3
26 Na=ta/siat; // in atoms/m^3
27 n= ni^2/Na; //holes concentration in holes/m^3
28 p=Na; //
29 mu_p=0.05; //holes mobilities in m^2/V-s
30 sptype=e*p*mu_p; // in mho/m
31 format('e',8)
32 disp(n,"(iii) electron concentration is , (holes/m^3)
    =")
33 format('v',3)
```

34 `disp(sptype, "(iii) conductivity is , (mho/m)=")`

---

#### Scilab code Exa 1.7 fremi level

```
1 //Example 1.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 //Nd1=Nc*exp-(Ec-Ef1)/kT ... Formula Used
8 Nc=1; //assume
9 kT=0.03; //eV
10 EcEf1=0.5; //position of Fermi level in V
11 Nd=1; //assume
12 Nd1=3*Nd; //After tripling the donor concentration
13 EcEf2=(EcEf1-(kT*(log(Nd1/Nd)))); //in eV
14 disp(EcEf2, "new position of Fermi-level is ,(eV)=")
```

---

#### Scilab code Exa 1.8 density

```
1 //Example 1.8:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10-19; // in V
7 Pp=10-1; // p-type silicon in ohm-m
8 Pn=10-1; // n-type silicon in ohm-m
9 mu_h=0.05; // holes mobilities in m2/V-s
10 mu_e=0.13; // electrons mobilities in m2/V-s
11 Na=1/(e*mu_h*Pp);
12 Nd=1/(e*mu_e*Pn);
```

```

13 format('e',9)
14 disp(Na,"(i). the density of impurity ,Na (m-3) = ")
15 format('e',8)
16 disp(Nd,"(ii). the density of impurity ,Nd (m-3) = "
    )

```

---

### Scilab code Exa 1.9 current

```

1 //Example 1.9:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10-19; // in V
7 Pp=10-1; // p-type silicon in ohm-m
8 Pn=10-1; // n-type silicon in ohm-m
9 mu_hsi=0.048; // holes mobilities in m2/V-s
10 mu_esi=0.135; // electrons mobilities in m2/V-s
11 nisi=1.5*1016; //in m-3
12 nesi=nisi; //
13 nhsi=nisi; //
14 mu_hge=0.19; // holes mobilities in m2/V-s
15 mu_ege=0.39; // electrons mobilities in m2/V-s
16 A=1*10-4; //area in m2
17 nige=2.4*1019; //in m-3
18 V=2; //in V
19 l=0.1; //in m
20 Isi= e*A*(V/l)*((nesi*mu_esi)+(nhsi*mu_hsi)); //in A
21 format('e',8)
22 disp(Isi,"Total current for silicon is ,(A)=")
23 //Current for silicon is calculated wrong in the
    textbook
24 nege=nige; //
25 nhge=nige; //
26 Ige= e*A*(V/l)*((nege*mu_ege)+(nhge*mu_hge)); //in A

```

```
27 format('e',9)
28 disp(Ige,"Total current for germanium is ,(A)=")
```

---

#### Scilab code Exa 1.10 hole concentration and conductivity

```
1 //Example 1.10:
2 clc;
3 clear;
4 close;
5 //given data :
6 nh=2*10^21;// acceptor atoms in atoms/m^3
7 Na=nh;
8 format('e',8)
9 disp(Na,"(i). hole concentration ,Na(atoms/m^3) = ")
10 mu_h=0.17;// mobility of holes in m^2/V-s
11 e=1.6*10^-19;// in C
12 sigma=nh*mu_h*e;
13 format('v',6)
14 disp(sigma,"conductivity ,(ohm^-1-m^-1) = ")
15 //conductivity is calculated wrong in the book
```

---

#### Scilab code Exa 1.11 donor concentration

```
1 //Example 1.11:
2 clc;
3 clear;
4 close;
5 //given data :
6 p=0.15;// in ohm-m
7 mu_e=0.39;// mobility of electron in m^2/V-s
8 e=1.6*10^-19;// in C
9 Na=1/(e*mu_e*p);
10 format('e',9)
```

```
11 disp(Na,"The value of donor concentration ,Na(m-3) =  
    ")
```

---

#### Scilab code Exa 1.12 resistivity

```
1 //Example 1.12:  
2 clc;  
3 clear;  
4 close;  
5 //given data :  
6 mu_n=0.13; // in m2/V-s  
7 mu_p=0.05; // in m2/V-s  
8 ni=1.5*1016; // in m-3  
9 e=1.6*10-19; // in C  
10 p=1/((e*ni)*(mu_n+mu_p));  
11 format('v',7)  
12 disp(p,"The resistivity ,p(ohm-m) = ")
```

---

#### Scilab code Exa 1.13 current

```
1 //Example 1.13:  
2 clc;  
3 clear;  
4 close;  
5 //given data :  
6 e=1.6*10-19; // electron charge in coulombs  
7 k=1.38*10-23; //Boltzmann constant in m2-kg/s2-K  
    ^-1  
8 T=300; //in Kelvin  
9 Vt=(k*T)/e; //in V  
10 I=240; //in mA  
11 eta=2; //  
12 Ve=0.8; //in V
```

```

13 V=0.7; //in V
14 Id=I*exp((V-Ve)/(eta*Vt)); //in mA
15 format('v',5)
16 disp(round(Id),"(i) Current is ,(mA)=")
17 Ir=(I/((exp(Ve/(eta*Vt)))-1))*10^6; //
18 format('v',4)
19 disp(round(Ir),"(ii) reverse saturation current is
    ,(nA)=")
20 //reverse saturation current is calculated wrong in
    the textbook

```

---

#### Scilab code Exa 1.14 diode current and voltage

```

1 //Example 1.14:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10^-19; // electron charge in coulombs
7 k=1.38*10^-23; //Boltzmann constant in m^2-kg/s^2-K
    ^-1
8 T=300; //in Kelvin
9 Vt=(k*T)/e; //in V
10 Ir1=10^-10; //in A
11 Ir2=10^-12; //in A
12 V21=((Vt)*log10(Ir1/Ir2))*2.3026; //in V
13 V211=0.5; //in V
14 V2=(1/2)*(V21+V211); //in V
15 V1=(1/2)*(V211-V21); //in V
16 I1=Ir2*exp(V2/Vt)*10^6; //in micro-A
17 I2=I1; //
18 format('v',8)
19 disp(V2,"diode voltage V2 is ,(V)=")
20 disp(V1,"diode voltage V1 is ,(V)=")
21 format('v',7)

```



```
22 disp(I1,"diode current is ,(micro-A)=")
23 //diode current is calculated wrong in the textbook
```

---

#### Scilab code Exa 1.15 voltage

```
1 //Example 1.15:
2 clc;
3 clear;
4 close;
5 //given data :
6 e=1.6*10^-19;// electron charge in coulombs
7 k=1.38*10^-23;//Boltzmann constant in m^2-kg/s^2-K
   ^-1
8 T=300;//in Kelvin
9 Vt=(k*T)/e;//in V
10 Ir1=10^-12;//in A
11 Ir2=10^-10;//in A
12 I21=Ir2/Ir1;//
13 It=2;//mA
14 I1=It/(1+I21)*10^3;//in micro-A
15 I2=It*10^3-I1;//in micro-A
16 I1=I2/I21;//in micro-A
17 x=((I1*10^-6)/Ir1);//
18 V=Vt*log10(x)*2.3026;//in V
19 format('v',6)
20 disp(V,"diode voltage is ,(V)=")
```

---

#### Scilab code Exa 1.16 voltage

```
1 //Example 1.16:
2 clc;
3 clear;
4 close;
```

```

5 //given data :
6 format('v',5)
7 T=27; //degree Celsius
8 Tk=273+T; //in Kelvin
9 e=1.6*10^-19; // electron charge in coulombs
10 k=1.38*10^-23; //Boltzmann constant in m^2-kg/s^2-K
    ^-1
11 J=10^4; //in Amp/m^2
12 Jo=200; //in mA/m^2
13 x=(J/(Jo*10^-3)); //
14 Ve=((log(x))*k*Tk)/e; //in V
15 disp(Ve," voltage to be applied is ,(V)=")

```

---

#### Scilab code Exa 1.17 resistance

```

1 //Example 1.17:
2 clc;
3 clear;
4 close;
5 format('v',5)
6 V=3; //in V
7 I=55; //in mA
8 Rdc=V/(I*10^-3); //in ohm
9 V2=26; //in mV
10 Rac=V2/I; //in ohm
11 disp(Rdc," static resistance is ,(ohm)=")
12 disp(Rac," dynamic resistance is ,(ohm)=")

```

---

#### Scilab code Exa 1.18 resistance

```

1 //Example 1.18:
2 clc;
3 clear;

```

```

4 close;
5 //given data :
6 format('v',5)
7 k=1.38*10^-23; // constant
8 T=27+273; // in K
9 eta=2;
10 e=1.6*10^-19; // in C
11 Vt=(k*T/e); // in V
12 V=0.5; // in V
13 Ir=10^-6; // in A
14 I=(Ir*10^3*(exp(V/(eta*Vt))-1)); // in A
15 R_dc=V*10^3/I;
16 disp(R_dc,"static resistance ,R_dc(ohm) = ")
17 R_ac=(eta*k*T)/(e*I*10^-3);
18 format('v',5)
19 disp(R_ac,"Dynamic resistance ,R_ac(ohm) = ")
20 // answer is wrong in textbook

```

---

#### Scilab code Exa 1.19 resistance

```

1 //Example 1.19:
2 clc;
3 clear;
4 close;
5 //given data :
6 V=1.2; // in V
7 Vk=0.7; // in V
8 I_F=100; // in mA
9 R_B=(V-Vk)/(I_F*10^-3);
10 V_R=10; // in V
11 I_R=1; // in micro-A
12 R_R=V_R/I_R;
13 format('v',3)
14 disp(R_B,"the bulk resistance ,R_B(ohm) = ")
15 disp(R_R,"the reverse resistance ,R_R(M-ohm) = ")

```

```

16 eta=2;
17 I=5; // in mA
18 R_ac=eta*26/I;
19 format('v',5)
20 disp(R_ac,"ac resistance ,R_ac(ohm) = ")

```

---

#### Scilab code Exa 1.20 capacitance

```

1 //Example 1.20:
2 clc;
3 clear;
4 close;
5 //given data :
6 epsilon_0=8.85*10^-12; // in farada/m
7 K=12; // constant for silicon
8 epsilon=epsilon_0*K
9 A=1*10^-8; // in m^2
10 W=5*10^-7; // in m
11 Ct=epsilon*A*10^14/W;
12 format('v',6)
13 disp(Ct,"the transition capacitance ,Ct(PF) = ")

```

---

#### Scilab code Exa 1.21 resistance

```

1 //Example 1.21:
2 clc;
3 clear;
4 close;
5 //given data :
6 V=0.2; // in V
7 I=1; // in micro-A
8 R_dc=V*10^3/I;
9 R_ac=26/(I*10^3);

```

```
10 format('v',5)
11 disp(R_dc,"The static resistance ,R_ac(k-ohm) = ")
12 format('v',6)
13 disp(R_ac,"the dynamic resistance ,R_ac(ohm) = ")
```

---

## Chapter 2

# Special Purpose Diodes

Scilab code Exa 2.1 maximum current

```
1 //Example 2.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Pmax=364; //dissipation in milliwatt
7 Vz=9.1; //in V
8 Izmax=Pmax/Vz; //in mA
9 format('v',4)
10 disp(Izmax,"maximum current the diode can handle is
    ,(mA)=")
```

---

Scilab code Exa 2.2 resistance

```
1 //Example 2.2:
2 clc;
3 clear;
4 close;
```

```

5 //given data :
6 mip=15; //in volt
7 op=6.8; //output potential in volt
8 pd=mip-op; //potential difference across series
  resistor
9 I1=5; //load current in mA
10 nmip=20; //new maximum input voltage in volt
11 pd1=nmip-op; //new potential difference across series
  resistor
12 I11=20; //new load current in mA
13 R=((pd1-pd)/((I11-I1)*10^-3)); //resistance in ohm
14 format('v',6)
15 disp(R,"value of series resistance is ,(ohm)=")

```

---

### Scilab code Exa 2.3 current

```

1 //Example 2.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 V=120; //in V
7 Vz=50; //in V
8 vd5=V-Vz; //voltage drop across 5 ohm resistor
9 R=5; // in ohm
10 I5=vd5/R; //current through 5 ohm resistor
11 R1=10; // in k-ohm
12 I1=Vz/(R1*10^3); //current through load resistor
13 Iz=I5-I1; //in A
14 format('v',7)
15 disp(Iz,"current through zener diode is ,(A)=")

```

---

## Chapter 3

# Bi Polar Junction Transistor

Scilab code Exa 3.1 variation in alpha and value of beta

```
1 //Example 3.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Beta=50; //amplification factor
7 dbb=1; //percentage variation in degree celsius
8 daa=dbb/50; //variation in degree celsius
9 format('v',5)
10 disp(daa,"(i) variation in alpha for a silicon BJT
      is ,(%/degree-Celsius)=")
11 temp=325; //in K
12 t=25; //degree celsius
13 Beta1=dbb*t; //in %
14 nBeta=Beta+(Beta1/100)*t; //
15 format('v',6)
16 disp(nBeta,"new value of Beta is ,=")
```

---

Scilab code Exa 3.2 current amplification factor



```

1 //Example 3.2:
2 clc;
3 clear;
4 close;
5 format('v',4)
6 //given data :
7 del_Ic=1*10^-3;// in A
8 del_Ib=50*10^-6;// in A
9 Beta=del_Ic/del_Ib;
10 disp(Beta,"The current amplification factor ,Beta = "
      )

```

---

**Scilab code Exa 3.3** base current

```

1 //Example 3.3:
2 clc;
3 clear;
4 close;
5 format('v',5)
6 //given data :
7 alfa=0.88;
8 Ie=1;// in mA
9 Ic=alfa*Ie;// in mA
10 I_B=Ie-Ic;
11 disp(I_B,"Base current ,(mA) = ")

```

---

**Scilab code Exa 3.4** short circuit current gain

```

1 //Example 3.4:
2 clc;
3 clear;
4 close;
5 format('v',5)

```

```

6 //given data :
7 del_Ic=0.95*10^-3; // in A
8 del_Ie=1*10^-3; // in A
9 alfa=del_Ic/del_Ie;
10 disp(alfa,"the short circuit current gain, = ")

```

---

### Scilab code Exa 3.5 collector and base current

```

1 //Example 3.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 Ie=5*10^-3; // in A
8 alfa=0.95;
9 I_co=10*10^-6; // in A
10 Ic=((alfa*Ie)+I_co)*10^3;
11 Ib=(Ie-(Ic*10^-3))*10^6;
12 disp(Ic,"Collector current ,(mA) = ")
13 disp(Ib,"Base current ,(micro-A) = ")

```

---

### Scilab code Exa 3.6 Ic Ib and Ico

```

1 //Example 3.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ie=5; // in mA
7 alfa=0.99;
8 I_co=0.005; // in mA
9 Ic=((alfa*Ie)+I_co);

```

```

10 Ib=(Ie-Ic);
11 Beta=alfa/(1-alfa);
12 I_CEO=I_co/(1-alfa);
13 format('v',6)
14 disp(Ic,"Ic ,(mA) = ")
15 format('v',4)
16 disp(Ib*10^3,"Ib ,(micro-A) = ")
17 disp(Beta,"Beta = ")
18 format('v',6)
19 disp(I_CEO*10^3,"I_CEO(micro-A) = ")

```

---

**Scilab code Exa 3.7** change in collector current

```

1 //Example 3.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 alfa=0.9;// constant
7 Beta=alfa/(1-alfa);
8 Del_Ib=4;// in mA
9 Del_Ic=Beta*Del_Ib;
10 format('v',4)
11 disp(Del_Ic,"the change in the collector current ,(mA
    ) = ")

```

---

**Scilab code Exa 3.8** emitter current

```

1 //Example 3.8:
2 clc;
3 clear;
4 close;
5 //given data :

```

```
6 Beta=40;
7 Ib=25; // base current in micro-A
8 Ic=Beta*Ib;
9 Ie=(Ib+Ic)*10^-3;
10 format('v',6)
11 disp(Ie,"Ie ,(mA) = ")
```

---

### Scilab code Exa 3.9 beta

```
1 //Example 3.9:
2 clc;
3 clear;
4 close;
5 //given data :
6 alfa=0.98; // constant
7 Beta=alfa/(1-alfa);
8 format('v',4)
9 disp(Beta,"Beta = ")
```

---

### Scilab code Exa 3.10 error

```
1 //Example 3.10:
2 clc;
3 clear;
4 close;
5 //given data :
6 Beta=100; // constant
7 Ib=20*10^-6; // in A
8 I_co=500*10^-9; // in A
9 Ic1=((Beta*Ib)+(1+Beta)*I_co)*10^3;
10 Ic2=(Beta*Ib)*10^3;
11 Error=(Ic1-Ic2)*100/Ic1;
12 format('v',5)
```

```
13 disp(Error,"The error ,(%) = ")
14 //answer is wrong in the txtbook
```

---

**Scilab code Exa 3.11** change in base current

```
1 //Example 3.11:
2 clc;
3 clear;
4 close;
5 //given data :
6 alfa=0.98; //
7 del_Ie=5; // in mA
8 del_Ic=alfa*del_Ie; // in mA
9 del_Ib=del_Ie-del_Ic;
10 format('v',4)
11 disp(del_Ib,"change in base current ,(mA) = ")
```

---

**Scilab code Exa 3.12** collector current base current and alfa

```
1 //Example 3.12:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ie=8.4; // in mA
7 cr=0.8/100; // carriers recombine in base in %
8 Ib=cr*Ie;
9 format('v',6)
10 disp(Ib,"(a). The base current ,Ib(mA) = ")
11 Ic=Ie-Ib;
12 format('v',5)
13 disp(Ic,"(b). The collector current ,Ic(mA) = ")
14 alfa=Ic/Ie;
```

```
15 format('v',6)
16 disp(alfa,"(c). the value of alfa = ")
```

---

### Scilab code Exa 3.13 ac current gain

```
1 //Example 3.13:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ie1=20; // in mA
7 Ie2=15; // in mA
8 Ib1=0.48; // in mA
9 Ib2=0.32; // in mA
10 del_Ie=(Ie1-Ie2)*10^-3; // in A
11 del_Ib=(Ib1-Ib2)*10^-3; // in A
12 del_Ic=del_Ie-del_Ib; // in A
13 alfa=del_Ic/del_Ie; //
14 Beta=del_Ic/del_Ib;
15 format('v',5)
16 disp(alfa,"ac current gain in common base
    arrangement, = ")
17 format('v',4)
18 disp(Beta,"ac current gain in common emitter
    arrangement, = ")
```

---

### Scilab code Exa 3.14 Beta I<sub>ceo</sub> and collector current

```
1 //Example 3.14:
2 clc;
3 clear;
4 close;
5 //given data :
```

```

6  alfa=0.992; // constant
7  Beta=alfa/(1-alfa);
8  format('v',5)
9  disp(Beta,"(a) Beta= ")
10 I_CB0=48*10^-9; // in A
11 I_CEO=(1+Beta)*I_CB0*10^6;
12 format('v',3)
13 disp(I_CEO,"(a) I_CEO (micro-A) = ")
14 Ib=30*10^-6; // in A
15 Ic=((Beta*Ib)+(1+Beta)*I_CB0)*10^3;
16 format('v',5)
17 disp(Ic,"(b) Collector current ,Ic(mA) = ")

```

---

**Scilab code Exa 3.15** collector current alfa and beta

```

1  //Example 3.15:
2  clc;
3  clear;
4  close;
5  //given data :
6  format('v',5)
7  Ie=9.6; //emitter current in mA
8  Ib=0.08; //base current in mA
9  Ic=Ie-Ib; //
10 format('v',5)
11 disp(Ic,"(a). collector current ,Ic(mA) = ")
12 alfa=Ic/Ie;
13 format('v',5)
14 disp(alfa,"(b). alfa = ")
15 alfa=0.99; //
16 Beta=alfa/(1-alfa)
17 format('v',4)
18 disp(Beta,"(c). Beta = ")

```

---

**Scilab code Exa 3.16** collector current

```
1 //Example 3.16:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ib=68*10^-6; // in A
7 Ie=30*10^-3; // in A
8 Beta=440; // constant
9 alfa=Beta/(1+Beta);
10 Ic=alfa*Ie*10^3;
11 format('v',6)
12 disp(Ic," Collector current ,Ic (mA) = ")
```

---



# Chapter 4

## Small signal amplifiers

Scilab code Exa 4.1 voltage

```
1 //Example 4.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 Rc=4.7; // in ohm
8 Vcc=24; // in V
9 Ic=1.5; //in mA
10 //this is given as 15 mA in textbook which is wrong
11 Vce=Vcc-(Ic*Rc*10^-3*10^3); //in V
12 disp(Vce,"(i) Collector to emitter voltage ,Vce(V) =
    ")
13 Ic1=0; //in A
14 Vce1=Vcc-Ic1*Rc; //in V
15 format('v',4)
16 disp(Vce1,"(ii) Collector to emitter voltage ,Vce(V)
    = ")
```

---

### Scilab code Exa 4.2 vce

```
1 //Example 4.2:
2 clc;
3 clear;
4 close;
5 //given data :
6 Beta=100;
7 Rb=200*10^3; // in ohm
8 Rc=1*10^3; // in ohm
9 Vcc=10; // in V
10 Ib=Vcc/Rb; // in A
11 Ic=Beta*Ib; //in A
12 Vce=Vcc-(Ic*Rc);
13 format('v',4)
14 disp(Vce," Collector to emitter voltage ,Vce(V) = ")
```

---

### Scilab code Exa 4.3 base resistance

```
1 //Example 4.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 Vcc=20; // in V
8 Vbe=0.7; // in V
9 Rc=2; //in kilo-ohm
10 Icsat= Vcc/Rc; //in mA
11 Beta=200; //
12 Ib=(Icsat/Beta)*10^3; //in micro-A
13 Rb=((Vcc-Vbe)/(Ib))*10^3; //in kilo-ohm
14 disp("Rb < "+string(Rb)+" kilo-ohm")
```

---

#### Scilab code Exa 4.4 operating point

```
1 //Example 4.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=15; // in V
7 Rb=200; // in k-ohm
8 Rc=2; // in k-ohm
9 Beta=50;
10 Ib=(Vcc/(Rb*10^3+(Beta*Rc*10^3)))*10^6; //in micro-A
11 Ic=Beta*Ib*10^-3; //in mA
12 Vce=Vcc-(Ic*10^-3*(Rc*10^3));
13 format('v',4)
14 disp(Ic," collector current ,Ic(mA) = ")
15 disp(Vce," Collector to emitter voltage ,Vce(V) = ")
```

---

#### Scilab code Exa 4.5 resistor

```
1 //Example 4.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=15; // in V
7 Vce=6; // in V
8 Rc=3*10^3; // in ohm
9 Beta=50;
10 Ic=(Vcc-Vce)/Rc;
11 Ib=Ic/Beta;
12 Rb=((Vcc/Ib)-(Beta*Rc))*10^-3;
```

```
13 format('v',5)
14 disp(Rb,"The value of resistoe ,Rb(k-ohm) = ")
```

---

#### Scilab code Exa 4.6 operating point

```
1 //Example 4.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=12; // in V
7 Rb1=70; // in k-ohm
8 Rb2=70; // in k-ohm
9 Beta=50;
10 Rc=2; // in k-ohm
11 Ib=Vcc/((Rb1+Rb2+(Beta*Rc))*10^3);
12 Ic=Beta*Ib*10^3;
13 Vce=Vcc-(Ic*Rc);
14 format('v',4)
15 disp(Ic," collector current ,Ic(mA) = ")
16 disp(Vce," Collector to emitter voltage ,Vce(V) = ")
```

---

#### Scilab code Exa 4.7 operating point

```
1 //Example 4.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=9; // in V
7 Rb=50; // in k-ohm
8 Rc=250; // in ohm
9 Re=500; // in ohm
```

```

10 Beta=80;
11 Ib=Vcc/(Rb*10^3+(Beta*Re));
12 Ic=Beta*Ib*10^3;
13 Vce=Vcc-(Ic*10^-3*(Rc+Re));
14 format('v',3)
15 disp(Ic," collector current ,Ic(mA) = ")
16 disp(Vce," Collector to emitter voltage ,Vce(V) = ")

```

---

#### Scilab code Exa 4.8 operating point

```

1 //Example 4.8:
2 clc;
3 clear;
4 close;
5 //given data :
6 R2=4; // in k-ohm
7 R1=40; // in k-ohm
8 Vcc=22; // in V
9 Rc=10; // in k-ohm
10 Re=1.5; // in k-ohm
11 Vbe=0.5; // in V
12 Voc=R2*10^3*Vcc/((R1+R2)*10^3);
13 Ic=(Voc-Vbe)/(Re*10^3);
14 Vce=Vcc-(Rc+Re)*Ic*10^3;
15 format('v',5)
16 disp(Vce," Collector to emitter voltage ,Vce(V) = ")

```

---

#### Scilab code Exa 4.9 maximum collector current

```

1 //Example 4.9:
2 clc;
3 clear;
4 close;

```

```

5 //given data :
6 Bv=12;//battery voltage in V
7 Cl=6;//collector load in k-ohm
8 CC=Bv/Cl;
9 format('v',4)
10 disp(CC,"Collector current ,(mA) = ")

```

---

**Scilab code Exa 4.10** maximum collector current

```

1 //Example 4.10:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',6)
7 Bv=12;//battery voltage in V
8 P=2;// power in Watt
9 Ic=(P/Bv)*10^3;
10 disp(Ic,"The maximum collector current ,Ic(mA) = ")

```

---

**Scilab code Exa 4.11** gain

```

1 //Example 4.11:
2 clc;
3 clear;
4 close;
5 //given data :
6 del_ic=1;// in mA
7 del_ib=10;// in micro-A
8 del_Vbe=0.02;// in V
9 del_ib=10*10^-6;// in A
10 Rc=2;// in k-ohm
11 Rl=10;// in k-ohm

```

```

12 Beta=del_ic/(del_ib*10^3);//
13 format('v',5)
14 disp(Beta," Current gain ,Beta = ")
15 Ri=(del_Vbe/del_ib)*10^-3;
16 format('v',4)
17 disp(Ri," Input impedance ,Ri(k-ohm) = ")
18 Rac=Rc*Rl/(Rc+Rl);
19 format('v',5)
20 disp(Rac," Effective load ,Rac(k-ohm) = ")
21 Av=round(Beta*Rac/Ri);
22 format('v',4)
23 disp(Av," Voltage gain ,Av = ")
24 Ap=Beta*Av;
25 format('v',6)
26 disp(Ap," power gain ,Ap = ")

```

---

Scilab code Exa 4.12 output voltage

```

1 //Example 4.12:
2 clc;
3 clear;
4 close;
5 //given data :
6 Rc=10; // in k-ohm
7 Rl=10; // in k-ohm
8 Beta=100;
9 Ri=2.5;
10 Iv=2; // input voltage in mV
11 Rac=Rc*Rl/(Rc+Rl);
12 Av=round(Beta*Rac/Ri);
13 Ov=Av*Iv*10^-3;
14 format('v',4)
15 disp(Ov," Output voltage ,(V) = ")

```

---

### Scilab code Exa 4.13 gain and resistance

```
1 //Example 4.13:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 I=1;
8 hfe=46;
9 hoe=80*10^-6; // in mho
10 hre=5.4*10^-4;
11 hie=800; // in ohm
12 RL=5*10^3; // in ohm
13 Aie=hfe/(I+(hoe*RL));
14 Zie=hie-(hre*RL*Aie);
15 Ave=(Aie*RL)/Zie;
16 Rg=500; // in ohm
17 Zoe=((hie+Rg)/(hoe*(hie+Rg)-(hfe*hre)))/10^3;
18 Ape=Aie*Ave;
19 disp(Aie,"Current gain ,Aie = ")
20 format('v',6)
21 disp(Zie,"Input resistance ,Zie(ohm) = ")
22 disp(Ave,"Voltage gain ,Ave = ")
23 format('v',5)
24 disp(Zoe,"Output resistance ,Zoe(k-ohm) = ")
25 format('v',7)
26 disp(Ape,"Power gain ,Ape = ")
27 //voltage gain and power gain are calculated wrong
    in the textbook
```

---

### Scilab code Exa 4.14 gain and voltage



```

1 //Example 4.14:
2 clc;
3 clear;
4 close;
5 //given data :
6 A=100; //gain without feedback
7 Beta=1/25; //feed back ratio
8 Af=(A/(1+(Beta*A))); //gain with feedback
9 disp(Af,"(i) gain with feedback is ,=")
10 ff=Beta*A; //feedback factor
11 disp(ff,"feedback factor is ,=")
12 vi=50; //mV
13 Vo=Af*vi*10^-3; //in V
14 disp(Vo,"output voltage is ,(V)=")
15 fv=Beta*Vo; //in V
16 format('v',5)
17 disp(fv,"feedback voltage is ,(V)=")
18 vin=vi*(1+Beta*A); //mV
19 disp(vin,"new increased input voltage is ,(mV)=")

```

---

#### Scilab code Exa 4.15 voltage gain

```

1 //Example 4.15:
2 clc;
3 clear;
4 close;
5 //given data :
6 A=1000; //gain without feedback
7 fctr=0.40; //gain reduction factor
8 Af=A-fctr*A; //gain with feedback
9 Beta=((A/Af)-1)/A; //feed back ratio
10 A2=800 ; //reduced gain
11 Af2=((A2)/(1+(Beta*A2))); //
12 format('v',6)
13 disp(Af2,"(i) voltage gain is ,=")

```

```

14 prfb= ((A-A2)/A)*100; //percentage reduction without
    feedback
15 format('v',4)
16 disp(prfb,"(ii) percentage reduction without
    feedback is ,(%)=")
17 prwfb= ((Af-Af2)/Af)*100; //percentage reduction
    without feedback
18 format('v',6)
19 disp(prwfb,"percentage reduction with feedback is ,(%)
    )=")

```

---

#### Scilab code Exa 4.16 small change in gain

```

1 //Example 4.16:
2 clc;
3 clear;
4 close;
5 //given data :
6 A=200; //gain without feedback
7 Beta=0.25; //feed back ratio
8 gc=10; //percent gain change
9 dA=gc/100; //
10 dAf= ((1/(1+Beta*A)))*dA; //
11 format('v',7)
12 disp(dAf,"small change in gain is,=")

```

---

#### Scilab code Exa 4.17 input voltage

```

1 //Example 4.17:
2 clc;
3 clear;
4 close;
5 //given data :

```

```

6  format('v',5)
7  A=200; //gain without feedback
8  Beta=0.05; //feed back ratio
9  Af=(A/(1+(Beta*A))); //gain with feedback
10 disp(Af," gain with negative feedback is ,=")
11 Dn=10; //percentage distortion
12 format('v',6)
13 Dn1=(Dn/(1+A*Beta)); //percentage Distortion with
    negative feedback
14 ff=Beta*A; //feedback factor
15 vo=0.5; //initial output voltage
16 vi=A*vo; //in V
17 vin=vi/Af; //in V
18 disp(Dn1," percentage Distortion with negative
    feedback is ,(%)=")
19 disp(vin,"new input voltage is ,(V)=")
20 //gain and input voltage are calculated wrong in the
    textbook

```

---

**Scilab code Exa 4.18** percentage of feedback

```

1  //Example 4.18:
2  clc;
3  clear;
4  close;
5  //given data :
6  format('v',5)
7  A=50; //gain without feedback
8  Af=10; //gain with feedback
9  Beta=((A/Af)-1)/A*100; //feed back ratio
10 disp(Beta," percentage of feedback is ,(%)=")

```

---

**Scilab code Exa 4.19** band width

```

1 //Example 4.19:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 Bw=200; //bandwidth in kHz
8 vg=40; //dB
9 fb=5; //percentage negative feedback
10 A=40; //gain without feedback
11 Beta=fb/100; //feed back ratio
12 Af=(A/(1+(Beta*A))); //gain with feedback
13 Bwf= (A*Bw)/Af; //Bandwidth with feedback
14 disp(Bwf," new band-width is ,(kHz)=")

```

---

Scilab code Exa 4.20 percentage reduction

```

1 //Example 4.20:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 A=50; //gain without feedback
8 Af=25; //gain with feedback
9 Beta=((A/Af)-1)/A; //feed back ratio
10 Ad=40; //new gain after ageing
11 Af1=(Ad/(1+(Beta*Ad))); //new gain with feedback
12 df=Af-Af1; // reduction in gain
13 pdf= (df/Af)*100; //percentage reduction in gain
14 disp(pdf," percentage reduction in gain is ,(%)=")

```

---

Scilab code Exa 4.21 Av and beta

```
1 //Example 4.21:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',5)
7 Af=100;//gain with feedback
8 vi=50;//in mV
9 vi1=60;//in mV
10 AAf=vi1/vi;//
11 A=AAf*Af;//
12 Beta=((A/Af)-1)/A;//feed back ratio
13 disp(A,"Av is ,=")
14 format('v',8)
15 disp(Beta," feedback factor is ,=")
```

---

# Chapter 5

## Power Amplifiers

Scilab code Exa 5.1 efficiency

```
1 //Example 5.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Pac=0.1; //in W
7 Vcc=20; //in V
8 Ic=20; //in mA
9 Pdc=Vcc*Ic*10^-3; //in W
10 eta=(Pac/Pdc)*100; //efficiency
11 format('v',4)
12 disp(eta," efficiency is ,(%)=")
```

---

Scilab code Exa 5.2 collector current

```
1 //Example 5.2:
2 clc;
3 clear;
```

```

4 close;
5 //given data :
6 Pac=2;//in W
7 Vcc=12;//in V
8 Ic=(Pac*sqrt(2)*sqrt(2))/Vcc;//in A
9 format('v',5)
10 disp(Ic,"maximum collector current is ,(A)=")

```

---

**Scilab code Exa 5.3** collector efficiency and power rating

```

1 //Example 5.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 Pac=3;//in W
7 Pdc=10;//in W
8 eta=(Pac/Pdc)*100;//percentage efficiency
9 format('v',4)
10 disp(eta,"collector efficiency is ,(%)=")
11 disp(Pdc,"power rating of transistor is ,(W)=")

```

---

**Scilab code Exa 5.4** power

```

1 //Example 5.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 dIc=100;//in mA
7 Rl=6;//in ohm
8 mv=dIc*Rl*10^-3;//in V
9 pd=mv*dIc;//in mW

```

```

10 disp(pd,"(i) power developed in loudspeaker is ,(mW)
    =")
11 dVc=10; //in V
12 oi=(dVc/dIc)*10^3; //in ohm
13 Rl=6; //in ohm
14 n=sqrt(oi/Rl); //turn ratio of transformer
15 tsv=dVc/n; //om V
16 Il=tsv/Rl; //in A
17 ptr= Il^2*Rl*10^3; //in mW
18 format('v',5)
19 disp(ptr,"(ii) power transferred to loudspeaker is
    ,(mw)=")
20 //in textbook in second case there is one point
    deviation in the answer.

```

---

#### Scilab code Exa 5.5 power

```

1 //Example 5.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 n=10; //turn ratio
7 Rl=10; //ohm
8 Rld=n^2*Rl; //in ohm
9 Ic=100; //in mA
10 Irms=Ic/(sqrt(2)); //in mA
11 P=Irms^2*Rld; //in W
12 format('v',3)
13 disp(P*10^-6,"maximum power output is ,(W)=")

```

---

#### Scilab code Exa 5.6 harmonic distortions and change in power



```

1 //Example 5.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 //ie=15*sin 400*t+1.5*sin 800*t + 1.2*sin 1200*t +
   0.5*sin 1600*t given equation
7 I2=1.5; //in A
8 I1=15; //in A
9 I3=1.2; //in A
10 I4=0.5; //in A
11 D2=(I2/I1)*100; //Second percentage harmonic
   distortion
12 D3=(I3/I1)*100; //Third percentage harmonic
   distortion
13 //in book I2 is mentioned wrongly in place of I1
14 D4=(I4/I1)*100; //Fourth percentage harmonic
   distortion
15 disp(" part (i)")
16 disp(D2,"Second percentage harmonic distortion (D2)
   is ,(%)=")
17 disp(D3,"Third percentage harmonic distortion (D3)
   is ,(%)=")
18 format('v',5)
19 disp(D4,"Fourth percentage harmonic distortion (D4)
   is ,(%)=")
20 disp(" part (ii)")
21 D=sqrt(D2^2+D3^2+D4^2)/100; //Distortion Factor
22 P1=1; //assume
23 P=(1+D^2)*P1; //in W
24 peri=((P-P1)/P1)*100; //percentage increase in power
   due to distortion
25 disp(peri,"percentage increase in power due to
   distortion is ,(%)=")

```

---

Scilab code Exa 5.7 power dissipated

```
1 //Example 5.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vcc=15; //in V
7 Vpeak=24/2; //in V
8 Rl=100; //in ohm
9 Ipeak= Vpeak/Rl; //in A
10 Pdc=Vcc*(2/(%pi))*Ipeak; //in W
11 pad=(1/2)*(Vpeak^2)/Rl; //in W
12 pd=Pdc-pad; //in W
13 pde=pd/2; //in W
14 disp(pde*10^3,"power dissipated by each transistor
      is ,(mW)=")
```

---

# Chapter 6

## Field Effect Transistors

Scilab code Exa 6.1 drain resistance transconductance and amplification factor

```
1 //Example 6.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vgs= [0;0;0.3]; //in V
7 Vds=[5;10;10]; //in V
8 Id=[8;8.2;7.6]; //in mA
9 dVds=Vds(2)-Vds(1); //in V
10 dId=Id(2)-Id(1); //in mA
11 rd=(dVds/dId); //in kilo-ohm
12 format('v',4)
13 disp(rd,"(i) A.C. Drain resistance is ,(kilo-ohm)=")
14 dVgs=Vgs(3)-Vgs(2); //in V
15 dId1=Id(2)-Id(3); //in mA
16 gm=dId1/dVgs; //in mA/volt
17 format('v',3)
18 disp(gm,"(ii) Transconductance is ,(mS)=")
19 mu=gm*rd; //A/V
20 format('v',4)
```

```
21 disp(mu,"(iii) Amplification factor is ,=")
22 //Transconductance and Amplification factor are
    calculated wrong in the textbook
```

---

### Scilab code Exa 6.2 mutual conductance

```
1 //Example 6.2:
2 clc;
3 clear;
4 close;
5 //given data :
6 I1=1; // in mA
7 I2=1.2; // in mA
8 del_ID=(I2-I1);
9 V1=-3; // in V
10 V2=-2.9; // in V
11 del_VGS=V2-V1; // in V
12 gm=del_ID/del_VGS;
13 format('v',4)
14 disp(gm,"mutual conductance ,gm(mS) = ")
```

---

### Scilab code Exa 6.3 pinch off voltage

```
1 //Example 6.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',4)
7 a=5.6*10^-6/2; // channel width in m
8 epsilon0=8.86*10^-12; // in F/m
9 epsilon=12*epsilon0; // in F/m
10 Nd=10^21; // in m^-3
```

```

11 e=1.6*10^-19; // in V
12 Vp=e*Nd*a^2/(2*epsilon);
13 disp(Vp,"Pinch off voltage ,Vp(V) = ")

```

---

#### Scilab code Exa 6.4 ID gm and gmo

```

1 //Example 6.4:
2 clc;
3 clear;
4 close;
5 //given data :
6 I_DES=8.7; // in mA
7 V1=-3; // in V
8 V_GS=-1; // in V
9 ID=I_DES*(1-(V_GS/V1))^2;
10 format('v',6)
11 disp(ID,"(i). ID(mA) = ")
12 gmo=-(2*I_DES/V1);
13 format('v',4)
14 disp(gmo,"(ii). gmo(mS) = ")
15 gm=gmo*(1-(V_GS/V1));
16 format('v',6)
17 disp(gm,"(iii). gm(mA) = ")

```

---

#### Scilab code Exa 6.5 Vgs

```

1 //Example 6.5:
2 clc;
3 clear;
4 close;
5 //given data :
6 format('v',4)
7 ID=3; // in mA

```

```

8 I_DSS=9; // in mA
9 Vp=-4.5; // in V
10 Vgs=-Vp*(sqrt(ID/I_DSS)-1);
11 disp(Vgs,"Vgs(V) = ")

```

---

Scilab code Exa 6.6 voltage amplification

```

1 //Example 6.6:
2 clc;
3 clear;
4 close;
5 //given data :
6 gm=3; //Transconductance in mS
7 rl=10; //load resistance in kilo-ohm
8 av=gm*rl; //
9 format('v',4)
10 disp(av,"the voltage amplification is ,=")

```

---

Scilab code Exa 6.7 output voltage

```

1 //Example 6.7:
2 clc;
3 clear;
4 close;
5 //given data :
6 Rl=20; //in kilo-ohm
7 Rs=1; //in kilo-ohm
8 Rg=1; //in M-ohm
9 Cs=25; //in micro-F
10 mu=20; //amplification factor
11 rd=100; //in kilo-ohm
12 vi=2; //in V
13 f=1; //in kilo-Hz

```

```
14 Xc=((1/(2*pi*f*10^3*Cs*10^-6))); //in ohm
15 A=((mu*Rl*10^3)/((rd+Rl)*10^3)); //Voltage gain
16 Vo=A*vi; //in V
17 format('v',5)
18 disp(Vo," amplifier output signal voltage is ,(V)=")
```

---

# Chapter 9

## Silicon Controlled Rectifier

Scilab code Exa 9.1 average voltage

```
1 //Example 9.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vm=200; // in V
7 theta=30; //firing angle in degree
8 vdc=((Vm/%pi)*(1+cosd(theta))); //in V
9 format('v',5)
10 disp(round(vdc),"average value of voltage is ,(V)=")
```

---

Scilab code Exa 9.2 dc load current rms load current amd power dissipated

```
1 //Example 9.2:
2 clc;
3 clear;
4 close;
```



```

5 //given data :
6 Va=300; // in V
7 Vm=300*sqrt(2); //in V
8 Rl=50; //in ohm
9 theta1=90; //firing angle in degree
10 idc=((Vm/(2*pi*Rl))*(1+cosd(theta1))); //in A
11 format('v',6)
12 disp(idc,"(i) the dc load current is ,(A)=")
13 irms=Va/(2*Rl); //in A
14 format('v',4)
15 disp(round(irms),"(ii) the rms load current is ,(A)=")
16 P=irms^2*Rl; //in W
17 format('v',5)
18 disp(round(P),"(iii) the power dissipated by the
    load is ,(W)=")

```

---

**Scilab code Exa 9.3** firing angle conducting angle and average current

```

1 //Example 9.3:
2 clc;
3 clear;
4 close;
5 //given data :
6 Ih=0; //in A
7 Vi=100; // in V
8 Vm=200; //in V
9 Rl=100; //in ohm
10 theta1=asind(Vi/Vm); //firing angle in degree
11 ca=180-theta1; //conducting angle in degree
12 format('v',4)
13 disp(theta1,"(i) firing angle is ,(degree)=")
14 format('v',5)
15 disp(ca,"(ii) conducting angle is ,(degree)=")
16 av=((Vm/(2*pi))*(1+cosd(theta1))); //in V

```

```
17 ac=av/R1; //in A
18 format('v',7)
19 disp(ac,"(iii) average current is ,(A)=")
20 //average current is wrong in the textbook
```

---

# Chapter 10

## The Unijunction Transistor

Scilab code Exa 10.1 stand off and peak point voltage

```
1 //Example 10.1:
2 clc;
3 clear;
4 close;
5 //given data :
6 Vbb=20; // in V
7 eta=0.6; // instrinsic stand off ratio
8 Vb=0.7; // in V
9 sov=eta*Vbb; // Stand off voltage
10 format('v',4)
11 disp(sov,"(i). Stand off voltage ,(V) = ")
12 Vp=(eta*Vbb)+Vb;
13 format('v',6)
14 disp(Vp,"(ii). Peak point voltage ,Vp(V) = ")
```

---

Scilab code Exa 10.2 time period

```
1 //Example 10.2:
```

```

2  clc;
3  clear;
4  close;
5  format('v',6)
6  //given data :
7  Vbb=20; // in V
8  C=100; //in micro-farad
9  R=100; //in kilo-ohms
10 Vp=10; // in V
11 eta=Vp/Vbb; // instrinsic stand off ratio
12 T= ((C*10^-12*R*10^3 *log(1/(1-eta))))*10^7; //in
    micro-seconds
13 format('v',6)
14 disp(T,"time period of the saw tooth waveform
    generated is ,(micro-seconds)=")

```

---

### Scilab code Exa 10.3 resistance

```

1  //Example 10.3:
2  clc;
3  clear;
4  close;
5  //given data :
6  eta=0.6; // instrinsic stand off ratio
7  Rbb=10; // interbase resistance in k-ohm
8  Rb1=eta*Rbb;
9  Rb2=Rbb-Rb1;
10 format('v',4)
11 disp(Rb1," Resistance ,Rb1(k-ohm) = ")
12 disp(Rb2," Resistance ,Rb1(k-ohm) = ")

```

---