

Scilab Textbook Companion for
Electronic Devices and Circuits
by D. C. Kulshreshtha¹

Created by
Harpreet Singh
B. TECH
Others

VYAS INSTITUTE OF ENGINEERING & TECHNOLOGY
College Teacher

None
Cross-Checked by
Bhavani

July 28, 2014

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Electronic Devices and Circuits

Author: D. C. Kulshreshtha

Publisher: New Age International, New Delhi

Edition: 2

Year: 2006

ISBN: 978-81-224-1857-6

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introduction to Electronics	8
2 Semiconductor Physics	13
3 Semiconductor Diode	15
4 Bipolar Junction Transistors	26
5 Field Effect Transistors	33
6 Transistor Biasing and Stabilization	39
7 Small Signal Single Stage Amplifier	52
8 Multistage Amplifiers	63
9 Power Amplifiers	70
10 Feedback in Amplifiers	75
11 Tuned Voltage Amplifiers	81
12 Sinusoidal Oscillators	85
14 Operational Amplifiers	89
15 Electronic Instruments	92

List of Scilab Codes

Exa 1.1	Find the range of tolerance	8
Exa 1.2	Find the range of tolerance	9
Exa 1.3	Find the equivalent current source	9
Exa 1.4	Find percentage variation in load current and load voltage	10
Exa 2.1	Calculate the conductivity and resistivity of germanium	13
Exa 2.2	Determine the conductivity of extrinsic semiconductor	13
Exa 3.1	find the value of threshold voltage	15
Exa 3.2	determine dc resistance of silicon diode	15
Exa 3.3	determine dc and ac resistance of silicon diode	16
Exa 3.4	determine ac resistance of silicon diode	17
Exa 3.5	Find current through diode	17
Exa 3.6	Find current through resistance in given figure	18
Exa 3.7	Find current drawn by the battery	19
Exa 3.8	determine dc current through load and rectification efficiency and peak inverse voltage	20
Exa 3.9	determine dc voltage across load and peak inverse voltage across each diode	20
Exa 3.10	find dc power supplied to load and efficiency and PIV rating of the diode	21
Exa 3.11	Calculate output voltage and current through load and voltage across series resistor and current and power dissipated in zener diode	22
Exa 3.12	Calculate max and min values of zener diode current .	23
Exa 3.13	determine value of the series resistor and wattage rating	24
Exa 3.14	Find the capacitance of a varactor diode	25
Exa 4.1	determine the collector and base current	26

Exa 4.2	determine the base and collector current and exact and approax dc alpha	26
Exa 4.3	Determine the base current	27
Exa 4.4	determine dynamic input resistance	27
Exa 4.5	find dc current gain in common emitter configuration .	28
Exa 4.6	calculate ac alpha and beta	28
Exa 4.7	Calculate beta and I_{CEO} and exact and approax collector current	29
Exa 4.8	determine dynamic input resistance	30
Exa 4.9	determine dynamic input resistance and dc and ac current gain	30
Exa 4.10	calculate ac current gain in CE and CC configuration .	31
Exa 5.1	Calculate saturation voltage and saturation current . .	33
Exa 5.2	Find the value of drain current	33
Exa 5.3	Calculate V_{GS} and V_{DS} saturation	34
Exa 5.4	Calculate drain current I_D for N channel	35
Exa 5.5	Calculate drain current I_D for P channel	36
Exa 5.6	Find the value of drain current	36
Exa 5.7	Find the value of I_D	37
Exa 5.8	Calculate the dynamic drain resistance	38
Exa 6.1	Determine the Q point	39
Exa 6.2	Determine the Q point	40
Exa 6.3	Determine R_B and percentage change in collector current due to temperature rise	40
Exa 6.4	Determine the Q point at two different B	42
Exa 6.5	determine Q point in collector to base bias circuit . .	43
Exa 6.6	Calculate the collector current and change in it if B is changed by three times of previous B	43
Exa 6.7	Calculate the value of all three current I_E and I_C and I_B	44
Exa 6.8	Calculate max and min value of emitter current	45
Exa 6.9	Determine the value of base resistance	46
Exa 6.10	Determine the collector current at two different B . . .	47
Exa 6.11	Calculate Q point in voltage divider	48
Exa 6.12	Solve the voltage divider accurately by applying thevenins theorem	49
Exa 6.13	determine the Q point for the emitter bias circuit . .	50
Exa 6.14	Calculate V_{GS} and R_S	51

Exa 7.1	Calculate max current and check will the capacitor act as short for given frequency	52
Exa 7.2	Check whether the capacitor is an effective bypass for the signal currents of lowest frequency 20 Hz	53
Exa 7.3	Calculate the value of capacitor required	53
Exa 7.4	Calculate voltage and current gain and input and output resistance	54
Exa 7.5	Solve previous example using hybrid pie model	55
Exa 7.6	Determine the value of output voltage	57
Exa 7.7	Calculate voltage gain and input resistance	57
Exa 7.8	Calculate the value of gm at different values of Vgs	58
Exa 7.9	Find the output signal voltage of the amplifier	59
Exa 7.10	Determine the small signal voltage gain and input and output resistance	60
Exa 7.11	Determine the small signal voltage gain and input and output resistance	61
Exa 7.12	Calculate the voltage gain of the FET	61
Exa 8.1	Express the gain in decibel	63
Exa 8.2	Determine power and voltage gain	64
Exa 8.3	Calculate the overall voltage gain	64
Exa 8.4	Calculate quiescent output voltage and small signal voltage gain	65
Exa 8.5	Calculate the maximum voltage gain and bandwidth of multistage amplifier	67
Exa 8.6	Calculate the midband voltage gain and bandwidth of cascade amplifier	68
Exa 8.7	Calculate the input and output impedance and voltage gain	68
Exa 9.1	Determine the turns ratio of the transformer	70
Exa 9.2	Determine the output impedance of the transistor	70
Exa 9.3	Determine the efficiency of a single ended transformer	71
Exa 9.4	Determine input and output power and efficiency	72
Exa 9.5	Calculate the percentage increase in output power	72
Exa 9.6	Calculate harmonic distortion and percentage increase in output voltage due to this	73
Exa 10.1	Determine the gain of feedback amplifier	75
Exa 10.2	Determine the gain of feedback amplifier in dB	75
Exa 10.3	Calculate the percentage of output fed back to input	76

Exa 10.4	Calculate the internal gain and percentage of output fed back to input	76
Exa 10.5	Calculate the gain with and without feedback and feedback factor	77
Exa 10.6	Calculate the gain of feedback amplifier and feedback factor	77
Exa 10.7	Calculate percentage change in the overall gain	78
Exa 10.8	Calculate percentage change in the overall gain	78
Exa 10.9	Determine the input resistance of feedback amplifier	79
Exa 10.10	Calculate the percentage of negative feedback to input	80
Exa 11.1	Calculate frequency and impedance and current and voltage across each element at resonance	81
Exa 11.2	Calculate frequency and impedance and current at resonance and current in coil and capacitor	82
Exa 11.3	Calculate impedance and quality factor and bandwidth	83
Exa 12.1	Calculate frequency of oscillations	85
Exa 12.2	Calculate frequency of oscillations and feedback factor and voltage gain	85
Exa 12.3	Calculate frequency of oscillations	86
Exa 12.4	Calculate frequency of oscillations	87
Exa 12.5	Determine the series and parallel resonant frequencies	87
Exa 14.1	Calculate voltage gain and input and output resistance	89
Exa 14.2	Find the output voltage	89
Exa 14.4	Design an adder circuit using an op amp	90
Exa 14.5	Calculate CMRR in dB	91
Exa 14.6	Calculate the output voltage	91
Exa 15.1	Calculate shunt resistance and multiplying factor	92
Exa 15.2	Calculate shunt resistance	92
Exa 15.3	Caluclate the series resistance to convert it into voltmeter	93
Exa 15.4	Calculate multiplier resistance and voltage multiplying factor	94
Exa 15.5	Calculate reading and error of each voltmeter	94
Exa 15.6	Determine rms value of the ac voltage	96
Exa 15.7	Determine rms value and frequency of the sine voltage	96

Chapter 1

Introduction to Electronics

Scilab code Exa 1.1 Find the range of tolerance

```
1 //Find the range of tolerance
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //color coding
8 orange=3;
9 gold=5;
10 yellow=4;
11 violet=7;
12 //band pattern
13 band1=yellow;
14 band2=violet;
15 band3=orange;
16 band4=gold;
17 //resistor color coding
18 r=(band1*10+band2)*10^(band3);
19 tol=r*(band4/100)//tolerance
20 ulr=r+tol;//upper limit of resistance
21 llr=r-tol;//lower limit of resistance
```

```
22 printf('The Range of resistance is %.2f k to %.2f  
k ',l1r/1000,ulr/1000);
```

Scilab code Exa 1.2 Find the range of tolerance

```
1 //Find the range of tolerance  
2 clear;  
3 clc;  
4 //soltion  
5 //given  
6  
7 //color coding  
8 blue=6;  
9 gold=-1;  
10 gray=8;  
11 silver=10;  
12 //band pattern  
13 band1=gray;  
14 band2=blue;  
15 band3=gold;  
16 band4=silver;  
17 //resistor color coding  
18 r=(band1*10+band2)*10^(band3);  
19 tol=r*(band4/100) //tolerance  
20 ulr=r+tol; //upper limit of resistance  
21 l1r=r-tol; //lower limit of resistance  
22 printf('The Range of resistance is %.2f to %.2f  
' ,l1r,ulr);
```

Scilab code Exa 1.3 Find the equivalent current source

```
1  
2 //Find the equivalent current source
```

```

3 clear;
4 clc;
5 //soltion
6 //given
7 Vs=2; //Volts           //dc voltage source
8 Rs=1; //ohm             //internal resistance
9 Rl=1; //ohm             //load resistance
10 Ise=Vs/Rs; //ampere   //equivalent current source
11
12 // In accordance to figure 1.23a
13 I11=Ise*(Rs/(Rs+Rl)); //using current divider concept
14 V11=I11*Rl;
15 printf("\nIn accordance to figure 1.23a \n");
16 printf("The Load current (current source) Il= %dA\n"
       ,I11);
17 printf("The Load voltage (current source) Vl= %dV\n\
       ",V11);
18
19 // In accordance to figure 1.23b
20 V12=Vs*(Rs/(Rs+Rl)); //using voltage divider concept
21 I12=V12/Rl;
22 printf("\nIn accordance to figure 1.23b \n");
23 printf("The Load voltage (voltage source) Vl= %dV\n"
       ,V12);
24 printf("The Load current (voltage source) Il= %dA\n\
       ",I12);
25 printf("Therefore they both provide same voltage and
       current to load");

```

Scilab code Exa 1.4 Find percentage variation in load current and load voltage

```

1
2 //Find percentage variation in load current and load
   voltage

```

```

3 clear;
4 clc;
5 //soltion
6 //given
7 Vs=10; //volt//Supply voltage
8 Rs=100; //ohm//internal resistance
9
10 // In accordance to figure 1.24a
11 //For 1 - 10
12 Rl11=1; //ohm//min extreme value of Rl
13 Rl12=10; //ohm//max extreme value of Rl
14 I111=Vs/(Rs+Rl11);
15 I112=Vs/(Rs+Rl12);
16 Pi1=(I111-I112)*100/I111;//Percentage variation in
   current
17 V111=I111*Rl11;
18 V112=I112*Rl12;
19 Pv1=(V112-V111)*100/V112;//Percentage variation in
   voltage
20 printf("\nIn accordance to figure 1.24a \n");
21 printf("Percentage variation in Current(1-10 ) %.2
   f percent\n",Pi1);
22 printf("Percentage variation in Voltage(1-10 ) %.1
   f percent\n\n",Pv1);
23
24 // In accordance to figure 1.24b
25 //For 1 k - 10 k
26 Rl21=1000; //ohm//min extreme value of Rl
27 Rl22=10000; //ohm//max extreme value of Rl
28 I121=Vs/(Rs+Rl21);
29 I122=Vs/(Rs+Rl22);
30 Pi2=(I121-I122)*100/I121;//Percentage variation in
   current
31 V121=I121*Rl21;
32 V122=I122*Rl22;
33 Pv2=(V122-V121)*100/V122;//Percentage variation in
   voltage
34 printf("\nIn accordance to figure 1.24b \n");

```

```
35 printf("Percentage variation in Current(1-10      ) %d  
         percent \n",Pi2);  
36 printf("Percentage variation in Voltage(1-10      ) %.1  
         f percent \n\n",Pv2);  
37 // In book the percentage variation in voltage(1 k  
     -10 k ) is 9 percent due to  
38 // the incorrect value of I122 i.e. 0.000999 Amp  
     correct value is 0.0009901 Amp
```

Chapter 2

Semiconductor Physics

Scilab code Exa 2.1 Calculate the conductivity and resistivity of germanium

```
1 //Calculate the conductivity and resistivity of  
germanium  
2 clear;  
3 clc;  
4 //soltion  
5 //given  
6 q=1.6*10^-19; //Coulomb           //charge of an  
electron  
7 ni=2.5*10^19; //per m^3          //concentration  
8 un=0.36; //m^2/Vs                //mobility of electron  
9 up=0.17; //m^2/Vs                //mobility of holes  
10 con=q*ni*(un+up);             //conductivity  
11 res=(1/con);                  //resistivity  
12 printf("The conductivity is %.2f S/m \n",con);  
13 printf("The resistivity is %.2f m ",res);
```

Scilab code Exa 2.2 Determine the conductivity of extrinsic semiconductor

```
1 //Determine the conductivity of extrinsic
   semiconductor
2 clear;
3 clc;
4 //soltion
5 //given
6 e=1.6*10^-19; //Coulomb           //charge of an
   electron
7 ni=1.5*10^16; //per m^3          //concentration
8 un=0.13; //m^2/Vs                //mobility of electron
9 up=0.05; //m^2/Vs                //mobility of holes
10 Si=5*10^28; //per m^3           //atomic density in
    silicon
11 dop=(1/(2*10^8));             //concentration of an
    antimony per silicon atoms
12 Nd=dop*Si; //per m^3           //donor concentratiaon
13 n=Nd; //per m^3                //free electron
    concentration
14 p=(ni^2/Nd); //per m ^3      // hole concentration
15 con=e*(n*un+p*up);
16 printf("The conductivty is %.1f S/m \n",con);
```

Chapter 3

Semiconductor Diode

Scilab code Exa 3.1 find the value of threshold voltage

```
1 //find the value of threshold voltage
2 clear;
3 clc;
4 //soltion
5 //given
6 t1=25; // C //initial temperature
7 t2=100; // C //final temperature
8 V=2*10^-3; //V per celsius degree//decrease in
    barrier potential per degree
9 V0=0.7 //V//Potential at normal temperature
10 Vd=(t2-t1)*V; //decrease in barrier potential
11 Vt=V0-Vd; //threshold volatge at 100 C
12 printf("Threshold volatge at 100 C = %.2f V",Vt);
```

Scilab code Exa 3.2 detrenmine dc resistance of silicon diode

```
1 //detrenmine dc resistance of silicon diode
2 clear;
```

```

3  clc;
4 //soltion
5 //given
6
7 //At Id = 2 mA
8 Id=2*10^-3; //Ampere//diode current
9 Vd=0.5; //V//voltage(from given curve)
10 Rf=(Vd/Id);
11 printf("The dc resistance is %d \n",Rf);
12
13 //At Id = 20 mA
14 Id=20*10^-3; //Ampere//diode current
15 Vd=0.75; //V//voltage(from given curve)
16 Rf=(Vd/Id);
17 printf("The dc resistance is %.1f \n",Rf);
18
19 //At Vd = - 10 V
20 Id=-2*10^-6; //Ampere//diode current (from given curve
    )
21 Vd=-10; //V//voltage
22 Rf=(Vd/Id);
23 printf("The dc resistance is %d M \n",Rf/10^6);

```

Scilab code Exa 3.3 determine dc and ac resistance of silicon diode

```

1 //determine dc & ac resistance of silicon diode
2 clear;
3 clc;
4 //soltion
5 //given
6 Id=20*10^-3; //A//diode current
7 Vd=0.75; //V// as given in the V-I graph
8 Rf=Vd/Id;
9 printf("The dc resistance of diode is %.1f \n",Rf)
    ;

```

```
10
11 //From Graph the values of dynamic voltage and
   current are
12 //which is equal to MN and NL repectively (in graph)
13 del_Vd=(0.8-0.68); //V
14 del_Id=(40-0)*10^-3; //A
15 rf=del_Vd/del_Id;
16 printf("The ac resistance of the diode is %d    ",rf)
```

Scilab code Exa 3.4 determine ac resistance of silicon diode

```
1 //determine ac resistance of silicon diode
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //At Id =10mA
8 Id=10; //mA
9 rf=25/Id;
10 printf("The ac resistance of the diode is(At Id= 10
      mA) %.1f \n",rf)
11
12 //At Id =20mA
13 Id=20; //mA
14 rf=25/Id;
15 printf("The ac resistance of the diode is(At Id= 20
      mA) %.2f    ",rf)
```

Scilab code Exa 3.5 Find current through diode

```
1 //Find current through diode
2 clear;
```

```

3 clc;
4 //soltion
5 //given
6 Vt=0.3; //V// Threshold voltage
7 rf=25; //ohm// average resistance
8
9 //assuming it to be ideal
10 //from fig 3.19
11 Vaa=10; //V// supply
12 R1=45; //ohm
13 R2=5; //ohm
14 Vab=Vaa*R2/(R1+R2);
15 //Vab>Vt therefore diode is forward bias and no
   current flow through R2
16 Idi=Vaa/R1;           //for ideal
17 printf("The diode current (for ideal) is %.0f mA\n",
         Idi*1000);
18
19 //assuming it to be real
20 //Thevenin's equivalent circuit parameters of fig
   3.19
21 Vth=Vaa*R2/(R1+R2);
22 Rth=R1*R2/(R1+R2);
23 Idr=(Vth-Vt)/(Rth+rf);          //for real
24 printf("The diode current (for real) is %.1f mA",Idr
         *1000);

```

Scilab code Exa 3.6 Find current through resistance in given figure

```

1 //Find current through resistance in given figure
2 clear;
3 clc;
4 //soltion
5
6 //From fig

```

```

7 Vaa=20; //V// supply
8 Vt=0.7; //V// threshold voltage of diode
9 rf=5; //ohm //forward resistance
10 R=90; //ohm// given resistor
11
12 //Diode D1 and D4 are forward bias and D2 and D3 are
   reverse biased
13
14 Vnet=Vaa-Vt-Vt;
15 Rt=R+rf+rf;
16 I=Vnet/Rt;
17 printf("Current through 90 ohm resistor is %.0f mA",
         I*1000);

```

Scilab code Exa 3.7 Find current drawn by the battery

```

1 //Find current drawn by the battery
2 clear;
3 clc;
4 //soltion
5
6 //From fig
7 Vaa=10; //V// supply
8 R1=100; //ohm
9 R2=100; //ohm
10
11 //Forward Bias
12 Id=Vaa/R1;
13 printf("Current drawn from battery (forward bias) %
         .1f A\n", Id);
14
15 //Reverse Bias
16 Rnet=R1+R2;
17 Id=Vaa/Rnet;
18 printf("Current drawn from battery (reverse bias) %

```

.2 f A" ,Id);

Scilab code Exa 3.8 determine dc current through load and rectification efficiency and peak inverse voltage

```
1 //determine dc current through load and
   rectification efficiency and peak inverse voltage
2 clear;
3 clc;
4 //soltion
5 //given
6 TR=31/2; //Turn ratio of the transformer
7 rf=20; // Dynamic forward resistance
8 Rl=1000; // Load resistance
9 Vt=0.66; //V// Threshold voltage of diode
10 V=220; //V// input voltage of transformer
11 Vp=sqrt(2)*220//V//peak value of primary voltage
12Vm=(1/TR)*Vp;
13 Im=(Vm-Vt)/(rf+Rl);
14 Idc=Im/%pi;
15 n=40.6/(1+rf/Rl);
16 printf("The dc current through load is %d mA\n",Idc
      *1000);
17 printf("The rectification efficiency is %.1f percent
      \n",n);
18 printf("Peak inverse voltage =Vm = %.2 f V\n",Vm)
```

Scilab code Exa 3.9 determine dc voltage across load and peak inverse voltage across each diode

```
1 //determine dc voltage across load and peak inverse
   voltage across each diode
2 clear;
```

```

3 clc;
4 //soltion
5 //given
6 TR=12/1; //Turn ratio of the transformer
7 V=220; //V//input voltage of transformer
8 Vp=sqrt(2)*220//V//peak value of primary voltage
9Vm=(1/TR)*Vp;
10 Vdc=(2*Vm)/%pi;
11 printf("The dc voltage across load %.1f V\n",Vdc);
12 printf("Peak inverse voltage (for bridge rectifier)
    = %.1f V\n",Vm);
13 printf("Peak inverse voltage (for centre tap
    rectifier) = %.2f V\n",2*Vm);

```

Scilab code Exa 3.10 find dc power supplied to load and efficiency and PIV rating of the diode

```

1 //find dc power supplied to load and efficiency and
   PIV rating of the diode
2 clear;
3 clc;
4 //soltion
5 //given
6 rf=2; // Dynamic forward resistance
7 Rs=5; // resistaqnce of secondary
8 Rl=25; // Load resistance
9 Idc=0.1; //A//dc current to a load
10 Pdc=Idc^2*Rl; //dc power
11 n=(81.2*Rl)/(Rl+rf+Rs); //efficiency
12 Im=(%pi*Idc)/2; //peak value current
13 Vm=Im*(Rl+rf+Rs); //peak voltage
14 Vlm=Vm-Im*(rf+Rs); //peak voltage
   across load
15 PIV=Vm+Vlm;
16 printf("The dc power supplied to the load is %.2f W\

```

```

        n" ,Pdc);
17 printf("Efficiency = %.2f percent\n",n);
18 printf("The peak inverse voltage is %.2f V",PIV);

```

Scilab code Exa 3.11 Calculate output voltage and current through load and voltage across series resistor and current and power dissipated in zener diode

```

1 // Calculate output voltage and current through load
   and voltage across series resistor and current
   and power dissipated in zener diode
2 clear;
3 clc;
4 //soltion
5 //given
6 Vi=110; //V           //input voltage
7 Rl=6*10^3; // ohm      //load resistance
8 Rs=2*10^3; //ohm       //series resistance
9 Vz=60; //V            //Zener voltage
10 V=Vi*Rl/(Rs+Rl);
11
12 //This V>Vz therefore Zener diode is ON
13
14 Vo=Vz;             //output voltage
15 I1=Vo/Rl;          //Current through load resistance
16 Vs=Vi-Vo;          //Voltage drop across the series
                      resistor
17 Is=Vs/Rs;          //current through the series
                      resistor
18 Iz=Is-I1;          ///By applying kirchhoff's law
19 Pz=Vz*Iz;          //Power dissipated accross zener
                      diode
20
21 printf("The output voltage is %.0f V\n",Vo);
22 printf("The current through load resistance is %.0f

```

```

mA\n" ,I1*1000);
23 printf("Voltage across series resistor is %.0f V\n",
Vs)
24 printf("Current in zener diode is %.0f mA\n" ,Iz
*1000)
25 printf("Power dissipated by zener diode %.0f mW" ,Pz
*1000);

```

Scilab code Exa 3.12 Calculate max and min values of zener diode current

```

1
2 //Calculate max and min values of zener diode
   current
3 clear;
4 clc;
5 //soltion
6 //given
7 Vimin=80; //V           //minimum input voltage
8 Vimax=120; //V           //maximum input voltage
9 Rl=10*10^3; // ohm       //load resistance
10 Rs=5*10^3; //ohm         // series resistance
11 Vz=50; //V             //Zener voltage
12 V=Vimin*Rl/(Rs+Rl);
13
14 //This V>Vz therefore Zener diode is ON
15
16 //For minimum value of zener diode
17
18 Vo=Vz;                 //output voltage
19 Vs=Vimin-Vo;           //Voltage drop across the series
   resistor
20 Is=Vs/Rs;              //current through the series
   resistor
21 I1=Vo/Rl;              //Current through load resistance
22 Izmin=Is-I1;

```

```

23 printf("\nMinimum values of zener diode current is %f mA\n", Izmin*1000);
24
25 //For maximum value of zener diode
26
27 Vo=Vz;           //output voltage
28 Vs=Vimax-Vo;    //Voltage drop across the series
29 Is=Vs/Rs         //current through the series
30 resistor
31 Il=Vo/Rl;        //Current through load resistance
32 Izmax=Is-Il;
33 printf("Maximum values of zener diode current is %.0f mA", Izmax*1000);

```

Scilab code Exa 3.13 determine value of the series resistor and wattage rating

```

1 //determine value of the series resistor and wattage
rating
2 clear;
3 clc;
4 //soltion
5 //given
6 Vi=12; //V           //input voltage
7 Vz=7.2; //V           //Zener voltage
8 Izmin=10*10^-3; //A      //min current through
zener diode
9 Ilmax=100*10^-3; //A      //max current through
load
10 Ilmin=12*10^-3; //A      //min current through
load
11
12 Vs=Vi-Vz;          //Voltage drop across the series
resistor

```

```

13 Is=Izmin+Ilmax;           //Current through the series
   resistor
14 Rs=Vs/Is;
15 printf("The series resistor so that 10mA current
   flow through zener diode is %.1f \n",Rs);
16
17 Izmax=Is-Ilmin;          //max zener through zener diode
18 Pmax=Izmax*Vz;
19 printf("The maximum wattage rating is %.1f mW",Pmax
   *1000);

```

Scilab code Exa 3.14 Find the capacitance of a varactor diode

```

1 //Find the capacitance of a varactor diode
2 clear;
3 clc;
4 //soltion
5 //given
6 C=5; //pf//capcitance of varactor diode at V=4V
7 V=4; //V
8 K=C*sqrt(4);
9
10 //When bias voltage is increased upto 6 V
11 Vn=6; //V//new bias voltage
12 Cn=K/(sqrt(Vn));
13 printf("Capacitance (At 6 V ) = %.3f pf",Cn);

```

Chapter 4

Bipolar Junction Transistors

Scilab code Exa 4.1 determine the collector and base current

```
1 //determine the collector and base current
2 clear;
3 clc;
4 //soltion
5 //given
6 a=0.98; //dc alpha
7 Ie=5*10^-3; //A//emitter current
8 Ico=2*10^-6; //A//collector reverse leakage current
9 Ic=a*Ie+Ico;
10 Ib=Ie-Ic;
11 printf("The collector current is %.3f mA\n",Ic*1000)
    ;
12 printf("The base current is %.0f uA",Ib*10^6);
```

Scilab code Exa 4.2 determine the base and collector current and exact and approax dc alpha

```
1 //determine the base and collector current and exact
    and approax dc alpha
```

```

2 clear;
3 clc;
4 //soltion
5 //given
6 Ie=8.4*10^-3 //A// emitter current
7 Icbo=0.1*10^-6; //A// reverse leakage current
8 Ib=0.008*Ie; //A// base current
9 Ic=Ie-Ib;
10 Icinj=Ic-Icbo;
11 a0=Icinj/Ie;
12 a=Ic/Ie;
13 printf("Base current is %.1f uA\n", Ib*10^6);
14 printf("Collector current %.4f mA\n", Ic*1000);
15 printf("Exact value of alphha = %.7f\n", a0);
16 printf("Approax value of alpha = %.3f", a);

```

Scilab code Exa 4.3 Determine the base current

```

1 //Determine the base current
2 clear;
3 clc;
4 //soltion
5 //given
6 a=0.96;           //dc alpha
7 Rc=2*10^3; //ohm      //resistor across collector
8 Vc=4; //V          //Voltage drop across the
                      //collector resistor
9 Ic=Vc/Rc;         //Colletor current
10 Ie=Ic/a;          //Emmitter current
11 Ib=Ie-Ic;         //Base current
12 printf("The base current is %.0f uA", Ib*10^6)

```

Scilab code Exa 4.4 determine dynamic input resistance

```

1 //determine dynamic input resistance
2 clear;
3 clc;
4 //soltion
5 //given
6 Ie=2; //mA
7 Vcb=10; //V
8
9 //Taking points around Ie & Vcb from graph
10 del_Ie=(2.5-1.5)*10^-3; //A
11
12 //corresponding change in Veb
13 del_Veb=(0.9-0.8); //V
14 rib=del_Veb/del_Ie;
15 printf("The dynamic input resistance of transistor
      is %.0f    ",rib);

```

Scilab code Exa 4.5 find dc current gain in common emitter configuration

```

1 //find dc current gain in common emitter
   configuration
2 clear;
3 clc;
4 //soltion
5 //given
6 a=0.98; //dc current gain in common base
   configuration
7 B=a/(1-a);
8 printf("The dc current gain in common emitter
   configuration is %.0f",B);

```

Scilab code Exa 4.6 calculate ac alpha and beta

```

1 // calculate ac alpha and beta
2 clear;
3 clc;
4 //soltion
5 //given
6 ic=0.995 //mA// Emitter current change
7 ie=1 //mA// collector current change
8 a=ic/ie;
9 B=a/(1-a);
10 printf("The ac alpha is %.3f\n",a)
11 printf("The common emitter ac current gain is %.0f",
B);

```

Scilab code Exa 4.7 Calculate beta and Iceo and exact and approax collector current

```

1 // Calculate beta and Iceo and exact and approax
   collector current
2 clear;
3 clc;
4 //soltion
5 //given
6 a0=0.992; //dc current gain in common base
   configuration
7 Icbo=48*10^-9; //A
8 Ib=30*10^-6; //A//base current
9 B=a0/(1-a0);
10 Iceo=Icbo/(1-a0);
11 printf("Beta= %.0f\n",B);
12 printf("Iceo= %.0.f uA\n",Iceo*10^6);
13 Ic=B*Ib+Iceo;
14 Ica=B*Ib; //approax
15 printf("Exact collector current %.3f mA\n",Ic*1000);
16 printf("Approax collector current %.2f mA",Ica*1000)
;
```

Scilab code Exa 4.8 determine dynamic input resistance

```
1 //determine dynamic input resistance
2 clear;
3 clc;
4 //soltion
5 //given
6 Vbe=0.75; //V
7 Vce=2; //V
8
9 //Taking points around Vbe=0.75V from graph
10 del_Vbe=(0.98-0.9); //V
11
12 //corresponding change in ib
13 del_ib=(68-48)*10^-6; //A
14
15 rie=del_Vbe/del_ib;
16 printf("The dynamic input resistance of transistor
      is %.0f k ",rie/1000);
```

Scilab code Exa 4.9 determine dynamic input resistance and dc and ac current gain

```
1 //determine dynamic input resistance and dc and ac
   current gain
2 clear;
3 clc;
4 //soltion
5 //given
6 Ib=30*10^-6; //A
7 Vce=10; //V
```

```

8 Ic=3.6*10^-3; //A           //from graph
9
10 //Taking points around Vce = 10V from graph
11 del_Vce=(12.5-7.5); //V
12
13 //corresponding change in ic
14 del_ic=(3.7-3.5)*10^-3; //A
15
16 roe=del_Vce/del_ic;
17 printf("The dynamic output resistance of transistor
      is %.0f k \n",roe/1000);
18
19 //dc current gain
20 Bo=Ic/Ib;
21 printf("The dc current gain is %.0f\n",Bo);
22
23 //ac current gain
24
25 del_ic=(4.7-2.5)*10^-3;    //the collector current
      change is from 3.5mA to 4.7mA as we can see from
      graph when we change ib from 40mA to 20mA
26 del_ib=(40-20)*10^-6;
27 B=del_ic/del_ib;
28 printf("The ac current gain is %.0f\n",B);

```

Scilab code Exa 4.10 calculate ac current gain in CE and CC configuration

```

1 // calculate ac current gain in CE and CC
      configuration
2 clear;
3 clc;
4 //soltion
5 //given
6 a=0.99;

```

```
7 B=a/(1-a);
8 printf("The ac current gain in CE configuration is %
.0 f\n",B);
9 y=1+B;
10 printf("The ac current gain in CC configuration is %
.0 f",y);
```

Chapter 5

Field Effect Transistors

Scilab code Exa 5.1 Calculate saturation voltage and saturation current

```
1 // Calculate saturation voltage and saturation
   current
2 clear;
3 clc;
4 // soltion
5 // given
6 Vp=-4 //V           // pinch off voltage
7 Idss=12*10^-3; //A    // drain to source current
   with gate shorted
8 Vgs=-2; //V          // gate to source voltage
9 Vds=Vgs-Vp;
10 Id=Idss*(Vds/Vp)^2;
11 printf("Saturation Voltage is %.0 f V\n",Vds);
12 printf("Saturation current is %.0 f mA",Id*10^3);
```

Scilab code Exa 5.2 Find the value of drain current

```
1 //Find the value of drain current
```

```

2 clear;
3 clc;
4 //soltion
5 //given
6 Vgso=-5; //V           //gate to source cut off
    voltage
7 Idss=20*10^-3; //A      //drain to source current with
    gate shorted
8
9 //At vgs = -2 V
10 vgs=-2; //V           input voltage
11 id=Idss*(1-(vgs/Vgso))^2;          //Schockley 's
    equation
12 printf("Drain current is (At vgs = -2 V) %.1f mA\n", 
    id*10^3);
13
14 //At vgs = -4 V
15 vgs=-4; //V           input voltage
16 id=Idss*(1-(vgs/Vgso))^2;          //Schockley 's
    equation
17 printf("Drain current is (At vgs = -4 V) %.1f mA\n", 
    id*10^3);
18
19 //At vgs = -8 V
20 printf("Drain current is 0 A (At vgs = -8 V) because
    gate is biased beyond cut off ");

```

Scilab code Exa 5.3 Calculate Vgs and Vds saturation

```

1 //Calculate Vgs and Vds saturation
2 clear;
3 clc;
4 //soltion
5 //given
6 Vp=5 //V           //pinch off voltage

```

```

7 Idss=-15*10^-3; //A      // drain to source current
    with gate shorted
8 Id=-3*10^-3; //A          //saturation current
9 Vgs=Vp*(1-sqrt(Id/Idss));
10 Vds=Vgs-Vp;
11 printf("The gate to source voltage (Vgs) is %.3f V\n
        ",Vgs);
12 printf("The saturation voltage is Vds(sat)= %.3f V" ,
        Vds);
13
14 // THe value of Vgs = 2.115V and Vds= -2.885V in
book because of the calculation error

```

Scilab code Exa 5.4 Calculate drain current Id for N channel

```

1 //Calculate drain current Id for N channel
2 clear;
3 clc;
4 //soltion
5 //given
6 Vp=5//V           //pinch off voltage
7 Idss=18*10^-3; //A      //drain to source current with
    gate shorted
8
9 //For Vgs= - 3 V
10 Vgs=-3; //V
11 Id=Idss*(1-(Vgs/(-Vp)))^2;
12 printf("The drain current Id(For Vgs= -3V) = %.2f mA
        \n",Id*10^3);
13
14 //For Vgs= 2.5 V
15 Vgs=2.5; //V
16 Id=Idss*(1-(Vgs/(-Vp)))^2;
17 printf("The drain current Id(For Vgs= 2.5V) = %.1f
        mA",Id*10^3);

```

Scilab code Exa 5.5 Calculate drain current Id for P channel

```
1 //Calculate drain current Id for P channel
2 clear;
3 clc;
4 //soltion
5 //given
6 Vp=-5 //V           //pinch off voltage
7 Idss=18*10^-3; //A    //drain to source current with
                           gate shorted
8
9 //For Vgs= -3V
10 Vgs=-3; //V
11 Id=Idss*(1-(Vgs/(-Vp)))^2;
12 printf("The drain current Id (For Vgs= -3V) = %.2f
          mA\n", Id*10^3);
13
14 //For Vgs= 2.5V
15 Vgs=2.5; //V
16 Id=Idss*(1-(Vgs/(-Vp)))^2;
17 printf("The drain current Id (For Vgs= 2.5V) = %.1f
          mA", Id*10^3);
```

Scilab code Exa 5.6 Find the value of drain current

```
1 //Find the value of drain current
2 clear;
3 clc;
4 //soltion
5 //given
6 Vt=2; //V           //threshold voltage
```

```

7 K=0.25*10^-3; // A/V^2      //conductivity parameter
8 Vgs=3; //V      //gate supply
9 Vds=2; //V      //saturation voltage
10 Vdsm=Vgs-Vt;           //minimum voltage required to
                           pinch off
11
12 // Vds > Vdsm therefore the device is in saturation
   region
13
14 Id=K*(Vgs-Vt)^2;
15 printf("The drain current is %.2f mA", Id*1000);

```

Scilab code Exa 5.7 Find the value of Id

```

1 //Find the value of Id
2 clear;
3 clc;
4 //soltion
5 //given
6 Vt=1.5; //V      //threshold voltage
7 Id=2*10^-3; //A
8 Vgs=3; //V      //gate supply
9 Vds=5; //V      //saturation voltage
10 Vdsm=Vgs-Vt;           //minimum voltage required to
                           pinch off
11
12 // Vds > Vdsm therefore the device is in saturation
   region
13
14 // Calculating K
15 K=Id/((Vgs-Vt)^2);           // A/V^2      //
                           conductivity parameter
16
17 //Calculating Id for Vgs= 5 V and Vds= 6 V
18 Vgs=5; //V      //gate supply

```

```
19 Vds=6; //V      //saturation voltage
20 Id=K*((Vgs-Vt)^2);
21 printf("The drain current is %.2f mA", Id*1000);
```

Scilab code Exa 5.8 Calculate the dynamic drain resistance

```
1 //Calculate the dynamic drain resistance
2 clear;
3 clc;
4 //soltion
5 //given
6 gm=200*10^-6; //S          trans conductance
7 u=80; //           amplification factor
8 rd=u/gm;
9 printf("The dynamic drain resistance is %.0f k ", rd
       /1000);
```

Chapter 6

Transistor Biasing and Stabilization

Scilab code Exa 6.1 Determine the Q point

```
1 //Determine the Q point
2 clear;
3 clc;
4 //soltion
5 //given
6 B=50;           //dc beta
7 Rc=2.2*10^3; //ohm      //resistor connected to
                  collector
8 Rb=270*10^3; //ohm      //resistor connected to base
9 Vcc=9; //V          //Voltage supply across the
                  collector resistor
10 Vbe=0.7; //V        //base to emitter voltage
11 Ib=(Vcc-Vbe)/Rb; //Base current
12 Ic=B*Ib;         //Colletor current
13 Ics=Vcc/Rc;       //Colletor saturation current
14
15 //Actual Ic is the smaller of the above two values
16
17 Vce=Vcc-Ic*Rc;
```

```
18 printf("The Q point is (%.2f V, %.1f mA)", Vce, Ic  
    *1000);  
19 //In book Vce = 5.7 V because of approaximation
```

Scilab code Exa 6.2 Determine the Q point

```
1 //Determine the Q point  
2 clear;  
3 clc;  
4 //soltion  
5 //given  
6 B=150;           //dc beta  
7 Rc=1*10^3; //ohm      //resistor connected to  
                   collector  
8 Rb=100*10^3; //ohm      //resistor connected to base  
9 Vcc=10; //V          //Voltage supply across the  
                   collector resistor  
10 Vbe=0.7; //V         //base to emitter voltage  
11 Ib=(Vcc-Vbe)/Rb;   //Base current  
12 Ic=B*Ib;           //Colletor current  
13 Ics=Vcc/Rc;        //Colletor saturation current  
14  
15 //Actual Ic is the smaller of the above two values i  
   .e. Ic(sat) and since the transistor is in  
       saturation mode therefore Vce will become 0  
16  
17 Vce=0;  
18 printf("The Q point is (%d V, %.0f mA)", Vce, Ics  
    *1000);
```

Scilab code Exa 6.3 Determine Rb and percentage change in collector current due to temperature rise

```

1 //Determine Rb and percentage change in collector
   current due to temperature rise
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //Calculating the base resistance
8 B=20;           //dc beta
9 Rc=1*10^3; //ohm      //resistor connected to
   collector
10 Ic=1*10^-3; //A        //collector current
11 Vcc=6; //V          //Voltage supply across the
   collector resistor
12 Vbe=0.3; //V        //for germanium
13 Icbo=2*10^-6; //A      //collector to base leakage
   current
14
15 Ib=(Ic-(1+B)*Icbo)/B;
16 Rb=(Vcc-Vbe)/Ib;
17
18 printf("The value of resistor Ib is %.4f k = 120
   k \n",Rb/1000);
19
20 Rb=120*10^3; //ohm      approax
21
22 //Now when temperature rise
23 Icbo=10*10^-6; //A      //collector to base leakage
   current
24 B=25;           //dc beta
25 Ic1=B*Ib+(B+1)*Icbo;           //changed collector
   current
26 perc=(Ic1-Ic)*100/Ic;           //percentage increase
27 printf("The percentage change in collector current
   is %.0f percent",perc);

```

Scilab code Exa 6.4 Determine the Q point at two different B

```
1 //Determine the Q point at two different B
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //At B=50
8
9 B=50;           //dc beta
10 Rc=2*10^3; //ohm      //resistor connected to
    collector
11 Rb=300*10^3; //ohm      //resistor connected to base
12 Vcc=9; //V          //Voltage supply across the
    collector resistor
13 Ib=Vcc/Rb;        //Base current
14 Ic=B*Ib;         //Colletor current
15 Ics=Vcc/Rc;       //Colletor saturation current
16
17 //Actual Ic is the smaller of the above two values
18
19 Vce=Vcc-Ic*Rc;
20 printf("The Q point (At B=50) is (%.0 f V, %.1 f mA)\n"
    ,Vce,Ic*1000);
21
22 //At B=150
23
24 B1=150;           //dc beta
25 Ic1=B*Ib;        //Colletor current
26 Ics1=Vcc/Rc;       //Colletor saturation current
27
28 //Actual Ic is the smaller of the above two values i
    .e. Ic(sat) and since the transistor is in
```

```

    saturation mode therefore Vce will become 0
29
30 Vce=0;
31 printf("The Q point (At B=150) is (%d V, %.1f mA)\n"
32           ,Vce,Ics*1000);
33 printf("The factor at which collector current
34 increases %.0f" ,Ics1/Ic);

```

Scilab code Exa 6.5 determine Q point in collector to base bias circuit

```

1 //determine Q point in collector to base bias
   circuit
2 clear;
3 clc;
4 //soltion
5 //given
6 B=100;           //dc beta
7 Rc=500; //ohm      //resistor connected to collector
8 Rb=500*10^3; //ohm //resistor connected to base
9 Vcc=10; //V         //Voltage supply across the
   collector resistor
10 Ib=Vcc/(Rb+B*Rc); //Base current
11 Ic=B*Ib;          //Colletor current
12 Ics=Vcc/Rc;        //Colletor saturation current
13
14 //Actual Ic is the smaller of the above two values
15
16 Vce=Vcc-(Ic+Ib)*Rc;
17 printf("The Q point is (%.1f V, %.1f mA)" ,Vce,Ic
           *1000);

```

Scilab code Exa 6.6 Calculate the collector current and change in it if B is changed by three times of previous B

```
1 //Calculate the collector current and change in it
   if B is changed by three times of previous B
2 clear;
3 clc;
4 //soltion
5 //given
6 B=50;           //dc beta
7 Rc=2*10^3; //ohm      //resistor connected to
   collector
8 Rb=300*10^3; //ohm      //resistor connected to base
9 Vcc=9; //V          //Voltage supply across the
   collector as it is PNP so taking positive
10 Ib=Vcc/(Rb+B*Rc); //Base current
11 Ic=B*Ib;          //Colletor current
12 printf("Collector current (B=50)= %.3f mA\n",Ic
   *1000);
13 //Now B=150
14 B=3*B;           //three times of previous B
15 Ib1=Vcc/(Rb+B*Rc); //Base current
16 Ic1=B*Ib1;        //Colletor current
17 printf("Collector current (B=150)= %.2f mA\n",Ic1
   *1000);
18 printf("The factor at which collector current
   increases %.0f", Ic1/Ic);
```

Scilab code Exa 6.7 Calculate the value of all three current I_e and I_c and I_b

```
1 //Calculate the value of all three current  $I_e$  and  $I_c$ 
   and  $I_b$ 
2 clear;
3 clc;
```

```

4 //soltion
5 //given
6 B=90;           //dc beta
7 Rc=1*10^3; //ohm      //resistor connected to
                     collector
8 Rb=500*10^3; //ohm      //resistor connected to base
9 Re=500; //ohm      //resistor connected to emitter
10 Vcc=9; //V          //Voltage supply across the
                         collector resistor
11 Ib=Vcc/(Rb+B*Re);           //Base current
12 Ic=B*Ib;                  //Collector current
13 Ie=Ic+Ib;                  //Emitter current
14 printf("Base current = %.1f uA \nCollector current =
             %.3f mA \nEmitter current = %.4f mA", Ib*10^6, Ic
             *10^3, Ie*10^3);

```

Scilab code Exa 6.8 Calculate max and min value of emitter current

```

1 //Calculate max and min value of emitter current
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //At B=50
8
9 B=50;           //dc beta
10 Rc=75; //ohm      //resistor connected to collector
11 Re=100; //ohm      //resistor connected to emitter
12 Rb=10*10^3; //ohm      //resistor connected to base
13 Vcc=6; //V          //Voltage supply across the
                         collector resistor
14 Vbe=0.3; //V          //for germanium
15 Ib=(Vcc-Vbe)/(Rb+(1+B)*Re);           //Base current
16 Ie=(1+B)*Ib;

```

```

17 Vce=Vcc-(Rc+Re)*Ie
18 printf("Minimum emitter current %.2f mA\n", Ie*10^3);
19 printf("The collector to emitter volatge is %.2f V\n"
      , Vce);
20
21 //At B=300
22
23 B1=300;           //dc beta
24 Ib1=(Vcc-Vbe)/(Rb+(1+B1)*Re);           //Base current
25 Ie1=(1+B1)*Ib1;
26 Vce1=Vcc-(Rc+Re)*Ie1
27 //Here Vce1= -1.4874 V but can never have negative
   voltage because Ie1 is wrong as it can't be more
   than saturation value therefore
28 Ie1=Vcc/(Rc+Re);
29
30 //And Vce=0 V
31
32 Vce1=0; //V
33 printf("Maximum emitter current %.2f mA\n", Ie1*10^3)
      ;
34 printf("The collector to emitter volatge(saturation)
      is %.0f V\n", Vce1);

```

Scilab code Exa 6.9 Determine the value of base resistance

```

1 //Determine the value of base resistance
2 clear;
3 clc;
4 //soltion
5 //given
6
7 B=100;           //dc beta
8 Rc=200; //ohm    //resistor connected to collector
9 Re=500; //ohm    //resistor connected to emitter

```

```

10 Vcc=9; //V           //Voltage supply across the
   collector as it is PNP so taking positive
11 Vce=4.5; //V           //Collector to emitter voltage
12 Ic=(Vcc-Vce)/(Rc+Re);
13 Ib=Ic/B;
14 Rb=(Vcc-B*Re*Ib)/Ib;
15 printf("The value of base resistance is %.0f k ",Rb
         /1000);

```

Scilab code Exa 6.10 Determine the collector current at two different B

```

1 //Determine the collector current at two different B
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //At B=50
8
9 B=50;                  //dc beta
10 Rc=2; //ohm          //resistor connected to collector
11 Re=1000; //ohm        //resistor connected to emitter
12 Rb=300*10^3; //ohm    //resistor connected to base
13 Vcc=9; //V           //Voltage supply across the
   collector resistor
14 Ib=Vcc/(Rb+B*Re);    //Base current
15 Ic=B*Ib;             //Colletor current
16 printf("the collector current at (B=50)= %.3f mA\n",
         Ic*1000);
17
18 //At B=150
19
20 B1=150;               //dc beta
21 Ib1=Vcc/(Rb+B1*Re);  //Base current
22 Ic1=B1*Ib1;           //Colletor current

```

```

23 printf("the collector current at (B=150)= %.0f mA\n"
24 ,Ic1*1000);
24 printf("The factor at which collector current
25 increases %.2f", Ic1/Ic);
25
26 //IN BOOK Ic (AT B=50)= 1.25 mA and Ic1 / Ic=2.4 DUE TO
26 APPROXIMATION

```

Scilab code Exa 6.11 Calculate Q point in voltage divider

```

1 //Calculate Q point in voltage divider
2 clear;
3 clc;
4 //soltion
5 //given
6 B=100;           //dc beta
7 Rc=2*10^3; //ohm      //resistor connected to
8 collector
9 R1=10*10^3; //ohm      //voltage divider resistor 1
10 R2=1*10^3; //ohm      //voltage divider resistor 2
11 Re=200; //ohm      //resistor connected to emitter
11 Vcc=10; //V          //Voltage supply across the
12 collector resistor
12 Vbe=0.3; //V          //base to emitter voltage
13
14 I=Vcc/(R1+R2);      //current through voltage
15 divider
15 Vb=I*R2;           //voltage at base
16 Ve=Vb-Vbe;
17 Ie=Ve/Re;
18 Ic=Ie           //approaximating Ib is nearly equal to
18 0
19 Vc=Vcc-Ic*Rc;
20 Vce=ceil(Vc)-Ve;
21 printf("The Q point is (%.1f V, %.0f mA)", Vce, Ic)

```

```

        *1000);

22 Ibc=I/20;      //critical value of base current
24 Ib=Ic/B;      //actual base current
25
26 //Since Ib < Ibc , hence assumption is alright

```

Scilab code Exa 6.12 Solve the voltage divider accurately by applying thevenins theorem

```

1
2 //Solve the voltage divider accurately by applying
   thevenin's theorem
3 clear;
4 clc;
5 //soltion
6 //given
7 B=100;           //dc beta
8 Rc=2*10^3; //ohm    //resistor connected to
                     collector
9 R1=10*10^3; //ohm    //voltage divider resistor 1
10 R2=1*10^3; //ohm    //voltage divider resistor 2
11 Re=200; //ohm     //resistor connected to emitter
12 Vcc=10; //V         //Voltage supply across the
                     collector resistor
13 Vbe=0.3; //V        //base to emitter voltage
14
15 Vth=Vcc*R2/(R1+R2);
16 Rth=R1*R2/(R1+R2);
17
18 printf("\nThevenin equivalent voltage Vth = %.5f V" ,
   Vth);
19 printf("\nThevenin equivalent resistance Rth = %.2f
   ohm" ,Rth);
20

```

```

21 Ib=(Vth-Vbe)/(Rth+(1+B)*Re);
22 Ic=B*Ib;
23 Ie=Ic+Ib;
24 Vce=Vcc-Ic*Rc-Ie*Re;
25 printf("\nThe accurate value of Ic = %.5f mA",Ic
    *10^3);
26 printf("\nThe accurate value of Vce = %.6f V",Vce);
27 Icp=3*10^-3; // Current calculated by voltage
    divider in previous example
28 Vcep=3.4; // Voltage calculated by voltage divider
    in previous example
29 Err_Ic=(Ic-Icp)*100/Ic;
30 Err_Vce=(Vce-Vcep)*100/Vce;
31 printf("\nError in Ic= %.1f percent\n",Err_Ic);
32 printf("Error in Vce= %.0f percent",Err_Vce);
33
34 // The errors and The accurate values are different
35 // because of the approaximation in Vth and Rth in
    book
36
37 // In Book Ic = 2.8436 mA and Vce = 3.73839 V
38 // Error in Ic = -5.5%
39 // Error in Vce = +9%

```

Scilab code Exa 6.13 determine the Q point for the emitter bias circuit

```

1 //determine the Q point for the emitter bias circuit
2 clear;
3 clc;
4 //soltion
5 //given
6 B=100;           //dc beta
7 Rc=5*10^3; //ohm      //resistor connected to
    collector
8 Rb=10*10^3; //ohm      //resistor connected to base

```

```

9 Re=10*10^3; //ohm           //resistor connected to
   emitter
10 Vcc=12; //V                 //Voltage supply across the
    collector resistor
11 Vee=15; //V                 //supply at emitter
12 Ie=Vee/Re;
13 Ic=Ie;
14 Vce=Vcc-Ic*Rc;
15 printf("The Q point is (%.1f V, %.1f mA)", Vce, Ic
    *1000);

```

Scilab code Exa 6.14 Calculate Vgs and Rs

```

1 //Calculate Vgs and Rs
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Vp=2; //V
8 Idss=1.75*10^-3; //A          //drain current at Vgs=0
9 Vdd=24; //V                  //drain to supply source
10 Id=1*10^-3; //A            //drain current
11 Vgs=(-Vp)*(1-sqrt(Id/Idss));
12 Rs=abs(Vgs)/Id;
13 printf("Vgs = %.3f V\n", Vgs);
14 printf("Rs = %.0f      ", Rs);

```

Chapter 7

Small Signal Single Stage Amplifier

Scilab code Exa 7.1 Calculate max current and check will the capacitor act as short for given frequency

```
1 //Calculate max current and check will the capacitor
   act as short for given frequency
2 clear;
3 clc;
4 //soltion
5 //given
6
7 C=100*10^-6; //Farad
8 Rs=1*10^3; //ohm
9 Rl=4*10^3; //ohm
10 Vs=1; //V
11 Imax=Vs/(Rs+Rl);
12 fc=1/(2*pi*(Rs+Rl)*C)      //critical frequency
13 fh=10*fc;                  //Border frequency
14 printf("Maximum current is %.0f uA\n", Imax*10^6);
15 printf("fh = %.2f Hz\n", fh);
16 printf("As long as source frequency is greater than
   %.2f Hz, the coupling capacitor acts like an ac
```

```
    short for 20Hz to 20kHz." ,fh)  
17  
18 //In book Imax is 200mA but there is misprinting of  
   'm' in mA it should be uA
```

Scilab code Exa 7.2 Check whether the capacitor is an effective bypass for the signal currents of lowest frequency 20 Hz

```
1 //Check whether the capacitor is an effective bypass  
   for the signal currents of lowest frequency 20  
   Hz  
2 clear;  
3 clc;  
4 //soltion  
5 //given  
6  
7 C=100*10^-6; //Farad  
8 Rs=1*10^3; //ohm  
9 Rl=4*10^3; //ohm  
10 f=20; //Hz           //lowest frequency  
11 Xc=1/(2*pi*f*C)      //reactance of capacitor at  
                           20Hz  
12 Rth=Rs*Rl/(Rs+Rl);     //Thevenin's equivalent  
                           resistance  
13 printf("Xc < Rth/10 = %.1f      < %.1f f      is satisfied  
          \n",Xc,Rth/10);  
14 printf("The capacitor of 100uF will work as a good  
         bypass for frequencies greater than 20 Hz ")
```

Scilab code Exa 7.3 Calculate the value of capacitor required

```
1 //Calculate the value of capacitor required  
2 clear;
```

```

3  clc;
4  //soltion
5  //given
6
7  Rs1=20*10^3; //ohm
8  Rs2=30*10^3; //ohm
9  Rl1=40*10^3; //ohm
10 Rl2=80*10^3; //ohm
11 Rl3=80*10^3; //ohm
12 Rth=Rs1*Rs2/(Rs1+Rs2);           //Thevenin 's
13 Rl_=Rl2*Rl3/(Rl2+Rl3);
14 Rl=Rl1*Rl_/(Rl1+Rl_);          //Equivalent load
15 f=50; //Hz                  //lowest frequency
16 R=Rth+Rl;
17 C=10/(2*pi*f*R)
18 printf("The required value of coupling capacitor is
%0.0 f uF",C*10^6);

```

Scilab code Exa 7.4 Calculate voltage and current gain and input and output resistance

```

1 //Calculate voltage and current gain and input and
   output resistance
2 clear;
3 clc;
4 //soltion
5
6 function [z]=prll(r1,r2)//Function for the parallel
   combination of resistor
7     z=r1*r2/(r1+r2);
8 endfunction
9
10 // given
11

```

```

12 //DC analysis
13 Vcc=12; //V
14 Rb=200*10^3; //ohm
15 Rc=1*10^3; //ohm
16 B=100; // beta
17 Ib=Vcc/Rb;
18 Ic=B*Ib;
19 Icsat=Vcc/Rc;
20 Vce=Vcc-Ic*Rc;
21 printf("The Q point of DC analysis= (%.0f V, %.0f mA
    )\n",Vce,Ic*1000);
22
23 //AC analysis
24 Rl=1*10^3; //ohm
25 hfe=B;
26 hie=2*10^3; //ohm
27 hoe_1=40*10^3; //ohm           // 1/hoe
28 Rac=prll(Rc,Rl);
29 Av=-hfe*Rac/hie;
30 printf("The voltage gain = %.0f\n",Av);
31
32 //Since (1/hoe) > Rac therefore entire current will
   flows through Rac
33 Io=-100*Ib;
34 Ac=Io/Ib;
35 printf("The current gain = %.0f\n",Ac);
36
37 Ri=prll(Rb,hie);
38 Ro=prll(Rl,prll(Rc,hoe_1));
39 printf("The input resistance= %.0f k \n",Ri/1000);
40 printf("The output resistance= %.1f k ",Ro/1000);
41
42 //In book the voltage gain is 25 due to skipping of
   '-' in printing

```

Scilab code Exa 7.5 Solve previous example using hybrid pie model

```
1 //Solve previous example using hybrid pie model
2 clear;
3 clc;
4 //soltion
5 function [z]=prll(r1,r2)//Function for the parallel
    combination of resistor
6     z=r1*r2/(r1+r2);
7 endfunction
8
9 //given
10
11 Vcc=12; //V
12 Rb=200*10^3; //ohm
13 Rc=1*10^3; //ohm
14 Rl=1*10^3; //ohm
15 B=100; // beta
16 hie=2*10^3; //ohm
17 hoe_1=40*10^3; //ohm           // 1/hoe
18
19 Ib=Vcc/Rb;
20 Ic=B*Ib;
21 Rac=prll(Rc,Rl);
22 gm=Ic/(25*10^-3);
23 rpi=B/gm;
24 ri=hie;
25 rb=ri-rpi;
26 ro=hoe_1;
27 Vi=poly(0,"Vi");           //let the input be Vi
28 Vpi=Vi*rpi/(rpi+rb);
29 Vo=-gm*Vpi*Rac;          //output voltage
30 Av=Vo/Vi;
31 printf("The voltage gain ");
32 disp(Av);
33 //In book voltage gain is -24.96 due to
    appraoximation
```

Scilab code Exa 7.6 Determine the value of output voltage

```
1 //Determine the value of output voltage
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Vcc=12; //V
8 Rb=150*10^3; //ohm
9 Rc=5*10^3; //ohm
10 B=200; // beta
11 hie=2*10^3; //ohm
12 ro=60*10^3; //ohm      // 1/hoe
13 Vi=1*10^-3; //V
14 Ib=Vcc/Rb;
15 Ic=B*Ib;
16 Icsat=Vcc/Rc;
17 // Icsat < Ic therefore transistor is in saturation
    mode and outpuut voltage wil be zero
18 Vo=0;
19 printf("The output voltage= %.0 f V",Vo);
```

Scilab code Exa 7.7 Calculate voltage gain and input resistance

```
1 //Calculate voltage gain and input resistance
2 clear;
3 clc;
4 //soltion
5
6 function [z]=prll(r1,r2)//Function for the parallel
    combination of resistor
```

```

7      z=r1*r2/(r1+r2);
8  endfunction
9
10 // given
11 R1=75*10^3; //ohm
12 R2=7.5*10^3; //ohm
13 Rc=4.7*10^3; //ohm
14 Re=1.2*10^3; //ohm
15 Rl=12*10^3; //ohm
16 B=150;
17 ri=2*10^3; //ohm
18 Vcc=15; //V
19 Vb=Vcc*R2/(R1+R2);
20 Ve=Vb;           // since Vbe=0
21 Ie=Ve/Re;
22 Ic=Ie;
23 Icsat=Vcc/(Rc+Re);
24 // Ic < Icsat therefore transistor is in active mode
25 Vce=Vcc-Ic*(Rc+Re);
26 printf("The Q point of DC analysis= (%.1f V, %.3f mA
) \n",Vce,Ic*1000);
27
28 Rac=prll(Rc,Rl);
29 Av=-B*Rac/ri;
30 printf("The voltage gain = %.1f \n",Av);
31 Ri_=prll(ri,R2);
32 printf("The input resistance= %.2f k \n",Ri_/1000);

```

Scilab code Exa 7.8 Calculate the value of gm at different values of Vgs

```

1
2 // Calculate the value of gm at different values of
   Vgs
3 clear;
4 clc;

```

```

5 //soltion
6 //given
7
8 Idss=8*10^-3; //A
9 Vp=4; //V
10 //At Vgs= -0.5 V
11 Vgs= -0.5; //V
12 gmo=2*Idss/(abs(Vp));
13 gm=gmo*(1-(Vgs/(-Vp)));
14 printf("gmo = %.0 f mS\n",gmo*1000);
15 printf("gm (At Vgs = -0.5V) =%.1 f mS\n",gm*1000);
16
17 //At Vgs= -1.5 V
18 Vgs= -1.5; //V
19 gmo=2*Idss/(abs(Vp));
20 gm=gmo*(1-(Vgs/(-Vp)));
21 printf("gm (At Vgs = -1.5V) =%.1 f mS\n",gm*1000);
22
23 //At Vgs= -2.5 V
24 Vgs= -2.5; //V
25 gmo=2*Idss/(abs(Vp));
26 gm=gmo*(1-(Vgs/(-Vp)));
27 printf("gm (At Vgs = -2.5V) =%.1 f mS\n",gm*1000);

```

Scilab code Exa 7.9 Find the output signal voltage of the amplifier

```

1 //Find the output signal voltage of the amplifier
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Rd=12*10^3; //ohm
8 Rg=1*10^6; //ohm
9 Rs=1*10^3; //ohm

```

```

10 Cs=25*10^-6; //F
11 u=80;           //amplification factor
12 rd=200*10^3;  //ohm
13 Vi=0.1;        //V
14 f=1*10^3;      //Hz          //input frequency
15 Xcs=1/(2*pi*f*Cs);
16 //This is much smaller than Rs therefore it is
   bypassed
17
18 gm=u/rd;
19 Av=gm*(rd*Rd/(rd+Rd));
20 Vo=Av*Vi;
21 printf("The output voltage is %.3f V",Vo);

```

Scilab code Exa 7.10 Determine the small signal voltage gain and input and output resistance

```

1 //Determine the small signal voltage gain and input
   and output resistance
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Rd=2*10^3; //ohm
8 rd=100*10^3; //ohm
9 Rg=1*10^6; //ohm
10 gm=2*10^-3; //S
11 Av=-gm*(rd*Rd/(rd+Rd));
12 Ri=Rg;
13 Ro=rd*Rd/(rd+Rd);
14 printf("The small signal voltage gain = %.0f\ninput
   resistance= %.0f M \noutput resistance = %.0f
   k ",Av,Ri/10^6,Ro/1000);

```

Scilab code Exa 7.11 Determine the small signal voltage gain and input and output resistance

```
1 //Determine the small signal voltage gain and input  
    and output resistance  
2 clear;  
3 clc;  
4 //soltion  
5 //given  
6  
7 R1=500*10^3; //ohm  
8 R2=50*10^3; //ohm  
9 Rd=5*10^3; //ohm  
10 Rs=100; //ohm  
11 Rl=5*10^3; //ohm  
12 gm=1.5*10^-3; //S  
13 rd=200*10^3; //ohm  
14 Rg=R1*R2/(R1+R2);  
15 Rac=Rd*Rl/(Rd+Rl);  
16 Av=-gm*Rac;  
17 Ri=Rg;  
18 Ro=(rd*Rac/(rd+Rac));  
19 printf("The small signal voltage gain = %.2f\ninput  
    resistance= %.2f k \noutput resistance = %.1f  
    k ",Av,Ri/1000,Ro/1000);
```

Scilab code Exa 7.12 Calculate the voltage gain of the FET

```
1 //Calculate the voltage gain of the FET  
2 clear;  
3 clc;  
4 //soltion
```

```
5 // given
6
7 Idss=8*10^-3; //A
8 Vp=4; //V
9 rd=25*10^3; //ohm
10 Rd=2.2*10^3; //ohm      //by the help of figure
11 Vgs=-1.8; //V
12 gmo=2*Idss/(abs(Vp));
13 gm=gmo*(1-(Vgs/(-Vp)));
14 Av=-gm*(rd*Rd/(rd+Rd));
15 printf("The voltage gain of the FET %.2f",Av);
```

Chapter 8

Multistage Amplifiers

Scilab code Exa 8.1 Express the gain in decibel

```
1 // Express the gain in decibel
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //Power gain of 1000
8 Pg1=1000;
9 Pg1d=10*log10(Pg1);
10 printf("Power gain (in dB)= %.0f dB\n",Pg1d);
11
12 //Voltage gain of 1000
13 Vg1=1000;
14 Vg1d=20*log10(Vg1);
15 printf("Voltage gain (in dB)= %.0f dB\n",Vg1d);
16
17 //Power gain of 1/100
18 Pg2=1/100;
19 Pg2d=10*log10(Pg2);
20 printf("Power gain (in dB)= %.0f dB\n",Pg2d);
21
```

```
22 //Voltage gain of 1/100
23 Vg2=1/100;
24 Vgd2=20*log10(Vg2);
25 printf(" Voltage gain (in dB)= %.0 f dB\n",Vgd2);
```

Scilab code Exa 8.2 Determine power and voltage gain

```
1
2 //Determine power and voltage gain
3 clear;
4 clc;
5 //soltion
6 //given
7
8 //For Gain = 10 dB
9 G=10; //dB
10 Pg1=10^(G/10);           //taking antilog
11 Vg1=10^(G/20);           //taking antilog
12 printf("\nFor Gain = %.0 f dB",G)
13 printf("\nPower gain ratio = %.0 f \n",Pg1);
14 printf("Voltage gain ratio = %.2 f \n",Vg1);
15
16 //For Gain 3 dB
17 G=3; //dB
18 Pg2=10^(G/10);           //taking antilog
19 Vg2=10^(G/20);           //taking antilog
20 printf("\nFor Gain = %.0 f dB\n",G)
21 printf("Power gain ratio = %.0 f \n",Pg2);
22 printf("Voltage gain ratio = %.3 f \n",Vg2);
```

Scilab code Exa 8.3 Calculate the overall voltage gain

```
1 //Calculate the overall voltage gain
```

```

2 clear;
3 clc;
4 //soltion
5 //given
6
7 A1=80
8 A2=50
9 A3=30
10 Ad=20*log10(A1)+20*log10(A2)+20*log10(A3);;
11
12 //Alternatively
13 A=A1*A2*A3;
14 Ad=20*log10(A);
15 printf("The Voltage gain is %.2f dB",Ad);

```

Scilab code Exa 8.4 Calculate quiescent output voltage and small signal voltage gain

```

1 //Calculate quiescent output voltage and small
   signal voltage gain
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //At input Voltage =3V
8 Vi1=3; //V           //input voltage
9 Vbe=0.7; //V
10 B=250;
11 Vcc=10; //V           //Supply
12 Re1=1*10^3; //ohm
13 Rc1=3*10^3; //ohm
14 Re2=2*10^3; //ohm
15 Rc2=4*10^3; //ohm
16 Vb1=Vi1;          //Voltage at the base of transistor

```

```

T1
17 Ve1=Vb1-Vbe;           //Voltage at the emitter of
    transistor T1
18 Ie1=Ve1/Re1;
19 Ic1=Ie1;
20 Vc1=Vcc-Ic1*Rc1;
21 Vb2=Vc1;
22 Ve2=Vb2-Vbe;
23 Ie2=Ve2/Re2;
24 Ic2=Ie2;
25 Vo1=Vcc-Ic2*Rc2;
26 printf("The quiescent output voltage(At input
    Voltage =3 V ) is %.1f V\n",Vo1);
27
28 //At input Voltage =3.2 V
29 Vi2=3.2; //V           //input voltage
30 Vb1=Vi2;           //Voltage at the base of transistor
    T1
31 Ve1=Vb1-Vbe;           //Voltage at the emitter of
    transistor T1
32 Ie1=Ve1/Re1;
33 Ic1=Ie1;
34 Vc1=Vcc-Ic1*Rc1;
35 Vb2=Vc1;
36 Ve2=Vb2-Vbe;
37 Ie2=Ve2/Re2;
38 Ic2=Ie2;
39 Vo2=Vcc-Ic2*Rc2;
40 printf("The quiescent output voltage (At input
    Voltage =3.2 V) is %.1f V\n",Vo2);
41
42 //Small Signal input and output voltage
43 vi=Vi2-Vi1;
44 vo=Vo2-Vo1;
45 Av=vo/vi;
46 printf("The small signal voltage gain is %.0f ",Av)

```

Scilab code Exa 8.5 Calculate the maximum voltage gain and bandwidth of multistage amplifier

```
1 //Calculate the maximum voltage gain and bandwidth
   of multistage amplifier
2 clear;
3 clc;
4 //soltion
5 //FUNCTIONS
6
7 function [z]=prll(r1,r2)//Function for the parallel
   combination of resistor
8 z=r1*r2/(r1+r2);
9 endfunction
10
11 //given
12 rin=10*10^6; //ohm           //input resistance of JFET
13 Rd=10*10^3; //ohm
14 Rs=500; //ohm
15 Rg=470*10^3; //ohm
16 Rl=470*10^3; //ohm
17 Cc=0.01*10^-6; //Farad
18 Csh=100*10^-12; //Farad
19 Cs=50*10^-6; //Farad
20 rd=100*10^3; //ohm
21 gm=2*10^-3; //S
22 Rac2=prll(Rd,Rl);
23 Rac1=prll(Rd,Rg);
24 Req=prll(rd,prll(Rd,Rl));
25 Am=ceil(gm*Req);
26 Am2=Am*Am;           //Voltage gain of two stage
   amplifier
27 printf("Voltage gain of two stage amplifier= %.0f\n"
   ,Am2);
```

```

28 R_=prll(rd,Rd)+prll(Rg,rin);
29 f1=1/(2*pi*Cc*R_);           //lower cutoff frequency
30 f1_=f1/(sqrt(sqrt(2)-1));
31 f2=1/(2*pi*Csh*Req);        //upper cutoff frequency
32 f2_=f2*(sqrt(sqrt(2)-1));
33 BW=f2_-f1_;
34 printf("Bandwidth= %.1f kHz",BW/1000);
35
36 //There is a slight error in f1 due to use of R'(
    here R_)=479 k and in f2 due to approaximation
    of Req there is a slight variation

```

Scilab code Exa 8.6 Calculate the midband voltage gain and bandwidth of cascade amplifier

```

1 // Calculate the midband voltage gain and bandwidth
   of cascade amplifier
2 clear;
3 clc;
4 //soltion
5 //given
6 Am=8;           //midband voltage gain of individual
   MOSFET
7 BW=500*10^3 //Hz
8 f2=BW;
9 n=4;
10 A2m=Am^n;
11 f2_=f2*(sqrt((2^(1/n))-1));
12 printf("Midband voltage gain = %.0f\n",A2m);
13 printf("Overall Bandwidth= %.1f kHz",f2_/1000);

```

Scilab code Exa 8.7 Calculate the input and output impedance and voltage gain

```

1 //Calculate the input and output impedance and
   voltage gain
2 clear;
3 clc;
4 //soltion
5 //FUNCTIONS
6
7 function [z]=prll(r1,r2)//Function for the parallel
   combination of resistor
8     z=r1*r2/(r1+r2);
9 endfunction
10
11 hie=1.1*10^3; //ohm      = rin
12 hfe=120; //      = B
13
14 //the values of Rac2, Zi, Zo are as per diagram
15 Rac2=prll(3.3*10^3,2.2*10^3);
16 Rac1=prll(6.8*10^3,prll(56*10^3,prll
   (5.6*10^3,1.1*10^3)));
17 Zi=prll(5.6*10^3,prll(56*10^3,1.1*10^3));
18 Zo=prll(3.3*10^3,2.2*10^3);
19
20 printf("Input Resistance = %.3f k \nOutput
   Resistance = %.2f k \n",Zi/1000,Zo/1000);
21
22 Am2=-hfe*Rac2/(hie);
23 Am1=-hfe*Rac1/(hie);
24 Am=Am1*Am2;
25 Am=20*log10(Am);
26 printf("The Overall Voltage gain is %.2f dB",Am);

```

Chapter 9

Power Amplifiers

Scilab code Exa 9.1 Determine the turns ratio of the transformer

```
1 //Determine the turns ratio of the transformer
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R1=8; //ohm
8 R1_=5*10^3; //ohm
9 TR=sqrt(R1_/R1);           //Turns ratio
10 printf("Turns Ratio= %.0f : 1",TR);
```

Scilab code Exa 9.2 Determine the output impedance of the transistor

```
1 //Determine the output impedance of the transistor
2 clear;
3 clc;
4 //soltion
5 //given
```

```

6
7 TR=16/1;      //turn ratio
8 Rl=4; //ohm    //loudspeaker impedance
9 ro=(TR^2)*Rl;
10 printf("The output impedance of the transistor %.0f
           ",ro);

```

Scilab code Exa 9.3 Determine the efficiency of a single ended transformer

```

1
2 //Determine the efficiency of a single ended
   transformer
3 clear;
4 clc;
5 //soltion
6 //given
7
8 Vceq=10; //V      //supply voltage
9
10 //At Vp=10V
11 Vp=10; //V
12 Vce_max1=Vceq+Vp;
13 Vce_min1=Vceq-Vp;
14 n1=50*((Vce_max1-Vce_min1)/(Vce_max1+Vce_min1))^2;
15 printf("Efficiency (At Vp = 10V)= %.0f percent\n",n1
           );
16
17 //At Vp=5V
18 Vp=5; //V
19 Vce_max2=Vceq+Vp;
20 Vce_min2=Vceq-Vp;
21 n2=50*((Vce_max2-Vce_min2)/(Vce_max2+Vce_min2))^2;
22 printf("Efficiency (At Vp = 5V)= %.1f percent\n",n2)
           ;
23

```

```

24 //At Vp=1V
25 Vp=1; //V
26 Vce_max3=Vceq+Vp;
27 Vce_min3=Vceq-Vp;
28 n3=50*((Vce_max3-Vce_min3)/(Vce_max3+Vce_min3))^2;
29 printf("Efficiency (At Vp = 1V)= %.1f percent\n",n3)
;
```

Scilab code Exa 9.4 Determine input and output power and efficiency

```

1 //Determine input and output power and efficiency
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Vcc=20; //V      //supply voltage
8 Rl=4; //
9 Vp=15; //V
10 Ip=Vp/Rl;
11 Idc=Ip/%pi;
12 Pi=Vcc*Idc;
13 Po=((Vp/2)^2)/Rl;
14 n=100*Po/Pi;
15 printf("Input power %.2f W\n",Pi);
16 printf("Output power %.2f W\n",Po);
17 printf("Efficiency = %.0f percent\n",n);
```

Scilab code Exa 9.5 Calculate the percentage increase in output power

```

1 //Calculate the percentage increase in output power
2 clear;
3 clc;
```

```

4 //soltion
5 //given
6
7 D=0.2; //harmonic distortion
8 P=(1+D^2); //Total power increase
9
10 //percent increase= (Pi*(1+D^2)-Pi)*100/Pi;
11 //taking out and cancelling Pi
12 PI=(P-1)*100;
13 printf("The percentage increase in output power= %.0
           f percent",PI);

```

Scilab code Exa 9.6 Calculate harmonic distortion and percentage increase in output voltage due to this

```

1 //Calculate harmonic distortion and percentage
   increase in output voltage due to this
2 clear;
3 clc;
4 //soltion
5 //given
6
7 I1=60; //A
8 I2=6; //A
9 I3=1.2; //A
10 I4=0.6; //A
11 D2=I2/I1;
12 D3=I3/I1;
13 D4=I4/I1;
14 printf("The Harmonic distortion of each component\
           nD2= %.0 f percent\nD3= %.0 f percent\nD4= %.0 f
           percent\n",D2*100,D3*100,D4*100);
15
16 D=sqrt((D2)^2+(D3)^2+(D4)^2);
17 printf("The Total Harmonic distortion = %.0 f percent

```

```
\n" ,D*100);  
18 P=(1+D^2); //Total power increase  
19  
20 //percent increase= (Pi*(1+D^2)-Pi)*100/Pi;  
21 //taking out and cancelling Pi  
22 PI=(P-1)*100;  
23 printf("The percentage increase in output power= %.0  
f percent",PI);
```

Chapter 10

Feedback in Amplifiers

Scilab code Exa 10.1 Determine the gain of feedback amplifier

```
1 //Determine the gain of feedback amplifier
2 clear;
3 clc;
4 //soltion
5 //given
6
7 A=100;           //internal gain
8 B=0.1; //feedback factor
9 Af=A/(1+A*B);
10 printf("The gain of feedback amplifier %.2 f",Af);
```

Scilab code Exa 10.2 Determine the gain of feedback amplifier in dB

```
1 //Determine the gain of feedback amplifier in dB
2 clear;
3 clc;
4 //soltion
5 //given
```

```
6
7 Ad=60; //dB      //internal gain in dB
8 A=10^(Ad/20);   //internal gain
9 B=1/20; //feedback factor
10 Af=A/(1+A*B);
11 Af_d=20*log10(Af);
12 printf("The gain of feedback amplifier %.2f dB",Af_d)
;
```

Scilab code Exa 10.3 Calculate the percentage of output fed back to input

```
1 // Calculate the percentage of output fed back to
   input
2 clear;
3 clc;
4 //soltion
5 //given
6
7 A=600;      //internal gain
8 Af=50;       //gain of feedback amplifier
9 B=(A/Af -1)/A;
10 printf("The percentage of output fed back to input=
    %.3f percent",B*100);
```

Scilab code Exa 10.4 Calculate the internal gain and percentage of output fed back to input

```
1 // Calculate the internal gain and percentage of
   output fed back to input
2 clear;
3 clc;
4 //soltion
5 //given
```

```
6
7 Af=80;      //gain of feedback amplifier
8 Vi=0.05; //V      //input with feedback
9 Vi_=4*10^-3; //V      //input without feedback
10 Vo_=Af*Vi;
11 A=Vo_/_Vi_;
12 printf("The internal gain is %.0 f\n",A);
13 B=(A/Af-1)/A;
14 printf("The percentage of output fed back to input=
%.2 f percent",B*100);
```

Scilab code Exa 10.5 Calculate the gain with and without feedback and feedback factor

```
1 //Calculate the gain with and without feedback and
   feedback factor
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Vo_=5; //V          //output voltage
8 Vi=0.2; //V      //input with feedback
9 Vi_=0.05; //V      //input without feedback
10 A=Vo_/_Vi_;
11 Af=Vo_/_Vi;
12 printf("The gain without feedback is %.0 f\n",A);
13 printf("The gain with feedback is %.0 f\n",Af);
14 B=(A/Af-1)/A;
15 printf("The feedback factor= %.0 f percent",B*100);
```

Scilab code Exa 10.6 Calculate the gain of feedback amplifier and feedback factor

```

1 // Calculate the gain of feedback amplifier and
   feedback factor
2 clear;
3 clc;
4 //soltion
5 //given
6
7 A=100;           //internal gain
8 N=20; //dB      //negative feedback
9 B=(10^(-N/(-20))-1)/A;          //taking antilog
10 Af=A/(1+A*B);
11 printf("The feedback factor= %.0f percent\n",B*100);
12 printf("The gain of the feedback amplifier is %.0f\n"
         ,Af);

```

Scilab code Exa 10.7 Calculate percentage change in the overall gain

```

1 // Calculate percentage change in the overall gain
2 clear;
3 clc;
4 //soltion
5 //given
6
7 A=1000;           //internal gain
8 N=40; //dB      //negative feedback
9 D=10^((-N)/-20); //D=(1+AB)    desensitivity
10 dA_A=10; //percent //dA/A
11 dAf_Af=dA_A/D; //dAf/Af
12 printf("The percentage change in the overall gain= %
         .1f percent",dAf_Af);

```

Scilab code Exa 10.8 Calculate percentage change in the overall gain

```

1 //Calculate percentage change in the overall gain
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Adb=60; //dB      //internal gain in dB
8 B=0.005;           //feedback factor
9 A=10^(Adb/(20));    //taking antilog
10 dA_A=-12; //percent //dA/A
11 D=(1+A*B);      //D=(1+AB)   desensitivity
12 dAf_Af=dA_A/D;    //dAf/Af
13 printf("The percentage change in the overall gain
reduces by %.1f percent", -dAf_Af);

```

Scilab code Exa 10.9 Determine the input resistance of feedback amplifier

```

1 //Determine the input resistance of feedback
amplifier
2 clear;
3 clc;
4 //soltion
5 //given
6
7 A=250;          //internal gain
8 B=0.1; //feedback factor
9 Ri=1.1*10^3; //ohm      //input resistance
10 Rif=Ri*(1+A*B);
11 printf("The input resistance of feedback amplifier %
.1f k ",Rif/1000);
12 //The ans in book is incorrect due to use of (2+A*B)
instead of (1+A*B) the ans in book is 29.7 k

```

Scilab code Exa 10.10 Calculate the percentage of negative feedback to input

```
1 //Calculate the percentage of negative feedback to
   input
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Adb=60; //dB      //internal gain in dB
8 A=10^(Adb/(20)); //taking antilog
9 Ro=12*10^3; //ohm    //output resistance
10 Rof=600; //ohm
11 B=(Ro/Rof-1)/A;
12 printf("The percentage of negative feedback to input
           = %.1f percent",B*100);
```

Chapter 11

Tuned Voltage Amplifiers

Scilab code Exa 11.1 Calculate frequency and impedance and current and voltage across each element at resonance

```
1 //Calculate frequency and impedance and current and
   voltage across each element at resonance
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R=12; //ohm
8 L=200*10^-6; //H
9 C=300*10^-12; //F
10 Vs=9; //V
11 fo=1/(2*pi*sqrt(L*C));
12 Z=R;      //impedance
13 printf("The Resonant frequency= %.1f kHz\n",fo/1000)
14 ;
14 printf("The impedance Z= %.0f \n",Z);
15
16 Io=Vs/R;
17 printf("The Source current= %.2f A\n",Io);
18
```

```

19 Vl=Io*(2*pi*f0*L);
20 Vc=Io/(2*pi*f0*C);
21 Vr=Io*R;
22 printf("The voltage across the inductor =%.1f V\n", Vl);
23 printf("The voltage across the capacitor =%.1f V\n", Vc);
24 printf("The voltage across the resistor =%.0f V\n", Vr);
25 //There is a slight variation in voltage across
   capacitor due to the approaximation

```

Scilab code Exa 11.2 Calculate frequency and impedance and current at resonance and current in coil and capacitor

```

1 //Calculate frequency and impedance and current at
   resonance and current in coil and capacitor
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R=10; //ohm
8 L=100*10^-6; //H
9 C=100*10^-12; //F
10 Vs=10; //V
11 fo=1/(2*pi*sqrt(L*C));
12 Zp=L/(C*R);      //impedance
13 printf("The Resonant frequency= %.3f MHz\n", fo/10^6)
   ;
14 printf("The impedance Z= %.0f k \n", Zp/1000);
15
16 Io=Vs/Zp;
17 printf("The Source current= %.0f uA\n", Io*10^6);
18

```

```

19 X1=(2*pi*fo*L);
20 Xc=1/(2*pi*fo*C);
21 Z1=sqrt(X1^2+R^2);
22 Z2=Xc;
23 Ic=Vs/Z2;
24 Il=Ic;
25 printf("The current in the coil = %.0f mA\n",Il
    *1000);
26 printf("The current in the capacitor = %.0f mA\n",Ic
    *1000);

```

Scilab code Exa 11.3 Calculate impedance and quality factor and bandwidth

```

1 //Calculate impedance and quality factor and
   bandwidth
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R=10; //ohm
8 L=150*10^-6; //H
9 C=100*10^-12; //F
10 fo=1/(2*pi*sqrt(L*C));
11 Zp=L/(C*R);      //impedance
12 printf("The impedance Z= %.0f k \n",Zp/1000);
13
14 X1=(2*pi*fo*L);
15 Q=X1/R;
16 BW=fo/Q;
17 printf("The Quality factor of the circuit =%.1f \n",
    Q);
18 printf("The Band width of the circuit =%.1f kHz\n",
    BW/1000);

```


Chapter 12

Sinusoidal Oscillators

Scilab code Exa 12.1 Calculate frequency of oscillations

```
1 // Calculate frequency of oscillations
2 clear;
3 clc;
4 //soltion
5 //given
6
7 L=55*10^-6; //H
8 C=300*10^-12; //F
9 fo=1/(2*pi*sqrt(L*C));
10 printf("The frequency of oscillations= %.0 f kHz\n",
    fo/1000);
```

Scilab code Exa 12.2 Calculate frequency of oscillations and feedback factor and voltage gain

```
1 // Calculate frequency of oscillations and feedback
   factor and voltage gain
2 clear;
```

```

3 clc;
4 //soltion
5
6 function [z]=prll(r1,r2)//Function for the parallel
    combination of resistor
7     z=r1*r2/(r1+r2);
8 endfunction
9
10 //given
11 C1=0.001*10^-6;//F
12 C2=0.01*10^-6;//F
13 L=15*10^-6;//H
14 C=prll(C1,C2);
15 fo=1/(2*pi*sqrt(L*C));
16 printf("The frequency of oscillations= %.2f MHz\n",
    fo/10^6);
17 B=C1/C2;
18 Amin=1/B;
19 printf("The feedback factor of the circuit =%.1f \n"
    ,B);
20 printf("The circuit needs a minimum voltage gain of
    %.0f",Amin);

```

Scilab code Exa 12.3 Calculate frequency of oscillations

```

1 //Calculate frequency of oscillations
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R=10*10^3;//ohm
8 C=0.01*10^-6;//F
9 fo=1/(2*pi*R*C*sqrt(6));
10 printf("The frequency of oscillations= %.1f Hz\n",fo

```

) ;

Scilab code Exa 12.4 Calculate frequency of oscillations

```
1 //Calculate frequency of oscillations
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R=22*10^3; //ohm
8 C=100*10^-12; //F
9 fo=1/(2*pi*R*C);
10 printf("The frequency of oscillations= %.2f KHz\n",
    fo/1000);
```

Scilab code Exa 12.5 Determine the series and parallel resonant frequencies

```
1 //Determine the series and parallel resonant
   frequencies
2 clear;
3 clc;
4 //soltion
5
6 function [z]=prll(r1,r2)//Function for the parallel
   combination of resistor
7     z=r1*r2/(r1+r2);
8 endfunction
9
10 // given
11
12 L=3; //H
```

```
13 Cm=10*10^-12; //F
14 Cs=0.05*10^-12; //F
15 fs=1/(2*pi*sqrt(L*Cs));
16 printf("The series resonant frequency =%.0f kHz\n",
         fs/1000);
17
18 Cp=prll(Cm,Cs);
19 fp=1/(2*pi*sqrt(L*Cp));
20 printf("The parallel resonant frequency =%.0f kHz",
         fp/1000);
```

Chapter 14

Operational Amplifiers

Scilab code Exa 14.1 Calculate voltage gain and input and output resistance

```
1 //Calculate voltage gain and input and output
   resistance
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R1=20*10^3; //ohm
8 Rf=2000*10^3; //ohm
9 Ac1=-Rf/R1;
10 Ricl=R1;
11 Ro=0;
12 printf("The voltage gain= %.0 f\n",Ac1);
13 printf("The input resistance =%.0 f k \n",R1/1000);
14 printf("The output resistance =%.0 f \n",Ro);
```

Scilab code Exa 14.2 Find the output voltage

```

1 //Find the output voltage
2 clear;
3 clc;
4 //soltion
5 //given
6
7 R1=20*10^3; //ohm
8 Rf=2000*10^3; //ohm
9 v1=4; //V
10 v2=3.8; //V
11 vo=v2*(1+Rf/R1)-(Rf/R1)*v1;
12 printf("The output voltage= %.1 f V" ,vo);

```

Scilab code Exa 14.4 Design an adder circuit using an op amp

```

1 //Design an adder circuit using an op amp
2 clear;
3 clc;
4 //soltion
5 //given
6
7 //Vo=-(V1+10*V2+100*V3)
8 Rf=100*10^3; //ohm
9 C1=1;           // coefficient of V1
10 C2=10;          // coefficient of V2
11 C3=100;         // coefficient of V3
12 R1=Rf/C1;
13 R2=Rf/C2;
14 R3=Rf/C3;
15 printf("R1 = %.0 f k \n" ,R1/1000);
16 printf("R2 = %.0 f k \n" ,R2/1000);
17 printf("R3 = %.0 f k \n" ,R3/1000);

```

Scilab code Exa 14.5 Calculate CMRR in dB

```
1 //Calculate CMRR in dB
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Ad=100;           //differential mode gain
8 Ac=0.01;          //common mode gain
9 CMRR=20*log10(Ad/Ac);
10 printf("The CMRR in dB %.0 f dB", CMRR);
```

Scilab code Exa 14.6 Calculate the output voltage

```
1 //Calculate the output voltage
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Ad=2000;           //differential mode gain
8 CMRR=10000;
9 V1=10^-3; //V
10 V2=0.9*10^-3; //V
11 Vd=V1-V2;
12 Vc=(V1+V2)/2;
13 Vo=Ad*Vd*(1+Vc/(CMRR*Vd));
14 printf("The output voltage is %.2 f mV", Vo*1000);
```

Chapter 15

Electronic Instruments

Scilab code Exa 15.1 Calculate shunt resistance and multiplying factor

```
1 //Calculate shunt resistance and multiplying factor
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Im=5*10^-3; //A
8 Rm=20; //ohm
9 I=5; //A
10 Rsh=Rm*Im/(I-Im);
11 n=I/Im;
12 printf("Shunt resistance= %.5f \n",Rsh);
13 printf("Multiplying factor= %.0f",n);
```

Scilab code Exa 15.2 Calculate shunt resistance

```
1 //Calculate shunt resistance
2 clear;
```

```

3  clc;
4 //soltion
5 //given
6
7 //At I= 1 mA
8 I1=1*10^-3; //A
9 Im=0.1*10^-3; //A
10 Rm=500; //ohm
11 Rsh=Rm*Im/(I1-Im);
12 printf("Shunt resistance= %.4f \n",Rsh);
13
14
15 //At I= 1 mA
16 I2=10*10^-3; //A
17 Rsh=Rm*Im/(I2-Im);
18 printf("Shunt resistance= %.4f \n",Rsh);
19
20
21 //At I= 1 mA
22 I3=100*10^-3; //A
23 Rsh=Rm*Im/(I3-Im);
24 printf("Shunt resistance= %.4f \n",Rsh);

```

Scilab code Exa 15.3 Caluclate the series resistance to convert it into voltmeter

```

1 //Caluclate the series resistance to convert it into
   voltmeter
2 clear;
3 clc;
4 //soltion
5 //given
6
7 Im=100*10^-6; //A
8 Rm=100; //ohm

```

```
9 V=100; //V
10 Rs=V/I_m-R_m;
11 printf("The value of series resistance is %.1f k ", 
    Rs/1000);
```

Scilab code Exa 15.4 Calculate multiplier resistance and voltage multiplying factor

```
1 //Calculate multiplier resistance and voltage
   multiplying factor
2 clear;
3 clc;
4 //soltion
5 //given
6
7 I_m=50*10^-6; //A
8 R_m=1000; //ohm
9 V=50; //V
10 Rs=V/I_m-R_m;
11 printf("The value of multiplier resistance is %.0f
      k \n",Rs/1000);
12 V_m=I_m*R_m;
13 n=V/V_m;
14 printf("Voltage multiplying factor =%.0f",n);
```

Scilab code Exa 15.5 Calculate reading and error of each voltmeter

```
1 //Calculate reading and error of each voltmeter
2 clear;
3 clc;
4 //soltion
5
```

```

6 function [z]=prll(r1,r2)//Function for the parallel
    combination of resistor
7     z=r1*r2/(r1+r2);
8 endfunction
9
10 //given
11
12 S_A=1000; // /V          //sensitivity
13 S_B=20000; // /V         //sensitivity
14 R=50; //V           //range of voltmeter
15 Vs=150; //V          //Supply
16 R1=100*10^3; //ohm
17 R2=50*10^3; //ohm
18 Vt=Vs*(R2/(R1+R2));
19
20 //Voltmeter A
21 Ri1=S_A*R;
22 Rxy_A=prll(Ri1,R2);      //total resistance at X and
    Y
23 V1=Vs*(Rxy_A/(Rxy_A+R1));
24 printf("The voltmeter indicates %.0 f V\n",V1);
25
26 //Voltmeter B
27 Ri2=S_B*R;
28 Rxy_B=prll(Ri2,R2);      //total resistance at X and
    Y
29 V2=Vs*(Rxy_B/(Rxy_B+R1));
30 printf("The voltmeter indicates %.2 f V\n",V2);
31
32 e1=(Vt-V1)*100/Vt;
33 e2=(Vt-V2)*100/Vt;
34 printf("The error in the reading of voltmeter A = %
    .0 f percent\n",e1);
35 printf("The error in the reading of voltmeter A = %
    .1 f percent",e2);

```

Scilab code Exa 15.6 Determine rms value of the ac voltage

```
1 //Determine rms value of the ac voltage
2 clear;
3 clc;
4 //soltion
5 //given
6
7 l=8.3; //cm           //length of the trace
8 D=5; // V/cm          //deflection sensitivty
9 Vpp=l*D;
10 Vrms=Vpp/(2*sqrt(2));
11 printf("The rms value of the ac voltage %.2f V",Vrms)


---


```

Scilab code Exa 15.7 Determine rms value and frequency of the sine voltage

```
1 //Determine rms value and frequency of the sine
  voltage
2 clear;
3 clc;
4 //soltion
5 //given
6
7 l=3.5; //cm           //length of the trace
8 D=2; // V/cm          //deflection sensitivty
9 Vpp=l*D;
10 Vrms=Vpp/sqrt(2);
11 printf("The rms value of the sine voltage = %.2f V\n",
         ,Vrms);
12 x=4; // cm            //one cycle length on x axis
```

```
13 t=0.5*10^-3; // s/cm      //timebase setting
14 T=x*t;
15 f=1/T;
16 printf("The frequency of the sine voltage = %.1f kHz
",f/1000);
```
