

Scilab Textbook Companion for
Electronic Devices and Circuits
by I. J. Nagrath¹

Created by
Ashutosh Kumar
B.Tech.
Computer Engineering
Dr. A.P.J. Abdul Kalam Technical University
College Teacher
None
Cross-Checked by
Chaitanya

July 11, 2017

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electronic Devices and Circuits

Author: I. J. Nagrath

Publisher: Prentice-hall Of India Pvt.ltd

Edition: 1

Year: 2007

ISBN: 9788120331952

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 SEMICONDUCTORS DIODE AND DIODE CIRCUITS	5
2 TRANSISTORS AND OTHER DEVICES	32
3 SMALL SIGNAL MODELS AMPLIFICATION AND BI-ASING	42
4 SMALL SIGNAL AMPLIFIERS FREQUENCY RESPONSE	71
5 Large Signals Amplifiers	97
6 Feedback Amplifiers And Oscillators	110
7 Operational Amplifiers	119
8 Multivibrators And Switching Regulators	130
9 Integrated Circuit Fabrication	139
10 Circuit Theory	142
11 Cathode Ray Oscilloscope	149

List of Scilab Codes

Exa 1.1	Example	5
Exa 1.2	Example	6
Exa 1.3	Example	6
Exa 1.4	Example	7
Exa 1.5	Example	8
Exa 1.6	Example	8
Exa 1.7	Example	9
Exa 1.9	Example	10
Exa 1.11	Example	11
Exa 1.12	Example	11
Exa 1.13	Example	12
Exa 1.14	Example	13
Exa 1.15	Example	14
Exa 1.16	Example	15
Exa 1.17	Example	17
Exa 1.18	Example	17
Exa 1.19	Example	18
Exa 1.20	Example	19
Exa 1.24	Example	20
Exa 1.25	Example	20
Exa 1.26	Example	22
Exa 1.27	Example	23
Exa 1.28	Example	23
Exa 1.29	Example	25
Exa 1.30	Example	27
Exa 1.32	Example	27
Exa 1.33	Example	28
Exa 1.34	Example	29

Exa 1.35	Example	30
Exa 1.36	Example	31
Exa 2.1	Example	32
Exa 2.2	Example	33
Exa 2.3	Example	34
Exa 2.4	Example	34
Exa 2.5	Example	35
Exa 2.7	Example	36
Exa 2.8	Example	36
Exa 2.10	Example	37
Exa 2.13	Example	38
Exa 2.14	Example	38
Exa 2.15	Example	39
Exa 2.16	Example	40
Exa 3.1	Example	42
Exa 3.2	Example	43
Exa 3.3	Example	43
Exa 3.4	Example	44
Exa 3.5	Example	45
Exa 3.6	Example	45
Exa 3.7	Example	46
Exa 3.8	Example	47
Exa 3.9	Example	48
Exa 3.10	Example	49
Exa 3.11	Example	51
Exa 3.12	Example	51
Exa 3.13	Example	52
Exa 3.14	Example	53
Exa 3.15	Example	55
Exa 3.16	Example	55
Exa 3.17	Example	56
Exa 3.18	Example	58
Exa 3.19	Example	59
Exa 3.20	Example	60
Exa 3.21	Example	61
Exa 3.22	Example	62
Exa 3.23	Example	64
Exa 3.24	Example	64

Exa 3.25	Example	65
Exa 3.26	Example	66
Exa 3.28	Example	67
Exa 3.29	Example	68
Exa 3.30	Example	69
Exa 3.31	Example	70
Exa 4.1	Example	71
Exa 4.2	Example	72
Exa 4.3	Example	72
Exa 4.4	Example	73
Exa 4.5	Example	74
Exa 4.6	Example	75
Exa 4.7	Example	76
Exa 4.8	Example	77
Exa 4.9	Example	78
Exa 4.10	Example	80
Exa 4.11	Example	82
Exa 4.12	Example	83
Exa 4.13	Example	83
Exa 4.14	Example	84
Exa 4.15	Example	85
Exa 4.16	Example	87
Exa 4.17	Example	88
Exa 4.18	Example	89
Exa 4.19	Example	91
Exa 4.21	Example	93
Exa 4.23	Example	95
Exa 5.1	Example	97
Exa 5.2	Example	98
Exa 5.3	Example	99
Exa 5.4	Example	100
Exa 5.5	Example	101
Exa 5.6	Example	102
Exa 5.7	Example	104
Exa 5.8	Example	105
Exa 5.9	Example	106
Exa 5.10	Example	107
Exa 5.12	Example	108

Exa 5.13	Example	109
Exa 6.1	Example	110
Exa 6.2	Example	111
Exa 6.3	Example	111
Exa 6.4	Example	112
Exa 6.5	Example	112
Exa 6.7	Example	113
Exa 6.8	Example	114
Exa 6.9	Example	115
Exa 6.10	Example	116
Exa 6.11	Example	117
Exa 6.12	Example	117
Exa 6.13	Example	118
Exa 7.1	Example	119
Exa 7.2	Example	120
Exa 7.3	Example	120
Exa 7.4	Example	121
Exa 7.6	Example	121
Exa 7.7	Example	122
Exa 7.8	Example	123
Exa 7.9	Example	124
Exa 7.10	Example	124
Exa 7.11	Example	125
Exa 7.14	Example	126
Exa 7.21	Example	127
Exa 7.22	Example	127
Exa 7.23	Example	128
Exa 8.1	Example	130
Exa 8.2	Example	131
Exa 8.3	Example	132
Exa 8.4	Example	133
Exa 8.5	Example	134
Exa 8.6	Example	135
Exa 8.7	Example	136
Exa 8.8	Example	137
Exa 9.2	Example	139
Exa 9.3	Example	140
Exa 9.4	Example	140

Exa 9.5	Example	141
Exa 10.1	Example	142
Exa 10.2	Example	142
Exa 10.3	Example	143
Exa 10.4	Example	144
Exa 10.5	Example	144
Exa 10.6	Example	145
Exa 10.7	Example	145
Exa 10.9	Example	146
Exa 10.10	Example	147
Exa 10.11	Example	148
Exa 11.2	Example	149
Exa 11.3	Example	150
Exa 11.4	Example	151

Chapter 1

SEMICONDUCTORS DIODE AND DIODE CIRCUITS

Scilab code Exa 1.1 Example

```
1 //Variable declaration
2 A=6.022*10**23 //avagadro's number(/m^3)
3 d=2.7*10**6 //density of aluminium conductor(
  g/m^3)
4 a=26.98 // atomic weight aluminium
  conductor(g/g-atom)
5 D=10**4. //current density(A/m^2)
6 e=1.6*10**-19 //electronic charge(C)
7
8 //Calculations
9 //Part a
10 n=A*d/a //number of atoms(n/m^3)
11
12 //Part b
13 u=D/(n*e) //drift velocity (m/s)
14
15 //Results
16 printf ("number of atoms per cubic meter is %.3f *
  10**28/m^3",n/10**28)
```

```
17 printf ( " drift velocity is %.2e m/s",u)
```

Scilab code Exa 1.2 Example

```
1 //Variable declaration
2 n=10**23 //number of electrons(n/m^3)
3 e=1.6*10**-19 //electronic charge(C)
4 u=0.4 //mobility(m^2/Vs)
5 a=10**-7 //cross sectional area(m^2)
6 l=15*10**-2 //conductor length(m)
7
8 //Calculations
9 //Part a
10 G=n*e*u //conductivity(S/m)
11
12 //Part b
13 R=1/(a*G) //resistance(ohm)
14
15 //Results
16 printf ("conductivity of the conductor is %.1e S/m",
17 G)
17 printf ("resistance of the conductor is %.1f ohm",R)
```

Scilab code Exa 1.3 Example

```
1 //Variable declaration
2 A=6.022*10**23 //avagadro's number
3 d=5.32*10**6 //density of Ge at 300k(g/m^3)
4 a=72.60 //atomic weight of Ge(g/g-atom)
5 e=1.6*10**-19 //electronic charge(C)
6 ni=2.4*10**19 //intrinsic concentration(electron-
7 hole pairs/m^3)
7 un=0.39 //electron mobility(m^2/V.s)
```

```

8 up=0.19          //hole mobility(m^2/V.s)
9
10 //Calculations
11 //Part a
12 nA=A*d/a        //number of atoms(nA/m^3) using
    avagadro's law
13 x=nA/ni         //Germanium atoms/electron hole
    pair
14
15 //Part b
16 g=(un+up)*e*ni  //intrinsic conductivity(S/m)
17 r=1/g           //intrinsic resistivity(ohm.m)
18
19 //Results
20 printf("the relative concentration of Ge and
    electron hole pairs is %.2e atoms/electron-hole
    pair",x)
21 printf("the intrinsic resistivity of Ge is %.3f ohm
    .m",r)

```

Scilab code Exa 1.4 Example

```

1 //Variable declaration
2 ni=1.5*10**16    //intrinsic concentration(electron-
    hole pairs/m^3)
3 n=4.99*10**28   //number of Si atoms(atoms/m^3)
4 un=0.13         //electron mobility(m^2/V.s)
5 up=0.05         //hole mobility(m^2/V.s)
6 e=1.6*10**-19  //electronic charge(c)
7
8 //Calculation
9 //Part a
10 g=e*ni*(un+up) //intrinsic conductivity(S/m)
11 r=1/g          //intrinsic resistivity(ohm.m)
12 Nd=n/10**8     //doped silicon(atoms/m^3)=nn,

```

```

    majority carriers
13 pn=ni**2/Nd      //minority carrier density(holes/m
    ^3)
14
15 //Part b
16 k=e*un*Nd      //conductivity(S/m)
17                //using Nd in place of nn as Nd=nn
18 rho=1/k        //resistivity(ohm.m)
19
20 //Results
21 printf ("the minority carrier density of Si is %.2e
    holes/m^3 ",pn)
22 printf ("the resistivity of Si is %.2e ohm.m",rho)

```

Scilab code Exa 1.5 Example

```

1
2
3 //Variable declaration
4 Vo=0.7          //contact potential(V)
5 Vf=0.4          //forward biasing voltage(V)
6
7 //Calculation
8 x=exp(-20*(Vo-Vf))/exp(-20*Vo) //increase in
    probability of majority carriers
9
10 //Result
11 printf ("increase in probability of majority
    carriers is %.f times",x)

```

Scilab code Exa 1.6 Example

1

```

2
3 //Variable declaration
4 I=10 //Ge diode carries current (mA)
5 V=0.2 //forward bias voltage (V)
6
7 //Calculation
8 //Part a
9 Is=I/(exp(40*V)-1) //reverse current (mA)
10
11 //part b
12 I1=1*10**3
13 V1=(log(1/3.355*10**3 + 1))/40 //voltage (V)
14 I2=100*10**-3 //current (mA)
15 V2=(log(100/3.355*10**3+1))/40 //voltage (V)
16
17 //Part c
18 Is1=4*Is //reverse saturation
    current doubles for every 10 degree celcius temp
    rise ,so for 20 degree rise it will be 4 timese/
19 x=37.44 //let x=e/kT
20 I3=Is1*(exp(x*V)) //current when temp doubles (mA)
21
22 //Results
23 printf ("the reverse current is %.3f mA",Is/1e-3)
    //incorrect units given in the textbook
24 printf ("bias voltages are %.3f V and %.3f V resp",
    V1,V2)
25 printf ("Is at 20 degree is %.2f uA and diode
    current at 0.2 V is %.2f mA",Is1/1e-3,I3)

```

Scilab code Exa 1.7 Example

```

1 //Variable declaration
2 V=3. //Voltage (V)
3 Req=300. //total resistance as per circuit(

```

```

    ohm)
4 Rfa=20           //forward resistance(ohm)
5 Vt=0.7          //Thevinine's voltage(V)
6 Rfb=0           //forward resistance(ohm)
7
8 //Calculations
9 //Part a
10 I=V/Req        //current(A)
11
12 //Part b
13 Id=(V-Vt)/Req  //diode current(mA)
14
15 //Part c
16 Rf=20           //forward resistance(ohms)
17 Id1=(V-Vt)/(Req+Rfa) //diode current(mA)
18
19 //Results
20 printf("current in this case is %.2f A",I)
21 printf("diode current is %.2f mA",(Id/1E-3))
22 printf("diode current is %.2f mA" ,(Id1/1E-3))

```

Scilab code Exa 1.9 Example

```

1 //Variable declaration
2 Vx=1.4           //voltage at point X(V)
3 Vt=0.7          //diode voltage(V)
4 Vcc=5           //cathode voltage(V)
5 R=1             //circuit resistance(ohm)
6 Vs=Vx-Vt       //supply voltage(V)
7
8 //Calculations
9 I1=(Vcc-Vt-Vs)/R //current through D1(mA) for 0<
    Vs<0.7
10 I2=0           //current through D2 and D3
11 I1=(Vcc-Vt-Vs)/R //for Vs>0.7 as D2 and D3

```

```

    conducts
12
13 // Results
14 printf (" I1 for 0<Vs<0.7 is %.1f mA" ,I1)
15 printf (" I2 for 0<Vs<0.7 is %.1f mA" ,I2)
16 printf (" I1 and I2 for Vs>0.7 is %.1f mA" ,I1)

```

Scilab code Exa 1.11 Example

```

1 //Variable declaration
2 Vz=100           //zener voltage (V)
3 Rz=25           //diode resistance (ohm)
4 I1=0.05         //load current (A)
5 Iz=0.01        //zener diode current (A)
6 Rs=250         //supply resistance (ohm)
7
8 // Calculations
9 V1=Vz+(Iz*Rz)   //load voltage (V)
10 Vs=V1+(I1+Iz)*Rs //supply voltage (V)
11 VL=V1*1.01     //increase in V1 (V)
12 IZ=(VL-Vz)/Rz //increase in zener current
13 VS=V1+(I1+IZ)*Rs //increase in supply voltage (V)
14 Vss=(VS-Vs)/Vs //%increase in supply voltage (V)
15 P=I1*VL        //power consumed (W)
16
17 // Results
18 printf ("load voltage is %.2f V" ,V1)
19 printf ("supply voltage is %.2f V" ,Vs)
20 printf ("increase in supply voltage is %.3f V" ,VS)
21 printf ("power consumed is %.2f W" ,P)

```

Scilab code Exa 1.12 Example


```

1 //Variable declaration
2 Vbb=5           //bias voltage(V)
3 Rl=1           //resistance(ohm)
4 Id=4.4         //from the figure(mA)
5
6 //Part a
7 i=Vbb/Rl       //load line intercepts the Id axis
   at i(mA)
8 Vl=Id*Rl       //load voltage(V)
9
10 //Part b
11 Vd=Vbb-Vl     //diode voltage(V)
12 P=Vd*Id       //power absorbed in diode(mW)
13
14 //Part c
15 Ida=1.42      //diode current(mA) for 2V
16 Idb=7.35      //diode current(mA) for 8V
17
18 //Part d
19 Idc=8.7       //diode current(mA) for Rl=0.5k ohm
20 Idl=2.2       //diode current(mA) for Rl=2k ohm
21
22 //Results
23 printf ("diode current is %.1f mA and voltage across
   the load is %.1f V", Id,Vl)
24 printf ("power absorbed in diode is %.2f mW",P)
25 printf ("diode current for Vbb=2V is %.2f mA and for
   Vbb=8V is %.2f mA",Ida,Idb)
26 printf ("diode current for Rl=0.5 kohm is %.1f mA
   and for Rl=2 kohm is %.1f mA",Idc,Idl)

```

Scilab code Exa 1.13 Example

```

1 //Variable declaration
2 T=300           //temperature(k)

```

```

3 Ig=100*10**-3      // current (mA)
4 Is=1*10**-9       // current (nA)
5 x=0.0259          // x=kT/e
6
7 // Calculations
8 Voc=x*log(Ig/Is+1) // as Voc=kT/e*ln((Ig/Is)+1)
   where ln((Ig/Is)+1)=18.42 after solving
9 Isc=Ig
10
11 // Result
12 printf ("for a solar cell Voc is %.3f V and Isc is %
   . f mA",Voc,Isc/1E-3)

```

Scilab code Exa 1.14 Example

```

1
2
3 //Variable declaration
4 Idc=0.1           //dc current(A)
5 Rf=0.5            //forward resistance(ohms)
6 Rl=20             //load resistance(ohm)
7 Rs=1              //secondary resistance of
   transformer(ohm)
8
9 //Calculations
10 //Part a
11 Vdc=Idc*Rl        //dc voltage(V)
12 Vm=(%pi/2)*(Vdc+Idc*(Rs+Rf)) //mean voltage(V)
13 Vrms=Vm/sqrt(2)   //rms value of voltage(V)
   )
14
15 //Part b
16 Pdc=Idc**2*Rl    //dc power supplied
   to the load
17

```

```

18 //Part c
19 PIV=2*Vm //PIV rating for each
    diode(V)
20
21 //Part d
22 Im=(%pi/2)*Idc //peak value of current(mA
    )
23 Irms=Im/sqrt(2) //rms value of current(A)
24 Pac=Irms**2*(Rs+Rf+Rl) //ac power input(W)
25
26 //Part e
27 eta=(Pdc/Pac)*100 //conversion
    efficiency
28
29 //Part f
30 Vr=((Rs+Rf)/Rl)*100 //voltage regulation(V
    )
31
32 //results
33 printf ("rms value of voltage is %.2f V",Vrms)
34 printf ("dc power supplied to load is %.1f W",Pdc)
35 printf ("PIV rating for each diode %.2f V",PIV)
36 printf ("ac input power is %.3f W",Pac)
37 printf ("conversion efficiency %.1f %%",eta)
38 printf ("voltage regulation %.1f %%",Vr)

```

Scilab code Exa 1.15 Example

```

1
2 //Variable declaration
3 Vt=1
4 V1=12
5 Vm=63.63 //peak voltage(V) as
    Vm=sqr root of 2*45
6 Idc=8. //charging current(A)

```

```

7
8 // Calculations
9 // Part a
10 theta1= asind((Vt+Vl)/Vm)
11 theta2=180-theta1
12 //Rl=((2*Vm*cos(theta1))-(2*(%pi-2*theta1)*(Vt+Vl)))/
    /(Idc*%pi)
13 Rl=(2*sqrt(2)*45*cosd(11.8) - (2*(%pi-2*0.206)*(Vt+
    Vl)))/(Idc*%pi)
14
15 function ans = ft(wt)
16     ans =((((sqrt(2)*45*sin(wt))-(Vt+Vl))/Rl)*wt)
    **2)
17 endfunction
18 // Part b
19 integ = intg(theta1,theta2,ft)
20 disp ( integ)
21 Irms = (integ/%pi)**0.5
22 Pl=Irms**2*Rl //power loss in
    resistance (W)
23
24 // Part c
25 P=Vl*Idc //power supplied to
    battery (W)
26
27 // results
28 printf (" Resistance to be added is %.2 f Ohms" ,R1)
29 printf (" power supplied to battery is %.f W" ,P)

```

Scilab code Exa 1.16 Example

```

1
2
3 // Variable declaration
4 Rf=5 //forward resistance (ohms)

```

```

5 Vo=20 //output voltage(V)
6 Rs=10 //secondary resistance of
   transformer(ohm)
7
8 //Calculations
9 //Part a
10 Idc=0.1 //dc current(A)
11 Vm=Vo*(sqrt(2)) //mean voltage(V)
12 Vdc=(2*Vm/(%pi))-Idc*(Rs+2*Rf) //dc voltage(V)
13
14 //Part b
15 Idc1=0.2 //full load dc current(A)
16 Vdc2=((2*(sqrt(2))*Vo)/(%pi))-Idc1*(Rs+2*Rf) //full
   load dc voltage(V)
17 Rl=Vdc2/Idc1 //load resistance(ohm)
18 x=((2*Rf+Rs)/Rl)*100 //% regulation
19
20 //Part c
21 Idc=0.2 //dc current(A)
22 Im=(%pi)*Idc/2 //peak current(mA)
23 Ilrms=Im/sqrt(2) //rms current(mA)
24 Vlrms=Ilrms*Rl //load rms voltage(V)
25
26 //Part d
27 Vldc=14 //load dc
   voltage(V)
28 Vlacrms=sqrt(Vlrms**2-Vldc**2) //rms value of ac
   component(V)
29
30 //Results
31 printf("dc voltage %.f V",Vdc)
32 printf("regulation is %.2f %%",x)
33 printf("rms value of output voltage at dc load
   current is %.2f V",Vlrms)
34 printf("rms value of ac component of voltage %.2f V
   ",Vlacrms)

```

Scilab code Exa 1.17 Example

```
1 //Variable declaration
2 Vh=60.           //higher output voltage(V)
3 Vl=45.           //lower output voltage(V)
4 fz=50.           //frequency(Hz)
5 Vr=15.           //peak to peak ripple voltage(V)
6 Rl=600.          //resistance(ohms)
7
8 //Calculations
9 Vldc=(Vh+Vl)/2   //avg load dc voltage(V) as voltage
                   drops from 60 to 45
10 Idc=Vldc/Rl     //dc current(A)
11 T=1/fz          //discharging time(ms)
12 C=(Idc*T)/Vr    //linear discharge rate(uF)
13 C1=C*2          //new capacitance(uF)
14
15 Vr1 = (20*120*1000)/(1200*254)
16 Idc1=(Vh-(Vr1/2))/Rl           //dc load current
                                   (mA)
17
18 //Results
19 printf ("value of capacitance is %.f uF",C/1E-6)
20 printf ("Vr1 is %d V" ,Vr1)
21 printf ("dc load current Idc is %.f mA",Idc1/1E-3)
22 printf("Note : Answer may be vary because of
         rounding off error.")
```

Scilab code Exa 1.18 Example

```
1
2
```

```

3 //Variable declaration
4 Vdc=30 //dc voltage(V)
5 V1=220 //source voltage(V)
6 f=50 //frequency(Hz)
7 R1=1000 //load resistance(k
    ohms)
8 Vr = 15
9
10 //Calculations
11 C=100/f*R1 //as Vdc/Vr=100
12 Vm=Vdc+0.01*(30/2) //peak voltage(
    V)
13 V2=Vm/(sqrt(2)) //secondary voltage(V)
14 r=V1/V2 //transformer turn
    ratio
15
16 //Results
17 printf ("capacitor filter is %.f uF",C)
18 printf ("transformer turn ratio is %.2f",r)

```

Scilab code Exa 1.19 Example

```

1
2
3 //Variable declaration
4 Idc=60*10**-3 //dc current(A)
5 Vm=60 //peak volage(V)
6 f=50 //frequency(Hz)
7 C=120*10**-6 //capacitance(F)
8
9 //Calculations
10 //Part a
11 Vrms=Idc/(4*(sqrt(3))*f*C*Vm) //rms voltage(V)
12 Vr=2*(sqrt(3))*Vrms //ripple factor(V)
13

```

```

14 //Part b
15 Vdc=Vm-(Vr/2) //by simplifying
16 Vdc = 57.6 // V
17 //Part c
18 r=(Vrms/Vdc)*100 //ripple factor
19
20 //Results
21 printf ("ripple factor is %.3f Vdc",Vr)
22 printf ("dc voltage is %.1f V",Vdc)
23 printf ("ripple factor %.3f %%",r)

```

Scilab code Exa 1.20 Example

```

1
2
3 // Calculations
4 //Part a
5 //      200*1.141      4
6 //v1(t)=-----(1- cos628t)
7 //      3.14      3
8 //      200*1.141      800*1.141
9 //v2(t)=----- - ----- cos(628t+<(V2/V1
10 //      3.14      3*3.14
11 //
12 //V2/V1|w=0 =0.8;V2/V1|w=628 =6.43*10^-4 <V2/V1|w
13 //      =628 =180
14 //v2(t)=72.02+0.0538 cos628t
15
16 //Part b
17 vrms=0.0538
18 vdc=sqrt(2)*72.02
19 r=vrms/vdc
20

```



```
21 //Results
22 printf ("ripple factor is %.2e",r)
```

Scilab code Exa 1.24 Example

```
1
2
3 //Variable declaration
4 Vz=2 //zener voltage(V)
5 r1=10 //resistance after reducing
   circuit by thevinin(ohms)
6 r2=20 //resistance after reducing
   circuit by thevinin(ohms)
7 V1=7.5 //voltage after circuit
   reduction(V)
8 V2=15 //voltage after circuit
   reduction(V)
9 Rz=100/3 //zener resistance(ohms)
10
11 //Calculations
12 Vab=V2-(((V2-V1)/(r1+r2))*r2) //thevinin
   voltage at ab(V)
13 Rth=(Vab*r2)/(Vab+r2) //thevinin
   resistance at ab(ohms)
14 Vd=Vab-Vz //diode
   voltage(V)
15 Id=Vd/(Rth+Rz) //diode
   current(A)
16
17 //Results
18 printf ("diode current is %.2 f A",Id)
```

Scilab code Exa 1.25 Example

```

1 //Variable declaration
2 Vd=0.7 //diode voltage(V)
3 Ro=18 //output resistance(k
    ohms)
4 R1=2 //diode1 resistance(k
    ohms)
5 R2=2 //diode2 resistance(k
    ohms)
6
7 //Calculations
8 //Part a
9 V1=10 //voltage to D1(V)
10 V2=0 //voltage to D2(V)
11 Io=(V1-Vd)/(R1+Ro) //output current (mA)
12 Vo=Io*Ro //output voltage (V)
13
14 //Part b
15 V1=5 //voltage to D1(V)
16 V2=0 //voltage to D2(V)
17 Io=(V1-Vd)/(R1+Ro) //output current (mA)
18 Vo1=Io*Ro //output voltage (V)
19
20 //Part c
21 V1=10 //voltage to D1(V)
22 V2=5 //voltage to D2(V)
23 Vo=8.37 //as D1 only conducts ,so ,
    Vo is same as in part a
24 Vd1=V2-Vo //assume D1 conducts
25 Vo2=8.37 //D2 does not conduct as
    as Vd1 is negative
26
27 //Part d
28 V1=5 ; V2=5 //voltage to D1 and D2(
    V)
29 Id1=(V1-Vd-Vo)/2 //diode1 current (mA)
30 Io=Vo/Ro //output current (mA)
31 Vo3=(Ro*(V1-Vd))/(Ro+1) //output voltage (V)
32

```

```

33 printf ("a)output voltage is %.2f V" ,Vo)
34 printf ("b)output voltage is %.2f V" ,Vo1)
35 printf ("c)output voltage is %.2f V" ,Vo2)
36 printf ("d)output voltage is %.2f V" ,Vo3)

```

Scilab code Exa 1.26 Example

```

1 //Variable declaration
2 Vs=10. //supply voltage(V)
3 Rs=1 //supply resistane(ohm)
4 Vl=10. //load voltage(V)
5 Vi=50. //nput voltage(V)
6 Iz=32 //zener diode current(
    mA)
7 Is=40 //supply current(mA)
8
9 //Calculations
10 //Part a (Rl is min when Iz=0)
11 Is=(Vi-Vs)/Rs //source current(mA)
12 Rlmin=Vl/(Vi-Vs) //load resistance
    minimum(ohm)
13
14 //Part b(Rl is maximum when Iz=32 mA)
15 Il=(Is-Iz)*10**-3 //load current(A)
16 Rlmax=Vl/Il //maximum load resistance
    (k ohms)
17 P=Vl*Iz //max diode wattage
    consumed(mW)
18
19 //Results
20 printf ("Range of Rl is %.2f ohm to %.2f k ohm" ,(
    Rlmin/1E-3),(Rlmax/1E+3))
21 printf (" Il = %.e A",Il)
22 printf ("max power consumed is %.f mW",P)

```

Scilab code Exa 1.27 Example

```
1 //Variable declaration
2 Vz=20 //zener voltage(V)
3 Izmax=50 //maximum zener current(mA)
4 Rz=0 //zener resistance(ohms)
5 Rl=2. //load resistance(ohm)
6 Vl=20. //as Vz=Vl(V)
7 Rs=0.25 //source resistance(k ohms)
8
9 //Calculations
10 //Part a
11 Il=Vl/Rl //load current(mA)
12 Vsmin=(Rs+Rl)*Il //as Iz is floating so Iz=0
13
14 //Part b
15 Is=Izmax+Il //source current(mA)
16 Vsmax=Vz+(Is*Rs) //maximum source voltage(V)
17
18 //Results
19 printf ("Vsmin %.1f V",Vsmin)
20 printf ("Range of input voltage is %.1f to %.1f V",
    Vsmin, Vsmax)
```

Scilab code Exa 1.28 Example

```
1 //Variable declaration
2 Ilmax=100 //load maximum current(mA)
3 Ilmin=0 //load minimum current(mA)
4 Rz=0.05 //zener diode resistance(
    ohms)
```

```

5  Rs=10.                //source resistance(k ohms
   )
6  Vl=16.015            //load voltage(V)
7  Vl1=16.              //nominal load voltage(V)
8  Vs=20                //source voltage(V)
9  Vz=16                //zener diode voltage(V)
10
11 // Calculations
12 //Case 1 (i)
13 Iz=(Vl-Vl1)/Rz       //zener current(mA)
14 Is=Iz+Ilmax          //supply current(A)
15
16 //Case 1 (ii)
17 Is1=(Vs-Vz)/(Rs+Rz)  //supply current(mA)
18 Vl2=Vl1+(Is1*Rz)     //voltage(V)
19 Vr=((Vl2-Vl)/Vl1)*100 //voltage regulation
20
21 //Case 2 (i)
22 Vs=18                //supply voltage(V)
23 Ilmax=0.1            //load current max(A)
24 Vl=16.005           //load voltage(V)
25 Iz=(Vl-Vl1)/Rz       //zener current(mA)
26 Is2=Ilmax+Iz         //supply current(A)
27
28 //Case 2 (ii)
29 Ilmin=0
30 Iz1=(Vs-Vl1)/(Rs+Rz) //minimum diode current(
   mA)
31 Vl=Vl1+(Iz*Rz)       //load voltage at Ilmin(
   V)
32
33 //Part a
34 //Variable declaration
35 Is=0.4                //supply current(A)
36 Vs=20                //supply voltage(V)
37 Vl=16.015            //load voltage(V)
38 Iz=0.3                //zener current(mA)
39

```

```

40 // Calculations
41 P=Is**2*Rs //power dissipated by Rs(W)
42
43 //Part b
44 Pd=Vl*Iz //power dissipated (W)
45 Po=(Vs**2)/Rs //output power(W)
46
47 printf ("maximum power dissipated by Rs is %.1f W",P
)
48 printf ("maximum power dissipated by diode is %.3f W
",Pd)
49 printf ("minimum diode current is %.3f A",Iz1)
50 printf ("voltage regulation is %.2f %%",Vr)
51 printf ("output shorted will be %.1f W",Po)

```

Scilab code Exa 1.29 Example

```

1
2
3 //Variable declaration
4 Vrms=20 //secondary voltage(V)
5 Rs=10 //Winding resistance(ohm)
6 Rf=5 //diode has forward
resistance(ohms)
7 Idc=2*10**-3 //load current(mA)
8
9 //Calculations
10 //Part a
11 Vdc=(Vrms*(sqrt(2)))/(%pi) //no load Vdc
12
13 //Part b
14 Vldc=Vdc-(Idc*(Rs+Rf)) //dc
output voltage when load is 20mA
15
16 //Part c

```

```

17 Rl=Vldc/Idc //load
    resistance(ohms)
18 r=((Rs+Rf)/Rl)*100 //
    percentage regulation(%)
19
20 //Part d
21 Im=Idc*(%pi) //peak
    current(mA)
22 Ilrms=Im/2 //rms
    load current(mA)
23 Vlrms=Ilrms*Rl //rms
    load voltage(V)
24 Vlrmsac=sqrt((Vlrms**2)-(Vldc**2)) //Ripple
    voltage rms(V)
25 f=50*2 //rippLe
    frequency(Hz)
26
27 //Part e
28 eta=((2*(%pi)**2)/(1+((Rs+Rf)/Rl)))*100 //
    efficiency
29
30 //Part f
31 PIV=Vrms*(sqrt(2)) //peak
    inverse voltage(V)
32 Vm= PIV
33 //Results
34 printf("no load dc voltage is %.f V",Vdc)
35 printf("dc output voltage when the load is drawing
    20 mA is %.2f V",Vldc)
36 printf("percentage regulation at this load is %.2f
    %%", (r/1E-1))
37 printf("ripple voltage rms is %.2f V and ripple
    frequency is %.f Hz",Vlrmsac,f)
38 printf("power conversion efficiency is %.1f %%", (
    eta/1E+2))
39 printf("PIV is %.f V",PIV)

```

Scilab code Exa 1.30 Example

```
1
2
3 //Variable declaration
4 V1=24 //battery voltage(V)
5 Vm=60*(sqrt(2)) //peak voltage(V)
6 Ip=2.5 //peak current(A)
7 c=20 //charge(Ah)
8
9 //Calculations
10 //Part a
11 theta=asin(V1/Vm) //angle at which conduction
    begins
12 Rs=(Vm-V1)/Ip //source resistance(ohms)
13
14 //Part b
15 Idc=(Vm/(%pi)*Rs)*(cos(theta))-(((%pi)-(2*theta))/2*
    %pi)*(V1/Rs) //load current(A)
16 T=c/Idc
    //time to deliver 20Ah(h)
17
18 //Results
19 printf ("resistance connected in series is %.1f ohm"
    ,Rs)
20 printf ("time required to deliver a charge of 20 Ah
    is %.1f h", (T/1E-3))
21 printf ("Idc %.2f A", (Idc/1E+3))
```

Scilab code Exa 1.32 Example


```

1
2
3 //Variable declaration
4 R=25. //external resistance(ohms)
5 Vm=200. //peak value of voltage(V) as
    vs=200 sinwt
6 Rf=50. //forward resistance(ohms)
7
8 //Calculations
9 //Part a
10 Id=Vm/(2*Rf+R) //diode current(peak)
11
12 //Part b
13 Idc=(2*Id)/%pi //dc current(A)
14
15 //Part c
16 PIV=Vm/2 //peak value of voltage
    across D1
17 PIVac=100/%pi //average value of voltage across
    D1
18
19 //Part d
20 Im=Id //peak value of current(A)
21 Irms=Im/(sqrt(2)) //rms value of current(A)
22
23 //Results
24 printf ("peak value of current is %.1f A",Id)
25 printf ("dc current is %.2f A",Idc)
26 printf ("across D1 are peak voltage is %.1f V and
    average voltage is %.1f V",PIV,PIVac)
27 printf ("Irms is %.2f A",Irms)

```

Scilab code Exa 1.33 Example

1

```

2
3 //Variable declaration
4 f=50. //frequency (Hz)
5 dv=7. //difference between maximum and
    minimum(25-18) voltages across the load (V)
6 Ic=100. //load current (mA)
7
8 //Calculations
9 dt=1/(2*f) //time of discharge (seconds)
10 C=Ic/(dv/dt) //capacitance (uF)
11
12 //Results
13 printf ("value of capacitor is %.2 f uF" ,(C/1E-3))

```

Scilab code Exa 1.34 Example

```

1
2
3 //Variable declaration
4 Vr=10. //peak to peak
    ripple voltage (V)
5 Vm=50. //peak output
    voltage (V)
6 C=300. //Capacitance (uF)
7 Rl=470. //load resistance (
    ohms)
8 f=50. //frequency (Hz)
9
10 //Calculations
11 //Part a
12 Vdc=Vm-(Vr/2) //dc voltage (V)
13 C=Vdc/(f*Vr*Rl) //capacitance (mF)
14
15 //Part b
16 C1=300*10**-6 //capacitance is

```

```

    increased (uF)
17 Vr=2*Vm/((2*f*C1*R1)+1)
18 Vdc=Vm-Vr/2 //load voltage
    ripple (V)
19 Idc=Vdc/R1 //average load
    current (mA)
20
21 // Results
22 printf ("value of capacitor is %.1f mF", (C/1E-6))
23 printf ("load voltage ripple is %.2f V and average
    load current is %.1f mA", Vdc, (Idc/1E-4))

```

Scilab code Exa 1.35 Example

```

1
2
3 // Variable declaration
4 vo=7.5 //instantaneous voltage (V)
5 R1=15 //resistance (k ohms)
6 Von=0.5 //voltage of diode when on (V
    )
7
8 // Calculations
9 Rth=(R1*vo)/(R1+vo) //equivalent
    resistance (V)
10 T=2*(%pi)/10**4 //time period (ms)
11 t1=(asin(Von/2.5))/10**4 //timings when D1
    conducts (ms)
12 t2=(T/2)-t1
13
14 // Results
15 printf ("time period is %.3f ms", (T/1E-3))
16 printf ("t1 is %.3e ms", t1)
17 printf ("t2 is %.3f ms", (t2/1E-3))

```

Scilab code Exa 1.36 Example

```
1
2
3 //Variable declarations
4 v=12 //output voltage(V)
5 vm=20. //peak voltage(V)
6 v1=8 //output voltage(V) for
    negative half cycle
7 vm1=20. //peak voltage(V) for
    negative half cycle
8
9 //Calculations
10 t1=(asin(v/vm))/10**4 //for positive half
    cycle when D1 conducts
11 t2=(0.1*%pi)-t1/1e-3
12 t3=(asin(v1/vm1))/10**4 //for negative half
    cycle when D2 conducts
13 t4=(0.1*(%pi))+t3/1e-3
14 t5=(0.2*(%pi))-t3/1e-3
15
16 //Results
17 printf ("t1 is %.3 f ms",t1/1e-3)
18 printf ("t2 is %.2 f ms",t2)
19 printf ("t3 is %.3 f ms",t3/1e-3)
20 printf ("t4 is %.3 f ms",t4)
21 printf ("t5 is %.3 f ms",t5)
22 printf ("vo is -5.33+6.66*sin(10**4*.15)")
```

Chapter 2

TRANSISTORS AND OTHER DEVICES

Scilab code Exa 2.1 Example

```
1 //Variable declaration
2 Rb=200 //base resistance(ohm)
3 Vbe=0.7 //base emitter voltage drop(
  V) in active region
4 Vbb=5 //base voltage of bipolar
  transistor(V)
5 beeta=100 //current gain
6 Rc=3 //collector resistance(k
  ohms)
7 Vcc=10 //voltage given to the
  collector(V)
8
9 //Calculations
10 Ib=(Vbb-Vbe)/Rb //base current(mA)
11 Ic=beeta*Ib //collector current(mA)
12 Vcb=-Vbe-(Rc*Ic)+Vcc //collector base voltage
  drop(V)
13
14 //Results
```

```

15 printf ("Base current Ib = %.4f mA",Ib)
16 printf ("Collector current Ic = %.2f mA",Ic)
17 printf ("Reverse bias collector junction Vcb = %.2f
    V",Vcb)

```

Scilab code Exa 2.2 Example

```

1 //Variable declaration
2 Vbb=5 //base voltage of bipolar
    transistor(V)
3 Vbe=0.7 //base emitter voltage drop(V)
    in active region
4 Rb=150 //base resistance(ohm)
5 beeta=125 //curret gain
6 Rc=3 //collector resistance(k ohms)
7 Vcc=10 //supply voltage(V)
8 Vce=0.2 //collector to emitter voltage(V)
    )
9
10 //Calculations
11 //Part a
12 Ib=(Vbb-Vbe)/Rb //base current(mA)
13 Ic=beeta*Ib //collector current(mA)
14 Vcb=-Vbe-(Rc*Ic)+Vcc //collector base voltage drop(
    V)
15
16 //Part b -for npn transistor
17 Vbe=0.8 //base emitter voltage drop(V)
    in saturation
18 Ic=(Vcc-Vce)/Rc //collector current(mA)
19 Ib=(Vbb-Vbe)/Rb //base current(mA)
20 Ibmin=Ic/beeta //minimum base current(mA) to go
    into saturation(mA)
21
22 //Results

```

```

23 printf ("In active region , base current is %.1e mA
    and collector current is %.2f mA" ,Ib,Ic)
24 printf ("base current and collector current in npn
    are %.2e mA and %.2f mA resp." ,Ib,Ic)
25 printf ("base current minimum is %.3f mA" ,Ibmin)

```

Scilab code Exa 2.3 Example

```

1 //Variable declaration
2 Vbb=5 //base voltage of bipolar
    transistor (V)
3 Vbe=0.7 //base emitter voltage drop (V)
    in active region
4 Rb=50 //base resistance (ohm)
5 beeta=50 //current gain
6 Re=1.8 //emitter resistance (k ohms)
7 Vcc=10 //supply voltage (V)
8 Vce=0.2 //collector to emitter voltage
    (V)
9
10 // Calculations
11 Ib=(Vbb-Vbe)/(Rb+Re*(beeta+1)) //base current (
    mA)
12 Ic=beeta*Ib //collector
    current (mA)
13 Ie=Ib+Ic //emitter
    current (mA)
14
15 // Results
16 printf ("values are Ib: %.2f mA, Ic: %.2f mA and Ie
    : %.2f mA" ,Ib,Ic,Ie)

```

Scilab code Exa 2.4 Example

```

1 //Variable declaration
2 Vbe=0.7 //base to emitter
   voltage (V)
3 Rb=250 //base resistance(k
   ohms)
4 Vcc=10 //supply voltage(V)
5 Rl=0.5 //load resistance(k
   ohms)
6
7 // Calculations
8 Ic=Vcc/Rl //collector current(mA)
9 IbQ=(Vcc-Vbe)/Rb //Ib at operating point
   (uA)
10 IcQ=8 //Ic at operating point
   (mA)
11 VceQ=6 //Vce at operating
   point (V)
12
13 //Results
14 printf (" values are IbQ : %.4f uA,IcQ: %.f mA and
   Vcc : %.f V",IbQ,IcQ,Vcc)
15 printf (" collector current Ic is %d mA and output
   voltage ,vL=6-2 sinwt V",Ic)

```

Scilab code Exa 2.5 Example

```

1 //Variable declaration
2 Vgs=12 //gate to source voltage(V)
3 Vt=4 //threshold voltage(V)
4 Id=12.8 //drain current(mA)
5 K=0.0002 //device parameter
6 Vdd=24 //drain voltage(V)
7 Vds=8 //drain to source voltage(V)
8 Vgs=8
9

```



```

10 // Calculations
11 Id=K*((Vds-Vt)^2) //drain current at Vds=8V
12 Rd=(Vdd-Vds)/Id //drain resistance(k ohms)
13
14 //Result
15 printf ("diode resistance is %.f ohms",Rd)

```

Scilab code Exa 2.7 Example

```

1 //Variable declaration
2 Vds=7.5 //drain to source voltage(V)
3 Id=5 //drain current(mA)
4
5 //Calculations
6 Vgs=-1.5 //gate to source voltage(V)
7 Vgg=-Vgs //gate voltage=gate to source
    voltage(V)
8
9 //Result
10 printf ("gate voltage is %.1f V",Vgg)

```

Scilab code Exa 2.8 Example

```

1 //Variable declaration
2 Vds=7.5 //drain to source voltage(V)
    )
3 Idss=8. //drain current for Vgs(V)
4 Vgs=2. //gate to source voltage(V)
5 Vp=4. //peak voltage(V)
6
7 //Calculations
8 Id=Idss*((Vp-Vgs)/Vp)**2 //drain current(mA)
9

```

```

10 //Result
11 printf ("diode current is %.1f mA",Id)

```

Scilab code Exa 2.10 Example

```

1 //Variable declaration
2 beeta=160 //current gain
3 Vee=10 //emitter voltage(V)
4 Rb=400 //base resistance(k ohms)
5 Veb=0.8 //emitter to base voltage(V)
6 Re=2.5 //emitter resistance(k ohms)
7 Rc=1.5 //collector resistance(k
    ohms)
8
9 //Calculations
10 //Part a
11 Ib=(Vee-Veb)/((Re*(1+beeta))+Rb) //base current(
    uA)
12 Ic=beeta*Ib //collector
    current(mA)
13 Ie=(beeta+1)*Ib //emitter
    current(mA)
14 Vce=Vee-(Re*Ie)-(Rc*Ic) //emitter to
    collector voltage(V)
15 Vce=-Vce //collector to
    emitter voltage(V)
16
17 //Part b
18 beeta=80 //current gain
19 Ib1=(Vee-Veb)/((Re*(1+beeta))+Rb) //base current(
    uA)
20 Ic1=beeta*Ib1 //collector
    current(mA)
21 Ie1=(beeta+1)*Ib1 //emitter
    current(mA)

```

```

22 Vce1=-(Vee-(Ie1*Re)-(Rc*Ic1))           //collector to
    emitter voltage(V)
23
24 //Result
25 printf (" collector current and Vce for beeta=160 are
    %.2f mA and V" ,Ic,Vce)
26 printf (" Ic and Vce for beeta=80 are %.2f mA and V" ,
    Ic,Vce1)

```

Scilab code Exa 2.13 Example

```

1
2 //Variable declaration
3 K=2                               //device parameter
4 Rd=2.5*10**3                       //drain resistance(k ohms)
5 Rs= Rd
6 R1=100*10**3                       //resistance(ohms)
7 R2=200*10**3                       //resistance(ohms)
8 Vdd=12                             //drain voltage(V)
9 Vt=4                               //threshold voltage(V)
10
11 //Calculations
12 Vgg=(R2*Vdd)/(R1+R2)
13 syms Id
14 expr=solve([Id**2-3.28*Id+2.56],[Id])
15 disp(expr)
16 Id=1.28
17 Vds=Vdd-5*Id
18
19 //Result
20 printf (" Id is %.2f mA and Vds is %.1f V" ,Id,Vds)

```

Scilab code Exa 2.14 Example

```

1 //Variable declaration
2 k=2. //device parameter
3 Vt=-1. //threshold voltage(V)
4 Vdd=-12. //drain voltage(V)
5 R1=300. //resistance (kohms)
6 R2=100. //resistance (kohms)
7
8 //Calculations
9 //Part a
10 Vgs=-2 //gate to source voltage(V)
11 Vgg=(R2*Vdd)/(R1+R2) //gate voltage(V)
12 Id=k*((Vgs-Vt)**2) //drain current(mA)
13 Rs=(Vgs-Vgg)/Id //source resistance(k ohms)
    as Id=Is ,Kvl in GS loop
14 Is=Id
15
16 //Part b
17 Vds=-4 //drain to source voltage(
    V)
18 Rd=(-Vdd+Vds-(Is*Rs))/Id //applying kvl in DS loop
19
20 //Part c
21 Vt=-1.5 //threshold voltage(V)
22 Vgg=-1.5 //gate voltage using Id
    formula
23 R2new=(Vgg*R1)/(Vdd-Vgg) //new resistance(k ohms
    )
24
25 //Results
26 printf ("a)source resistance is %.1f kohm",Rs)
27 printf ("b)drain resistance is %.1f kohm",Rd)
28 printf ("c)R2new is %.2f kohm",R2new)

```

Scilab code Exa 2.15 Example

```

1
2
3 //Variable declaration
4 Vp=-4 //peak voltage(V)
5 Idss=10 //drain current for Vgs(V)
6 Vdd=18 //drain voltage(V)
7 Rs=2 //source resistance(ohms)
8 Rd=2 //drain resistance(ohms)
9 R1=450*10**3 //resistance(ohms)
10 R2=90*10**3 //resistance(ohms)
11
12 //Calculations
13 Vgg=(R2*Vdd)/(R1+R2)
14 syms Id
15 expr=solve([20*Id**2-148*Id+245],[Id])
16 disp(expr)
17 Id1=2.5
18 Vds=Vdd-((Rs+Rd)*Id1)
19
20 //Result
21 printf("Id is %.1f mA and Vds is %.1f V",Id1,Vds)

```

Scilab code Exa 2.16 Example

```

1
2
3 //Variable declaration
4 Vp=4 //peak voltage(V)
5 Idss=12. //drain current for Vgs(V)
6 Vdd=12 //drain voltage(V)
7 Id=4. //drain current(mA)
8 Vds=6 //drain to source voltage(V)
9
10 //Calculations
11 Rs=(Vp/4)*(1-(sqrt(Id/Idss))) //by Id=Idss(1-(

```

```
    Vgs/Vp))^2 and putting Vgs=4Rs in it and solving
12 Rd=((Vdd+Vds)/Id)-Rs //solving
    equation -Vdd-Vds+(Id*(Rd+Rs))=0
13
14 //Result
15 printf ("source resistance is %.2f kohm",Rs)
16 printf ("drain resistance %.2f kohms",Rd)
```

Chapter 3

SMALL SIGNAL MODELS AMPLIFICATION AND BIASING

Scilab code Exa 3.1 Example

```
1 //Variable declaration
2 beeta=100           //current gain
3 Ic=2.5             //collector current (mA)
4 Io=-0.5            //output current (mA)
5 Rl=2.5             //load resistance (kohm)
6
7 //Calculations
8 rpi=beeta*(25/Ic)  //dynamic resistance (ohms)
9 Ib=Io/(-beeta)     //as Io=-beeta*Ib
10 Vs=rpi*Ib         //signal voltage (V)
11 Vo=Rl*Io          //output voltage (V)
12 Av=Vo/Vs          //voltage gain
13 Ai=Io/Ib          //current gain
14
15 //Results
16 printf ("signal voltage is %.1f mV",Vs)
17 printf ("current gain is %.1f",Ai)
```

```
18 printf ("voltage gain is %.f",Av/1E-3)
```

Scilab code Exa 3.2 Example

```
1
2
3 //Variable declaration
4 Id=1.6 //drain current(mA)
5 Vgs=-3 //gate to source voltage(V)
6 Id1=.4 //drain current(mA)
7 Vgs1=-4 //gate to source voltage(V)
8 Vp=-5 //peak voltage(V) by solving
    equations 1.6=Idss(1+3/Vp)^2 and .4=Idss(1+4/Vp)
    ^2
9 Idss=10 //small signal drain current(mA
    ) by solving equations 1.6=Idss(1+3/Vp)^2 and .4=
    Idss(1+4/Vp)^2
10
11 //Calculations
12 gmo=-(2*Idss)/Vp //transconductance(
    mS)
13 gm=gmo*(sqrt(Id/Idss)) //transconductance(uS)
14 gm1=gmo*(sqrt(Id1/Idss)) //transconductance(uS)
15
16 //Results
17 printf ("Idss and Vp are %.f mA and %.f V",Idss,Vp)
18 printf ("gmo is %.f mS",gmo)
19 printf ("gm at Id is %.f gm at Id1 is %.f uS",gm/1E
    -3,gm1/1E-3)
```

Scilab code Exa 3.3 Example

```
1 //Variable declaration
```



```

2 gm=1600          //gm(us)
3 rd=50           //resistance(kohms)
4 Rl=5            //load resistance(kohms)
5
6 //Calculations
7 Av=-gm*Rl       //Vgs=Vs from circuit model
8                 //Vo=-(gm*Vgs)*Rl
9                 //as Av=Vo/Vs=-gm*Rl
10
11 //Result
12 printf("voltage gain of the circuit is %.f",Av/1E
        +3)

```

Scilab code Exa 3.4 Example

```

1 //Variable declaration
2 beta=100.        //current gain
3 rpi=2*10**3      //dynamic resistance(ohms)
4 rx=500           //resistance(ohms)
5 ro=250*10**3     //output resistance(ohms)
6 R1=50*10**3      //resistance(k ohms)
7 R2=10*10**3      //resistance(k ohms)
8 Rc=5*10**3       //collector current(k ohms)
9 Rl=5*10**3.      //load current(k ohms)
10 Rs=1*10**3      //source resistance(k ohms)
11
12 //Calculations
13 Rb=(R1*R2)/(R1+R2) //equivalent
    resistance of R1 and R2(kohms)
14 r=rpi+rx         //series resistance
    of rpi and rx(k ohms)
15 gm=beta/rpi      //transconductance(
    mS)
16 Vo=-gm*((Rc*Rl)/(Rc+Rl))*0.526 //output voltage(V)
    as

```

```

17 Av=Vo //voltage gain
18 Ai=Av*((Rs+((Rb*r)/(Rb+r)))/Rl) //current gain
19
20 //Results
21 printf ("source to load voltage gain is %.2f",Av)
22 printf ("source to load current gain is %f",Ai)
23 disp ("Note : Solution given in the textbook is
        incorrect")

```

Scilab code Exa 3.5 Example

```

1 //Variable declaration
2 beta=100. //current gain
3 rd=50*10**3 //internal dynamic resistance(ohms)
4 gm=5*10**-3 //transconductance(mS)
5 R1=50*10**3 //resistance(ohms)
6 R2=10*10**3 //resistance(ohms)
7 Rs=10*10**3 //source current(ohms)
8 Rg=1*10**6. //gate resistance(ohms)
9 Rd=10*10**3 //drain resistance(ohms)
10
11 //Calculations
12 Vgs=(Rg/(Rs+Rg)) //gate to source
    voltage (V) as Vgs=Vs((Rg/(Rs+Rg))
13 Av=-Vgs*gm*((rd*Rd)/(rd+Rd)) //voltage gain ,Av=
    Vo/Vs and Vo=-gmVgs(rd||Rd)
14 Ai=Av*((Rs+Rg)/Rd) //current gain
15
16 //Results
17 printf ("source to load voltage gain is %.f",Av)
18 printf ("source to load current gain is %.f",Ai)

```

Scilab code Exa 3.6 Example

```

1 //Variable declaration
2 Rs=500 //collector current(k ohms)
3 Io=-1*10**-3 //output current(mA)
4 Rc=5*10**3. //collector resistance(ohms)
5 hie=2*10**3
6 hoe=10*10**-6.
7 hfe=100.
8 hre=5*10**-4
9 Rb=50*10**3. //base resistance(ohms)
10
11 //Calculations
12 Io1=-1/(1+Rc*hoe)*hfe //as Io=-1/(1+Rc*hoe)*hfe*Ib
13 Ib=-1/Io1 //base current(uA)
14 Vo=Io*Rc //output voltage(V)
15 Vi=hie*Ib+Vo*hre //input voltage(V)
16 Is=Ib+Vi/Rb //source current(ohms)
17 Ai=Io/Is //current gain
18 Vs=(Is*Rs)+Vi //source voltage(V)
19 Av=Vo/Vs //voltage gain
20
21 //Results
22 printf ("source to load voltage gain is %.f",Av/1E
-3)
23 printf ("source to load current gain is %.f",Ai/1E
-3)

```

Scilab code Exa 3.7 Example

```

1 //Variable declaration
2 beeta=100. //current gain
3 Ic=4. //collector current(mA)
4 Vbe=0.7 //base to emitter voltage(V)
5 Re=2. //emitter resistance(ohms)
6 Vcc=32. //supply voltage(V)
7 abeeta=40. //actual current gain

```

```

8
9 // Calculations
10 Ib=Ic/beeta //base current (mA
    )
11 Rb=(Vcc-Vbe-((Ib+Ic)*Re))/Ib // as Vcc=(Ib*Rb)+
    Vbe+(Ib+Ic)*Re
12 Ib=(Vcc-Vbe-8)/(Rb+Re) // as Vcc=Rb*Ib+
    Vbe+(Ib+Ic)*Re
13 Ic1=abeeta*Ib // collector
    current (mA)
14 deltaIc=Ic-Ic1 //change in
    collector current (mA)
15
16 // Result
17 printf ("change in Ic when beeta=40 is %.1f mA",
    deltaIc)

```

Scilab code Exa 3.8 Example

```

1 // Variable declaration
2 Rb1=36 //base resistance 1(kohms)
3 Rb2=12 //base resistance 2(kohms)
4 Rc=4 //emitter resistance (kohms)
    )
5 Re=1.8 //emitter resistance (kohms)
6 Vcc=12 //supply voltage (V)
7 Vbe=0.7 //base to emitter voltage (V)
    )
8
9 // Calculations
10 Rb=(Rb1*Rb2)/(Rb1+Rb2) //base resistance (ohms)
11 Vbb=Vcc*(Rb2/(Rb1+Rb2)) //voltage supply to base (V)
12 // (10.8*Ib)+(1.8*Ic)=2.3
    equation 1... solving
    -Vbb+RbIb+Vbe+(Ib+Ic)Re

```

```

13                                     //(1.8*Ib)+(5.8*Ic)+Vce=12
                                     equation 2 solving -
                                     Vcc+RcIc+Vce+(Ob+Ic)Re
14 //Part a
15 beeta=50                            //current gain
16 Ib=2.3/100.8                        //(10.8*Ib)+(90*Ib)=2.3 , using
    -Vbb+Rb*Ib+Vbe+(Ib+Ic)*Re
17                                     //as Ic=50Ib and putting this
                                     in equation 1
18 Icq=Ib*beeta
19 Vceq=Vcc-(1.8*Ib)-(5.8*Icq) //from equation 2
20
21 //Part b
22 beeta=150                            //current gain
23 Ib=2.3/280.8                        //(10.8*Ib)+(270*Ib)=2.3, using
    -Vcc+Rc*Ic+Vce+(Ib+Ic)*Re
24                                     //as Ic=150Ib and putting this
                                     in equation 1
25 Icq1=Ib*beeta
26 Vceq1=Vcc-(1.8*Ib)-(5.8*Icq1)        //from
    equation 2
27
28 //Results
29 printf ("when beeta increases by 300%%,Icq increases
    by %.1f %%", (Icq1-Icq)/Icq1*100)
30 printf ("when beeta increases by 300%%, Vceq
    increases by %.f %%", (Vceq-Vceq1)/Vceq*100)

```

Scilab code Exa 3.9 Example

```

1 //Variable declaration
2 Ic=4                                //collector current (mA)
3 Vce=8                                //collector emitter
    voltage (V)
4 beeta=100                            //current gain

```

```

5 Rb2=24 //base resistance(kohms)
6 Vbe=0.7 //base to emitter voltage(
  V)
7 Rc=4 //collector current(kohm)
8 Re=2 //emitter resistance(kohms)
9 Ib=0.04 //base current(mA)
10
11 // Calculations
12 //Part a
13 Vcc=(Ic*Rc)+Vce+Ic*Re //from formula Vcc=
  IcRc+Vce+(Ic+Ib)Re.. eq 1
14
15 //Part b
16 Rb1=Rb2*(Vcc-(Vbe+Ic*Re))/((Vbe+Ic*Re)+Ib) //from
  eq 1 and also from Vbb= Vcc(Rb2/(Rb1+Rb2))
17 Rb=(Rb1*Rb2)/(Rb1+Rb2) //base
  resistance(ohms)
18 Vbb=(Vcc*Rb2)/(Rb1+Rb2) //supply
  to base(V)
19
20 //Part c
21 abeeta=40 //actual
  current gain
22 Ib1=((Vbe+Re*Ic)-Vbe)/((1+abeeta)*2+Rb) //from
  equation Vbb=IbRb+Vbe+(Ic+Ib)Re
23 Ic1=abeeta*Ib1 //
  collector gain
24
25 //Results
26 printf ("a)Vcc is %.1f V",Vcc)
27 printf ("b) values are Rb1: %.2f KOhms,Rb : %.2f kohm
  and Vbb : %.2f V" ,Rb1,Rb,Vbb)
28 printf ("c) actual value of Ic1 : %.2f mA",Ic1)

```

Scilab code Exa 3.10 Example

```

1 //Variable declaration
2 Vcc=10 //supply voltage(V)
3 Rc=4.7 //collector current(kohms)
4 Rb=250 //base resistance(kohms)
5 Re=1.2 //emitter resistance(kohms)
6 beeta=100 //current gain
7 Vbe=0.7 //base to emitter voltage(V)
8
9 //Calculations
10 //Part a
11 Ib=(Vcc-Vbe)/(Rb+(beeta*(Rc+Re))) //base current(
    uA)
12 Ic=beeta*Ib //collector
    current(mA)
13 Vce=Vcc-Ic*(Rc+Re) //collector to
    emitter voltage(V)
14 //Part b
15 beeta1=150 //current gain
16 Ib1=(Vcc-Vbe)/(Rb+(beeta1*(Rc+Re))) //base current(
    mA)
17 Ic1=beeta1*Ib1 //collector
    current(mA)
18 Vce1=Vcc-Ic1*(Rc+Re) //collector to
    emitter voltage(V)
19 deltaIc=((Ic1-Ic)/Ic)*100 //small change
    in Ic(mA)
20 deltaVce=((Vce-Vce1)/Vce)*100 //small change
    in Vce(V)
21
22 //Results
23 printf ("values of Ic is %.2f mA and Vce : %.2f V",
    Ic,Vce)
24 printf ("values of Ic1 is %.2f mA and Vce1 is %.2f V
    ",Ic1,Vce1)
25 printf ("%%% change in Ic is %.2f %% and in Vce is %
    .2f %% ",deltaIc,deltaVce)

```

Scilab code Exa 3.11 Example

```
1 //Variable declaration
2 Id=3 //drain current (mA)
3 Vds=12 //drain source voltage (V)
4 Vgs=-3 //gate source voltage (V)
5 Vdd=36 //drain voltage (V)
6 Vgg=12 //gate voltage (V)
7 Rg=12 //gate resistance (Mohms)
8
9 //Calculations
10 R1=(Rg*Vdd)/Vgg //resistance (Mohms)
11 R2=(Rg*R1)/(R1-Rg) //resistance (kohms)
12 Rs=(Vgg-Vgs)/Id //resistance (kohms)
13 Rd=(Vdd-Vds-Id*Rs)/Id //as  $V_{dd}-I_d R_d-V_{ds}-I_d R_s$ 
14 Vgs=-3.6 //consider Vgs increases
    by 20%
15 Idnew=(Vgg-Vgs)/Rs //new drain current (mA)
16
17 //Results
18 printf ("value of R1 : %.f MOhm , R2: %.f Mohms, Rs
    : %.f KOhm and Rd: %.f kohms",R1,R2,Rs,Rd)
19 printf ("new Id is %.2f mA",Idnew)
```

Scilab code Exa 3.12 Example

```
1
2 //Variable declaration
3 k=0.0002 //device parameter
4 Vt=4 //thevinin voltage (V)
5 Vdd=24 //drain voltage (V)
6 Id0=3 //drain current (mA)
```



```

7
8 // Calculations
9 Vgs=(sqrt(Id0/k))+4 // as Id=k(Vgs-Vt)^2
10 Rd=-(Vgs-Vdd)/Id0 // as Vds=Vdd-IdRd and Vgs=
    Vds=7.87
11 k=0.0003 //device parameter
12
13 syms Id
14 expr = solve([Id**2-7.5*Id+13.7],[Id])
15 printf ("equation has 2 solutions")
16 disp(expr) //
    putting value of k=0.0003 in eq of Id,
17 Id1=3.15 // we
    get Vgs=Vds=24-5.4Id and putting Vgs again in Id
    we get,
18 // Id^2-7.5Id
    +13.7=0
19
20 Idchange=((Id1-Id0)/Id0)*100
    //changed Id(mA)
21
22 // Result
23 printf ("change in Id is %.1f %% increase",Idchange)

```

Scilab code Exa 3.13 Example

```

1 //Variable declaration
2 Vt=2 //threshold voltage(V)
3 Id=8 //drain current(mA)
4 Vgs=6. //gate to source
    voltage(V)
5 k=0.5 //device parameter
6 Vdd=24 //drain voltage(V)
7 Vds=10 //drain to source

```

```

        voltage(V)
8
9 // Calculations
10 // Part a
11 Vgs1=4 //
    gate to source voltage(V)
12 Id1=k*(Vgs1-Vt)**2
    //drain current(mA)
13
14 // Part b
15 Vgg=3*Vgs1
    //gate voltage(V)
16 R2=(Vdd/Vgg)-1 //
    resistance(Mohms)
17 Rs=(Vgg-Vgs1)/2
    //source resistance(k ohms)
18 Rd=(Vdd-Vds-Id1*Rs)/2
19
20 // part c
21 K=1.5*k //increased by 50%
22 Vgs2=3.67 //solving  $12=V_{gs}+4I_d$  and
    Id=0.75(Vgs-2)^2
23 Id2=2.08 //drain current when k is
    increased(mA)
24 Vds1=Vdd-Id2*(Rd+Rs) //drain to source voltage(
    V)
25
26 // Results
27 printf ("drain current defined by Vgs=4 and Vds=10
    is %.1f mA", Id1)
28 printf ("value of Rs,Rd,R2 are %.1f k ohms %.1f k
    ohms %.1f Mohms resp.", Rs, Rd, R2)
29 printf ("actual value of Id and Vds are %.2f mA %.2f
    mA and %.2f V resp.", Id2, Vds1, Vds)

```

Scilab code Exa 3.14 Example

```
1 //Variable declaration
2 Ic=10 //collector current (mA)
3 beeta=100 //current gain
4 Vbe=0.7 //base to emitter
   voltage (V)
5 Vcc=10 //supply voltage (V)
6
7 //Calculations
8 //Part a
9 R=(beeta*(Vcc-Vbe))/((beeta+2)*Ic) //
   resistance (k ohms)
10 beeta1=200 //
   current gain
11 Ic1=(beeta1/(beeta1+2))*((Vcc-Vbe)/R) //
   collector current (mA)
12 Icchange=((Ic-Ic1)/Ic) //
   change in collector current (mA)
13
14 //Part b
15 Ic2=0.1 //
   collector current (mA)
16 R1=(beeta*(Vcc-Vbe))/((beeta+2)*Ic) //
   resistance (k ohms)
17 Ic3=(beeta1/(beeta1+2))*((Vcc-Vbe)/R1) //
   collector current (mA)
18 Icchange1=((Ic2-Ic3)/Ic2) //
   change in collector current (mA)
19
20 //Results
21 printf ("%%" change in Ic is %.1f %% increase",
   Icchange)
22 printf ("%%" change in Ic is %.1f %% increase",
   Icchange1)
```

Scilab code Exa 3.15 Example

```
1 //Variable declaration
2 Vcc=6 //supply voltage(V)
3 R=1.2 //resistance(k ohms)
4 Vbe=0.7 //base to emitter voltage
   (V)
5 beeta=100. //current gain
6
7 //Calculations
8 //Part a
9 Ir=(Vcc-Vbe)/R //current(mA)
10 I=(beeta/(beeta+3))*Ir //current(mA) as
   transistors are identiical ,I=Ie
11
12 //Result
13 printf ("load current I is %.2f mA ",I)
```

Scilab code Exa 3.16 Example

```
1
2
3 //Variable declaration
4 Idss=10 //drain current for zero bias(
   mA)
5 Vp=-4 //peak voltage(V)
6 Idq=2.5 //quienscent drain current(mA)
7 Id=Idq
8 Vdd=24 //voltage drain drain(V)
9 Vgg=4 //gate voltage(V)
10 R1=22 //resistance(Mohms)
11
```

```

12 // Calculations
13 // Part a
14 Vgs=Vp*(1-(sqrt(Id/Idss))) // solving Id=Idss
    (1-Vgs/Vp)^2
15 Rs=(Vgg-Vgs)/Id // as Vgg-Vgs
    -IdRs=0 ,Id=Is
16 Rd=2.5*Rs // given
17 R2=(Vgg*R1)/(R1-Vgg) // from Vgg=(
    R1*R2)/(R1+R2)
18
19 // Part b
20 gmo=-(2*Idss)/Vp //
    transconductance (mS)
21 gm=gmo*(sqrt(Id/Idss)) // transconductance
    (mS)
22
23 // Part c
24 Av=-gm*Rd // voltage
    gain
25
26 // Results
27 printf (" values of Rs : %.1f Kohms, Rd : %.1f k ohms
    and R2 is %.1f M ohms",Rs,Rd,R2)
28 printf (" value of gm is %.1f mS and gmo is %.1f mS",
    gm,gmo)
29 printf (" voltage amplification is %.1f",Av)

```

Scilab code Exa 3.17 Example

```

1
2
3 // Variable declaration
4 beeta=98. // current gain
5 rpi=1.275 // dynamic
    resistance(k ohms)

```

```

6 Rb=220. //base resistance
   (k ohms)
7 Re=3.3 //emitter
   resistance(k ohms)
8 Vcc=12. //supply voltage(
   V)
9 Vbe=0.7 //base to emitter
   voltage(V)
10
11 //Calculations
12 //Part a
13 x=rpi/(1+beeta)
14 Av=Re/(Re+x) //voltage gain
15
16 //Part b
17 Zb=rpi+(1+beeta)*Re //impedance(k ohms)
18 Zi=(Zb*Rb)/(Zb+Rb) //input impedance(k
   ohms)
19 Zo=(Re*x)/(Re+x) //output impedance(k
   ohms)
20
21 //Part c
22 Ib=(Vcc-Vbe)/(Rb+(Re*(1+beeta))) //as Ie=(1+
   beeta)*Ib
23 Ic=beeta*Ib //collector
   current(mA)
24 rpi=beeta*(25/Ic) //dynamic
   resistance(k ohms)
25
26 //Results
27 printf ("voltage gain is %.3f",Av)
28 printf ("input impedance is %.1f KOhm and output
   impedance is %.1f ohms",Zi,Zo/1E-3)
29 printf ("value of Ic is %.3f mA",Ic)
30 printf ("value of rpi is %.3f k ohms",rpi/1E+3)

```

Scilab code Exa 3.18 Example

```
1
2
3 //Variable declaration
4 Idss=16 //drain current
   bias to zero (mA)
5 Vp=-4 //pinch off
   voltage (V)
6 Rg=1 //gate resistance(
   ohms)
7 Rs=2.2 //source
   resistance (ohm)
8 Vdd=9 //drain drain
   voltage (V)
9
10 //Calculations
11 //Part a
12 //Id=Idss*(1-(Vgs/Vp))**2
13 // putting value of Vgs=2.2*Id inequation of Id ,we
   get
14 //Id**2-3.84Id+3.31
15
16 syms Id
17 expr=solve([Id**2-3.84*Id+3.31],[Id])
18 disp(expr)
19 Id1=1.3
20 Vgs=-Id1*Rs
   //gate to source voltage (V)
21 gm0=-(2*Idss)/Vp
   //transconductance (mS)
22 gm=gm0*(1-(Vgs/Vp))
   //transconductance (mS)
23 rm=1/gm
```

```

    //transresistance(k ohms)
24 Av=(Rs*gm)/(1+(Rs*gm))
    //voltage gain
25
26 //Part b
27 Zi=Rg
    //input impedance(Mohms)
28 Zo=(Rs*rm)/(Rs+rm)
    //output impedance(ohms)
29
30 //Results
31 printf ("voltage gain is %.3f",Av)
32 printf ("input and output impedences are %.f Mohms
    and %.1f ohms",Zi,Zo/1E-3)

```

Scilab code Exa 3.19 Example

```

1
2
3 //Variable declaration
4 Re=0.56 //emitter
    resistance(k ohms)
5 beta=1600 //current gain
6 R1=110 //resistance(k ohms)
    )
7 R2=330 //resistance(k ohms)
    )
8
9 //Calculations
10 //Part a
11 Av1=Re*(beta+1) //voltage gain
12
13 //part b
14 Rb=(R1*R2)/(R1+R2) //base resistance(k
    ohms)

```



```

15 Vs=(1.56/(Re*(beta+1)))+1           //source voltage(V)
16 Avs=1/Vs
17
18 //part c
19 R=1+(1+beta)*Re
    //resistance presented to Ib
20 I=Rb/(Rb+R)
    //I=Ib/Ii
21 Ai=(1+beta)*I
    //current gain
22
23 //part d
24 Rl=10*10**3                          //load
    resistance(ohm)
25 Re1=(Re*Rl)/(Re+Rl)                  //emitter
    resistance(k ohms)
26 R1=1+(1+beta)*Re1                    //resistance
    presented to Ib(k ohms)
27 I1=Rb/(Rb+R1)                        //I1=Ib/Ii
28 Ai1=(beta+1)*I1                      //current
    gain
29 Av2=Re1*(1+beta)                     //voltage
    gain
30
31 //Results
32 printf ("a)voltage gain is %.2f",Av1)
33 printf ("b)Avs is %.2f",Avs)
34 printf ("c)Ai is %.2f ",Ai)
35 printf ("when output Vo1 feeds a load of 10 k ohms
    Ai is %d and Av2 is %.f",Ai1,Av2)

```

Scilab code Exa 3.20 Example

```

1 //Variable declaration
2 beeta1=120.                          //current gain

```

```

3  beeta2=160.                //current gain
4  Vcc=18                    //supply voltage(V)
5  Rc=0.1                    //collector
    resistance(ohms)
6  Rb=2*10**3.              //base resistance(
    ohms)
7  Vbe=0.7                  //base to emitter
    voltage(V)
8
9  // Calculations
10 Ib1=(Vcc-Vbe)/(Rb+(beeta1*beeta2*Rc)) //base current(
    uA)
11 Ib2=beeta1*Ib1           //base current(
    mA)
12 Ie1=(beeta1+1)*Ib1      //emitter
    current(mA)
13 Ic=Ie1+(beeta2*Ib2)     //collector
    current(mA)
14 Vo=Vcc-(Ic*Rc)          //output voltage
    (V)
15 Vi=Vo-Vbe                //input voltage(
    V)
16
17 // Results
18 printf ("dc biased current is %.1f mA",Ic)
19 printf ("output voltage %.2f V",Vo)
20 printf ("input voltage %.2f V",Vi)

```

Scilab code Exa 3.21 Example

```

1
2
3 //Variable declaration
4 deltaId=2.                //change in Id(mA
    )

```

```

5  deltaVgs=1.                                //change in Vgs(V
   )
6  deltaVds=5.                                //change in Vds(V
   )
7  Idss=10.                                   //drain current
   biased to zero(mA)
8  Id=5.                                       //drain current(
   mA)
9  Vp=-6.                                     //pinch off
   voltage(V)
10
11 // Calculations
12 //Part a
13 gm=(deltaId)/(deltaVgs)                    //
   transconductance (mS)
14 rds=(deltaVds)/(deltaId)                   //resistance (k
   ohms)
15 gm0=-(2*Idss)/Vp                           //
   transconductance (mS)
16 gm=gm0*(sqrt(Id/Idss))                     //transconductance (mS)
17
18 //Part b
19 R1=4.5                                       //resistance (k
   ohms)
20 R2=2                                         //resistance (k
   ohms)
21 Av=gm*((R1*R2)/(R1+R2))                    //voltage gain
22
23 // Results
24 printf ("drain current biased to zero is %.1f mA and
   pinch off voltage is %.1f V",Idss,Vp)
25 printf ("value of gm and rds are %.2f mS and %.2f k
   ohms",gm,rds)
26 printf ("small signal amplifier gain is %.2f ",Av)

```

Scilab code Exa 3.22 Example

```

1
2
3 //Variable declaration
4 Idson=0.2
5 Vgs=5 //gate to source voltage(
   V)
6 Vdd=12 //drain voltage(V)
7 Vt=2 //thevinine voltage(V)
8 R1=100. //resistance(k ohms)
9 R2=100. //resistance(k ohms)
10 Rd=30 //drain resistance(K ohms
   )
11 Rs=6 //source resistance(k
   ohms)
12 deltaVdd=0.3 //change in Vdd(V)
13 rds=50 //internal drain to
   source resistance()
14
15 //Calculations
16 //Part a
17 k=Idson/((Vgs-Vt)**2) //device
   parameter
18 Vgg=Vdd*(R1/(R1+R2)) //gate voltage(V)
19 Vgs=4.89 //gate to source
   voltage(V)
20 Id=k*(Vgs-Vt)**2 //drain current(
   mA)
21 Vds=Vdd-((Rd+Rs)*Id) //drain to source
   voltage(V)
22 gm=2*(sqrt(k*Id)) //transconductance(mS)
23 deltaVgg=deltaVdd*(R2/(R1+R2)) //change in Vgg(V
   )
24
25 vgs=0.105 //as vgs=0.15-6id
   where id=u*vgs/(rds+Rs+Rd)=0.74vgs after solving
26 id= 0.074*vgs*10**3

```

```

27
28 //Results
29 printf ("id is %.2f uA",id)

```

Scilab code Exa 3.23 Example

```

1
2
3 //Variable declaration
4 deltaId=1 //change in Id(mA)
5 deltaVgs=0.75 //change in Vgs(V)
6 rd=100 //internal drain
   resistance(k ohms)
7 Rd=100 //drain resistance
   (k ohms)
8 Vgs=2 //as Vgs= 2sinwt
9
10 //Calculations
11 gm=(deltaId)/(deltaVgs) //transconductance
   (m)
12 Vo=-gm*Vgs*((rd*Rd)/(rd+Rd)) // as Vi=2sin(w*t)
13
14 //Results
15 printf ("value of Vo is %.f *sinwt mV",Vo)

```

Scilab code Exa 3.24 Example

```

1 //Finding resistance
2
3 //Variable declaration
4 Rd=4 //drain resistance(ohms)
5 Rs=2.5 //ource resistance(ohms)
6 R1=200*10**3 //resistance(ohms)

```

```

7 R2=100*10**3           //resistance (ohms)
8 gm=2.5                 //transconductance (mS)
9 rd=60                  //internal drain resistance (
    ohms)
10
11 //Calculations
12 //Part b
13 Ro=Rs/(1+(((1+gm*rd)*Rs)/(rd+Rd))) //output
    resistance (ohms)
14
15 //Part c
16 Rd1=0                 //drain
    resistance
17 Ro1=Rs/(1+(((1+gm*rd)*Rs)/rd)) //output
    resistance (ohms)
18
19 //Results
20 printf ("value of Ro is %.f ohms",Ro/1E-3)
21 printf ("value of Ro1 is %.f ohms",Ro1/1E-3)

```

Scilab code Exa 3.25 Example

```

1 //Variable declaration
2 beeta=100              //current gain factor
3 Vbe=0.7                //base to emitter
    voltage (V)
4 Rb=250                 //base resistance (k
    ohms)
5 Vee=10                 //emitter voltage (V)
6 Re=1                   //emitter resistance (
    k ohms)
7
8 //Calculations
9 Ib=(Vee-Vbe)/(Rb+1+beeta) // solving Rb*Ib+Vbe
    +(Ic+Ib)=Vee and putting Ic+Ib=(1+beeta)Ib

```

```

10 Ic=beeta*Ib //collector current(
    mA)
11 rpi=beeta*(25/Ic) //dynamic resistance
    (ohms)
12 Vi=(rpi*Ib)+(1+beeta)*Re*Ib //input voltage(V)
13 Ri=Vi/Ib //input resistance(k
    ohms)
14
15 //Results
16 printf ("value of Ri is %.1f K ohms",Ri/1E+1)

```

Scilab code Exa 3.26 Example

```

1 //Variable declaration
2 beeta=125 //current gain
3 gm=35 //transconductance(
    mS)
4 Re=4 //emitter resistance
    (k ohms)
5 Rb=1.5 //base resistance(k
    ohms)
6
7 //Calculations
8 //Part a
9 rpi=beeta/gm //dynamic resistance(
    k ohms)
10 Ri=rpi+((1+beeta)*Re) //input resistance(k
    ohms)
11 Ro=((Rb+rpi)*Re)/((Rb+rpi)+((1+beeta)*Re)) //output
    resistance(ohms) as Ro=Vo/Isc
12
13 //Part b
14 f=((1+beeta)*Re)/(Rb+rpi+((1+beeta)*Re)) //transfer
    function
15

```

```

16 //Results
17 printf ("value of Ri is %.1f K ohms and Ro is %.4f k
    ",Ri ,Ro)
18 printf ("transfer function is %.2f",f)

```

Scilab code Exa 3.28 Example

```

1 //Variable declaration
2 Vcc=16 //supply voltage(V)
3 Vc=12 //collector voltage(V)
4 Ic=8 //collector current(mA)
5 Ic1=12
6 deltaIc=2000 //collector current(uA)
7 deltaVce=4 //collector emitter voltage(
    Vce)
8 deltaIb=20 //base current(mA)
9 Rl=2. //load reistance(k ohms)
10
11 //Calculations
12 hfe=(deltaIc)/(deltaIb)
13 hoe=(deltaIc)/(deltaVce)
14 Rdc=Vcc/Ic //dc resistance(k
    ohms)
15 Rac=Vc/Ic1 //ac resistance(k
    ohms)
16 Re=Rdc-Rac //emitter
    resistance(k ohms)
17 Rac1=(Rac*Rl)/(Rac+Rl) //for load of 2
    kohms, Rc=Rac
18 Icq=Vcc/(Rac1+Rdc) //Ic at
    operatingpoint(mA)
19 Vceq=Vcc-(Icq*Rdc) //Vc at operating
    point(V)
20
21 //Results

```



```

22 printf ("value of hfe and hoe are %d uS and %d uS",
    hfe, hoe)
23 printf ("value Rc and Re are %d k ohms and %d k ohms
    resp.", Rac, Re)
24 printf ("value of Icq and Vce %d mA and %.1f V resp.
    ", Icq, Vceq)

```

Scilab code Exa 3.29 Example

```

1 //Variable declaration
2 hfe=120 //current gain
3 r1=1.5 //resistance(k ohms)
4 Vi=1 //input voltage(V)
5 hoe=50*10**-3 //output conductance with input
    open circuited
6 Rs=2 //source resistance(k ohms)
7 Vbe=0.7 //base to emitter voltage(V)
8 Vcc=10 //supply voltage(V)
9 r3=0.33 //resistance(k ohms)
10 r4=5.8 //rsistance(k ohms)
11 r5=27 //rsistance(k ohms)
12 hoe=50*10**-3 //output conductance with input
    open circuited
13
14 //Calculations
15 //Part a
16 Vbb=Vcc*(r4/(r4+r5)) //voltage to bae(V)
17 Rb=(r5*r4)/(r5+r4) // as Vbb-Vbe=RbIb+(
    hfe+1)Ib*R, here hfe=beeta
18 ib=(Vbb-Vbe)/(Rb+(hfe+1)*r3) //instantaneous base
    current (mA)
19 hie=(0.02/ib)*10**3
20 Ib=Vi/hie //base current (mA)
21 h=hfe*Ib
22 Avo=-h*r1 //voltage gain

```

```

23
24 //Part b
25 r=1/hoe //resistance(k ohms)
26 R1=(r*r1)/(r+r1) //resistance(k ohms)
27 R=(R1*Rs)/(R1+Rs) //resistance(k ohms)
28 Ib1=1/(Rs+R) //base current(mA)
29 h1=hfe*Ib1
30 Avl=-h1*R //voltage gain
31
32 //Results
33 printf ("hie and Avo are %.f and %.1f",hie,Avo/1E-3)
34 printf (" Avl is %.2 f",Avl)

```

Scilab code Exa 3.30 Example

```

1 //Variable declaration
2 Rl=20 //load resistance(ohms)
3 Vcc=30 //supply voltage(V)
4 beeta=150 //current gain
5 Re=2200 //emitter resistance(ohms)
6 Rb=350 //base resistance(k ohms)
7 Vbe=0.7 //base to emitter voltage(V)
8 Is=10**-3 //source current(A)
9 r1=2000 //resistance(ohms)
10
11 //Calculations
12 Ib=(Vcc-Vbe)/(Rb+(1+beeta)*Re) //base current(uA)
13 Ic=beeta*Ib //collector current(mA)
14 rpi=beeta*(25/Ic) //dynamic resistance(
ohms)
15 R=(Re*Rl)/(Re+Rl) //resistance(ohms)
16 Ib1=17.95 //round the base
emitter(as Rb>>2 kohms,it is ignored)
17 Vl=(beeta+1)*Ib1*R //load voltage(V)

```

```

18 Av1=V1 //Voltage gain
19 I1=V1/R1 //load current(A
   )
20 Ail=I1/Is //current gain
21
22 //Results
23 printf ("overall voltage gain is %.2f",Av1/1E+3)
24 printf ("overall current gain is %.f",Ail/1E+3)

```

Scilab code Exa 3.31 Example

```

1 //Variable declaration
2 Vcc=15 //supply voltage(V)
3 beeta=30 //current gain
4 R=.47 //emitter resistance(ohms)
5 Vbe=0.7 //base to emitter voltage(V)
6 Vo=5 //output voltage(V)
7
8 //Calculations
9 Vbb=Vcc/2 //base
   voltage(V)
10 Ib=Vo/(R*930) //from equation(i)
11 R1=((6.1-4.98)/0.0114)*2 //
   resistance(k ohms)
12
13 //Results
14 printf ("value of R1 is %.f K ohms",R1)

```

Chapter 4

SMALL SIGNAL AMPLIFIERS FREQUENCY RESPONSE

Scilab code Exa 4.1 Example

```
1
2
3 //Variable declaration
4 Vs = 1. //source voltage(V)
5 C = 100*10^-6 //value of capacitance(uF)
6 r1 = 1 //resistance 1(k ohms)
7 r2 = 4 //resistance 2(k ohms)
8 R = 5 //total resistance ,R = r1+r2
9
10 //Calculations
11 Imax = Vs/(r1+r2)*10^3 //maximum current(uA)
12 fc = 1/(2*(%pi)*C*R) //critical frequency(Hz)
13 //As  $\omega C R = 1$  and  $\omega = 2 * \pi * f$ 
14 f = 10*fc //lowest frequency(Hz)
15 )
```

```

16 //Results
17 printf ("maximum current %.1f uA",Imax)
18 printf ("critical frequency %.3f Hz",fc/1E+3)
19 printf ("lowest frequency %.2f Hz",f/1E+3)

```

Scilab code Exa 4.2 Example

```

1
2
3 //Variable declaration
4 C = 100*10^-6 //capacitance(uF)
5 Rg = 1. //galvanometer resistance(k oms)
6 Rl = 4. //load resistance(k ohms)
7
8 //Calculations
9 Rth = (Rg*Rl)/(Rg+Rl) //thevinine's equivalent
    resistance
10 fc = 1/(2*(%pi)*C*Rth) //critical frequency(Hz)
11 f = fc*C //lowest frequency(Hz)
12
13 //Results
14 printf ("lowest frequency at which the point A gets
    grounded is %.1f Hz",f/1E-2)

```

Scilab code Exa 4.3 Example

```

1
2
3 //Variable declaration
4 rpi = 600 //dynamic junction
    resistance(ohms)
5 beta = 100 //common emitter current
    gain

```

```

6 Vs = 5.                //source voltage (V)
7 Rs = 400              //source resistance (ohms)
8 R = 10                //resistance (k ohms)
9
10 // Calculations
11 Ib = Vs/(Rs+rpi)     //base current (uA)
12 Vo = R*beta*Ib      //output voltage (V)
13 Rin = rpi           //input resistance (ohms)
14 Rout = R            //output resistance (k ohms)
15
16 // Results
17 printf ("output voltage is %.1f V",Vo)
18 printf ("input resistance %.1f ohms",Rin)
19 printf ("output resistance %.1f k ohms",Rout)

```

Scilab code Exa 4.4 Example

```

1 //Variable declaration
2 gm = 1.                //transconductance (mS)
3 rd = 40                //dynamic drain
   resistance (k ohms)
4 Rd1 = 40              //JFET 1 drain resistance
   (k ohms)
5 Rd2 = 10              //JFET 2 drain resistance
   (k ohms)
6
7 // Calculations
8 Avo = (-gm*((rd*Rd1)/(rd+Rd1)))*(-gm*((rd*Rd2)/(rd+
   Rd2)))                //voltage gain
9
10 // Results
11 printf ("Avo is %.1f ",Avo)

```

Scilab code Exa 4.5 Example

```
1 //Variable declaration
2 beta = 125 //common emitter current gain
3 rpi = 2.5 //dynamic junction resistance(k
  ohms)
4 rd = 40 //dynamic drain resistance(k
  ohms)
5 gm = 2 //transconductance(mS)
6 Vs = 1 //assume, source voltage(V)
7 Rs = 10 //source resistance(k ohms)
8 Rc = 1 //collector resistance(k ohms)
9 rb = 2 //resistance(k ohms)
10 Vgs = 1 //gate to source voltage(V)
11
12 //Calculations
13 //Part a
14 R = (rd*Rs)/(rd+Rs) //equivalent resistance(k
  ohms)
15 Ib = gm*Vgs*(R/(rpi+R)) //base current(mA)
16 Vo = beta*Ib*Rc //output voltage(V)
17 Avo = Vo //voltage gain
18
19 //Part b
20 Ib1 = Vs/(rb+rpi) //base current(mA) after
  interchanging stages of JFET and BJT
21 Vgs1 = beta*Ib1*Rc //gate to source voltage(V)
  after interchanging stages of JFET and BJT
22 Vo1 = gm*Vgs1*R //output voltage(V) after
  interchanging stages of JFET and BJT
23 Avo1 = Vo1 //voltage gain after
  interchanging stages of JFET and BJT
24
25 //Results
26 printf ("Avo is %.1f ",Avo)
27 printf ("Avo1 when BJT and FET stages are reversed
  is %.f",Avo1)
```

Scilab code Exa 4.6 Example

```
1
2
3 //Variable declaration
4 Cc1 = 1*10^-6 //coupling capacitor
   1(uF)
5 Cc2 = 1*10^-6 //coupling capacitor 2
   (uF)
6 Rs = 10^3 //source resistance(k
   ohms)
7 rpi = 2*10^3 //dynamic junction
   resistance(k ohms)
8 Rc = 4500 //collector
   resistance(ohms)
9 Rl = 9*10^3 //load resistance(k
   ohms)
10 w = 100 //corner frequency(
   rad/s)
11
12 //Calculations
13 w11 = 1/(Cc1*(Rs+rpi)) //corner
   frequency input circuit (rad/s)
14 w12 = 1/(Cc2*(Rc+Rl)) //corner
   frequency output circuit(rad/s)
15 f = w11/(2*(%pi)) //lower cutoff
   frequency(Hz)
16 Zin = complex((Rs+rpi),-(1/(w*Cc1))) //input
   impedance(k ohms)
17 Zout = complex(Rc,-(1/(w*Cc2))) //output
   impedance(k ohms)
18
19 //Results
20 printf ("lower cut-off freq is %.f Hz",f)
```



```

21 disp ("ohms", Zin , " Zin")
22 disp ("ohms" ,Zout , " Zout")

```

Scilab code Exa 4.7 Example

```

1
2
3 //Variable declaration
4 Re = 1.5*10^3 //collector resistance(
    ohms)
5 Rc = Re
6 Rs = 600 //source resistance(
    ohms)
7 Rl = 2*10^3 //load resistance(ohms
    )
8 beta = 100 //common emitter
    current gain
9 rpi = 1*10^3 //dynamic junction
    resistance(ohms)
10 f = 50 //frequency (Hz)
11
12 //Calculations
13 w = 2*f*(%pi) //corner frequency(rad/s)
14 CE = 1/(w*(Rs+rpi)) //capacitance(uF)
15 Ce = CE*(beta+1) //capacitance(uF)
16 w11 = w/10 //corner frequency
    input circuit (rad/s)
17 w12 = w11/20 //corner frequency
    output circuit(rad/s)
18 Cc1 = 1/(w11*(Rs+rpi)) //coupling capacitor
    1(uF)
19 Cc2 = 1/(w12*(Rc+Rl)) //coupling capacitor
    2 (uF)
20
21 //Results

```

```

22 printf ("Ce is %.f uF", Ce/1E-6)
23 printf ("Cc1 is %.1f uF", Cc1/1e-6)
24 printf ("Cc2 is %.2f uF", Cc2/1E-5)

```

Scilab code Exa 4.8 Example

```

1
2
3 //Variable declaration
4 gm = 2.5*10^-3 //transconductance (mS)
5 Rd = 6*10^3 //drain resistance (ohms)
6 rd = 200*10^3 //dynamic drain resistance
   (ohms)
7 Cc1 = 0.12*10^-6 //coupling capacitors (uF)
8 Cc2 = Cc1
9 Rs = 1*10^3 //source resistance (ohms)
10 Rg = 0.1*10^6 //R1 || R2
11 Cgs = 12*10^-9 //gate to source capacitor
   (pF)
12 Cgd = 2*10^-9 //gate to drain capacitor (
   pF)
13 Co1 = 10 // as Co1 = C1+Cw = 10
14
15 //Calculations
16 //Part a
17 Ro = (rd*Rd)/(rd+Rd) //equivalent
   resistance of rd and Rd(ohms)
18 Vo = -gm*((rd*Rd)/(rd+Rd)) //as Vgs = Vs
19 Avo = Vo //Avo = Vo/Vs
   = (-gm*Vs*((rd*Rd)/(rd+Rd)))/Vs = Vo
20
21 //Part b
22 f11 = 1/(2*(%pi)*Cc1*(Rs+Rg))
23
24 //Part c

```

```

25 Ceq = Cgs+(Cgd*(1+gm*Ro)) //on
    application of miller theorem
26 Co = Co1+Cgd*(1+(1/(gm*Ro))) //
    output capacitance(pF)
27 f21 = 1/(2*(%pi)*Ceq*((Rs*Rg)/(Rs+Rg))) //input
    circuit cutoff frequency(MHz)
28 f22 = 1/(2*(%pi)*Co*Ro)*10^3 //output
    circuit cutoff frequency(MHz)
29 fH = f22 //
    cutoff frequency of high frequency band(MHz)
30
31 //Results
32 printf ("a)mid freq gain is %.1f",Avo)
33 printf ("b)input circuit cut-off is %.1f Hz",f11)
34 printf ("c)high freq input cutoff is %.2f and output
    cutoff is %.2f MHz",f21/1E+3,f22/1E-3)
35 printf ("high freq cut-off is %.2f MHz",fH/1E-3)

```

Scilab code Exa 4.9 Example

```

1
2
3 //Variable declaration
4 beta = 50. //common emitter current
    gain
5 R1 = 11.5 //resistance(k ohms)
6 R2 = 41.4 //resistance(k ohms)
7 Vcc = 10. //supply voltage to
    collector(V)
8 Rc = 5. //collector resistance(k
    ohms)
9 Re = 1. //emitter resistance(k ohms)
10 Rs = 1. //source resistance(k ohms)
11 Vbe = 0.7 //base emitter voltage(V)
12 Rl = 10. //load resistance(k ohms)

```

```

13 Cc1 = 20*10^-6.      //coupling capacitors(uF)
14 Cc2 = Cc1
15 Ce = 150*10^-6.      //emitter capacitor(uF)
16 Cpi = 100
17 Cu = 5.
18
19 //Calculations
20 //Part a
21 Rb = (R1*R2)/(R1+R2)      //R1||R2(k ohms
   )
22 Vbb = Vcc*(R1/(R1+R2))    //suply voltage
   to base(V)
23 Ib = (Vbb-Vbe)/(Rb+(Rs*(1+beta))) //base current(
   mA)
24 Ic = beta*Ib              //collector
   current(mA)
25 Vce = Vcc-(Ic*Rc)-(Ic+Ib)*Re //collector to
   emitter voltage(V)
26 rpi = (25*beta)*10^-3/Ic //dynamic
   junction resistance(K ohms)
27
28 //Part b
29 rpi = 1                    //dynamic
   junction resistance(K ohms)
30 R = (rpi*Rb)/(rpi+Rb)     //equivalent
   resistance(rpi||Rb)
31 Vbe = (R*Rs)/(R+Rs)       //base to
   emitter voltage(V)
32 Ib1 = Vbe/rpi             //base current(
   mA)
33 Ro = (Rc*Rl)/(Rc+Rl)     //Rc||Rl(k ohms
   )
34 Vo = -(beta*Ib1*Ro)       //output voltage
   (V)
35 Avo = Vo                  //voltage gain
36
37 //Part c
38 r1 = (Rs*Rb)/(Rs+Rb)     //Rs||Rb(k ohms)

```

```

39 w11 = 1/(Cc1*(Rs+R))           //low freq
    cutoff(rad/s)
40 w12 = 1/(Cc2*(Rc+Rl))         //high freq
    cutoff(rad/s)
41 w1p = 1/((Ce/(beta+1))*(r1+rpi)) //low cutoff freq
    (rad/s)
42
43 //Part d
44 Co1 = 5                         //as Co1 = Cw+Cl
45 gm = beta/rpi                   //transconductance(
    mS)
46 Ceq = Cpi+(Cu*(1+(gm*Ro)))     //equivalent
    capacitance(pF)
47 Rs1 = (Rb*Rs)/(Rb+Rs)          //Rb||Rs(k ohms)
48 r2 = (Rs1*rpi)/(Rs1+rpi)       //Rs1||rpi(k ohms)
49 w21 = 10^12/(Ceq*r2*10^3)      //low freq
    cutoff(MHz)
50
51 //Results
52 printf ("a)dc bias values are Vbb : %.2f V, Ib : %.4
    f mA, Ic : %.2f mA, Vce : %.3f V, rpi : %.f k
    ohms",Vbb,Ib,Ic,Vce,rpi)
53 printf ("mid freq gain is %.2f ",Avo)
54 printf ("low freq cut-off is %.f rad/s",w1p/1E+3)
55 printf ("high cut-off freq is %.2e rad/s",w21)

```

Scilab code Exa 4.10 Example

```

1
2
3 //Variable declaration
4 Qcoil = 75.                       //coil inductance
5 f = 200.                           //frequency(Hz)
6 BW = 4.                             //bandwidth(kHz)
7 C = 470*10^-9.                     //capacitance(pF)

```

```

8
9 // Calculations
10 // Part a
11 Qcircuit = f/BW // circuit
    inductance
12 L = 1/(((2*(%pi)*f)^2)*C) // inductance (mH)
13
14 // Part b
15 R = Qcircuit*2*(%pi)*f*L // resistance (k ohms)
16
17 // Part c
18 r = (2*(%pi)*f*L)/Qcoil // internal
    resistance (ohms)
19 req = (Qcoil^2)*r // equivalent
    resistance (k ohms)
20 ro = (R*req)/(req-R) // output
    resistance (k ohms)
21
22 // Part d
23 BW = 5 // bandwidth (kHz
    )
24 Qcircuit = f/BW // circuit
    inductance
25 Req = Qcircuit*2*(%pi)*f*L // equivalent
    resistance (k ohms)
26 Rl = (Req*R)/(R-Req) // load
    resistance (k ohms)
27
28 // Results
29 printf ("a) coil inductance is %.2f mH",L)
30 printf ("b) circuit output impedance at resonant freq
    is %.2f K ohms",R/1E+3)
31 printf ("c) internal resistance ro is %.2f k ohms",ro
    /1E+3)
32 printf ("d) value of load resistance is %.2f k ohms",
    Rl/1E+3)

```

Scilab code Exa 4.11 Example

```
1
2
3 //Variable declaration
4 fo = 50 //output frequency
   (KHz)
5 L = 10^-3 //inductance(H)
6 ro = 100 //output
   resistance(k ohms)
7 Q = 80 //coil inductance
8 Ri = 10 //input resistance
   (k ohms)
9 beta = 125 //common emitter
   current gain
10
11 //Calculations
12 //Part a
13 C = 1/(((2*(%pi)*fo)^2)*L) //tunning capacitance(
   nF)
14 r = (2*(%pi)*fo*L)/Q //internal resistance
   (k ohms)
15 req = (Q^2)*r //equivalent
   resistance(k ohms)
16 R = (ro*req)/(ro+req) //ro || req(k ohms)
17 Avo = -(beta*R)/Ri //voltage gain
18
19 //Part b
20 Qcircuit = R/(2*(%pi)*fo*L) //circuit inductance
21 BW = fo/Qcircuit //bandwidth
22
23 //Results
24 printf ("a) value of capacitance is %.f nF",C/1E-3)
25 printf (" gain is %.1f",Avo)
```

```
26 printf ("b)bandwidth is %.f Hz",BW/1E-3)
27 printf ("Note : value used for beta in textbook is
    wrong in the solution")
```

Scilab code Exa 4.12 Example

```
1 //Variable declaration
2
3 f = 1*10^6 //radio frequency(Hz)
4 beta = 50 //common emitter
    current gain
5 fT = 5*10^6 //short circuit current
    gain bandwidth product(Hz)
6
7 //Calculations
8 betaf = fT/f //measurement of short
    circuit current gain
9 fbeta = fT/beta //frequency at beta(Hz)
10
11 //Results
12 printf ("frequency is %.f Hz",fbeta)
13 if fbeta<1*10^6 then
14     printf ("transistor is not suitable for 1Mhz
        amplifier as fbeta is less than 1Mhz")
15 else
16     printf ("transistor is suitable for 1Mhz
        amplifier")
17 end
```

Scilab code Exa 4.13 Example

```
1
2
```



```

3 //Variable declaration
4 rpi = 2 //dynamic junction
   resistance(K ohms)
5 beta = 50. //common emitter
   current gain
6 f = 1 //frequency(MHz)
7 beta1 = 2.5 //common emitter
   current gain
8 f1 = 20*10^6 //frequency(Hz)
9
10 //Calculations
11 fT = beta1*f1 //short circuit
   current gain bandwidth product(Hz)
12 fbeta = fT/beta //frequency at beta(
   Hz)
13 Cpi = 1/(2*(%pi)*fbeta*rpi) //dynamic capacitance(
   pF)
14
15 //Results
16 printf ("fT is %.f MHz",fT/1e+6)
17 printf ("fB is %.f MHz",fbeta/1e+6)
18 printf ("Cpi is %.f pF",Cpi/1e-9)

```

Scilab code Exa 4.14 Example

```

1
2
3 //Variable declaration
4 R1 = 60 //resistance(k ohms)
5 R2 = 140 //resistance(k ohms)
6 Rs = 4 //source resistance(k ohms)
7 Re = 3 //emitter resistance(k ohms)
8 Rc = 4 //collector resistance(k
   ohms)
9 Vcc = 10 //supply voltage to

```

```

    collector (V)
10 Vbe = 0.7 //base to emitter voltage (V)
11 beta = 100 //common emitter current
    gain
12 Av0 = -30 //voltage gain
13
14 // Calculations
15 //Part a
16 Rb = (R1*R2)/(R1+R2) //R1 || R2 (k
    ohms)
17 Vth = (Vcc*R1)/(R1+R2) //thevinine 's
    voltage (V)
18 Ib = (Vth-Vbe)/(Rb+(beta+1)*Re) //base current
    (uA)
19 Ic = Ib*beta //collector
    current (mA)
20 Vce = Vcc-(Rc*Ic)-((beta+1)*Ib*Re) //collector to
    emitter voltage (V)
21
22 //Part b
23 rpi = ((25*beta)/Ic)*10^-3 //dynamic
    junction resistance (k ohms)
24 r = (Rb*rpi)/(Rb+rpi) //resistance
    across Vs
25 Ib1 = r/((Rs+r)*rpi) //base current (
    mA)
26 Rl = (-Rc*Av0)/(Av0+(beta*Ib1*Rc)) //load
    resistance (k ohms)
27
28 // Results
29 printf ("value of Ic and Vce are %.3f mA and %.2f V"
    ,Ic,Vce)
30 printf ("Rl is %.2f k ohms",Rl)

```

Scilab code Exa 4.15 Example

```

1
2
3 //Variable declaration
4 R1 = 25. //resistances(k ohms)
5 R2 = 100. //resistances(k ohms)
6 Re = 2. //emitter resistance(k
    ohms)
7 Vcc = 10. //supply voltage to
    collector
8 Vbe = 0.7 //base to emitter
    voltage(V)
9 beta = 100. //common emitter
    current gain
10 Av0 = 160 //voltage gain
11 Rs = 1 //source resistance(k
    ohms)
12 Vs = 1 //source voltage(V)
13 Rl = 12.5 //load resistance(k
    ohms)
14 Rc1 = 20. //collector resistance
    (k ohms)
15
16 //Calculations
17 //Part a
18 Rb = (R1*R2)/(R1+R2) //R1||R2
19 Vth = (Vcc*R1)/(R1+R2) //thevinines
    voltage(V)
20 Ib = (Vth-Vbe)/(Rb+(beta+1)*Re) //base current(uA)
21 Ic = Ib*beta //collector
    current(mA)
22 rpi = (25*beta)*10^-3/Ic //dynamic
    junction resistance(k ohms)
23
24 //Part b
25 Ib1 = 1/rpi //small signal
    analysis
26 Rc = -Av0/(-beta*Ib1) //collector
    resistance()

```

```

27
28 //Part c
29 r = (Rc1*rpi)/(Rc1+rpi)           //Rc1 || rpi1 (k
    ohms)
30 Ib2 = (Vs*r)/((1+r)*rpi)         //base curret
    (mA)
31 Rc2 = 6.84                       //collector
    resistance(k ohms)
32 Av0 = -(beta*Ib2)*((R1*Rc2)/(R1+Rc2)) //voltage
    gain
33
34 //Results
35 printf ("value of Ic %.3f mA and rpi is %.2f k ohms"
    ,Ic,rpi)
36 printf ("Rc is %.2f k ohms",Rc)
37 printf ("Av0 is %.1f",Av0)

```

Scilab code Exa 4.16 Example

```

1 //Variable declaration
2 R1 = 12.           //resistance(k ohms)
3 R2 = 100.         //resistance(k ohms)
4 Rc = 2           //collector resistance(k
    ohms)
5 Ic = 1.2         //collector current(mA)
6 beta = 60       //common emitter current
    gain
7 Ib1 = 1         //(say)
8 Rs = 1          //source resistance(k ohms)
9 Vs = 1          //source vcoltage(say)
10
11 //Calculations
12 //Part a
13 rpi = ((25*beta)/Ic)*10^-3       //dynamic junction
    resistance(k ohms)

```

```

14 Rb = (R1*R2)/(R1+R2)           //R1||R2(k ohms)
15 r = (Rb*rpi)/(Rb+rpi)         //Rb|| rpi(k ohms)
16 Ro1 = (Rc*rpi)/(Rc+rpi)       //Rc|| rpi(k ohms)
17 Vo1 = -(beta*Ib1*Ro1)         //base to emitter
    voltage(V)
18 Vbe2 = Vo1
19 Ib2 = Vo1/rpi                 //base current(mA)
20 Ai = Ib2/Ib1                 //current gain
21
22 //Part b
23 Ib11 = (Rs*r)/((Rs+r)*rpi)    //base currents(
    mA)
24 Ib21 = Ib11*Ai               //base current(mA)
25 Avo1 = Ib21*rpi              //voltage gain
26 Vo1 = Avo1
27
28 //Results
29 printf ("current gain is %.2f",Ai)
30 printf ("overall voltage gain is %.2f",Avo1)
31 printf ("Note : solution in the textbook is
    incorrect")

```

Scilab code Exa 4.17 Example

```

1 //Variable declaration
2 beta = 50.                    //common emitter current
    gain
3 R1 = 25.                      //resistance(k ohms)
4 R2 = 75.                      //resistance(k ohms)
5 Ic = 1.25                     //collector current(mA)
6 Vcc = 10                      //supply voltage to
    collector(V)
7 s = 10*10^-3                 //signal strength(V)
8 Rs = 0.5                      //output impedance(k ohms)
9 Vo = 1                        //output voltage(V)

```

```

10 Vs = 1. //source voltage(V)
11 V1 = 12 //load at output terminal(
    V1)
12 Vbe = 0.7 //base to emitter voltage(
    V)
13 R1 = 12
14
15 //Calculations
16 rpi = ((25*beta)/Ic) //dynamic junction
    resistance(k ohms)
17 Rb = (R1*R2)/(R1+R2) //R1||R2(k ohms)
18 r = (Rb*rpi*10^-3)/(Rb+rpi*10^-3) //Rb
    ||rpi(k ohms)
19 Avo = ((Vo*rpi)/Vcc) //voltage
    gain
20 Ib = (r*Vs)/(Rs+r)*Vs //base
    current(mA)
21 Rc = (R1*Avo)/(beta*Ib*R1-Avo) //collector
    resistance(k ohms)
22 Vth = (Vcc*R1)/(R1+R2) //thevinine
    's voltage(V)
23 Ib1 = Ic/beta //base
    current(mA)
24 Re = (Vth-Vbe-(Rb*Ib1))/((beta+1)*Ib1) //emitter
    resistance(k ohms)
25
26 //Results
27 printf ("value of Rc is %.2f and Re is %.2f k ohms",
    Rc,Re)
28 printf (" Vth value is wrong substituted in the book
    ")

```

Scilab code Exa 4.18 Example

1

```

2
3 //Variable declaration
4 Cpi = 20*10^-9 //opening capacitor (F)
5 Cu = 5*10^-9
6 C = 50*10^-9 //here C = C1+Cw
7 rpi = 3.75*10^3 //dynamic drain resistance(
    ohms)
8 r1 = 4*10^3 //resistance (ohms)
9 r2 = 42*10^3 //resistance (ohms)
10 r3 = 303*10^3 //resistance (ohms)
11 f = 20 //frequency (Hz)
12 beta = 100 //common emitter current
    gain
13 Rl = 10*10^3 //load resistance (ohms)
14
15 //Calculations
16 //Part a
17 Req = (((r1*r2)/(r1+r2)+rpi)*r3)/(((r1*r2)/(r1+r2)+
    rpi)+r3) //equivalent resistance (ohms)
18 Ce = (beta+1)/(2*(%pi)*f*Req) //emitter capacitance
    (uF)
19
20 //Part b
21 gm = beta/rpi //transconductance
22 Ro = (Rl*r1)/(r1+Rl) //output resistance
    (k ohms)
23 Ceq = Cpi+(Cu*(1+gm*Ro)) //equivalent
    capacitance (pF)
24 Co = C+(Cu*(1+(1/(gm*Ro)))) //output
    capacitance (pF)
25 r = (rpi*r1)/(rpi+r1) //rpi || r1
26 w21 = 1/(Ceq*r) //lower cutoff
    frequency (MHz)
27 w22 = 1/(Co*Ro) //higher cutoff
    frequenct (MHz)
28
29 //Part c

```

```

30 gm = 79.2
31 Ro = 0.75
32 Ceqnew = 20+(5*(1+((gm*Ro))))           //as gain is
    reduced to 75% of original value
33 wHnew = (10^12)/(Ceqnew*r)/10**6
    //corner value of high frequency(Mrad/s)
34 fHnew = wHnew/(2*(%pi))                 //new
    value of higher frequency cutoff(KHz)
35
36 //Results
37 printf ("a) value of bypass capacitor Ce is %.f uF",
    Ce/1E-6)
38 if w21>w22 then
39     printf ("higher frequency is w21")
40 else
41     printf ("higher frequency is w22")
42 end
43
44 printf ("b) high frequency cut-off is %.2f Mrad/s",
    w22/1E+3)
45 printf ("c) high frequency cut-off is %.3f MHz", fHnew
    )

```

Scilab code Exa 4.19 Example

```

1
2
3 //Variable declaration
4 Vcc = 3.           //supply voltage to
    collector(V)
5 Vee = -3.         //supply voltage to
    emitter(V)
6 r1 = 40.          //resistance(ohms)
7 r2 = 25.          //resistance(ohms)
8 r3 = 1.56         //resistance(ohms)

```



```

9 Vs = 3. //source voltage(V)
10 beta = 200 //common emitter current
    gain
11 r4 = 0.6 //resistance(ohms)
12 r5 = 0.15 //resistance(ohms)
13 Vbe = 0.7 //base to emitter
    voltage
14 r = 0.5 //resistance(k ohms)
15 fL = 20 //frequency(Hz)
16 Req1 = 24.24 //solving r || (Rth+rpi+R
    ) || Re
17 f = 2 //non dominant cutoff
    freq is fL/10 i.e 20/10
18
19 //Calculations
20 //Part a
21 Vth = Vs-(((Vcc-Vee)/(r1+r2))*r1) //
    thevinine 's voltage(V)
22 Rth = (r1*r2)/(r1+r2) //
    thevinine 's voltage(V)
23 Ib = (Vth-Vbe+Vcc)/(Rth+((r4+r5)*(beta+1))) //base
    current(mA)
24 Ic = Ib*beta //
    Collector current(mA)
25 Vo = Vcc-(r3*Ic) //
    output voltage(V)
26
27 //Part b
28 rpi = (25*beta)/Ic //
    dynamic drain resistance(ohms)
29 R = r4*(beta+1) //
    resistance(k ohms)
30 ro = (rpi*R)/(rpi+R) //rpi ||
    R(k ohms)
31 Req = r+((Rth*ro)/(Rth+ro)) //
    equivalent resistance(k ohms)
32 Cc1 = 1/(Req*2*(%pi)*fL) //coupling
    capacitor(uF)

```

```

33
34 //Part c
35 Ce = 1/(2*(%pi)*fL*Req1) //emitter
    capacitance(uF)
36 CE = beta*Ce //emitter
    capacitance(uF) after current gain
37
38 //Part d
39 Ce1 = 1/(2*(%pi)*f*Req1) //emitter
    capacitance(uF)
40 CE1 = beta*Ce1 //emitter
    capacitance(uF) after current gain
41 Csum = Cc1+CE1 //total
    capacitance(uF)
42
43 //Results
44 printf ("a)Ic and Vo are %.2f mA and %.f V",Ic,Vo)
45 printf ("b)Cc1 is %.3f uF",Cc1/1E-3)
46 printf ("c)Ce is %.1f uF",CE/1E-3)
47 printf ("d)Csum is %.3f uF",Csum/1E-2)

```

Scilab code Exa 4.21 Example

```

1
2
3 //Variable declaration
4 gm = 2 //transconductance
5 rd = 200*10^3 //dynamic drain resistance(
    ohms)
6 Cgs = 10 //gate to source
    capacitance(pF)
7 Cgd = 0 //gate to drain capacitance
    (pF)
8 Rs = 1*10^3 //source resistance(ohms)
9 Rg = 1*10^6 //Rg = R1||R2

```

```

10 Rd = 5*10^3           //drain resistance(ohms)
11 Rs1 = 2              //resistance(k ohms)
12 Cc1 = 0.1*10^-6     //coupling capacitors(F)
13 Cc2 = Cc1
14 Co = 10*10^-12      //output capacitance(F)
15 Vgs = 1              //gate to source voltage(V)
16
17 // Calculations
18 //Part a
19 R = (Rd*rd)/(Rd+rd)  //Rd||rd(k ohms)
20 Avo = -Vgs*gm*R      //voltage gain
21 Vo = Avo
22
23 //Part b
24 w11 = 1/(Cc1*(Rs*Rg)) //corner freq(rad/s)
25 wL = w11             //input circuit
    corner freq(rad/s)
26
27 //Part c
28 w22 = 10^12/((Cgs*R)*10^3) //output circuit
    corner frequency(rad/s)
29 wH = w22/(2*%pi)
30
31 //Part d
32 G = -Avo*wH          //gain bandwidth
    product
33
34 //Part e
35 Rd = 4*10^3          //drain resistance
    reduced(ohms)
36 Rnew = (Rd*rd)/(Rd+rd) //new resistance(
    ohms)
37 Avo1 = -Vgs*gm*Rnew  //new voltage gain
38 BWnew = (10^8/Rnew)/(2*%pi) //new
    bandwidth(Mrad/s)
39 Gnew = -Avo1*BWnew   //gain bandwidth
    product new
40

```

```

41 //Results
42 printf ("a)Avo is %.2 f" ,Avo/1E+3)
43 printf ("b)wL is %.2 f rad/s" ,wL/1E-3)
44 printf ("c)wH is %.1 f MHz" ,wH/1E+3)
45 printf ("d)G is %.2 f MHz" ,G/1E+6)
46 printf ("e)Gnew is %.1 f MHz" ,Gnew/1E+6)

```

Scilab code Exa 4.23 Example

```

1
2
3 //Variable declaration
4 gm = 1 //transconductance
5 rd = 40 //dynamic drain resistance
   (k ohms)
6 Cgs = 5 //gate to source
   capacitance (pF)
7 Cgd = 1 //gate to drain
   capacitance (pF)
8 Cds = 1 //drain to source
   capacitance (pF)
9 Avo1 = 20. //voltage gain of JFET 1
10 Avo2 = 8. //voltage gain of JFET 2
11 R1 = 5 //resistance(k ohms)
12 R2 = 20 //resistance(k ohms)
13 R3 = 8 //resistance(k ohms)
14
15 //Calculations
16 //Part a
17 Avo = Avo1*Avo2 //voltage gain
18 Ceq1 = Cgs+Cgd*(1+Avo1) //input circuit for
   first JFET
19 Co1 = Cds+(Cgd*(1+(1/Avo1))) //output circuit for
   first JFET
20 Ceq2 = Cgs+Cgd*(1+Avo2) //input circuit for

```

```

    second JFET
21 Co2 = Cds+(Cgd*(1+(1/Avo2))) //output circuit for
    second JFET
22
23 //Part b
24 w21 = 1/(R1*Ceq1) //input circuit
    frequency
25 w2 = 10^12/(R2*10^3*(Co1+Ceq2)) //common
    circuit frequency
26 w22 = 1/(R3*Co2) //output circuit
    frequency
27
28
29 //Results
30 printf ("a)Avo is %.1f",Avo)
31 printf ("b)w21,w2,w22 are %.2f Mrad/sec , %.2f Mrad/
    sec and %.2f Mrad/sec",w21/1E-3,w2/1E+6,w22/1E-3)
32 printf ("nondominant corner freq is %.2f Mrad/sec",
    w2/1E+6)

```

Chapter 5

Large Signals Amplifiers

Scilab code Exa 5.1 Example

```
1
2
3 //Variable declaration
4 Rb=1*10**3 //base resistance (ohms
   )
5 Vcc=20 //supply voltage(V)
6 Rc=20 //collector resistance
   (ohms)
7 beeta=25 //current gain
8 Vbe=0.7 //base to emitter
   voltage (V)
9 ib=10*10**-3 //base current (ohms)
10
11 //Calculations
12 Ibq=(Vcc-Vbe)/Rb //current (A)
13 Icq=beeta*Ibq //current (A)
14 Vceq=Vcc-(Icq*Rc) //collector voltage(V
   )
15 ic=beeta*ib //collector current (A
   )
16 Po=((ic/(sqrt(2)))**2)*Rc //output voltage (V)
```

```

17 Pi=Vcc*Icq //input power(W)
18 eta=(Po/Pi)*100 //efficiency
19 Pd=Pi-((Icq**2)*Rc)-Po //power dissipated(W)
20
21 //Results
22 printf ("input power is Pi %.1f W",Pi)
23 printf ("output power is Po %.1f W",Po)
24 printf ("power dissipated is %.1f W",Pd)

```

Scilab code Exa 5.2 Example

```

1
2
3 //Variable declaration
4 Rl=500 //load resistance(
   ohms)
5 Vceq=50 //queinscent
   collector voltage(V)
6 beetamin=30 //current gain
   minimum(at Q)
7 Icq=0.4 //queinscent
   collector current(A)
8 Ibq=8 //queinscent base
   current(mA)
9
10 //Calculations
11 Rac=Vceq/Icq //ac resistance(
   ohms)
12 beeta=(Icq*10**-3)/Ibq //current gain
13 Re=5/Icq //emitter
   resistance(ohms)
14 Rc=(512.5*Rac)/(512.5-Rac) //as Re+Rl
   =500+12.5=512.5
15 Vcc=5+Vceq+(Icq*Rc) //supply voltage(
   V)

```

```

16 Rb=(betamin*Re)/10 //base resistance
    (ohms)
17 R1=39.5 //solving 125=Rc
    |(R1+Re) and Vbb=Vcc*(R1/(R1+R2))
18 R2=750
19 Pi=120*Icq //Vcc chosen as
    120
20 r=(Rc*R1)/(Rc+R1)
21 Poac=(100/(2*sqrt(2)))**2/r //output power(W)
22 etamax=Poac/Pi //efficiency
23 Poac1=(100/(2*sqrt(2)))**2/R1 //ac power absorbed by
    load(W)
24 eta=Poac1/Pi
25 Pc=(Icq**2)*Rc //power lost in Rc(W
    )
26 Pe=(Icq**2)*Re //power lost in Re(W
    )
27 Pd=Pi-Pc-Pe-Poac //power consumed(W
    )
28
29 //Results
30 printf("input power is Pi %.1f W",Pi)
31 printf("output power is Po %.2f W",Poac)
32 printf("dissipated power is %.2f W",Pd)
33 printf("values of R1,R2,Re and Rc are %.1f ohms, %
    .1f ohms, %.1f ohms and %.f ohms resp.",R1,R2,Re,
    Rc)
34 printf("Note : Calculated value of Rc is wrong in
    the book")

```

Scilab code Exa 5.3 Example

```

1
2
3 //Variable declaration

```



```

4 Pmax=10 //power maximum(W)
5 Ic=1 //collector current(
  A)
6 Vcemax=100 //max collector to
  emitter current(V)
7 Vcemin=2 //min collector to
  emitter current(V)
8
9 //Calculations
10 //Part a
11 Vceq=46 //Vce at Q point
12 Icq=0.21 //Ic at Q point
13 Vcc=92 //supply voltage(V)
14 ic=0.42 //collector current(A)
15
16 //Part b
17 Rl=Vceq/Icq //load resistance(
  ohms)
18
19 //Part c
20 Pi=Vcc*Icq //input power(W)
21 Po=((ic/(2*sqrt(2)))**2)*Rl //output power(W)
22 eta=(Po/Pi)*100 //efficiency
23
24 //Results
25 printf ("Rl for maximum power input is %.f ohms",Rl)
26 printf ("input power is is %.1f W",Pi)
27 printf ("Po is %.1f",Po)
28 printf ("eta is %.1f %%",eta)

```

Scilab code Exa 5.4 Example

```

1
2
3 //Variable declaration

```

```

4 Vcc=15 //supply voltage(V)
5 beeta=40. //current gain
6 Icq=5. //Ic at Q(mA)
7 Vceq=7.5 //Vce at Q(V)
8 icswing=10 //swing in ic(mA)
9
10 //Calculations
11 //Part a
12 Rl=Vceq/Icq*10**-3 //load resistance(ohms)
13
14 //Part b
15 Ibq=Icq/beeta //base current at Q(uA)
16
17 //Part c
18 ibswing=icswing/beeta //swing in
    ib(mA)
19 Pac=Rl*(icswing/(2*sqrt(2)))**2 //ac power(W)
20 Pdc=Vcc*(Icq*10**-3) //dc power(W)
    )
21 eta=(Pac/Pdc)*100 //efficiency
22
23 //Results
24 printf ("a) value of Rl is %.f ohms",Rl/1E-6)
25 printf ("b) Ibq is %.f uA",Ibq/1E-3)
26 printf ("c) ac power output is %.2f mW",Pac/1E-3)
27 printf ("efficiency is %.1f %%",eta)
28 printf ("corresponding swing in ib is %.2f mA",
    ibswing)

```

Scilab code Exa 5.5 Example

```

1
2
3 //Variable declaration
4 Vcc=10 //supply voltage(V)

```

```

5 Vce=10
6 Icq=140*10**-3           //Ic at Q point(A)
7 Rl=8                     //load resistance(ohms)
8 vce=16                   //instantaneous
   collector to emitter voltage(V)
9 ic=235*10**-3           //instantaneous
   collector current(A)
10
11 //Calculations
12 RL=Vcc/Icq
13 r=sqrt(RL/Rl)           //load
   resistance for max ac swing(ohms)
14 Po=(vce*ic)/(2*sqrt(2)*2*sqrt(2)) //output power(
   W)
15 Pi=Vcc*Icq             //
   input power(W)
16 eta=Po/Pi              //
   efficiency
17 Pd=Pi-Po              //
   dissipated power(W)
18
19 //Results
20 printf ("a)transformation ratio is %.f",r)
21 printf ("c)power output is %.2f W",Po)
22 printf ("efficiency is %.2f %%",eta*100)

```

Scilab code Exa 5.6 Example

```

1
2
3 //Variable declaration
4 Rl=4.5                   //load resistance(ohms)
5 Vceq=50                 //Vc at point Q(V)
6 Icq=400*10**-3         //Ic at Q(A)
7 Re=12.5                 //emitter resistance(ohms)

```

```

8 Vcemax=90 //from figure
9 Vcemin=10 //from figure
10 Icmax=730 //max Ic (mA)
11 Icmin=30 //min Ic (mA)
12
13 // Calculations
14 //Part a
15 Rac=Vceq/Icq //ac resistance (ohms)
16 n=sqrt(Rac/Rl) //as n=N1/N2 and Rac=(N1/N2)
    ^2*Rl
17
18 //Part b
19 Vcc=Vceq+(Icq*Re) //supply voltage (V)
20
21 //Part c
22 vce=Vcemax-Vcemin
    //
    instantaneous collector to emitter voltage (V)
23 ic=Icmax-Icmin
    //
    instantaneous collector current (mA)
24 Po=(vce*ic)/((2*sqrt(2))*(2*sqrt(2))) //output
    voltage (V)
25 Pi=Vcc*Icq //input
    voltage (V)
26 eta=(Po/Pi)*100 //efficiency
27 Pd=Pi-(Icq**2*Re)-Po*10**-3 //dissipated power (W)
28
29 // Results
30 printf ("a)transformation ratio is %.2f",n)
31 printf ("b)Vcc is %.1f V",Vcc)
32 printf ("c)power efficiency for the load is %.1f %%"
    ,eta/1E+3)
33 printf ("power dissipated is %.1f W",Pd)

```

Scilab code Exa 5.7 Example

```

1
2 //Variable declaration
3 Vcc=30 //supply voltage(V)
4 Rl=16 //load resistance(ohms
   )
5 n=2 //transformation ratio
6 Im=1 //peak value of
   current(A)
7 etamax=78.54 //max efficiency(%)
8
9 //Calculations
10 //Part a
11 Rl1=Rl*(n/2)**2 //load resistance(
   ohms)
12 Pi=(2*Vcc*Im)/%pi //input power(W)
13 Pimax=(2*Vcc**2)/((%pi)*Rl1) //input power max(W)
14
15 //Part b
16 Po=((Im**2)*Rl1)/2 //output power(W)
17 Pomax=(Vcc**2)/(2*Rl1) //output power max(
   W)
18
19 //Part c
20 eta=Po/Pi //efficiency
21
22
23 //Part d
24 P=((2*Vcc*Im)/%pi)-((Im**2*Rl1)/2) //Power
   dissipated by transistors(W)
25 Pd=P/2 //power
   dissipated by each transistors
26 Pmax=(2*Vcc**2)/((%pi)**2*Rl1) //max power

```

```

    dissipated by transistors
27 Pdmax=Pmax/2 //max power
    dissipated by each transistor
28
29 //Results
30 printf ("a)input power is %.1f W and max input
    power is %.2f W",Pi,Pimax)
31 printf ("b)output power %.1f W and max output power
    is %.2f W",Po,Pomax)
32 printf ("c)power efficiency for the load is %.2f %%
    and its max value is %.2f %%",eta/1E-2,etamax)
33 printf ("power dissipated by each transiator is %.1f
    W and max value is %.1f W",Pd,Pdmax)

```

Scilab code Exa 5.8 Example

```

1
2 //Variable declaration
3 Pd=10
4
5 //Calculations
6 //Part a
7 Poacmax=10. //as Pd=Po(ac)max by
    class A
8
9 //Part b
10 Pd=2*Poacmax //power dissipated (W)
11 Poacmax1=146/2 //max output power by
    class B
12 f=Poacmax1/Poacmax //factor by which power
    of class B is greater than class A
13
14 //Results
15 printf ("maximum signal output powerclass A produce
    is %.1f W",Poacmax)

```

```

16 printf ("maximum signal output powerclass produce
    is %.1f W",Poacmax1)
17 printf ("factor by which power in class b is larger
    than power in class A transformer is %.1f",f)

```

Scilab code Exa 5.9 Example

```

1
2
3 //Variable declaration
4 Vcc=30. //supply voltage(V)
5 Im=1 //peak value of
    current(A)
6 Rl=10. //load resistance(
    ohms)
7
8 //Calculations
9 //Part a
10 Pi=(Vcc*Im)/%pi //input power(W)
11 Pimax=(Vcc**2)/(%pi*2*Rl) //max input power(W)
12
13 //Part b
14 Po=((Im**2)*Rl)/2 //output power(W)
15 Pomax=(Vcc**2)/(8*Rl) //output power max(W)
    )
16
17 //Part c
18 eta=Po/Pi //efficiency
19 etamax=Pomax/Pimax //efficiency max
20
21 //Part d
22 Pd=Pi-Po //Power
    dissipated by transistors(W)
23 Pmax=(Vcc**2)/(2*(%pi)**2*Rl) //max power
    dissipated by transistors

```

```

24
25 // Results
26 printf ("a)input power is %.2f W and max input power
        is %.2f W",Pi,Pimax)
27 printf ("b)output power is %.1f W and max output
        power is %.2f W",Po,Pomax)
28 printf ("c)power efficiency for the load is %.2f %%
        and its max value is %.2f %%",eta/1E-2,etamax/1E
        -2)
29 printf ("power dissipated and its max value are %.2f
        W and %.2f W",Pd,Pmax)

```

Scilab code Exa 5.10 Example

```

1
2
3 // Variable declaration
4 P1=2 //transistor power(W)
5 R1=5*10**3. //load resistance()
6 Ic=35 //collector current(mA)
   )
7
8 // Calculations
9 Bo=40-Ic
10 B1=sqrt((2*P1)/R1)
11 B2=Bo
12 D2=(B2/B1)*100 //second harmonic
   distortion(%)
13
14 // Results
15 printf ("second harmonic distortion is %.2f %%", (D2
        /1E+3))

```

Scilab code Exa 5.12 Example

```
1
2
3 //Variable declaration
4 Vcc=15. //supply voltage(
    V)
5 Rl=10. //load resistance
    (ohms)
6
7 //Calculations
8 //Part a
9 Immax=Vcc/Rl //max peak current
    (A)
10 Irmsmax=Immax/(sqrt(2)) //max rms current(A)
11 Pomax=Irmsmax**2*Rl //max output power
    (W)
12 Pi=(2*Vcc*Immax)/%pi //max input power(W)
13 eta=Pomax/Pi //efficiency
14
15 //Part b
16 Im=(2*Vcc)/(%pi*Rl) //peak
    current(A)
17 Pdmmax=((2*Vcc*Im)/(%pi))-((Im**2*Rl)/2) //max
    power dissipated(W)
18 eta1=((Im**2)*Rl*%pi)/(2*2*Vcc*Im) //
    efficiency
19
20 //Results
21 printf ("a)max signal output power, collector
    dissipation are %.2f W , %.2f W and efficiency
    is %.2f %%", Pomax, Pi, eta/1E-2)
22 printf ("b)max dissipation of each transistor and
    corresponding efficiency is %.2f W and %.1f resp.
    ", Pdmmax, eta1)
```

Scilab code Exa 5.13 Example

```
1 // Calculations
2 eta=0.5 //As  $Po(ac)=Vcc^2/2*\pi^2*Rl$  and
    $Pi(dc)=Vcc^2/\pi^2*Rl$ 
3 //put these in  $eta=Po(ac)/Pi(dc)$ 
   which is  $1/2=0.5$ 
4
5 // Results
6 printf ("push pull amplifier efficiency is %.f %%",
   eta/1E-2)
```

Chapter 6

Feedback Amplifiers And Oscillators

Scilab code Exa 6.1 Example

```
1 //Variable declaration
2 Vo=12.           //output voltage (V)
3 f=1.5*10**3     //frequency (Hz)
4 h=0.25          //second harmonic content (%)
5 ho=2.5          //reduced harmonic content of
   output (%)
6 A=100           //power amplifier gain
7
8 //Calculations
9 Vd=Vo*h         //second harmonic content in
   output (V)
10 Vd1=Vo*ho      //reduced value of second
   harmonic content (V)
11 beta=((Vd1/Vd)-1)/A //feedback gain from formula
   Vd1=Vd/(1+beta*A)
12 Vs=Vo*(1+beta*A)/A //signal voltage (V) from
   formula (A/(1+Beta*A))*Vs
13 V=Vo/A         //signal input needed without
   feedback
```

```

14 s=Vs/V //additional signal
    amplification needed before feedback amplifier
15
16 //Results
17 printf ("feedback gain is %.2f",beta)
18 printf ("signal input to the overall system is %.1f"
    ,s)

```

Scilab code Exa 6.2 Example

```

1 //Variable declaration
2 w2=10**4. //corner frequency(rad/s)
3 w2new=10**5. //new corner frequency(rad/s)
4 Ao=1000. //high frequency response
5
6 //Calculations
7 beta=((w2new/w2)-1)/Ao //feedback factor
8 Anew=Ao/(1+beta*Ao) //overall gain of amplifier
    from formula w2new=w2(1+beta*Ao)
9 p=w2*Ao //gain bandwidth product
    without feedback from formula Anew=Ao/1+beta*Ao
10 pnew=Anew*w2new //gain bandwidth product with
    feedback
11
12 //Results
13 printf ("beta is %.3f",beta)
14 printf ("overall gain is %.1f",Anew)
15 printf ("gain-bandwidth products with and without
    feedback are %.1f and %.1f resp.",p,pnew)

```

Scilab code Exa 6.3 Example

```

1 //Variable declaration

```

```

2 A=100. //high frquency
   response
3 Af=100 //gain
4 A1=A**2 //forward gain
5 A1new=50 //gain reduces
   to 50%
6
7 //Calculations
8 beta=((A1/Af)-1)/A1 //feedback
   factor
9 Afnew=A1new**2/(1+beta*A1new**2) //new value of
   A
10 g=Af-Afnew //reduction in
   overall gain
11
12 //Results
13 printf ("%%" change in gain of feedback unit is %.2f
   ",g)

```

Scilab code Exa 6.4 Example

```

1 //Variable declaration
2 beta=0.008 //positive gain
3
4 //Calculations
5 Ao=-(8/beta)**(1/3) //A=Ao/2,so beta(A^3)
   =-1
6
7 //Results
8 printf ("%%" change in gain of feedback unit is %.f",
   Ao/1E-1)

```

Scilab code Exa 6.5 Example

```

1
2 //Variable declarations
3 A = complex(0,60)           // amplifier
4 B = complex(0,30)         // amplifier
5 AB = A*B
6 C = (1+A)/AB              //condition for
   oscillation
7 phi = phasemag(C)         //phase
8
9 //Result
10 printf ( "C = %.4f with phase = %.2f ",abs(C),phi)

```

Scilab code Exa 6.7 Example

```

1 //Variable declaration
2 Rbb=8*10**3               //base resistance(k
   ohms)
3 eta=0.7                  //efficiency
4 R1=0.2                   //R1(k ohms)
5 Rt=40*10**3             //Rt(ohms)
6 Ct=0.12*10**-6         //capacitance(F)
7 Vv=2                     //capacitor is charged
   to voltage(V)
8 Iv=10*10**-3            //current to capacitor(A
   )
9 Ip=10*10**-3            //peak current(A)
10 Vd=0.7                 //diode voltage(V)
11 V=12.                  //voltage(V)
12
13 //Calculations
14 //Part a
15 Rb1=eta*Rbb             //base resistance(ohms)
16 Rb2=Rbb-Rb1            //base resistance(ohms)
17
18 //Part b

```

```

19 Vp=Vd+((Rb1+R1)*V/(Rbb+R1)) //peak voltage (V)
20
21 //Part c
22 Rtmin=(V-Vv)/Iv //Rt minimum(k ohms)
23 Rtmax=(V-Vp)/Ip //Rt minimum(k ohms)
24
25 //Part d
26 Rb11=.12 //resistance during
    discharge(ohms)
27 t1=Rt*Ct*1.27 //charging time(mS)
28 t2=(Rb11+R1)*Ct*1.52 //discharging time(uS)
29 T=t1+t2 //cycle time
30 foscE=1/T //oscillations frequency(Hz)
31 foscA=1/(Rt*Ct*1.2) //oscillations frequency(Hz)
32
33 //Part e
34 vR1=(R1*V)/(R1+Rbb) //vR1 at discharging
    period
35 vR1d=(R1*(Vp-Vd))/(R1+Rb11) //vR1 at
    discharging period
36
37 //Results
38 printf ("Rb1 and Rb2 are %.1f k ohms and %.1f k ohms
    resp.",Rb1/1E+3,Rb2/1E+3)
39 printf ("Vp is %.1f V",Vp)
40 printf ("Rtmin is %.f k ohms and Rtmax is %.f k ohms
    ,hence Rt is in the range",Rtmin/1E+3,Rtmax/1E+1)
41 printf ("foscE is %.f Hz and foscA is %.f Hz",foscE,
    foscA)
42 printf ("vR1 is %.3f and vRd1 is %.2f V ",vR1/1E-3,
    vR1d)
43 printf("(range of Rt is wrong in the book)")

```

Scilab code Exa 6.8 Example

```

1 //Variable declaration
2 A=1500 //voltage gain
3 beta=1/25. //current gain
4
5 //Calculations
6 //Part a
7 Af=A/(1+A*beta) //voltage gain with
  feedback
8
9 //Part b
10 g=0.1 //amplifier gain
  changes by 10%=0.1
11 gf=g/(1+A*beta) //% by which its gain
  in feedback mode changes dAf/Af
12
13 //Results
14 printf (" Amplifier gain with feedback is %.1f ",Af)
15 printf ("%%" by which gain in feedback changes is %.3
  f %%",gf/1E-2)

```

Scilab code Exa 6.9 Example

```

1 //Variable declaration
2 A=500 //voltage gain
3 beta=1/20. //current gain
4 Ro=50*10**3 //output resistance(ohms)
5 Ri=1.5*10**3 //input resistance(ohms)
6
7 //Calculations
8 //Part a
9 Af=A/(1+A*beta) //voltage gain with
  feedback
10
11 //Part b
12 Rif=Ri*(1+(A*beta)) //input resistance(k

```



```

    ohms)
13 Rof=Ro/(1+A*beta)           //output resistance (k
    ohms)
14
15 //Results
16 printf ("Amplifier gain is %.2f",Af)
17 printf ("input resistance is %.f K ohms and output
    resistance is %.2f kW",Rif/1E+3,Rof/1E+3)

```

Scilab code Exa 6.10 Example

```

1 //Variable declaration
2 Ro=50*10**3                 //output resistance (ohms
    )
3 Rd=10*10**3                //drain resistance (ohms)
4 R1=800*10**3               //resistance (ohms)
5 R2=200*10**3               //resistance (ohms)
6 gm=5500*10**-6             //transconductance (us)
7
8 //Calculations
9 r=(Rd*Ro)/(Rd+Ro)          //Rd||Ro
10 R=R1+R2                    //combined resistance
    of R1 and R2
11 Rl=(R*r)/(R+r)             //load resistance (ohms)
12 A=-gm*Rl                   //voltage gain without
    feedback
13 beta=R2/(R1+R2)            //current gain
14 Af=A/(1+A*beta)            //voltage gain with
    feedback
15
16 //Results
17 printf ("Amplifier gain with feedback is %.1f and
    without feedback is %.1f",Af/1E+1,A)

```

Scilab code Exa 6.11 Example

```
1 //Variable declaration
2 Re=1.25*10**3           //emitter resistance (ohms
   )
3 Rc=4.8*10**3           //collector resistance (
   ohms)
4 Rb=800*10**3           //base resistance (ohms)
5 rpi=900                 //dynamic resistance (ohms
   )
6 Vcc=16                  //supply voltage (V)
7 beta=100.               //current gain
8
9 //Calculations
10 A=-(beta/rpi)          //amplifier voltage gain
11 B=-Re
12 V=(A*Rc)/(1+B*A)      //V=Vo/Vs
13
14 //Results
15 printf (" Amplifier voltage gain is %.1f",V)
```

Scilab code Exa 6.12 Example

```
1
2
3 //Variable declaration
4 C1=800*10**-9           //capacitance (F)
5 C2=2400*10**-9         //capacitance (F)
6 L=50*10**-6             //inductance (H)
7
8 //Calculations
```

```

9 Ceq=(C1*C2)/(C1+C2) //equivalent
   capacitance (F)
10 fo=1/(2*%pi*sqrt(L*Ceq)) //output frequency (Hz)
11
12 //Results
13 printf ("the oscillation frequency is %.2f KHz",fo/1
   E+3)

```

Scilab code Exa 6.13 Example

```

1
2
3 //Variable declaration
4 C=200*10**-9 //capacitance (F)
5 Lrcf=0.5*10**-3 //shunt across L2
6 L1=800*10**-6 //inductance (H)
7 L2=800*10**-6 //inductance (H)
8 M=200*10**-6
9
10 //Calculations
11 L21=(L2*Lrcf)/(L2+Lrcf) //effective
   value of L2(uH)
12 Leq=L1+L21+2*M //
   equivalent inductance (H)
13 fo=1/(2*%pi*sqrt(Leq*C)) //output frequency (
   Hz)
14
15 //Results
16 printf ("the oscillation frequency is %.2f KHz",fo/1
   E+3)

```

Chapter 7

Operational Amplifiers

Scilab code Exa 7.1 Example

```
1 //Variable declaration
2 V1=120 //negative terminal Vn(uV)
3 V2=80 //positive terminal Vp(uV)
4 Ad=10**3 //difference mode gain
5
6
7 //Calculations
8 Vd=V1-V2 //difference mode signal(uV)
9 Vc=(V1+V2)/2 //common mode signal(uV)
10
11 //Part a
12 CMRR=100. //common mode rejection
    ratio
13 Vo=Ad*Vd*(1+(Vc/(CMRR*Vd))) //output voltage(mV)
14
15 //Part b
16 CMRR=10**5. //common mode
    rejection ratio
17 Vo1=Ad*Vd*(1+(1/CMRR)*(Vc/Vd)) //output voltage(mV)
18
19 //Results
```

```
20 printf ("output voltage is %.f mV",Vo/1E+3)
21 printf ("output voltage is %.f mV",Vo1/1E+3)
```

Scilab code Exa 7.2 Example

```
1 //Variable declaration
2 deltavi=0.5 //change in vi(V)
3 deltat=10 //change in time(us)
4 s=1 //slew rate(V/us)
5
6 //Calculations
7 Kvf=(s*deltat)/deltavi //closed loop gain of
   amplifier
8
9 //Results
10 printf ("closed loop gain of amplifier is %.1f",Kvf)
```

Scilab code Exa 7.3 Example

```
1
2
3 //Variable declaration
4 f=50*10**3. //OPAMP frequency(Hz)
5 Vm=0.02 //maximum value of
   signal voltage(V)
6 S=.5*10**6 //slew rate(V/s)
7
8 //Calculations
9 Kvf=S/(2*(%pi)*f*Vm) //closed loop gain of
   amplifier
10
11 //Results
12 printf ("closed loop gain of amplifier is %.f",Kvf)
```

Scilab code Exa 7.4 Example

```
1 //Variable declaration
2 Ic=100 //current at quinscent point(uA)
3 beta=2000. //current gain
4 Ad=250 //difference mode gain
5 CMRR=5000 //as 74 dB=5000,common mode
   rejection ratio(dB)
6
7 //Calculations
8 rpi=(25*beta)/Ic //dynamic internal resistance(k
   ohms)
9 gm=beta/rpi //transconductance(mS)
10 Re=CMRR/gm //emitter resistance(k ohms)
11 Rc=(Ad*2)/gm //collector resistance(k ohms)
   from formula Ad=gmRc/2
12 Rin=2*rpi //input resistance(k ohms)
13
14 //Results
15 printf ("Re is %.1f k ohms",Re)
16 printf ("Rc is %.1f k ohms",Rc)
17 printf ("input resistance is %.1f k ohms",Rin)
```

Scilab code Exa 7.6 Example

```
1 //Variable declaration
2 Ic=.428 //current at quinscent point(uA)
3 beta=200. //current gain
4 //as 74 dB=5000,common mode
   rejection ratio(dB)
5 Rc=10. //collector resistance(k ohms)
```

```

6 Re=16.           //emitter resistance(k ohms)
7 Vcc=15.         //supply voltage(V)
8
9 //Calculations
10 //Part b
11 Ibq=Icq/beta    //Ib at Q(uA)
12 rpi=(25*beta)/Icq //dynamic resistance(k ohms)
13 gm=beta/rpi     //transconductance
14
15 //Part b
16 vo1=Vcc-(Icq*Rc) //terminal 1 voltage(V)
17 vo2=vo1         //terminal 2 voltage(V)
18
19 //Part c
20 Ad=(gm*Rc)/2    //differential mode gain
21 Ac=Rc/(2*Re)    //common mode gain
22 CMRR=Ad/Ac      //common mode rejection ratio
23
24 //Part d
25 Rid=2*rpi       //differential input
    resistance(k ohms)
26 rpi=11.7        //dynamic resistance(k
    ohms)
27 Ric=rpi+(2*(beta+1)*Re) //common mode input
    resistance(k ohms)
28
29 //Results
30 printf ("Icq is %.3f mA, and Ibq is %.2f uA",Icq,Ibq
    /1E-3)
31 printf ("vo1 and vo2 have same value as %.1f V",vo1)
32 printf ("Ad : %.f , Ac : %.3f and CMRR is %.f",Ad/1E
    -3,Ac,CMRR/1E-3)
33 printf ("Rid is %.1f K ohms and Ric is %.2f Mohms",
    Rid/1E+3,Ric/1E+3)

```

Scilab code Exa 7.7 Example

```
1 //Variable declaration
2 R1=10. //series resistance(K ohms)
3 Rf=10**3. //feedback resistance(k
    ohms)
4 vo=-5. //output voltage(V)
5 Ri=1000 //input resistance(k ohms)
6 Av=2.5*10**5 //gain
7
8 //Calculations
9 v1=-vo*(R1/Rf) //input signal voltage(V)
10 vi=-vo/Av //inverting voltage(V)
11 i1=((v1*10**-3)-vi)/R1 //current through R1(uA)
12 ii=vi/Ri //inverting current(uA)
13 iF=-ii //forward current(uA)
14
15 //Results
16 printf ("value of vi is %.e mV",vi)
17 printf ("value of ii: %.e uA i1: %.e uA and iF is %.
    e uA",ii,i1,iF)
```

Scilab code Exa 7.8 Example

```
1 //Variable declaration
2 Vs=4 //source voltage(V)
3 R1=10. //resistance(k ohms)
4 Vb=2 //voltage at point A and point
    B
5 Va=2
6 Rf=30 //forward resistance(k ohms)
7
8 //Calculations
9 I=(Vs-Vb)/R1 //current(mA)
10 Vo=(-I*Rf)+Vb //output voltage(V)
```



```
11
12 //Result
13 printf ("output voltage %.1f V",Vo)
```

Scilab code Exa 7.9 Example

```
1 //Variable declaration
2 Rf=2 //as vs=2sinwt and vo=(1+Rf/Rs)*vb
   and vB=vA=vs
3 Rs=1
4
5
6 //Calculations
7 vo=(1+(Rf/Rs))*2 //output voltage(V)
8
9 //Result
10 printf ("output voltage %.1f sinwt",vo)
```

Scilab code Exa 7.10 Example

```
1 //Variable declaration
2 Ro=100. //output resistance(ohms)
3 vo=10. //output voltage(V)
4 A=10**5. //gain
5 Ri=100*10**3 //input resistance(ohms)
6 Rs=1*10**3. //resistance(ohms)
7 Rl=10*10**3 //load resistance(ohms)
8
9 //Calculations
10 //Part i
11 iL=vo/Rl //load current(mA)
12 Avi=vo+(iL*Ro) //voltage gain without
   feedback
```

```

13 vi=Avi/A // voltage (V)
14 ii=vi/Ri // current (A)
15 vs=vo+ii*(Rs+Ri) // source voltage (V)
16
17 //Part ii
18 Avf=vo/vs //voltage gain with
    feedback
19
20
21 //Part iii
22 Rif=vs/ii //input resistance (ohms)
23 Rof=Ro/A //output resistance (ohms)
24
25 //Results
26 printf ("vs is %.4f v",vs)
27 printf ("vo/vs that is Avf is %.f",Avf)
28 printf ("input and output resistances are %.2f , %.3
    f ohms",Rif,Rof)

```

Scilab code Exa 7.11 Example

```

1 //Variable declaration
2 Vb=3 //voltage at A and B
3 Va=Vb
4 R1=40*10**3. //input resistance (ohms)
5 t=50*10**-3 //time after switch is
    open (mS)
6 V1=5 //input voltage (V)
7
8 //Calculations
9 //Part a
10 vo=-3 //as Va=Vb=3
11
12 //Part b
13 i1=(V1-Vb)/R1 //input current (A)

```

```

14 vo1=(-250*50*10**-3)- Vb           //vo at 50 mS
15
16 //Result
17 printf ("output voltage %1f V",vo1)
18
19 // Note : Answer in book is wrong.

```

Scilab code Exa 7.14 Example

```

1
2
3 //Variable declaration
4 BW=30*10**3           //specified bandwidth(k Hz
   )
5 fc=18*10**3          //centered frequency(Hz)
6 R1=20                //resistance(k ohms)
7 R2=180               //resistance(k ohms)
8 C=1.2*10**-9         //capacitance(F)
9 G=40                 //pass band gain(dB)
10 g=20                //pass region gain(dB)
11
12 //Calculationsv
13 fc1=fc-(BW/2)        //high pass section
   frequency(Hz)
14 fc2=fc+(BW/2)        //low pass section
   frequency(Hz)
15 Rfc1=1/(2*%pi*fc1*C) //high pass section resistance
   (k ohms)
16 Rfc2=1/(2*%pi*fc2*C) //low pass section resistance(
   k ohms)
17 Gfc1=G-g             //gain at frequency 0.3KHz
   (dB)
18 Gfc2=G-2*6          //gain at frequency 132KHz
   (dB)
19

```

```

20 // Results
21 printf ("R1 and R2 are %.1f K ohms and %.1f K ohms",
        R1,R2)
22 printf ("Rfc1 is %.f k ohms and Rfc2 is %.f k ohms",
        Rfc1/1E+3,Rfc2/1E+3)
23 printf ("filter gain at frequencies 0.3 KHz is %.1f
        dB and 132 k Hz are %.1f dB",Gfc1,Gfc2)

```

Scilab code Exa 7.21 Example

```

1 // Variable declaration
2 R=250 //resistance(k ohms)
3
4 // Calculations
5 //part a
6 R1=-R/(-5) // as vo=-5va+3vb(given),so when vb=0,
        vo/voa=-250/R1=-5
7
8 //part b
9 R2=R1/(2-1) // as va=0
10 // vx=(R1/R1+R)*vob=(1/6)*vb
11 // vy=(R2/R1+R2)*vb
12 // vx=vy
13 // (1/6)*vob=(R2/R1+R2)*vb
14 // vob=3vb
15 // (1/6)*3=R2/(50+R2)
16
17 // Result
18 printf ("R1 and R2 are %.1f K ohms and %.1f K ohms",
        R1,R2)

```

Scilab code Exa 7.22 Example

```

1 //Variable declaration
2 R1=10*10**3 //resistance(k
   ohms)
3 C1=10**-6 //capacitance(uF)
4 C=0.1*10**-6 //capacitance(uF)
5 R=100*10**3 //resistance(k
   ohms)
6
7 //Calculations
8 //part b
9 wc1=1/C1*R1 //angular frequency(
   rad/s)
10 wc2=1/C*R //angular frequency(
   rad/s)
11 wc=wc2 //angular frequency(rad/
   s)
12 wc1=wc2
13
14 //Results
15 printf ("wc1 is %.2f rad/s",wc1/1E+10)
16 printf ("wc2 is %.2f rad/s",wc2/1e+10)

```

Scilab code Exa 7.23 Example

```

1 //Variable declaration
2 vo1=5 //say (V)
3 K=25 //proportionality constant
4 Q=250 //volume of fluid passed
   across metering point(cm^3)
5 R1=2.5 //output resistance(k ohms)
6
7 //Calculations
8 C1=(K*Q)/(R1*vo1) //capacitor(nF)
9
10 //Results

```

```
11 printf ("C1 is %.f uF", C1/1E+1)
12 printf ("vo1 is -5 V when Q=250 cm^3")
```

Chapter 8

Multivibrators And Switching Regulators

Scilab code Exa 8.1 Example

```
1 //Variable declaration
2 C=0.1 //capacitance(uF)
3 R1=10 //resistance(k ohms)
4 R2=2.3 //resistance(k ohms)
5 Vcc=12. //supply voltage(V)
6 R1=10**3. //resistance(k ohms)
7
8 //Calculations
9 //Part a
10 f=1/(0.693*C*(R2+R1/2)) //frequency(Hz)
11
12 //Part b
13 D=(1+(R2/R1))/(1+2*(R2/R1))*100 //duty
    cycle
14
15 //Part c
16 //(i)
17 T1=0.693*C*(R1+R2) //time
    period through R1(ms)
```

```

18 T2=0.693*R2*C //time
    period through R2(ms)
19 Pavg=(Vcc/R1)**2*(T1/(T1+T2)) //average
    power dissipated during current sourcing(mW)
20
21 //Part d
22 Pavg1=(T2/(T1+T2))*(Vcc/R1)**2 //average
    power dissipated during current sinking(mW)
23
24 //Results
25 printf (" %.2f kHz",f)
26 printf ("duty cycle is %.2f %%",D)
27 printf ("average power dissipated in current
    sourcing is %.3f mW",Pavg/1E-3)
28 printf ("average power dissipated in current sinking
    is %.3f mW",Pavg1/1e-3)

```

Scilab code Exa 8.2 Example

```

1
2
3 //Variable declaration
4 t=1 //time constant
5 e=1.8 //e=R1/R2 min=1.8
6 e1=9. //e1=R1/R2 max=9
7
8 //Calculations
9 Betamin=1/(1+e) //current gain
    minimum
10 Betamax=1/(1+e1) //current gain
    maximum
11 Tmax=2*t*log((1+Betamin)/(1-Betamin))
12 Tmin=2*t*log((1+Betamax)/(1-Betamax))
13 fmin=1/Tmax //minimum freq (Hz)
14 fmax=1/Tmin //maximum freq (k Hz)

```



```

15
16 // Results
17 printf ("fmin is %.f Hz and fmax is %.1f KHz",fmin/1
    E-3,fmax)

```

Scilab code Exa 8.3 Example

```

1
2
3 // Variable declaration
4 C=0.01 // capacitance (uF)
5 R2=15 // resistance (k ohms)
6 Va2=4 // voltage (V)
7 Vcc=15. // supply voltage (V)
8 R1=33 // resistance (k ohms)
9
10 // Calculations
11 Va1=0.67*Vcc // voltage (V)
12 Vamax=Va1+Va2 // Va maximum (V)
13 Vamin=Va1-Va2 // Va minimum (V)
14 T1max=C*(R1+R2)*(log((1-(Vamax/(2*Vcc)))/(1-(Vamax/
    Vcc)))) //time period (ms)
15 T1min=C*(R1+R2)*(log((1-(Vamin/(2*Vcc)))/(1-(Vamin/
    Vcc)))) //time period (ms)
16 T2=0.693*R2*C
17 fmax=1/(T1min+T2) //maximum
    frequency (K Hz)
18 fmin=1/(T1max+T2) //miniimum
    frequency (K Hz)
19
20 // Results
21 printf ("minimum freq is %.2f",fmin)
22 printf ("maximum freq is %.2f",fmax)
23 printf (" (solution given in the textbook is
    incorrect)");

```

Scilab code Exa 8.4 Example

```
1 //Variable declaration
2 Vi=25 //input voltage(V)
3 Vsmax=30 //supply voltage max(V
   )
4 Vomn=12 //output minimum voltage
   or load voltage(V)
5 V1=12
6 R1=20 //load voltage (V)
7 Io=15. //output current(mA)
8 Iq=3. //quinscent current of
   regulator (mA)
9 Vo=20. //output voltage(V)
10
11 //Calculations
12 //Part a
13 //(i)
14 Vimax=Vsmax //maximum
   permissible voltage(V)
15 Ro=0 //for Vomn=beta=0
16 //(ii)
17 Vomax=Vi-2
18 betaVomax=Vomax-Vomn //output
   voltage (V)
19 R2max=(R1*betaVomax)/(Vomax-betaVomax) //R2max(k
   ohms)
20 //(iii)
21 R3=betaVomax/Io //R3(k ohms)
22
23 //Part b
24 Vt=(Iq*betaVomax)/Io //common
   terminal fall (V)
25 Vomn1=V1+Vt //voltage
```

```

        output minimum(V)
26
27 //Part c
28 betaVo=Vo-V1 //output
        voltage(V)
29 beta=betaVo/Vo //current gain
30 R2=(R1*betaVo)/(Vo-betaVo) //R2(ohms)
31
32 //Results
33 printf ("a) i) max permissible supply voltage is %.1f
        V", Vimax)
34 printf ("ii) output voltage range for Vi=25V is %.1f
        V to %.1f V and R2max is %.f k ohms", Vomax,
        R2max)
35 printf ("iii) R3 is %.2f kohms", R3)
36 printf ("b) Vomax is %.1f V", Vomax)
37 printf ("c) R2 is %.2f ohms and R3 is %.3f ohms", R2,
        R3)

```

Scilab code Exa 8.5 Example

```

1 //Variable declaration
2 A=.0025 //voltage gain
3 Vi=8 //input voltage(V)
4 R2=1.5 //resistance 2(k ohms)
5 R1=1 //resistance 1(k ohms)
6 V1=5 //load voltage(V)
7
8 //Calculations
9 beta=R2/(R1+R2) //current gain
10 Vo=V1/(1-beta) //output voltage(V)
11 Vo1=(A*Vi)/(1+(A*beta)-beta) //output voltage
        ripple if Vi=8Vp-p
12
13 //Results

```

```

14 printf ("Vo is %.1f V",Vo)
15 printf ("expression of output voltage ripple %.2f Vp
    -p",Vo1)

```

Scilab code Exa 8.6 Example

```

1 //Variable declaration
2 Ro=7.5 //output
    resistance (ohms)
3 hfe=50
4 Ve=20 //voltage given
    to emitter (V)
5 Vbe=0.8 //base to
    emitter voltage (V)
6 Vc=15 //collector
    voltage (V)
7 P=12 //maximum power
    dissipation (W)
8 Ib1=5 //for minimum
    load current I1=0,Ib=5
9
10 //Calculations
11 Io=(Vc/Ro)*10**3 //output
    current (A)
12 I1=76 //load current
    (mA)
13 Is=I1+5 //supply
    current (mA)
14 Ic=Io-Is //collector
    current (A)
15 Ib=Ic/hfe //base current
    (mA)
16 Ie=Ic-Ib //emitter
    current (mA)
17 Pt=(Ve*Ie)-(Vc*Ic) //power

```

```

    dissipated in transistor (W)
18 P1=(Ve-Vbe)*Is-Vc*I1           //power
    dissipated in LR
19 Vimax=(P+Vc*(Ic*10**-3))/(Ie*10**-3) //input
    voltage maximum
20 Iomin=hfe*Ib1                 //output
    current minimum (mA)
21
22 //Results
23 printf ("power dissipated in the transistor is %.2f
    W and in LR is %.3f W",Pt/1E+3,P1/1E+3)
24 printf ("maximum permissible input voltage is %.2f V
    ",Vimax)
25 printf ("minimum load current for load voltage to
    remain stabalized is %.1f mA",Iomin)

```

Scilab code Exa 8.7 Example

```

1 //Variable declaration
2 VL=12           //load voltage (V)
3 I=2.           //current at 12 V
4 V=240          //dc source (V)
5 d=17/50.       //duty cycle
6 d1=0.6         //duty cycle
7 eta1=0.8       //efficiency
8 Vdc = 12
9 //Calculations
10 P=VL*I         //average load power (W
    )
11 Isav=(1*d)/2   //average supply
    current (A)
12 Pav=V*Isav     //average supply power
    (W)
13 eta=(P/Pav)*100 //regulator efficiency
14 Isav1=(1*d1)/2 //average supply

```

```

    current(A)
15 I1=(eta1*V*Isav1)/Vdc           //load current(A)
16 Po=I1*Vdc                       //power output(W)
17
18 //Results
19 printf ("regulator efficiency is %.1f %%",eta)
20 printf ("average supply current is %.1f A",I1)
21 printf ("power output is %.1f W",Po)

```

Scilab code Exa 8.8 Example

```

1 //Variable declaration
2 Vs=200                          //dc source voltage(V)
3 I1=5                             //current to load voltage(A)
4 V1=15                             //load voltage(V)
5 eta=.85                          //efficiency
6 f=20                             //oscillator frequency(Hz)
7 iSmax=2.6                        //peak value of supply current
    (A)
8 P=100                            //full load power supply(W)
9 pdf=0.4                          //pulse duty factor
10
11 //Calculations
12 Isav=(V1*I1)/(Vs*eta)           //average peak supply
    current(A)
13 iS=(2*Isav)/pdf                 //supply current(A)
14 T=1000/f                        //oscillation time period(uS
    )
15 tp=pdf*T                        //transistor time(us)
16 d=iS/tp                         //change in iS with respect
    to time(A/us)
17 tp1=iSmax/d                    //transistor time(us)
18 pdf1=tp1/T                     //pulse duty factor
19 Isav1=(iSmax*pdf1)/2           //average peak supply
    current(A)

```

```
20 eta1=(P*100)/(Vs*Isav1) //efficiency
21
22 //Results
23 printf ("peak value of supply current is %.3f A",
        Isav)
24 printf ("pdf is %.3f ",pdf)
25 printf ("overall efficienc is %.1f %%",eta1)
```

Chapter 9

Integrated Circuit Fabrication

Scilab code Exa 9.2 Example

```
1 //Variable declaration
2 t=1 //thickness(mil)
3 e=1.6*10**-19 //charge on electron(C)
4 Pp=10**17 //concentration of phosphorous
   (atoms/cm^3)
5 Bn=5*10**16 //boron concentration(atoms/cm
   ^3)
6 un=.135 //mobility(m^2/Vs)
7
8 //Calculations
9 n=(Pp-Bn)*10**6 //net concentration(atoms/cm
   ^3)
10 g=e*un*n //conductivity()
11 rho=10**6/(g*25) //resistivity(ohm mil)
12 Rs=rho/t //sheet resistance(ohm mil^2)
13
14 //Results
15 printf ("Sheet resistance is %.f ohm(mil**2)",Rs)
```

Scilab code Exa 9.3 Example

```
1 //Variable declaration
2 R=20*10**3 //resistance of resistor(
   ohms)
3 w=25 //width(um)
4 Rs=200 //sheet resistance(ohm/
   square)
5 R1=5*10**3 //resistance(ohms)
6
7 //Calculations
8 //Part a
9 l=(R*w)/Rs //length required to
   fabricate 20 kohms(um)
10
11 //Part b
12 L=25 //length of resistor of 5 k ohms(um
   )
13 w1=(Rs*L)/R1 //width required to fabricate 5
   kohms(um)
14
15 //Results
16 printf ("length required to fabricate 20 kohms
   resistor is %.1f um",l)
17 printf ("width required to fabricate 5 kohms
   resistor is %.1f um",w1)
```

Scilab code Exa 9.4 Example

```
1 //Variable declaration
2 C=0.4*10**-12 //capacitance(pF/um^2)
3 A=10**-12 //area of film(m^2)
4 d=400*10**-10 //thickness of SiO2(
   amstrong)
5 Eo=8.849*10**-12 //absolute electrical
```

```

        permittivity of free space
6
7 // Calculations
8 Er=(C*d)/(Eo*A)           //relative dielectric
        constant
9
10 // Results
11 printf ("relative dielectric constant of SiO2 is %.f
        ",Er)
12 printf(" Note : Solution given in the textbook is
        incorrect")

```

Scilab code Exa 9.5 Example

```

1 //Variable declaration
2 C=250*10**-12           //capacitance(pF)
3 d=500*10**-10         //thickness of SiO2
        layer(amstrong)
4 Eo=8.849*10**-12       //absolute electrical
        permittivity of free space
5 Er=3.5                 //relative dielectric
        constant
6
7 // Calculations
8 A=(C*d)/(Eo*Er)       //chip area(um^2)
9
10 // Results
11 printf ("chip area needed for a 250 pF MOS
        capacitor %.2f um^2",A/1e-7)
12 printf("Note: Solution given in the textbook is
        incorrect")

```

Chapter 10

Circuit Theory

Scilab code Exa 10.1 Example

```
1 //Variable declaration
2 i1=4.           //current through r1(A)
3 v3=3           //voltage(V)
4 v4=8           //voltage(V)
5 r3=3           //resistance(ohms)
6 r2=2           //resistance(ohms)
7 r4=4           //resistance(ohms)
8
9 //Calculations
10 i3=v3/r3       //current through r3(A)
11 i4=v4/r4       //current through r4(A)
12 i2=-(i3+i4-i1)/2 //current through r2(A)
13 v2=i2*r2       //voltage through r2(V)
14
15 //Result
16 printf ("v2 is %.1f V",v2)
```

Scilab code Exa 10.2 Example

```

1 //Variable declaration
2 v1=6 //current through r1(A)
3 i2=2 //voltage through r3(V)
4 i3=4 //voltage through r4(V)
5 r3=2 //resistance(ohms)
6 v3=3 //voltage through r3(ohms)
7 r2=2 //resistance(ohms)
8 r4=3 //resistance(ohms)
9
10 //Calculations
11 v2=i2*r2 //voltage through r2(ohms)
12 v3=i3*r3 //voltage through r3(ohms)
13 v4=4*i2+v3-v2-v1 //voltage through r4(ohms)
14 i4=v4/r4 //current through r4(A)
15
16 //Result
17 printf (" i4 is %.f A",i4)

```

Scilab code Exa 10.3 Example

```

1
2 //Calculations
3 a = [7 -3 -4 ; -3 6 -2 ; -4 -2 11] //solving three
    linear mesh equations
4 b = [-11;3;25]
5 x = a\b
6
7 v=x(3) - x(2) //
    voltage across 2mho conductance(V)
8
9 //Results
10 printf ("v is %.1f V",v)

```

Scilab code Exa 10.4 Example

```
1
2 //Variable declaration
3 R=20 //resistance across
      which voltage is to be calculated(ohms)
4
5 //Calculations
6 a = [35 -20 ; -20 50] //solving two linear mesh
      equations
7 b = [50;-100]
8 x = a\b
9 i=x(1)-x(2) //current through 20 ohms
      resistor(ohms)
10 V=20*i //voltage across 20 ohms(V)
11
12 //Results
13 printf ("i is %.2f",i)
14 printf ("voltage across 20 ohms is %.1f V",V)
```

Scilab code Exa 10.5 Example

```
1 //Variable declaration
2 Vs=16. //source voltage(V)
3
4 //Calculations
5 //Part b
6 I=0 //current through 10 V
7 Is=-4*(I-(Vs/32)) //current of current source(A)
8
9 //Part c
10 Is1=16 //current of current source(A)
11 I=0 //current through 10 V
12 Vs1=(I+(Is1/4))*32 //source voltage(V)
13
```

```

14 //Results
15 printf (" Is is %.f A",Is)
16 printf (" Vs1 is %.f V",Vs1)

```

Scilab code Exa 10.6 Example

```

1 //Variable declaration
2 V=9 //voltmeter of voltage(V)
3 i=9 //ammeter current of 9V
4 r1=1 //resistance(ohms)
5 r2=3 //resistance(ohms)
6 r=5 //resistance parallel to
   ammeter(ohms)
7
8 //Calculations
9 Isc=((i*r)-V)/(r1+r) //short circuiting a and
   b and converting current source to a voltage
   source(A)
10 Ro=((r+r1)*r2)/((r+r1)+r2) //output resistance(ohms)
11
12 //Results
13 printf (" Isc is %.f A",Isc)
14 printf (" Ro is %.f ohms",Ro)

```

Scilab code Exa 10.7 Example

```

1
2 //Variable declaration
3 syms t //symbol defined
4 et1 = complex(50,86.6) //defining complex number
5
6 //calculations

```

```

7 et = (real(et1)*sqrt(2)*cos(314*t))+imag(et1)*sqrt
      (2)*cos(314*t+90) //expression
8
9 //Result
10 disp ( et)

```

Scilab code Exa 10.9 Example

```

1
2 //Variable declarations
3 syms V1 V2
4
5
6 //Calculations
7 V = 0.3*V1
                                     //
      voltage(V)
8 I1 = 0.007*V1
                                     //
      current
9 y11 = I1/V1
                                     //y
      parameter
10
11 I2 = -V/40
                                     //
      current
12 y21 = I2/V1
                                     //y
      parameter
13
14 I2 = V2/(((40+100)*200.)/((40+100)+200.))
                                     //y parameter
15 y22 = I2/V2 //incorrect answer in textbook
      //y parameter

```

```

16
17 I1 = (-I2*200)/300
18 y12 = I1/V2 //current
           //incorrect answer in textbook
           //y parameter
19
20 //Results
21 disp ("mho" , y11+y12 ,"y11+y12 is")
22 disp ("mho" , y22+y12 ,"y22+y12 is")
23 disp ("mho" , y21-y12 ,"y21-y12 is")
24 disp ( "\n(The difference in answers is due to the
           y12 and y21 values calculated wrongly in the
           textbook)")

```

Scilab code Exa 10.10 Example

```

1 //Variable declaration
2
3 //port 2 open circuited ,port 1 excited
4 z11= complex(1075,1075) //as z11=
           V1/I1=(1.52<45)/(10**3<0)=1075+1075j
5 z21 = complex(2022,-1075) //as z21
           =V2/I1=(2.29<-28)/(10**3<0)=2022+1075j
6
7 //port 1 open circuited and port 2 excited
8 z12= complex(0,-1075) //as z12
           =V1/I2=(1.075<-90)/(10**3<0)=-1075j
9 z22= complex(751,-1073) //as z22=
           V2/I2=(1.31<-55)/(10**3<0)=751-j1073
10
11 //Calculations
12 z=z11-z12 //parameters with
           reference to circuit
13 z1=z22-z12
14 z2=z21-z12

```



```
15
16 //Results
17 printf ("z11-z12(z) is ")
18 disp(z)
19 printf ("z22-z12(z1) is")
20 disp(z1)
21 printf ("z21-z12(z2) is")
22 disp(z2)
```

Scilab code Exa 10.11 Example

```
1 //Variable declaration
2 V2=6/7. //voltage source(V)
3
4 //Calculations
5 Rth=V2 //thevinin resistance(
   ohms)
6 Z1=Rth //load resistance(ohms)
7
8 //Result
9 printf ("load resistance is %.3f ohms",Z1)
```

Chapter 11

Cathode Ray Oscilloscope

Scilab code Exa 11.2 Example

```
1 //Variable declaration
2 E=120 //electric field (V/m)
3 B=5*10**-5 //magnetic field (T)
4 q=1.6*10**-19 //charge on electron (C)
5 u=10**6 //velocity of electron (m/s)
6 m=9.1*10**-31 //mass of electron (Kg)
7 a=9.81 //acceleration of gravitation
   (m/s^2)
8
9 //Calculations
10 //Part a
11 fe=q*E //force on electron due to
   electric field (N)
12
13 //Part
14 fm=B*q*u //force on electron due to
   magnetic field (N)
15
16 //Part c
17 fg=m*a //force on electron due to
   gravitational field (N)
```

```

18
19 //Results
20 printf ("force on electron due to electric field is
    %.2e N",fe)
21 printf ("force on electron due to magnetic field is
    %.e N",fm)
22 printf ("force on electron due to gravitational
    field is %.4e N",fg)

```

Scilab code Exa 11.3 Example

```

1
2
3 //Variable declaration
4 T1=1200. //temperature(k)
5 T2=1000. //temperature(k)
6 Ww=1.2*10**5 //work function(eV)
7 k=8.62
8 Ie1=200 //emission current
    density
9 T3=1500. //temperature(k)
10
11 //Calculations
12 Ie2=Ie1*(T2/T1)**2*exp(-(Ww/k)*((1/T2)-(1/T1)))
    //current density(mA/cm^2) at 1000k
13 Ie3=Ie1*(T3/T1)**2*exp(-(Ww/k)*((1/T3)-(1/T1)))
    //current density(mA/cm^2) at 1000k
14
15 //Results
16 printf ("current density at 1000 k is %.2f mA/cm^2",
    Ie2)
17 printf ("current density at 1500 k is %.2f mA/cm^2",
    Ie3)

```

Scilab code Exa 11.4 Example

```
1
2
3 //Variable declaration
4 Ls=40 //distance from screen(m)
5 d=1.5 //distance between plates(
   cm)
6 Va=1200 //accelerating potential(V
   )
7 L=3 //length of CRT(m)
8 e=1.6*10**-19 //charge on electron(C)
9 m=9.1*10**-31 //mass of electron(Kg)
10 Y=4*10**-2 //vertical deflection(V)
11
12 //Calculations
13 //Part a
14 U=sqrt((2*e*Va)/m) //velocity of electron upon
   striking screen(m/s)
15
16 //Part
17 Vd=(2*d*Va*Y)/(L*Ls) //deflecting voltage(V)
18
19 //Part c
20 Vdmax=(m*d**2*U**2)/(e*L**2) //maximum allowable
   deflection(V)
21
22 //Results
23 printf ("velocity of electron upon stricking the
   screen is %.3e m/s",U)
24 printf ("deflecting voltage is %.f V",Vd/1E-2)
25 printf ("maximum allowable deflection is %.f V",
   Vdmax)
```
