

Scilab Textbook Companion for  
Radio Frequency Circuit Design  
by R. Ludwig And G. Bogdanov<sup>1</sup>

Created by  
Monisha Dhirmalani  
Engineering  
Others  
Mumbai University  
College Teacher  
Monali Chaudhari  
Cross-Checked by

May 20, 2016

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Radio Frequency Circuit Design

**Author:** R. Ludwig And G. Bogdanov

**Publisher:** Pearson Education India, New Delhi

**Edition:** 2

**Year:** 2011

**ISBN:** 978-81-317-6218-9

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Introduction	6
2 Transmission line analysis	13
3 The Smith Chart	22
4 Single and Multiport Networks	25
5 An Overview of RF Filter Design	27
6 Active RF Components	32
7 Active RF Component Modelling	47
8 Matching and biasing networks	54
9 RF Transistor Amplifier Design	57
10 Oscillators and Mixers	74

# List of Scilab Codes

Exa 1.1	Intrinsic wave impedance . . . . .	6
Exa 1.2	Comparing Inductances at different frequencies . . . . .	6
Exa 1.3	Frequency response of high frequency resistor . . . . .	7
Exa 1.4	Frequency response of high frequency capacitor . . . . .	8
Exa 1.5	frequency response of high frequency inductor . . . . .	10
Exa 2.1	Magnetic field inside and outside infinitely long current carrying wire . . . . .	13
Exa 2.3	Transmission line parameters of a parallel copper plate transmission line . . . . .	15
Exa 2.5	Phase velocity and Wavelength of PCB material . . . . .	15
Exa 2.6	Input Impedance for a short circuited transmission line . . . . .	17
Exa 2.7	Input impedance of open circuited transmission line . . . . .	17
Exa 2.8	Quarter wave parallel plate line transformer . . . . .	19
Exa 2.9	Power considerations of a transmission line . . . . .	20
Exa 2.10	Return Loss of Transmission line section . . . . .	21
Exa 3.2	Input Impedance . . . . .	22
Exa 3.4	SWR circles . . . . .	22
Exa 4.3	Internal resistances and current gain of BJT . . . . .	25
Exa 4.7	S parameters and resistive elements of T network . . . . .	25
Exa 5.1	Resonance frequency of a Bandpass filter . . . . .	27
Exa 5.2	Quality factors of a filter . . . . .	29
Exa 6.1	Conductivity of Si and Ge and GaAs . . . . .	32
Exa 6.2	Barrier Voltage of a pn Junction . . . . .	34
Exa 6.3	Depletion Layer Capacitance of a pn Junction . . . . .	34
Exa 6.4	Parameters of a Schottky diode . . . . .	37
Exa 6.7	Maximum forward current gain of bipolar junction transistor . . . . .	37

Exa 6.8	Thermal analysis involving a BJT mounted on a heat sink . . . . .	38
Exa 6.9	Drain saturation current in a MESFET . . . . .	38
Exa 6.10	Current Voltage characteristics of a MESFET . . . . .	40
Exa 6.11	Computation of HEMT related electric characteristics	44
Exa 7.1	Small signal pn diode model . . . . .	47
Exa 7.4	Parameters of BJT . . . . .	50
Exa 7.5	Cutoff frequency of GaAs MESFET . . . . .	52
Exa 7.6	Small signal Hybrid pi parameters without Miller Effect	53
Exa 8.11	Efficiency of different types of amplifiers . . . . .	54
Exa 8.12	Design of passive biasing networks for a BJT in CE config	56
Exa 9.1	Power relations for an RF amplifier . . . . .	57
Exa 9.7	Computation of source gain circles for a unilateral design	58
Exa 9.8	Design of 18 dB single stage MESFET amplifier . . . . .	59
Exa 9.13	Amplifier design using the constant operating gain circles	61
Exa 9.14	Design of small signal amplifier for minimum noise figure and specified gain . . . . .	64
Exa 9.15	Constant VSWR design for given gain and noise figure	67
Exa 10.1	Design of a Colpitt oscillator . . . . .	74
Exa 10.2	Prediction of resonance frequencies of quartz crystal .	75
Exa 10.3	Adding a positive feedback element to initiate oscillations	76
Exa 10.6	Dielectric resonator oscillator design . . . . .	79
Exa 10.8	Local oscillator frequency selection . . . . .	81

# List of Figures

1.1	Frequency response of high frequency resistor . . . . .	8
1.2	Frequency response of high frequency capacitor . . . . .	9
1.3	frequency response of high frequency inductor . . . . .	11
2.1	Magnetic field inside and outside infinitely long current carrying wire . . . . .	14
2.2	Input Impedance for a short circuited transmission line . . . . .	16
2.3	Input impedance of open circuited transmission line . . . . .	18
2.4	Quarter wave parallel plate line transformer . . . . .	19
3.1	SWR circles . . . . .	23
5.1	Resonance frequency of a Bandpass filter . . . . .	28
5.2	Quality factors of a filter . . . . .	29
6.1	Conductivity of Si and Ge and GaAs . . . . .	33
6.2	Depletion Layer Capacitance of a pn Junction . . . . .	35
6.3	Drain saturation current in a MESFET . . . . .	39
6.4	Current Voltage characterisites of a MESFET . . . . .	41
6.5	Computation of HEMT related electric characteristics . . . . .	45
7.1	Small signal pn diode model . . . . .	48
8.1	Efficiency of different types of amplifiers . . . . .	55
9.1	Computation of source gain circles for a unilateral design . . . . .	58
9.2	Design of 18 dB single stage MESFET amplifier . . . . .	60
9.3	Amplifier design using the constant operating gain circles . . . . .	62
9.4	Design of small signal amplifier for minimum noise figure and specified gain . . . . .	65

9.5	Constant VSWR design for given gain and noise figure . . .	72
9.6	Constant VSWR design for given gain and noise figure . . .	73
10.1	Adding a positive feedback element to initiate oscillations . .	77
10.2	Dielectric resonator oscillator design . . . . .	82
10.3	Dielectric resonator oscillator design . . . . .	83



# Chapter 1

## Introduction

Scilab code Exa 1.1 Intrinsic wave impedance

```
1 mu0=4*%pi*10^-7; // defining permeability of free
   space
2 epsilon0=8.85*10^-12; // defining permittivity of
   free space
3 z0=sqrt(mu0/epsilon0); // calculating intrinsic
   impedance
4 epsilon_r=4.6; // defining relative permittivity
5 vp=1/sqrt(mu0*epsilon0*epsilon_r); // calculating
   phase velocity
6 f1=30*10^6;
7 f2=3*10^9;
8 lambda1=vp/(f1);
9 lambda2=vp/(f2);
10 disp('metre',lambda1,'Wavelength corresponding to f1
   '); // displaying wavelengths
11 disp('metre',lambda2,'Wavelength corresponding to f2
   '); // displaying wavelengths
```

---

Scilab code Exa 1.2 Comparing Inductances at different frequencies

```

1 mu0=4*%pi*10^-7;
2 a=8*2.54*10^-5; //radius of copper wire
3 sigmac=64.5*10^6; //conductivity of copper
4 l=2*10^-2; //length of wire
5 rdc=1/(%pi*a*a*sigmac);
6 f1=100*10^6;
7 f2=2*10^9;
8 f3=5*10^9;
9 skindepth1=1/sqrt(%pi*mu0*f1*sigmac);
10 skindepth2=1/sqrt(%pi*mu0*f2*sigmac);
11 skindepth3=1/sqrt(%pi*mu0*f3*sigmac);
12 Lin1=(a*rdc)/(2*skindepth1*2*%pi*f1); //internal
    inductance
13 Lin2=(a*rdc)/(2*skindepth2*2*%pi*f2); //internal
    inductance
14 Lin3=(a*rdc)/(2*skindepth3*2*%pi*f3); //internal
    inductance
15 temp=log(2*l/a)/log(%e);
16 Lex=mu0*l*(temp-1)/(2*%pi); //external inductance
17 disp("metre",skindepth1,"Skin depth at f1");
18 disp("metre",skindepth2,"Skin depth at f2");
19 disp("metre",skindepth3,"Skin depth at f3");
20 disp("Henry",Lin1,"Internal inductance at f1");
21 disp("Henry",Lin2,"Internal inductance at f2");
22 disp("Henry",Lin3,"Internal inductance at f3");
23 disp("Henry",Lex,"External inductance");

```

---

### Scilab code Exa 1.3 Frequency response of high frequency resistor

```

1 f=10^4:10^5:10^10;
2 w=2*%pi.*f;
3 mu0=4*%pi*10^-7;
4 l=2*2.5*10^-2;

```

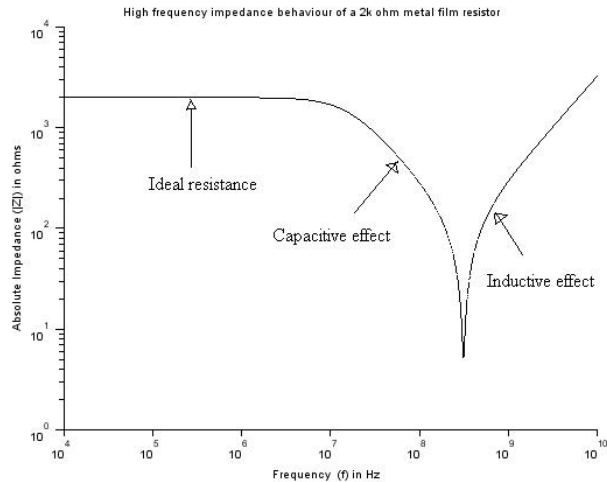


Figure 1.1: Frequency response of high frequency resistor

```

5 a=2.032*10^-4;
6 temp=log(2*l/a)/log(%e);
7 lex=mu0*l*(temp-1)/(2*pi); //external inductance
8 r=2*10^3; // resistance
9 c=5*10^-12; //capacitance
10 z=w*lex*i+1 ./ (w*c*i+1/r); //impedance
11 plot2d("gll",f,abs(z));
12 title("High frequency impedance behaviour of a 2k
        ohm metal film resistor");
13 xlabel('Frequency (f) in Hz');
14 ylabel('Absolute Impedance (|Z|) in ohms');

```

---

#### Scilab code Exa 1.4 Frequency response of high frequency capacitor

```

1 f=10^6:10^7:10^10;
2 rs=(4.8*10^-6).*sqrt(f);

```

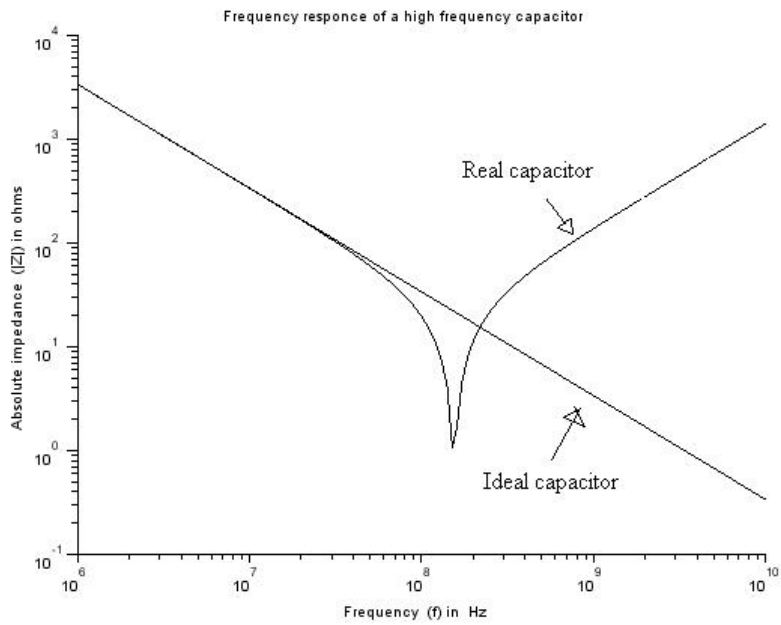


Figure 1.2: Frequency response of high frequency capacitor

```

3 re=(33.9*10^12) ./f;
4 c=47*10^-12;
5 w=2*%pi.*f;
6 l=2*1.25*10^-2;
7 a=2.032*10^-4;
8 temp=log(2*l/a)/log(%e);
9 lex=mu0*l*(temp-1)/(2*%pi);           //external
    inductance
10 z=1 ./((1 ./re +w*c*%i)+rs+w.*lex*%i); // impedance of
    frequency dependent capacitor
11 zideal=1 ./(w*c*%i);           //impedance of an ideal
    capacitor
12 plot2d("gll",f,abs(z));
13 plot2d(f,abs(zideal));
14 title("Frequency response of a high frequency
    capacitor");
15 xlabel('Frequency (f) in Hz');
16 ylabel('Absolute impedance (|Z|) in ohms');

```

---

### Scilab code Exa 1.5 frequency response of high frequency inductor

```

1 f=10^7:10^8:10^10;
2 w=2*%pi.*f;
3 N=3.5;           //number of turns
4 rad=0.05*0.0254;
5 len=0.05*0.0254;           //length of wire
6 a=(5*0.0254*10^-3)/2;
7 u0=4*%pi*10^-7;
8 sig_cu=64.516*10^6;
9 e0=8.854*10^-12;
10 l=(%pi*rad^2*u0*(N^2))/len;
11 c=(e0*4*%pi*rad*(N^2)*a)/len;
12 r=(2*rad*N)/(sig_cu*(a^2));

```

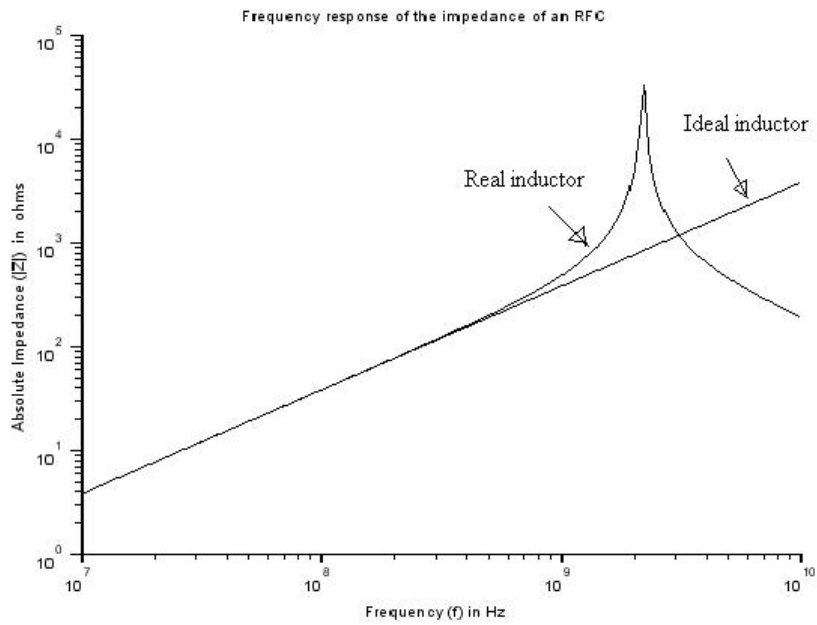


Figure 1.3: frequency response of high frequency inductor

```
13 z=1 ./((1 ./ (r+w*i*l))+w*i*c); //impedance
14 zideal=w*i.*l; //impedance of an
    ideal inductor
15 plot2d("gll",f,abs(z));
16 plot2d(f,abs(zideal));
17 title("Frequency response of the impedance of an RFC
    ");
18 xlabel('Frequency (f) in Hz');
19 ylabel('Absolute Impedance (|Z|) in ohms');
```

---

## Chapter 2

# Transmission line analysis

**Scilab code Exa 2.1** Magnetic field inside and outside infinitely long current carrying wire

```
1 I=5; //current in infinitely long wire
2 a=0.005; //radius of infinitely long wire
3 r_max=10*a;
4 N=100;
5 r=(0:N)/N*r_max;
6 for k=1:N+1
7   if(r(k)<=a)
8     H(k)=I*r(k)/(2*%pi*a*a);
9   else
10    H(k)=I/(2*%pi*r(k));
11  end;
12 end;
13 plot(r*1000,H);
14 plot([a a]*1000,[0 160], 'r:');
15 title("Magnetic field distribution vs. distance from
        the center");
16 xlabel("Distance from the center of the wire ,mm");
17 ylabel("Magnetic field ,A/m");
```



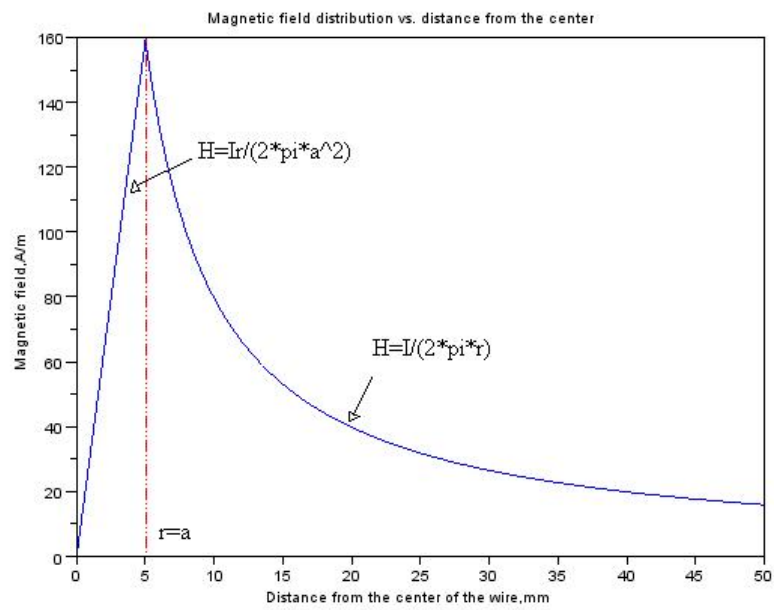


Figure 2.1: Magnetic field inside and outside infinitely long current carrying wire

---

**Scilab code Exa 2.3** Transmission line parameters of a parallel copper plate transmission line

```
1 f=1*10^9;
2 w=6*10^-3; //width
3 d=1*10^-3; //seperation
4 epsilon_r=2.25;
5 epsilon_0=8.85*10^-12;
6 sigma_diel=0.125;
7 sigma_cond=64.5*10^6;
8 mu0=4*pi*10^-7;
9 skindepth=1/sqrt(pi*sigma_cond*mu0*f);
10 r=2/(w*sigma_cond*skindepth);
11 L=2/(w*sigma_cond*2*pi*f*skindepth);
12 c=epsilon_0*epsilon_r*w/d;
13 G=sigma_diel*w/d;
14 disp("R,L,G,C parameters of a parallel copper plate
      transmission line ")
15 disp(r,"Resistance in ohm/m");
16 disp(L,"Inductance in Henry/m");
17 disp(c,"Capacitance in Farad/m");
18 disp(G,"Conductance in mS/m");
```

---

**Scilab code Exa 2.5** Phase velocity and Wavelength of PCB material

```
1 epsilon_r=4.6;
2 f=2*10^9;
3 z0=50; //line impedance
4 mu0=4*pi*10^-7;
5 epsilon_0=8.85*10^-12;
6 zf=sqrt(mu0/epsilon_0); //free space impedance
```

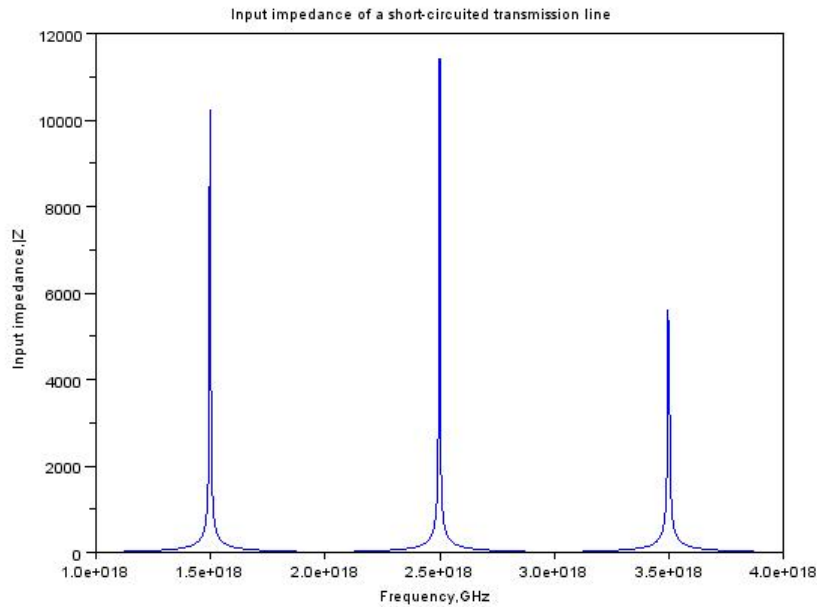


Figure 2.2: Input Impedance for a short circuited transmission line

```

7 temp=((epsilon-1)/(epsilon+1))*(0.23+(0.11/
    epsilon));
8 temp1=2*pi*(z0/zf)*sqrt((epsilon+1)/2);
9 A=temp+temp1;
10 wtoh=(8*e^A)/((e^2*A)-2);
11 Eff=(epsilon+1)/2+(epsilon-1)/2*1/(sqrt(1+12*(1/(
    wtoh)))));
12 vp=3*10^8/sqrt(Eff);
13 lambda=vp/f;
14 disp("metre/second",vp,"Phase velocity");
15 disp("metre",lambda,"Wavelength");

```

---

**Scilab code Exa 2.6** Input Impedance for a short circuited transmission line

```
1 L=209.4*10^-9; //line inductance in H/m
2 C=119.5*10^-12; //line capacitance in F/m
3 vp=1/sqrt(L*C); // phase velocity
4 Z0=sqrt(L/C); // characteristic line impedance
5 d=0.1; // line length
6 N=500; // number of sampling points
7 f=1*10^9+3*10^9*(0:N)/N; // set frequency range
8 Z=tan(2*%pi*f*d/vp); // short circuit impedance
9 plot(f/1*10^9,abs(Z0*Z));
10 title('Input impedance of a short-circuited
        transmission line');
11 xlabel('Frequency ,GHz');
12 ylabel('Input impedance ,|Z|');
```

---

**Scilab code Exa 2.7** Input impedance of open circuited transmission line

```
1 L=209.4*10^-9; //line inductance in H/m
2 C=119.5*10^-12; //line capacitance in F/m
3 vp=1/sqrt(L*C); // phase velocity
4 Z0=sqrt(L/C); // characteristic line impedance
5 d=0.1; // line length
6 N=500; // number of sampling points
7 f=1e9+4e9*(0:N)/N; // set frequency range
8 Z=cotg(2*%pi*f*d/vp); // short circuit impedance
9 plot(f/1e9,abs(Z0*Z));
10 title('Input impedance of an open-circuited line');
11 xlabel('Frequency , GHz');
12 ylabel('Input impedance |Z| , {\Omega}');
```

---

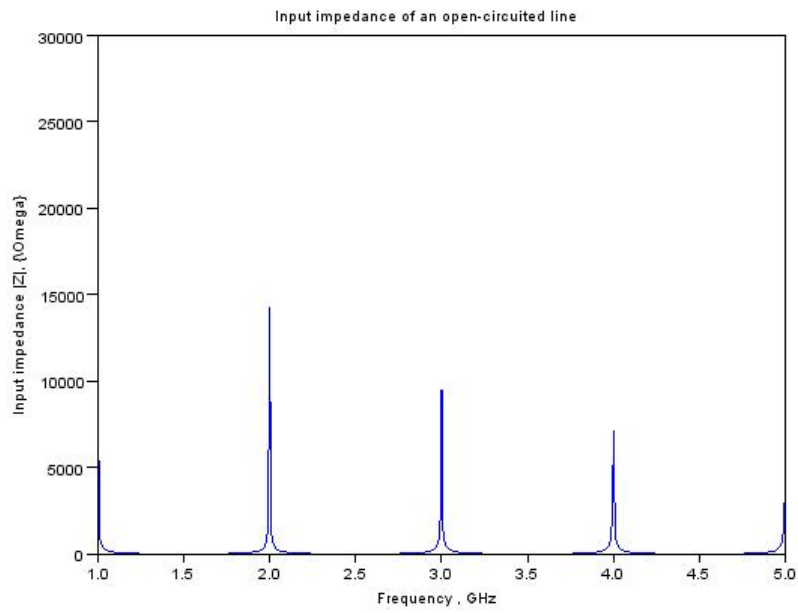


Figure 2.3: Input impedance of open circuited transmission line

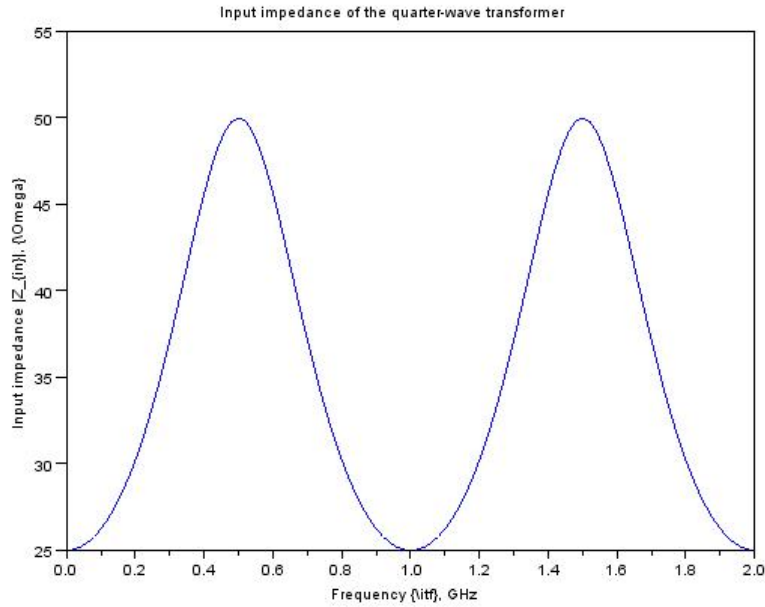


Figure 2.4: Quarter wave parallel plate line transformer

**Scilab code Exa 2.8** Quarter wave parallel plate line transformer

```

1 ZL=25; //input impedance
2 Z0=50; //characteristic impedance
3 epsilon_r=4;
4 dp=0.001;
5 f0=500e6;
6 mu0=4*%pi*1e-7;
7 epsilon0=8.85e-12;
8 Zline=sqrt(Z0*ZL); //line impedance
9 w=dp/Zline*sqrt(mu0/epsilon0/epsilon_r);

```

```

10 L=mu0*dp/w; //inductance
11 C=epsilon0*epsilon_r*w/dp; //capacitance
12 vp=1/sqrt(L*C); //phase velocity
13 Z0=sqrt(L/C);
14 d=1/(4*f0*sqrt(L*C));
15 N=100;
16 f=2e9*(0:N)/N;
17 betta=2*pi*f/vp;
18 Z=Zline*((ZL+%i*Zline*tan(betta*d))./(Zline+%i*ZL*
    tan(betta*d)));
19 plot(f/1e9,real(Z));
20 title('Input impedance of the quarter-wave
    transformer');
21 xlabel('Frequency {\itf}, GHz');
22 ylabel('Input impedance |Z_{in}|, {\Omega}');

```

---

**Scilab code Exa 2.9** Power considerations of a transmission line

```

1 Zg=50; //generator impedance
2 Zo=75; //intrinsic impedance
3 Zl=40; //line impedance
4 Vg=5; //generator voltage
5 Ts=(Zg-Zo)/(Zg+Zo); //reflection coefficient at
    source
6 To=(Zl-Zo)/(Zl+Zo); //reflection coefficient at load
7 temp=1-(To^2);
8 temp1=(1-Ts)^2;
9 temp2=(1-Ts*To)^2;
10 Pin=((Vg)^2*temp1*temp2)/(8*Zo*temp); //input power
11 P1=Pin; //power delivered to the load
12 disp("Watts",P1,"The Power delivered to the load is
    same as that at the input—>");

```

---

**Scilab code Exa 2.10** Return Loss of Transmission line section

```
1 RL=20; //load resistance
2 Zo=50; //intrinsic impedance
3 Rin=50; //input resistance
4 Tin=10^(-RL/20); //reflection coefficient at input
5 Rg1=Rin*(1+Tin)/(1-Tin);
6 Rg2=Rin*(1-Tin)/(1+Tin);
7 disp("Ohms",Rg1," Source resistance for positive Tin="
      ");
8 disp("Ohms",Rg2," Source resistance for negative Tin="
      ");
```

---



# Chapter 3

## The Smith Chart

Scilab code Exa 3.2 Input Impedance

```
1 Z1=30+%i*60; //load impedance
2 Z0=50; // intrinsic impedance
3 d=2*10^-2; //length of wire
4 f=2*10^9;
5 c=3*10^8;
6 T0=((Z1-Z0)/(Z1+Z0)); //load reflection coefficient
7 beta=((2*pi*f)/(0.5*c));
8 T=-0.32-%i*0.55;
9 Zin=Z0*((1+T)/(1-T)); //input impedance
10 disp("Ohms",Zin,"Input impedance—>");
```

---

Scilab code Exa 3.4 SWR circles

```
1 Z0=50; //define 50 Ohm characteristic impedance
2 Z=[50 48.5 75+%i*25 10-%i*5]; //define impedances
   for this example
```

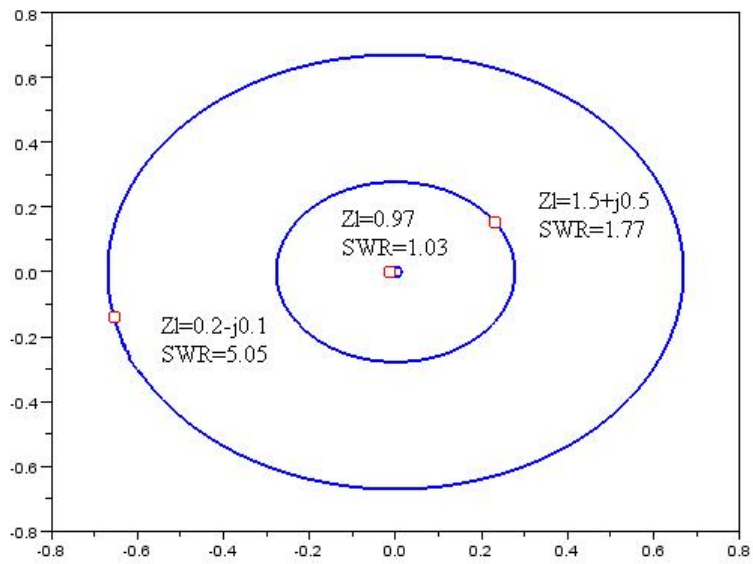


Figure 3.1: SWR circles

```
3 Gamma=(Z-Z0)./(Z+Z0) //compute corresponding
  reflection coefficients
4 SWR=(1+abs(Gamma))./(1-abs(Gamma)); //find the SWRs
5 a=0:0.01:2*%pi;
6 for n=1:length(Z)
7
8 plot(abs(Gamma(n))*cos(a),abs(Gamma(n))*sin(a),'b',
  linewidth',2);
9 plot(real(Gamma(n)), imag(Gamma(n)),'ro');
10 end;
11
12 for n=1:length(Z)
13     if n~=1
14         end;
15 end;
```

---

## Chapter 4

# Single and Multiport Networks

Scilab code Exa 4.3 Internal resistances and current gain of BJT

```
1 hie=5*10^3; //input impedance
2 hre=2*10^-4; //voltage feedback ratio
3 hfe=250; // small signal current gain
4 hoe=20*10^-6; //output admittance
5 rbc=hie/hre; // calculating base-collector
   resistance
6 rbe=hie/(1-hre); //calculating base-emitter
   resistance
7 beta=(hre+hfe)/(1-hre); //c calculating current gain
8 rce=hie/(hoe*hie-hre*hfe-hre); //collector-emitter
   resistance
9 disp("Ohms",rbc,"base collector resistance");
10 disp("Ohms",rbe,"base emitter resistance");
11 disp("Ohms",rce,"collector emitter resistance");
12 disp(beta,"current gain");
```

---

Scilab code Exa 4.7 S parameters and resistive elements of T network

```
1 Zin=50; //input impedance
2 Z0=50;
3 // defining scattering parameters
4 S11=0;
5 S22=0;
6 S21=1/sqrt(2);
7 S12=1/sqrt(2);
8 R1=((sqrt(2)-1)/(sqrt(2)+1))*Z0;
9 R2=R1;
10 R3=2*sqrt(2)*Z0;
11 disp(S21,S12,S22,S11," Scattering parameters");
12 disp(" Ohms",R3," Ohms",R2," Ohms",R1," Resistance
    values R1,R2,R3:");
```

---

# Chapter 5

## An Overview of RF Filter Design

Scilab code Exa 5.1 Resonance frequency of a Bandpass filter

```
1  stacksize('max');
2  C=2*10^-12;
3  L=5*10^-9;
4  R=20;
5  Z0=50;
6  //f=[10^7:10^8:10^11];
7  //define frequency range
8  f_min=10e6; //lower frequency limit
9  f_max=100e9; // upper frequency limit
10 N=100; // number of points in the graph
11 f=f_min*((f_max/f_min).^((0:N)/N)); // compute
    frequency points on log scale
12 w=2*%pi.*f;
13 A=(w.*w*L*C-1)/(w*C);
14 S21=2*Z0./(2*Z0+R+%i*A);
15 f0=1./(2*%pi*sqrt(L*C));
16 disp("Hertz",f0,"Resonance frequency");
```

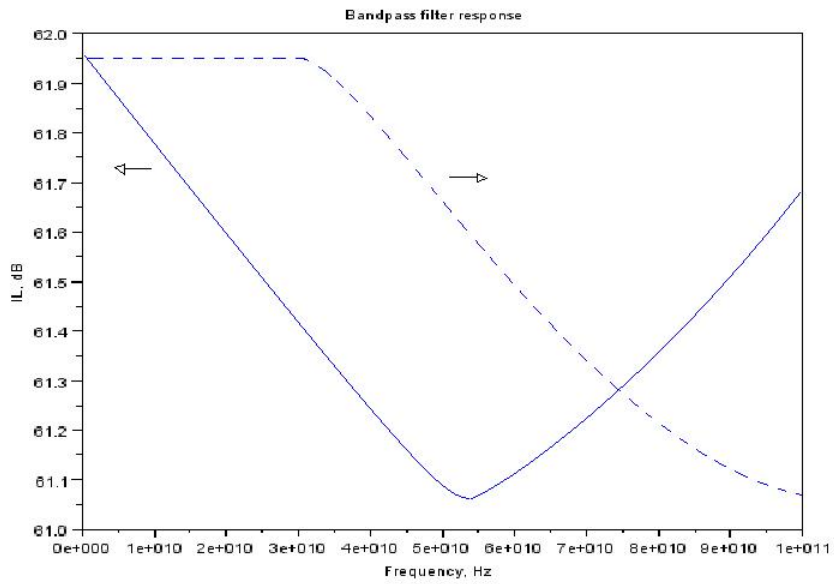


Figure 5.1: Resonance frequency of a Bandpass filter

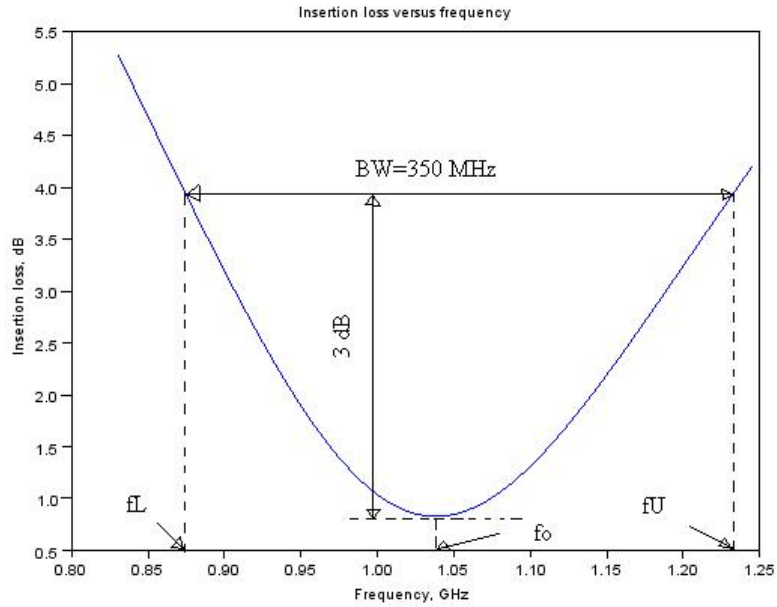


Figure 5.2: Quality factors of a filter

**Scilab code Exa 5.2** Quality factors of a filter

```

1 //define problem parameters
2
3 Z0=50; //characteristic line impedance
4 ZG=50; //source impedance
5 ZL=50; //load impedance
6
7 //series RLC filter parameters
8 R=10;

```



```

 9 L=50e-9;
10 C=0.47e-12;
11
12 VG=5; //generator voltage
13
14 //compute series resonance frequency
15 w0=1/sqrt(L*C);
16 f0=w0/(2*pi);
17
18 //define a frequency range
19 delta=0.2;
20 w=((1-delta):2*delta/1000:(1+delta))*w0;
21
22 //compute quality factors
23 Q_LD=w0*L/(R+2*ZL) //loaded quality factor
24 Q_F=w0*L/R //filter quality factor
25 Q_E=w0*L/(2*ZL) //external quality factor
26
27 // compute Bandwidth
28 BW=f0/Q_LD
29
30 //compute input and load power
31 P_in=VG^2/(8*Z0)
32 P_L=P_in*Q_LD^2/Q_E^2
33
34 //compute insertion loss and load factor
35 epsilon=w/w0-w0./w;
36 LF=(1+epsilon.^2*Q_LD^2)/(1-Q_LD/Q_F)^2;
37 IL=10*log10(LF);
38
39 disp(Q_LD,"Loaded Quality Factor");
40 disp(Q_F,"Filter Quality Factor");
41 disp(Q_E,"External Quality Factor");
42 disp("Watts",P_in,"Input Power");
43 disp("Watts",P_L,"Power delivered to the load");
44 disp("Hertz",f0,"resonance frequency of the filter")
    ;
45 disp("Hertz",BW,"Bandwidth of the filter");

```

```
46 plot(w/2/%pi/1e9,IL);
47 title('Insertion loss versus frequency');
48 xlabel('Frequency , GHz');
49 ylabel('Insertion loss , dB');
```

---

# Chapter 6

## Active RF Components

Scilab code Exa 6.1 Conductivity of Si and Ge and GaAs

```
1 //define physical constants
2 q=1.60218e-19;
3 k=1.38066e-23;
4
5 // define material properties
6 Nc_300=[1.04e19 2.8e19 4.7e17];
7 Nv_300=[6e18 1.04e19 7e18];
8 mu_n= [3900 1500 8500];
9 mu_p= [1900 450 400];
10 Wg= [0.66 1.12 1.424];
11
12 T0=273;
13 T=-50:250; // temperature range in centigrade
14
15 sigma=zeros([3 length(T)]);
16
17 for s=1:3 //loop through all semi conductor
    materials
18     Nc=Nc_300(s)*((T+T0)/300).^ (3/2);
```

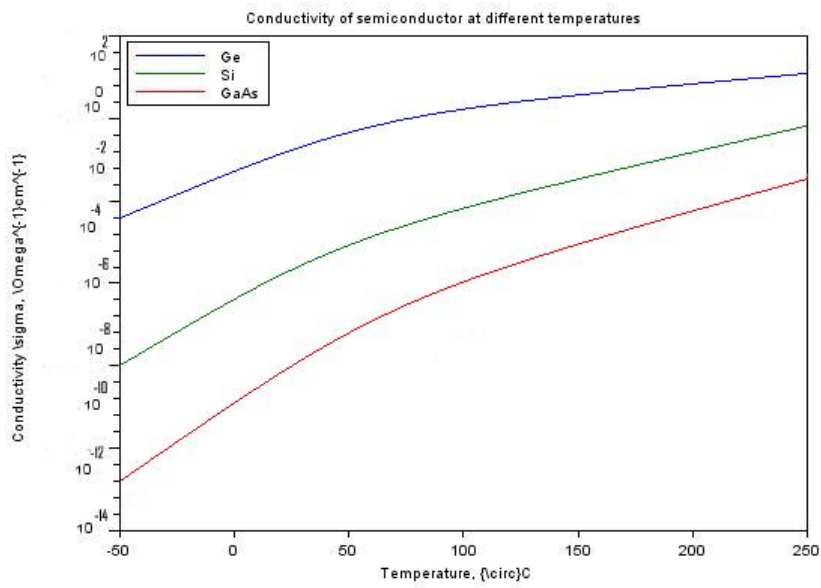


Figure 6.1: Conductivity of Si and Ge and GaAs

```

19     Nv=Nv_300(s)*((T+T0)/300).^ (3/2);
20     sigma=[q*sqrt(Nc.*Nv).*(exp(-Wg(s)./(2*k*(T+T0)/q)))
            *(mu_n(s)+mu_p(s))];
21     end;
22
23     plot(T,sigma(1),T,sigma(2),T,sigma(3));
24     legend('Ge','Si','GaAs',2);
25     title('Conductivity of semiconductor at different
            temperatures');
26     xlabel('Temperature, {\circ}C');
27     ylabel('Conductivity \sigma, \Omega^{-1}cm^{-1}');

```

---

### Scilab code Exa 6.2 Barrier Voltage of a pn Junction

```

1 // doping concentrations
2 Na=1*10^18;
3 Nd=5*10^15;
4 //intrinsic concentrations
5 ni=1.5*10^10;
6 T=300;
7 term=(Na*Nd)/(ni*ni);
8 k=1.38*10^-23;
9 q=1.6*10^-19;
10 Vdiff=(k*T)*log(term)/q;
11 disp("Volts",Vdiff,"Barrier voltage");

```

---

### Scilab code Exa 6.3 Depletion Layer Capacitance of a pn Junction

```

1 //define problem parameters
2

```

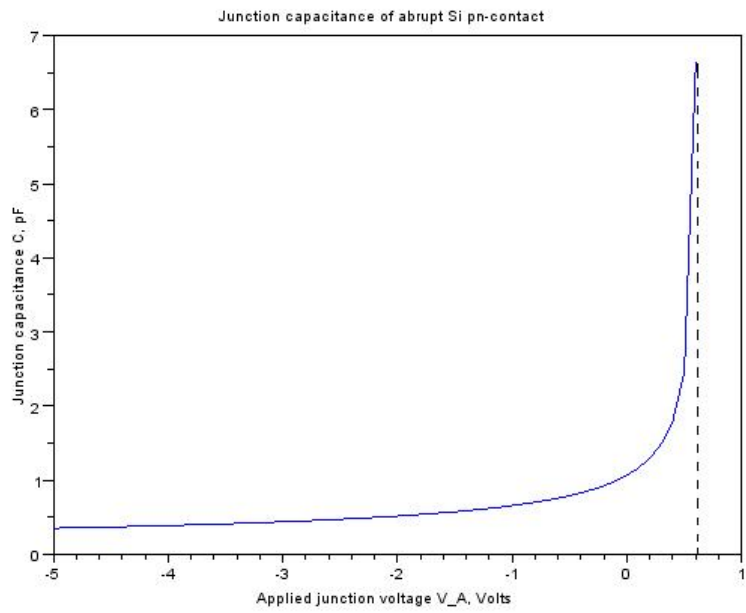


Figure 6.2: Depletion Layer Capacitance of a pn Junction

```

3 ni=1.5e10*1e6; //intrinsic carrier concentration in
  Si [m(-3)]
4 Na=1e15*1e6; //acceptor doping concentration [m(-3)
  ]
5 Nd=5e15*1e6; //donor concentration [m(-3)]
6 A=1e-4*1e-4; //cross sectional area [m2]
7 eps_r=11.9; //cross sectional area [m2]
8
9 //define physical constants (SI units)
10 q=1.60218e-19; //electron charge
11 k=1.38066e-23; //Boltzmann's constant
12 eps0=8.85e-12; //permittivity of free space
13
14 eps=eps_r*eps0;
15
16 T=300; //temperatuure
17
18 //compute diffusion barrier voltage
19 Vdiff=k*T/q*log(Na*Nd/ni^2)
20
21 //junction capacitance at zero applied voltage
22 C0=A*sqrt(q*eps/(1/Na+1/Nd)/2/Vdiff)
23
24 //extents of the space charge region
25 dn=sqrt(2*eps*Vdiff/q*Na/Nd/(Na+Nd));
26 dp=sqrt(2*eps*Vdiff/q*Nd/Na/(Na+Nd));
27
28 //define range for applied voltage
29 VA=-5:0.1:Vdiff;
30
31 //compute junction capacitance
32 C=C0*(1-VA/Vdiff).^(-1/2);
33
34 plot(VA,C/1e-12);
35 title('Junction capacitance of abrupt Si pn-contact'
  );
36 xlabel('Applied junction voltage V_A, Volts');
37 ylabel('Junction capacitance C, pF');

```

---

**Scilab code Exa 6.4** Parameters of a Schottky diode

```
1 //doping concentrations
2 Nc=2.8*10^19;
3 Nd=1*10^16;
4 term=Nc/Nd;
5 k=1.38*10^-23; //Boltzman's constant
6 q=1.6*10^-19; //charge
7 Vc=(k*T)*log(term)/q;
8 Vm=5.1; //workfunction
9 X=4.05; //affinity
10 Vd=(Vm-X)-Vc; //Barrier Voltage
11 Epsilon=11.9*8.854*10^-12;
12 ds=sqrt((2*Epsilon*Vd)/(q*Nd));
13 A=1*10^-4; //cross-sectional area
14 Cj=(A*Epsilon)/(ds); //junction capacitance
15 disp("Volts",Vc,"Conduction Band potential");
16 disp("Volts",Vd,"Built in Barrier Voltage");
17 disp("metre",ds,"Space Charge Width");
18 disp("Farads",Cj,"Junction Capacitance");
```

---

**Scilab code Exa 6.7** Maximum forward current gain of bipolar junction transistor

```
1 Ndemitter=1*10^19; // donor concentration in emitter
2 Nabase=1*10^17; //acceptor concentration in base
3 de=0.8*10^-6; //spatial extent of the emitter
4 db=1.2*10^-6; //spatial extent of the base
5 alpha=2.8125;
6 beta=(alpha*Ndemitter*de)/(Nabase*db);
7 disp(beta,"Maximum forward current gain");
```

---



**Scilab code Exa 6.8** Thermal analysis involving a BJT mounted on a heat sink

```
1 Tj=150;
2 Ts=25;
3 Pw=15;
4 Rthjs=(Tj-Ts)/Pw; // Junction-to-solder point
   resistance
5 Rthca=2;
6 Rthhs=10;
7 Ta=60;
8 Rthtot=Rthjs+Rthca+Rthhs; //total thermal resistance
9 Pth=(Tj-Ta)/(Rthtot); //dissipated power
10 disp(" Watts",Pth,"Maximum dissipated power");
```

---

**Scilab code Exa 6.9** Drain saturation current in a MESFET

```
1 //define problem parameters
2 Nd=1e16*1e6;
3 d=0.75e-6;
4 W=10e-6;
5 L=2e-6;
6 eps_r=12;
7 Vd=0.8;
8 mu_n=8500e-4;
9 Vgs=0:-0.01:-4;
10
11 //define physical constants
12 q=1.60218e-19; // electron charge
13 eps0=8.85e-12; // permittivity of free space
```

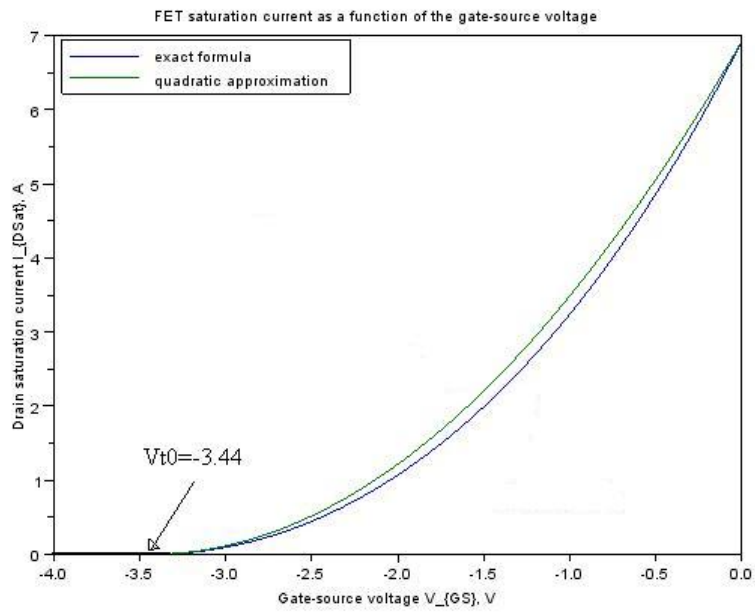


Figure 6.3: Drain saturation current in a MESFET

```

14
15 eps=eps_r*eps0;
16
17 //pinch-off voltage
18 Vp=q*Nd*d^2/(2*eps)
19
20 //threshold voltage
21 Vt0=Vd-Vp
22
23 //conductivity of the channel
24 sigma=q*mu_n*Nd
25
26 //Channel conductance
27 G0=q*sigma*Nd*W*d/L
28
29 //saturation current using the exact formula
30 Id_sat=G0*(Vp/3-(Vd-Vgs)+2/(3*sqrt(Vp))*(Vd-Vgs)
    .^(3/2)).*(1-(Vgs<Vt0));
31 Idss=Id_sat(1)
32
33 //saturation current using the quadratic law
    approximation
34 Id_sat_square=Idss*(1-Vgs/Vt0)^2;
35
36 plot(Vgs,Id_sat,Vgs,Id_sat_square);
37 legend('exact formula', 'quadratic approximation',2)
    ;
38 title('FET saturation current as a function of the
    gate-source voltage');
39 xlabel('Gate-source voltage V_{GS}, V');
40 ylabel('Drain saturation current I_{DSat}, A');

```

---

**Scilab code Exa 6.10** Current Voltage characteristics of a MESFET

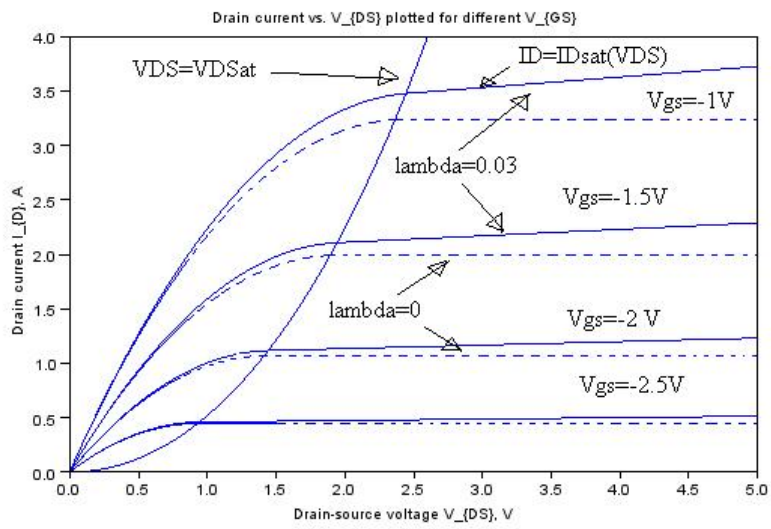


Figure 6.4: Current Voltage characteristics of a MESFET

```

1 //define problem parameters
2 Nd=1e16*1e6;
3 d=0.75e-6;
4 W=10e-6;
5 L=2e-6;
6 eps_r=12;
7 Vd=0.8;
8 mu_n=8500*1e-4;
9 lambda=0.03;
10
11 //define physical constants
12 q=1.60218e-19; //electron charge
13 eps0=8.85e-12; //permittivity of free space
14
15 eps=eps_r*eps0;
16
17 // pinch-off voltage
18 Vp=q*Nd*d^2/(2*eps)
19
20 //threshold voltage
21 Vt0=Vd-Vp
22
23 //conductivity of the channel
24 sigma=q*mu_n*Nd
25
26 //channel conductance
27 G0=q*sigma*Nd*W*d/L
28
29 //define the range for gate source voltage
30 Vgs_min=-2.5;
31 Vgs_max=-1;
32 Vgs=Vgs_max:-0.5:Vgs_min;
33
34 //drain source voltage
35 Vds=0:0.01:5;
36
37 //compute drain saturation voltage
38 Vds_sat=Vgs-Vt0;

```

```

39
40 //first the drain current is taken into account the
    channel length modulation
41 for n=1:length(Vgs)
42     if Vgs(n)>Vt0
43         Id_sat=G0*(Vp/3-(Vd-Vgs(n))+2/(3*sqrt(Vp))*(Vd
            -Vgs(n))^(3/2));
44     else
45         Id_sat=0;
46     end;
47
48     Id_linear=G0*(Vds-2/(3*sqrt(Vp)).*((Vds+Vd-Vgs(n)
            ).^(3/2)-(Vd-Vgs(n))^(3/2))).*(1+lambda*Vds);
49     Id_saturation=Id_sat*(1+lambda*Vds);
50     Id=Id_linear.*(Vds<=Vds_sat(n))+Id_saturation.*(
            Vds>Vds_sat(n));
51     plot(Vds,Id);
52 set(gca(),"auto_clear","off");
53 end;
54
55 //next the channel length modulation is not taken
    into account
56 for n=1:length(Vgs)
57     if Vgs(n)>Vt0
58         Id_sat=G0*(Vp/3-(Vd-Vgs(n))+2/(3*sqrt(Vp))*(Vd
            -Vgs(n))^(3/2));
59     else
60         Id_sat=0;
61     end;
62
63     Id_linear=G0*(Vds-2/(3*sqrt(Vp)).*((Vds+Vd-Vgs(n)
            ).^(3/2)-(Vd-Vgs(n))^(3/2)));
64     Id_saturation=Id_sat;
65     Id=Id_linear.*(Vds<=Vds_sat(n))+Id_saturation.*(
            Vds>Vds_sat(n));
66     plot(Vds,Id);
67 end;
68

```

```

69 //computation of drain saturation current
70
71 Vgs=0:-0.01:-4;
72 Vds_sat=Vgs-Vt0;
73
74 Id_sat=G0*(Vp/3-(Vd-Vgs)+2/(3*sqrt(Vp))*(Vd-Vgs)
      .^(3/2)).*(1+lambda*Vds_sat).*(1-(Vgs<Vt0));
75
76 plot(Vds_sat, Id_sat);
77
78 mtlb_axis([0 5 0 4]);
79 title('Drain current vs. V_{DS} plotted for
      different V_{GS}');
80 xlabel('Drain-source voltage V_{DS}, V');
81 ylabel('Drain current I_{D}, A');

```

---

**Scilab code Exa 6.11** Computation of HEMT related electric characteristics

```

1 //define problem parameters
2 Nd=1e18*1e6;
3 Vb=0.81;
4 eps_r=12.5;
5 d=50e-9;
6 dWc=3.5e-20;
7 W=10e-6;
8 L=0.5e-6;
9 mu_n=8500*1e-4;
10
11 //define physical constants
12 q=1.60218e-19;//electron charge
13 eps0=8.85e-12;//permittivity of free space
14

```

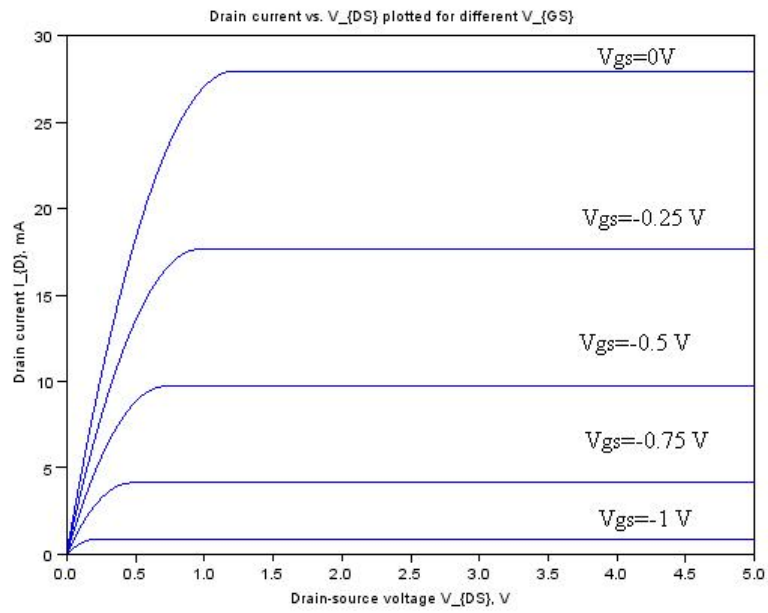


Figure 6.5: Computation of HEMT related electric characteristics



```

15 eps=eps_r*eps0;
16
17 //pinch-off voltage
18 Vp=q*Nd*d^2/(2*eps)
19
20 //threshold voltage
21 Vth=Vb-dWc/q-Vp
22
23 //drain-source applied voltage range
24 Vds=0:0.01:5;
25
26 //gate-source voltages
27 Vgs_r=-1:0.25:0;
28
29
30
31
32 for n=1:length(Vgs_r)
33     Vgs=Vgs_r(n);
34     Id=mu_n*W*eps/(L*d)*((Vds*(Vgs-Vth)-Vds.*Vds/2)
        .*(1-(Vds>(Vgs-Vth)))+1/2*(Vgs-Vth)^2*(1-(Vds
        <=(Vgs-Vth))));
35     plot(Vds,Id/1e-3);
36     set(gca(),"auto_clear","off");
37 end;
38
39
40 title('Drain current vs. V_{DS} plotted for
        different V_{GS}');
41 xlabel('Drain-source voltage V_{DS}, V');
42 ylabel('Drain current I_{D}, mA');

```

---

# Chapter 7

## Active RF Component Modelling

Scilab code Exa 7.1 Small signal pn diode model

```
1 //define problem parameters
2 TT=500e-12; // transit time
3 T0=300; //temperature
4 Is0=5e-15; // reverse saturation current at 300K
5 Rs=1.5; // series resistance
6 nn=1.16; //emission coefficient
7
8 // parameters needed to describe temperature
  behavior of
9 // the band-gap energy in Si
10 alpha=7.02e-4;
11 beta=1108;
12 Wg0=1.16;
13 pt=3;
14
15 // quiescent current
16 Iq=50e-3;
```

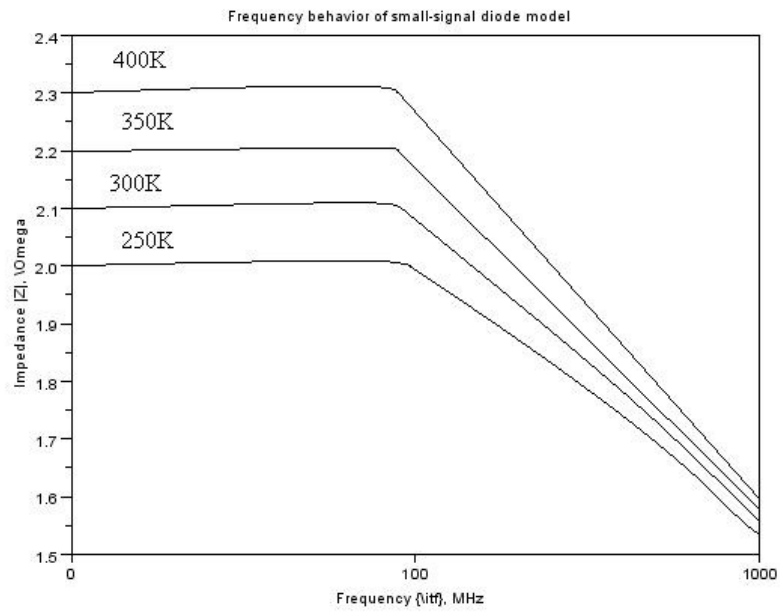


Figure 7.1: Small signal pn diode model

```

17
18 // frequency range 10MHz to 1GHz
19 f_min=10e6; // lower limit
20 f_max=1e9; //upper limit
21 N=300; // number of points in the graph
22 f=f_min*((f_max/f_min).^((0:N)/N)); // compute
    frequency points on log scale
23
24 // temperatures for which analysis will be performed
25 T_points=[250 300 350 400];
26
27 // define physical constants
28 q=1.60218e-19; // electron charge
29 k=1.38066e-23; // Boltzmann's constant
30
31 for n=1:length(T_points)
32     T=T_points(n);
33     s=sprintf('T=%f\n',T);
34     Vt=k*T/q;
35
36     Wg=Wg0-alpha*T^2/(beta+T);
37     s=sprintf('%s    Wg(T)=%f\n',s,Wg);
38
39     Is=Is0*(T/T0)^(pt/nn)*exp(-Wg/Vt*(1-T/T0));
40     s=sprintf('%s    Is(T)=%fe\n',s,Is);
41
42     Vq=nn*Vt*log(1+Iq/Is);
43     s=sprintf('%s    Vq(T)=%f\n',s,Vq);
44
45     Rd=nn*Vt/Iq;
46     s=sprintf('%s    Rd(T)=%f\n',s,Rd);
47
48     Cd=Is*TT/nn/Vt*exp(Vq/nn/Vt);
49     s=sprintf('%s    Cd(T)=%fpF\n',s,Cd/1e-12)
50
51     Zc=1./(%i*2*%pi*f*Cd);
52
53     Zin=Rs+Rd*Zc./(Rd+Zc);

```

```

54
55     plot(f/1e6,abs(Zin));
56     set(gca(),"auto_clear","off");
57 end;
58
59 title('Frequency behavior of small-signal diode
        model');
60 xlabel('Frequency {\itf}, MHz');
61 ylabel('Impedance |Z|, \Omega');

```

---

#### Scilab code Exa 7.4 Parameters of BJT

```

1 //first we define all parameters for the transistor
  and the circuit
2 Z0=50; //characteristic imedance of the system
3
4 Vcc=3.6; //power supply voltage
5 Vce=2; //collector voltage
6 Ic=10e-3; //collector current
7
8 T=300; //ambient temperature (300K)
9
10 //transistor parameters (they are very similar to
    BFG403W)
11 beta=145; // current gain
12 Is=5.5e-18; // saturation current
13 VAN= 30; // forward Early voltage
14 tau_f=4e-12; // forward transition time
15 rb=125; // base resistance
16 rc=15; // collector resistance
17 re=1.5; // emitter resistance
18 Lb=1.1e-9; // base inductance
19 Lc=1.1e-9; // collector inductance
20 Le=0.5e-9; // emitter inductance
21 Cjc=16e-15; // collector junction capacitance at

```

```

    zero applied voltage
22 mc=0.2;      // collector junction grading
    coefficient
23 Cje=37e-15; // emitter junction capacitance at zero
    applied voltage
24 me=0.35;    // emitter junction grading coefficient
25 phi_be=0.9; // base-emitter diffusion potential
26 phi_bc=0.6; // base-collector diffusion potential
27 Vbe=phi_be; // base-emitter voltage
28
29 // some physical constants
30 k=1.38e-23; // Boltzmann's constant
31 q=1.6e-19;  // elementary charge
32 VT=k*T/q;   // thermal potential
33
34 disp('DC biasing parameters');
35
36 Ib=Ic/beta;
37 disp("Amperes",Ib,"Base current");
38
39 Rc=(Vcc-Vce)/Ic;
40 disp("Ohms",Rc,"Collector resistance");
41
42 Rb=(Vcc-Vbe)/Ib;
43 disp("Ohms",Rb,"Base resistance");
44
45
46 r_pi=VT/Ib;
47 disp("Ohms",r_pi,"Rpi");
48
49 r0=VAN/Ic;
50 disp("Ohms",r0,"R0");
51
52 gm=beta/r_pi;
53 disp("Mho",gm,"Gm");
54
55 Vbc=Vbe-Vce;
56 Cmu=Cjc*(1-Vbc/phi_bc)^(-mc);

```

```

57 disp(" Farads",Cmu," base collector capacitance");
58
59 if(Vbe<0.5*phi_be)
60     Cpi_junct=Cje*(1-Vbe/phi_be)^(-me);
61 else
62     C_middle=Cje*0.5^(-me);
63     k_middle=1-0.5*me;
64     Cpi_junct=C_middle*(k_middle+me*Vbe/phi_be);
65 end;
66
67 disp(" Farads",Cpi_junct," Junction Capacitance");
68
69 Cpi_diff=Is*tau_f/VT*exp(Vbe/VT);
70 disp(" Farads",Cpi_diff," Differential capacitance");
71
72 Cpi=Cpi_junct+Cpi_diff;
73 disp(" Farads",Cpi," Total Capacitance");
74
75 C_miller=Cmu*(1+gm*r_pi/(r_pi+rb)*Z0*r0/(r0+rc+Z0));
76 disp(" Farads",C_miller," Miller Capacitance");
77
78 C_input=Cpi+C_miller;
79 disp(" Farads",C_input," Total input capacitance");

```

---

### Scilab code Exa 7.5 Cutoff frequency of GaAs MESFET

```

1 l=1*10^-6; //length
2 w=200*10^-6; //width
3 d=0.5*10^-6; //depth
4 E0=8.854*10^-12;
5 Er=13.1;
6 q=1.6*10^-19; //electron charge
7 Nd=1*10^16; //doping concentration
8 mun=8500;
9 Vp=(q*Nd*d^2)/(2*Er*E0);

```

```

10 G0=(q*mun*Nd*w)/l;
11 gm=0.0358;
12 Cap=(E0*Er*w*l)/d;
13 fT=gm/(2*pi*Cap);
14 disp("Hertz",fT,"Cut off frequency");

```

---

**Scilab code Exa 7.6** Small signal Hybrid pi parameters without Miller Effect

```

1 Icq=6*10^-3;
2 Ibq=40*10^-6;
3 Van=30; //Early voltage
4 q=1.6*10^-19;
5 k=1.38*10^-23;
6 T=300;
7 fT=37*10^9; //Transition frequency
8 gm=(Icq*q)/(k*T);
9 beta0=Icq/Ibq;
10 r0=Van/Icq;
11 rpi=beta0/gm;
12 Cpi=(beta0)/(2*pi*fT*rpi);
13 disp("Hybrid pi parametrs without Miller effect");
14 disp("Mho",gm,"gm");
15 disp("Ohms",rpi,"Rpi");
16 disp("Farads",Cpi,"Cpi");
17 disp("Ohms",r0,"R0");
18 disp(beta0,"Beta0");

```

---



# Chapter 8

## Matching and biasing networks

Scilab code Exa 8.11 Efficiency of different types of amplifiers

```
1 theta=(1:1:360)/180*%pi; //define conduction angle
2
3 //compute efficiency
4 nu=-1/2*(theta-sin(theta))./(theta.*cos(theta/2)-2*
    sin(theta/2));
5
6 plot(theta/%pi*180,nu*100,'r','linewidth',2);
7 set(gca(),"auto_clear","off");
8 plot([0 180],[%pi/4*100 %pi/4*100],'b:');
9 plot([180 180],[0 %pi/4*100],'b:');
10 plot(180,%pi/4*100,'bo');
11 plot(360,50,'bo');
12 mtlb_axis([0 360 50 100]);
13 title('Maximum theoretical efficiency of the
    amplifier');
14 xlabel('Conduction angle \Theta_0, deg. ');
15 ylabel('Efficiency \eta, %');
```

---

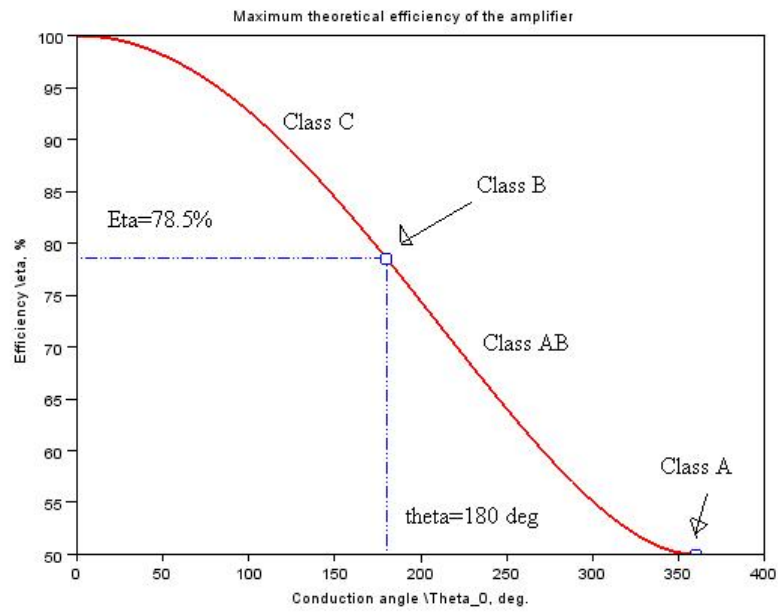


Figure 8.1: Efficiency of different types of amplifiers

**Scilab code Exa 8.12** Design of passive biasing networks for a BJT in CE config

```
1 Ic=10*10^-3; //Collector current
2 Vce=3;
3 Vcc=5;
4 beta=100; //current gain
5 Vbe=0.8;
6 I1=Ic+Ic/beta;
7 R1=(Vcc-Vce)/I1;
8 R2=(Vce-Vbe)/(Ic/beta);
9 Vx=1.5;
10 R3=(Vx-Vbe)/(Ic/beta);
11 Ix=10*(Ic/beta);
12 R11=(Vx/Ix);
13 R22=(Vcc-Vx)/(Ix+(Ic/beta));
14 R4=(Vcc-Vce)/Ic;
15 disp("Amperes",I1,"I1","Ohms",R1,"R1","Ohms",R2,"R2"
      ,"Ohms",R3,"R3","Ohms",R11,"R11","Ohms",R22,"R22"
      ,"Ohms",R4,"R4");
```

---

## Chapter 9

# RF Transistor Amplifier Design

Scilab code Exa 9.1 Power relations for an RF amplifier

```
1 //defining scattering parameters
2 S11=0.102-%i*0.281;
3 S21=0.305+%i*3.486;
4 S12=0.196-%i*0.03471;
5 S22=0.2828-%i*0.2828;
6
7 Vs=5;
8 Zs=40;
9 Zl=73;
10 Z0=50;
11
12 Ts=(Zs-Z0)/(Zs+Z0);
13 Tl=(Zl-Z0)/(Zl+Z0);
14 Tin=S11+(S21*S12*Tl)/(1-S22*Tl);
15 Tout=S22+(S12*S21*Ts)/(1-S11*Ts);
16
17 a=S21^2;
18 b=1-Ts^2;
19 c=1-Tl^2;
20
21 Gt=(c*a*b)/((1-Tl*Tout)^2*(1-S11*Ts)^2);
```

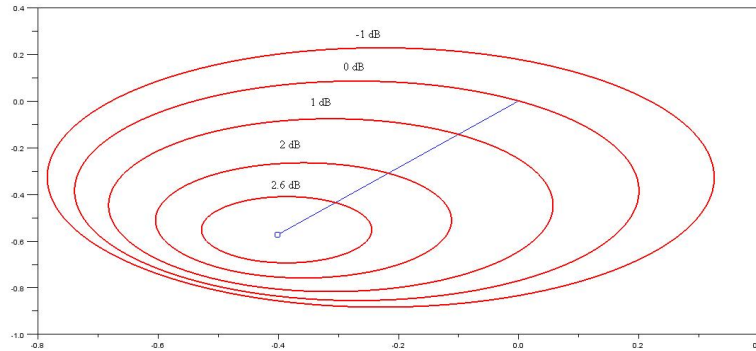


Figure 9.1: Computation of source gain circles for a unilateral design

```

22 Gtu=(c*a*b)/((1-T1*S22)^2*(1-S11*Ts)^2);
23 Ga=(a*b)/((1-Tout)^2*(1-S11*Ts)^2);
24 G=(a*c)/((1-Tin)^2*(1-S22*T1)^2);
25
26 d=abs(Gt);
27
28 Pin=(Z0*(Vs)^2)/((Zs+Z0)^2*(1-Tin*Ts)^2*2);
29 pinR=real(Pin);
30 pinI=imag(Pin);
31 Pinc=sqrt(pinR^2+pinI^2);
32 PA=78.1*10^-3;
33 Pl=PA*d;
34 disp(Pl,"Power delivered to load in watts");

```

---

**Scilab code Exa 9.7** Computation of source gain circles for a unilateral design

```

1 //define s11 parameter of the transistor
2 s11=0.7*exp(%i*(125)/180*%pi);

```

```

3
4 //compute the maximum gain achievable by the input
   matching network
5 Gs_max=1/(1-abs(s11)^2);
6 Gs_max_dB=10*log10(Gs_max)
7
8 //find the reflection coefficient for the maximum
   gain
9 Gs_opt=conj(s11);
10
11 //draw a straight line connecting Gs_opt and the
   origin
12 set(gca(),"auto_clear","off");
13 plot([0 real(Gs_opt)],[0 imag(Gs_opt)],'b');
14 plot(real(Gs_opt),imag(Gs_opt),'bo');
15
16 //specify the angle for the constant gain circles
17 a=(0:360)/180*pi;
18
19 //plot source gain circles
20 gs_db=[-1 0 1 2 2.6];
21 gs=exp(gs_db/10*log(10))/Gs_max;
22
23 for n=1:length(gs)
24     dg=gs(n)*conj(s11)/(1-abs(s11)^2*(1-gs(n)));
25     rg=sqrt(1-gs(n))*(1-abs(s11)^2)/(1-abs(s11)^2*(1-
       gs(n)));
26     plot(real(dg)+rg*cos(a),imag(dg)+rg*sin(a),'r','
       linewidth',2);
27 end;

```

---

**Scilab code Exa 9.8** Design of 18 dB single stage MESFET amplifier

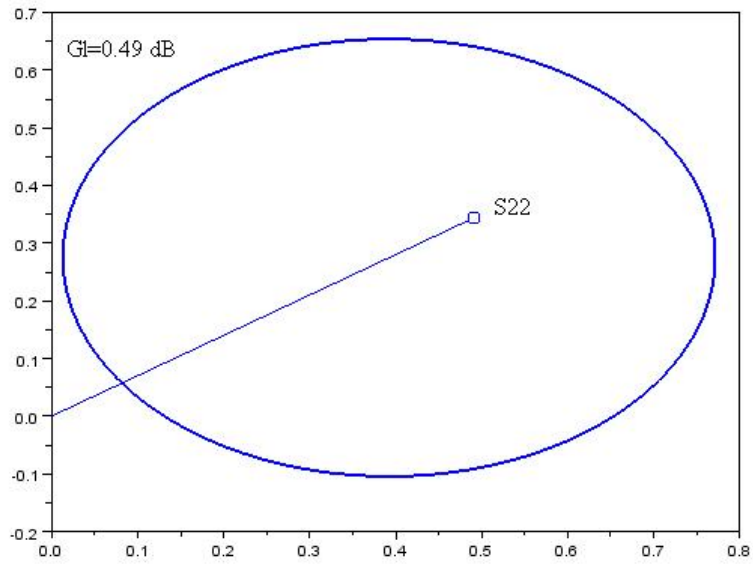


Figure 9.2: Design of 18 dB single stage MESFET amplifier

```

1 s11=0.5*exp(%i*(-60)/180*%pi);
2 s12=0.02*exp(%i*(-0)/180*%pi);
3 s21=6.5*exp(%i*(+115)/180*%pi);
4 s22=0.6*exp(%i*(-35)/180*%pi);
5
6 Gs_max=1/(1-abs(s11)^2);
7 Gl_max=1/(1-abs(s22)^2);
8
9 G0=abs(s21)^2;
10
11 Gmax=Gs_max*G0*Gl_max;
12 Gs_max_dB=10*log10(Gs_max)
13 Gl_max_dB=10*log10(Gl_max)
14 G0_dB=10*log10(G0)
15 Gmax_dB=10*log10(Gmax)
16 Ggoal_dB=18;
17 Gload_dB=Ggoal_dB-G0_dB-Gs_max_dB;
18 Gl_opt=conj(s22);
19
20 set(gca(),"auto_clear","off");
21 plot([0 real(Gl_opt)], [0 imag(Gl_opt)], 'b');
22 plot(real(Gl_opt), imag(Gl_opt), 'bo');
23 a=(0:360)/180*%pi;
24 gl=exp([Gload_dB]/10*log(10))/Gl_max;
25 dg=gl*conj(s22)/(1-abs(s22)^2*(1-gl));
26 rg=sqrt(1-gl)*(1-abs(s22)^2)/(1-abs(s22)^2*(1-gl));
27 plot(real(dg)+rg*cos(a), imag(dg)+rg*sin(a), 'b', '
    linewidth', 2);

```

---

**Scilab code Exa 9.13** Amplifier design using the constant operating gain circles

```
1 //define the S-parameters of the transistor
```



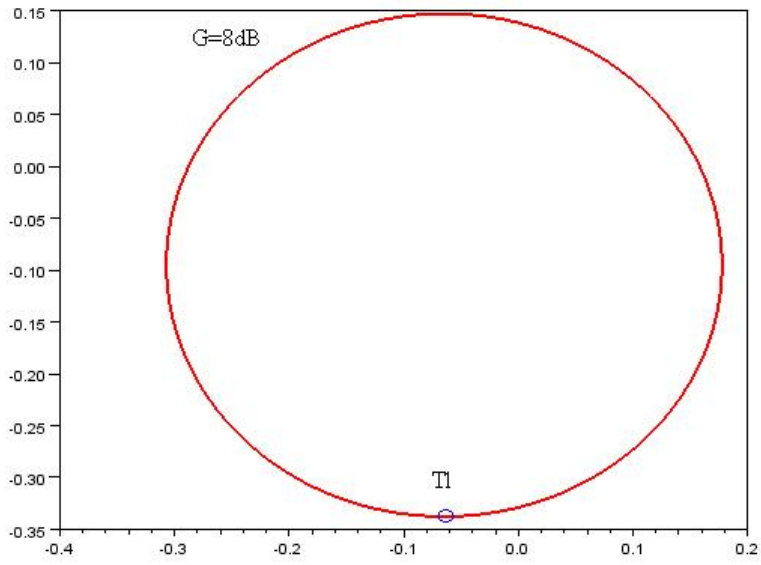


Figure 9.3: Amplifier design using the constant operating gain circles

```

2 s11=0.3*exp(%i*(+30)/180*%pi);
3 s12=0.2*exp(%i*(-60)/180*%pi);
4 s21=2.5*exp(%i*(-80)/180*%pi);
5 s22=0.2*exp(%i*(-15)/180*%pi);
6
7 K=1.18
8
9 //find the maximum gain
10 Gmax=abs(s21/s12)*(K-sqrt(K^2-1));
11 Gmax_dB=10*log10(Gmax)
12
13 //specify the target gain
14 G_goal_dB=8; //would like to build an amplifier with
    8dB gain
15 G_goal=10^(G_goal_dB/10); //convert from dB to
    normal units
16
17 //find constant operating power gain circles
18 go=G_goal/abs(s21)^2;
19
20 //find the center of the constant operating power
    gain circle
21 dgo=go*conj(s22-conj(s11))/(1+go*(abs(s22)^2));
22
23
24 //find the radius of the circle
25 rgo1=sqrt(1-2*K*go*abs(s12*s21)+go^2*abs(s12*s21)^2)
    ;
26 rgo=rgo1/abs(1+go*(abs(s22)^2));
27
28 //plot a circle in the Smith Chart
29 a=(0:360)/180*%pi;
30
31 set(gca(),"auto_clear","off");
32 plot(real(dgo)+rgo*cos(a),imag(dgo)+rgo*sin(a),'r','
    linewidth',2);
33
34 //choose the load reflection coefficient

```

```

35 zL=1-%i*0.53
36 GL=(zL-1)/(zL+1);
37
38 plot(real(GL), imag(GL), 'bo');
39
40 [Ro, Theta]=polar(atan(imag(Gs), real(Gs)));
41 Gin=s11+s12*s21*GL/(1-s22*GL);
42 Gs=conj(Gin);
43 Gs_abs=abs(Gs)
44 Gs_angle=(Theta/%pi)*180;
45
46 zs=(1+Gs)/(1-Gs);

```

---

**Scilab code Exa 9.14** Design of small signal amplifier for minimum noise figure and specified gain

```

1 global Z0;
2 Z0=50;
3
4 //define the S-parameters of the transistor
5 s11=0.3*exp(%i*(+30)/180*%pi);
6 s12=0.2*exp(%i*(-60)/180*%pi);
7 s21=2.5*exp(%i*(-80)/180*%pi);
8 s22=0.2*exp(%i*(-15)/180*%pi);
9
10 //pick the noise parameters of the transistor
11 Fmin_dB=1.5
12 Fmin=10^(Fmin_dB/10);
13 Rn=4;
14 Gopt=0.5*exp(%i*45/180*%pi);
15
16 //compute a noise circle
17 Fk_dB=1.6;

```

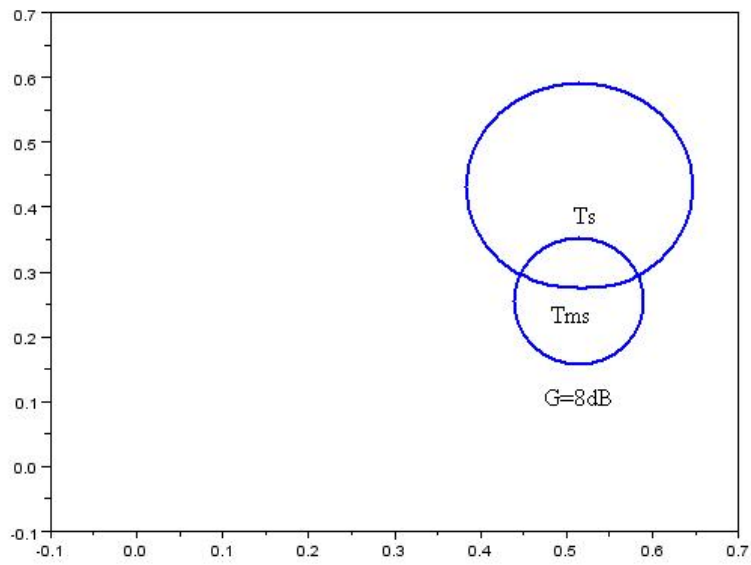


Figure 9.4: Design of small signal amplifier for minimum noise figure and specified gain

```

18 Fk=10^(Fk_dB/10);
19
20
21 Qk=abs(1+Gopt)^2*(Fk-Fmin)/(4*Rn/Z0) //noise circle
    parameter
22 dfk=Gopt/(1+Qk); //circle center location
23 rfk=sqrt((1-abs(Gopt)^2)*Qk+Qk^2)/(1+Qk) //circle
    radius
24
25
26 //plot a noise circle
27 a=[0:360]/180*pi;
28 set(gca(),"auto_clear","off");
29 plot(real(dfk)+rfk*cos(a),imag(dfk)+rfk*sin(a),'b','
    linewidth',2);
30
31 // plot optimal reflection coefficient
32 plot(real(Gopt),imag(Gopt),'bo');
33
34
35 //specify the desired gain
36 G_goal_dB=8;
37 G_goal=10^(G_goal_dB/10);
38
39 //find the constant operating power gain circles
40 go=G_goal/abs(s21)^2; // normalized the gain
41 dgo=go*conj(s22-conj(s11))/(1+go*(abs(s22)^2)); //
    center
42
43 rgo=sqrt(1-2*K*go*abs(s12*s21)+go^2*abs(s12*s21)^2);
44 rgo=rgo/abs(1+go*(abs(s22)^2));
45
46 //map a constant gain circle into the Gs plane
47 rgs=rgo*abs(s12*s21/(abs(1-s22*dgo)^2-rgo^2*abs(s22)
    ^2));
48 dgs=((1-s22*dgo)*conj(s11-dgo)-rgo^2*s22)/(abs(1-s22
    *dgo)^2-rgo^2*abs(s22)^2);
49

```

```

50 //plot a constant gain circle in the Smith Chart
51 set(gca(),"auto_clear","off");
52 plot(real(dgs)+rgs*cos(a),imag(dgs)+rgs*sin(a),'r','
    linewidth',2);
53
54
55
56 //choose a source reflection coefficient Gs
57 Gs=dgs+%i*rgs;
58 plot(real(Gs), imag(Gs), 'ro');
59 //text(real(Gs)-0.05,imag(Gs)+0.08,'\bf\Gamma_S');
60
61 //find the actual noise figure
62 F=Fmin+4*Rn/Z0*abs(Gs-Gopt)^2/(1-abs(Gs)^2)/abs(1+
    Gopt)^2;
63
64 //print out the actual noise figure
65 Actual_F_dB=10*log10(F)

```

---

**Scilab code Exa 9.15** Constant VSWR design for given gain and noise figure

```

1 global Z0;
2 Z0=50;
3
4 //define the S-parameters of the transistor
5 s11=0.3*exp(%i*(+30)/180*%pi);
6 s12=0.2*exp(%i*(-60)/180*%pi);
7 s21=2.5*exp(%i*(-80)/180*%pi);
8 s22=0.2*exp(%i*(-15)/180*%pi);
9
10 //noise parameters of the transistor
11 Fmin_dB=1.5
12 Fmin=10^(Fmin_dB/10);
13 Rn=4;

```

```

14 Gopt=0.5*exp(%i*45/180*%pi);
15
16
17 //compute a noise circle
18 Fk_dB=1.6;//desired noise performance
19 Fk=10^(Fk_dB/10);
20
21 Qk=abs(1+Gopt)^2*(Fk-Fmin)/(4*Rn/Z0); //noise circle
    parameter
22 dfk=Gopt/(1+Qk); //circle center location
23 rfk=sqrt((1-abs(Gopt)^2)*Qk+Qk^2)/(1+Qk); //circle
    radius
24
25
26 //plot a noise circle
27 a=[0:360]/180*%pi;
28 set(gca(),"auto_clear","off");
29 plot(real(dfk)+rfk*cos(a),imag(dfk)+rfk*sin(a),'b','
    linewidth',2);
30
31 //specify the goal gain
32 G_goal_dB=8;
33 G_goal=10^(G_goal_dB/10);
34
35
36 //find constant operating power gain circles
37 go=G_goal/abs(s21)^2; //normalized gain
38 dgo=go*conj(s22-delta*conj(s11))/(1+go*(abs(s22)^2))
    ; //center
39
40 rgo=sqrt(1-2*K*go*abs(s12*s21)+go^2*abs(s12*s21)^2);
41 rgo=rgo/abs(1+go*(abs(s22)^2)); //radius
42
43 //map a constant gain circle into the Gs plane
44 rgs=rgo*abs(s12*s21/(abs(1-s22*dgo)^2-rgo^2*abs(s22)
    ^2));
45 dgs=((1-s22*dgo)*conj(s11-delta*dgo)-rgo^2*s22)/(abs
    (1-s22*dgo)^2-rgo^2*abs(s22)^2);

```

```

46
47 //plot constant gain circle in the Smith Chart
48 set(gca(),"auto_clear","off");
49 plot(real(dgs)+rgs*cos(a),imag(dgs)+rgs*sin(a),'r','
    linewidth',2);
50
51
52 //choose a source reflection coefficient Gs
53 Gs=dgs+%i*rgs;
54
55 //find the corresponding GL
56 GL=(s11-conj(Gs))/(delta-s22*conj(Gs));
57
58 //find the actual noise figure
59 F=Fmin+4*Rn/Z0*abs(Gs-Gopt)^2/(1-abs(Gs)^2)/abs(1+
    Gopt)^2;
60
61 %% print out the actual noise figure
62 Actual_F_dB=10*log10(F)
63
64 //find the input and output reflection coefficients
65 Gin=s11+s12*s21*GL/(1-s22*GL);
66 Gout=s22+s12*s21*Gs/(1-s11*Gs);
67
68
69 //find the VSWRin and VSWRout
70 Gimn=abs((Gin-conj(Gs))/(1-Gin*Gs));
71 Gomn=abs((Gout-conj(GL))/(1-Gout*GL));
72
73 VSWRin=(1+Gimn)/(1-Gimn); //VSWRin should be unity
    since we used the constant operating gain
    approach
74 VSWRout=(1+Gomn)/(1-Gomn);
75
76 //specify the desired VSWRin
77 VSWRin=1.5;
78
79 //find parameters for constant VSWR circle

```



```

80 Gimn=(1-VSWRin)/(1+VSWRin)
81 dvimn=(1-Gimn^2)*conj(Gin)/(1-abs(Gimn*Gin)^2); //
    circle center
82 rvimn=(1-abs(Gin)^2)*abs(Gimn)/(1-abs(Gimn*Gin)^2);
    //circle radius
83
84 //plot VSWRin=1.5 circle in the Smith Chart
85 plot(real(dvimn)+rvimn*cos(a),imag(dvimn)+rvimn*sin(
    a),'g','linewidth',2);
86
87
88 //plot a graph of the output VSWR as a function of
    the Gs position on the constant VSWRin circle
89 Gs=dvimn+rvimn*exp(%i*a);
90 Gout=s22+s12*s21*Gs./(1-s11*Gs);
91
92 //find the reflection coefficients at the input and
    output matching networks
93 Gimn=abs((Gin-conj(Gs))./(1-Gin*Gs));
94 Gomn=abs((Gout-conj(GL))./(1-Gout*GL));
95
96 //and find the corresponding VSWRs
97 VSWRin=(1+Gimn)./(1-Gimn);
98 VSWRout=(1+Gomn)./(1-Gomn);
99
100 figure; //open new figure for the VSWR plot
101 plot(a/%pi*180,VSWRout,'r',a/%pi*180,VSWRin,'b','
    linewidth',2);
102 legend('VSWR_{out}','VSWR_{in}');
103 title('Input and output VSWR as a function of \
    Gamma.S position');
104 xlabel('Angle \alpha, deg. ');
105 ylabel('Input and output VSWRs');
106 mtlb_axis([0 360 1.3 2.3])
107
108
109 //choose a new source reflection coefficient
110 Gs=dvimn+rvimn*exp(%i*85/180*%pi);

```

```

111
112 //find the corresponding output reflection
      coefficient
113 Gout=s22+s12*s21*Gs./(1-s11*Gs);
114
115 //compute the transducer gain in this case
116 GT=(1-abs(GL)^2)*abs(s21)^2.*(1-abs(Gs).^2)./abs(1-
      GL*Gout).^2./abs(1-Gs*s11).^2;
117 GT_dB=10*log10(GT)
118
119 //find the input and output matching network
      reflection coefficients
120 Gimn=abs((Gin-conj(Gs))./(1-Gin*Gs));
121 Gomn=abs((Gout-conj(GL))./(1-Gout*GL));
122
123 //and find the corresponding VSWRs
124 VSWRin=(1+Gimn)./(1-Gimn)
125 VSWRout=(1+Gomn)./(1-Gomn)
126
127 //also compute the obtained noise figure
128 F=Fmin+4*Rn/Z0*abs(Gs-Gopt)^2/(1-abs(Gs)^2)/abs(1+
      Gopt)^2;
129 F_dB=10*log10(F)

```

---

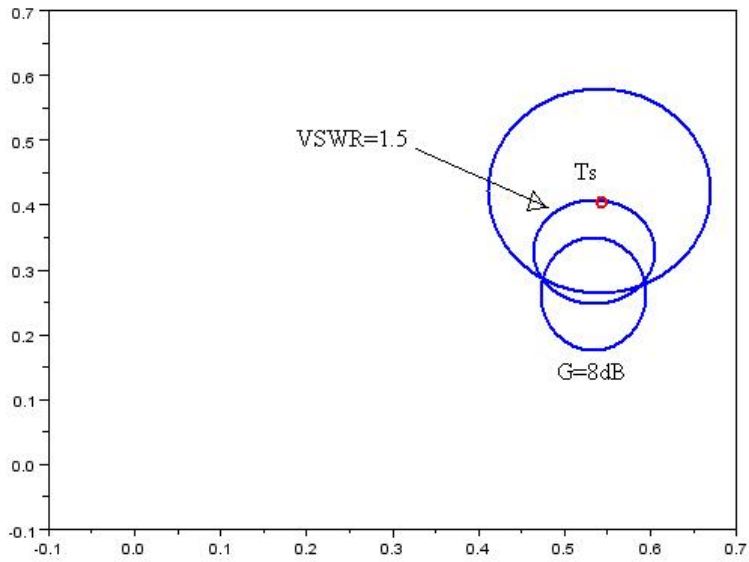


Figure 9.5: Constant VSWR design for given gain and noise figure

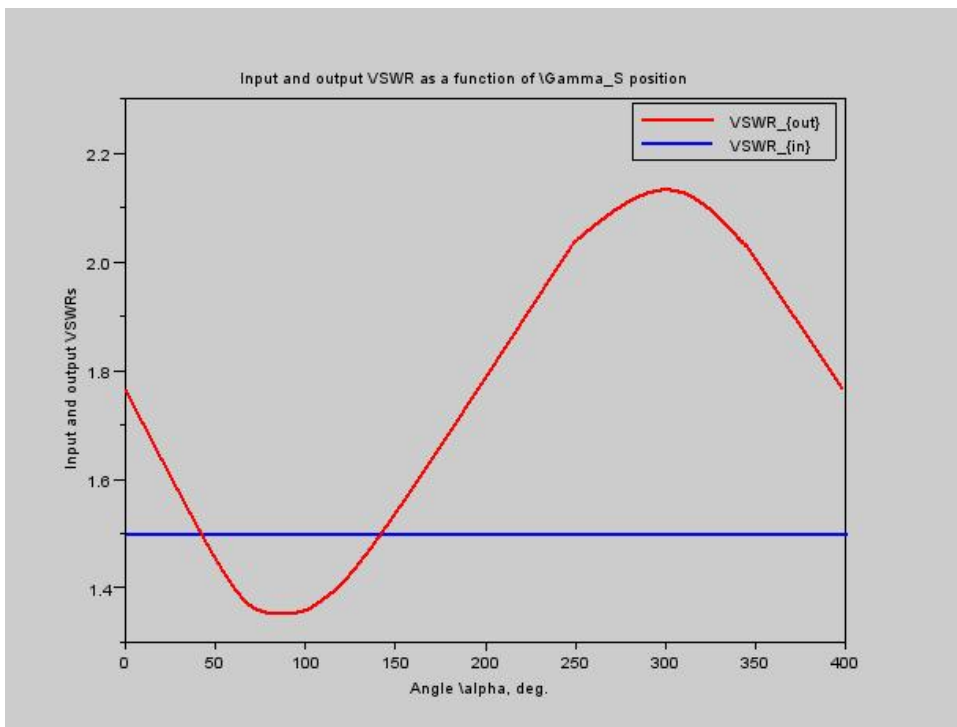


Figure 9.6: Constant VSWR design for given gain and noise figure

# Chapter 10

## Oscillators and Mixers

Scilab code Exa 10.1 Design of a Colpitt oscillator

```
1 fo=200*10^6;
2 Vce=3;
3 Ic=3*10^-3;
4
5 Cbc=0.1*10^-15;
6 rBE=2*10^3;
7 rCE=10*10^3;
8 Cbe=100*10^-15;
9 L3=50*10^-9;
10 L=50*10^-9;
11 gm=0.11666;
12
13 disp("DC values of Hparameters are");
14 h11=rBE;
15 h12=0;
16 h21=rBE*gm;
17 h22=1/rCE;
18
19 disp("Mho",h22,"h22",h21,"h21",h12,"h12","Ohms",h11,
      "h11");
20 k=h21/(h11*h22-h21*h12);
```

```

21 A=(1+k)/L;
22 B=A^2;
23 C=16*k*(%pi)^2*fo^2*(h22/h11);
24 D=8*k*(%pi)^2*fo^2;
25 C2=(A+sqrt(B+C))/D;
26 C1=k*C2;
27
28 disp("H parameters at resonance frequency");
29 w=2*%pi*fo;
30 E=1+%i*w*(Cbe+Cbc)*rBE;
31
32 hie=rBE/E;
33 hre=(%i*w*Cbc*rBE)/E;
34 hfe=(rBE*(gm-%i*w*Cbc))/E;
35 hoe=h22+(%i*w*Cbc*(1+gm*rBE+%i*w*Cbe*rBE))/E;
36 disp("Mho",hoe,"hoe",hfe,"hfe",hre,"hre","Ohms",hie,
      "hie");

```

---

## Scilab code Exa 10.2 Prediction of resonance frequencies of quartz crystal

```

1  stacksize("max");
2  //define crystal parameters
3  Lq=0.1;
4  Rq=25;
5  Cq=0.3*10^-12;
6  C0=1*10^-12;
7
8  //find series resonance frequency
9  ws0=1/sqrt(Lq*Cq);
10 disp(ws0);
11 ws=ws0*(1+Rq^2/2*C0/Lq);
12 fs=ws/2/%pi
13
14 //find parallel resonance frequency
15 wp0=sqrt((Cq+C0)/(Lq*Cq*C0));

```

```

16 wp=wp0*(1-Rq^2/2*C0/Lq);
17 fp=wp/2/%pi
18
19 //define frequency range for this plot
20 f=(0.9:0.00001:1.1)*1e6;
21 w=2*%pi*f;
22
23 //find abmittance of the resonator
24 Y=%i.*w*C0+1./(Rq+%i*(w*Lq-1./(w*Cq)));
25
26 plot(f/1e6,abs(imag(Y)));
27 mtlb_axis([0.9 1.1 1e-10 1e-1]);
28 title('Admittance of the quartz crystal resonator');
29 xlabel('Frequency {\itf}, MHz');
30 ylabel('Susceptance |B|, \Omega');

```

---

**Scilab code Exa 10.3** Adding a positive feedback element to initiate oscillations

```

1 Z0=50;
2 //oscillation frequency
3 f=2*10^9;
4 w=2*%pi*f;
5 //transistor S-parameters at oscillation frequency
6
7 s_tr=[0.94*exp(%i*174/180*%pi),0.013*exp(-%i*98/180*
      %pi);1.9*exp(-%i*28/180*%pi),1.01*exp(-%i*17/180*
      %pi)];
8 s11=ss2tf(1,1);
9 s12=ss2tf(1,2);
10 s21=ss2tf(2,1);
11 s22=ss2tf(2,2);
12

```

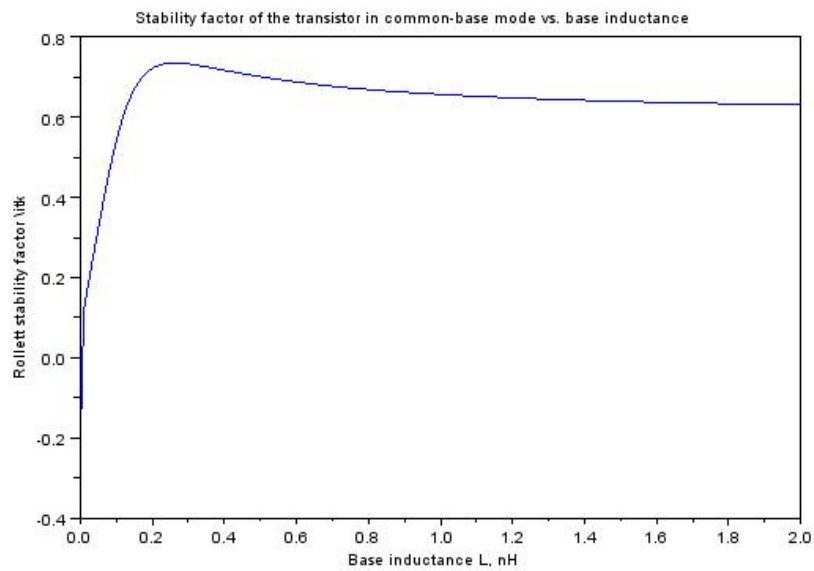


Figure 10.1: Adding a positive feedback element to initiate oscillations



```

13 //find the Z-parameters of the transistor
14 z_tr=ss2tf(s_tr,Z0);
15
16 //attempt to add inductor to base in order to
    increase instability
17 L=(0:0.01:2)*1e-9;
18
19 Z_L=%i*w*L;
20 z_L=[1,1;1,1];
21
22 N=length(L);
23
24 //create variables for the S-parameters of the
    transistor with the inductor
25 s11=zeros([1 N]);
26 s12=zeros([1 N]);
27 s21=zeros([1 N]);
28 s22=zeros([1 N]);
29
30 //Rollett stability factor
31 K=zeros([1 N]);
32
33 for n=1:N
34     z_total=z_tr+z_L*Z_L(n);
35     s_total=ss2tf(z_total,Z0);
36     s11(n)=s_total(1,1);
37     s12(n)=s_total(1,2);
38     s21(n)=s_total(2,1);
39     s22(n)=s_total(2,2);
40     K(n)=(1-abs(s11(n))^2-abs(s22(n))^2+abs(det(
        s_total))^2)/2/abs(s12(n)*s21(n));
41 end;
42
43 plot(L/1e-9,K);
44 title('Stability factor of the transistor in common-
    base mode vs. base inductance');
45 xlabel('Base inductance L, nH');
46 ylabel('Rollett stability factor \itk')

```

---

**Scilab code Exa 10.6** Dielectric resonator oscillator design

```
1 //define the S-paramters of the transistor at
   resonance frequency
2 s11=1.1*exp(%i*(170)/180*%pi);
3 s12=0.4*exp(%i*(-98)/180*%pi);
4 s21=1.5*exp(%i*(-163)/180*%pi);
5 s22=0.9*exp(%i*(-170)/180*%pi);
6
7 s=[s11 , s12 ; s21 , s22];
8
9 //define oscillation frequency
10 f0=8e9;
11 w0=2*%pi*f0;
12
13 //define parameters of the dielectric resonator
14 Z0=50;
15 beta=7;
16 R=beta*2*Z0;
17 Qu=5e3;
18
19 //compute equivalent L and C
20 L=R/(Qu*w0);
21 C=1/(L*w0^2);
22
23 //find output reflection coefficient of the DR
24 Gout_abs=beta/(1+beta);
25 Gout_angle=-atan(imag(s11),real(s11))/%pi*180;
26
27 //compute electrical length of the transmission line
   for the DR
28 theta0=-1/2*Gout_angle
29 Gout=Gout_abs*exp(%i*Gout_angle*%pi/180);
30
```

```

31 //find the output impedance of the DR
32 Zout=Z0*(1+Gout)/(1-Gout)
33
34
35 // find the equivalent capacitance (it will be
    necessary for the computation of the oscillator
    without DR)
36 CC=-1/(w0*imag(Zout))
37
38 Rs=50;
39
40 //define the frequency for the plot
41 delta_f=0.05e9; //frequency range
42 f=f0-delta_f/2 : delta_f/100 : f0+delta_f/2;
43 w=2*%pi*f;
44
45 if theta0<0
46     theta0=360+theta0;
47 end;
48
49 theta=theta0*f/f0/180*%pi;
50
51 //repeat the same computations as above, but for
    specified frequency range
52 Gs=(Rs-Z0)/(Rs+Z0);
53 G1=Gs*exp(-%i*2*theta);
54 R1=Z0*(1+G1)/(1-G1);
55 Zd=1./(1/R+1./(%i*w*L+%i*w*C));
56 R1d=R1+Zd;
57 G1d=(R1d-Z0)/(R1d+Z0);
58 G2=G1d.*exp(-%i*2*theta);
59
60 //compute the output reflection coefficient (we have
    oscillations if |Gout|>1)
61 Gout=s22+s12*s21*G2./(1-s11*G2);
62
63 figure;
64 plot(f/1e9,abs(Gout),'b','linewidth',2);

```

```

65 title('Output reflection coefficient of the
        oscillator with DR');
66 xlabel('Frequency f, GHz');
67 ylabel('Output reflection coefficient |\Gamma_{out}|
        ');
68 mtlb_axis([7.975 8.025 0 14]);
69
70
71 //Redefine the frequency range (we have to increase
        it in order to be able to observe any variations
        in the response
72 delta_f=5e9;
73 f=f0-delta_f/2 : delta_f/100 : f0+delta_f/2;
74 w=2*pi*f;
75
76 //Compute the output reflection coefficient of the
        oscillator but with DR replaced by a series
        combination of resistance and capacitance
77 ZZ2=real(Zout)+1./(%i*w*CC);
78 GG2=(ZZ2-Z0)./(ZZ2+Z0);
79 GG=s22+s12*s21*GG2./(1-s11*GG2);
80
81 figure;
82 plot(f/1e9,abs(GG),'r','linewidth',2);
83 title('Output reflection coefficient of the
        oscillator without DR');
84 xlabel('Frequency f, GHz');
85 ylabel('Output reflection coefficient |\Gamma_{out}|
        ');

```

---

Scilab code Exa 10.8 Local oscillator frequency selection

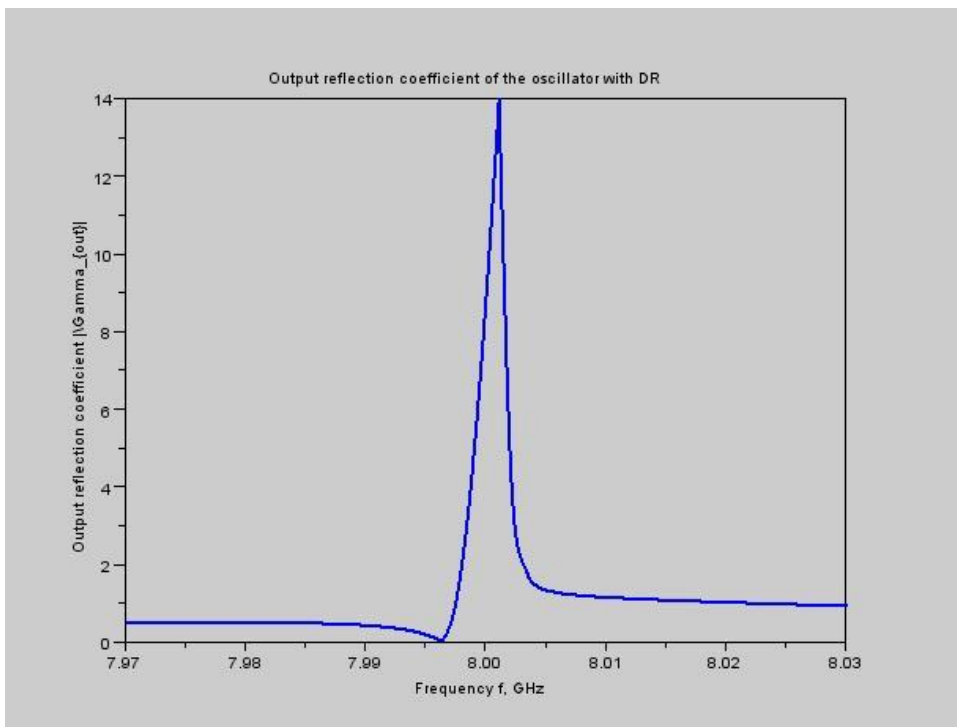


Figure 10.2: Dielectric resonator oscillator design

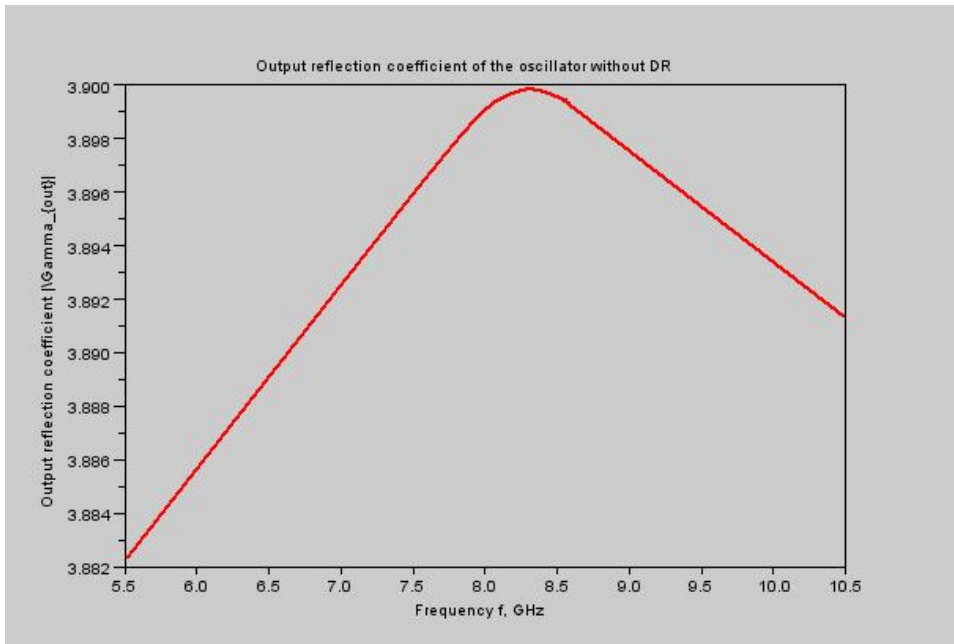


Figure 10.3: Dielectric resonator oscillator design

```

1 fRF=1.89*10^9; //RF frequency
2 BW=20*10^6; //Bandwidth
3 fIF=200*10^6; //Intermediate Frequency
4 flo=fRF+fIF; //Local oscillator frequency
5 Q=fIF/BW; //Quality factor
6 disp(Q,"Quality Factor");

```

---