

Scilab Textbook Companion for
Radio Frequency Circuit Design
by R. Ludwig And G. Bogdanov¹

Created by
Monisha Dhirmalani
Engineering
Others
Mumbai University
College Teacher
Monali Chaudhari
Cross-Checked by

August 10, 2013

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Radio Frequency Circuit Design

Author: R. Ludwig And G. Bogdanov

Publisher: Pearson Education India, New Delhi

Edition: 2

Year: 2011

ISBN: 978-81-317-6218-9

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Introduction	8
2 Transmission line analysis	15
3 The Smith Chart	24
4 Single and Multiport Networks	27
5 An Overview of RF Filter Design	29
6 Active RF Components	34
7 Active RF Component Modelling	49
8 Matching and biasing networks	56
9 RF Transistor Amplifier Design	59
10 Oscillators and Mixers	76

List of Scilab Codes

Exa 1.1	Intrinsic wave impedance	8
Exa 1.2	Comparing Inductances at different frequencies	8
Exa 1.3	Frequency response of high frequency resistor	9
Exa 1.4	Frequency response of high frequency capacitor	10
Exa 1.5	frequency response of high frequency inductor	12
Exa 2.1	Magnetic field inside and outside infinitely long current carrying wire	15
Exa 2.3	Transmission line parameters of a parallel copper plate transmission line	17
Exa 2.5	Phase velocity and Wavelength of PCB material	17
Exa 2.6	Input Impedance for a short circuited transmission line	19
Exa 2.7	Input impedance of open circuited transmission line	19
Exa 2.8	Quarter wave parallel plate line transformer	21
Exa 2.9	Power considerations of a transmission line	22
Exa 2.10	Return Loss of Transmission line section	23
Exa 3.2	Input Impedance	24
Exa 3.4	SWR circles	24
Exa 4.3	Internal resistances and current gain of BJT	27
Exa 4.7	S parameters and resistive elements of T network	27
Exa 5.1	Resonance frequency of a Bandpass filter	29
Exa 5.2	Quality factors of a filter	31
Exa 6.1	Conductivity of Si and Ge and GaAs	34
Exa 6.2	Barrier Voltage of a pn Junction	36
Exa 6.3	Depletion Layer Capacitance of a pn Junction	36
Exa 6.4	Parameters of a Schottky diode	39
Exa 6.7	Maximum forward current gain of bipolar junction transistor	39

Exa 6.8	Thermal analysis involving a BJT mounted on a heat sink	40
Exa 6.9	Drain saturation current in a MESFET	40
Exa 6.10	Current Voltage characterisitcs of a MESFET	42
Exa 6.11	Computation of HEMT related electric characteristics	46
Exa 7.1	Small signal pn diode model	49
Exa 7.4	Parameters of BJT	52
Exa 7.5	Cutoff frequency of GaAs MESFET	54
Exa 7.6	Small signal Hybrid pi parameters without Miller Effect	55
Exa 8.11	Efficiency of different types of amplifiers	56
Exa 8.12	Design of passive biasing networks for a BJT in CE config	58
Exa 9.1	Power relations for an RF amplifier	59
Exa 9.7	Computation of source gain circles for a unilateral design	60
Exa 9.8	Design of 18 dB single stage MESFET amplifier	61
Exa 9.13	Amplifier design using the constant operating gain circles	63
Exa 9.14	Design of small signal amplifier for minimum noise figure and specified gain	66
Exa 9.15	Constant VSWR design for given gain and noise figure	69
Exa 10.1	Design of a Colpitt oscillator	76
Exa 10.2	Prediction of resonance frequencies of quartz crystal	77
Exa 10.3	Adding a positive feedback element to initiate oscillations	78
Exa 10.6	Dielectric resonator oscillator design	81
Exa 10.8	Local oscillator frequency selection	83

List of Figures

1.1	Frequency response of high frequency resistor	10
1.2	Frequency response of high frequency capacitor	11
1.3	frequency response of high frequency inductor	13
2.1	Magnetic field inside and outside infinitely long current carrying wire	16
2.2	Input Impedance for a short circuited transmission line	18
2.3	Input impedance of open circuited transmission line	20
2.4	Quarter wave parallel plate line transformer	21
3.1	SWR circles	25
5.1	Resonance frequency of a Bandpass filter	30
5.2	Quality factors of a filter	31
6.1	Conductivity of Si and Ge and GaAs	35
6.2	Depletion Layer Capacitance of a pn Junction	37
6.3	Drain saturation current in a MESFET	41
6.4	Current Voltage characterisitcs of a MESFET	43
6.5	Computation of HEMT related electric characteristics	47
7.1	Small signal pn diode model	50
8.1	Efficiency of different types of amplifiers	57
9.1	Computation of source gain circles for a unilateral design . .	60
9.2	Design of 18 dB single stage MESFET amplifier	62
9.3	Amplifier design using the constant operating gain circles . .	64
9.4	Design of small signal amplifier for minimum noise figure and specified gain	67

9.5	Constant VSWR design for given gain and noise figure	74
9.6	Constant VSWR design for given gain and noise figure	75
10.1	Adding a positive feedback element to initiate oscillations	79
10.2	Dielectric resonator oscillator design	84
10.3	Dielectric resonator oscillator design	85

Chapter 1

Introduction

Scilab code Exa 1.1 Intrinsic wave impedance

```
1 mu0=4*pi*10^-7; // defining permeability of free  
space  
2 epsilon0=8.85*10^-12; // defining permittivity of  
free space  
3 z0=sqrt(mu0/epsilon0); // calculating intrinsic  
impedance  
4 epsilonr=4.6; // defining relative permittivity  
5 vp=1/sqrt(mu0*epsilon0*epsilonr); // calculating  
phase velocity  
6 f1=30*10^6;  
7 f2=3*10^9;  
8 lambda1=vp/(f1);  
9 lambda2=vp/(f2);  
10 disp('metre',lambda1,'Wavelength corresponding to f1  
' ); //displaying wavelengths  
11 disp('metre',lambda2,"Wavelength corresponding to f2  
' ); //displaying wavelengths
```

Scilab code Exa 1.2 Comparing Inductances at different frequencies

```

1 mu0=4*pi*10^-7;
2 a=8*2.54*10^-5; //radius of copper wire
3 sigmac=64.5*10^6; //conductivity of copper
4 l=2*10^-2; //length of wire
5 rdc=1/(%pi*a*a*sigmac);
6 f1=100*10^6;
7 f2=2*10^9;
8 f3=5*10^9;
9 skindepth1=1/sqrt(%pi*mu0*f1*sigmac);
10 skindepth2=1/sqrt(%pi*mu0*f2*sigmac);
11 skindepth3=1/sqrt(%pi*mu0*f3*sigmac);
12 Lin1=(a*rdc)/(2*skindepth1*2*pi*f1); //internal
    inductance
13 Lin2=(a*rdc)/(2*skindepth2*2*pi*f2); //internal
    inductance
14 Lin3=(a*rdc)/(2*skindepth3*2*pi*f3); //internal
    inductance
15 temp=log(2*l/a)/log(%e);
16 Lex=mu0*l*(temp-1)/(2*pi); //external inductance
17 disp("metre",skindepth1,"Skin depth at f1");
18 disp("metre",skindepth2,"Skin depth at f2");
19 disp("metre",skindepth3,"Skin depth at f3");
20 disp("Henry",Lin1,"Internal inductance at f1");
21 disp("Henry",Lin2,"Internal inductance at f2");
22 disp("Henry",Lin3,"Internal inductance at f3");
23 disp("Henry",Lex,"External inductance");

```

Scilab code Exa 1.3 Frequency response of high frequency resistor

```

1 f=10^4:10^5:10^10;
2 w=2*pi.*f;
3 mu0=4*pi*10^-7;
4 l=2*2.5*10^-2;

```

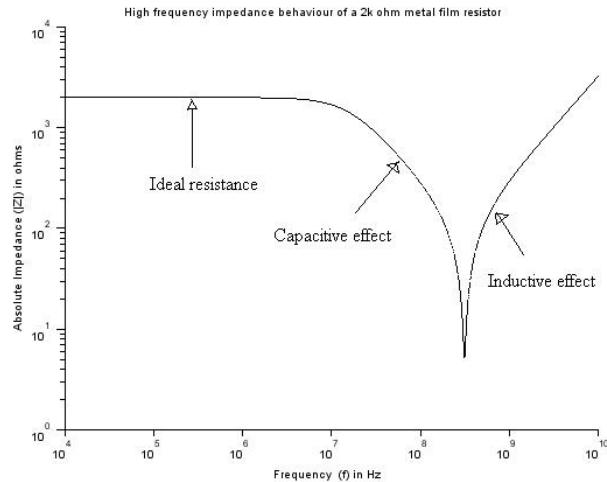


Figure 1.1: Frequency response of high frequency resistor

```

5 a=2.032*10^-4;
6 temp=log(2*pi*a)/log(%e);
7 lex=mu0*1*(temp-1)/(2*pi); // external inductance
8 r=2*10^3; // resistance
9 c=5*10^-12; // capacitance
10 z=w*lex*%i+1 ./(w*c*%i+1/r); //impedance
11 plot2d("gll",f,abs(z));
12 title("High frequency impedance behaviour of a 2k
ohm metal film resistor");
13 xlabel('Frequency (f) in Hz');
14 ylabel('Absolute Impedance (|Z|) in ohms');

```

Scilab code Exa 1.4 Frequency response of high frequency capacitor

```

1 f=10^6:10^7:10^10;
2 rs=(4.8*10^-6).*sqrt(f);

```

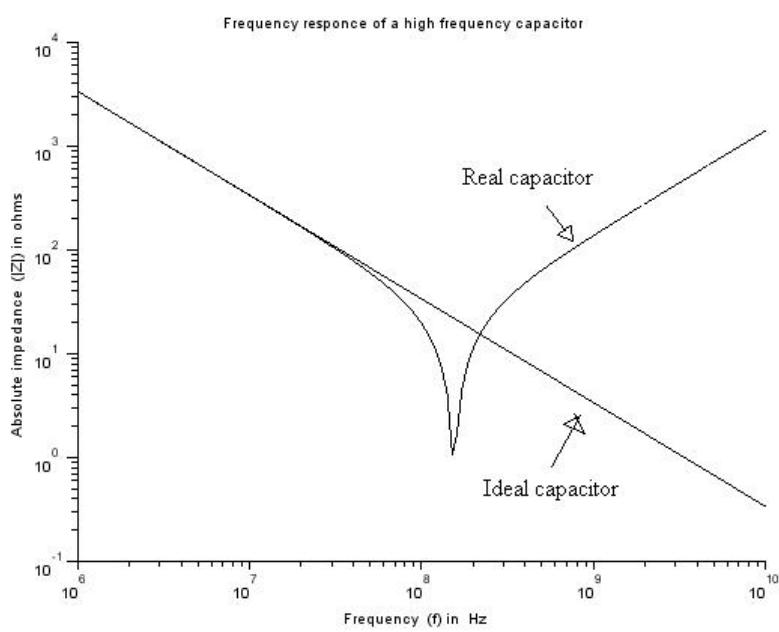


Figure 1.2: Frequency response of high frequency capacitor

```

3 re=(33.9*10^12) ./f;
4 c=47*10^-12;
5 w=2*pi.*f;
6 l=2*1.25*10^-2;
7 a=2.032*10^-4;
8 temp=log(2*l/a)/log(%e);
9 lex=mu0*l*(temp-1)/(2*pi);           // external
                                         inductance
10 z=1 ./(1 ./re +w*c*%i)+rs+w.*lex*%i; // impedance of
                                             frequency dependent capacitor
11 zideal=1 ./(w*c*%i);      //impedance of an ideal
                                         capacitor
12 plot2d("gll",f,abs(z));
13 plot2d(f,abs(zideal));
14 title("Frequency responce of a high frequency
                                         capacitor");
15 xlabel('Frequency (f) in Hz');
16 ylabel('Absolute impedance (|Z|) in ohms');

```

Scilab code Exa 1.5 frequency response of high frequency inductor

```

1 f=10^7:10^8:10^10;
2 w=2*pi.*f;
3 N=3.5;          //number of turns
4 rad=0.05*0.0254;
5 len=0.05*0.0254;        //length of wire
6 a=(5*0.0254*10^-3)/2;
7 u0=4*pi*10^-7;
8 sig_cu=64.516*10^6;
9 e0=8.854*10^-12;
10 l=(pi*rad^2*u0*(N^2))/len;
11 c=(e0*4*pi*rad*(N^2)*a)/len;
12 r=(2*rad*N)/(sig_cu*(a^2));

```

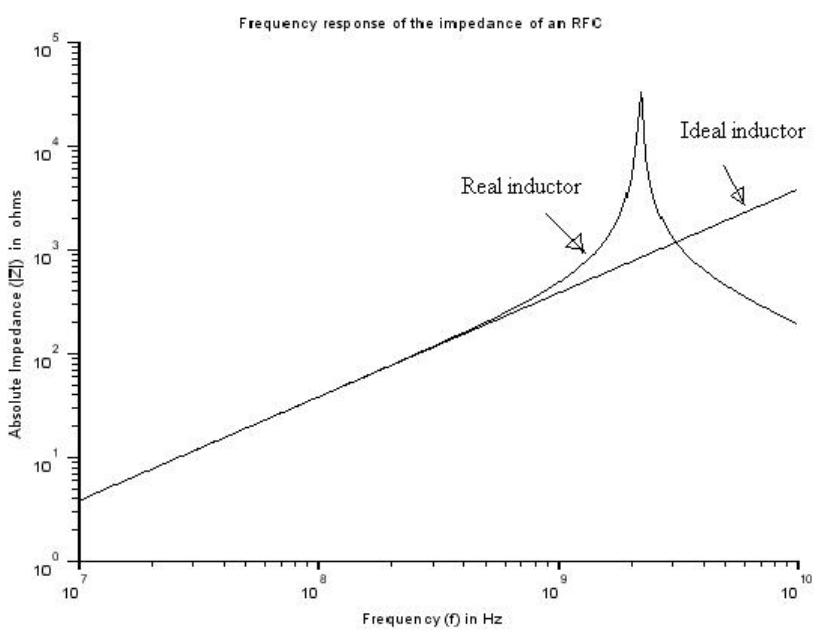


Figure 1.3: frequency response of high frequency inductor

```
13 z=1 ./((1 ./(r+w*i*l))+w*i*c); //impedance
14 zideal=w*i.*l; //impedance of an
    ideal inductor
15 plot2d("gll",f,abs(z));
16 plot2d(f,abs(zideal));
17 title("Frequency response of the impedance of an RFC
    ");
18 xlabel('Frequency (f) in Hz');
19 ylabel('Absolute Impedance (|Z|) in ohms');
```

Chapter 2

Transmission line analysis

Scilab code Exa 2.1 Magnetic field inside and outside infinitely long current carrying wire

```
1 I=5; //current in infinitely long wire
2 a=0.005; //radius of infinitely long wire
3 r_max=10*a;
4 N=100;
5 r=(0:N)/N*r_max;
6 for k=1:N+1
7 if(r(k)<=a)
8 H(k)=I*r(k)/(2*pi*a*a);
9 else
10 H(k)=I/(2*pi*r(k));
11 end;
12 end;
13 plot(r*1000,H);
14 plot([a a]*1000,[0 160], 'r:');
15 title("Magnetic field distribution vs. distance from
the center");
16 xlabel("Distance from the center of the wire ,mm");
17 ylabel("Magnetic field ,A/m");
```

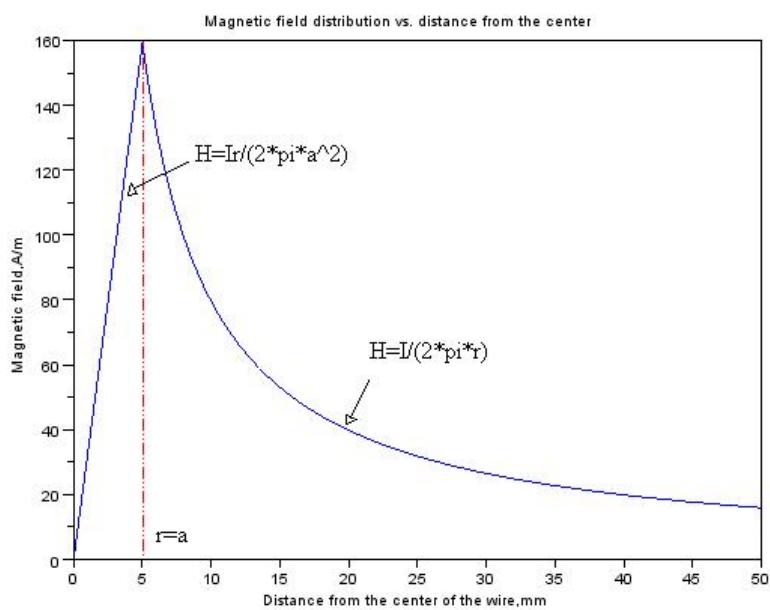


Figure 2.1: Magnetic field inside and outside infinitely long current carrying wire

Scilab code Exa 2.3 Transmission line parameters of a parallel copper plate transmission line

```
1 f=1*10^9;
2 w=6*10^-3; //width
3 d=1*10^-3; //seperation
4 epsilonr=2.25;
5 epsilon0=8.85*10^-12;
6 sigma_diel=0.125;
7 sigma_cond=64.5*10^6;
8 mu0=4*pi*10^-7;
9 skindepth=1/sqrt(pi*sigma_cond*mu0*f);
10 r=2/(w*sigma_cond*skindepth);
11 L=2/(w*sigma_cond*2*pi*f*skindepth);
12 c=epsilon0*epsilon_r*w/d;
13 G=sigma_diel*w/d;
14 disp("R,L,G,C parameters of a parallel copper plate
transmission line ")
15 disp(r,"Resistance in ohm/m");
16 disp(L,"Inductance in Henry/m");
17 disp(c,"Capacitance in Farad/m");
18 disp(G,"Conductance in mS/m");
```

Scilab code Exa 2.5 Phase velocity and Wavelength of PCB material

```
1 epsilonr=4.6;
2 f=2*10^9;
3 z0=50; //line impedance
4 mu0=4*pi*10^-7;
5 epsilon0=8.85*10^-12;
6 zf=sqrt(mu0/epsilon0); //free space impedance
```

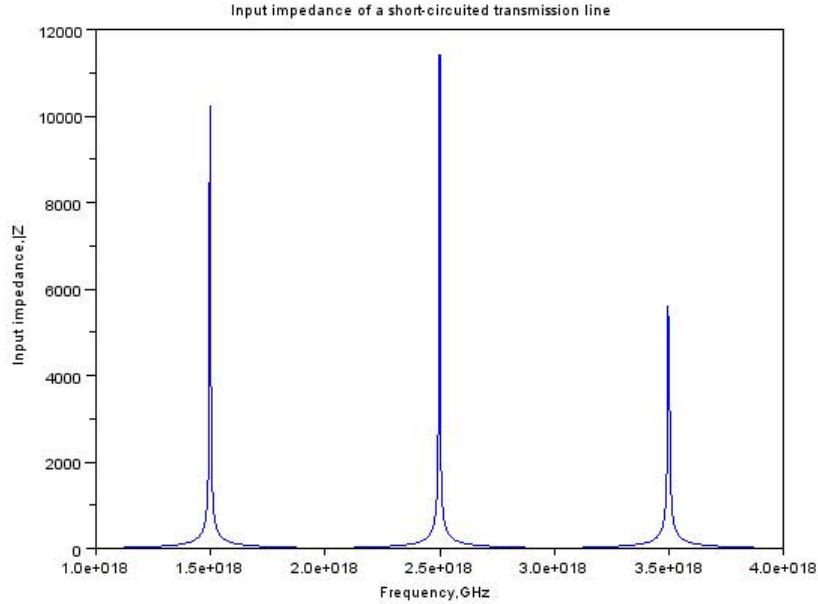


Figure 2.2: Input Impedance for a short circuited transmission line

```

7 temp=((epsilonr-1)/(epsilonr+1))*(0.23+(0.11/
    epsilonr));
8 temp1=2*pi*(z0/zf)*sqrt((epsilonr+1)/2);
9 A=temp+temp1;
10 wtoh=(8*e^A)/((e^2*A)-2);
11 Eff=(epsilonr+1)/2+(epsilonr-1)/2*1/sqrt(1+12*(1/(
    wtoh)));
12 vp=3*10^8/sqrt(Eff);
13 lambda=vp/f;
14 disp("metre/second",vp,"Phase velocity");
15 disp("metre",lambda,"Wavelength");

```

Scilab code Exa 2.6 Input Impedance for a short circuited transmission line

```
1 L=209.4*10^-9; //line inductance in H/m
2 C=119.5*10^-12; //line capacitance in F/m
3 vp=1/sqrt(L*C); // phase velocity
4 Z0=sqrt(L/C); // characteristic line impedance
5 d=0.1; // line length
6 N=500; // number of sampling points
7 f=1*10^9+3*10^9*(0:N)/N; // set frequency range
8 Z=tan(2*pi*f*d/vp); // short circuit impedance
9 plot(f/1*10^9,abs(Z0*Z));
10 title('Input impedance of a short-circuited
    transmission line');
11 xlabel("Frequency ,GHz");
12 ylabel("Input impedance ,|Z|");
```

Scilab code Exa 2.7 Input impedance of open circuited transmission line

```
1 L=209.4*10^-9; //line inductance in H/m
2 C=119.5*10^-12; //line capacitance in F/m
3 vp=1/sqrt(L*C); // phase velocity
4 Z0=sqrt(L/C); // characteristic line impedance
5 d=0.1; // line length
6 N=500; // number of sampling points
7 f=1e9+4e9*(0:N)/N; // set frequency range
8 Z=cotg(2*pi*f*d/vp); // short circuit impedance
9 plot(f/1e9,abs(Z0*Z));
10 title('Input impedance of an open-circuited line');
11 xlabel('Frequency , GHz');
12 ylabel('Input impedance |Z| , {\Omega}')";
```

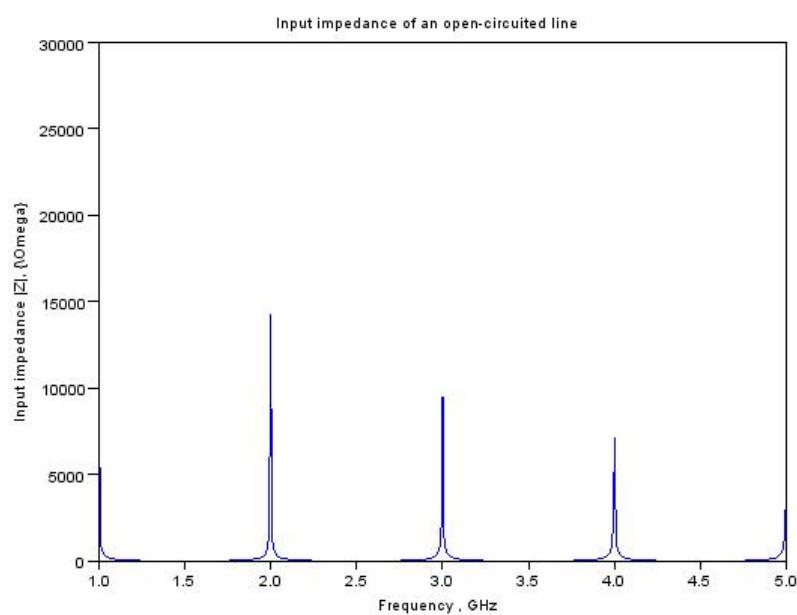


Figure 2.3: Input impedance of open circuited transmission line

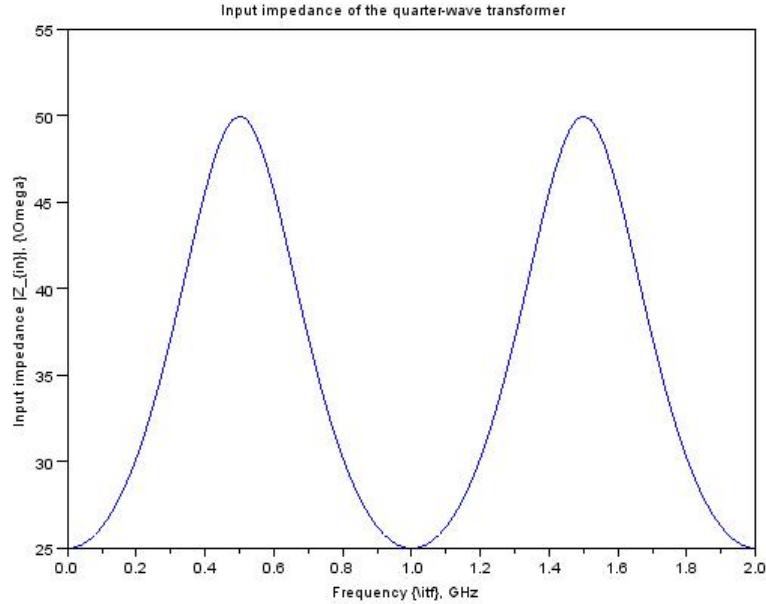


Figure 2.4: Quarter wave parallel plate line transformer

Scilab code Exa 2.8 Quarter wave parallel plate line transformer

```

1 ZL=25; //input impedance
2 Z0=50; //characteristic impedance
3 epsilonnr=4;
4 dp=0.001;
5 f0=500e6;
6 mu0=4*pi*1e-7;
7 epsilon0=8.85e-12;
8 Zline=sqrt(Z0*ZL); //line impedance
9 w=dp/Zline*sqrt(mu0/epsilon0/epsilonnr);

```

```

10 L=mu0*dp/w; //inductance
11 C=epsilon0*epsilon_r*w/dp; //capacitance
12 vp=1/sqrt(L*C); //phase velocity
13 Z0=sqrt(L/C);
14 d=1/(4*f0*sqrt(L*C));
15 N=100;
16 f=2e9*(0:N)/N;
17 betta=2*pi*f/vp;
18 Z=Zline*((ZL+%i*Zline*tan(betta*d))./(Zline+%i*ZL*
tan(betta*d)));
19 plot(f/1e9,real(Z));
20 title('Input impedance of the quarter-wave
transformer');
21 xlabel('Frequency \it{f}, GHz');
22 ylabel('Input impedance |Z_{in}|, {\Omega}');


```

Scilab code Exa 2.9 Power considerations of a transmission line

```

1 Zg=50; //generator impedance
2 Zo=75; //intrinsic impedance
3 Zl=40; //line impedance
4 Vg=5; //generator voltage
5 Ts=(Zg-Zo)/(Zg+Zo); //reflection coefficient at
source
6 To=(Zl-Zo)/(Zl+Zo); //reflection coefficient at load
7 temp=1-(To^2);
8 temp1=(1-Ts)^2;
9 temp2=(1-Ts*To)^2;
10 Pin=((Vg)^2*temp1*temp2)/(8*Zo*temp); //input power
11 Pl=Pin; //power delivered to the load
12 disp("Watts",Pl,"The Power delivered to the load is
same as that at the input-->");


```

Scilab code Exa 2.10 Return Loss of Transmission line section

```
1 RL=20; //load resistance
2 Zo=50; //intrinsic impedance
3 Rin=50; //input resistance
4 Tin=10^(-RL/20); //reflection coefficient at input
5 Rg1=Rin*(1+Tin)/(1-Tin);
6 Rg2=Rin*(1-Tin)/(1+Tin);
7 disp("Ohms",Rg1,"Source resistance for positive Tin=" );
8 disp("Ohms",Rg2,"Source resistance for negative Tin=" );
```

Chapter 3

The Smith Chart

Scilab code Exa 3.2 Input Impedance

```
1 Z1=30+%i*60; //load impedance
2 Z0=50; // intrinsic impedance
3 d=2*10^-2; //length of wire
4 f=2*10^9;
5 c=3*10^8;
6 T0=((Z1-Z0)/(Z1+Z0)); //load reflection coefficient
7 beta=((2*pi*f)/(0.5*c));
8 T=-0.32-%i*0.55;
9 Zin=Z0*((1+T)/(1-T)); //input impedance
10 disp("Ohms",Zin,"Input impedance-->");
```

Scilab code Exa 3.4 SWR circles

```
1 Z0=50; //define 50 Ohm characteristic impedance
2 Z=[50 48.5 75+%i*25 10-%i*5]; //define impedances
   for this example
```

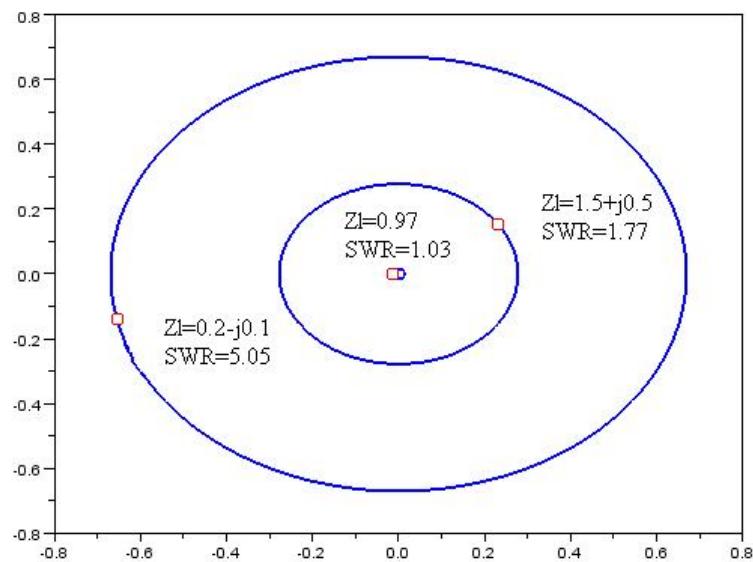


Figure 3.1: SWR circles

```

3 Gamma=(Z-Z0)./(Z+Z0) //compute corresponding
    reflection coefficients
4 SWR=(1+abs(Gamma))./(1-abs(Gamma)); //find the SWRs
5 a=0:0.01:2*pi;
6 for n=1:length(Z)
7
8 plot(abs(Gamma(n))*cos(a),abs(Gamma(n))*sin(a),'b',...
    linewidth',2);
9 plot(real(Gamma(n)), imag(Gamma(n)), 'ro');
10 end;
11
12 for n=1:length(Z)
13     if n~=1
14         end;
15 end;

```

Chapter 4

Single and Multiport Networks

Scilab code Exa 4.3 Internal resistances and current gain of BJT

```
1 hie=5*10^3; //input impedance
2 hre=2*10^-4; //voltage feedback ratio
3 hfe=250; // small signal current gain
4 hoe=20*10^-6; //output admittance
5 rbc=hie/hre; // calculating base-collector
    resistance
6 rbe=hie/(1-hre); // calculating base-emitter
    resistance
7 beta=(hre+hfe)/(1-hre); //c calculating urrent gain
8 rce=hie/(hoe*hie-hre*hfe-hre); //collector-emitter
    resistance
9 disp("Ohms",rbc,"base collector resistance");
10 disp("Ohms",rbe,"base emitter resistance");
11 disp("Ohms",rce,"collector emitter resistance");
12 disp(beta,"current gain");
```

Scilab code Exa 4.7 S parameters and resistive elements of T network

```
1 Zin=50; //input impedance
2 Z0=50;
3 // defining scattering parameters
4 S11=0;
5 S22=0;
6 S21=1/sqrt(2);
7 S12=1/sqrt(2);
8 R1=((sqrt(2)-1)/(sqrt(2)+1))*Z0;
9 R2=R1;
10 R3=2*sqrt(2)*Z0;
11 disp(S21,S12,S22,S11," Scattering parameters");
12 disp("Ohms",R3,"Ohms",R2,"Ohms",R1," Resistance
      values R1,R2,R3:");
```

Chapter 5

An Overview of RF Filter Design

Scilab code Exa 5.1 Resonance frequency of a Bandpass filter

```
1 stacksize('max');
2 C=2*10^-12;
3 L=5*10^-9;
4 R=20;
5 Z0=50;
6 //f=[10^7:10^8:10^11];
7 //define frequency range
8 f_min=10e6; //lower frequency limit
9 f_max=100e9; // upper frequency limit
10 N=100; // number of points in the graph
11 f=f_min*((f_max/f_min).^(0:N)/N)); // compute
    frequency points on log scale
12 w=2*pi.*f;
13 A=(w.*w*L*C-1)/(w*C);
14 S21=2*Z0./(2*Z0+R+%i*A);
15 f0=1./(2*pi*sqrt(L*C));
16 disp("Hertz",f0,"Resonance frequency");
```

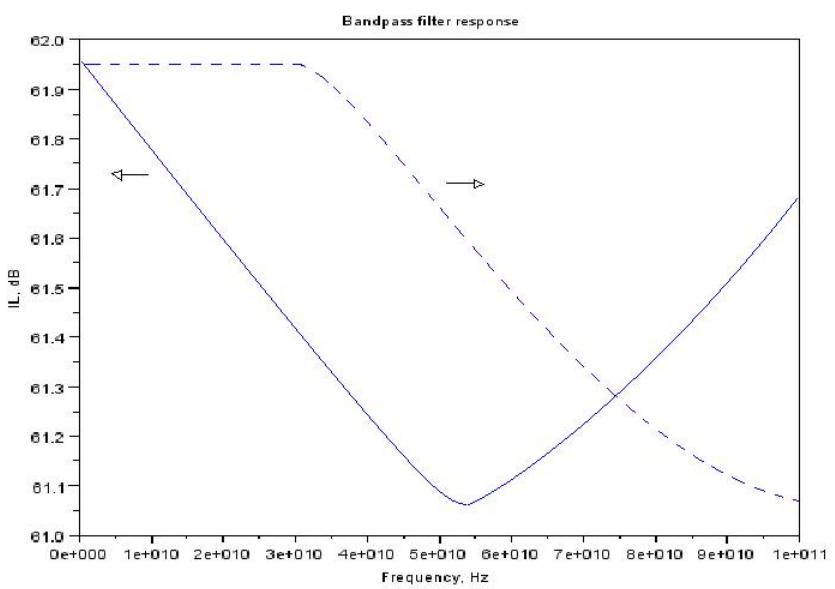


Figure 5.1: Resonance frequency of a Bandpass filter

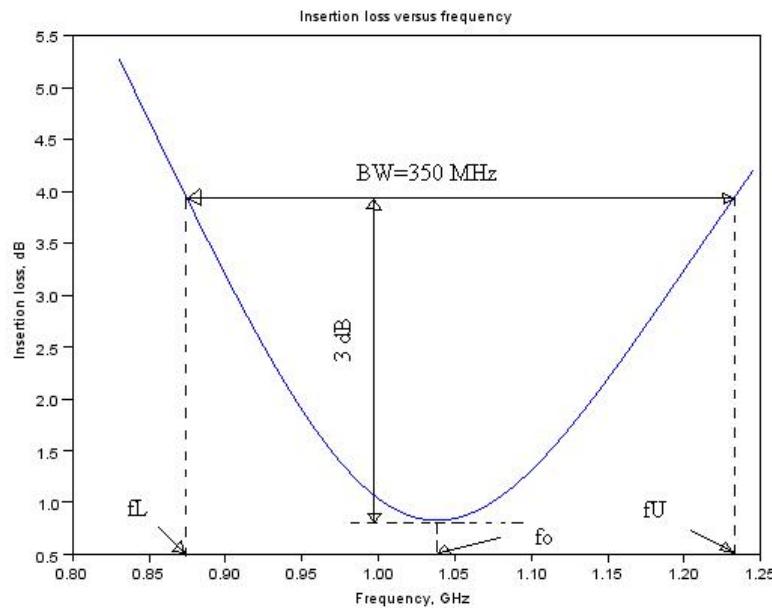


Figure 5.2: Quality factors of a filter

Scilab code Exa 5.2 Quality factors of a filter

```

1 // define problem parameters
2
3 Z0=50; //characteristic line impedance
4 ZG=50; //source impedance
5 ZL=50; //load impedance
6
7 //series RLC filter parameters
8 R=10;

```

```

9 L=50e-9;
10 C=0.47e-12;
11
12 VG=5; //generator voltage
13
14 //compute series resonance frequency
15 w0=1/sqrt(L*C);
16 f0=w0/(2*pi);
17
18 //define a frequency range
19 delta=0.2;
20 w=((1-delta):2*delta/1000:(1+delta))*w0;
21
22 //compute quality factors
23 Q_LD=w0*L/(R+2*ZL) //loaded quality factor
24 Q_F=w0*L/R //filter quality factor
25 Q_E=w0*L/(2*ZL) //external quality factor
26
27 // compute Bandwidth
28 BW=f0/Q_LD
29
30 //compute input and load power
31 P_in=VG^2/(8*Z0)
32 P_L=P_in*Q_LD^2/Q_E^2
33
34 //compute insertion loss and load factor
35 epsilon=w/w0-w0./w;
36 LF=(1+epsilon.^2*Q_LD.^2)/(1-Q_LD/Q_F).^2;
37 IL=10*log10(LF);
38
39 disp(Q_LD,"Loaded Quality Factor");
40 disp(Q_F,"Filter Quality Factor");
41 disp(Q_E,"External Quality Factor");
42 disp("Watts",P_in,"Input Power");
43 disp("Watts",P_L,"Power delivered to the load");
44 disp("Hertz",f0,"resonance frequency of the filter")
        ;
45 disp("Hertz",BW,"Bandwidth of the filter");

```

```
46 plot(w/2/%pi/1e9, IL);
47 title('Insertion loss versus frequency');
48 xlabel('Frequency , GHz');
49 ylabel('Insertion loss , dB');
```

Chapter 6

Active RF Components

Scilab code Exa 6.1 Conductivity of Si and Ge and GaAs

```
1 // define physical constants
2 q=1.60218e-19;
3 k=1.38066e-23;
4
5 // define material properties
6 Nc_300=[1.04e19 2.8e19 4.7e17];
7 Nv_300=[6e18 1.04e19 7e18];
8 mu_n=[3900 1500 8500];
9 mu_p=[1900 450 400];
10 Wg=[0.66 1.12 1.424];
11
12 T0=273;
13 T=-50:250; // temperature range in centigrade
14
15 sigma=zeros([3 length(T)]);
16
17 for s=1:3 //loop through all semi conductor
18     materials
19         Nc=Nc_300(s)*((T+T0)/300).^(3/2);
```

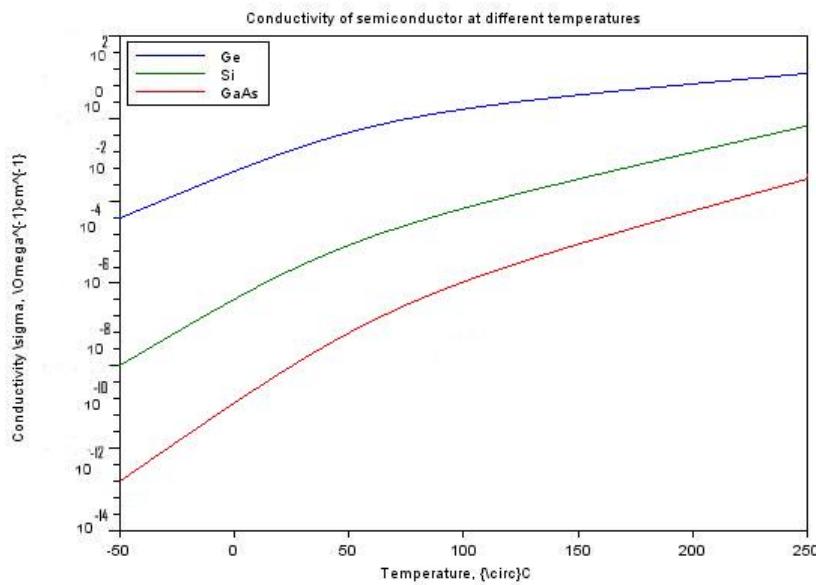


Figure 6.1: Conductivity of Si and Ge and GaAs

```

19 Nv=Nv_300(s)*((T+T0)/300).^(3/2);
20 sigma=[q*sqrt(Nc.*Nv).*(exp(-Wg(s)./(2*k*(T+T0)/q)))
21 *(mu_n(s)+mu_p(s))];
22 end;
23 plot(T,sigma(1),T,sigma(2),T,sigma(3));
24 legend('Ge','Si','GaAs',2);
25 title('Conductivity of semiconductor at different
26 temperatures');
27 xlabel('Temperature , {\circ}C');
28 ylabel('Conductivity \sigma , \Omega^{-1}cm^{-1}');

```

Scilab code Exa 6.2 Barrier Voltage of a pn Junction

```

1 // doping concentrations
2 Na=1*10^18;
3 Nd=5*10^15;
4 //intrinsic concentrations
5 ni=1.5*10^10;
6 T=300;
7 term=(Na*Nd)/(ni*ni);
8 k=1.38*10^-23;
9 q=1.6*10^-19;
10 Vdiff=(k*T)*log(term)/q;
11 disp("Volts",Vdiff,"Barrier voltage");

```

Scilab code Exa 6.3 Depletion Layer Capacitance of a pn Junction

```

1 //define problem parameters
2

```

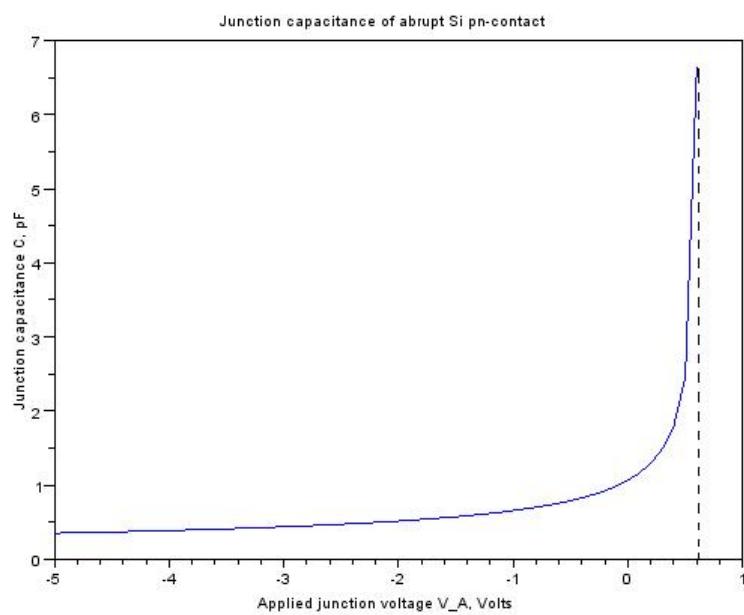


Figure 6.2: Depletion Layer Capacitance of a pn Junction

```

3 ni=1.5e10*1e6; //intrinsic carrier concentration in
5   Si [m^(-3)]
4 Na=1e15*1e6; //acceptor doping concentration [m^(-3)]
6   ]
5 Nd=5e15*1e6; //donor concentration [m^(-3)]
6 A=1e-4*1e-4; //cross sectional area [m^2]
7 eps_r=11.9; //cross sectional area [m^2]
8
9 //define physical constants (SI units)
10 q=1.60218e-19; //electron charge
11 k=1.38066e-23; //Boltzmann's constant
12 eps0=8.85e-12; //permittivity of free space
13
14 eps=eps_r*eps0;
15
16 T=300; //temperatuure
17
18 //compute diffusion barrier voltage
19 Vdiff=k*T/q*log(Na*Nd/ni^2)
20
21 //junction capacitance at zero applied voltage
22 C0=A*sqrt(q*eps/(1/Na+1/Nd)/2/Vdiff)
23
24 //extents of the space charge region
25 dn=sqrt(2*eps*Vdiff/q*Na/Nd/(Na+Nd));
26 dp=sqrt(2*eps*Vdiff/q*Nd/Na/(Na+Nd));
27
28 //define range for applied voltage
29 VA=-5:0.1:Vdiff;
30
31 //compute junction capacitance
32 C=C0*(1-VA/Vdiff).^( -1/2 );
33
34 plot(VA,C/1e-12);
35 title('Junction capacitance of abrupt Si pn-contact',
      );
36 xlabel('Applied junction voltage V_A, Volts');
37 ylabel('Junction capacitance C, pF');

```

Scilab code Exa 6.4 Parameters of a Schottky diode

```
1 //doping concentrations
2 Nc=2.8*10^19;
3 Nd=1*10^16;
4 term=Nc/Nd;
5 k=1.38*10^-23; //Boltzman's constant
6 q=1.6*10^-19; //charge
7 Vc=(k*T)*log(term)/q;
8Vm=5.1; //workfunction
9 X=4.05; //affinity
10 Vd=(Vm-X)-Vc; //Barrier Voltage
11 Epsilon=11.9*8.854*10^-12;
12 ds=sqrt((2*Epsilon*Vd)/(q*Nd));
13 A=1*10^-4; //cross-sectional area
14 Cj=(A*Epsilon)/(ds); //junction capacitance
15 disp("Volts",Vc,"Conduction Band potential");
16 disp("Volts",Vd,"Built in Barrier Voltage");
17 disp("metre",ds,"Space Charge Width");
18 disp("Farads",Cj,"Junction Capacitance");
```

Scilab code Exa 6.7 Maximum forward current gain of bipolar junction transistor

```
1 Ndemitter=1*10^19; // donor concentration in emitter
2 Nabase=1*10^17; //acceptor concentration in base
3 de=0.8*10^-6; //spatial extent of the emitter
4 db=1.2*10^-6; //spatial extent of the base
5 alpha=2.8125;
6 beta=(alpha*Ndemitter*de)/(Nabase*db);
7 disp(beta,"Maximum forward current gain");
```

Scilab code Exa 6.8 Thermal analysis involving a BJT mounted on a heat sink

```
1 Tj=150;
2 Ts=25;
3 Pw=15;
4 Rthjs=(Tj-Ts)/Pw; //Junction-to-solder point
    resistance
5 Rthca=2;
6 Rthhs=10;
7 Ta=60;
8 Rhttot=Rthjs+Rthca+Rthhs; //total thermal resistance
9 Pth=(Tj-Ta)/(Rhttot); //dissipated power
10 disp("Watts",Pth,"Maximum dissipated power");
```

Scilab code Exa 6.9 Drain saturation current in a MESFET

```
1 //define problem parameters
2 Nd=1e16*1e6;
3 d=0.75e-6;
4 W=10e-6;
5 L=2e-6;
6 eps_r=12;
7 Vd=0.8;
8 mu_n=8500e-4;
9 Vgs=0:-0.01:-4;
10
11 //define physical constants
12 q=1.60218e-19;// electron charge
13 eps0=8.85e-12;// permittivity of free space
```

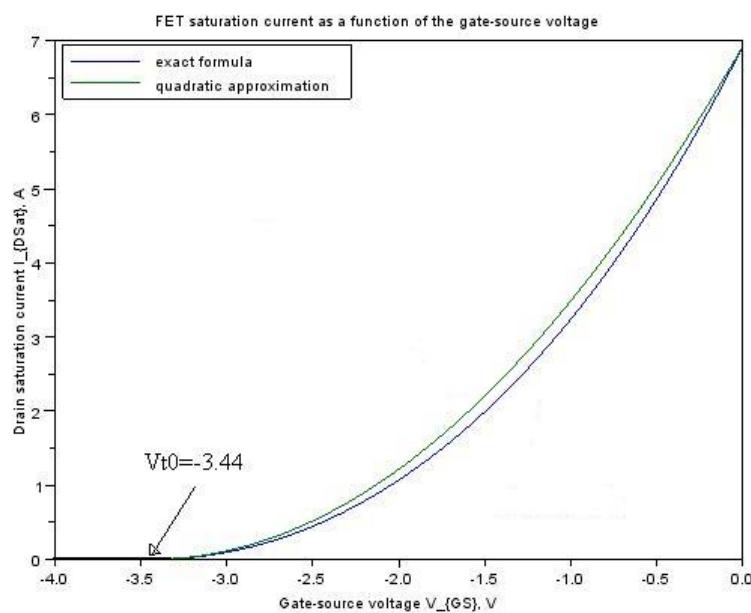


Figure 6.3: Drain saturation current in a MESFET

```

14
15 eps=eps_r*eps0;
16
17 //pinch-off voltage
18 Vp=q*Nd*d^2/(2*eps)
19
20 //threshold voltage
21 Vt0=Vd-Vp
22
23 //conductivity of the channel
24 sigma=q*mu_n*Nd
25
26 //Channel conductance
27 G0=q*sigma*Nd*W*d/L
28
29 //saturation current using the exact formula
30 Id_sat=G0*(Vp/3-(Vd-Vgs)+2/(3*sqrt(Vp))*(Vd-Vgs)
   .^(3/2)).*(1-(Vgs<Vt0));
31 Idss=Id_sat(1)
32
33 //saturation current using the quadratic law
   approximation
34 Id_sat_square=Idss*(1-Vgs/Vt0)^2;
35
36 plot(Vgs,Id_sat,Vgs,Id_sat_square);
37 legend('exact formula', 'quadratic approximation',2)
   ;
38 title('FET saturation current as a function of the
   gate-source voltage');
39 xlabel('Gate-source voltage V_{GS}, V');
40 ylabel('Drain saturation current I_{DSat}, A');

```

Scilab code Exa 6.10 Current Voltage characterisites of a MESFET

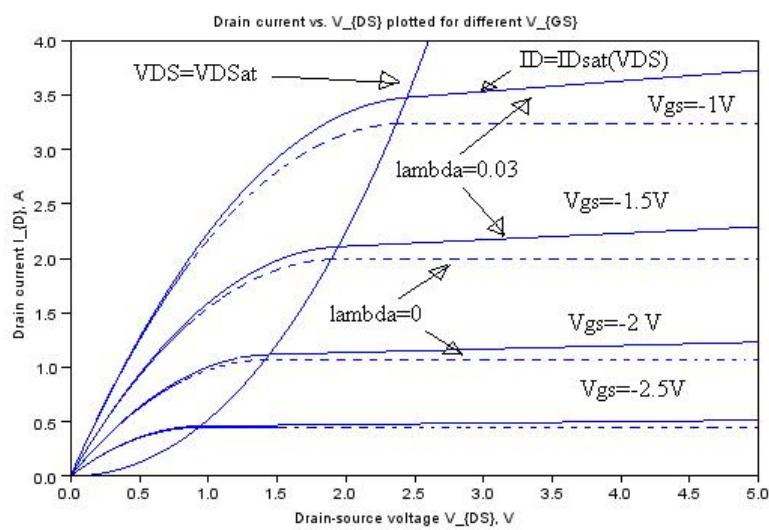


Figure 6.4: Current Voltage characterisitcs of a MESFET

```

1 // define problem parameters
2 Nd=1e16*1e6;
3 d=0.75e-6;
4 W=10e-6;
5 L=2e-6;
6 eps_r=12;
7 Vd=0.8;
8 mu_n=8500*1e-4;
9 lambda=0.03;
10
11 // define physical constants
12 q=1.60218e-19; //electron charge
13 eps0=8.85e-12; //permittivity of free space
14
15 eps=eps_r*eps0;
16
17 // pinch-off voltage
18 Vp=q*Nd*d^2/(2*eps)
19
20 // threshold voltage
21 Vt0=Vd-Vp
22
23 // conductivity of the channel
24 sigma=q*mu_n*Nd
25
26 //channel conductance
27 G0=q*sigma*Nd*W*d/L
28
29 //define the range for gate source voltage
30 Vgs_min=-2.5;
31 Vgs_max=-1;
32 Vgs=Vgs_max:-0.5:Vgs_min;
33
34 //drain source voltage
35 Vds=0:0.01:5;
36
37 //compute drain saturation voltage
38 Vds_sat=Vgs-Vt0;

```

```

39
40 // first the drain current is taken into account the
   channel length modulation
41 for n=1:length(Vgs)
42   if Vgs(n)>Vt0
43     Id_sat=G0*(Vp/3-(Vd-Vgs(n))+2/(3*sqrt(Vp))*(Vd
       -Vgs(n))^(3/2));
44   else
45     Id_sat=0;
46   end;
47
48   Id_linear=G0*(Vds-2/(3*sqrt(Vp)).*((Vds+Vd-Vgs(n))
       .^(3/2)-(Vd-Vgs(n))^(3/2))).*(1+lambda*Vds);
49   Id_saturation=Id_sat*(1+lambda*Vds);
50   Id=Id_linear.*((Vds<=Vds_sat(n))+Id_saturation.*(
       Vds>Vds_sat(n));
51   plot(Vds,Id);
52 set(gca(),"auto_clear","off");
53 end;
54
55 //next the channel length modulation is not taken
   into account
56 for n=1:length(Vgs)
57   if Vgs(n)>Vt0
58     Id_sat=G0*(Vp/3-(Vd-Vgs(n))+2/(3*sqrt(Vp))*(Vd
       -Vgs(n))^(3/2));
59   else
60     Id_sat=0;
61   end;
62
63   Id_linear=G0*(Vds-2/(3*sqrt(Vp)).*((Vds+Vd-Vgs(n))
       .^(3/2)-(Vd-Vgs(n))^(3/2)));
64   Id_saturation=Id_sat;
65   Id=Id_linear.*((Vds<=Vds_sat(n))+Id_saturation.*(
       Vds>Vds_sat(n));
66   plot(Vds, Id);
67 end;
68

```

```

69 // computation of drain saturation current
70
71 Vgs=0:-0.01:-4;
72 Vds_sat=Vgs-Vt0;
73
74 Id_sat=G0*(Vp/3-(Vd-Vgs)+2/(3*sqrt(Vp))*(Vd-Vgs)
75 .^(3/2)).*(1+lambda*Vds_sat).*(1-(Vgs<Vt0));
76 plot(Vds_sat, Id_sat);
77
78 mtlb_axis([0 5 0 4]);
79 title('Drain current vs. V_{DS} plotted for
80 different V_{GS}');
81 xlabel('Drain-source voltage V_{DS}, V');
82 ylabel('Drain current I_{D}, A');

```

Scilab code Exa 6.11 Computation of HEMT related electric characteristics

```

1 // define problem parameters
2 Nd=1e18*1e6;
3 Vb=0.81;
4 eps_r=12.5;
5 d=50e-9;
6 dWc=3.5e-20;
7 W=10e-6;
8 L=0.5e-6;
9 mu_n=8500*1e-4;
10
11 // define physical constants
12 q=1.60218e-19; //electron charge
13 eps0=8.85e-12; //permittivity of free space
14

```

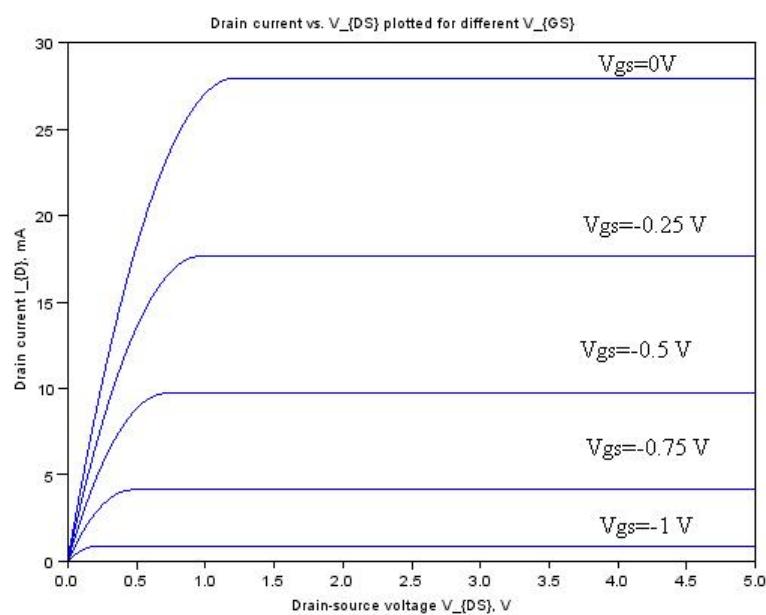


Figure 6.5: Computation of HEMT related electric characteristics

```

15 eps=eps_r*eps0;
16
17 //pinch-off voltage
18 Vp=q*Nd*d^2/(2*eps)
19
20 //threshold voltage
21 Vth=Vb-dWc/q-Vp
22
23 //drain-source applied voltage range
24 Vds=0:0.01:5;
25
26 //gate-source voltages
27 Vgs_r=-1:0.25:0;
28
29
30
31
32 for n=1:length(Vgs_r)
33     Vgs=Vgs_r(n);
34     Id=mu_n*W*eps/(L*d)*((Vds*(Vgs-Vth)-Vds.*Vds/2)
35         .* (1-(Vds>(Vgs-Vth)))+1/2*(Vgs-Vth)^2*(1-(Vds
36         <=(Vgs-Vth))));
37 plot(Vds,Id/1e-3);
38     set(gca(),"auto_clear","off");
39 end;
40
41 title('Drain current vs. V_{DS} plotted for
42 different V_{GS}');
43 xlabel('Drain-source voltage V_{DS}, V');
44 ylabel('Drain current I_{D}, mA');

```

Chapter 7

Active RF Component Modelling

Scilab code Exa 7.1 Small signal pn diode model

```
1 //define problem parameters
2 TT=500e-12; // transit time
3 T0=300; //temperature
4 Is0=5e-15; // reverse saturation current at 300K
5 Rs=1.5; // series resistance
6 nn=1.16; //emission coefficient
7
8 // parameters needed to describe temperature
// behavior of
9 // the band-gap energy in Si
10 alpha=7.02e-4;
11 beta=1108;
12 Wg0=1.16;
13 pt=3;
14
15 // quiescent current
16 Iq=50e-3;
```

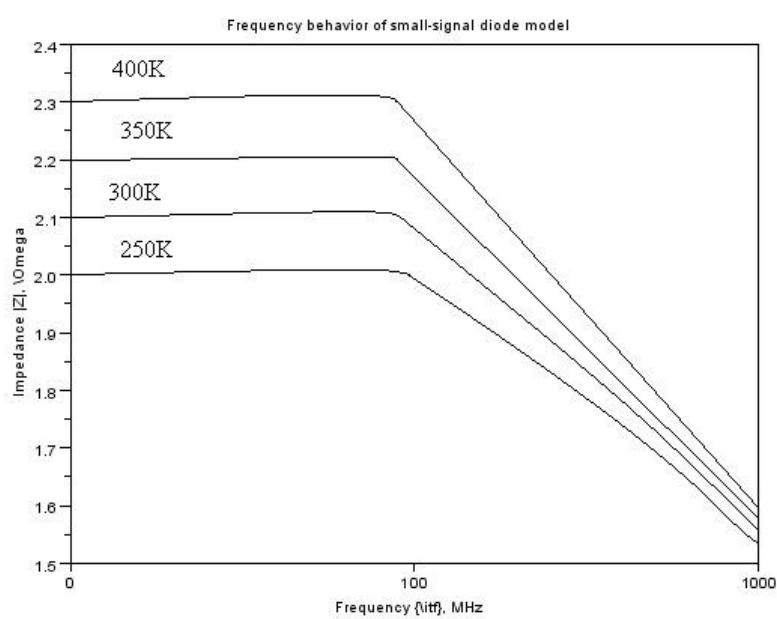


Figure 7.1: Small signal pn diode model

```

17
18 // frequency range 10MHz to 1GHz
19 f_min=10e6; // lower limit
20 f_max=1e9; //upper limit
21 N=300; // number of points in the graph
22 f=f_min*((f_max/f_min).^(0:N)/N)); // compute
   frequency points on log scale
23
24 // temperatures for which analysis will be performed
25 T_points=[250 300 350 400];
26
27 // define physical constants
28 q=1.60218e-19; // electron charge
29 k=1.38066e-23; // Boltzmann's constant
30
31 for n=1:length(T_points)
32     T=T_points(n);
33     s=sprintf('T=%f\n',T);
34     Vt=k*T/q;
35
36     Wg=Wg0-alpha*T^2/(beta+T);
37     s=sprintf('%s    Wg(T)=%f\n',s,Wg);
38
39     Is=Is0*(T/T0)^(pt/n)*exp(-Wg/Vt*(1-T/T0));
40     s=sprintf('%s    Is(T)=%e\n',s,Is);
41
42     Vq=nn*Vt*log(1+Iq/Is);
43     s=sprintf('%s    Vq(T)=%f\n',s,Vq);
44
45     Rd=nn*Vt/Iq;
46     s=sprintf('%s    Rd(T)=%f\n',s,Rd);
47
48     Cd=Is*TT/nn/Vt*exp(Vq/nn/Vt);
49     s=sprintf('%s    Cd(T)=%fpF\n',s,Cd/1e-12)
50
51     Zc=1./(%i*2*pi*f*Cd);
52
53     Zin=Rs+Rd*Zc./(Rd+Zc);

```

```

54
55 plot(f/1e6,abs(Zin));
56 set(gca(),"auto_clear","off");
57 end;
58
59 title('Frequency behavior of small-signal diode
       model');
60 xlabel('Frequency {\it f}, MHz');
61 ylabel('Impedance |Z|, \Omega');

```

Scilab code Exa 7.4 Parameters of BJT

```

1 // first we define all parameters for the transistor
   and the circuit
2 Z0=50; //characteristic imedance of the system
3
4 Vcc=3.6; //power supply voltage
5 Vce=2; //collector voltage
6 Ic=10e-3; //collector current
7
8 T=300; //ambient temperature (300K)
9
10 //transistor parameters (they are very similar to
    BFG403W)
11 beta=145; // current gain
12 Is=5.5e-18; // saturation current
13 VAN= 30; // forward Early voltage
14 tau_f=4e-12; // forward transition time
15 rb=125; // base resistance
16 rc=15; // collector resistance
17 re=1.5; // emitter resistance
18 Lb=1.1e-9; // base inductance
19 Lc=1.1e-9; // collector inductance
20 Le=0.5e-9; // emitter inductance
21 Cjc=16e-15; // collector junction capacitance at

```

```

        zero applied voltage
22 mc=0.2;      // collector junction grading
               coefficient
23 Cje=37e-15; // emitter junction capacitance at zero
               applied voltage
24 me=0.35;     // emitter junction grading coefficient
25 phi_be=0.9;  // base-emitter diffusion potential
26 phi_bc=0.6;  // base-collector diffusion potential
27 Vbe=phi_be; // base-emitter voltage
28
29 // some physical constants
30 k=1.38e-23;  // Boltzmann's constant
31 q=1.6e-19;   // elementary charge
32 VT=k*T/q;    // thermal potential
33
34 disp('DC biasing parameters');
35
36 Ib=Ic/beta;
37 disp("Amperes", Ib, "Base current");
38
39 Rc=(Vcc-Vce)/Ic;
40 disp("Ohms", Rc, "Collector resistance");
41
42 Rb=(Vcc-Vbe)/Ib;
43 disp("Ohms", Rb, "Base resistance");
44
45
46 r_pi=VT/Ib;
47 disp("Ohms", r_pi, "Rpi");
48
49 r0=VAN/Ic;
50 disp("Ohms", r0, "R0");
51
52 gm=beta/r_pi;
53 disp("Mho", gm, "Gm");
54
55 Vbc=Vbe-Vce;
56 Cmu=Cjc*(1-Vbc/phi_bc)^(-mc);

```

```

57 disp("Farads",Cmu,"base collector capacitance");
58
59 if(Vbe<0.5*phi_be)
60     Cpi_junct=Cje*(1-Vbe/phi_be)^(-me);
61 else
62     C_middle=Cje*0.5^(-me);
63     k_middle=1-0.5*me;
64     Cpi_junct=C_middle*(k_middle+me*Vbe/phi_be);
65 end;
66
67 disp("Farads",Cpi_junct,"Junction Capacitance");
68
69 Cpi_diff=Is*tau_f/VT*exp(Vbe/VT);
70 disp("Farads",Cpi_diff,"Differential capacitance");
71
72 Cpi=Cpi_junct+Cpi_diff;
73 disp("Farads",Cpi,"Total Capacitance");
74
75 C_miller=Cmu*(1+gm*r_pi/(r_pi+rb)*Z0*r0/(r0+rc+Z0));
76 disp("Farads",C_miller,"Miller Capacitance");
77
78 C_input=Cpi+C_miller;
79 disp("Farads",C_input,"Total input capacitance");

```

Scilab code Exa 7.5 Cutoff frequency of GaAs MESFET

```

1 l=1*10^-6; //length
2 w=200*10^-6; //width
3 d=0.5*10^-6; //depth
4 E0=8.854*10^-12;
5 Er=13.1;
6 q=1.6*10^-19; //electron charge
7 Nd=1*10^16; //doping concentration
8 mun=8500;
9 Vp=(q*Nd*d^2)/(2*Er*E0);

```

```
10 G0=(q*mun*Nd*w)/l;
11 gm=0.0358;
12 Cap=(E0*Er*w*l)/d;
13 fT=gm/(2*pi*Cap);
14 disp("Hertz",fT,"Cut off frequency");
```

Scilab code Exa 7.6 Small signal Hybrid pi parameters without Miller Effect

```
1 Icq=6*10^-3;
2 Ibq=40*10^-6;
3 Van=30; //Early voltage
4 q=1.6*10^-19;
5 k=1.38*10^-23;
6 T=300;
7 fT=37*10^9; //Transition frequency
8 gm=(Icq*q)/(k*T);
9 beta0=Icq/Ibq;
10 r0=Van/Icq;
11 rpi=beta0/gm;
12 Cpi=(beta0)/(2*pi*fT*rpi);
13 disp("Hybrid pi parametrs without Miller effect");
14 disp("Mho",gm,"gm");
15 disp("Ohms",rpi,"Rpi");
16 disp("Farads",Cpi,"Cpi");
17 disp("Ohms",r0,"R0");
18 disp(beta0,"Beta0");
```

Chapter 8

Matching and biasing networks

Scilab code Exa 8.11 Efficiency of different types of amplifiers

```
1 theta=(1:1:360)/180*pi; //define conduction angle
2
3 //compute efficiency
4 nu=-1/2*(theta-sin(theta))./(theta.*cos(theta/2)-2*
    sin(theta/2));
5
6 plot(theta/%pi*180,nu*100,'r','linewidth',2);
7 set(gca(),"auto_clear","off");
8 plot([0 180],[%pi/4*100 %pi/4*100],'b:');
9 plot([180 180],[0 %pi/4*100],'b:');
10 plot(180,%pi/4*100,'bo');
11 plot(360,50,'bo');
12 mtlb_axis([0 360 50 100]);
13 title('Maximum theoretical efficiency of the
    amplifier');
14 xlabel('Conduction angle \Theta_0 , deg.');
15 ylabel('Efficiency \eta , %');
```

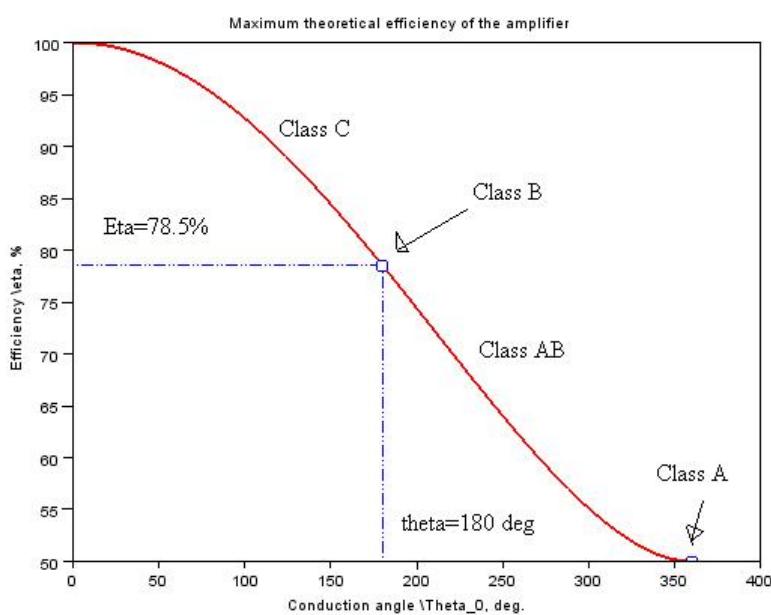


Figure 8.1: Efficiency of different types of amplifiers

Scilab code Exa 8.12 Design of passive biasing networks for a BJT in CE config

```
1 Ic=10*10^-3; // Collector current
2 Vce=3;
3 Vcc=5;
4 beta=100; //current gain
5 Vbe=0.8;
6 I1=Ic+Ic/beta;
7 R1=(Vcc-Vce)/I1;
8 R2=(Vce-Vbe)/(Ic/beta);
9 Vx=1.5;
10 R3=(Vx-Vbe)/(Ic/beta);
11 Ix=10*(Ic/beta);
12 R11=(Vx/Ix);
13 R22=(Vcc-Vx)/(Ix+(Ic/beta));
14 R4=(Vcc-Vce)/Ic;
15 disp("Amperes",I1,"I1","Ohms",R1,"R1","Ohms",R2,"R2",
      "Ohms",R3,"R3","Ohms",R11,"R11","Ohms",R22,"R22",
      "Ohms",R4,"R4");
```

Chapter 9

RF Transistor Amplifier Design

Scilab code Exa 9.1 Power relations for an RF amplifier

```
1 // defining scattering parameters
2 S11=0.102-%i*0.281;
3 S21=0.305+%i*3.486;
4 S12=0.196-%i*0.03471;
5 S22=0.2828-%i*0.2828;
6
7 Vs=5;
8 Zs=40;
9 Zl=73;
10 Z0=50;
11
12 Ts=(Zs-Z0)/(Zs+Z0);
13 Tl=(Zl-Z0)/(Zl+Z0);
14 Tin=S11+(S21*S12*Tl)/(1-S22*Tl);
15 Tout=S22+(S12*S21*Ts)/(1-S11*Ts);
16
17 a=S21^2;
18 b=1-Ts^2;
19 c=1-Tl^2;
20
21 Gt=(c*a*b)/((1-Tl*Tout)^2*(1-S11*Ts)^2);
```

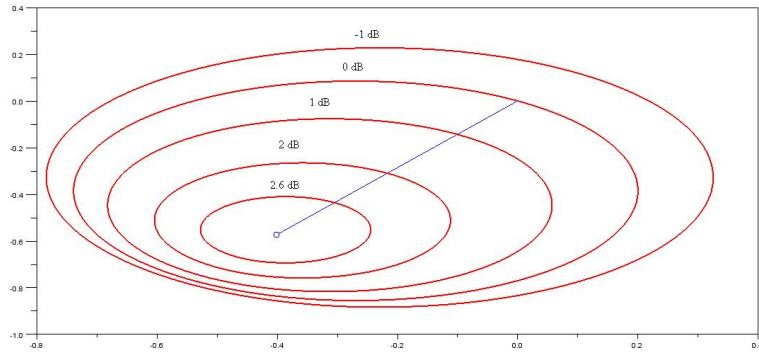


Figure 9.1: Computation of source gain circles for a unilateral design

```

22 Gtu=(c*a*b)/((1-Tl*S22)^2*(1-S11*Ts)^2);
23 Ga=(a*b)/((1-Tout)^2*(1-S11*Ts)^2);
24 G=(a*c)/((1-Tin)^2*(1-S22*Tl)^2);
25
26 d=abs(Gt);
27
28 Pin=(Z0*(Vs)^2)/((Zs+Z0)^2*(1-Tin*Ts)^2*2);
29 pinR=real(Pin);
30 pinI=imag(Pin);
31 Pinc=sqrt(pinR^2+pinI^2);
32 PA=78.1*10^-3;
33 P1=PA*d;
34 disp(P1,"Power delivered to load in watts");

```

Scilab code Exa 9.7 Computation of source gain circles for a unilateral design

```

1 //define s11 parameter of the transistor
2 s11=0.7*exp(%i*(125)/180*pi);

```

```

3
4 //compute the maximum gain achievable by the input
   matching network
5 Gs_max=1/(1-abs(s11)^2);
6 Gs_max_dB=10*log10(Gs_max)
7
8 //find the reflection coefficient for the maximum
   gain
9 Gs_opt=conj(s11);
10
11 //draw a straight line connecting Gs-opt and the
   origin
12 set(gca(),"auto_clear","off");
13 plot([0 real(Gs_opt)],[0 imag(Gs_opt)],'b');
14 plot(real(Gs_opt),imag(Gs_opt),'bo');
15
16 //specify the angle for the constant gain circles
17 a=(0:360)/180*pi;
18
19 //plot source gain circles
20 gs_db=[-1 0 1 2 2.6];
21 gs=exp(gs_db/10*log(10))/Gs_max;
22
23 for n=1:length(gs)
24     dg=gs(n)*conj(s11)/(1-abs(s11)^2*(1-gs(n)));
25     rg=sqrt(1-gs(n))*(1-abs(s11)^2)/(1-abs(s11)^2*(1-
           gs(n)));
26     plot(real(dg)+rg*cos(a),imag(dg)+rg*sin(a),'r',
           linewidth',2);
27 end;

```

Scilab code Exa 9.8 Design of 18 dB single stage MESFET amplifier

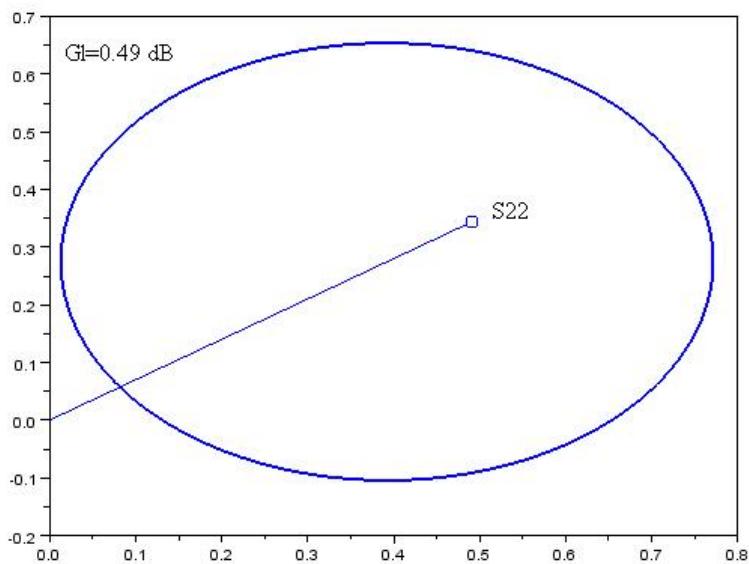


Figure 9.2: Design of 18 dB single stage MESFET amplifier

```

1 s11=0.5*exp(%i*(-60)/180*pi);
2 s12=0.02*exp(%i*(-0)/180*pi);
3 s21=6.5*exp(%i*(+115)/180*pi);
4 s22=0.6*exp(%i*(-35)/180*pi);
5
6 Gs_max=1/(1-abs(s11)^2);
7 Gl_max=1/(1-abs(s22)^2);
8
9 G0=abs(s21)^2;
10
11 Gmax=Gs_max*G0*Gl_max;
12 Gs_max_dB=10*log10(Gs_max)
13 Gl_max_dB=10*log10(Gl_max)
14 G0_dB=10*log10(G0)
15 Gmax_dB=10*log10(Gmax)
16 Ggoal_dB=18;
17 Gload_dB=Ggoal_dB-G0_dB-Gs_max_dB;
18 Gl_opt=conj(s22);
19
20 set(gca(),"auto_clear","off");
21 plot([0 real(Gl_opt)],[0 imag(Gl_opt)],'b');
22 plot(real(Gl_opt),imag(Gl_opt),'bo');
23 a=(0:360)/180*pi;
24 g1=exp([Gload_dB]/10*log(10))/Gl_max;
25 dg=g1*conj(s22)/(1-abs(s22)^2*(1-g1));
26 rg=sqrt(1-g1)*(1-abs(s22)^2)/(1-abs(s22)^2*(1-g1));
27 plot(real(dg)+rg*cos(a),imag(dg)+rg*sin(a),'b',
      linewidth',2);

```

Scilab code Exa 9.13 Amplifier design using the constant operating gain circles

```
1 // define the S-parameters of the transistor
```

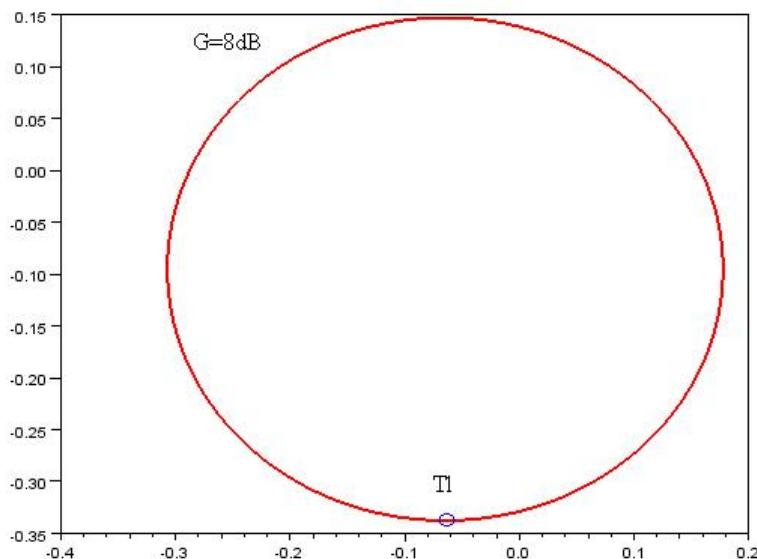


Figure 9.3: Amplifier design using the constant operating gain circles

```

2 s11=0.3*exp(%i*(+30)/180*pi);
3 s12=0.2*exp(%i*(-60)/180*pi);
4 s21=2.5*exp(%i*(-80)/180*pi);
5 s22=0.2*exp(%i*(-15)/180*pi);
6
7 K=1.18
8
9 //find the maximum gain
10 Gmax=abs(s21/s12)*(K-sqrt(K^2-1));
11 Gmax_dB=10*log10(Gmax)
12
13 //specify the target gain
14 G_goal_dB=8; //would like to build an amplifier with
               8dB gain
15 G_goal=10^(G_goal_dB/10); //convert from dB to
               normal units
16
17 //find constant operating power gain circles
18 go=G_goal/abs(s21)^2;
19
20 //find the center of the constant operating power
   gain circle
21 dgo=go*conj(s22-conj(s11))/(1+go*(abs(s22)^2));
22
23
24 //find the radius of the circle
25 rgo1=sqrt(1-2*K*go*abs(s12*s21)+go^2*abs(s12*s21)^2)
      ;
26 rgo=rgo1/abs(1+go*(abs(s22)^2));
27
28 //plot a circle in the Smith Chart
29 a=(0:360)/180*pi;
30
31 set(gca(),"auto_clear","off");
32 plot(real(dgo)+rgo*cos(a),imag(dgo)+rgo*sin(a),'r',
      'linewidth',2);
33
34 //choose the load reflection coefficient

```

```

35 zL=1-%i*0.53
36 GL=(zL-1)/(zL+1);
37
38 plot(real(GL),imag(GL), 'bo');
39
40 [Ro, Theta]=polar(atan(imag(Gs)), real(Gs)));
41 Gin=s11+s12*s21*GL/(1-s22*GL);
42 Gs=conj(Gin);
43 Gs_abs=abs(Gs)
44 Gs_angle=(Theta/pi)*180;
45
46 zs=(1+Gs)/(1-Gs);

```

Scilab code Exa 9.14 Design of small signal amplifier for minimum noise figure and specified gain

```

1 global Z0;
2 Z0=50;
3
4 //define the S-parameters of the transistor
5 s11=0.3*exp(%i*(+30)/180*pi);
6 s12=0.2*exp(%i*(-60)/180*pi);
7 s21=2.5*exp(%i*(-80)/180*pi);
8 s22=0.2*exp(%i*(-15)/180*pi);
9
10 //pick the noise parameters of the transistor
11 Fmin_dB=1.5
12 Fmin=10^(Fmin_dB/10);
13 Rn=4;
14 Gopt=0.5*exp(%i*45/180*pi);
15
16 //compute a noise circle
17 Fk_dB=1.6;

```

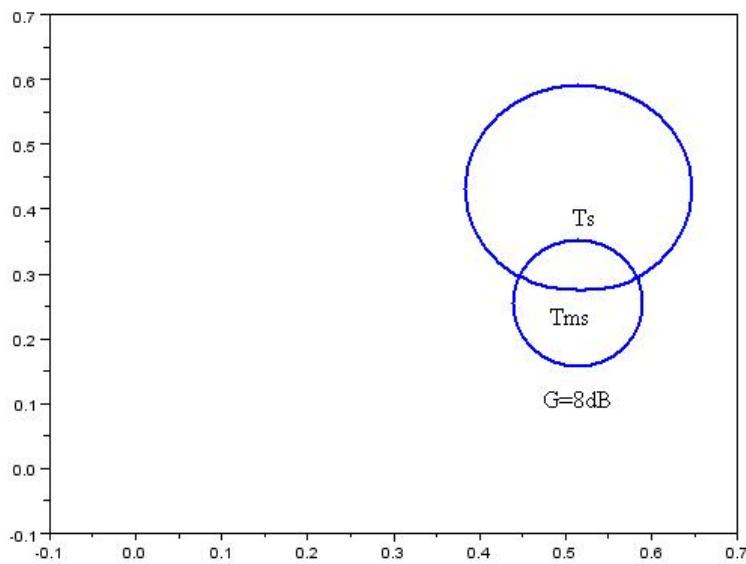


Figure 9.4: Design of small signal amplifier for minimum noise figure and specified gain

```

18 Fk=10^(Fk_dB/10);
19
20
21 Qk=abs(1+Gopt)^2*(Fk-Fmin)/(4*Rn/Z0) // noise circle
   parameter
22 dfk=Gopt/(1+Qk); // circle center location
23 rfk=sqrt((1-abs(Gopt)^2)*Qk+Qk^2)/(1+Qk) // circle
   radius
24
25
26 // plot a noise circle
27 a=[0:360]/180*pi;
28 set(gca(),"auto_clear","off");
29 plot(real(dfk)+rfk*cos(a),imag(dfk)+rfk*sin(a),'b',
   linewidth',2);
30
31 // plot optimal reflection coefficient
32 plot(real(Gopt),imag(Gopt),'bo');
33
34
35 // specify the desired gain
36 G_goal_dB=8;
37 G_goal=10^(G_goal_dB/10);
38
39 // find the constant operating power gain circles
40 go=G_goal/abs(s21)^2; // normalized the gain
41 dgo=go*conj(s22-conj(s11))/(1+go*(abs(s22)^2)); // center
42
43 rgo=sqrt(1-2*K*go*abs(s12*s21)+go^2*abs(s12*s21)^2);
44 rgo=rgo/abs(1+go*(abs(s22)^2));
45
46 // map a constant gain circle into the Gs plane
47 rgs=rgo*abs(s12*s21/(abs(1-s22*dgo)^2-rgo^2*abs(s22)^2));
48 dgss=((1-s22*dgo)*conj(s11-dgo)-rgo^2*s22)/(abs(1-s22*dgo)^2-rgo^2*abs(s22)^2);
49

```

```

50 // plot a constant gain circle in the Smith Chart
51 set(gca(),"auto_clear","off");
52 plot(real(dgs)+rgs*cos(a),imag(dgs)+rgs*sin(a), 'r', 'linewidth',2);
53
54
55
56 //choose a source reflection coefficient Gs
57 Gs=dgs+%i*rgs;
58 plot(real(Gs), imag(Gs), 'ro');
59 //text( real(Gs)-0.05,imag(Gs)+0.08,'bf\Gamma_S');
60
61 //find the actual noise figure
62 F=Fmin+4*Rn/Z0*abs(Gs-Gopt)^2/(1-abs(Gs)^2)/abs(1+
Gopt)^2;
63
64 //print out the actual noise figure
65 Actual_F_dB=10*log10(F)

```

Scilab code Exa 9.15 Constant VSWR design for given gain and noise figure

```

1 global Z0;
2 Z0=50;
3
4 //define the S-parameters of the transistor
5 s11=0.3*exp(%i*(+30)/180*pi);
6 s12=0.2*exp(%i*(-60)/180*pi);
7 s21=2.5*exp(%i*(-80)/180*pi);
8 s22=0.2*exp(%i*(-15)/180*pi);
9
10 //noise parameters of the transistor
11 Fmin_dB=1.5
12 Fmin=10^(Fmin_dB/10);
13 Rn=4;

```

```

14 Gopt=0.5*exp(%i*45/180*%pi);
15
16
17 //compute a noise circle
18 Fk_dB=1.6; //desired noise performance
19 Fk=10^(Fk_dB/10);
20
21 Qk=abs(1+Gopt)^2*(Fk-Fmin)/(4*Rn/Z0); //noise circle
     parameter
22 dfk=Gopt/(1+Qk); //circle center location
23 rfk=sqrt((1-abs(Gopt)^2)*Qk+Qk^2)/(1+Qk); //circle
     radius
24
25
26 //plot a noise circle
27 a=[0:360]/180*%pi;
28 set(gca(),"auto_clear","off");
29 plot(real(dfk)+rfk*cos(a),imag(dfk)+rfk*sin(a),'b',
     linewidth',2);
30
31 //specify the goal gain
32 G_goal_dB=8;
33 G_goal=10^(G_goal_dB/10);
34
35
36 //find constant operating power gain circles
37 go=G_goal/abs(s21)^2; //normalized gain
38 dgo=go*conj(s22-delta*conj(s11))/(1+go*(abs(s22)^2))
     ; //center
39
40 rgo=sqrt(1-2*K*go*abs(s12*s21)+go^2*abs(s12*s21)^2);
41 rgo=rgo/abs(1+go*(abs(s22)^2)); //radius
42
43 //map a constant gain circle into the Gs plane
44 rgs=rgo*abs(s12*s21/(abs(1-s22*dgo)^2-rgo^2*abs(s22)
     ^2));
45 dgs=((1-s22*dgo)*conj(s11-delta*dgo)-rgo^2*s22)/(abs
     (1-s22*dgo)^2-rgo^2*abs(s22)^2);

```

```

46
47 // plot constant gain circle in the Smith Chart
48 set(gca(),"auto_clear","off");
49 plot(real(dgs)+rgs*cos(a),imag(dgs)+rgs*sin(a),'r','
      linewidth',2);
50
51
52 //choose a source reflection coefficient Gs
53 Gs=dgs+%i*rgs;
54
55 //find the corresponding GL
56 GL=(s11-conj(Gs))/(delta-s22*conj(Gs));
57
58 //find the actual noise figure
59 F=Fmin+4*Rn/Z0*abs(Gs-Gopt)^2/(1-abs(Gs)^2)/abs(1+
      Gopt)^2;
60
61 // print out the actual noise figure
62 Actual_F_dB=10*log10(F)
63
64 //find the input and output reflection coefficients
65 Gin=s11+s12*s21*GL/(1-s22*GL);
66 Gout=s22+s12*s21*Gs/(1-s11*Gs);
67
68
69 //find the VSWRin and VSWRout
70 Gimn=abs((Gin-conj(Gs))/(1-Gin*Gs));
71 Gomn=abs((Gout-conj(GL))/(1-Gout*GL));
72
73 VSWRin=(1+Gimn)/(1-Gimn); //VSWRin should be unity
      since we used the constant operating gain
      approach
74 VSWRout=(1+Gomn)/(1-Gomn);
75
76 // specify the desired VSWRin
77 VSWRin=1.5;
78
79 //find parameters for constant VSWR circle

```

```

80 Gimn=(1-VSWRin)/(1+VSWRin)
81 dvimn=(1-Gimn^2)*conj(Gin)/(1-abs(Gimn*Gin)^2); // 
    circle center
82 rvimn=(1-abs(Gin)^2)*abs(Gimn)/(1-abs(Gimn*Gin)^2);
    //circle radius
83
84 //plot VSWRin=1.5 circle in the Smith Chart
85 plot(real(dvimn)+rvimn*cos(a),imag(dvimn)+rvimn*sin(
    a),'g','linewidth',2);
86
87
88 //plot a graph of the output VSWR as a function of
    the Gs position on the constant VSWRin circle
89 Gs=dvimn+rvimn*exp(%i*a);
90 Gout=s22+s12*s21*Gs./(1-s11*Gs);
91
92 //find the reflection coefficients at the input and
    output matching networks
93 Gimn=abs((Gin-conj(Gs))./(1-Gin*Gs));
94 Gomn=abs((Gout-conj(GL))./(1-Gout*GL));
95
96 //and find the corresponding VSWRs
97 VSWRin=(1+Gimn)./(1-Gimn);
98 VSWRout=(1+Gomn)./(1-Gomn);
99
100 figure; //open new figure for the VSWR plot
101 plot(a/%pi*180,VSWRout,'r',a/%pi*180,VSWRin,'b',
    'linewidth',2);
102 legend('VSWR_{out}', 'VSWR_{in}');
103 title('Input and output VSWR as a function of \
    Gamma_S position');
104 xlabel('Angle \alpha, deg.');
105 ylabel('Input and output VSWRs');
106 mtlb_axis([0 360 1.3 2.3])
107
108
109 //choose a new source reflection coefficient
110 Gs=dvimn+rvimn*exp(%i*85/180*pi);

```

```

111
112 // find the corresponding output reflection
   coefficient
113 Gout=s22+s12*s21*Gs./(1-s11*Gs);
114
115 // compute the transducer gain in this case
116 GT=(1-abs(GL)^2)*abs(s21)^2.*((1-abs(Gs).^2)./abs(1-
   GL*Gout).^2./abs(1-Gs*s11).^2;
117 GT_dB=10*log10(GT)
118
119 // find the input and output matching network
   reflection coefficients
120 Gimn=abs((Gin-conj(Gs))./(1-Gin*Gs));
121 Gomn=abs((Gout-conj(GL))./(1-Gout*GL));
122
123 // and find the corresponding VSWRs
124 VSWRin=(1+Gimn)./(1-Gimn)
125 VSWRout=(1+Gomn)./(1-Gomn)
126
127 // also compute the obtained noise figure
128 F=Fmin+4*Rn/Z0*abs(Gs-Gopt)^2/(1-abs(Gs)^2)/abs(1+
   Gopt)^2;
129 F_dB=10*log10(F)

```

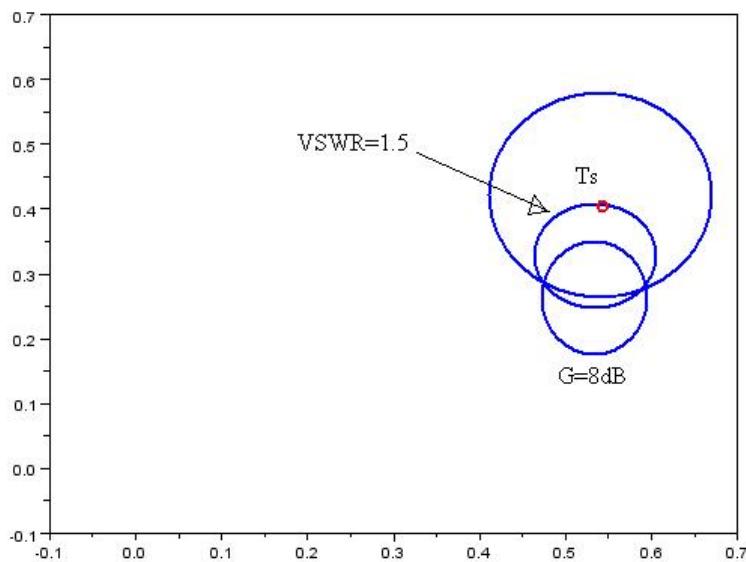


Figure 9.5: Constant VSWR design for given gain and noise figure

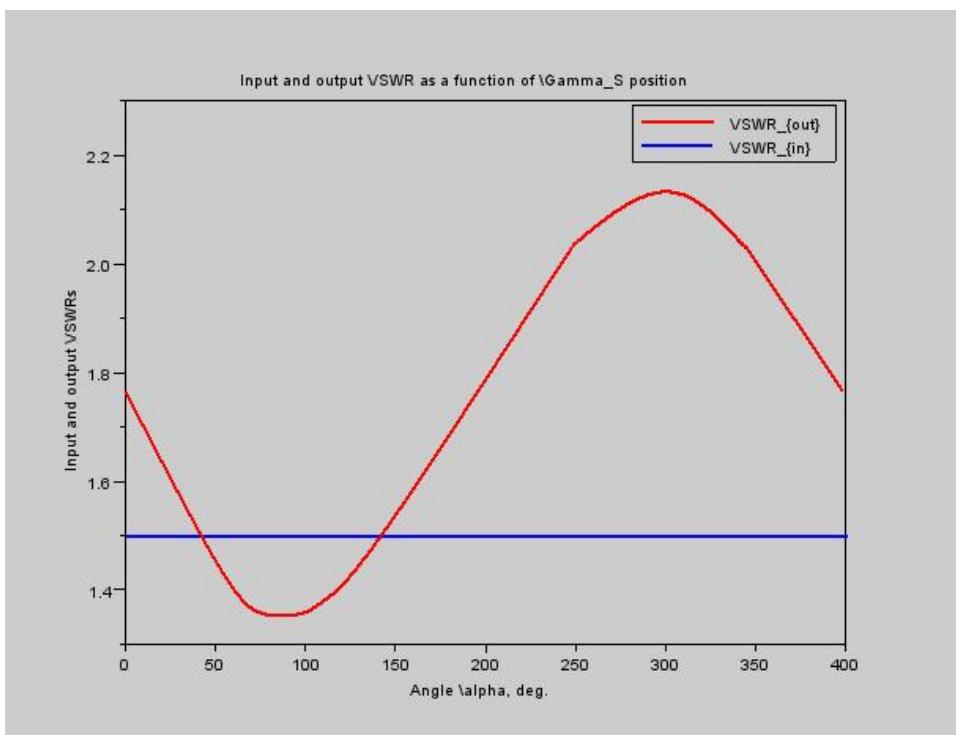


Figure 9.6: Constant VSWR design for given gain and noise figure

Chapter 10

Oscillators and Mixers

Scilab code Exa 10.1 Design of a Colpitt oscillator

```
1 fo=200*10^6;
2 Vce=3;
3 Ic=3*10^-3;
4
5 Cbc=0.1*10^-15;
6 rBE=2*10^3;
7 rCE=10*10^3;
8 Cbe=100*10^-15;
9 L3=50*10^-9;
10 L=50*10^-9;
11 gm=0.11666;
12
13 disp("DC values of Hparameters are");
14 h11=rBE;
15 h12=0;
16 h21=rBE*gm;
17 h22=1/rCE;
18
19 disp("Mho",h22,"h22",h21,"h21",h12,"h12","Ohms",h11,
      "h11);
20 k=h21/(h11*h22-h21*h12);
```

```

21 A=(1+k)/L;
22 B=A^2;
23 C=16*k*(%pi)^2*fo^2*(h22/h11);
24 D=8*k*(%pi)^2*fo^2;
25 C2=(A+sqrt(B+C))/D;
26 C1=k*C2;
27
28 disp("H parameters at resonance frequency");
29 w=2*%pi*fo;
30 E=1+%i*w*(Cbe+Cbc)*rBE;
31
32 hie=rBE/E;
33 hre=(%i*w*Cbc*rBE)/E;
34 hfe=(rBE*(gm-%i*w*Cbc))/E;
35 hoe=h22+(%i*w*Cbc*(1+gm*rBE+%i*w*Cbe*rBE))/E;
36 disp("Mho",hoe,"hoe",hfe,"hfe",hre,"hre","Ohms",hie,
      "hie");

```

Scilab code Exa 10.2 Prediction of resonance frequencies of quartz crystal

```

1 stacksize("max");
2 //define crystal parameters
3 Lq=0.1;
4 Rq=25;
5 Cq=0.3*10^-12;
6 C0=1*10^-12;
7
8 //find series resonance frequency
9 ws0=1/sqrt(Lq*Cq);
10 disp(ws0);
11 ws=ws0*(1+Rq^2/2*C0/Lq);
12 fs=ws/2/%pi
13
14 //find parallel resonance frequency
15 wp0=sqrt((Cq+C0)/(Lq*Cq*C0));

```

```

16 wp=wp0*(1-Rq^2/2*C0/Lq);
17 fp=wp/2/%pi
18
19 //define frequency range for this plot
20 f=(0.9:0.00001:1.1)*1e6;
21 w=2*pi*f;
22
23 //find admittance of the resonator
24 Y=%i.*w*C0+1./(Rq+%i*(w*Lq-1./(w*Cq)));
25
26 plot(f/1e6,abs(imag(Y)));
27 mtlb_axis([0.9 1.1 1e-10 1e-1]);
28 title('Admittance of the quartz crystal resonator');
29 xlabel('Frequency {\itf}, MHz');
30 ylabel('Susceptance |B|, \Omega');

```

Scilab code Exa 10.3 Adding a positive feedback element to initiate oscillations

```

1 Z0=50;
2 //oscillation frequency
3 f=2*10^9;
4 w=2*pi*f;
5 //transistor S-parameters at oscillation frequency
6
7 s_tr=[0.94*exp(%i*174/180*pi),0.013*exp(-%i*98/180*
    %pi);1.9*exp(-%i*28/180*pi),1.01*exp(-%i*17/180*
    %pi)];
8 s11=ss2tf(1,1);
9 s12=ss2tf(1,2);
10 s21=ss2tf(2,1);
11 s22=ss2tf(2,2);
12

```

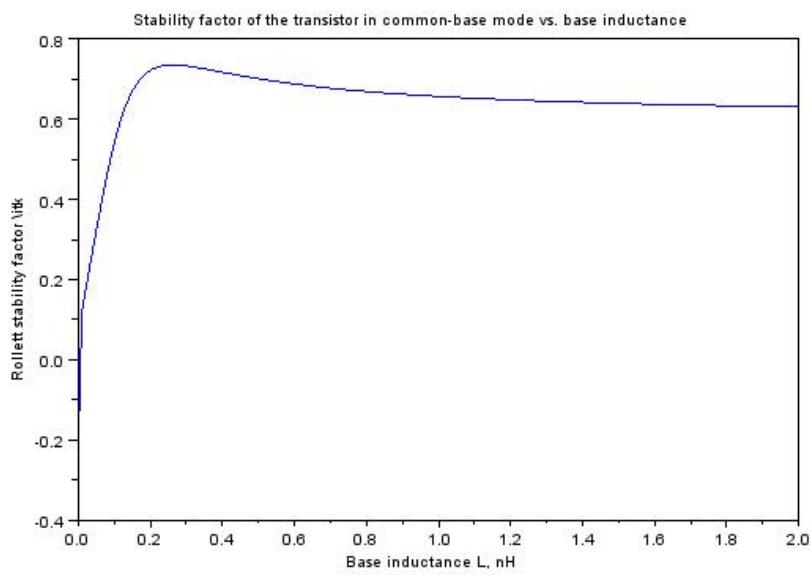


Figure 10.1: Adding a positive feedback element to initiate oscillations

```

13 // find the Z-parameters of the transistor
14 z_tr=ss2tf(s_tr,Z0);
15
16 //attempt to add inductor to base in order to
   increase instability
17 L=(0:0.01:2)*1e-9;
18
19 Z_L=%i*w*L;
20 z_L=[1,1;1,1];
21
22 N=length(L);
23
24 //create variables for the S-parameters of the
   transistor with the inductor
25 s11=zeros([1 N]);
26 s12=zeros([1 N]);
27 s21=zeros([1 N]);
28 s22=zeros([1 N]);
29
30 // Rollett stability factor
31 K=zeros([1 N]);
32
33 for n=1:N
34     z_total=z_tr+z_L*Z_L(n);
35     s_total=ss2tf(z_total,Z0);
36     s11(n)=s_total(1,1);
37     s12(n)=s_total(1,2);
38     s21(n)=s_total(2,1);
39     s22(n)=s_total(2,2);
40     K(n)=(1-abs(s11(n))^2-abs(s22(n))^2+abs(det(
           s_total))^2)/2/abs(s12(n)*s21(n));
41 end;
42
43 plot(L/1e-9,K);
44 title('Stability factor of the transistor in common-
   base mode vs. base inductance');
45 xlabel('Base inductance L, nH');
46 ylabel('Rollett stability factor \itk')

```

Scilab code Exa 10.6 Dielectric resonator oscillator design

```
1 // define the S-paramters of the transistor at
   resonance frequency
2 s11=1.1*exp(%i*(170)/180*pi);
3 s12=0.4*exp(%i*(-98)/180*pi);
4 s21=1.5*exp(%i*(-163)/180*pi);
5 s22=0.9*exp(%i*(-170)/180*pi);
6
7 s=[s11,s12;s21,s22];
8
9 //define oscillation frequency
10 f0=8e9;
11 w0=2*pi*f0;
12
13 //define parameters of the dielectric resonator
14 Z0=50;
15 beta=7;
16 R=beta*2*Z0;
17 Qu=5e3;
18
19 //compute equivalent L and C
20 L=R/(Qu*w0);
21 C=1/(L*w0^2);
22
23 //find output reflection coefficient of the DR
24 Gout_abs=beta/(1+beta);
25 Gout_angle=-atan(imag(s11),real(s11))/pi*180;
26
27 //compute electrical length of the transmission line
   for the DR
28 theta0=-1/2*Gout_angle
29 Gout=Gout_abs*exp(%i*Gout_angle*pi/180);
30
```

```

31 // find the output impedance of the DR
32 Zout=Z0*(1+Gout)/(1-Gout)
33
34
35 // find the equivalent capacitance (it will be
   necessary for the computation of the oscillator
   without DR)
36 CC=-1/(w0*imag(Zout))
37
38 Rs=50;
39
40 // define the frequency for the plot
41 delta_f=0.05e9; //frequency range
42 f=f0-delta_f/2 : delta_f/100 : f0+delta_f/2;
43 w=2*pi*f;
44
45 if theta0<0
46   theta0=360+theta0;
47 end;
48
49 theta=theta0*f/f0/180*pi;
50
51 // repeat the same computations as above, but for
   specified frequency range
52 Gs=(Rs-Z0)/(Rs+Z0);
53 G1=Gs*exp(-%i*2*theta);
54 R1=Z0*(1+G1)./(1-G1);
55 Zd=1./(1/R+1./(%i*w*L+%i*w*C));
56 R1d=R1+Zd;
57 G1d=(R1d-Z0)./(R1d+Z0);
58 G2=G1d.*exp(-%i*2*theta);
59
60 // compute the output reflection coefficient (we have
   oscillations if |Gout|>1)
61 Gout=s22+s12*s21*G2./(1-s11*G2);
62
63 figure;
64 plot(f/1e9,abs(Gout), 'b', 'linewidth',2);

```

```

65 title('Output reflection coefficient of the
       oscillator with DR');
66 xlabel('Frequency f, GHz');
67 ylabel('Output reflection coefficient |\Gamma_{out}|');
68 mtlb_axis([7.975 8.025 0 14]);
69
70
71 // Redefine the frequency range (we have to increase
   it in order to be able to observe any variations
   in the response
72 delta_f=5e9;
73 f=f0-delta_f/2 : delta_f/100 : f0+delta_f/2;
74 w=2*pi*f;
75
76 // Compute the output reflection coefficient of the
   oscillator but with DR replaced by a series
   combination of resistance and capacitance
77 ZZ2=real(Zout)+1./(%i*w*CC);
78 GG2=(ZZ2-Z0)./(ZZ2+Z0);
79 GG=s22+s12*s21*GG2./(1-s11*GG2);
80
81 figure;
82 plot(f/1e9,abs(GG),'r','linewidth',2);
83 title('Output reflection coefficient of the
       oscillator without DR');
84 xlabel('Frequency f, GHz');
85 ylabel('Output reflection coefficient |\Gamma_{out}|');

```

Scilab code Exa 10.8 Local oscillator frequency selection

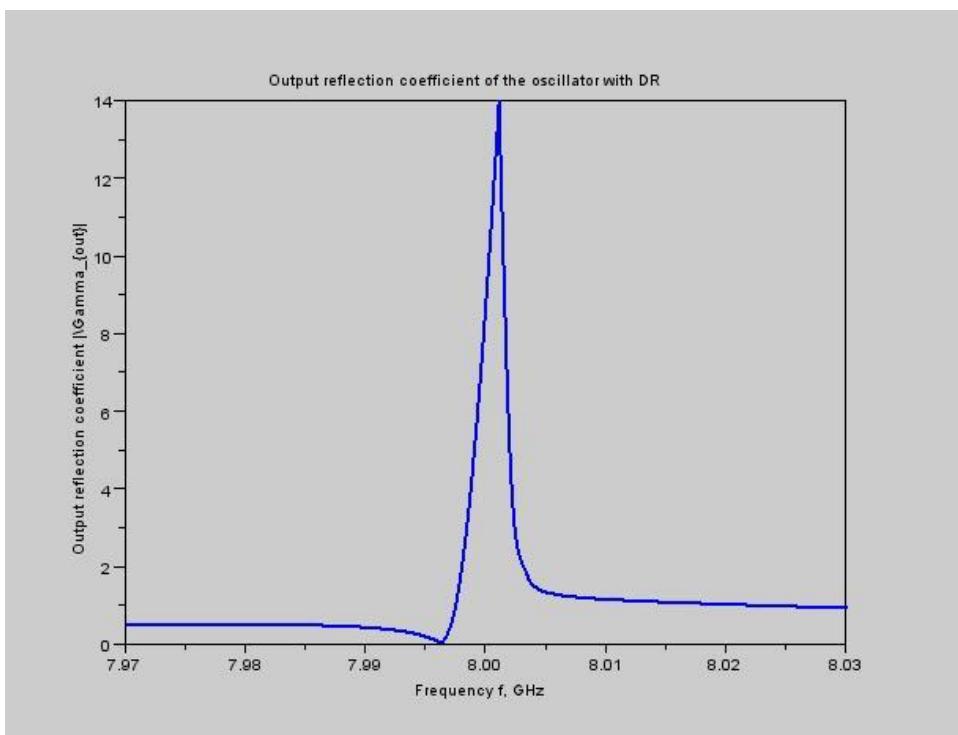


Figure 10.2: Dielectric resonator oscillator design

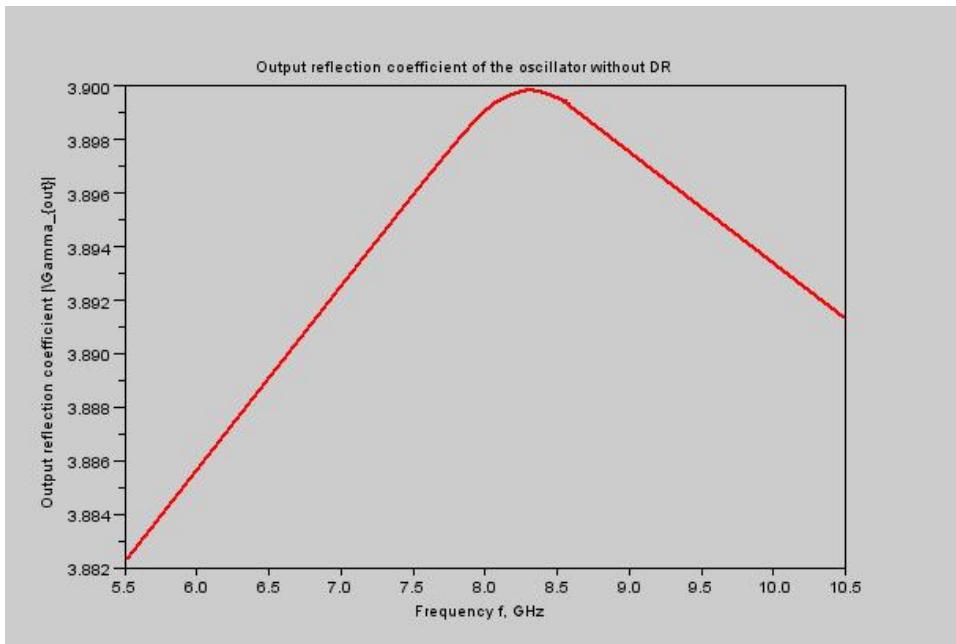


Figure 10.3: Dielectric resonator oscillator design

```

1 fRF=1.89*10^9; //RF frequency
2 BW=20*10^6; //Bandwidth
3 fIF=200*10^6; //Intermediate Frequency
4 flo=fRF+fIF; //Local oscillator frequency
5 Q=fIF/BW; //Quality factor
6 disp(Q,"Quality Factor");

```
