

Scilab Textbook Companion for
Digital Principles And Applications
by D. P. Leach And A. P. Malvino¹

Created by
Kapu Venkat Sayeesh
B.Tech (pursuing)
Electronics Engineering
NIT, Warangal
College Teacher
S.K.L.V Sai Prakash
Cross-Checked by
Giridharan, IITB

August 15, 2013

¹Funded by a grant from the National Mission on Education through ICT,
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab
codes written in it can be downloaded from the "Textbook Companion Project"
section at the website <http://scilab.in>

Book Description

Title: Digital Principles And Applications

Author: D. P. Leach And A. P. Malvino

Publisher: Tata McGraw - Hill, New Delhi

Edition: 6

Year: 2006

ISBN: 0-07-060175-5

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	5
1 Digital Principles	11
2 Digital Logic	12
3 Combinational Logic Circuits	30
4 Data processing circuits	48
5 Number Systems and Codes	57
6 Arithmetic Circuits	71
7 Clocks and Timing Circuits	95
8 Flip Flops	110
9 Registers	119
10 Counters	127
11 Design of Sequential Circuit	143
12 D to A Conversion and A to D conversion	150
13 Memory	156
14 Digital Integrated circuits	158

15 Applications	161
16 A Simple Computer Design	166

List of Scilab Codes

Exa 1.1	Finding duty cycle	11
Exa 1.2	Maximum decimal count for a counter	11
Exa 2.1	7404 waveform	12
Exa 2.2	7404 waveform	14
Exa 2.3	truth table for given figure	17
Exa 2.4	truth table for given figure	17
Exa 2.9	proving two circuits are logically equal	18
Exa 2.10	truth table for NOR NOR circuit	19
Exa 2.11	timing diagram for NOR NOR	19
Exa 2.12	proving two circuits are logically equal	23
Exa 2.13	truth table for NAND NAND circuit	24
Exa 2.14	timing diagram for NAND NAND circuit	24
Exa 2.15	detecting all bits low in a register	28
Exa 3.1	Boolean Algebra	30
Exa 3.2	Boolean Algebra	30
Exa 3.3	Testing a circuit using logic clip	31
Exa 3.4	Sum of Products	32
Exa 3.5	Boolean Algebra	33
Exa 3.6	Gives a simplified Boolean equation	34
Exa 3.7	simplest logic for given Truth table	34
Exa 3.8	simplest logic for given logic equation	35
Exa 3.9	Product of sums	35
Exa 3.10	sop for the karnaugh map	37
Exa 3.11	POS form of karnaugh map	37
Exa 3.12	POS form of karnaugh map	38
Exa 3.13	Quine Mcclusky method	38
Exa 3.14	Dynamic hard	42
Exa 4.1	4 to 1 mux using 2 to 1 mux	48

Exa 4.2	Realizing boolean equation using 8 to 1 mux	48
Exa 4.3	32 to 1 mux using 16 to 1 and 2 to 1 muxes	51
Exa 4.4	74154 IC y12	51
Exa 4.7	realizing boolean equation using 3 to 8 decoder	52
Exa 4.8	current in LED	53
Exa 4.9	which LED lights up for given input conditions	53
Exa 4.10	output of 74147 when button 6 is pressed	54
Exa 4.11	priority encoder	55
Exa 5.1	Binary to decimal conversion	57
Exa 5.2	Binary to decimal conversion	59
Exa 5.3	decimal equivalent of 2 Mb	61
Exa 5.4	Decimal to binary conversion	62
Exa 5.5	Binary number having all ones	63
Exa 5.6	Decimal to binary conversion	64
Exa 5.7	binary to hexadecimal	65
Exa 5.8	hexadecimal to decimal	66
Exa 5.9	decimal to hexadecimal and binary	67
Exa 5.10	decimal to hexadecimal and binary	68
Exa 5.11	decimal to hexadecimal and binary	69
Exa 6.1	8bit binary adder	71
Exa 6.2	16 bit binary adder	73
Exa 6.3	first generation microcomputers addition	74
Exa 6.4	binary subtraction	76
Exa 6.5	adding 8 bit unsigned numbers	78
Exa 6.6	subtraction of unsigned numbers	81
Exa 6.7	overflow case	83
Exa 6.8	2s compliment	85
Exa 6.9	2s compliment	88
Exa 6.10	2s compliment subtraction	90
Exa 6.12	final carry in a CLA	93
Exa 7.1	clock cycle time	95
Exa 7.2	maximum clock frequency	95
Exa 7.3	frequency limits of the clock	96
Exa 7.4	Schmitt trigger	98
Exa 7.5	frequency of oscillation for 555 timer	99
Exa 7.6	finding Ra and C in 555 timer circuit	99
Exa 7.7	output pulse width for the timer	100
Exa 7.8	value of C necessary to change pulse width to given values	101

Exa 7.9	monostable multivibrator	101
Exa 7.10	74123	105
Exa 7.11	finding timing capacitor values	108
Exa 8.4	RS flipflop	110
Exa 8.5	positive edge triggered RS flip flop	111
Exa 8.6	negative edge triggered RS flip flop	111
Exa 8.7	T flip flop	112
Exa 8.9	JK master slave	112
Exa 8.10	fictitious flip flop excitation table	115
Exa 8.12	state transition diagram for given circuit	117
Exa 8.13	D flip flop to RS flip flop	118
Exa 9.1	shift register serial input	119
Exa 9.2	shift register serial input and output graph	120
Exa 9.4	54164 shift register	125
Exa 9.5	54164 shift register	125
Exa 9.8	74ls174	126
Exa 9.9	7495A	126
Exa 10.1	ripple counter clock frequency	127
Exa 10.2	number of flip flops required to construct a counter	127
Exa 10.3	Output waveforms for a 7493A connected as a mod 16 counter	129
Exa 10.5	Expression for AND gate connected to the leg of OR gate that drives clock input to flip flop Qd in 74193	131
Exa 10.6	Expression for 4 input AND gate connected to the leg of OR gate that conditions the J and K inputs to the Qd flip flop in a 74191	132
Exa 10.7	number of flip flops required to construct a counter	132
Exa 10.8	what modulus counters can be constructed with given number of flip flops e	133
Exa 10.9	mod 6 counter	133
Exa 10.10	Expression for a gate to decode count 8 in a 7492A	137
Exa 10.12	mod 12 counter	137
Exa 10.13	4 bit binary counter presettable	138
Exa 10.14	self correcting modulo 6 counter	140
Exa 10.15	sequence generator	142
Exa 11.1	synchronous sequential logic circuit	143
Exa 11.2	vending machine	145
Exa 11.5	Reducing state transition diagrams	146

Exa 11.6	asynchronous sequential circuit	147
Exa 11.7	asynchronous sequential circuit problem in operation	148
Exa 11.8	asynchronous sequential circuit	149
Exa 12.1	binary equivalent weight of each bit in a 4bit system	150
Exa 12.2	5 bit resistive divider	151
Exa 12.3	5 bit ladder	151
Exa 12.4	5 bit ladder	152
Exa 12.5	5 bit ladder	152
Exa 12.6	5 bit ladder	153
Exa 12.8	DAC0808	153
Exa 12.9	resolution of 9 bit D to A	154
Exa 12.10	resolution	154
Exa 12.11	counter type A to D converter	154
Exa 12.13	10 bit A to D converter	155
Exa 13.2	structure of binary address	156
Exa 13.3	decimal and hexadecimal address for the given binary address	156
Exa 14.1	diode forward or reverse	158
Exa 14.2	Diode current	159
Exa 14.3	current in the given circuit	159
Exa 14.4	n channel MOSFET inverter	160
Exa 15.1	Timing of a six digit display	161
Exa 15.4	Basic frequency counter	162
Exa 15.5	4 decimal digit frequency counter	162
Exa 15.6	instrument to measure time period	163
Exa 15.9	ADC0804	163
Exa 15.10	ADC3511	164
Exa 15.11	ADC3511	165
Exa 15.12	ADD3501	165
Exa 16.1	size of PC IR ACC MAR MDR	166
Exa 16.6	Number of clock cycles needed to execute a program	167
AP 1	3-variable kmap(abx)	168
AP 2	returns number of 1s in a matrix	172
AP 3	returns number of 0s in a matrix	173
AP 4	4-variable kmap with don't cares	173
AP 5	number of zeros and ones	181
AP 6	3-variable kmap(a)	181
AP 7	2-variable kmap	186

AP 8	3-variable kmap	187
AP 9	4-variable kmap(sx1x2)	192
AP 10	4-variable kmap	199
AP 11	4-variable kmap pos	207

List of Figures

2.1	7404 waveform	13
2.2	7404 waveform	15
2.3	timing diagram for NOR NOR	20
2.4	timing diagram for NAND NAND circuit	25
3.1	Dynamic hard	43
7.1	Schmitt trigger	97
7.2	monostable multivibrator	102
7.3	monostable multivibrator	103
7.4	74123	105
7.5	74123	106
8.1	JK master slave	113
9.1	shift register serial input and output graph	121
10.1	Output waveforms for a 7493A connected as a mod 16 counter	128
10.2	mod 6 counter	134

Chapter 1

Digital Principles

Scilab code Exa 1.1 Finding duty cycle

```
1 //Example 1.1
2 clc;
3 clear;
4 f= 5 * 10^6 ; //given
5 T=1/f; // caculating the time period .
6 H = 0.05 * 10^-6 / T ;
7 printf('Time period of the waveform is T = %f us\n',
       T); //displaying results
8 printf(" Duty cycle H = %f %%" ,H*100);
```

Scilab code Exa 1.2 Maximum decimal count for a counter

```
1 //Example 1.2
2 clc;
3 clear;
4 n=8; // given no of flip flops
5 max_count = 2^n -1 ;
6 printf("Maximum count = %d" ,max_count);
```

Chapter 2

Digital Logic

Scilab code Exa 2.1 7404 waveform

```
1 //exmaple 2.1
2 //7404
3 clc
4 close
5 clear
6 //frq= input('Enter the square wave frequency in KHz
7 :');
8 frq=1 ;// frequency in KHz
9 t=(1/frq)*100;
10 t=round(t)
11 for r=1:t*10
12     inputc(r)=0;
13     outputc(r)=0;
14 end
15 p=1;
16 while p<t*10          // making arrays
17     to plot the curve
18     if p==1 | modulo(p,t)==0 then
19         for k=1:t/2
```

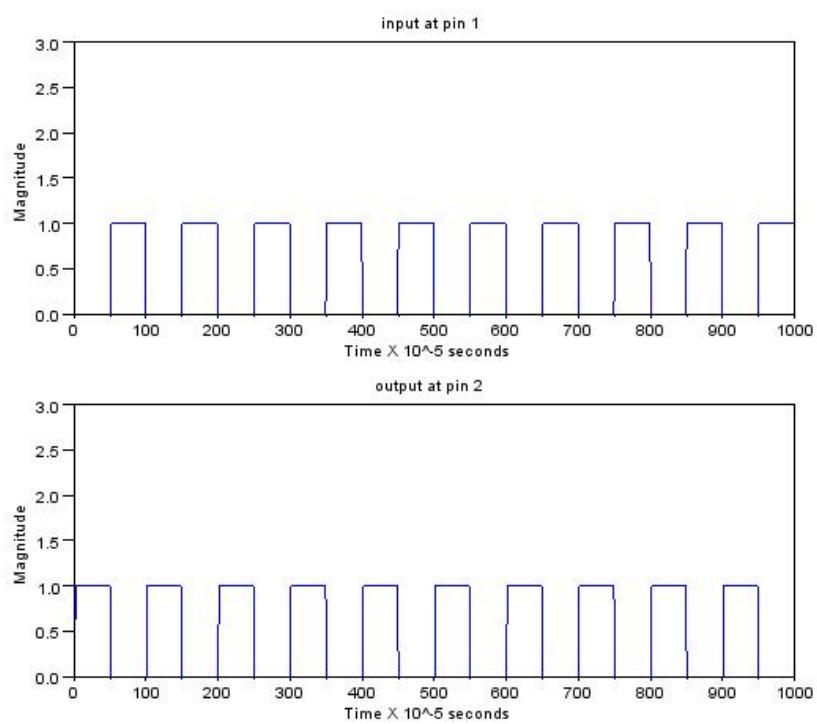


Figure 2.1: 7404 waveform

```

18         inputc(p+k)=0;
19         outputc(p+k)=1;
20     end
21     p=p+t/2;
22 else
23     inputc(p)=1;
24     outputc(p)=0;
25     p=p+1;
26 end
27 end
28 y=[3 3];
29 subplot(2,1,1)      //ploting the curves
30 title('input at pin 1')
31 xlabel('Time X 10^-5 seconds');
32 ylabel('Magnitude')
33 plot(inputc)
34 plot(y)
35 subplot(2,1,2)
36 title('output at pin 2')
37 xlabel('Time X 10^-5 seconds');
38 ylabel('Magnitude')
39 plot(outputc)
40 plot(y)

```

Scilab code Exa 2.2 7404 waveform

```

1 //exmaple 2.2
2 //7404
3 clc
4 close
5 clear
6 //frq= input('Enter the square wave frequency in KHz
:');
```

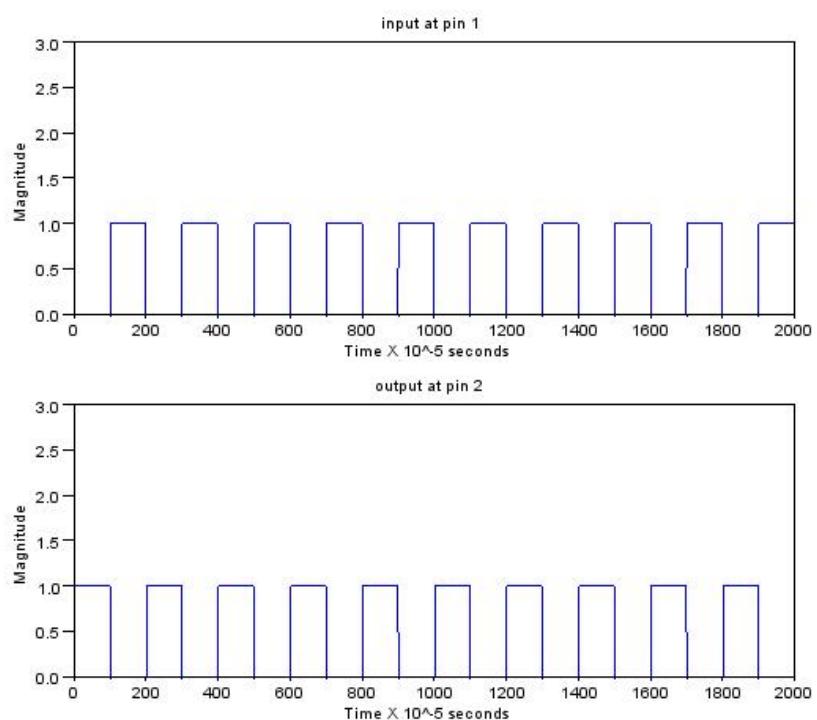


Figure 2.2: 7404 waveform

```

7 frq=0.5 ; //KHz
8 t=(1/frq)*100;
9 t=round(t)
10 for r=1:t*10
11     inputc(r)=0;
12     outputc(r)=0;
13 end
14 p=1;
15 while p<t*10                                //
16     making arrays t plot the curve
17     if p==1 | modulo(p,t)==0 then
18         for k=1:t/2
19             inputc(p+k)=0;
20             outputc(p+k)=1;
21         end
22         p=p+t/2;
23     else
24         inputc(p)=1;
25         outputc(p)=0;
26         p=p+1;
27     end
28 end
29 y=[3 3];
30 subplot(2,1,1)      //ploting the graphs
31 title('input at pin 1')
32 xlabel('Time X 10^-5 seconds');
33 ylabel('Magnitude')
34 plot(inputc)
35 plot(y)
36 subplot(2,1,2)
37 title('output at pin 2')
38 xlabel('Time X 10^-5 seconds');
39 ylabel('Magnitude')
40 plot(outputc)
41 plot(y)

```

Scilab code Exa 2.3 truth table for given figure

```
1 // exmple 2.3
2 clc
3 clear
4 close
5 a=[0 0 1 1];
6 b=[0 1 0 1];
7 for i=1:4
8     r(i)= bitor(bitcmp(a(i),1), bitcmp(b(i),1))
        // given expression
9 end
10 disp(' A      B      Y')
11 for i = 1 : 4
12     Y(i,1)=a(i);
13     Y(i,2)=b(i);
14     Y(i,3)=r(i);
15 end
16 disp(Y); //displaying truth table
17 disp(' ' '1' represents a HIGH(H) and ' '0'
represents a LOW(L)')
```

Scilab code Exa 2.4 truth table for given figure

```
1 // exmple 2.4
2 clear
3 clc
4 a=[0 0 1 1];
5 b=[0 1 0 1];
6 for i=1:4
7     r(i)= bitand(bitcmp(a(i),1), bitcmp(b(i),1)) //
given expression
```

```

8 end
9 disp(' A B Y')
10 for i = 1 : 4
11     Y(i,1)=a(i);
12     Y(i,2)=b(i);
13     Y(i,3)=r(i);
14 end
15 disp(Y); // displaying truth table
16 disp(' ' '1' represents a HIGH(H) and ' '0'
represents a LOW(L)')

```

Scilab code Exa 2.9 proving two circuits are logically equal

```

1 //Example 2.9
2 clc
3 clear
4 close
5 a=[0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1];
6 b=[0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1];
7 c=[0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1];
8 d=[0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1];
9 for i=1:16 // finding Y for all 16 cases
10    x=bitor(a(i),b(i));
11    y=bitor(c(i),d(i));
12    r(i)=bitand(x,y);
13    x1=bitcmp(x,1);
14    y1=bitcmp(y,1);
15    z=bitor(x1,y1);
16    r1(i)=bitcmp(z,1);
17 end
18 disp(' Y Y1');
19 for i = 1 : 16
20     Y(i,1)=r1(i);
21     Y(i,2)=r(i);
22 end

```

```
23 disp(Y); // displaying result
24 disp('Both are logically equivalent');
```

Scilab code Exa 2.10 truth table for NOR NOR circuit

```
1 // exmple 2.10
2 clc
3 clear
4 a=[0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1];
5 b=[0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1];
6 c=[0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1];
7 d=[0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1];
8 for i=1:16
9     x=bitor(a(i),b(i));
10    y=bitor(c(i),d(i));
11    r(i)=bitand(x,y);
12 end
13 disp('Truth table :');
14 disp(' A      B      C      D      Y')
15 for i = 1 : 16 //displaying truth table
16     Y(i,1)=a(i);
17     Y(i,2)=b(i);
18     Y(i,3)=c(i);
19     Y(i,4)=d(i);
20     Y(i,5)=r(i);
21 end
22 disp(Y);
```

Scilab code Exa 2.11 timing diagram for NOR NOR

```
1 // exmple 2.11
```

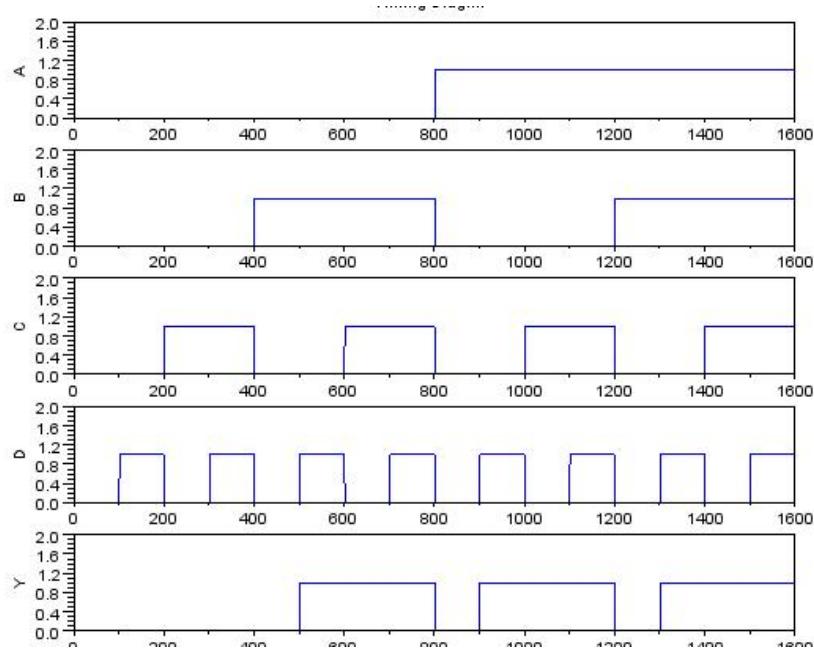


Figure 2.3: timing diagram for NOR NOR

```

2 clc
3 clear
4 close
5 a=[0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1];
6 b=[0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1];
7 c=[0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1];
8 d=[0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1];
9 for i=1:16
10     x=bitor(a(i),b(i));
11     y=bitor(c(i),d(i));
12     r(i)=bitand(x,y);
13 end
14 Y=r
15 ap=1;
16 bp=1;
17 cp=1;
18 dp=1; Yp=1;
19 for i=1:16      //Making array to plot the timing

```

```

diagram
20      if a(i)==1 then
21          for o=1:100
22              a1(ap)=1;
23              ap=ap+1;
24          end
25      else
26          for o=1:100
27              a1(ap)=0;
28              ap=ap+1;
29          end
30      end
31      if b(i)==1 then
32          for o=1:100
33              b1(bp)=1;
34              bp=bp+1;
35          end
36      else
37          for o=1:100
38              b1(bp)=0;
39              bp=bp+1;
40          end
41
42      end
43      if c(i)==1 then
44          for o=1:100
45              c1(cp)=1;
46              cp=cp+1;
47          end
48      else
49          for o=1:100
50              c1(cp)=0;
51              cp=cp+1;
52          end
53      end
54      if d(i)==1 then
55          for o=1:100
56              d1(dp)=1;

```

```

57         dp=dp+1;
58     end
59 else
60     for o=1:100
61         d1(dp)=0;
62         dp=dp+1;
63     end
64 end
65 if Y(i)==1 then
66     for o=1:100
67         Y1(Yp)=1;
68         Yp=Yp+1;
69     end
70 else
71     for o=1:100
72         Y1(Yp)=0;
73         Yp=Yp+1;
74     end
75 end
76 end
77 z=[2 2];
78 subplot(5,1,1); //plotting timing diagram
79 title('Timing Diagram');
80 plot(z);
81 plot(a1);
82 ylabel('A');
83 subplot(5,1,2);
84 plot(z);
85 ylabel('B');
86 plot(b1);
87 subplot(5,1,3);
88 plot(z);
89 ylabel('C');
90 plot(c1);
91 subplot(5,1,4);
92 plot(z);
93 ylabel('D');
94 plot(d1);

```

```
95 subplot(5,1,5);
96 plot(z);
97 ylabel('Y');
98 xlabel('Time in milli seconds');
99 plot(Y1);
```

Scilab code Exa 2.12 proving two circuits are logically equal

```
1 //Example 2.12
2 clc
3 clear
4 a=[0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1];
5 b=[0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1];
6 c=[0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1];
7 d=[0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1];
8 for i=1:16 // finding Y and y1 for all possible inpt
cases
9 x=bitand(a(i),b(i));
10 y=bitand(c(i),d(i));
11 r(i)=bitor(x,y);
12 x1=bitcmp(x,1);
13 y1=bitcmp(y,1);
14 z=bitand(x1,y1);
15 r1(i)=bitcmp(z,1);
16 end
17 disp(' Y Y1');
18 for i = 1 : 16 // displaying result
19 Y(i,1)=r(i);
20 Y(i,2)=r1(i);
21 end
22 disp(Y);
23 disp('Both are logically equivalent');
```

Scilab code Exa 2.13 truth table for NAND NAND circuit

```
1 // exmple 2.13
2 //NAND - NAND
3 clc
4 clear
5 close
6 a=[0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1];
7 b=[0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1];
8 c=[0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1];
9 d=[0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1];
10 for i=1:16
11     x=bitand(a(i),b(i));
12     y=bitand(c(i),d(i));
13     r(i)=bitor(x,y);
14 end
15 disp('Truth table :');
16 disp(' A B C D Y')
17 for i = 1 : 16 // displaying the truth table
18     Y(i,1)=a(i);
19     Y(i,2)=b(i);
20     Y(i,3)=c(i);
21     Y(i,4)=d(i);
22     Y(i,5)=r(i);
23 end
24 disp(Y);
```

Scilab code Exa 2.14 timing diagram for NAND NAND circuit

```
1 // exmple 2.14
2 clc
3 clear
4 close
```

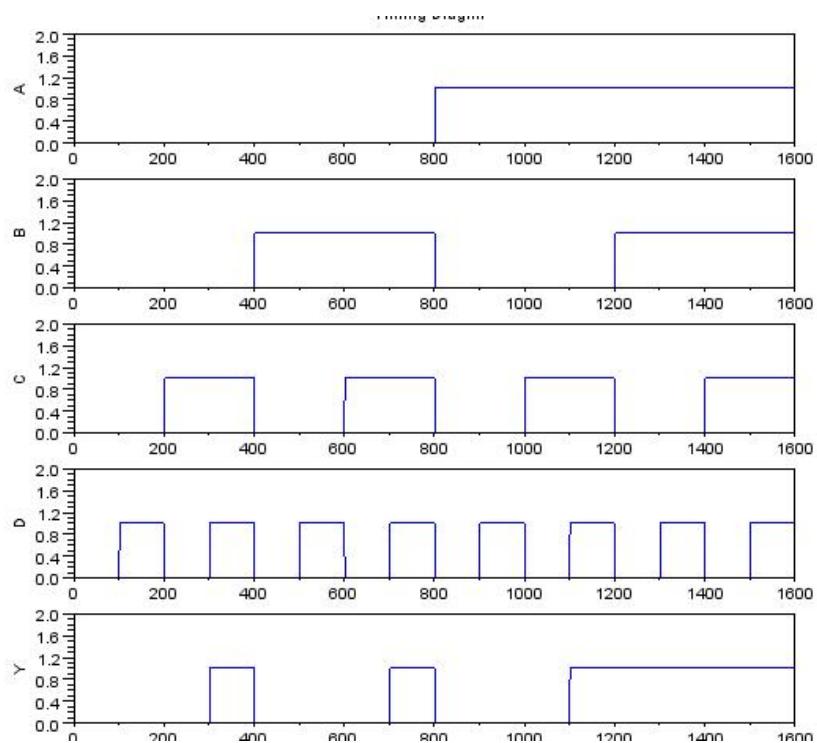


Figure 2.4: timing diagram for NAND NAND circuit

```

5  a=[0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1];
6  b=[0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1];
7  c=[0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1];
8  d=[0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1];
9  for i=1:16
10    x=bitand(a(i),b(i));
11    y=bitand(c(i),d(i));
12    r(i)=bitor(x,y);
13 end
14 Y=r
15 ap=1;
16 bp=1;
17 cp=1;
18 dp=1; Yp=1;
19 for i=1:16      //Making arrays to plot the timing
diagram
20  if a(i)==1 then
21    for o=1:100
22      a1(ap)=1;
23      ap=ap+1;
24    end
25  else
26    for o=1:100
27      a1(ap)=0;
28      ap=ap+1;
29    end
30
31 end
32 if b(i)==1 then
33  for o=1:100
34    b1(bp)=1;
35    bp=bp+1;
36    //z(bp)=3
37  end
38 else
39  for o=1:100
40    b1(bp)=0;
41    bp=bp+1;

```

```

42          // z(bp)=3
43      end
44
45  end
46 if c(i)==1 then
47     for o=1:100
48         c1(cp)=1;
49         cp=cp+1;
50         end
51     else
52         for o=1:100
53             c1(cp)=0;
54             cp=cp+1;
55             end
56
57 end
58 if d(i)==1 then
59     for o=1:100
60         d1(dp)=1;
61         dp=dp+1;
62         end
63     else
64         for o=1:100
65             d1(dp)=0;
66             dp=dp+1;
67             end
68
69     end
70 if Y(i)==1 then
71     for o=1:100
72         Y1(Yp)=1;
73         Yp=Yp+1;
74         end
75     else
76         for o=1:100
77             Y1(Yp)=0;
78             Yp=Yp+1;
79             end

```

```

80
81      end
82
83  end
84 z=[2 2];
85 subplot(5,1,1); // plotting timing diagram
86 title('Timing Diagrm');
87 plot(z);
88 plot(a1);
89 ylabel('A');
90 subplot(5,1,2);
91 plot(z);
92 ylabel('B');
93 plot(b1);
94 subplot(5,1,3);
95 plot(z);
96 ylabel('C');
97 plot(c1);
98 subplot(5,1,4);
99 plot(z);
100 ylabel('D');
101 plot(d1);
102 subplot(5,1,5);
103 plot(z);
104 ylabel('Y');
105 xlabel('Time in milli seconds');
106 plot(Y1);

```

Scilab code Exa 2.15 detecting all bits low in a register

```

1 //example 2.15
2 clc
3 clear
4 s=0; // s from the register
5 s(1)=input('Enter the value at S0 :')

```

```
6 s(2)=input('Enter the value at S1 : ')
7 s(3)=input('Enter the value at S2 : ')
8 s(4)=input('Enter the value at S3 : ')
9 s(5)=input('Enter the value at S4 : ')
10 s(6)=input('Enter the value at S5 : ')
11 s(7)=input('Enter the value at S6 : ')
12 s(8)=input('Enter the value at S7 : ')
13 count =0;
14 for i =1 :8 //loop to detect a '1'
15     if s(i)==1 then
16         disp('ZERO is LOW');
17         break;
18     end
19     count =count+1;
20 end
21 if count==8 then
22     disp('ZERO is HIGH');
23 end;
```

Chapter 3

Combinational Logic Circuits

Scilab code Exa 3.1 Boolean Algebra

```
1 //example 3.1
2 clc;
3 clear;
4 disp("we can minimize the given equation as:");
5 disp('Y = AB' + AB = A(B' + B));
6 disp('Therefore , Y = A(1) = A');
7 disp('this says that output Y equals to A, so all we
     hve to do is connect a wire between input A and
     output Y.');
```

Scilab code Exa 3.2 Boolean Algebra

```
1 //example 3.2
2
3 clc;
4 clear;
5 disp("Multipl the factors of the foregoing equation
     to get");
```

```

6 disp('Y = A' 'A + A' 'B + BA +BB');
7 disp('it becomes , Y = A' 'B + AB + B ');
8 disp('We can factor the foregoong equation as
      follows :');
9 disp('Y = B(A' ' + A) + B = B + B = B ');
10 disp('this says that output Y equals to B, so all we
       have to do is connect a wire between input B and
       output Y.');

```

Scilab code Exa 3.3 Testing a circuit using logic clip

```

1 //example 3.3
2 clc;
3 clear;
4 //disp(' Enter the inputs for AND gate ');
5 //for i=1:7
6 //printf("Enter wether the led %d is on or off (1 or
     0) :" ,i);
7 //a(i)=input(' ');
8 //end;
9 //disp('Enter the inputs for OR gate ')
10 //for i=1:7
11 //printf("Enter wether the led %d is on or off (1 or
     0) :" ,i);
12 //b(i)=input(' ');
13 //end;
14 a= [0 1 0 1 1 0 0]; //lights on a logic clip
15 b= [0 0 0 0 1 1 0];
16 k=bitand(a(1),a(2));
17 k2 = bitand(a(4),a(5));
18 k3=bitor(b(1),b(2));
19 k4 = bitor(b(4),b(5));
20 if a(3) ~= k then // checking which gate is faulty
21     disp("The first AND gate is defective ");
22 elseif a(6) ~= k2 then

```

```

23         disp("The second AND gate is defective ");
24 elseif b(3) ~= k3 then
25     disp("The first OR gate is defective ");
26 elseif b(6) ~= k4 then
27     disp("The second OR gate is defective ");
28 else
29     disp('All the gates are working correctly ');
30 end

```

Scilab code Exa 3.4 Sum of Products

```

1 //example 3.4
2 clc;
3 clear;
4 disp('Given the truth table has high output for
      following conditons :');
5 a=[0 0 0 ; 0 1 0 ; 1 0 0 ; 1 1 0 ] //given input
      conditions for which output is high
6 disp(a)
7 for (i=1:4)
8     if a(i,1)==1 then
9         b(i,1)= 'A'
10    else
11        b(i,1)= 'A^'
12    end
13    if a(i,2)==1 then
14        b(i,2)= 'B'
15    else
16        b(i,2)= 'B^'
17    end
18    if a(i,3)==1 then
19        b(i,3)= 'C'
20    else
21        b(i,3)= 'C^'
22    end

```

```

23 end
24 disp('When you OR these products you get :') // 
    displaying sum of products
25 x=strcat([b(1,1) b(1,2) b(1,3) " + " b(2,1) b(2,2) b
    (2,3) " + " b(3,1) b(3,2) b(3,3) " + " b(4,1) b
    (4,2) b(4,3)]);
26 disp(x)

```

Scilab code Exa 3.5 Boolean Algebra

```

1 //example 3.5
2 clc;
3 clear;
4 disp('The boolean equation is :');
5 disp('Y = A''B''C'' + A''BC'' + AB''C'' + ABC'''');
6 disp('Since C'' is common to each term , factor as
    follows :');
7 disp('Y = (A''B + A''B + AB'')C'''');
8 disp('Again , factor to get :');
9 disp('Y = [A''(B'' + B) + A(B'' + B)]C'''');
10 disp('Now, simplify the foregoing as follows :');
11 disp('Y=[A''(1) + A(1)]C'' = (A'' + A)C'''');
12 disp(' or Y= C'''');
13 disp('This final equation means that you don ''t even
    need a logic circuit . All you need is a wire
    connecting input C'' to output Y.'');

```

check Appendix AP 10 for dependency:

kmap.sci

check Appendix AP 2 for dependency:

noof.sci

Scilab code Exa 3.6 Gives a simplified Boolean equation

```
1 //example 3.6
2 // this program needs kmap.sci and noof.sci
3 clc
4 Y=[7 9 10 11 12 13 14 15]; //given logic equation
5 k=[0 0 0 0;0 0 1 0 ; 1 1 1 1; 0 1 1 1]; //
minimizing it using 4-variable kmap
6 disp("The minimal expression of Y from the
following Kmap is :");
7 kmap(k); //calling the Kmap function
```

check Appendix AP 10 for dependency:

kmap.sci

check Appendix AP 2 for dependency:

noof.sci

Scilab code Exa 3.7 simplest logic for given Truth table

```
1 //example 3.7
2 // this program needs kmap.sci and noof.sci
3 clc;
4 disp('The kanaurgh map for given truth table will be
:');
5 disp('      C' 'D' ' C' 'D' CD' 'CD' '');//displaying
the given kmap
6 disp('A' 'B' ' 1   0   0   0 ');
7 disp('A' 'B' ' 0   0   0   0 ');
8 disp('AB' ' x   x   x   x ');
9 disp('AB' ' 0   0   x   x ');
10 disp('The truth table has output one only for the
input condition 0000. The corresponding
fundamental product is A' 'B' 'C' 'D' ');
11 k=[1 0 0 0 ; 0 0 0 0; 0 0 0 0;0 0 0 0];
12 kmap(k); //calling the Kmap function
```

check Appendix AP 10 for dependency:

`kmap.sci`

check Appendix AP 2 for dependency:

`noof.sci`

Scilab code Exa 3.8 simplest logic for given logic equation

```
1 //example 3.8
2 // this program needs kmap.sci and noof.sci
3 clc;
4 disp('      C'D'   C'D  CD  CD'); // displaying
    the given kmap
5 disp('A'B', 0 0 0 0');
6 disp('A'B', 0 0 1 0');
7 disp('AB', x x x x');
8 disp('AB', 0 0 x x');
9 k=[0 0 0 0;0 0 1 0;0 0 0 1;0 0 0 0];
10 disp('In a Karnaugh map if don''t care condition
        exists , we may consider them as ones if that gives
        a larger group size.');
11 disp('The minimal expression from the given kmap is
        ');
12 kmap(k); //calling the kamp function
```

Scilab code Exa 3.9 Product of sums

```
1 //example 3.4
2 clc;
3 clear;
```

```

4 disp('Given the truth table has high output for
      following conditons :');
5 a=[0 0 0 ; 0 0 1 ; 0 1 0 ] //given truth table
6 disp(a)
7
8 for (i=1:3) //finding the terms in pos
9     if a(i,1)==0 then
10         b(i,1)= 'A'
11     else
12         b(i,1)= 'A^'
13     end
14     if a(i,2)==0 then
15         b(i,2)= 'B'
16     else
17         b(i,2)= 'B^'
18     end
19     if a(i,3)==0 then
20         b(i,3)= 'C'
21     else
22         b(i,3)= 'C^'
23     end
24 end
25 disp(b)
26 disp('The product-of-sums equation is :') //
      displaying the POS
27 x=strcat(["(" b(1,1) " + " b(1,2) " + " b(1,3) ")"
           (" b(2,1) " + " b(2,2) " + " b(2,3) ")") "(" b
           (3,1) " + " b(3,2) " + " b(3,3) ")"]);
28 disp(x)

```

check Appendix AP 10 for dependency:

kmap.sci

check Appendix AP 2 for dependency:

noof.sci

Scilab code Exa 3.10 sop for the karnaugh map

```
1 //example 3.10
2 // this program needs kmappos.sci and noof.sci
3
4 k=[0 0 0 0;0 0 1; 1 1 1 1;1 1 1 1];
5 disp("The minimal expression of Y from the following
      Kmap is :");
6 kmap(k);
7 disp('After complimenting and simplifying the
      Krarnugh map we get Y =:');
8 k=[1 1 1 1;1 1 1 0; 0 0 0 0;0 0 0 0 ];
9 kmap(k); //calling the Kmap function
```

check Appendix AP 11 for dependency:

kmappos.sci

check Appendix AP 2 for dependency:

noof.sci

Scilab code Exa 3.11 POS form of karnaugh map

```
1 //example 3.11
2 // this program needs kmappos.sci and noof.sci
3
4 clc
5 disp('The given kmap is '); //displaying the given
      kmap
6 disp(' C' 'D' ' C' 'D' 'CD' 'CD' ');
7 disp('A' 'B' ' 0' ' 0' ' 0' ' 0');
8 disp('A' 'B' ' 0' ' 0' ' 0' ' 1');
9 disp('AB' ' 1' ' 1' ' 1' ' 1');
10 disp('AB' ' 1' ' 1' ' 1' ' 1');
11 disp("The simplest POS form of following Kmap is :")
      ;
```

```
12
13 k= [0 0 0 0;0 0 0 1 ;1 1 1 1; 1 1 1 1];
14 kmappos(k); // calling the Kmappos function
```

check Appendix [AP 11](#) for dependency:

`kmappos.sci`

check Appendix [AP 2](#) for dependency:

`noof.sci`

Scilab code Exa 3.12 POS form of karnaugh map

```
1 //example 3.12
2 clc
3 disp('The given kmap is '); //displaying the given
   kmap
4 disp('      C' 'D' '  C' 'D  CD  CD' ');
5 disp('A' 'B' '  0    0    1    0');
6 disp('A' 'B    0    0    1    1');
7 disp('AB      x    x    x    1');
8 disp('AB'     x    x    x    0);
9 disp('In a Karnaugh map if don''t care condition
   exists , we may consider them as zeros if that
   gives a larger group size.');
10 disp("The simplest POS form of following Kmap is :")
;
11
12 k= [0 0 1 0;0 0 1 1 ;0 0 1 1; 0 0 1 0];
13 kmappos(k); //calling the Kmappos function
```

Scilab code Exa 3.13 Quine Mcclusky method

```

1 //example 3.1
2 clc;
3 clear;
4 a=[0 0 0 0 1 1 1 1;0 0 1 1 0 0 1 1;0 1 0 1 0 1 0 1];
    //from the truth table given
5 y=[0 0 1 0 0 0 1 1];
6 j=1;
7 for i=1:8 // finding for which input conditions the
    output is high
8     if y(i) == 1 then
9         x(j,:)= [a(1,i) a(2,i) a(3,i)];
10        j=j+1;
11    end
12 end
13 for i=1:j-1; // finding the first stage
14     f(i)=0;
15     c=0;
16     for m=3:-1:1
17         f(i) = f(i) + x(i,m)*(2^c);
18         c=c+1;
19     end
20 end
21 disp('stage 1'); //displaying first stage
22 x(:,4)=f;
23 disp('      A      B      C');
24 disp(x)
25 count=zeros(j-2,j-2)
26 pos=count;
27 for i=1:j-2 // for second stage comparing with each
    other
28     for k=1:j-i-1
29         for m=1:3
30             if x(i,m)==x(i+k,m) then
31                 count(i,k)=count(i,k)+1;
32             else
33                 pos(i,k)=m
34             end
35         end

```

```

36 end
37 end
38 r=1;
39 for i=1:j-2 //making a list of second stage
    elements
40     for m=1:j-2
41         if count(i,m)==2 then
42             posi(r) = pos(i,m);
43             sest(r,1) = x(i,4);
44             sest(r,2) = x(i+m,4);
45             r=r+1;
46         end
47     end
48 end
49 disp('stage 2'); //displaying second stage
50 disp(sest);
51 o=size(sest);
52 fin(1)=sest(1,1);
53 fin(2)=sest(1,2);
54 p=3;
55 for i=2:o(1,1) //removing redundancy in second stage
56     t=0;
57     ts=0;
58     for w=1:p-1
59         if fin(w)== sest(i,1) then
60             t=30;
61         end;
62         if fin(w) == sest(i,2) then
63             ts=40;
64         end
65     end
66     if t==0 then
67         fin(p)=sest(i,1);
68         finn(p-2)=i;
69         p=p+1;
70     end
71     if ts==0 then
72         fin(p)=sest(i,2)

```

```

73     finn(p-2)=i;
74     p=p+1;
75     end
76 end
77 ppp=size(finn) // selecting the prime implicants
78 l=1
79 fina(l)= finn(l);
80 for i=2:ppp(1,1)
81     q=0;
82     for b=1:l
83         if fina(b) == finn(i) then
84             q=89 ;
85         end
86     end
87     if q==0 then
88         fina(l+1)=finn(i);
89         l=l+1;
90         q=0;
91     end
92 end
93 kkk=size(fina);
94 i=1;
95 jj=0;
96 bi(1)=' ';
97 x(i)
98 po=1;
99 for k=1:kkk(1,1)+1
100 for p=1:3 // appending a string to make the
            expression
101     if p ~= posi(i) then
102         if p == 1 & x(i,p)==1 then
103             bi(po)=strcat([bi(po) 'A']);
104         elseif p== 1 &x(i,p)==0 then
105             bi(po)=strcat([bi(po) 'A' '']);
106         end
107         if p == 2 & x(i,p)==1 then
108             bi(po)=strcat([bi(po) 'B']);
109         elseif p== 2 &x(i,p)==0 then

```

```

110     bi(po)=strcat([bi(po) 'B' '']);
111     end
112     if p == 3 & x(i,p)==1 then
113     bi(po)=strcat([bi(po) 'C']);
114     elseif p== 3 &x(i,p)==0 then
115     bi(po)=strcat([bi(po) 'C' '']);
116     end
117     end
118 end
119 jj=jj+1;
120 if jj<=kkk(1,1) then
121 i=fina(jj);
122 bi(po)=strcat([bi(po) ' + ']);
123 end
124 end;
125 disp('The minimised expression is ');
126 disp(bi);

```

Scilab code Exa 3.14 Dynamic hard

```

1 //example 3.9
2 clc;
3 clear;
4 close;
5 c = [1 1 0 0 0 0 0 0]; //given values
6 a= [1 1 1 1 1 1 1];
7 b= [1 1 1 1 1 1 1];
8 for i=1:7
9     y1(i)=0
10    y2(i)=1
11    y3(i)=0
12    y4(i)=1
13    y(i)=0

```

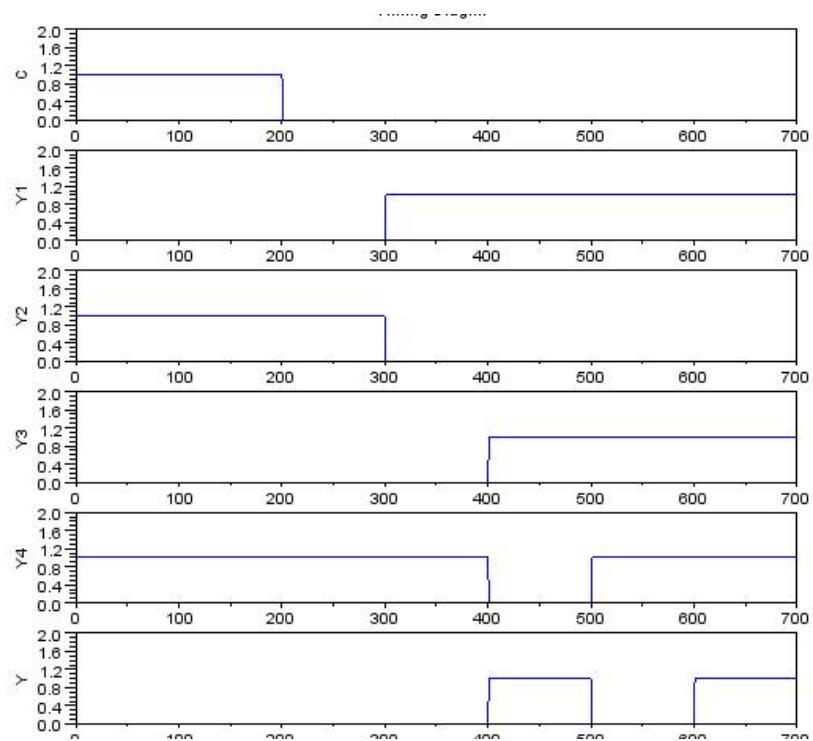


Figure 3.1: Dynamic hard

```

14 end
15 for(i=1: 7) // finding the Y values for next clock
    periods
16 y1(i+1) = bitcmp(c(i),1);
17 y2(i+1) = bitand(a(i),c(i));
18 end;
19 for i=1: 5
20 y3(i+2) = bitand(y1(i+1),b(i));
21 end;
22 for i=1:4
23 y4(i+3) = bitor(y3(i+2),y2(i+2));
24 end;
25 for i=1:3
26 y(i+4) = bitand(y4(i+3),y1(i+3));
27 end;
28 y11p=1;
29 y22p=1;
30 y33p=1;
31 y44p=1;
32 cp=1;
33 yf1p=1;
34 for i=1:7 // ploting all of them in to graph
35     if y1(i)==1 then
36         for o=1:100
37             y11(y11p)=1;
38             y11p=y11p+1;
39         end
40     else
41         for o=1:100
42             y11(y11p)=0;
43             y11p=y11p+1;
44         end
45     end
46     if y2(i)==1 then
47         for o=1:100
48             y21(y22p)=1;
49             y22p=y22p+1;
50         //z(bp)=3

```

```

51         end
52     else
53         for o=1:100
54             y21(y22p)=0;
55             y22p=y22p+1;
56             //z(bp)=3
57         end
58     end
59     if y3(i)==1 then
60         for o=1:100
61             y31(y33p)=1;
62             y33p=y33p+1;
63             //z(bp)=3
64         end
65     else
66         for o=1:100
67             y31(y33p)=0;
68             y33p=y33p+1;
69             //z(bp)=3
70         end
71     end
72     if y4(i)==1 then
73         for o=1:100
74             y41(y44p)=1;
75             y44p=y44p+1;
76             //z(bp)=3
77
78         end
79     else
80         for o=1:100
81             y41(y44p)=0;
82             y44p=y44p+1;
83             //z(bp)=3
84         end
85     end
86     if c(i)==1 then
87         for o=1:100
88             c1(cp)=1;

```

```

89         cp=cp+1;
90     end
91 else
92     for o=1:100
93         c1(cp)=0;
94         cp=cp+1;
95     end
96 end
97 if y(i)==1 then
98     for o=1:100
99         yf1(yf1p)=1;
100        yf1p=yf1p+1;
101    end
102 else
103     for o=1:100
104         yf1(yf1p)=0;
105         yf1p=yf1p+1;
106     end
107 end
108 end
109 z=[2 2]; //ploting the results
110 subplot(6,1,1);
111 title('Timing Diagram');
112 plot(c1);
113 plot(z);
114 ylabel('C');
115 subplot(6,1,2);
116 plot(y11);
117 ylabel('Y1');
118 plot(z);
119 subplot(6,1,3);
120 plot(y21);
121 ylabel('Y2');
122 plot(z);
123 subplot(6,1,4);
124 plot(z);
125 ylabel('Y3');
126 plot(y31);

```

```
127 subplot(6,1,5);
128 plot(z);
129 ylabel('Y4');
130 xlabel('Time in milli seconds');
131 plot(y41);
132 subplot(6,1,6);
133 plot(z);
134 ylabel('Y');
135 xlabel('Time in milli seconds');
136 plot(yf1);
```

Chapter 4

Data processing circuits

Scilab code Exa 4.1 4 to 1 mux using 2 to 1 mux

```
1 //example 4.1
2 clc;
3 clear;
4 disp('Logic equation for 2-to-1 Multiplexer :')
5 printf(' Y = A''D0 + AD1\n');
6 disp('Logic equation for 4-to-1 Multiplexer :')
7 printf(' Y = A''B''D0 + A''BD1 + AB''D2 + ABD3\n');
8 disp('This can be rewritten as ,')
9 printf(' Y= A''(B''D0 + BD1) + A(B''D2 + BD3)\n');
10 disp('Compare this with equation of 2-to-1 mux. We
      need two 2-to-1 multiplexer to realize the
      bracketed terms where B serves as select input.
      The output of these two multiplexers can be sent
      to a third multiplexer as data inputs where A
      serves as select input and we get the 4-to-1
      multiplexer.');
```

Scilab code Exa 4.2 Realizing boolean equation using 8 to 1 mux

```

1 //example 4.2
2 clc;
3 clear
4 a(1,1)=0 // taking input in this form 1 if A, 0 if A
' and 2 if no A in the term
5 a(1,2)=1
6 a(1,3)=2
7 a(2,1)=2
8 a(2,2)=0
9 a(2,3)=0
10 a(3,1)=1
11 a(3,2)=1
12 a(3,3)=1
13 p=3;
14 for i=1:3 // finding the minterms here
15     coun =0;
16     for j=1:3
17         if a(i,j)==2 then
18             coun = coun+1
19         end
20     end
21     if coun == 2 then
22         p=p+3
23     else if coun==1 then
24         p=p+1
25     end
26 end
27 end
28 n=4;
29 for m=4:p
30     for l=1:3
31         a(m,l)=0;
32     end
33 end
34 for i= 1:p
35     for j=1:3
36         if a(i,j) ==2 then
37             for k=1:3

```

```

38           a(n,k)=a(i,k)
39       end
40   a(i,j) = 0;
41   a(n,j)=1;
42   n=n+1;
43   end
44 end
45 end
46 for h=1:p
47   f(h)=0
48   c=2;
49 for m=1:3 //finding equivlent decimal values for
the minterms
50   f(h)= f(h) + a(h,m)*(2^c);
51   c=c-1;
52 end
53 end
54 disp('The min terms are :') //displaying the min
terms
55 disp(' A B C')
56 disp(a)
57 l=1
58 o(1,1)= f(l); // removing the repetitions in
minterms
59 for i=2:p
60   q=0;
61   for b=1:l
62     if o(1,b) == f(i) then
63       q=89 ;
64     end
65   end
66   if q==0 then
67     o(1,l+1)=f(i);
68     l=l+1;
69     q=0;
70   end
71 end
72 disp('The following data lines are to be given ''1''
```

```
        and remaining should be given ''0'); //  
        displaying the decimal equivlent of minterms  
73 disp(o);  
74 disp('For a 4-1 mux, we should give D0 =C'',D1 = ''1  
'',D2 = C'' and D3 = C with A and B as data  
selector inputs '');
```

Scilab code Exa 4.3 32 to 1 mux using 16 to 1 and 2 to 1 muxes

```
1 //example 4.3  
2 clc;  
3 clear;  
4 m(1)=32; //tking the given values  
5 m(2)=log2(m(1)) // making necessary calculations  
6 m(3)=m(2)-1;  
7 m(4)=m(1)/2;  
8 printf('A %d-to-1 multiplexer requires ',m(1));printf  
(' %d select lines , The lower ',m(2));printf(' %d  
select lines choose ',m(3));printf(' %d-to-1  
multiplexer outputs. The 2-to-1 multiplexers  
chooses one of the outpt of two ',m(4));printf('  
%d-to-1 multiplexers depending on what appears in  
the ',m(4));printf(' %dth select line.', m(2));  
//displaying the result
```

Scilab code Exa 4.4 74154 IC y12

```
1 //example 4.4  
2 clc;  
3 clear;  
4 r= input('Enter the value of R (0 or 1) :'); //  
    accepting the inputs from the user  
5 t= input('Enter the value of T (0 or 1) :');
```

```

6 sel = input('Enter the values of ABCD :');
7 strb = bitcmp(bitand(r,t),1);
8 if strb==0 then // checking whether strobe is high
    or low
9   if sel ==1100 then
10     y='The two pulses are steered to the Y12
        output';
11   else
12     y='The output Y12 remains in the High state'
        ;
13   end
14 else
15   y='The output Y12 remains in the High state';
16 end
17 disp(y) //displaying result

```

Scilab code Exa 4.7 realizing boolean equation using 3 to 8 decoder

```

1 //example 4.7
2 clc;
3 clear;
4 n=input('Enter the no.of terms in ur expression :');
    //accepting input from user
5 for i=1:n
6 a(1,i)=input('Enter the term (0-9) :');
7 end;
8 disp ('Since at the decoder output we get all the
        minterms we use them to get the required boolean
        functions by giving the output lines numbered ')
    ;
9 disp(a);      //displaying the result
10 disp('to a mlti-input OR gate.');

```

Scilab code Exa 4.8 current in LED

```
1 //example 4.8
2 clc;
3 clear;
4 //r=input('Enter the values of resistance in Kohms
5 //      :');
6 //v=input('Enter the forward voltage drop of LED(in
7 //      volts) :');
8 r=1//taking the given values for r and v
9 v=2
10 i=5-v/r; //calculating I
11 printf('The current through a LED is : %f mA', i);
12 //displaying I
```

Scilab code Exa 4.9 which LED lights up for given input conditions

```
1 //example 4.9
2 clc;
3 clear;
4
5 sel = input(' Enter the values of ABCD :');
6 a=sel;
7 q=1;
8 while(a>0) // finding the decimal equivlent
9     r=modulo(a,10);
10    b(1,q)=r;
11    a=a/10;
12    a=floor(a);
13    q=q+1;
14 end
15 f=0;
16 for m=1:q-1
17     c=m-1
18     f = f + b(1,m)*(2^c);
```

```

19 end
20 if f >9 then //checking the invalid condition
21     disp('Its a invalid input. Therefore ,none of the
          LEDs is on because all outputs lines are
          high' );
22 else //displaying the LED no if the inputs are
      valid
23     printf('\n LED %d lights up all. All other LEDs
          remain off because the other outputs are high
          . ',f);
24 end

```

Scilab code Exa 4.10 output of 74147 when button 6 is pressed

```

1 //example 4.10
2 clc;
3 clear;
4 //sel= input('Enter which is pressed(1 - 9) : ');
5 sel=6;
6 aa=sel;
7 for i=4:-1:1 //converting the sel input to binary
      notation
8     a(1,i)=modulo(aa,2);
9     b(1,i)=bitcmp(a(1,i),1);
10    aa=aa/2;
11    aa=floor(aa);
12 end
13 printf('When switch %d is pressed the ABCD output is
      : ',sel);
14 disp(b); //displaying the result
15 printf(' Which is equivalent to %d when the output
      is complimented.In the output above a ''0''
      represents a LOW and a ''1'' represents a HIGH. ,
      sel );

```

check Appendix AP 9 for dependency:

`kmapsx.sci`

check Appendix AP 2 for dependency:

`noof.sci`

Scilab code Exa 4.11 priority encoder

```
1 //example 4.11
2 //uses functions kmap.sci and noof.sci so run them
   before running this program ..
3 clc;
4 s=[0 1 1 1 1];
5 x1=[0 1 0 0 0];
6 x2=[0 0 1 0 0];
7 x3=[0 0 0 1 0];
8 for i=1:5
9     if s(i)==1 then // finding output A and B
10         if x1(i) == 1 then
11             a(i)=0;
12             b(i)=1;
13         elseif x2(i) == 1 then
14             a(i)=1;
15             b(i)=0;
16         elseif x3(i) == 1 then
17             a(i)=1;
18             b(i)=1;
19         else
20             a(i)=0;
21             b(i)=0;
22         end
23     else
24         a(i)=0;
25         b(i)=0;
```

```

26 end
27 end
28 for i = 1 : 5      // printin the state table
29     Y(i,1)=s(i);
30     Y(i,2)=x1(i);
31     Y(i,3)=x2(i);
32     Y(i,4)=x3(i);
33     Y(i,5)=a(i);
34     Y(i,6)=b(i);
35 end
36 disp('           Input           Output ');
37 disp('   S   X1   X2   X3   A   B ');
38 disp(Y);
39 kmp =[0 0 0 0;0 0 0 1 ;0 0 0 1;0 0 0 1]; //finding
        minimized expressin using 4-variable kmap
40 disp("The minimal expression of A from the
        following Kmap is :");
41 kmapsx(kmp);
42 kmp=[0 0 1 0;0 0 1 1 ;0 0 1 0;0 0 1 0]; //finding
        minimized expressin using 4-variable
        kmap
43 printf('\n');
44 disp( 'The minimal expression of B from the
        following Kmap is :')
45 kmapsx(kmp);

```

Chapter 5

Number Systems and Codes

Scilab code Exa 5.1 Binary to decimal conversion

```
1 //Example 5.1
2 clc
3 // clears the command window
4 clear
5 // clears all the variables
6 p=1;
7 // initialising variables
8 q=1;
9 z=0;
10 b=0;
11 w=0;
12 f=0;
13 format('v',18);
14 //increasing the precision to 18 .
15 //bin= input ("Enter the binary no to be converted
16 // to its decimal equivalent : ") // accepting
17 // the binary input from user
```

```

12 bin=110.001;
13 d= modulo(bin,1);

           //separating the decimal part and the integer
           part
14 d=d*10^10;
15 a=floor(bin);

           //removing the decimal part
16 while(a>0)

           //Loop to take the binary bits of integer in to a
           matrix
17 r=modulo(a,10);
18 b(1,q)=r;
19 a=a/10;
20 a=floor(a);
21 q=q+1;
22 end
23 for m=1:q-1

           //multipling the bits of integer with their
           position values and adding
24     c=m-1;
25     f = f + b(1,m)*(2^c);
26 end
27 while(d>0)

           //Loop to take the binary bits of decimal in to a
           matrix
28 e=modulo(d,2)
29 w(1,p)=e
30 d=d/10;
31 d=floor(d)
32 p=p+1;
33 end
34 for n=1:p-1

```

```

        // multiplying the bits of decimal with their
        position values and adding
35     z=z+w(1,n)*(0.5)^(11-n);
36 end
37 z=z*10000;

        // rounding off to 4 decimal values
38 z=round(z);
39 z=z/10000;
40 printf("The Decimal equivalent of the Binary number
        given is = %f",f+z);           //Displaying the final
        result

```

Scilab code Exa 5.2 Binary to decimal conversion

```

1 //Example 5.2
2 clc

        // clears the command window
3 clear

        // clears all the variables
4 p=1;

        // initialising variables
5 q=1;
6 z=0;
7 b=0;
8 w=0;
9 f=0;
10 format('v',18);

        //increasing the precision to 18 .
11 //bin= input ("Enter the binary no to be converted
        to its decimal equivalent : ")    // accepting

```

```

        the binary input from user
12 bin=1011.11;
13 d= modulo(bin,1);

        //separating the decimal part and the integer
        part
14 d=d*10^10;
15 a=floor(bin);

        //removing the decimal part
16 while(a>0)

        //Loop to take the binary bits of integer in to a
        matrix
17 r=modulo(a,10);
18 b(1,q)=r;
19 a=a/10;
20 a=floor(a);
21 q=q+1;
22 end
23 for m=1:q-1

        //multipliying the bits of integer with their
        position values and adding
24 c=m-1;
25 f = f + b(1,m)*(2^c);
26 end
27 while(d>0)

        //Loop to take the binary bits of decimal in to a
        matrix
28 e=modulo(d,2)
29 w(1,p)=e
30 d=d/10;
31 d=floor(d)
32 p=p+1;
33 end
34 for n=1:p-1
```

```

        // multipliyng the bits of decimal with their
        position values and adding
35     z=z+w(1,n)*(0.5)^(11-n);
36 end
37 z=z*10000;

        // rounding of to 4 decimal values
38 z=round(z);
39 z=z/10000;
40 printf("The Decimal equivalent of the Binary number
        given is = %f",f+z);

        // Displaying the final result

```

Scilab code Exa 5.3 decimal equivalent of 2 Mb

```

1 //Example 5.3
2 clc

        // clears the command window .
3 clear

        // clears all the variables .
4 format('v',18);

        // increasing the precision to 18 .
5 n=2; // given 2 mb
6 dec = n * 2^20 ;
7 printf("The decimal equivalent of 2Mb is = %f ",dec)
;

        // displaying the value .

```

Scilab code Exa 5.4 Decimal to binary conversion

```
1 //Example 5.3
2 clc
3
4 // clears the command window
5 clear
6
7 // clears all the variables
8 q=0;
9 b=0;
10 s=0;
11 format('v',18);
12
13 //increasing the precision to 18 .
14 //a=input("Enter the decimal no to be converted to
15 // its binary equivalent : ");           // accepting
16 // the decimal input from user
17 a=23.6;
18 d=modulo(a,1);
19
20 //separating the decimal part and the integer
21 // part
22 a=floor(a);
23
24 //removing the decimal part
25
26 while(a>0)
27
28 //taking integer part in to a matrix and convert
29 // to equivalent binary
30 x=modulo(a,2);
31 b= b + (10^q)*x;
32 a=a/2;
```

```

17      a=floor(a);
18      q=q+1;
19  end
20
21
22
23 for i=1:10

    // For values after decimal point converting to
    binary
24     d=d*2;
25     q=floor(d);
26     s=s+q/(10^i);
27     if d>=1 then
28         d=d-1;
29     end
30 end
31 k=b+s;
32 printf("The binary equivalent of the given decimal
number is = %f",k);

// displaying the final result.

```

Scilab code Exa 5.5 Binary number having all ones

```

1 //Example 5.5
2 clc

    //clears the command window
3 clear

    //clears all the variables
4 format('v',18)

//increasing the precision

```

```
5 n=32; // given 32 1's
6 dec=2^n - 1 ;
7 printf("The decimal equivalent of 32 bit number with
        all 1s is = %f ",dec); // displaying the
        result
```

Scilab code Exa 5.6 Decimal to binary conversion

```
1 //Example 5.6
2 clc
3 //clears the command window
4 clear
5 //clears all the variables
6 q=0;
7 b=0;
8 s=0;
9 format('v',18);
10 //increasing the precision to 18 .
11 //a=input("Enter the decimal no to be converted to
        its binary equivalent : "); // accepting
        the decimal input from user
12 a=363;
13 //taking the value given in problem
14 d=modulo(a,1);
15 //separating the decimal part and the integer
        part
16 a=floor(a);
17 //removing the decimal part
```

12

```

13 while(a>0)

    //taking integer part in to a matrix and convert
    to equivalent binary

14     x=modulo(a,2);
15     b= b + (10^q)*x;
16     a=a/2;
17     a=floor(a);
18     q=q+1;
19 end
20
21
22
23 for i=1:10

    // For values after decimal point converting to
    binary

24     d=d*2;
25     q=floor(d);
26     s=s+q/(10^i);
27     if d>=1 then
28         d=d-1;
29     end
30 end
31 k=b+s;
32 disp("The give decimal number is 363")
33 printf(" The binary equivalent of the given decimal
        number is = %f",k);

    // displaying the final result.

```

Scilab code Exa 5.7 binary to hexadecimal

```

1 //Example 5.7
2 clc

```

```

        // clears the command window
3  clear

        // clears all the variables
4  q=1;
5  b=0;
6  f=0;
7  bin=input("Enter the 8-bit binary address :");
                           // Taking the input
               binary bits from the user
8  a=floor(bin)
9  while(a>0)

        //Loop to take the binary bits in to a matrix(
array)
10    r=modulo(a,10);
11    b(1,q)=r;
12    a=a/10;
13    a=floor(a);
14    q=q+1;
15 end
16 for m=1:q-1

        // converrtting to decimal
17    c=m-1;
18    f = f + b(1,m)*(2^c);
19 end
20 c=dec2hex(f);
21 printf("The hexadecimal equivalent of the given
binary number is : %s",c);           //
displaying the value

```

Scilab code Exa 5.8 hexadecimal to decimal

```

1 //Example 5.8
2 clc

    // clear the command window
3 clear

    //clear the variables
4 a=input("Enter the hexadecimal number to be
        converted into decimal(enter in a single
        quotation) : ")           // taking the input from
        user
5 d=hex2dec(a);
6 printf("The decimal equivalent is : %d",d);

    //displaying the output

```

Scilab code Exa 5.9 decimal to hexadecimal and binary

```

1 //Example 5.9
2 clc                                // clears the
    command window
3 clear                                // clears
    the variables
4 q=0;
5 b=0;
6 //a=input(" enter the decimal no:")
7 a=65535;                            //
    giving the value specified in the problem
8 temp =a;                            //
9 format('v',18)                      //
    increasing the precision to 18
10 a=floor(a);
11 h=dec2hex(a);
12 while(a>0)                         //
    converting to binary

```

```

13     x=modulo(a,2);
14     b= b + (10^q)*x;
15     a=a/2;
16     a=floor(a);
17     q=q+1;
18 end
19 printf("Given decimal number is : %d\n",temp)
20 printf('The hexadecimal equivalent is = %s\n',h);
21 // displaying the results
21 printf('The binary equivalent is = %f',b );

```

Scilab code Exa 5.10 decimal to hexadecimal and binary

```

1 //Example 5.10
2 clc // clears the
      command window
3 clear // clears
      the variables
4 q=0;
5 b=0;
6 //a=input(" enter the decimal no:")
7 a=56000; // giving the value specified in the problem
8 temp=a;
9 format('v',18) // increasing the precision to 18
10 a=floor(a);
11 h=dec2hex(a);
12 while(a>0) // converting to binary
13     x=modulo(a,2);
14     b= b + (10^q)*x;
15     a=a/2;
16     a=floor(a);

```

```

17     q=q+1;
18 end
19 printf("Given decimal number is : %d\n",temp)
20 printf("The hexadecimal equivalent is = %s\n",h)
21 //displaying the results
22 printf("The binary equivalent is = %f\n",b);

```

Scilab code Exa 5.11 decimal to hexadecimal and binary

```

1 //chapter 5
2 //Example 5.11
3 //Q. convert decimal numbers to its hexadecimal and
   binary equivalent ?
4 //solution :
5 clc                                     // clears the
   command window
6 clear                                    // clears
   the variables
7 q=0;
8 b=0;
9 a=input("Enter the decimal no:")          // Enter
   the decimal nuber
10 format('v',18)                           //
   increasing the precision to 18
11 a=floor(a);
12 h=dec2hex(a);
13 while(a>0)                             //
   converting to binary
14     x=modulo(a,2);
15     b= b + (10^q)*x;
16     a=a/2;
17     a=floor(a);
18     q=q+1;
19 end
20 printf("The hexadecimal equivalent is = %s\n",h)

```

```
21 // displaying the results
22 printf("The binary equivalent is = %f", b)
```

Chapter 6

Arithmetic Circuits

Scilab code Exa 6.1 8bit binary adder

```
1 //exmple 6.1
2 clc;
3 clear;
4 //a=input(" enter the first 8 bit number :");
5 //b=input(" enter the second 8 bit number :");
6 a=01010111; // taking given inputs
7 b=00110101;
8 for i=1:8
9     a1(i)=modulo(a,10);
10    a=a/10;
11    a=round(a);
12    b1(i)=modulo(b,10);
13    b=b/10;
14    b=round(b);
15 end
16 car(1)=0;
17 for i=1:8      // adding both the inputs (binary
18     addition)
19     c1(i)=car(i)+a1(i)+ b1(i);
20     if c1(i)== 2 then
21         car(i+1)= 1;
```

```

21         c1(i)=0;
22     elseif c1(i)==3 then
23         car(i+1)= 1;
24         c1(i)=1;
25     else
26         car(i+1)=0;
27     end
28 end
29 c1(9)=car(9);
30 re=0;
31 format('v',18);
32 for i=1:9
33     re=re+(c1(i)*(10^(i-1)))
34 end
35 printf('The sum of given two binary numbers is %d\n',
36 ,re );
37 q=1;
38 b=0;
39 f=0;
40 a=re;
41 while(a>0)           // converting the result to a
42     hexadeciml no
43     r=modulo(a,10);
44     b(1,q)=r;
45     a=a/10;
46     a=floor(a);
47     q=q+1;
48 end
49 for m=1:q-1
50     c=m-1;
51     f = f + b(1,m)*(2^c);
52 end
53 hex=dec2hex(f);
54 printf(' The sum in hexadecimal notation is %s \n',
55 hex); //displaying result

```

Scilab code Exa 6.2 16 bit binary adder

```
1 //example 6.2
2 clc;
3 clear;
4 //a=input(" enter the first 16 bit binary number :");
5 //b=input(" enter the second 16 bit binarynumber :");
6 a=000011110101100;
7 b=001110000111111;
8 for i=1:16
9     a1(i)=modulo(a,10);
10    a=a/10;
11    a=round(a);
12    b1(i)=modulo(b,10);
13    b=b/10;
14    b=round(b);
15 end
16 car(1)=0;
17 for i=1:16      /// adding both the 16-bit inputs (
18     binary addition)
19     c1(i)=car(i)+a1(i)+ b1(i);
20     if c1(i)== 2 then
21         car(i+1)= 1;
22         c1(i)=0;
23     elseif c1(i)==3 then
24         car(i+1)= 1;
25         c1(i)=1;
26     else
27         car(i+1)=0;
28     end
29 c1(17)=car(17);
30 re=0;
31 format('v',25);
```

```

32 for i=1:17
33     re=re+(c1(i)*(10^(i-1)))
34 end
35 printf('The sum of given two binary numbers is %f\n',
36 ,re );
36 q=1;
37 b=0;
38 f=0;
39 a=re;
40 while(a>0)      // converting the result to a
41     hexadecim no
41     r=modulo(a,10);
42     b(1,q)=r;
43     a=a/10;
44     a=floor(a);
45     q=q+1;
46 end
47 for m=1:q-1
48     c=m-1
49     f = f + b(1,m)*(2^c);
50 end
51 hex=dec2hex(f);
52 printf(' Sum in decimal notation is %d\n',f);
53 printf(' Sum in hexadecimal notation is %s \n',hex);
53 //displaying result

```

Scilab code Exa 6.3 first generation microcomputers addition

```

1 //example 6.3
2 clc;
3 clear;
4 //a=input(" enter the first 8 bit number :");
5 //b=input(" enter the second 8 bit number :");
6 a=000011110101100;
7 b=001110000111111;

```

```

8  for i=1:16
9      a1(i)=modulo(a,10);
10     a=a/10;
11     a=round(a);
12     b1(i)=modulo(b,10);
13     b=b/10;
14     b=round(b);
15 end
16 car(1)=0;
17 for i=1:8
18     c1(i)=car(i)+a1(i)+ b1(i); // adding the
        Higher bytes
19     if c1(i)== 2 then
20         car(i+1)= 1;
21         c1(i)=0;
22     elseif c1(i)==3 then
23         car(i+1)= 1;
24         c1(i)=1;
25     else
26         car(i+1)=0;
27     end
28 end
29 c1(9)=car(9)
30 re=0;
31 format('v',18);
32 for i=1:9
33     re=re+(c1(i)*(10^(i-1)))
34 end
35
36 printf('The sum of lower bytes of two binary numbers
        is %d\n',re );
37 printf(' with a carry is %d\n',car(9));
38 re=re-(c1(9)*(10^8))
39 for i=9:16 // adding the Higher bytes
40     c1(i)=car(i)+a1(i)+ b1(i);
41     if c1(i)== 2 then
42         car(i+1)= 1;
43         c1(i)=0;

```

```

44     elseif c1(i)==3 then
45         car(i+1)= 1;
46         c1(i)=1;
47     else
48         car(i+1)=0;
49     end
50 end
51 c1(17)=car(17);
52 format('v',25);
53 ree=0;
54 for i=9:17
55     ree=ree+(c1(i)*(10^(i-9)));
56 end
57 for i=9:17
58     re=re+(c1(i)*(10^(i-1)))
59 end
60 printf(' The sum of upper bytes of the given
       numbers is %d\n',ree);
61 printf(' with a carry is %d\n',car(17)); // 
       displaying results
62 printf(' The total sum is %f',re );

```

Scilab code Exa 6.4 binary subtraction

```

1 //exmple 6.4
2 clc;
3 clear;
4 a=0;
5 b=0;
6 q=0;
7 //bb=input(" Enter the first no (in decimal) :");
8 //aa=input(" Enter the number from which first no
       has to substracted:");
9 aa=200; // taking the given input
10 bb=125;

```

```

11 while(aa>0)      // converting the inputs in to binary
12     numbers
13     x=modulo(aa,2);
14     a= a + (10^q)*x;
15     aa=aa/2;
16     aa=floor(aa);
17     q=q+1;
18 end
19 q=0;
20 while(bb>0)
21     x=modulo(bb,2);
22     b= b + (10^q)*x;
23     bb=bb/2;
24     bb=floor(bb);
25     q=q+1;
26 end
27 printf(' \nThe binary equivalent of first no is %f\n
28 ,b);
29 printf(' The binary equivalent of secnd no is %f\n\n
30 ,a);
31 for i=1:40
32     a1(i)=modulo(a,10);
33     a=a/10;
34     a=round(a);
35     b1(i)=modulo(b,10);
36     b=b/10;
37     b=round(b);
38 end
39 bro(1)=0;
40 for i=1:40
41     c1(i)=a1(i)- b1(i)-bro(i); // finding the
42         difference of the given inputs
43     if c1(i)== -1 then
44         bro(i+1)= 1;
45         c1(i)=1;
46     elseif c1(i)==-2 then
47         bro(i+1)= 1;
48         c1(i)=0;

```

```

45     else
46         bro(i+1)=0;
47     end
48
49 end
50 re=0;
51 format('v',18);
52 for i=1:40
53     re=re+(c1(i)*(10^(i-1)))
54 end
55 printf(' The difference of given two numbers is %f\n\
      ',re );
56 q=1;
57 b=0;
58 f=0;
59 a=re;
60 while(a>0)
61     r=modulo(a,10);
62     b(1,q)=r;
63     a=a/10;
64     a=floor(a);
65     q=q+1;
66 end
67 for m=1:q-1
68     c=m-1
69     f = f + b(1,m)*(2^c);
70 end
71 hex=dec2hex(f);
72 printf(' Sum in decimal notation is %d\n\n',f); // 
    displaying the results
73 printf(' Sum in hexadecimal notation is %s \n',hex);

```

Scilab code Exa 6.5 adding 8 bit unsigned numbers

1 //example 6.5

```

2
3 clc;
4 clear;
5 a=0;
6 b=0;
7 q=0;
8
9 //aa=input(" Enter the first no (in decimal) :");
10 //bb=input(" Enter the number from which first no
11 has to substracted :");
11 aa=150;
12 bb=85;
13 while(aa>0)           // converting the inputs in
14     to binary numbers
15     x=modulo(aa,2);
16     a= a + (10^q)*x;
17     aa=aa/2;
18     aa=floor(aa);
19     q=q+1;
20 end
21 q=0;
21 while(bb>0)
22     x=modulo(bb,2);
23     b= b + (10^q)*x;
24     bb=bb/2;
25     bb=floor(bb);
26     q=q+1;
27 end
28 printf(' \n The binary equivalent of first no is %f\n
29 n\n',a);
29 printf(' The binary equivalent of secnd no is %f\n\n
30 ,b);
30 for i=1:40
31     a1(i)=modulo(a,10);
32     a=a/10;
33     a=round(a);
34     b1(i)=modulo(b,10);
35     b=b/10;

```

```

36     b=round(b);
37 end
38
39 car(1)=0;
40 for i=1:40
41     c1(i)=car(i)+a1(i)+ b1(i); // addng both the
        inputs
42     if c1(i)== 2 then
43         car(i+1)= 1;
44         c1(i)=0;
45     elseif c1(i)==3 then
46         car(i+1)= 1;
47         c1(i)=1;
48     else
49         car(i+1)=0;
50     end
51 end
52 c1(41)=car(41);
53 re=0;
54 format('v',18);
55 for i=1:41
56     re=re+(c1(i)*(10^(i-1)))
57 end
58 printf(' The sum of given two binary numbers is %f\n
        \n',re );
59 q=1;
60 b=0;
61 f=0;
62 a=re;
63 while(a>0)
64     r=modulo(a,10);
65     b(1,q)=r;
66     a=a/10;
67     a=floor(a);
68     q=q+1;
69 end
70 for m=1:q-1
71     c=m-1;

```

```

72     f = f + b(1,m)*(2^c);
73 end
74 printf(' Sum in decimal notation is %d\n\n',f); // 
    displaying results
75 hex=dec2hex(f);
76 printf(' The sum in hexadecimal notation is %sH \n',
    hex);

```

Scilab code Exa 6.6 subtraction of unsigned numbers

```

1 //exmple 6.6
2 clc;
3 clear;
4 a=0;
5 b=0;
6 q=0;
7 //bb=input(" Enter the first no (in decimal) :");
8 //aa=input(" Enter the number from which first no
    has to substracted :");
9 aa=150;
10 bb=85;
11 while(aa>0) //// converting the inputs in to binary
    numbers
12     x=modulo(aa,2);
13     a= a + (10^q)*x;
14     aa=aa/2;
15     aa=floor(aa);
16     q=q+1;
17 end
18 nn=a
19 q=0;
20 while(bb>0)
21     x=modulo(bb,2);
22     b= b + (10^q)*x;
23     bb=bb/2;

```

```

24      bb=floor(bb);
25      q=q+1;
26  end
27 printf(' \nThe binary equivalent of first no is %f\n
28           ',b);
28 printf(' The binary equivalent of secnd no is %f\n\n
29           ',a);
29 for i=1:40
30     a1(i)=modulo(a,10);
31     a=a/10;
32     a=round(a);
33     b1(i)=modulo(b,10);
34     b=b/10;
35     b=round(b);
36 end
37
38 bro(1)=0;
39 for i=1:40
40     c1(i)=a1(i)- b1(i)-bro(i);
41     if c1(i)== -1 then
42         bro(i+1)= 1;
43         c1(i)=1;
44     elseif c1(i)==-2 then
45         bro(i+1)= 1;
46         c1(i)=0;
47     else
48         bro(i+1)=0;
49     end
50
51 end
52 re=0;
53 format('v',18);
54 for i=1:40
55     re=re+(c1(i)*(10^(i-1)))
56 end
57 printf(' The diference of given two numbers is %f\n\
58           ',re );
58 q=1;

```

```

59 b=0;
60 f=0;
61 a=re;
62 while(a>0) // converting the binary result to
               decimal then to hexadecimal
63     r=modulo(a,10);
64     b(1,q)=r;
65     a=a/10;
66     a=floor(a);
67     q=q+1;
68 end
69 for m=1:q-1
70     c=m-1
71     f = f + b(1,m)*(2^c);
72 end
73 hex=dec2hex(f);
74 printf(' Sum in decimal notation is %d\n\n',f);
75 printf(' Sum in hexadecimal notation is %s \n',hex);

```

Scilab code Exa 6.7 overflow case

```

1 //example 6.7
2 clc;
3 clear;
4 a=0;
5 b=0;
6 q=0;
7 //aa=input(" Enter the first no (in decimal) :");
8 //bb=input(" Enter the number from which first no
               has to subtracted :");
9 aa=175;
10 bb=118;
11 while(aa>0)      // converting the inputs in to binary
                     numbers
12     x=modulo(aa,2);

```

```

13      a= a + (10^q)*x;
14      aa=aa/2;
15      aa=floor(aa);
16      q=q+1;
17 end
18 q=0;
19 while(bb>0)
20     x=modulo(bb ,2);
21     b= b + (10^q)*x;
22     bb=bb/2;
23     bb=floor(bb);
24     q=q+1;
25 end
26 printf(' \n The binary equivalent of first no is %f\n
n\n',a);
27 printf(' The binary equivalent of secnd no is %f\n\n
',b);
28 for i=1:8
29     a1(i)=modulo(a,10);
30     a=a/10;
31     a=round(a);
32     b1(i)=modulo(b,10);
33     b=b/10;
34     b=round(b);
35 end
36
37 car(1)=0;
38 for i=1:8
39     c1(i)=car(i)+a1(i)+ b1(i); //adding the binary
        numbers ( binary addtion)
40     if c1(i)== 2 then
41         car(i+1)= 1;
42         c1(i)=0;
43     elseif c1(i)==3 then
44         car(i+1)= 1;
45         c1(i)=1;
46     else
47         car(i+1)=0;

```

```

48     end
49 end
50 c1(9)=car(9);
51 re=0;
52 format('v',18);
53 for i=1:8
54     re=re+(c1(i)*(10^(i-1)))
55 end
56 printf('If only 8 bits are taken the result will be
      as shown below \n\n');
57 printf(' and the sum of given two binary numbers
      will be %f\n\n',re );
58 q=1;
59 b=0;
60 f=0;
61 a=re;
62 while(a>0) //converting the binary output to
      hexadecimal
63     r=modulo(a,10);
64     b(1,q)=r;
65     a=a/10;
66     a=floor(a);
67     q=q+1;
68 end
69 for m=1:q-1
70     c=m-1;
71     f = f + b(1,m)*(2^c);
72 end
73 printf(' Sum in decimal notation is %d\n\n',f);
74 hex=dec2hex(f);
75 printf(' The sum in hexadecimal notation is %sH \n',
      hex);
76 printf(' \n with an overflow of %d\n\n',car(9));

```

Scilab code Exa 6.8 2s compliment

```

1 //example 6.8
2 clc;
3 clear;
4 re=0;
5 aaa=input('enter the number(in decimal) :');//  

   taking the signed number
6 m=aaa;
7 if aaa<0 then
8     aa=-1*aaa;
9     else aa=aaa;
10 end
11 a=0;
12 q=0;
13 while(aa>0)           //converting from decimal to  

   binary
14     x=modulo(aa,2);
15     a= a + (10^q)*x;
16     aa=aa/2;
17     aa=floor(aa);
18     q=q+1;
19 end
20 mm=a;
21 for i=1:8
22     a1(i)=modulo(a,10);
23     a=a/10;
24     a=round(a);
25     b1(i)=0;
26 end
27 b1(1)=1;
28 if aaa<0 then // making two's complement if the  

   number is less than zero
29     for i=1:8
30         a1(i)=bitcmp(a1(i),1);
31     end
32     car(1)=0;
33 for i=1:8
34     c1(i)=car(i)+a1(i)+ b1(i); // adding one (as a  

   part of finding 2's compliment

```

```

35      if c1(i)== 2 then
36          car(i+1)= 1;
37          c1(i)=0;
38      elseif c1(i)==3 then
39          car(i+1)= 1;
40          c1(i)=1;
41      else
42          car(i+1)=0;
43      end;
44 end;
45 c1(9)=car(9);
46 re=0;
47 format('v',18);
48 for i=1:9
49     re=re+(c1(i)*(10^(i-1)))
50 end;
51 printf('\nThe binary contents are %d\n\n',
52       re );
52 else
53     re=mm;
54 end;
55 if(aaa>0)
56     printf('\nThe biary contents are %d\n\n',mm);
57 end;
58 q=1;
59 b=0;
60 f=0;
61 a=re;
62 while(a>0) // converting the result to decimal then
63     to hexadecimal
63     r=modulo(a,10);
64     b(1,q)=r;
65     a=a/10;
66     a=floor(a);
67     q=q+1;
68 end
69 for m=1:q-1
70     c=m-1

```

```

71     f = f + b(1,m)*(2^c);
72 end
73 hex=dec2hex(f);
74 printf('The Hexadecimal contents are %sH',hex) ;//  

    displayin the result

```

Scilab code Exa 6.9 2s compliment

```

1 //example 6.9
2 clc;
3 clear;
4 //aaa=input( ' enter the number( in decimal) : ');
5 aaa=-19750 // given input
6 aa=-1*aaa;
7 format( 'v' ,18);
8 a=0;
9 q=0;
10 while(aa>0)           // converting it to binary
11     x=modulo(aa,2);
12     a= a + (10^q)*x;
13     aa=aa/2;
14     aa=floor(aa);
15     q=q+1;
16 end
17 for i=1:16
18     a1(i)=modulo(a,10);
19     a=a/10;
20     a=round(a);
21     b1(i)=0;
22 end
23 b1(1)=1;
24 for i=1:16           // finding the 2's
    compliment
25     a1(i)=bitcmp(a1(i),1);
26 end

```

```

27      car(1)=0;
28  for i=1:16
29      c1(i)=car(i)+a1(i)+ b1(i);
30      if c1(i)== 2 then
31          car(i+1)= 1;
32          c1(i)=0;
33      elseif c1(i)==3 then
34          car(i+1)= 1;
35          c1(i)=1;
36      else
37          car(i+1)=0;
38      end;
39  end;
40 c1(17)=car(17);
41 re=0;
42      for i=1:17
43          re=re+(c1(i)*(10^(i-1)))
44      end;
45      printf ('\n The 2 ''s compliment is ');
46      disp(re);
47      q=1;
48 b=0;
49 f=0;
50 a=re;
51 while(a>0)    // converting to hexadecimal
52     r=modulo(a,10);
53     b(1,q)=r;
54     a=a/10;
55     a=floor(a);
56     q=q+1;
57 end
58 for m=1:q-1
59     c=m-1
60     f = f + b(1,m)*(2^c);
61 end
62 hex=dec2hex(f);
63 printf ('\n In Hexadecimal notation is %sH\n\n',hex)
; // displaying the result

```

```
64 disp('As the memory of a first generation  
microcumputer is orgnised in bytes . The lower  
byte is stored in 2000 address and the higher  
byte is stored in 2001 address.');
```

Scilab code Exa 6.10 2s compliment subtraction

```
1 //example 6.10  
2 clc;  
3 clear;  
4 format('v',18);  
5 //bb=input('enter the first number(in decimal):');  
6 //aaa=input('enter the second number(negative) :');  
7 aaa=-12618  
8 bb=18357;  
9 aa=-1*aaa;  
10 a=0;  
11 q=0;  
12 while(aa>0)           // finding the binary  
    equivalents  
13     x=modulo(aa,2);  
14     a= a + (10^q)*x;  
15     aa=aa/2;  
16     aa=floor(aa);  
17     q=q+1;  
18 end  
19 r=0;  
20 b=0;  
21 while(bb>0)  
22     x=modulo(bb,2);  
23     b= b + (10^r)*x;  
24     bb=bb/2;  
25     bb=floor(bb);  
26     r=r+1;  
27 end
```

```

28 m=b
29 for i=1:16
30     a1(i)=modulo(a,10);
31     a=a/10;
32     a=round(a);
33     p1(i)=0;
34     b1(i)=modulo(b,10);
35     b=b/10;
36     b=round(b);
37 end
38 p1(1)=1;
39 for i=1:16           // finding the 2's compliment
40     of second number
41         a1(i)=bitcmp(a1(i),1);
42         end
43 car(1)=0;
44 for i=1:16
45     c1(i)=car(i)+a1(i)+ p1(i);
46     if c1(i)== 2 then
47         car(i+1)= 1;
48         c1(i)=0;
49     elseif c1(i)==3 then
50         car(i+1)= 1;
51         c1(i)=1;
52     else
53         car(i+1)=0;
54     end;
55 end;
56 re=0;
57 for i=1:16
58     re=re+(c1(i)*(10^(i-1)))
59 end;
60 printf(' The binary representation of first
61         number is ');
62 disp(m);
63 printf(' The 2 ''s compliment of second
64         number is ');
65 disp(re);

```

```

63 a1=c1;
64 ar(1)=0;
65 for i=1:8
66     c1(i)=ar(i)+a1(i)+ b1(i); // addin both the
       numbers (binary addition)
67     if c1(i)== 2 then          // lower byte
68         ar(i+1)= 1;
69         c1(i)=0;
70     elseif c1(i)==3 then
71         ar(i+1)= 1;
72         c1(i)=1;
73     else
74         ar(i+1)=0;
75     end
76 end
77 c1(9)=ar(9)
78 re=0;
79 format('v',18);
80 for i=1:8
81     re=re+(c1(i)*(10^(i-1)))
82 end
83 printf(' The sum of lower bytes of two binary
       numbers is %d\n',re );
84 printf(' with a carry is %d\n',ar(9));
85 for i=9:16
86     c1(i)=ar(i)+a1(i)+ b1(i); // upper byte
87     if c1(i)== 2 then
88         ar(i+1)= 1;
89         c1(i)=0;
90     elseif c1(i)==3 then
91         ar(i+1)= 1;
92         c1(i)=1;
93     else
94         ar(i+1)=0;
95     end
96 end
97 c1(17)=ar(17);
98 format('v',25);

```

```

99  ree=0;
100 for i=9:16
101     ree=ree+(c1(i)*(10^(i-9)));
102 end
103 for i=9:16
104     re=re+(c1(i)*(10^(i-1)))
105 end
106 printf(' The sum of upper bytes of the given
107     numbers is %d\n',ree);
108 printf(' with a carry is %d\n',ar(17)); //displaying
109 disp(re);
110 printf(' with a carry %d',ar(17));

```

Scilab code Exa 6.12 final carry in a CLA

```

1 //exmple 6.12
2 clc;
3 clear;
4 //a=input('Enter the first number A (4 bit) :');
5 //b=input('Enter the first number B (4 bit) :');
6 a=1111; // given values for a and b
7 b=0001;
8 for i=1:4
9     a1(i)=modulo(a,10);
10    a=a/10;
11    a=round(a);
12    b1(i)=modulo(b,10);
13    b=b/10;
14    b=round(b);
15 end
16 for i=1:4 //finding the generate and propagate
17     values for ech bit
18     g(i)=bitand(a1(i),b1(i));

```

```
18     p(i)=bitor(a1(i),b1(i));
19 end
20 c(1)=0;
21 for i=1:4 // finding the carry
22     c(i+1)= bitor(g(i),bitand(p(i),c(i)));
23 end
24 printf('The final carry is C3 = %d', c(5)); //  
displaying the result
```

Chapter 7

Clocks and Timing Circuits

Scilab code Exa 7.1 clock cycle time

```
1 //example 7.1
2 clear;
3 clc;
4 //for 50 kHz clock
5 clk_fraq1 = 50000;
6 c_t_500 = 1000/clk_fraq1;
7 //for 8-MHz clock
8 clk_fraq2 = 8000000;
9 c_t_8 = 10000000/clk_fraq2;
10 printf('Cycle time for 500-kHz clock is %f
    milliseconds \n',c_t_500); //displaying results
11 printf(' Cycle time for 8-MHz clock is %f micro
    seconds',c_t_8);
```

Scilab code Exa 7.2 maximum clock frequency

```
1 //example 7.2
2 clc;
```

```
3 clear;
4 //prop_delay = input('Enter the propagation delay in
      nano seconds: ');
5 prop_dely=24; // taking the given input
6 format('v',18); //setting the precision
7 max_clk_frq = 1/prop_delay; // making necessary
      calculations
8 max_clk_frq = max_clk_frq*10^3;
9 printf('maximum clock frequency is %f KHz',
      max_clk_frq); // displaying the result
```

Scilab code Exa 7.3 frequency limits of the clock

```
1 //example 7.3
2 clc;
3 clear;
4 //ppm = input('Enter the stability in parts per
      million (PPM): ');
5 //clk_fraq = input('Enter the clock frequency in MHz
      : ');
6 ppm= 5//taking the given values
7 clk_fraq= 5
8 mill= clk_fraq; //making necessary calculations
9 pp = mill*ppm;
10 pp = round(pp);
11 clk_fraq = clk_fraq*10^6;
12 o(1,1)=clk_fraq-pp;
13 o(1,2)=clk_fraq+pp;
14 printf('The clock frequency will be somewhere
      between %d and %d Hz',o); //displaying the result
```

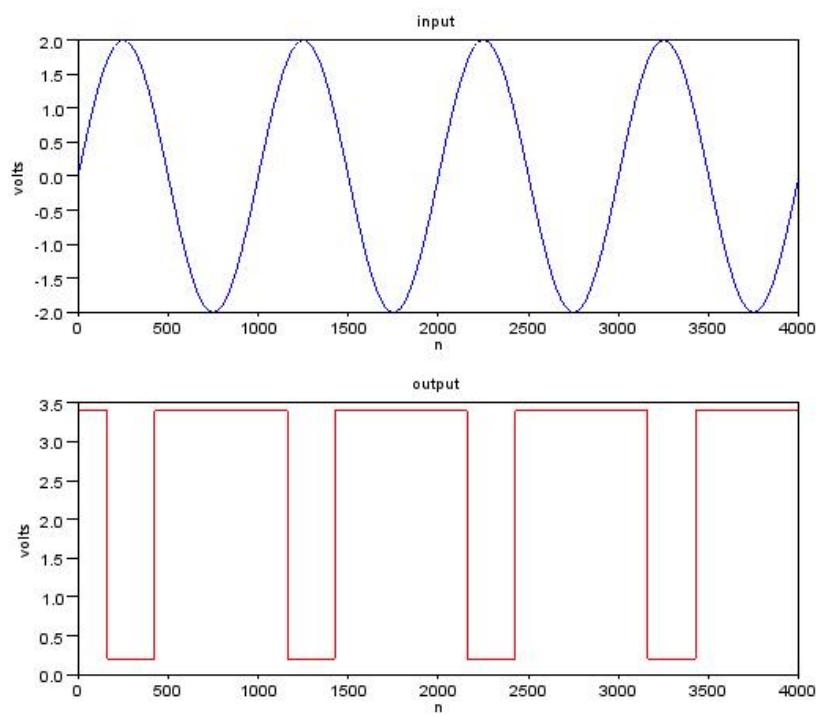


Figure 7.1: Schmitt trigger

Scilab code Exa 7.4 Schmitt trigger

```
1 //example 7.4
2 //schmitt trigger inverter
3 clear;
4 clc;
5 close;
6 //peak= input('Enter the peak voltage of sine wave
    in volts :');
7 //utp = input('Enter the upper trigger point in
    volts :');
8 //ltp = input('Enter the lower trigger point in
    volts :');
9 peak =2; // taking given values for inputs
10 utp=1.7;
11 ltp=0.9;
12 for i=1:4000
    sinn(i) = peak * sin(i*2*3.1416/1000); //drawing
        a sin wave with given amplitude
14 end
15 for j=1:4000      // making calculations to plot
    output
16     if modulo(j,1000)< 250 then
17         if sinn(j)<utp  then
18             result(j)=3.4;
19         else
20             result(j)=0.2;
21         end
22         elseif sinn(j)>ltp  then
23             result(j)=0.2
24         else
25             result(j)=3.4;
26     end
27 end
28 subplot(2,1,1)
29 plot(sinn); //ploting the input and output curves
30 xlabel('n');
31 title('input')
```

```
32 ylabel('volts');
33
34 subplot(2,1,2);
35 plot(result,'r');
36 xlabel('n');
37 title('output')
38 ylabel('volts');
```

Scilab code Exa 7.5 frequency of oscillation for 555 timer

```
1 //example 7.5
2 clc
3 clear
4 //Ra = input('Enter the value of the resistance RA
      in Kohms :');
5 //Rb = input('Enter the value of the resistance RB
      in Kohms :');
6 //C =input('Enter the value of the Capacitance C in
      micro farads :');
7 Ra=1 //taking the given input
8 Rb=1
9 C= 1 *10^-3
10 T= (Ra + 2*Rb)*C;
11 frq = 1.44 * (1/T); //substituting in the eqution
12 printf('Frequency of oscillation is %f KHz',frq); //
```

Scilab code Exa 7.6 finding Ra and C in 555 timer circuit

```
1 //example 7.6
2 clc
3 clear
```

```

4 //rb=input('Enter the value of the resistance RB in
      Kohms :');
5 //dc =input('Enter required duty cycle in % :');
6 //clk = input('Enter the provided clock frequency in
      MHz: ');
7 rb=0.75//taking the given values for input
8 dc=25
9 clk=1
10 ra = (rb*100/dc) - 2*rb;//making neccesary
      calculations
11 format('v',18);
12 t2 = dc/(clk*10^8);
13 C = t2/(693*rb)
14 C=C*10^12;
15 //C=round(C);
16 printf('The value of RA is %f Kohms\n',ra);//
      displaying the output
17 printf('The value of C is %f pico farads',C);

```

Scilab code Exa 7.7 output pulse width for the timer

```

1 //example 7.7
2 clc
3 clear
4 //Ra = input('Enter the value of the resistance RA
      in Kohms :');
5 //C =input('Enter the value of the Capacitance C in
      micro farads :');
6 Ra=10//taking given values
7 C=0.1
8 pw = 1.1*Ra*C //substituting in the equation
9 printf('pulse width is %f milliseconds',pw);//
      displaying result

```

Scilab code Exa 7.8 value of C necessary to change pulse width to given values

```
1 //example 7.8
2 clc
3 clear
4 //Ra = input('Enter the value of the resistance RA
    in Kohms :');
5 //pw =input('Enter the value of required pulse width
    in millisecondseconds :');
6 Ra=10//taking given values
7 pw=10
8 C = pw/(1.1*Ra); //substituting in the equation
9 printf('The required value of capacitance is %f
    microfarads',C); //displaying result
```

Scilab code Exa 7.9 monostable multivibrator

```
1 //example 7.9
2 clear
3 clc
4 close
5 //R = input('Enter the value of the resistance R in
    Kohms :');
6 //C =input('Enter the value of the Capacitance C in
    micro farads :');
7 sp = input('Enter the spacing between two input
    pulses in micro seconds :');
```

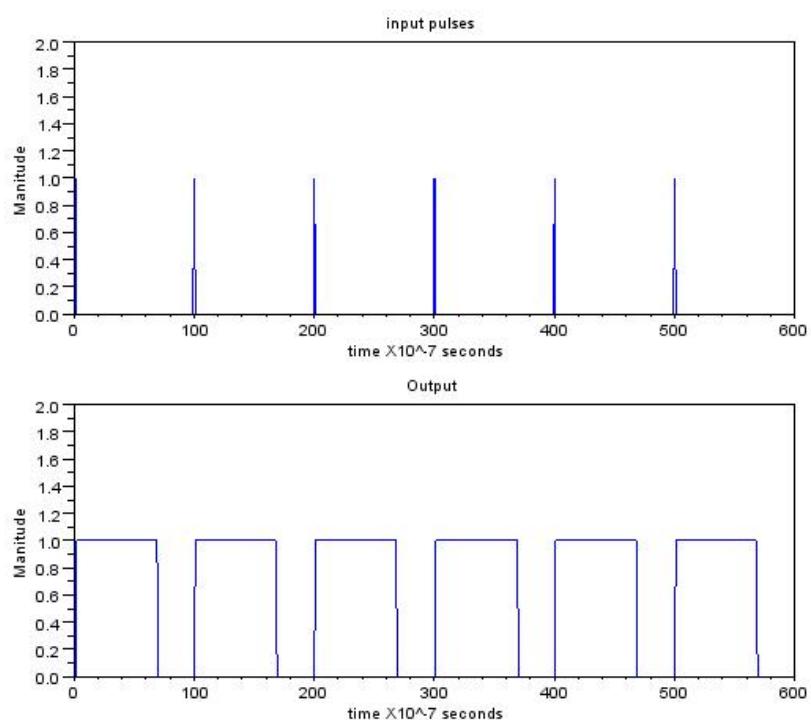


Figure 7.2: monostable multivibrator

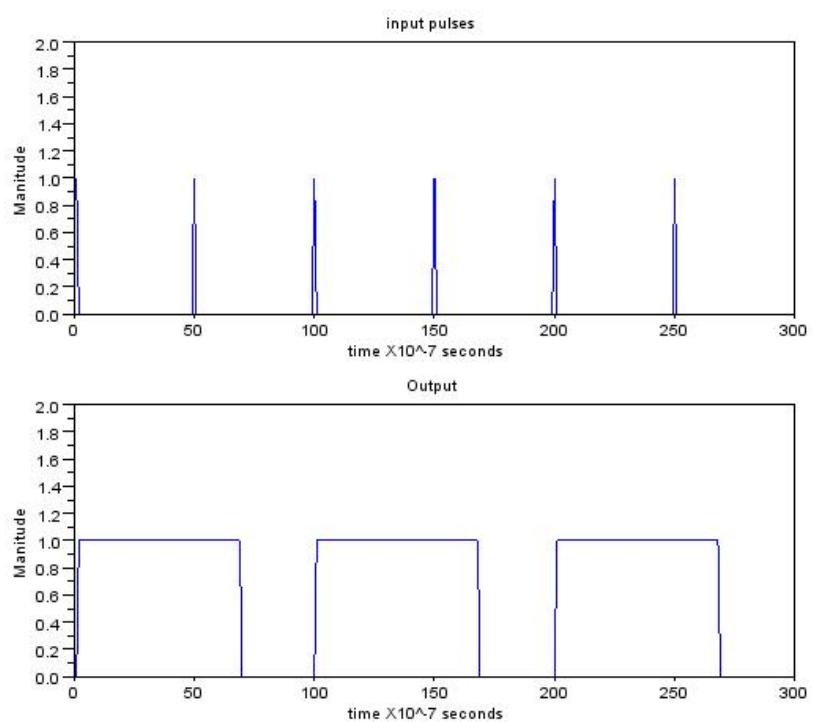


Figure 7.3: monostable multivibrator

```

8 R=1; //taking give values
9 C=0.01;
10 t= 693*R*C; // calculting time constant
11 tt=t*10;
12 p=1;
13 len=sp*60-1;
14 q=1;
15 for j=1:len //plotin the graphs
16     lo = sp*10;
17     f=modulo(j,lo);
18     if f==0 then
19         inpu(j)=1;
20     else
21         inpu(j)=0;
22     end
23     inpu(1)=1;
24 o(j)=2;
25 end
26 while q<len
27     result(q)=0;
28     q=q+1;
29 end
30 while p<len
31     if inpu(p)==1 then
32         for k=1:tt
33             result(p+k)=1;
34         end
35         p=p+tt;
36     else
37         result(p)=0;
38         p=p+1;
39     end
40 end
41 subplot(2,1,1); // ploting bothe graphs in same
window
42 plot(o);
43 plot(inpu);
44 xlabel('time X10^-7 seconds');

```

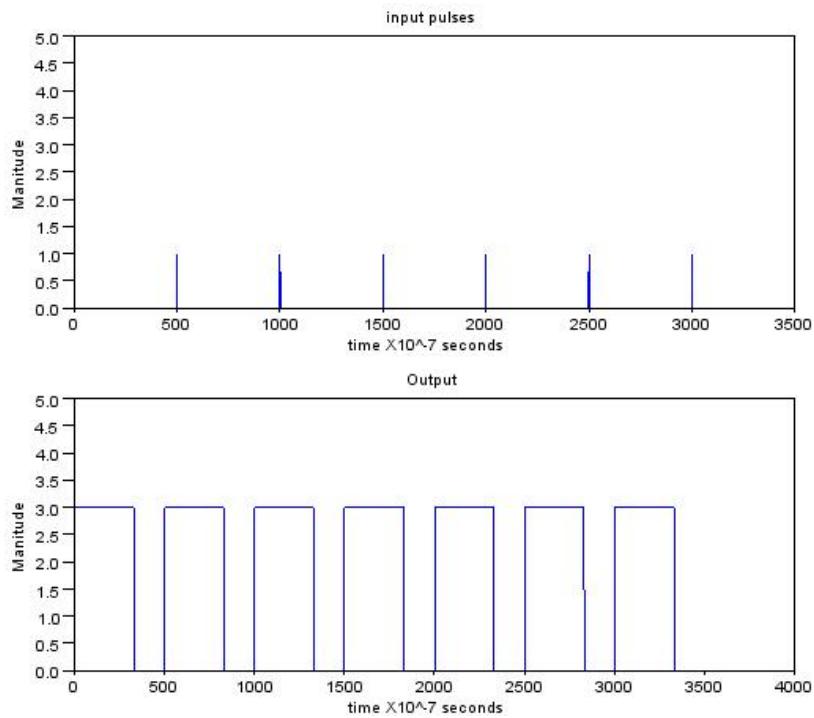


Figure 7.4: 74123

```

45 ylabel('Manitude') ;
46 title('input pulses');
47 subplot(2,1,2);
48 plot(o);
49 plot(result);
50 xlabel('time X10^-7 seconds');
51 ylabel('Manitude') ;
52 title('Output');

```

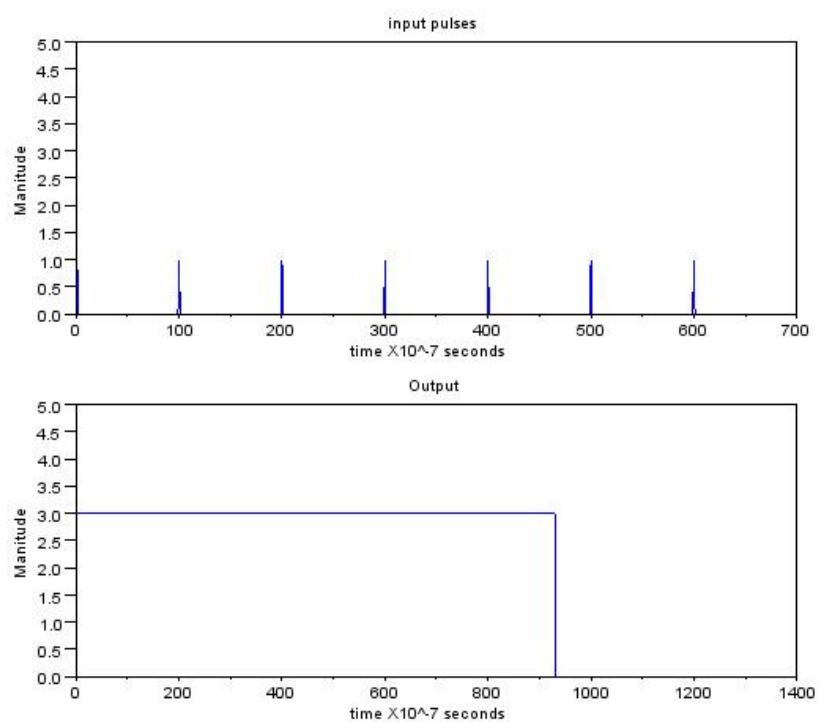


Figure 7.5: 74123

Scilab code Exa 7.10 74123

```
1 //example 7.10
2 clear
3 clc
4 close
5 //R = input('Enter the value of the resistance R in
6 // Kohms :');
7 //C =input('Enter the value of the Capacitance C in
8 // micro farads :');
9 sp = input('Enter the spacing between two input
10 // pulses in micro seconds :');
11 R=10;
12 C=0.01;
13 //sp=50;
14 //sp=10;
15 t= 330*R*C; // calculating time constant
16 printf('The output pulse width will be about %f
17 // micro seconds ',t);
18 tt=t*10;
19 p=1;
20 len=sp*60+1;
21 q=1;
22 for j=1:len // making arrays to plot the graphs
23     lo = sp*10;
24     f=modulo(j,lo);
25     if f==0 then
26         inpu(j)=1;
27     else
28         inpu(j)=0;
29     end
30     inpu(1)=1;
31     o(j)=5;
32 end
33 if sp<40 then
34 while q<2*len
35     result(q)=0;
36     q=q+1;
```

```

33 end
34 else
35 while q<1.2*len
36     result(q)=0;
37     q=q+1;
38 end
39 end
40 while p<len
41     if inpu(p)==1 then
42         for k=1:tt
43             result(p+k)=3;
44         end
45         p=p+1;
46     else
47         p=p+1;
48     end
49 end
50 end
51 subplot(2,1,1); // plotting bothe graphs in same
      window
52 plot(o);
53 plot(inpu);
54 xlabel('time X10^-7 seconds');
55 ylabel('Manitude');
56 title('input pulses');
57 subplot(2,1,2);
58 plot(o);
59 plot(result);
60 xlabel('time X10^-7 seconds');
61 ylabel('Manitude');
62 title('Output');

```

Scilab code Exa 7.11 finding timing capacitor values

1 //example 7.11

```
2 clc
3 clear
4 //R = input('Enter the value of the resistance R in
    Kohms :');
5 //pw =input('Enter the value of required pulse width
    in millisecondseconds :');
6 R=0.5; //taking the given values
7 format('v',18);
8 pw = 1 * 10^-3;
9 C = pw/(0.33*R); //calculating C
10 printf('The required value of capacitance is %f
    microfarads\n',C);
11 printf('The pulse delay capacitor is %f microfarads'
    ,(2*C));
```

Chapter 8

Flip Flops

Scilab code Exa 8.4 RS flipflop

```
1 //example 8.4
2 clc;
3 clear;
4 en=input("Enter the enable input level(1 or 0) : ");
5 r=input("enter the R input level(1 or 0) : "); // accepting the inputs from the user
6 s=input("enter the S input level(1 or 0) : ");
7 qn=input("Enter the previous output value(1 or 0) : ");
8
9 if en == 0 then // calculating the output
10     op = qn;
11 elseif (s==0 & r==0) then
12     op=qn;
13 elseif(s==1&r==1) then
14     disp('The inputs are illegal');
15     return;
16 else
17     op=s;
18
```

```
19 end
20
21 printf ('\n \noutput (Qn+1) = %d ',op); // displaying
      the output
```

Scilab code Exa 8.5 positive edge triggered RS flip flop

```
1 //example 8.5
2 clc;
3 clear;
4 disp('Here what happens at each point in time');
5 disp('Time t0: S = 0, R = 0, no change in Q (Q
      remains 0)');
6 disp('Time t1: S = 1, R = 0, Q changes from 0 to 1
      ');
7 disp('Time t2: S = 0, R = 1, Q resets to 0');
8 disp('Time t3: S = 1, R = 0, Q sets to 1 ');
9 disp('Time t4: S = 0, R = 0, no change in Q (Q
      remains 1)');
10 disp('Notice that either R or S, or both, are
      allowed to change state at any time, whether C is
      high or low. The only time both R and S must be
      stable (unchanging) is during the short PTs of
      the clock.');
```

Scilab code Exa 8.6 negative edge triggered RS flip flop

```
1 //example 8.6
2 clc;
3 clear;
4 disp('Here what happens at each point in time');
5 disp('Time t0: S = 0, R = 0, no change in Q (Q
      remains 0)');
```

```

6 disp('Time t1: S = 1, R = 0, Q changes from 0 to 1
');
7 disp('Time t2: S = 0, R = 1, Q resets to 0');
8 disp('Time t3: S = 1, R = 0, Q sets to 1');
9 disp('Time t4: S = 0, R = 0, no change in Q (Q
remains 1)');
10 disp('Notice that either R or S, or both, are
allowed to change state at any time, whether C is
high or low. The only time both R and S must be
stable (unchanging) is during the short NTs of
the clock.');

```

Scilab code Exa 8.7 T flip flop

```

1 //example 8.7
2 clc;
3 clear;
4 close;
5 printf("For input J and K = 0 output Qn+1 = Qn i.e
output does not change its state And for J = K =
1, The Output Qn+1 = Qn' i.e output toggles " );

```

Scilab code Exa 8.9 JK master slave

```

1 //example 8.9
2 clc
3 close
4 clear
5 disp("since J=K=1, the flip-flop simply toggles each
time the clock goes low, The waveform at Q has a
period twice of that of the waveform. In other

```

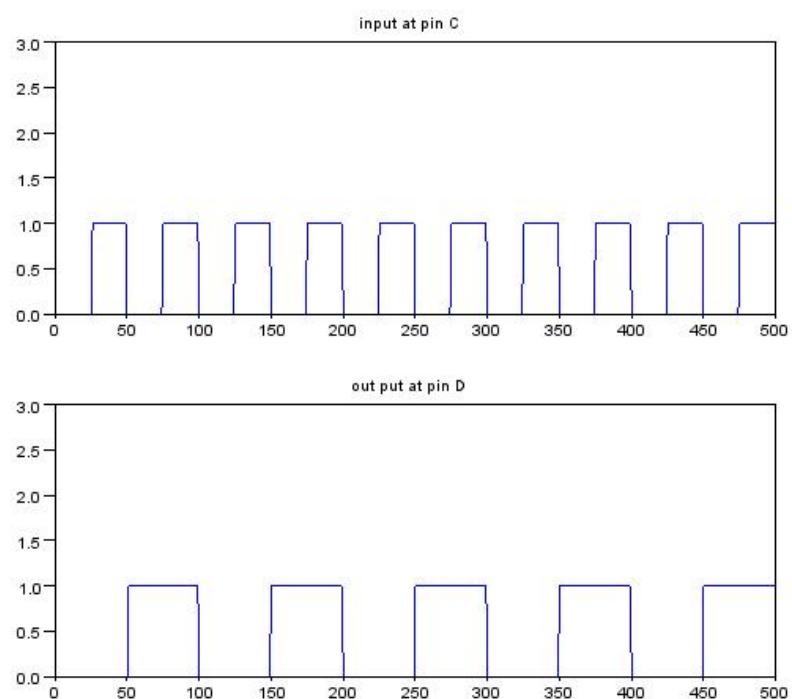


Figure 8.1: JK master slave

words, the frequency of Q is only one-half of that of . This circuit acts as a frequency divider --the output frequency divide by 2. Note that Q changes state on NTs of the clock. The waveforms are as shown in the figure ");

```

6 t=50; // taken time period
7 p=1;
8 while p<t*10 // taking values for plotting the graph
9     if p==1 | modulo(p,t)==0 then
10         for k=1:t/2
11             cin(p+k)=0;
12         end
13         p=p+t/2;
14     else
15         cin(p)=1;
16         p=p+1;
17     end
18 end
19 t=100;
20 p=1;
21 while p<t*5
22     if p==1 | modulo(p,t)==0 then
23         for k=1:t/2
24             dout(p+k)=0;
25         end
26         p=p+t/2;
27     else
28         dout(p)=1;
29         p=p+1;
30     end
31 end
32 y=[3 3];
33 subplot(2,1,1) // plotin both the plots in a single
window
34 title('input at pin C')
35 plot(cin)
36 plot(y)
37 subplot(2,1,2)

```

```
38 title('out put at pin D')
39 plot(dout)
40 plot(y)
```

Scilab code Exa 8.10 fictitious flip flop excitation table

```
1 //Example 8.10
2 clc
3 clear
4 close
5 b=[0 1 0 1 0 1 0 1]; //given truth tble for the
    fictitious flip flop
6 a = [0 0 1 1 0 0 1 1];
7 qn = [0 0 0 0 1 1 1 1];
8 for i=1:8
9 if(a(i)==0 & b(i)==0) then
10     qn1(i) = 0;
11 end;
12 if (a(i)==1 & b(i)== 1) then
13     qn1(i) = 1 ;
14 end;
15 if (a(i)==1 & b(i)== 0) then
16     qn1(i) = bitcmp(qn(i),1) ;
17 end;
18 if (a(i)==0 & b(i)== 1) then
19     qn1(i) = (qn(i)) ;
20 end;
21 end;
22 for i = 1 : 8 // printin the truth table
23     Y(i,1)=qn(i);
24     Y(i,2)=a(i);
25     Y(i,3)=b(i);
26     Y(i,4)=qn1(i);
27 end
28 disp('The given truth table is :');
```

```

29 disp(' Qn      A      B      Qn+1');
30 disp(Y);
31 disp('The transitions are shown below');
32 c1=0;
33 c2=0;
34 c3=0;
35 c4=0;
36 for j=1:8 //checking all possible cases to make a
               transition table
37         if(qn(j)==0) then
38             if(qn1(j) == 0) then
39                 if(c1==0) then
40                     disp('transition from 0 -----> 0');
41                     disp('      A      B ');
42                     c1=1;
43                     end;
44                     disp(Y(j,2:3));
45             end;
46         end;
47     end;
48     for j=1:8
49         if(qn(j)==0) then
50             if(qn1(j) == 1) then
51                 if(c2==0) then
52                     disp('transition from 0 -----> 1');
53                     disp('      A      B ');
54                     c2=1;
55                     end;
56                     disp(Y(j,2:3));
57             end;
58         end;
59     end;
60     for j=1:8
61         if(qn(j)==1) then
62             if(qn1(j) == 0) then
63                 if(c3==0) then
64                     disp('transition from 1 -----> 0');
65                     disp('      A      B ');

```

```

66          c3=1;
67          end;
68          disp (Y(j,2:3));
69      end;
70  end;
71 end;
72 for j=1:8
73     if(qn(j)==1) then
74         if(qn1(j) == 1) then
75             if(c4==0) then
76                 disp('transition from 1 ----> 1');
77                 disp('      A      B ');
78             c4=1;
79         end;
80         disp(Y(j,2:3));
81     end;
82 end;
83 end;

```

Scilab code Exa 8.12 state transition diagram for given circuit

```

1 //example 8.12
2
3 clc;
4 clear;
5 close;
6 qn=[0,0,1,1];
7 x=[0,1,0,1];
8 for i=1:4 // calculating Y for all possible cases
9     d(i)= bitxor(x(i),qn(i));
10    qn1(i) =d(i);
11    y(i)=bitand(x(i),bitcmp(qn(i),1));
12 end;
13 for i = 1 : 4 // displaying the state table
14     Y(i,1)=qn(i);

```

```
15      Y(i,2)=x(i);  
16      Y(i,3)=d(i);  
17      Y(i,4)=qn1(i);  
18      Y(i,5)= y(i);  
19      end  
20 disp('The state table is :');  
21 disp(' Qn X D Qn+1 Y');  
22 disp(Y);
```

Scilab code Exa 8.13 D flip flop to RS flip flop

```
1 //example 8.13  
2 clc;  
3 clear;  
4 disp('For SR flip flop  $Q_{n+1} = S + R'Q_n$  and for D  
flip-flop  $Q_{n+1} = D$ .');  
5 disp('Thus with  $D = S + R'Q_n$  we get circuit which  
behaves like SR flip-flop.');
```

Chapter 9

Registers

Scilab code Exa 9.1 shift register serial input

```
1 //example 9.1
2 clc;
3 clear;
4 close ;
5 //s = input ('Enter the number to be serially
       shifted in to the shift register ');
6 s=0100; // given serial input
7 for i = 4:-1:1
8     se(i) =modulo(s,10);
9     s=s/10;
10    s=round(s);
11 end
12 se(i+4)=0;
13 k=0;
14 for i = 2:6 // making state table
15     clk(k+1) = k;
16     q(i)=se(i-1);
17     if i>1 then
18         r(i) = q(i-1);
19     else
20         r(i) = 0;
```

```

21     end;
22     if i>2 then
23         s(i) = r(i-1);
24     else
25         s(i) =0;
26     end;
27     if i>3 then
28         t(i) =s(i-1);
29     else
30         t(i) =0;
31     end;
32     k=k+1;
33 end
34 for i = 1 : 5 // printing the state table
35     Y(i,1)=clk(i);
36     Y(i,2)=se(i);
37     Y(i,3)=q(i);
38     Y(i,4)=r(i);
39     Y(i,5)= s(i);
40     Y(i,6)=t(i);
41 end
42 disp('The state table is :');
43 disp('Clock Input Q R S T');
44 disp(Y);

```

Scilab code Exa 9.2 shift register serial input and output graph

```

1 //example 9.2
2 clc
3 clear
4 close
5 t1=100; // clock period
6 s=0100; //given serial input

```

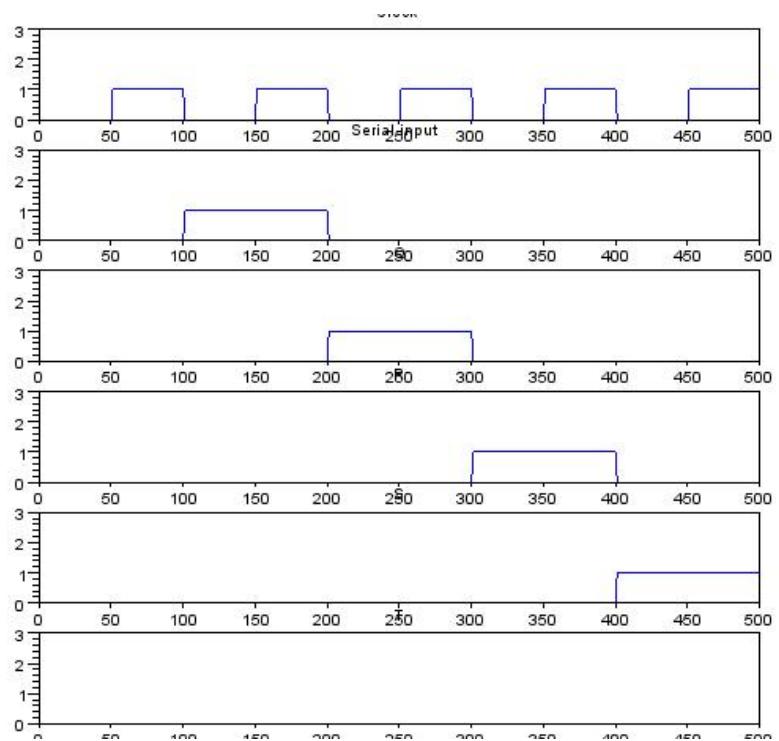


Figure 9.1: shift register serial input and output graph

```

7  for i = 4:-1:1
8      se(i) = modulo(s,10);
9      s=s/10;
10     s=round(s);
11 end
12 se(i+4)=0;
13 k=0;
14 for i = 2:6 //initially making a state table
15     clk(k+1) = k;
16     q(i)=se(i-1);
17     if i>1 then
18         r(i) = q(i-1);
19     else
20         r(i) =0;
21     end;
22     if i>2 then
23         s(i) = r(i-1);
24     else
25         s(i) =0;
26     end;
27     if i>3 then
28         t(i) =s(i-1);
29     else
30         t(i) =0;
31     end;
32     k=k+1;
33 end
34 for m=1:5 // drawing the graph
35     if(se(m)==1) then
36         v= ((m-1).*t1)
37         for u= 1: t1
38             se1(u+v)=1;
39             end
40     else
41         v= ((m-1)*t1)
42         for u= 1: t1
43             se1(u+v)=0;
44             end

```

```

45      end;
46
47      if (q(m)==1) then
48          v= ((m-1).*t1)
49          for u= 1: t1
50              q1(u+v)=1;
51              end
52      else
53          v= ((m-1)*t1)
54          for u= 1: t1
55              q1(u+v)=0;
56              end
57      end;
58      if (r(m)==1) then
59          v= ((m-1).*t1)
60          for u= 1: t1
61              r1(u+v)=1;
62              end
63      else
64          v= ((m-1)*t1)
65          for u= 1: t1
66              r1(u+v)=0;
67              end
68      end;
69      if (s(m)==1) then
70          v= ((m-1).*t1)
71          for u= 1: t1
72              s1(u+v)=1;
73              end
74      else
75          v= ((m-1)*t1)
76          for u= 1: t1
77              s1(u+v)=0;
78              end
79      end;
80      if (t(m)==1) then
81          v= ((m-1).*t1)
82          for u= 1: t1

```

```

83         t11(u+v)=1;
84         end
85     else
86         v= ((m-1)*t1)
87         for u= 1: t1
88             t11(u+v)=0;
89         end
90     end;
91 end;
92 p=1;
93 while p<t1*5
94     if p==1 | modulo(p,t1) == 1 then
95         for k=1:t1/2
96             cin(p+k)=0;
97         end
98         p=p+t1/2;
99     else
100         cin(p)=1;
101         p=p+1;
102     end
103 end
104 y=[3 3];
105 subplot(6,1,1) // making subplots to draw all
106 graphs in a single window
107 title('Clock')
108 plot(cin)
109 plot(y)
110 subplot(6,1,2)
111 title('Serial input')
112 plot(se1)
113 plot(y)
114 subplot(6,1,3)
115 title('Q')
116 plot(q1)
117 plot(y)
118 subplot(6,1,4)
119 title('R')
120 plot(r1)

```

```
120 plot(y)
121 subplot(6,1,5)
122 title('S')
123 plot(s1)
124 plot(y)
125 subplot(6,1,6)
126 title('T')
127 plot(t11)
128 plot(y)
```

Scilab code Exa 9.4 54164 shift register

```
1 //example 9.4
2 clc;
3 clear;
4 //b= input('Enter the number of bits :');
5 //c= input('Enter the clock frequency in Mhz :');
6 b= 8; // given values
7 c=10;
8 t= 1000/c;
9 printf('One clock period takes %d ns\n',t); // displaying the results
10 tt=t*b;
11 printf(' Time required by total bits required is %d ns ',tt);
```

Scilab code Exa 9.5 54164 shift register

```
1 //example 9.5
2 clc;
3 clear;
4 close;
5 //c= input('Enter the clock frequency in Mhz :');
```

```
6 c=10; //given clock frequency
7 t= 1000/c;
8 printf('The data must be stable for 30 ns\n'); // 
    displaying results
9 tc = t-30;
10 printf(' The data may be changing in %d ns ',tc);
```

Scilab code Exa 9.8 74ls174

```
1 //example 9.8
2 clc;
3 clear;
4 //s=input(" Enter the setup time in ns :");
5 //h=input(" Enter the hold time in ns :");
6 s=20; //given input values
7 h=5;
8 printf('The data input levels must be held steady
    foor a minimum of %d ns',(s+h)); // displayin
    the results
```

Scilab code Exa 9.9 7495A

```
1 //example 9.9
2 clc;
3 clear;
4 disp('The mode control line must be high. The data
    lines must be stable for more than 10 ns prior to
    the clock NTs . If the clock is stopped after
    the transition time T, the levels n the input
    data lines may be changed. However , if the clock
    is not stopped , the input data levels must be
    mainted. ')
```

Chapter 10

Counters

Scilab code Exa 10.1 ripple counter clock frequency

```
1 //example 10.1
2 clc;
3 clear;
4 //c= input('Enter the period of the waveform at C in
5 // micro seconds : ');
6 c=24; // given period of waveform
7 clk= c/8;
8 clkf = 1/(clk*10^-3);
9 printf('The clock period is %f micro seconds \n',clk
    );//displaying the results
9 printf('The clock frequenc must be %f KHz ', clkf);
```

Scilab code Exa 10.2 number of flip flops required to construct a counter

```
1 //example 10.2
2 clc;
3 clc
4 c=128; // given counters
```

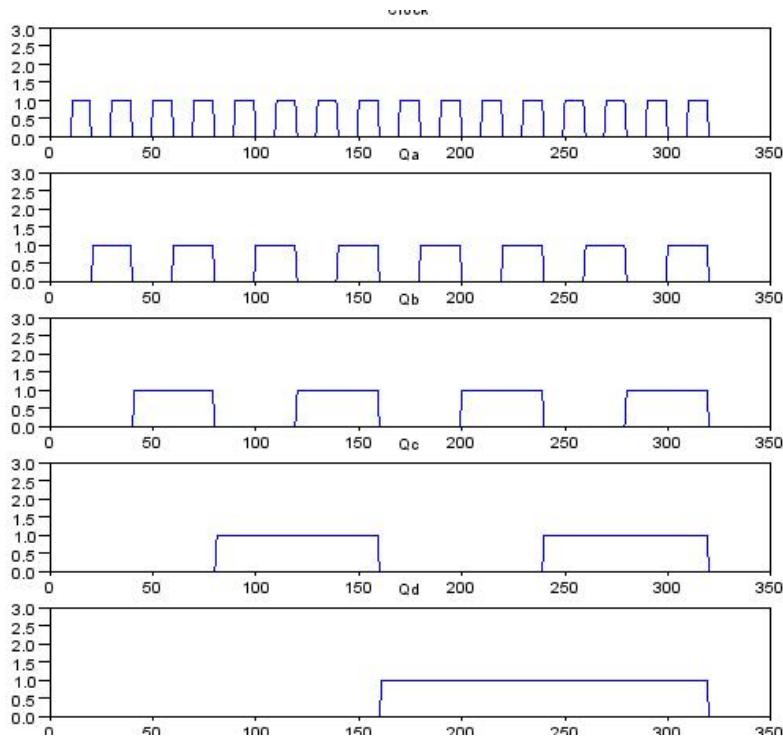


Figure 10.1: Output waveforms for a 7493A connected as a mod 16 counter

```

5 d=32;
6 e=64;
7 fc=log2(c); //making necessar calculations
8 fd=log2(d);
9 printf('A mod-128 conter should have %d flipflops\n',
       ,fc);
10 printf(' A mod-32 conter should have %d flipflops\n',
           ,fd); //displaying the results
11 fe=log2(e);
12 n=2^fe - 1 ;
13 printf(' The largest decimal no that can be stored
           in a mod-64 counter is %d',n);

```

Scilab code Exa 10.3 Output waveforms for a 7493A connected as a mod 16 counter

```
1 clc;
2 clear;
3 close;
4 t=320;
5 p=1;
6 while p<t*1 //making arrays for plotting
7     if p==1 | modulo(p,t)==0 then
8         for k=1:t/2
9             qd(p+k)=0;
10        end
11        p=p+t/2;
12    else
13        qd(p)=1;
14        p=p+1;
15    end
16 end
17 t=160;
18 p=1;
19 while p<t*2
20     if p==1 | modulo(p,t)==0 then
21         for k=1:t/2
22             qc(p+k)=0;
23         end
24         p=p+t/2;
25     else
26         qc(p)=1;
27         p=p+1;
28     end
29 end
30 t=80;
31 p=1;
```

```

32 while p<t*4
33     if p==1 | modulo(p,t)==0 then
34         for k=1:t/2
35             qb(p+k)=0;
36         end
37         p=p+t/2;
38     else
39         qb(p)=1;
40         p=p+1;
41     end
42 end
43 t=40;
44 p=1;
45 while p<t*8
46     if p==1 | modulo(p,t)==0 then
47         for k=1:t/2
48             qa(p+k)=0;
49         end
50         p=p+t/2;
51     else
52         qa(p)=1;
53         p=p+1;
54     end
55 end
56 t=20;
57 p=1;
58 while p<t*16
59     if p==1 | modulo(p,t)==0 then
60         for k=1:t/2
61             clk(p+k)=0;
62         end
63         p=p+t/2;
64     else
65         clk(p)=1;
66         p=p+1;
67     end
68 end
69 for i=320:350

```

```

70     clk(i)=0;
71     qa(i)=0;
72     qb(i)=0;
73     qc(i)=0;
74     qd(i)=0;
75 end;
76 y=[3 3]; //ploting the graphs
77 subplot(5,1,1)
78 title('Clock')
79 plot(clk)
80 plot(y)
81 subplot(5,1,2)
82 title('Qa')
83 plot(qa)
84 plot(y)
85 subplot(5,1,3)
86 title('Qb')
87 plot(qb)
88 plot(y)
89 subplot(5,1,4)
90 title('Qc')
91 plot(qc)
92 plot(y)
93 subplot(5,1,5)
94 title('Qd')
95 plot(qd)
96 plot(y)

```

Scilab code Exa 10.5 Expression for AND gate connected to the leg of OR gate that drives clock input to flip flop Qd in 74193

```

1 //example 10.5
2 clc;
3 clear;
4 printf('The correct expression is : (count-up clock)

```

```
' '(Qa)(Qb)(Qc)' );
```

Scilab code Exa 10.6 Expression for 4 input AND gate connected to the leg of OR gate that conditions the J and K inputs to the Qd flip flop in a 74191

```
1 //example 10.6
2
3 clc;
4 clear;
5 printf('The correct logic expression is : (down-up) ,
6      '(Qa)(Qb)(Qc)(enable)',');
```

Scilab code Exa 10.7 number of flip flops required to construct a counter

```
1 //example 10.7
2 clc;
3 clear;
4 mod = input("Enter the n value in your desired mod-n
5           counter:"); //taking the input
6 m=mod;
7 while 1
8   n= log2(mod); //checking whether the given number
9     is a power of 2
10   k=modulo(n,1);
11   if k==0 then
12     printf('The number of flip flops used in mod-%d
13           counter are: ',m); // if yes the print th
14           output.
15     printf('%d',n);
16   return;
17 end
18 mod =mod+1;
```

15 **end**

Scilab code Exa 10.8 what modulus counters can be constructed with given number of flip flops e

```
1 //example 10.8
2 clc;
3 clear;
4 //ff = input('Enter the no of flip-flops :');
5 ff=4; //given input
6 k=2^ff;
7 if(k==2) then //output display
8     printf('With given flipflop we can only count 2,
         we can have a modulus 2 counter');
9 else
10 printf('With given number of flip-flops the counter
         will have a natural count of %d\n',k);
11 printf('We can thus construct any counter that has a
         modulus between %d and 2 ',k )
12 end;
```

Scilab code Exa 10.9 mod 6 counter

```
1 //example 10.9
2
3 clc;
4 clear;
5 close;
6 c = [0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1
      0]; //taking the values for a mod -6 counter
```

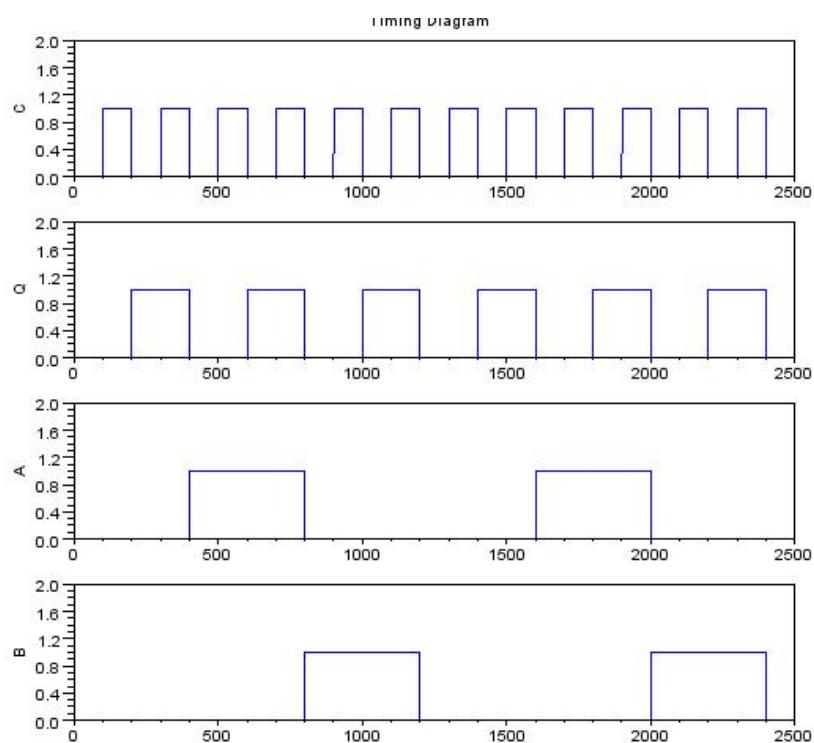


Figure 10.2: mod 6 counter

```

7 q = [0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1
0];
8 a = [0 0 0 0 1 1 1 1 0 0 0 0 0 0 0 0 0 0 1 1 1 1 0 0 0 0
0];
9 b = [0 0 0 0 0 0 0 0 1 1 1 1 0 0 0 0 0 0 0 0 0 0 1 1 1 1
0];
10 y1=q;
11 y2=a;
12 y3=b;
13 y11p=1;
14 y22p=1;
15 y33p=1;
16 y44p=1;
17 cp=1;
18 yf1p=1;
19 for i=1:25      // making arrays to draw the output
20     if y1(i)==1 then
21         for o=1:100
22             y11(y11p)=1;
23             y11p=y11p+1;
24             end
25     else
26         for o=1:100
27             y11(y11p)=0;
28             y11p=y11p+1;
29             end
30
31 end
32 if y2(i)==1 then
33     for o=1:100
34         y21(y22p)=1;
35         y22p=y22p+1;
36         end
37     else
38         for o=1:100
39             y21(y22p)=0;
40             y22p=y22p+1;
41             end

```

```

42
43 end
44 if y3(i)==1 then
45     for o=1:100
46         y31(y33p)=1;
47         y33p=y33p+1;
48     end
49 else
50     for o=1:100
51         y31(y33p)=0;
52         y33p=y33p+1;
53     end
54
55 end
56 if c(i)==1 then
57     for o=1:100
58         c1(cp)=1;
59         cp=cp+1;
60     end
61 else
62     for o=1:100
63         c1(cp)=0;
64         cp=cp+1;
65     end
66 end
67
68 end
69 z=[2 2];
70 subplot(4,1,1); //ploting the out put
71 title('Timing Diagram');
72 plot(c1);
73 plot(z);
74 ylabel('C');
75 subplot(4,1,2);
76 plot(y11);
77 ylabel('Q');
78 plot(z);
79 subplot(4,1,3);

```

```
80 plot(y21);
81 ylabel('A');
82 plot(z);
83 subplot(4,1,4);
84 plot(z);
85 ylabel('B');
86 plot(y31);
```

Scilab code Exa 10.10 Expression for a gate to decode count 8 in a 7492A

```
1 //example 10.10
2 clc;
3 clear;
4 printf('The correct expresion is ""8"" = Qd Qc '' Qb
    Qa'');
```

Scilab code Exa 10.12 mod 12 counter

```
1 //example 10.12
2 clc
3 clear
4 //pro= ('Enter the value to whic counter should
    progress:');
5 pro =11; // given input
6 q=1;
7 aa=pro;
8 for i=1:4          //converting the given number
    in to binary
9     x=modulo(aa,2);
10    b(q)=x;
11    aa=aa/2;
12    aa=floor(aa);
13    q=q+1;
```

```

14 end
15
16 bi=''; // then printing the NAND gate inputs
17 for i=1:4
18     if i==1 & b(i)==1 then
19         bi=strcat([bi 'Qa']);
20     elseif i==1 & b(i)== 0 ;
21         bi=strcat([bi 'Qa' '']);
22     end
23     if i==2 & b(i)==1 then
24         bi=strcat([bi 'Qb']);
25     elseif i==2 & b(i)== 0 ;
26         bi=strcat([bi 'Qb' '']);
27     end
28     if i==3 & b(i)==1 then
29         bi=strcat([bi 'Qc']);
30     elseif i==3 & b(i)== 0 ;
31         bi=strcat([bi 'Qc' '']);
32     end
33     if i==4 & b(i)==1 then
34         bi=strcat([bi 'Qd']);
35     elseif i==4 & b(i)== 0 ;
36         bi=strcat([bi 'Qd' '']);
37     end
38
39 end
40 disp('The NAND gate inputs must be :');
41 disp(bi)

```

Scilab code Exa 10.13 4 bit binary counter presettable

```

1 //example 10.13
2 clc;
3 clear
4 //pre=input(" Enter the number where the counter is

```

```

        preset");
5 pre = 1001; // given preset value
6 q=1;
7 b=0;
8 f=0;
9 a=pre;
10 while(a>0) //converting to decimal
11     r=modulo(a,10);
12     b(1,q)=r;
13     a=a/10;
14     a=floor(a);
15     q=q+1;
16 end
17 for m=1:q-1
18     c=m-1
19     f = f + b(1,m)*(2^c);
20 end
21 disp("The counter will count down to 15 , Then
         preset back to %d, The resulting state diagram is
         shown below");
22 for k=1:3
23 for i=9:-1:0 // this will print the states
24 printf ('%d ',i);
25 end;
26 printf ('15 ');
27
28 end;

```

check Appendix AP 8 for dependency:

kmap3.sci

check Appendix AP 2 for dependency:

noof.sci

check Appendix AP 3 for dependency:

noof0.sci

Scilab code Exa 10.14 self correcting modulo 6 counter

```
1 //example 10.14
2 //this program uses the following functions
3 //kmap3.sci
4 //noof.sci and noof0.sci
5 //the above programs should be executed before
   executing these programs
6 clc;
7 n= [ 0 0 0 ;
8      0 0 1 ;
9      0 1 0 ;
10     0 1 1 ;
11     1 0 0 ;
12     1 0 1 ;
13     1 1 0 ;
14     1 1 1 ];
15     for i= 1 : 5
16         n1(i,:)= n(i+1,:)
17     end
18     for i=6:8
19         n1(i,:)=[0 0 0]
20     end;
21 p=1;
22 for i= 1:3 //making the state table
23     for j = 1:8
24         if n(j,i)== 0
25             jf(j,p)= n1(j,i);
26             jf(j,p+1)= 2;
27         elseif n(j,i) == 1
28             jf(j,p)=2;
29             jf(j,p+1)=bitcmp(n1(j,i),1);
30         end
31     end
```

```

32     p=p+2
33 end;
34 disp('State tabel for mod 6 counter:'); //displaying
      the state table
35 di= [n n1 jf];
36 disp('   Cn      Bn      An      Cn1      Bn1      An1      Jc
      Kc      Jb      Kb      Ja      Ka');
37 disp(di);
38 disp('Here ''2'' represents a don''t care condition
      );
39 disp('These below Karnaugh maps give the design
      equations');
40
41 jc=[0 0 1 0;2 2 2 2] //Karnaugh Maps for the design
      equations
42 JC=kmap3(jc); //calling the 3-variable kmap
43 printf('\n\nJC = %s \n',JC); //displaying the result
44
45 kc=[2 2 2 2;0 1 1 1]
46 KC=kmap3(kc); //calling the 3-variable kmap
47 printf('\n\nKC = %s \n',KC); //displaying the result
48
49 jb=[0 1 2 2;0 0 2 2]
50 JB=kmap3(jb); //calling the 3-variable kmap
51 printf('\n\nJB = %s \n',JB); //displaying the result
52
53 kb=[2 2 1 0;2 2 1 1]
54 KB=kmap3(kb); //calling the 3-variable kmap
55 printf('\n\nKB = %s \n',KB); //displaying the result
56
57 ja=[1 2 2 1;1 2 2 0]
58 JA=kmap3(ja); //calling the 3-variable kmap
59 printf('\n\nJA = %s \n',JA); //displaying the result
60
61 ka=[2 1 1 2;2 1 1 2]
62 KA=kmap3(ka); //calling the 3-variable kmap
63 printf('\n\nKA = %s \n',KA); //displaying the result

```

check Appendix AP 7 for dependency:

kmap2.sci

Scilab code Exa 10.15 sequence generator

```
1 //example 10.15
2 //this program use kmap2.sci
3 //kmap2.sci should be executed before executing this
   program
4 clc;
5 a= [0 0 1 1]
6 b= [0 1 0 1]
7 y= [1 1 0 1]
8 k= [1 1 ; 0 1]
9 bi = kmap2(k); // calling 2-variable kmap
10 disp(" A B Y");
11 for i=1:3
12     Y(i,1) = a(i);
13     Y(i,2) = b(i);
14     Y(i,3) = y(i);
15 end
16 disp(Y);
17 disp('The minimised expression from karnaugh map is ')
      );// displaying the result
18 disp(bi);
```

Chapter 11

Design of Sequential Circuit

check Appendix [AP 6](#) for dependency:

`kmap3a.sci`

check Appendix [AP 2](#) for dependency:

`noof.sci`

check Appendix [AP 3](#) for dependency:

`noof0.sci`

Scilab code Exa 11.1 synchronous sequential logic circuit

```
1 //example 11.1
2 clc;
3 //this program requires
4 //kmap3a.sci to find the kmap
5 //noof.sci function used inside kmap
6 //noof0.sci function used inside kmap
7 n= [ 0 0 0;
8      0 0 1;
9      0 1 0;
10     0 1 1;
```

```

11      1 0 0;
12      1 0 1;
13      1 1 0;
14      1 1 1];
15      for i= 1:8      // printing the state synthesis
16          table
17          an1(i,1)=n(i,3);
18          dn(i,1)=n(i,3);
19          if n(i,1)==1 & n(i,2) ==1 & n(i,3)==0 then
20              z(i,1)=1;
21          else
22              z(i,1)=0;
23          end
24      end;
25 dis=[n an1 dn z];
26 disp('State Synthesis table :');
27 disp(' An X Y An1 Dn Z');
28 disp(dis);
29 printf('\n\n Design equations :\n');
30 Dn = [ 0 1 1 0;0 1 1 0];
31 Z= [ 0 0 0 0;0 0 0 1];
32 dn1= kmap3a(Dn);           // finding
33             the 3 variable kmap of Dn
34 printf('\n      Dn = %s \n\n',dn1);    // displaying
35             the minimized expression
36 z1= kmap3a(Z);           // finding
37             the 3 variable kmap of Z
38 printf('\n      Z = %s \n\n',z1);    // displaying
39             the minimized expression

```

check Appendix AP 4 for dependency:

`donkmapij.sci`

check Appendix AP 5 for dependency:

`noof1.sci`

Scilab code Exa 11.2 vending machine

```
1 // example 11.2
2 //this code needs
3 //donkmapij.sci // function to minimize given
   expression using a kmap
4 //noof1.sci
5 //above two shoulb be executed before executing this
   code
6 clc;
7 tt=[0 0 0 0 0 0 0 0 0 0; // given state synthesis
   table
8     0 0 0 1 0 0 0 0 0 0;
9     0 0 1 0 0 1 0 0 0 1;
10    0 0 1 1 1 0 0 0 1 0;
11    0 1 0 0 0 1 0 0 0 1;
12    0 1 0 1 0 1 0 0 0 1;
13    0 1 1 0 1 0 0 0 1 0;
14    0 1 1 1 0 0 1 0 0 0;
15    1 0 0 0 1 0 0 0 1 0;
16    1 0 0 1 1 0 0 0 1 0;
17    1 0 1 0 0 0 1 0 0 0;
18    1 0 1 1 0 0 1 1 0 0];
19 disp('State snthesis table for Vending machine
   problem'); //printing the staate synthesis table
20 disp('Present state      input      Next state      Output
   Db      Da');
21 disp('      Bn      An      I      J      Bn1      An1      X      Y
   ');
22 disp(tt);
23 printf('\n\n Design equations :\n');
24
25 printf('\n Design equation for DB\n');
26 db =[ 0 0 2 1 ; 0 0 2 1 ;1 0 2 0 ;0 1 2 0];
27 DB =donkmapij(db); // minimizing the expresion using
   4 variable kmap
28 printf('\n      DB = %s \n\n',DB); //displaing result
29
```

```

30 printf ('\n Design equation for DA\n');
31 da =[ 0 1 2 0;0 1 2 0 ;0 0 2 0;1 0 2 0];
32 DA =donkmapij(da); // minimizing the expresion using
4 variable kmap
33 printf ('\n      DA = %s \n\n',DA); // displaing result
34
35 printf ('\n Design equation for X\n');
36 x =[0 0 2 0;0 0 2 0;0 1 2 1; 0 0 2 1];
37 X =donkmapij(x); // minimizing the expresion using 4
variable kmap
38 printf ('\n      X = %s \n\n',X); // displaing result
39
40 printf ('\n Design equation for Y\n');
41 y=[0 0 2 0;0 0 2 0;0 0 2 1;0 0 2 0];
42 Y =donkmapij(y); // minimizing the expresion using 4
variable kmap
43 printf ('\n      Y = %s \n\n',Y); // displaing result

```

Scilab code Exa 11.5 Reducing state transition diagrams

```

1 //example 11.5
2 clc;
3 clear;
4 disp('Original table :'); //displaying original
table
5 disp('Present State    Next State    Present Output');
6 disp(' ', ' ', 'X=0', 'X=1', ' ');
7 disp(' ', 'a', 'a', 'b', '0', ' ');
8 disp(' ', 'b', 'c', 'd', '0', ' ');
9 disp(' ', 'c', 'd', 'e', '1', ' ');
10 disp(' ', 'd', 'c', 'b', '0', ' ');
11 disp(' ', 'e', 'b', 'c', '1', ' ');
12 disp('For states b and d except for next state X=1
rest are same. Now b and d would have been
equivalent if these next states are equivalent .')

```

For b next state is d and d, next state is b.
 Thus bd are equivalent if next states db are
 equivalent which can always be true. Thus b and d
 are equivlent and state b is retained.'')

```

13 disp('Table after first row elimination :'); // after
       first row elimination
14 disp('Present State      Next State      Present Output');
15 disp('                  X=0      X=1      ');
16 disp('      a          a          b          0      ');
17 disp('      b          c          b          0      ');
18 disp('      c          b          e          1      ');
19 disp('      e          b          c          1      ');
20 disp('Now repeating the same above step for c and e
      . Retaining c and replacing arll c's with e we
      get the below table ');
21 disp('Table after second row elimination :'); // after
       second row elimination
22 disp('Present State      Next State      Present Output');
23 disp('                  X=0      X=1      ');
24 disp('      a          a          b          0      ');
25 disp('      b          c          b          0      ');
26 disp('      c          b          c          1      ');
27
28 disp('Implication table method'); // by implication
      method
29 printf('d:d\nce\nnb:d(Ce)(bd)\nna:(ce)(bd)a\nP=(
      ce)(bd)(a)');

```

Scilab code Exa 11.6 asynchronous sequential circuit

```

1 //example 11.6
2 clc;
3 clear;
4 disp('To analyse the circuit we consider x = X(t- )
      where      is the cummulative propagatin delay from

```

```

    input side up to X. For all possible
    combinations of xAB we get X and Y following the
    logic relation as shown in the circuit and
    prepare the following Karnaugh map');
5 disp('Karnaugh map'); // displaying the kmap
6 disp(' AB')
7 disp('x 00 01 11 10');
8 disp('0 0/0 0/0 1/0 0/0');
9 disp('1 0/0 0/1 1/1 1/0');
10 disp('State where X = x are stable and primed.
    Outputs corresponding to each state and inpt
    combination are shown beside.');

```

Scilab code Exa 11.7 asynchronous sequential circuit problem in operation

```

1 //example 11.7
2 clc;
3 clear;
4 disp('Given karnaugh map '); //given kmap
5 disp(' 00 01 11 10');
6 disp('00 11 00 11 00');
7 disp('01 01 11 11 01');
8 disp('11 10 11 11 10');
9 disp('10 10 10 11 11');
10 disp('Yes, the circuit may face problem in its
    operation. When the circuit is at stable state
    xyAB = 1111 and input AB changes from 11 --> 10
    the circuit oscillates between xyAB = 1110 and xy
    AB = 1010. Also there can be a critical race
    problem if at stable state xyAB = 0001, input AB
    change from 01 to 00. The circuit may settle at
    xyAB = 0100 or xyAB = 1000 depending on which of
    x and y changes first at the feedback path. Non-
    critical race situation occurs if at stable

```

```
state xyAB = 0010 the input AB change from 10 to  
00.');
```

check Appendix [AP 1](#) for dependency:

kmap3abx.sci

check Appendix [AP 2](#) for dependency:

noof.sci

check Appendix [AP 3](#) for dependency:

noof0.sci

Scilab code **Exa 11.8** asynchronous sequential circuit

```
1 //example 11.8  
2 // this program requires  
3 //kmp3abx.sci  
4 //noof.sci  
5 //noof0.sci  
6 //above three functions are first execute before  
executing this program  
7 clc;  
8 disp('State table through karnaugh map'); // state  
table through kmap  
9 disp('      00      01      11      10');  
10 disp('a      a      a      b      b');  
11 disp('b      a      b      b      b');  
12 disp('If we represent current state a as x = 0 and b  
as x =1 the noutput X can be expressed as ');  
13 j=[0 0 1 1 ; 0 1 1 1];  
14 J= kmap3abx(j); // finding the minimized expresion  
using 3-variable kmap  
15 disp('The minimised expression J');  
16 disp(J); // displaying the minimized expression
```

Chapter 12

D to A Conversion and A to D conversion

Scilab code Exa 12.1 binary equivalent weight of each bit in a 4bit system

```
1 //chapter 12
2 //Example 12.1
3 //Q.Find the binary equivalent of each bit in a 4-
   bit system
4 //solution :
5 clc;
6 clear;
7 LSB = 1/(2^4-1); // calculating binary weights
8 LSB2 = 2*1/(2^4-1);
9 LSB3 = 4*1/(2^4-1);
10 MSB = 8*1/(2^4-1);
11 disp("Binary weight of each bit in a 4-bit system");
12 disp("LSB ="); // displaing the result
13 disp(LSB);
14 disp("LSB2 =");
15 disp(LSB2)
16 disp("LSB3 =");
17 disp(LSB3)
18 disp("MSB =");
```

```
19 disp(MSB) ;
```

Scilab code Exa 12.2 5 bit resistive divider

```
1 //Example 12.2
2 clc;
3 clear;
4 LSB = 1/(2^5-1); // calculating weights
5 LSB2 = 2*1/(2^5-1);
6 LSB3 = 4*1/(2^5-1);
7 change_LSB = 10 *LSB;
8 change_LSB2 = 10 *LSB2;
9 change_LSB3 = 10*LSB3;
10 op_vol= (10*2^0 + 0*2^1 + 10*2^2 +0*2^3 +10*2^4)
           /(2^5-1); // calculating output voltage
11 disp(" (a) LSB =");
12 disp(LSB);
13 disp(" (b) Second LSB =");
14 disp(LSB2)
15 disp(" Third LSB3 =");
16 disp(LSB3)
17 disp(' (c) change in output voltage caused by ');
18 disp("change in LSB =");
19 disp(change_LSB);
20 disp("change in second LSB =");
21 disp(change_LSB2)
22 disp("change in third LSB =");
23 disp(change_LSB3)
24 disp(" (d)output voltage for a digital input of 10101
      =");
25 disp(op_vol) ;
```

Scilab code Exa 12.3 5 bit ladder

```
1 //Example 12.3
2 clc;
3 clear;
4 for i=1:5
5     op_v(1,i)= 10/2^i; // calculating output voltages
                           corresponding to each bit
6 end
7 disp("output voltages corresponding to each bit are
          ") //displaying result
8 disp(op_v);
```

Scilab code Exa 12.4 5 bit ladder

```
1 //Example 12.4
2 clc
3 clear
4 V_A=0
5 //a=input(" Enter the binary digit(5 bits) :");
6 a=11010
7 for i=1:5
8     r=modulo(a,10);
9     b(1,i)=r;
10    a=a/10;
11    a=floor(a);
12 end
13 for j=1:5
14 V_A = V_A + 10*b(1,j)*2^(j-1);
15 end;
16 V_A=V_A/2^5;
17 disp("The output voltage in volts is ");
18 disp(V_A); // displaying the value
```

Scilab code Exa 12.5 5 bit ladder

```
1 //Example 12.5
2 clc;
3 clear;
4 ful_scale_voltage = 0 ;
5 for i=1:5
6     op_v(1,i)= 10/2^i;
7     ful_scale_voltage = ful_scale_voltage + op_v(1,i)
        ); // calculating the full scale voltage
8 end
9 disp(" full scale output voltage in volts is =");
10 disp(ful_scale_voltage)
```

Scilab code Exa 12.6 5 bit ladder

```
1 //Example 12.6
2 clc;
3 clear;
4 I=10/(3*10^3);
5 printf("Current each input digital voltage must be
        capable of supplying is =%f mA\n",I*1000)
6 ful_scale_voltage = 0 ;
7 for i=1:5
8     op_v(1,i)= 10/2^i;
9     ful_scale_voltage = ful_scale_voltage + op_v(1,i)
        );
10 end
11 V_A=ful_scale_voltage * (2*1000)/(1000+(2*1000));
12 printf("\n Output voltage Va = %f V",V_A);
```

Scilab code Exa 12.8 DAC0808

```
1 //Example 12.8
2 clc;
```

```
3 clear;
4 V0= 10*((1/2)+(1/4)+(1/32)+(1/128)); // calculating
      voltage when 1,2,5,7 re high
5 printf("Output voltage = %f V",V0)//displayin result
```

Scilab code Exa 12.9 resolution of 9 bit D to A

```
1 //Example 12.9
2 clc;
3 clear
4 resol = 1/512 * 100 ; // calculating resol
5 vol_resol = 1/512 *5 *1000;
6 printf("Resoluition in percentage = %f",resol);
7
8 printf("\n\n Voltage resolution = %f mV",vol_resol);
```

Scilab code Exa 12.10 resolution

```
1 //Example 12.10
2 clc;
3 clear;
4 disp("The LSB of an 11-bit system has a resolution
      of 1/2048");
5 re =ceil(10000/2048); // calculting the resolution
6 printf("\n\n 1/2048 x 10 = %d mV",re);
```

Scilab code Exa 12.11 counter type A to D converter

```
1 //Example 12.11
2 clc;
```

```
3 clear;
4 //bit = input(" Specify the converter bit length :")
5 //fre = input(" specify the clock frequency in kHz
6 bit =8;
7 fre = 500
8 max_conv_time = 2^bit * (1/(fre*1000));
9 avg_conv_time = 0.5 *max_conv_time;
10 max_conv_rate = 1/max_conv_time;
11 disp("Maximum Conversion Time = ");
12 disp(max_conv_time);
13 disp(" Average Conversion Time =");
14 disp(avg_conv_time);
15 disp("Maximum Conversion Rate =");
16 disp(max_conv_rate);
```

Scilab code Exa 12.13 10 bit A to D converter

```
1 //Example 12.13
2 clc
3 clear
4 quat_err = 1/1024 *100 ;
5 disp("If the analog portion to be constructed ti an
accuracy of 0.1")
6 printf("\nThe overall accuracy is in percentage = %f
",0.1 + quat_err)
```

Chapter 13

Memory

Scilab code Exa 13.2 structure of binary address

```
1 //example 13.2
2 clc;
3 clear;
4 close;
5 //cp = input('enter the capacity of the memory
       system in bits :');
6 cp=1024; // given capacity
7 n= log2(cp);
8 printf('The no of bits in the address word are : %d\
       ',n);
9 printf('The number of required rows are : %d\n',2^(n
       /2));
10 printf('The number of required columns are : %d',2^(
       n/2));
```

Scilab code Exa 13.3 decimal and hexadecimal address for the given binary address

```
1 //example 13.3
2 clc
3 clear
4 //bin(1,1) = input('Enter the first half string of
      binary number :');
5 //bin(1,2) = input('Enter the second half string of
      binary number :');
6 bin=['10110' '01101']; // given binry address
7 dec=bin2dec(bin); // finding decimal equivlent
8 hex=dec2hex(dec); //findin hexdecimal equivalent
9 disp('The decimal address is :');
10 disp(dec);
11 disp('The hexadecimal address is :');
12 disp(hex);
```

Chapter 14

Digital Integrated circuits

Scilab code Exa 14.1 diode forward or reverse

```
1 //example 14.1
2 clc;
3 clear;
4 close;
5 vdc = input('Enter the value of DC voltage Vdc in
    volts :');
6 r = input('Enter the value of resistace in K ohms :'
    );
7 v = input(' Enter the value of voltage across diode
    in volts :');
8
9 i = (vdc-v)/r ;
10 format('v',4);
11 if(i>0) // checking whether the diode is forward or
    reverse biased by checking current
12     disp('The diode is in forward bias');
13     disp('The diode current in mA is :');
14     disp(i);
15 else
16     disp('The diode is in Reverse bias');
17     disp('The diode current in mA is : 0.0');
```

```
18 end;
```

Scilab code Exa 14.2 Diode current

```
1 //example 14.2
2 clc;
3 clear;
4 close;
5 vdc = input('Enter the value of DC voltage Vdc in
    volts :');
6 r = input('Enter the value of resistace in K ohms :',
    );
7 //v = input(' Enter the value of voltage across
    diode in volts:');
8 v= 1.6;
9 i = (vdc-v)/r; // calculating the current
10      disp('The diode current in mA is :');
11      disp(i);
```

Scilab code Exa 14.3 current in the given circuit

```
1 //example 14.3
2 clc;
3 clear;
4 close;
5 v1 = input('Enter the value of V1 in volts :'); //
    taking the inpt voltage
6 disp('CASE - a');// case a
7 if (v1==0) then
8     disp('V2 = 5 V');
9     disp('I = 0 mA');
10 else
11     disp('V2 = 0 V')
```

```
12      disp('I = 5 mA')
13 end
14 disp('CASE - b'); // case b
15 if (v1==0) then
16     disp('V2 = 5 V')
17     disp('I = 5 mA')
18 else
19     disp('V2 = 0 V');
20     disp('I = 0 mA');
21
22 end
```

Scilab code Exa 14.4 n channel MOSFET inverter

```
1 //example 14.4
2 clc;
3 clear;
4 v1 = input('Enter the value of V1 in volts :'); // part a : v1 =0 ; part b : v1 =5v
5 if (v1==0) then // checking for V1
6     disp('V2 = 5 V');
7     disp('I = 0 mA');
8 else
9     disp('V2 = 0 V');
10    disp('I = 0.5 mA ');
11 end
```

Chapter 15

Applications

Scilab code Exa 15.1 Timing of a six digit display

```
1 //example 15.1
2 //timing for a six digit display
3 clc;
4 clear;
5 //f=input('Enter the repetition rate in Hz :');
6 //d= input('Enter the length of display :');
7 f=125; // given inputs
8 d=6;
9 format('v',5); //changing the precision of the
                  calculation
10 k=1000/f;
11 l=1000/(f*d); //making neccesary calculations
12 m=k-1;
13 printf('All digits must be serviced once every %f
          milliseconds \n',k);
14 printf('Each digit will be ON for : %f milliseconds \
          \n',l) ;
15 printf('and OFF for : %f milliseconds ',m); // 
                  displaying results
```

Scilab code Exa 15.4 Basic frequency counter

```
1 //example 15.4
2 clc;
3 clear;
4 //f=input('Enter the input square wave signal
      frequency in kHz:');
5 //t=input('Enter the gate enable time in seconds ');
6 //first part :
7 f=7.50;
8 t=0.1;
9 format('v',18);
10 m=t*f*1000; //making necessary calculations
11 printf('For t = %f seconds\n',t); // displaying
      results
12 printf('The counter will count up to : %f\n',m);
13 //part2
14 t=1;
15 printf('\n\nFor t = %f seconds\n',t);
16 m=t*f*1000;
17 printf('The counter will count up to : %f\n',m);
18 //part3
19 t=10;
20 m=t*f*1000;
21 printf('\n\nFor t = %f seconds\n',t);
22 printf('The counter will count up to : %f\n',m);
```

Scilab code Exa 15.5 4 decimal digit frequency counter

```
1 //example 15.5
2 clc;
```

3 **disp**('Assuming the counter began at 0000, the display would read 200 at the end of the first measurement period. It will read 400, then 600 and so on at the end of succeeding periods. This is because the counter capacity is exceeded each time, and it simply recycles through 0000. '');

Scilab code Exa 15.6 instrument to measure time period

```
1 //example 15.6
2 clc;
3 clear;
4 //s= input('Enter the clk freqency in kHz : ');
5 //f=input('Enter the frequency of the unknown input
       in Hz : ');
6 s=100; // taking the inputs
7 f=200;
8 g=1000000/f; // making neccesary calculations
9 c=g*s/1000;
10 c=round(c);
11 p=c*1000/s;
12 disp('Assuming that the conter and the display are
       initially at 00000'); //displaying results
13 printf('Enable gate time in micro secnds will be :
       %d\n',g);
14 printf('During the gate time the counter will be
       advced by (number of counts ) %d \n',c);
15 printf('The time period of the unknown input in
       micro-seconds is : %d',p);
```

Scilab code Exa 15.9 ADC0804

```
1 //example 15.9
```

```

2 clc ;
3 clear;
4 //part (a)
5 //an=input('Enter the analog input in volts :');
6 format('v',12); // changing the precision of
      calculation
7 an=2.5;
8 k=an*1000/19.53;
9 k= round(k);
10 m=dec2bin(k); // converting from decimal to binary
11 printf('The digital output is :%s\n',m);
12 //part(b)
13 //dg=input('Enter the digital output as a string :');
14 dg='00100010';
15 f=bin2dec(dg); // converting binary to decimal
16 y=f*19.53*10^-3;
17 printf(' The analog input in volts is :%f',y);

```

Scilab code Exa 15.10 ADC3511

```

1 //example 15.10
2 clc;
3 clear;
4 //v = input('Enter the reference voltage in volts
      :');
5 //an = input('Enter the analog input voltage in
      volts :');
6 v=2; // taking given input
7 an=1.25;
8 count = 2000*an/v ;
9 count = round(count);
10 printf('The ccount held in the counter for given
      analog input will be : %f',count);
11 d= an/v;
12 printf('\nThe duty cycle is : %f',d);

```

Scilab code Exa 15.11 ADC3511

```
1 // example 15.11
2 clc;
3 clear;
4 disp('The full scale count for ADC3511 is 1999 and
      for the ADC3711 is 3999. So, the largest value
      possible for the MSD in either case is 3 = 0011.
      clearly the MSB is not needed for th magnitue of
      the MSD. It is thus convenient to specif
      positive number when this bit is a 0 and a
      negtive number when this bit is a 1 .');
```

Scilab code Exa 15.12 ADD3501

```
1 //exmple 15.12
2 clc ;
3 clear;
4 disp('These two components establish the internal
      oscillator frequency used as the clock frequency
      in the cnverter according to the relationship fi
      =0.6/RC. In this case fi=320 kHz.');
```

Chapter 16

A Simple Computer Design

Scilab code Exa 16.1 size of PC IR ACC MAR MDR

```
1 //example 16.1
2 clc
3 clear
4 //len = input('Enter the length of each memory
   location in bits :');
5 //op = input('Enter the length of Opcode:');
6 len =16;
7 op=4;
8 nop= 2^4;    // calculating
9 nab = len-op;
10 memloc = 2^nab;
11 memsize = memloc*16;
12 mem=memsize/1024;
13 printf('(a)Maximum Number of Opcodes = %d \n',nop);
   // displaying
14 printf(' (b)Size of memory in Kilo bits = %d \n',mem
   );
15 printf(' (c)Size of PC and MAR = %d \n',nab );
16 printf('   Size of IR = %d\n',op);
17 printf('   Size of ACC and MDR = %d \n',len);
```

Scilab code Exa 16.6 Number of clock cycles needed to execute a program

```
1 //example 16.6
2 lda= input('Enter the number of LDA instructions :')
   ; // accepting the input from the user
3 add= input('Enter the number of ADD instructions :')
   ;
4 sub= input('Enter the number of SUB instructions :')
   ;
5 sta= input('Enter the number of STA instructions :')
   ;
6 shl= input('Enter the number of SHL instructions :')
   ;
7 hlt= input('Enter the number of HLT instructions :')
   ;
8 k= lda+add+sub+sta;
9 l=shl+hlt;
10 c= k*5 + l*4; // calculating the total no.of clk
    cycles required
11 printf('Total clock cycles required to execute are =
    %d ',c); // displaying result.
```

Appendix

Scilab code AP 1 3-variable kmap(abx)

```
1 //3-VARIABLE KMAP
2 //uses noof.sci and noof0.sci
3 //above two functions should be executed before
   executing this function .
4 function bi = kmap3abx(k)
5     n=4;
6     m=2
7
8 //k=[0 0 0 1;
9 // 0 1 1 1];
10 k(:,:,2)=zeros(m,n);
11     var=['x' 'A' 'B'];
12 //var=['w' 'x' 'y' 'z'];
13 p1=['x',' ','x'];
14 p2=['A','B',' ','; 'A','B','; 'AB','; 'AB',' '];
15 cmn4=4;
16 cmn2=2;
17 temp=1;
18 // printf('The minimal expression of the given
   Kmap ');
19 disp(k(:,:,1));
20 //disp(" is :");
21 //printf('f');
22 //printf("=");
23
24 bi = ' ';
```

```

25 //8 cells
26 for i=1:m
27     for j=1:n
28         if(k(i,j)~=1 & k(i,j)~=2)
29             temp=0;
30             break;
31         end
32     end
33 end
34 if(temp==1)
35     bi = strcat([bi "1"]);
36     return;
37 end
38 //4 cells
39 z1=ones(1,4);
40 z2=ones(4,1);
41 z3=ones(2,2);
42 temp1=[ '0' '1'];
43 temp2=[ '00'; '01'; '11'; '10'];
44 for t=1:m
45     z=k(t,:,:1);
46     no=noof(k(t,:,:2));
47     if(noof0(z)==0 & no<cmn4 & noof(z)>0)
48         k(t,:,:2)=z1;
49         a=strsplit(temp1(1,t));
50         for in=1:max(size(a))
51             if(a(in)=='0')
52                 bi = strcat([bi var(in) ',']);
53             end
54             if(a(in)=='1')
55                 bi = strcat([bi var(in)]);
56             end
57         end
58         bi = strcat([bi " + "]);
59     end
60 end
61 for i=1:m-1

```

```

62      for j=1:n
63          t1=i+1;
64          if(j==n)
65              t2=1;
66          else
67              t2=j+1;
68          end
69          z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
70              ,1)];
70          z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
71              ,2)];
71          no=noof(z5);
72          if(noof0(z4)==0 & no<cmn4 & noof(z4)>0)
73              k(i,j,2)=1;
74              k(i,t2,2)=1;
75              k(t1,j,2)=1;
76              k(t1,t2,2)=1;
77              a=strsplit(temp2(j,1));
78              b=strsplit(temp2(t2,1));
79              c=strncmp(a,b);
80              for in=1:max(size(c))
81                  if(c(in)==0 & a(in)=='0')
82                      bi = strcat([bi var(1+in) ' '
83                          '']);
84                  end
85                  if(c(in)==0 & a(in)=='1')
86                      bi = strcat([bi var(1+in)]);
87                      ;
88                  end
89                  end
90          end
91      end
92  end
93 //2 cells
94 z6=[1 1];
95 z7=z6';

```

```

96     for i=1:m
97         for j=1:n
98             t1=i+1;
99             if(j==n)
100                 t2=1;
101             else
102                 t2=j+1;
103             end
104             z8=[k(i,j,1) k(i,t2,1)];
105             z9=[k(i,j,2) k(i,t2,2)];
106             no1=noof(z9);
107             if(noof0(z8)==0 & no1<cmn2 & noof(z8)>0)
108                 k(i,j,2)=1;
109                 k(i,t2,2)=1;
110                 bi = strcat([bi p1(1,i)]);
111                 a=strsplit(temp2(j,1));
112                 b=strsplit(temp2(t2,1));
113                 c=strcmp(a,b);
114                 for in=1:max(size(c))
115                     if(c(in)==0 & a(in)=='0')
116                         bi = strcat([bi var(1+in) ' '
117                                         '']);
118                     bi = strcat([bi " + "]);
119                     end
120                     if(c(in)==0 & a(in)=='1')
121                         bi = strcat([bi var(1+in)]);
122                         ;
123                         bi = strcat([bi " + "]);
124                     end
125                 end
126             end
127             for i=1:m-1
128                 for j=1:n
129                     t1=i+1;
130                     if(j==n)
131                         t2=1;

```

```

132     else
133         t2=j+1;
134     end
135     z10=[k(i,j,1);k(t1,j,1)];
136     z11=[k(i,j,2);k(t1,j,2)];
137     no2=noof(z11);
138     if (noof0(z10)==0 & no2<cmn2 & noof(z10)
139         >0)
140         k(i,j,2)=1;
141         k(t1,j,2)=1;
142         bi = strcat([bi p2(j,1)]);
143         bi = strcat([bi " + "]);
144     end
145 end
146 //single cell
147 for i=1:m
148     for j=1:n
149         if(k(i,j,2)==0 & k(i,j,1)==1)
150             bi = strcat([bi p1(1,i)]);
151             bi = strcat([bi p2(j,1)]);
152             bi = strcat([bi " + "]);
153         end
154     end
155 end
156 bi = strcat([bi " 0 "]);
157 //disp(" ")
158
159 endfunction

```

Scilab code AP 2 returns number of 1s in a matrix

```

1 function res=noof(a) // this function returns the
2     no of 1's in the given matrix
3     res=0;
4     for i=1:max(size(a(:,1)))
5         for j=1:max(size(a(1,:)))
6             if(a(i,j)==1)

```

```

6             res=res+1;
7         end
8     end
9 end
10 endfunction

```

Scilab code AP 3 returns number of 0s in a matrix

```

1 function res=noof0(a) // to find the no of zeros in
    given matrix
2 res=0;
3 for i=1:max(size(a(:,1)))
4     for j=1:max(size(a(1,:)))
5         if(a(i,j)==0)
6             res=res+1;
7         end
8     end
9 end
10 endfunction

```

Scilab code AP 4 4-variable kmap with don't cares

```

1 //4-Variable KMAP
2 //returns a string of the minimized expression
3 //requires noof1.sci
4 //noof1.sci should be executed before executing this
    function
5 function bi = donkmapij(k)
6     n=4;
7     k(:,:,2)=zeros(n,n);
8     var=['I' 'J' 'Bn' 'An'];
9     p1=['I' 'J' '' 'I' 'J' 'IJ' 'IJ' ''];
10    p2=['Bn' 'An' '' ; 'Bn' 'An' ; 'BnAn' ; 'BnAn' '' ];
11    cmn4=4;
12    cmn2=2;
13    temp=1;
14    bi=' ';
15    disp(k(:,:,1));

```

```

16     for i=1:n
17         for j=1:n
18             if(k(i,j) ~= 1 | k(i,j) ~= 2)
19                 temp=0;
20                 break;
21             end
22         end
23     end
24     if(temp==1)
25         printf("1");
26         abort;
27     end
28 //checking the 8 cells cases
29 z1=ones(2,4);
30 z2=ones(4,2);
31 temp1=['00' '01' '11' '10'];
32 temp2=temp1';
33 for i=1:n
34     if(i==4)
35         t=1;
36     else
37         t=i+1;
38     end
39 z=[k(i,:,1);k(t,:,1)];
40 if(noof1(z,0)==0 & noof1(z,1)>1)
41     k(i,:,2)=[1 1 1 1];
42     k(t,:,2)=[1 1 1 1];
43     a=strsplit(temp2(i,1));
44     b=strsplit(temp2(t,1));
45     c=strncmp(a,b);
46     for in=1:max(size(c))
47         if(c(in)==0 & a(in)=='0')
48             bi = strcat([bi var(in) ' ']);
49         bi = strcat([bi " + "]);
50         break;
51     else
52         if(c(in)==0 & a(in)=='1')

```

```

53                      bi = strcat([bi var(in)])
54                      ;
55                      bi = strcat([bi " + "]);
56                      break;
57                  end
58              end
59          end
60      end
61      for j=1:n
62          if (j==4)
63              t=1;
64          else
65              t=j+1;
66          end
67          z=[k(:,j,1) k(:,t,1)];
68          if (noof1(z,0)==0 & noof1(z,1)>0)
69              k(:,j,2)=[1;1;1;1];
70              k(:,t,2)=[1;1;1;1];
71              a=strsplit(temp1(1,j));
72              b=strsplit(temp1(1,t));
73              c=strcmp(a,b);
74              for in=1:max(size(c))
75                  if (c(in)==0 & a(in)=='0')
76                      bi = strcat([bi var(2+in) ' '])
77                      ;
78                      bi = strcat([bi " + "]);
79                      break;
80                  else
81                      if (c(in)==0 & a(in)=='1')
82                          bi = strcat([bi var(2+in)]);
83                          ;
84                          bi = strcat([bi " + "]);
85                          break;
86                      end
87                  end
88              end
89          end
90      end
91  end

```

```

88    end
89    //checking the 4 cells cases
90    z1=ones(1,4);
91    z2=ones(4,1);
92    z3=ones(2,2);
93    temp1=[ '00' '01' '11' '10'];
94    temp2=temp1';
95    for t=1:n
96        z=k(t,:,:1);
97        no=noof1(k(t,:,:2),1);
98        if (noof1(z,0)==0 & no<cmn4 & noof1(z,1)
99            >0)
100            k(t,:,:2)=z1;
101            a=strsplit(temp1(1,t));
102            for in=1:max(size(a))
103                if (a(in)=='0')
104                    bi = strcat([bi var(in) ' ']);
105                end
106                if (a(in)=='1')
107                    bi = strcat([bi var(in)]);
108                end
109                bi = strcat([bi " + "]);
110            end
111        end
112        for t=1:n
113            z=k(:,t,1);
114            no=noof1(k(:,t,2),1);
115            if (noof1(z,0)==0 & no<cmn4 & noof1(z,1)>0)
116                k(:,t,2)=z2;
117                a=strsplit(temp2(t,1));
118                for in=1:max(size(a))
119                    if (a(in)=='0')
120                        bi = strcat([bi var(2+in) ' '']);
121                    end
122                    if (a(in)=='1')

```

```

123             bi = strcat([bi var(2+in)]);
124         end
125     end
126     bi = strcat([bi " + "]");
127 end
128 end
129 for i=1:n
130     for j=1:n
131         if(i==n)
132             t1=1;
133         else
134             t1=i+1;
135         end
136         if(j==n)
137             t2=1;
138         else
139             t2=j+1;
140         end
141         z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
142             ,1)];
143         z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
144             ,2)];
145         no=noof1(z5,1);
146         if(noof1(z4,0)==0 & no<cmn4 & noof1(z4
147             ,1)>0)
148             k(i,j,2)=1;
149             k(i,t2,2)=1;
150             k(t1,j,2)=1;
151             k(t1,t2,2)=1;
152             a=strsplit(temp2(i,1));
153             b=strsplit(temp2(t1,1));
154             c=strcmp(a,b);
155             for in=1:max(size(c))
156                 if(c(in)==0 & a(in)=='0')
157                     bi = strcat([bi ,var(in) ' '
158                         '']);
159                 end
160                 if(c(in)==0 & a(in)=='1')

```

```

157                      bi = strcat([bi var(in)]);
158                  end
159              end
160          a=strsplit(temp1(1,j));
161          b=strsplit(temp1(1,t2));
162          c=strncmp(a,b);
163          for in=1:max(size(c))
164              if(c(in)==0 & a(in)=='0')
165                  bi = strcat([bi ,var(2+in) ' ']);
166              end
167              if(c(in)==0 & a(in)=='1')
168                  bi = strcat([bi var(2+in)]);
169              ;
170          end
171          bi = strcat([bi " + "]);
172      end
173  end
174 //2 cells
175 z6=[1 1];
176 z7=z6';
177 for i=1:n
178     for j=1:n
179         if(i==n)
180             t1=1;
181         else
182             t1=i+1;
183         end
184         if(j==n)
185             t2=1;
186         else
187             t2=j+1;
188         end
189         z8=[k(i,j,1) k(i,t2,1)];
190         z9=[k(i,j,2) k(i,t2,2)];
191         no1=noof1(z9,1);
192

```

```

193      if (noof1(z8,0)==0 & no1<cmn2 & noof1(z8
194          ,1)>0)
195          k(i,j,2)=1;
196          k(i,t2,2)=1;
197          a=strsplit(temp1(1,j));
198          b=strsplit(temp1(1,t2));
199          c=strcmp(a,b);
200          for in=1:max(size(c))
201              if (c(in)==0 & a(in)=='0')
202                  bi = strcat([bi p1(1,i)]);
203                  bi = strcat([bi ,var(2+in) ,
204                      '']);
205                  bi = strcat([bi " + "]);
206              end
207              if (c(in)==0 & a(in)=='1')
208                  bi = strcat([bi p1(1,i)]);
209                  bi = strcat([bi var(2+in)])
210                      ;
211                  bi = strcat([bi " + "]);
212              end
213          end
214      for i=1:n
215          for j=1:n
216              if (i==n)
217                  t1=1;
218              else
219                  t1=i+1;
220              end
221              if (j==n)
222                  t2=1;
223              else
224                  t2=j+1;
225              end
226              z10=[k(i,j,1);k(t1,j,1)];
227              z11=[k(i,j,2);k(t1,j,2)];

```

```

228     no2=noof1(z11,1);
229     if(noof1(z10,0)==0 & no2<cmn2 & noof1(
230         z10,1)>0)
231         k(i,j,2)=1;
232         k(t1,j,2)=1;
233         a=strsplit(temp2(i,1));
234         b=strsplit(temp2(t1,1));
235         c=strcmp(a,b);
236         for in=1:max(size(c))
237             if(c(in)==0 & a(in)=='0')
238                 bi = strcat([bi p2(j,1)]);
239                 bi = strcat([bi var(in) ' ']);
240                 bi = strcat([bi " + "]);
241             end
242             if(c(in)==0 & a(in)=='1')
243                 bi = strcat([bi p2(j,1)]);
244                 bi = strcat([bi var(in)]);
245                 bi = strcat([bi " + "]);
246             end
247         end
248     end
249 end
//checking the single cell cases
for i=1:n
    for j=1:n
        if(k(i,j,2)==0 & k(i,j,1)==1)
            a=strsplit(temp1(1,j));
            b=strsplit(temp2(i,1));
            for in=1:max(size(a(:,1)))
                if(a(in,1)=='1')
                    bi = strcat([bi var(in+2)]);
                else
                    if(a(in,1)=='0')
                        bi = strcat([bi var(2+in)
                            ' '']);
                end
            end
        end
    end
end

```

```

263         end
264     end
265     for in=1:max(size(b(:,1)))
266         if(b(in,1)=='1')
267             bi = strcat([bi var(in)]);
268         else
269             if(b(in,1)=='0')
270                 bi = strcat([bi var(in)
271                             ' ' ']);
272             end
273         end
274         bi = strcat([bi " + "]);
275     end
276 end
277 bi = strcat([bi "0 "]);
278
279 endfunction

```

Scilab code AP 5 number of zeros and ones

```

1 function res=noof1(a,z) //this function returns both
    the no of zeros and ones in given matrix
2 res=0;
3 for i=1:max(size(a(:,1)))
4     for j=1:max(size(a(1,:)))
5         if(a(i,j)==z)
6             res=res+1;
7         end
8     end
9 end
10 endfunction

```

Scilab code AP 6 3-variable kmap(a)

```

1
2 //3-VARIABLE KMAP

```

```

3 // this function returns the a string containing the
   minimized expression for the given 3 variable
   kmap
4 //this function requires
5 //noof.sci
6 //noof0.sci
7 function bi = kmap3a(k)
8     n=4;
9     m=2
10    k(:,:,2)=zeros(m,n);
11    var=[ 'An' 'X' 'Y'];
12    p1=[ 'An' ' ' 'An'];
13    p2=[ 'X' 'Y' ' ' ; 'X' 'Y' ; 'XY' ; 'XY' ' '];
14
15    cmn4=4;
16    cmn2=2;
17    temp=1;
18    disp(k(:,:,1));
19    bi = ' ';
20 //checking all the 8 1's cases
21    for i=1:m
22        for j=1:n
23            if(k(i,j) ~= 1 & k(i,j) ~= 2)
24                temp=0;
25                break;
26            end
27        end
28    end
29    if(temp==1)
30        bi = strcat([bi "1"]);
31        return;
32    end
33 //checking all the 4 1's cases
34    z1=ones(1,4);
35    z2=ones(4,1);
36    z3=ones(2,2);
37    temp1=[ '0' '1' ];
38    temp2=[ '00' ; '01' ; '11' ; '10' ];

```

```

39   for t=1:m
40       z=k(t,: ,1);
41       no=noof(k(t,: ,2));
42       if (noof0(z)==0 & no<cmn4 & noof(z)>0)
43           k(t,: ,2)=z1;
44           a=strsplit(temp1(1,t));
45           for in=1:max(size(a))
46               if (a(in)== '0 ')
47                   bi = strcat([bi var(in) ' '']);
48               end
49               if (a(in)== '1 ')
50                   bi = strcat([bi var(in)]);
51               end
52           end
53           bi = strcat([bi " "]);
54       end
55   end
56   for i=1:m-1
57       for j=1:n
58           t1=i+1;
59           if (j==n)
60               t2=1;
61           else
62               t2=j+1;
63           end
64           z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
65               ,1)];
66           z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
67               ,2)];
68           no=noof(z5);
69           if (noof0(z4)==0 & no<cmn4 & noof(z4)>0)
70               k(i,j,2)=1;
71               k(i,t2,2)=1;
72               k(t1,j,2)=1;
73               k(t1,t2,2)=1;
74               a=strsplit(temp2(j,1));
75               b=strsplit(temp2(t2,1));

```

```

74         c=strcmp(a,b);
75         for in=1:max(size(c))
76             if(c(in)==0 & a(in)=='0')
77                 bi = strcat([bi var(1+in) ' '
78                             ]);;
79             end
80             if(c(in)==0 & a(in)=='1')
81                 bi = strcat([bi var(1+in)]);
82             ;
83         end
84     end
85 end
86 end
87 end
88 //checking all the 2 1's cases
89 z6=[1 1];
90 z7=z6';
91 for i=1:m
92     for j=1:n
93         t1=i+1;
94         if(j==n)
95             t2=1;
96         else
97             t2=j+1;
98         end
99         z8=[k(i,j,1) k(i,t2,1)];
100        z9=[k(i,j,2) k(i,t2,2)];
101        no1=noof(z9);
102        if(noof0(z8)==0 & no1<cmn2 & noof(z8)>0)
103            k(i,j,2)=1;
104            k(i,t2,2)=1;
105            bi = strcat([bi p1(1,i)]);
106            a=strsplit(temp2(j,1));
107            b=strsplit(temp2(t2,1));
108            c=strcmp(a,b);
109            for in=1:max(size(c))

```

```

110          if(c(in)==0 & a(in)=='0')
111              bi = strcat([bi var(1+in) ' '
112                           '']);
113          end
114          if(c(in)==0 & a(in)=='1')
115              bi = strcat([bi var(1+in)]);
116              ;
117          bi = strcat([bi " + "]);
118      end
119  end
120 end
121 end
122 for i=1:m-1
123     for j=1:n
124         t1=i+1;
125         if(j==n)
126             t2=1;
127         else
128             t2=j+1;
129         end
130         z10=[k(i,j,1);k(t1,j,1)];
131         z11=[k(i,j,2);k(t1,j,2)];
132         no2=noof(z11);
133         if(noof0(z10)==0 & no2<cmn2 & noof(z10)
134             >0)
135             k(i,j,2)=1;
136             k(t1,j,2)=1;
137             bi = strcat([bi p2(j,1)]);
138             bi = strcat([bi " + "]);
139         end
140     end
141 //checking if any single isolated 1's are left
142 for i=1:m
143     for j=1:n
144         if(k(i,j,2)==0 & k(i,j,1)==1)

```

```

145          bi = strcat([bi p1(1,i)]);
146          bi = strcat([bi p2(j,1)]);
147          bi = strcat([bi " + "]);
148      end
149  end
150 end
151 bi = strcat([bi " 0 "]);
152 endfunction

```

Scilab code AP 7 2-variable kmap

```

1 //this function minimizes a two variable boolean
   expression using kmap
2 function bi =kmap2(k)
3 var=[ 'A' 'B' , 'A' 'B' 'AB' 'AB' , ]
4 temp =1
5 for i=1:2 // intially checking for all 1's
6   for j=1:2
7     if k(i,j)==1 then
8       temp = temp + 1;
9     end
10    end
11  end
12 v=0;
13 bi = ' ' ;
14 if temp == 5 then
15   disp("The minimal expression is : 1");
16   v=1;
17 else
18 for i= 1 : 2 // considering all 2 1's cases
19   if k(i,1) == 1 & k(i,2) == 1 then
20     if i== 1 then
21       bi = strcat ([ bi 'A' , ] ) ;v=1;
22     else
23       bi = strcat ([ bi 'A' ] ) ;v=1;
24     end
25   bi = strcat ([ bi " + " ] );
26 end

```

```

27     if k(1,i) == 1 & k(2,i) == 1 then
28         if i== 1 then
29             bi = strcat ([ bi 'B' ''] );v=1;
30         else
31             bi = strcat ([ bi 'B'] );v=1;
32         end
33     end
34 end
35 end;
36 one(1)=k(2,1);
37 f=2;m=2;i=1;
38 for j=1:2
39     one(f)=k(i,j)
40     f=f+1;
41 end
42 i=2;
43 for j=2:-1:1
44     one(f)=k(i,j)
45     f=f+1;
46 end
47 one(6)=k(1,1);
48 if v==0 then // for isolated 1's
49     for i =2:5
50         if one(i)==1 & one(i+1)== 0 & one(i-1) ==0
51             then
52                 if m>0
53                     bi = strcat ([ bi " + "]);
54                     end;
55                     bi = strcat ([ bi var(i-1)]);
56                     m=m+1;
57             end
58     end
59 endfunction // final result will be stored in bi

```

Scilab code AP 8 3-variable kmap

1 //3-VARIABLE KMAP

```

2 // this function returns the a string containing the
   minimized expression for the given 3 variable
   kmap
3 //this function requires
4 //noof.sci
5 //noof0.sci
6 function bi = kmap3(k)
7     n=4;
8     m=2
9 k(:,:,2)=zeros(m,n);
10    var=[ 'Cn' 'Bn' 'An' ];
11    p1=[ 'Cn' '' 'Cn' ];
12    p2=[ 'Bn' 'An' '' ; 'Bn' 'An' ; 'BnAn' ; 'BnAn' '' ] ;
13    cmn4=4;
14    cmn2=2;
15    temp=1;
16    disp(k(:,:,1));
17 bi = ' ';
18 //checking all the 8 1's cases
19    for i=1:m
20        for j=1:n
21            if(k(i,j) ~= 1 & k(i,j) ~= 2)
22                temp=0;
23                break;
24            end
25        end
26    end
27    if(temp==1)
28        bi = strcat([bi "1"]);
29        return;
30    end
31 //checking all the 4 1's cases
32 z1=ones(1,4);
33 z2=ones(4,1);
34 z3=ones(2,2);
35 temp1=[ '0' '1' ];
36 temp2=[ '00' ; '01' ; '11' ; '10' ];
37 for t=1:m

```

```

38      z=k(t,:,1);
39      no=noof(k(t,:,2));
40      if (noof0(z)==0 & no<cmn4 & noof(z)>0)
41          k(t,:,2)=z1;
42          a=strsplit(temp1(1,t));
43          for in=1:max(size(a))
44              if (a(in)=='0')
45                  bi = strcat([bi var(in) ' ', ]);
46              end
47              if (a(in)=='1')
48                  bi = strcat([bi var(in)]);
49              end
50          end
51          bi = strcat([bi " + "]);
52      end
53  end
54  for i=1:m-1
55      for j=1:n
56          t1=i+1;
57          if (j==n)
58              t2=1;
59          else
60              t2=j+1;
61          end
62          z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
63          ,1)];
64          z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
65          ,2)];
66          no=noof(z5);
67          if (noof0(z4)==0 & no<cmn4 & noof(z4)>0)
68              k(i,j,2)=1;
69              k(i,t2,2)=1;
70              k(t1,j,2)=1;
71              k(t1,t2,2)=1;
72              a=strsplit(temp2(j,1));
73              b=strsplit(temp2(t2,1));
74              c=strcmp(a,b);

```

```

73         for in=1:max(size(c))
74             if(c(in)==0 & a(in)=='0')
75                 bi = strcat([bi var(1+in) ' '
76                               ]);;
76             end
77             if(c(in)==0 & a(in)=='1')
78                 bi = strcat([bi var(1+in)]);
79             end
80         end
81         bi = strcat([bi " "]);
82     end
83     end
84 end
85 end
86 //checking all the 2 1's cases
87 z6=[1 1];
88 z7=z6';
89 for i=1:m
90     for j=1:n
91         t1=i+1;
92         if(j==n)
93             t2=1;
94         else
95             t2=j+1;
96         end
97         z8=[k(i,j,1) k(i,t2,1)];
98         z9=[k(i,j,2) k(i,t2,2)];
99         no1=noof(z9);
100        if(noof0(z8)==0 & no1<cmn2 & noof(z8)>0)
101            k(i,j,2)=1;
102            k(i,t2,2)=1;
103            bi = strcat([bi p1(1,i)]);
104            a=strsplit(temp2(j,1));
105            b=strsplit(temp2(t2,1));
106            c=strcmp(a,b);
107            for in=1:max(size(c))
108                if(c(in)==0 & a(in)=='0')

```

```

109          bi = strcat([bi var(1+in) ''
110                      ,']);
110          bi = strcat([bi " + "]);
111      end
112      if(c(in)==0 & a(in)=='1')
113          bi = strcat([bi var(1+in)]);
114          ;
114          bi = strcat([bi " + "]);
115      end
116      end
117      end
118  end
119  end
120  for i=1:m-1
121      for j=1:n
122          t1=i+1;
123          if(j==n)
124              t2=1;
125          else
126              t2=j+1;
127          end
128          z10=[k(i,j,1);k(t1,j,1)];
129          z11=[k(i,j,2);k(t1,j,2)];
130          no2=noof(z11);
131          if(noof0(z10)==0 & no2<cmn2 & noof(z10)
131              >0)
132              k(i,j,2)=1;
133              k(t1,j,2)=1;
134              bi = strcat([bi p2(j,1)]);
135              bi = strcat([bi " + "]);
136          end
137      end
138  end
139 //checking if any single isolated 1's are left
140 for i=1:m
141     for j=1:n
142         if(k(i,j,2)==0 & k(i,j,1)==1)
143             bi = strcat([bi p1(1,i)]);

```

```

144             bi = strcat([bi p2(j,1)]);
145             bi = strcat([bi " + "]);
146         end
147     end
148 end
149 bi = strcat([bi " 0 "]);
150 endfunction

```

Scilab code AP 9 4-variable kmap(sx1x2)

```

1 function []=kmapsx(k) // this fnctions prints the
    minimied expression for the given kmap .
2 // it requires noof.sci
3 //so the above mentioned function shoub be execute
    before executing this function .
4
5 n=4;
6 k(:,:,2)=zeros(n,n);
7 var=['X2' 'X3' 'S' 'X1'];
8
9 p1=[ 'X2' 'X3' ' ' 'X2' 'X3' 'X2X3' 'X2X3' ' '];
10 p2=[ 'S' 'X1' ' ' ; 'S' 'X1' ; 'SX1' ; 'SX1' ' '];
11 cmn4=4;
12 cmn2=2;
13 temp=1;
14 disp(k(:,:,1));
15 disp(" is :");
16 disp(" ")
17 //checking the 16 cells case
18 for i=1:n
19     for j=1:n
20         if(k(i,j) ~=1)
21             temp=0;
22             break;
23         end
24     end
25 end
26 printf('      ');

```

```

27     if(temp==1)
28         printf("1");
29         abort;
30     end
31 // checking the 8 cells cases
32 z1=ones(2,4);
33 z2=ones(4,2);
34 temp1=['00' '01' '11' '10'];
35 temp2=temp1';
36 for i=1:n
37     if(i==4)
38         t=1;
39     else
40         t=i+1;
41     end
42 z=[k(i,:,:1);k(t,:,:1)];
43 if(z==z1)
44     k(i,:,:2)=[1 1 1 1];
45     k(t,:,:2)=[1 1 1 1];
46     a=strsplit(temp2(i,1));
47     b=strsplit(temp2(t,1));
48     c=strcmp(a,b);
49     for in=1:max(size(c))
50         if(c(in)==0 & a(in)=='0')
51             printf('%s ',var(in));
52             printf(' + ');
53             break;
54         else
55             if(c(in)==0 & a(in)=='1')
56                 printf(var(in));
57                 printf(' + ');
58                 break;
59             end
60         end
61     end
62 end
63 end
64 for j=1:n

```

```

65      if (j==4)
66          t=1;
67      else
68          t=j+1;
69      end
70      z=[k(:,j,1) k(:,t,1)];
71      if (z==z2)
72          k(:,j,2)=[1;1;1;1];
73          k(:,t,2)=[1;1;1;1];
74          a=strsplit(temp1(1,j));
75          b=strsplit(temp1(1,t));
76          c=strcmp(a,b);
77          for in=1:max(size(c))
78              if(c(in)==0 & a(in)=='0')
79                  printf('%,',var(2+in));
80                  printf(' + ');
81                  break;
82              else
83                  if(c(in)==0 & a(in)=='1')
84                      printf(var(2+in));
85                      printf(' + ');
86                      break;
87                  end
88              end
89          end
90      end
91  end
92 //checking the 4 cells cases
93 z1=ones(1,4);
94 z2=ones(4,1);
95 z3=ones(2,2);
96 temp1=['00' '01' '11' '10'];
97 temp2=temp1';
98 for t=1:n
99     z=k(t,:,:);
100    no=noof(k(t,:,:));
101    if(z==z1 & no<cmn4)
102        k(t,:,:)=z1;

```

```

103      a=strsplit(temp1(1,t));
104      for in=1:max(size(a))
105          if(a(in)=='0')
106              printf(' %s ',var(in));
107          end
108          if(a(in)=='1')
109              printf(var(in));
110          end
111      end
112      printf(" + ");
113  end
114 end
115 for t=1:n
116     z=k(:,t,1);
117     no=noof(k(:,t,2));
118     if(z==z2 & no<cmn4)
119         k(:,t,2)=z2;
120         a=strsplit(temp2(t,1));
121         for in=1:max(size(a))
122             if(a(in)=='0')
123                 printf(' %s ',var(2+in));
124             end
125             if(a(in)=='1')
126                 printf(var(2+in));
127             end
128         end
129         printf(" + ");
130     end
131 end
132 for i=1:n
133     for j=1:n
134         if(i==n)
135             t1=1;
136         else
137             t1=i+1;
138         end
139         if(j==n)
140             t2=1;

```

```

141     else
142         t2=j+1;
143     end
144     z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
145             ,1)];
145     z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
146             ,2)];
146     no=noof(z5);
147     if (z4==z3 & no<cmn4)
148         k(i,j,2)=1;
149         k(i,t2,2)=1;
150         k(t1,j,2)=1;
151         k(t1,t2,2)=1;
152         a=strsplit(temp2(i,1));
153         b=strsplit(temp2(t1,1));
154         c=strcmp(a,b);
155         for in=1:max(size(c))
156             if (c(in)==0 & a(in)=='0')
157                 printf('%s',var(in));
158             end
159             if (c(in)==0 & a(in)=='1')
160                 printf(var(in));
161             end
162         end
163         a=strsplit(temp1(1,j));
164         b=strsplit(temp1(1,t2));
165         c=strcmp(a,b);
166         for in=1:max(size(c))
167             if (c(in)==0 & a(in)=='0')
168                 printf('%s',var(2+in));
169             end
170             if (c(in)==0 & a(in)=='1')
171                 printf(var(2+in));
172             end
173         end
174         printf(" + ");
175     end
176 end

```

```

177    end
178    //checking all the 2 cells cases
179    z6=[1 1];
180    z7=z6';
181    for i=1:n
182        for j=1:n
183            if(i==n)
184                t1=1;
185            else
186                t1=i+1;
187            end
188            if(j==n)
189                t2=1;
190            else
191                t2=j+1;
192            end
193            z8=[k(i,j,1) k(i,t2,1)];
194            z9=[k(i,j,2) k(i,t2,2)];
195            no1=noof(z9);
196            if(z8==z6 & no1<cmn2 )
197                k(i,j,2)=1;
198                k(i,t2,2)=1;
199                a=strsplit(temp1(1,j));
200                b=strsplit(temp1(1,t2));
201                c=strcmp(a,b);
202                for in=1:max(size(c))
203                    if(c(in)==0 & a(in)=='0')
204                        printf(p1(1,i));
205                        printf(' %s ',var(2+in));
206                        printf(" + ");
207                    end
208                    if(c(in)==0 & a(in)=='1')
209                        printf(p1(1,i));
210                        printf(var(2+in));
211                        printf(" + ");
212                    end
213                end
214            end

```

```

215         end
216     end
217     for i=1:n
218         for j=1:n
219             if(i==n)
220                 t1=1;
221             else
222                 t1=i+1;
223             end
224             if(j==n)
225                 t2=1;
226             else
227                 t2=j+1;
228             end
229             z10=[k(i,j,1);k(t1,j,1)];
230             z11=[k(i,j,2);k(t1,j,2)];
231             no2=noof(z11);
232             if(z10==z7 & no2<cmn2)
233                 k(i,j,2)=1;
234                 k(t1,j,2)=1;
235                 a=strsplit(temp2(i,1));
236                 b=strsplit(temp2(t1,1));
237                 c=strcmp(a,b);
238                 for in=1:max(size(c))
239                     if(c(in)==0 & a(in)=='0')
240                         printf(p2(j,1));
241                         printf(' %s ',var(in));
242                         printf(" + ");
243                     end
244                     if(c(in)==0 & a(in)=='1')
245                         printf(p2(j,1));
246                         printf(var(in));
247                         printf(" + ");
248                     end
249                 end
250             end
251         end
252     end

```

```

253 // checking all the single cell cases
254 for i=1:n
255     for j=1:n
256         if(k(i,j,2)==0 & k(i,j,1)==1)
257             a=strsplit(temp1(1,j));
258             b=strsplit(temp2(i,1));
259             for in=1:max(size(a(:,1)))
260                 if(a(in,1)=='1')
261                     printf(var(in+2));
262                 else
263                     if(a(in,1)=='0')
264                         printf('"%s"', var(2+in))
265                         ;
266                     end
267                 end
268             for in=1:max(size(b(:,1)))
269                 if(b(in,1)=='1')
270                     printf(var(in));
271                 else
272                     if(b(in,1)=='0')
273                         printf('"%s"', var(in));
274                     end
275                 end
276             end
277             if(i~=4 & j~=4)
278                 printf(" + ");
279             end
280         end
281     end
282 end
283 printf("0");
284 endfunction

```

Scilab code AP 10 4-variable kmap

```

2 // this function prints the minimal expression of a
   given 4-variable kmap
3 // this program requires noof.sci
4 function []=kmap(k)
5     n=4;
6     k(:,:,2)=zeros(n,n);
7     var=['A' 'B' 'C' 'D'];
8 p1=[ 'A' 'B' ' ' 'A' 'B' 'AB' 'AB' ' '];
9 p2=[ 'C' 'D' ' ' ; 'C' 'D' ; 'CD' ; 'CD' ' '];
10    cmn4=4;
11    cmn2=2;
12    temp=1;
13    disp(k(:,:,1));
14    disp(" is :");
15    disp(" ")
16    //checking for 16 cells
17    for i=1:n
18        for j=1:n
19            if(k(i,j)~=1)
20                temp=0;
21                break;
22            end
23        end
24    end
25    printf('      ');
26    if(temp==1)
27        printf("1");
28        abort;
29    end
30    //checking 8 cells cases
31 z1=ones(2,4);
32 z2=ones(4,2);
33 temp1=['00' '01' '11' '10'];
34 temp2=temp1';
35 for i=1:n
36     if(i==4)
37         t=1;
38     else

```

```

39          t=i+1;
40      end
41 z=[k(i,:,:1);k(t,:,:1)];
42 if(z==z1)
43     k(i,:,:2)=[1 1 1 1];
44     k(t,:,:2)=[1 1 1 1];
45     a=strsplit(temp2(i,1));
46     b=strsplit(temp2(t,1));
47     c=strncmp(a,b);
48     for in=1:max(size(c))
49         if(c(in)==0 & a(in)=='0')
50             printf('%s',var(in));
51             printf(' + ');
52             break;
53         else
54             if(c(in)==0 & a(in)=='1')
55                 printf(var(in));
56                 printf(' + ');
57                 break;
58             end
59         end
60     end
61 end
62 end
63 for j=1:n
64     if(j==4)
65         t=1;
66     else
67         t=j+1;
68     end
69 z=[k(:,j,1) k(:,t,1)];
70 if(z==z2)
71     k(:,j,2)=[1;1;1;1];
72     k(:,t,2)=[1;1;1;1];
73     a=strsplit(temp1(1,j));
74     b=strsplit(temp1(1,t));
75     c=strncmp(a,b);
76     for in=1:max(size(c))

```

```

77         if(c(in)==0 & a(in)=='0')
78             printf('%,',var(2+in));
79             printf(' + ');
80             break;
81         else
82             if(c(in)==0 & a(in)=='1')
83                 printf(var(2+in));
84                 printf(' + ');
85                 break;
86             end
87         end
88     end
89 end
90
91 //checking all 4 cells cases
92 z1=ones(1,4);
93 z2=ones(4,1);
94 z3=ones(2,2);
95 temp1=['00' '01' '11' '10'];
96 temp2=temp1';
97 for t=1:n
98     z=k(t,: ,1);
99     no=noof(k(t,: ,2));
100    if(z==z1 & no<cmn4)
101        k(t,: ,2)=z1;
102        a=strsplit(temp1(1,t));
103        for in=1:max(size(a))
104            if(a(in)=='0')
105                printf('%,',var(in));
106            end
107            if(a(in)=='1')
108                printf(var(in));
109            end
110        end
111        printf(" + ");
112    end
113 end
114 for t=1:n

```

```

115      z=k(:,t,1);
116      no=noof(k(:,t,2));
117      if(z==z2 & no<cmn4)
118          k(:,t,2)=z2;
119          a=strsplit(temp2(t,1));
120          for in=1:max(size(a))
121              if(a(in)=='0')
122                  printf('%.s',var(2+in));
123              end
124              if(a(in)=='1')
125                  printf(var(2+in));
126              end
127          end
128          printf(" + ");
129      end
130  end
131  for i=1:n
132      for j=1:n
133          if(i==n)
134              t1=1;
135          else
136              t1=i+1;
137          end
138          if(j==n)
139              t2=1;
140          else
141              t2=j+1;
142          end
143          z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
144          ,1)];
145          z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
146          ,2)];
147          no=noof(z5);
148          if(z4==z3 & no<cmn4)
149              k(i,j,2)=1;
150              k(i,t2,2)=1;

```

```

151         a=strsplit(temp2(i,1));
152         b=strsplit(temp2(t1,1));
153         c=strcmp(a,b);
154         for in=1:max(size(c))
155             if(c(in)==0 & a(in)=='0')
156                 printf(' %s ',var(in));
157             end
158             if(c(in)==0 & a(in)=='1')
159                 printf(var(in));
160             end
161         end
162         a=strsplit(temp1(1,j));
163         b=strsplit(temp1(1,t2));
164         c=strcmp(a,b);
165         for in=1:max(size(c))
166             if(c(in)==0 & a(in)=='0')
167                 printf(' %s ',var(2+in));
168             end
169             if(c(in)==0 & a(in)=='1')
170                 printf(var(2+in));
171             end
172         end
173         printf(" + ");
174     end
175 end
176 //checking all 2 cells cases
177 z6=[1 1];
178 z7=z6';
179 for i=1:n
180     for j=1:n
181         if(i==n)
182             t1=1;
183         else
184             t1=i+1;
185         end
186         if(j==n)
187             t2=1;

```

```

189     else
190         t2=j+1;
191     end
192     z8=[k(i,j,1) k(i,t2,1)];
193     z9=[k(i,j,2) k(i,t2,2)];
194     no1=noof(z9);
195     if(z8==z6 & no1<cmn2 )
196         k(i,j,2)=1;
197         k(i,t2,2)=1;
198         a=strsplit(temp1(1,j));
199         b=strsplit(temp1(1,t2));
200         c=strcmp(a,b);
201         for in=1:max(size(c))
202             if(c(in)==0 & a(in)=='0')
203                 printf(p1(1,i));
204                 printf(' %s ',var(2+in));
205                 printf(" + ");
206             end
207             if(c(in)==0 & a(in)=='1')
208                 printf(p1(1,i));
209                 printf(var(2+in));
210                 printf(" + ");
211             end
212         end
213     end
214   end
215 end
216 for i=1:n
217   for j=1:n
218     if(i==n)
219       t1=1;
220     else
221       t1=i+1;
222     end
223     if(j==n)
224       t2=1;
225     else
226       t2=j+1;

```

```

227     end
228     z10=[k(i,j,1);k(t1,j,1)];
229     z11=[k(i,j,2);k(t1,j,2)];
230     no2=noof(z11);
231     if(z10==z7 & no2<cmn2)
232         k(i,j,2)=1;
233         k(t1,j,2)=1;
234         a=strsplit(temp2(i,1));
235         b=strsplit(temp2(t1,1));
236         c=strcmp(a,b);
237         for in=1:max(size(c))
238             if(c(in)==0 & a(in)=='0')
239                 printf(p2(j,1));
240                 printf(' %s ',var(in));
241                 printf(" + ");
242             end
243             if(c(in)==0 & a(in)=='1')
244                 printf(p2(j,1));
245                 printf(var(in));
246                 printf(" + ");
247             end
248         end
249     end
250 end
251 //checking for isolated cell
252 for i=1:n
253     for j=1:n
254         if(k(i,j,2)==0 & k(i,j,1)==1)
255             a=strsplit(temp1(1,j));
256             b=strsplit(temp2(i,1));
257             for in=1:max(size(a(:,1)))
258                 if(a(in,1)=='1')
259                     printf(var(in+2));
260                 else
261                     if(a(in,1)=='0')
262                         printf(' %s ',var(2+in))
263                         ;

```

```

264                     end
265                 end
266             end
267         for in=1:max(size(b(:,1)))
268             if(b(in,1)=='1')
269                 printf(var(in));
270             else
271                 if(b(in,1)=='0')
272                     printf(' %s ',var(in));
273                 end
274             end
275         end
276         if(i~=4 & j~=4)
277             printf(" + ");
278         end
279     end
280   end
281   printf(" 0");
282 endfunction

```

Scilab code AP 11 4-variable kmap pos

```

1 //this funtion prints the minimal expression in the
  Pruduct of sums form for a given 4-vriable kmap
2 //this program requires noof.sci
3 function []=kmappos(k)
4     n=4;
5     k(:,:,2)=zeros(n,n);
6     var=['A' 'B' 'C' 'D'];
7 p1=[ 'A + B' 'A + B' 'A' 'A' + B' 'A' 'A' + B'];
8 p2=[ 'C + D' ; 'C + D' ; 'C' 'C' + D' ; 'C' 'C' + D'];
9 cmn4=4;
10 cmn2=2;
11 temp=1;
12 disp(k(:,:,1));
13 disp(" is :");
14 disp(" ")

```

```

15 // checking for 16 cells
16 for i=1:n
17     for j=1:n
18         if(k(i,j) ~=1)
19             temp=0;
20             break;
21         end
22     end
23 end
24 printf('      ');
25 if(temp==1)
26     printf("1");
27     abort;
28 end
29 for i=1:n
30     for j=1:n
31         if(k(i,j) ~=0)
32             temp=0;
33             break;
34         end
35     end
36 end
37 printf('      ');
38 if(temp==1)
39     printf("0");
40     abort;
41 end
42
43 // checking for 8 cells cases
44 z1=zeros(2,4);
45 z2=zeros(4,2);
46 temp1=['00' '01' '11' '10'];
47 temp2=temp1';
48 for i=1:n
49     if(i==4)
50         t=1;
51     else
52         t=i+1;

```

```

53     end
54     z=[k(i,:,:1);k(t,:,:1)];
55     if(z==z1)
56         printf('(%');
57         k(i,:,:2)=[1 1 1 1];
58         k(t,:,:2)=[1 1 1 1];
59         a=strsplit(temp2(i,1));
60         b=strsplit(temp2(t,1));
61         c=strncmp(a,b);
62         for in=1:max(size(c))
63             if(c(in)==0 & a(in)=='0')
64                 printf(var(in));
65                 break;
66             else
67                 if(c(in)==0 & a(in)=='1')
68                     printf('%s ',' ',var(in));
69                     break;
70                 end
71             end
72         end
73         printf(')');
74     end
75 end
76 for j=1:n
77     if(j==4)
78         t=1;
79     else
80         t=j+1;
81     end
82     z=[k(:,j,1) k(:,t,1)];
83     if(z==z2)
84         printf('(%');
85         k(:,j,2)=[1;1;1;1];
86         k(:,t,2)=[1;1;1;1];
87         a=strsplit(temp1(1,j));
88         b=strsplit(temp1(1,t));
89         c=strncmp(a,b);
90         for in=1:max(size(c))

```

```

91         if(c(in)==0 & a(in)=='0')
92             printf(var(2+in));
93             break;
94         else
95             if(c(in)==0 & a(in)=='1')
96                 printf(' %s ',var(2+in));
97                 break;
98             end
99         end
100     end
101     printf(' ) ')
102 end
103 end
104 //checking for 4 cells cases
105 z1=zeros(1,4);
106 z2=zeros(4,1);
107 z3=zeros(2,2);
108 temp1=['00' '01' '11' '10'];
109 temp2=temp1';
110 for t=1:n
111     z=k(t,: ,1);
112     no=noof(k(t,: ,2));
113     if(z==z1 & no<cmn4)
114         printf('(' )
115         k(t,: ,2)=[1 1 1 1];
116         a=strsplit(temp1(1,t));
117         for in=1:max(size(a))
118             if(a(in)=='0')
119                 if in ~= 1 then
120                     printf(' + ');
121                 end
122                 printf(var(in));
123             end
124             if(a(in)=='1')
125                 if in ~= 1 then
126                     printf(' + ');
127                 end
128                 printf(' %s ',var(in));

```

```

129           end
130       end
131   printf(")");
132 end
133 end
134 for t=1:n
135 z=k(:,t,1);
136 no=noof(k(:,t,2));
137 if(z==z2 & no<cmn4)
138     printf('(');
139     k(:,t,2)=[1;1;1;1];
140     a=strsplit(temp2(t,1));
141     for in=1:max(size(a))
142         if(a(in)=='0')
143             if in ~= 1 then
144                 printf(' + ');
145             end
146             printf(var(2+in));
147         end
148         if(a(in)=='1')
149             if in ~= 1 then
150                 printf(' + ');
151             end
152             printf(' %s ',var(2+in));
153         end
154     end
155     printf(")");
156 end
157 end
158 for i=1:n
159     for j=1:n
160         if(i==n)
161             t1=1;
162         else
163             t1=i+1;
164         end
165         if(j==n)
166             t2=1;

```

```

167     else
168         t2=j+1;
169     end
170     z4=[k(i,j,1) k(i,t2,1);k(t1,j,1) k(t1,t2
171         ,1)];
172     z5=[k(i,j,2) k(i,t2,2);k(t1,j,2) k(t1,t2
173         ,2)];
174     no=noof(z5);
175     if (z4==z3 & no<cmn4)
176         printf('(')
177         k(i,j,2)=1;
178         k(i,t2,2)=1;
179         k(t1,j,2)=1;
180         k(t1,t2,2)=1;
181         a=strsplit(temp2(i,1));
182         b=strsplit(temp2(t1,1));
183         c=strcmp(a,b);
184         for in=1:max(size(c))
185             if(c(in)==0 & a(in)=='0')
186                 printf(var(in));
187             end
188             if(c(in)==0 & a(in)=='1')
189                 printf(' ',var(in));
190             end
191             a=strsplit(temp1(1,j));
192             b=strsplit(temp1(1,t2));
193             c=strcmp(a,b);
194             for in=1:max(size(c))
195                 if(c(in)==0 & a(in)=='0')
196                     printf(' + ');
197                     printf(var(2+in));
198                 end
199                 if(c(in)==0 & a(in)=='1')
200                     printf(' + ');
201                     printf(' %s ',var(2+in));
202             end

```

```

203                     end
204                     printf(")");
205                 end
206             end
207         end
208 //checking for 2 cells
209 z6=[0 0];
210 z7=z6';
211 for i=1:n
212     for j=1:n
213         if(i==n)
214             t1=1;
215         else
216             t1=i+1;
217         end
218         if(j==n)
219             t2=1;
220         else
221             t2=j+1;
222         end
223         z8=[k(i,j,1) k(i,t2,1)];
224         z9=[k(i,j,2) k(i,t2,2)];
225         no1=noof(z9);
226         if(z8==z6 & no1<cmn2 )
227
228             printf('(');
229             k(i,j,2)=1;
230             k(i,t2,2)=1;
231             a=strsplit(temp1(1,j));
232             b=strsplit(temp1(1,t2));
233             c=strcmp(a,b);
234             for in=1:max(size(c))
235                 if(c(in)==0 & a(in)=='0')
236                     printf(p1(1,i));
237                     printf(' + ');
238                     printf(var(2+in));
239                     printf(")");
240             end

```

```

241         if(c(in)==0 & a(in)=='1')
242             printf(p1(1,i));
243             printf(" + ");
244             printf( "%s", var(2+in));
245
246             printf(")");
247         end
248     end
249   end
250 end
251 end
252 for i=1:n
253   for j=1:n
254     if(i==n)
255       t1=1;
256     else
257       t1=i+1;
258     end
259     if(j==n)
260       t2=1;
261     else
262       t2=j+1;
263     end
264     z10=[k(i,j,1);k(t1,j,1)];
265     z11=[k(i,j,2);k(t1,j,2)];
266     no2=noof(z11);
267     if(z10==z7 & no2<cmn2)
268       printf('(');
269       k(i,j,2)=1;
270       k(t1,j,2)=1;
271       a=strsplit(temp2(i,1));
272       b=strsplit(temp2(t1,1));
273       c=strcmp(a,b);
274       for in=1:max(size(c))
275         if(c(in)==0 & a(in)=='0')
276           printf(p2(j,1));
277           printf(" + ");
278           printf(var(in));

```

```

279         printf(" )");
280     end
281     if(c(in)==0 & a(in)=='1')
282         printf(p2(j,1));
283         printf(" + ");
284         printf('"%s",var(in));
285
286         printf(" )");
287     end
288     end
289     end
290 end
291 //for single cell
292 for i=1:n
293     for j=1:n
294         if(k(i,j,2)==0 & k(i,j,1)==0)
295             printf('(');
296             a=strsplit(temp1(1,j));
297             b=strsplit(temp2(i,1));
298             for in=1:max(size(a(:,1)))
299                 if(a(in,1)=='1')
300                     printf('"%s",var(2+in));
301                     printf(" + ");
302                 else
303                     if(a(in,1)=='0')
304                         printf(var(in+2));
305
306                         printf(" + ");
307                     end
308                 end
309             end
310         end
311         for in=1:max(size(b(:,1)))
312             if(b(in,1)=='1')
313                 printf('"%s",var(in));
314                 if(in~=max(size(b(:,1))))
315                     printf(" + ");
316                 end

```

```
317     else
318         if(b(in,1)=='0')
319             printf(var(in));
320
321         if(in~=max(size(b(:,1))))
322             printf(' + ');
323         end
324
325         end
326     end
327 end
328 printf(")");
329 end
330 end
331 end
332 endfunction
```
