

Scilab Textbook Companion for
Electric Machines
by D. P. Kothari And I. J. Nagrath¹

Created by
Navdeep Kumar
B.E.
Electrical Engineering
Thapar University
College Teacher
Dr. sunil Kumar Singla
Cross-Checked by

May 20, 2016

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Electric Machines

Author: D. P. Kothari And I. J. Nagrath

Publisher: Tata McGraw Hill Education Pvt. Ltd., New Delhi

Edition: 4

Year: 2010

ISBN: 9780070699670

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
2 Magnetic circuits and Induction	5
3 Transformers	14
5 Basic Concepts in Rotating Machines	43
7 DC Machines	56
8 Synchronous Machines	98
9 Induction Machine	136
10 Fractional Kilowatt Motors	153
12 Motor Control by Static Power Convertors	161

List of Scilab Codes

Exa 2.1	calculating exciting current and corresponding flux linkages	5
Exa 2.2	Calculation of current reqd to produce flux in the given magnetic circuit	6
Exa 2.3	Determination of mmf of the exciting coil	7
Exa 2.4	Exciting current calculation needed to setup reqd flux	8
Exa 2.5	determination of excitation coil mmf	9
Exa 2.7	determination of self and mutual inductance bw 2 coils	10
Exa 2.8	determination of R_c R_g L W_f	11
Exa 2.9	calculation of hysteresis and eddy current losses	12
Exa 3.1	To determine no load power factor core loss current and magnetising current and no load ckt parameters of transformer	14
Exa 3.2	To calculate no load current and its pf and no load power drawn from mains	14
Exa 3.3	To calculate primary and scndary side impedences current and their pf and real power and calculate terminal voltage	16
Exa 3.4	To calculate primary current and its pf	17
Exa 3.5	Equivalent circuit referred to HV side LV side	18
Exa 3.6	To find the voltage at the load end of the transformer when load is drawing transformer current	19
Exa 3.7	Approx equivalent ckt referred to hv and lv sides resp	20
Exa 3.8	to calculate open ckt current power and pf when LV excited at rated voltage voltage at which HV side is excited ip power and its pf	21
Exa 3.10	To find exciting current and expess impedance in pu in both HV and LV sides	22

Exa 3.11	o calculate efficiency of transformer	23
Exa 3.13	comparing all day efficiencies for diff given load cycles	23
Exa 3.14	To calculate volatage regulation volatage at load terminals and operating efficiency	25
Exa 3.15	To determine voltage regulation and efficiency	26
Exa 3.16	to calculate voltage ratings kva ratings and efficieny of autotransformer	27
Exa 3.17	To determine the rating and full load efficiency of autotransformer	27
Exa 3.18	To calculate sec line voltage line current and output va	28
Exa 3.19	To compute all the currents and voltages in all windings of Y D transformer	29
Exa 3.20	to find the load voltage when it draws rated current from transformer	30
Exa 3.21	to calculate fault currentin feeder lines primary and secondary lines of receiving end transformers	31
Exa 3.22	To calculate voltage and kva rating of 1ph transformer	32
Exa 3.23	to calculate reactance in ohms line voltage kva rating series reactance for YY and YD conn	33
Exa 3.24	find how 2 transformers connected in parallel share the load	35
Exa 3.25	find pu value of the equivalent ckt steady state short ckt current and voltages	36
Exa 3.26	to calculate line currents of 3 ph side	37
Exa 3.27	to calculate magnitude and phase of secondary current	38
Exa 3.28	to calculate sec voltage magnitude and ph	38
Exa 3.29	to calculate L1 and L2 and coupling coefficient	40
Exa 3.30	to calculate leakage inductance magnetising inductance mutual inductance and selfinductance	40
Exa 3.31	to calculate percentage voltage reg and efficiency	41
Exa 5.1	To calculate harmanic factor for stator	43
Exa 5.2	to find the frequency and phase and line voltages	44
Exa 5.3	to find the phase and line voltages	44
Exa 5.4	to calculate flux per pole	45
Exa 5.5	to calculate useful flux per pole and ares of pole shoe	46
Exa 5.6	To calculate em power developed mech power fed torque provided by primemover	46
Exa 5.9	To determine peak value of fundamental mmf	47

Exa 5.10	to calculate field current and flux per pole and to calculate open ckt ph and line voltages and to calculate field current	48
Exa 5.11	to find fundamental mmf wave speed and its peak value	49
Exa 5.12	to calculate resultant air gap flux per pole	49
Exa 5.13	To calculate resultant AT per pole and peak air gap flux density rotor AT per pole stator AT and its angle with the resultant AT stator current	50
Exa 5.14	to determine in F2 peak rotor AT max torque ele ip at max torque for motoring mode and open ckt voltage for generating mode	51
Exa 5.15	to find motor speed	52
Exa 5.16	to find voltage available bw slip rings and its freq . . .	52
Exa 5.18	to find no of poles slip and freq of rotor currents at full load motor speed at twice of full load	53
Exa 5.19	to calculate amplitude of travelling wave mmf peak value of air flux density velocity of wave current freq at some desired velocity	54
Exa 7.1	to calculate no of parrallel path	56
Exa 7.2	to find spacing bw brushes	56
Exa 7.3	to calculate relevant pitches for wave windings	57
Exa 7.4	to find distance bw brushes	57
Exa 7.5	to find the torque and gross mech power developed . .	58
Exa 7.6	to calculate ratio of generator speed to motor speed .	58
Exa 7.7	to calculate speed of motor	59
Exa 7.8	to calculate electromagnetic power and torque	60
Exa 7.9	to calculate electromagnetic power	60
Exa 7.10	to calculate cross and demagnetising turns per pole . .	61
Exa 7.11	to calculate no of conductors on each pole piece	61
Exa 7.12	to calculate no of turns reqd on each interpole	62
Exa 7.13	to calculate mmf per pole and speed at no load in rpm	62
Exa 7.14	to estimate at full load internal induced emf voltage drop caused y armature rxn and field current armature rxn demagnitisation	63
Exa 7.16	to calculate terminal voltage and rated output current and calculate no of series turns per pole	64
Exa 7.21	to determine demagnetising AT per pole and no of series turns reqd	65

Exa 7.22	to compute terminal voltage at rated voltage current .	66
Exa 7.23	to calculate no series turns	67
Exa 7.24	to find generator output	68
Exa 7.25	to find power to the load	69
Exa 7.28	to compute the generator induced emf when fully loaded in long shunt compound and short shunt compound .	70
Exa 7.29	to find field current and field resistance at rated terminal voltage em power and torque	71
Exa 7.32	to determine the reduction of flux per pole due to ar- mature rxn	72
Exa 7.33	to determine internal em torque developed	72
Exa 7.34	to determine speed calculate internal torque developed on load and no load	73
Exa 7.36	to sketch speed the speed torque characteristics of the series motor connected to mains by calculating speed and torque values at diff values of armature current	74
Exa 7.37	to determine the power delivered to the fan torque de- veloped by the motor and calculate external resistance to be added to armature ckt	75
Exa 7.38	to determine the starting torque developed	76
Exa 7.39	to determine speed and mech power	77
Exa 7.40	to calculate the mmf per pole on no load and speed developed	77
Exa 7.41	to calculate demagnetising ampeare turns em torque starting torque and no of turns of the series field	78
Exa 7.42	to determine shunt field current of the motor demag- netising effect of armature rxn determine series field turns per pole speed of motor	79
Exa 7.43	to find the no of starter sections reqd and resistance of each section	80
Exa 7.44	to find the lower current limit motor speed at each stud	81
Exa 7.45	to calculate the ratio of full load speed to no load speed	82
Exa 7.46	to calculate load torque motor speed and line current .	83
Exa 7.47	to calculate armature current speed and value of exter- nal resistance in field ckt	84
Exa 7.48	to determine speed and torque of the motor	85
Exa 7.50	to determine speed regulation load speed and power reg- ulation and compare power wasted in both cases	86

Exa 7.52	to determine armature current	87
Exa 7.54	to find speed and ratio of mech op	88
Exa 7.55	to calculate the armature voltage reqd	88
Exa 7.56	to find the range of generator field current motor current and speed	89
Exa 7.57	to calculate mc eff as a generator and max eff when generating and motoring	90
Exa 7.59	to determine rotational loss no load armature current and speed and also find speed regulation and to calculate armature current for given em torque	92
Exa 7.60	to determine load torque and motor eff armature current for max motor eff and ots value	93
Exa 7.61	to calculate rotational loss armature resistance eff line current and speed	94
Exa 7.62	to calculate eff of motor and generator	95
Exa 7.63	to calculate torque constt value of rotational loss stalled torque and stalled current of motor armature current anad eff motor op and eff	95
Exa 8.2	to determine voltage regulation by mmf method	98
Exa 8.3	to calculate syn chronous reactance leakage reactance voltage regulation	98
Exa 8.6	to calculate the excitation emf	99
Exa 8.7	to compute the max power and torque terminal voltage	100
Exa 8.8	max power supplied power angle d corresponding field current	101
Exa 8.9	to calculate the generator current and its pf	102
Exa 8.10	to calculate armature resistance sync reactance full load stray load loss Rac Rdc various categories of losses at full load full load eff	103
Exa 8.11	to calculate net power op eff line current and pf	105
Exa 8.12	to find pf	105
Exa 8.13	to determine excitation emf torque angle stator current pf max power kVAR delivered	106
Exa 8.14	to calculate armature current pf power angle power shaft torques kVar	107
Exa 8.15	find the excitation emf mech power developed pf	108
Exa 8.16	to find power angle field current	109

Exa 8.17	to calculate motor eff excitation emf and power angle max power op corresponding net op	110
Exa 8.18	find the change in the power angle	111
Exa 8.19	to find no of poles MVA rating prime mover rating and op torque	112
Exa 8.20	to determine the magnitude of E_g E_m and min value of E_m to remain mc in synchronism	112
Exa 8.21	to determine armature current pf power angle mech power developed and eff	113
Exa 8.22	to find armature current power factor and power ip . .	114
Exa 8.23	to calculate pu adjusted sync reactance feild reactance reactive power op rotor power angle	115
Exa 8.25	to calculate the excitation emf power angle	116
Exa 8.26	calculate excitation emf	117
Exa 8.27	to calculate generator terminal voltage excitation emf power angle	117
Exa 8.28	to find max pu power pu armature current pu reactive power	118
Exa 8.29	to calculate power angle excitation emf field current .	119
Exa 8.30	to find max andmin pu field excitation	120
Exa 8.31	to calculate synchronising power and torque coeff per deg mech shift	121
Exa 8.32	to calculate synchronising power per elec deg pu sync torque per mech deg	122
Exa 8.33	to calculate sync current power and torque	123
Exa 8.34	to calculate value of syncpower	123
Exa 8.35	to determine op current and pf	124
Exa 8.36	to find the pf and current supplied by the mc	125
Exa 8.37	to find initial current current at the end of 2 cycles and at the end of 10s	125
Exa 8.39	to calculate sync reactance voltage regulation torque an- gle ele power developed voltage and kva rating	126
Exa 8.40	to determine mc and pf	127
Exa 8.41	to calculate excitation emf torque angle eff shaft op . .	128
Exa 8.42	to caculate generator current pf real power excitation emf	129
Exa 8.43	to clculate pf angle torque angle equivalent capicitor and inductor value	130

Exa 8.44	to determine X_s saturated scr X_s unsat and I_f generator current	131
Exa 8.45	find motor pf	132
Exa 8.46	to find exciting emf neglecting saliency and accounting saliency	132
Exa 8.47	calculate excitation emf max load motor supplies torque angle	133
Exa 8.49	find no load freq setting sys freq at no load freq of swing generator system trip freq	134
Exa 9.1	to compute cu loss in rotoe windings input to the motor efficiency	136
Exa 9.2	to calculate torque resistance to be added to rotor ckt	137
Exa 9.3	to find slip at max torque full load slip and rotor current at starting	138
Exa 9.4	to calculate stator current pf net mech op torque motor performance	139
Exa 9.5	to determine ckt model parameters parameters of thevenin equivalent max torque and slip stator current pf and eff	140
Exa 9.6	to calculate starting torque and current full load current pf torque internal and overall eff slip and max torque .	142
Exa 9.9	to determine the line current pf power ip shaft torque mech op and efficiency	143
Exa 9.10	to calculate max torque and slip starting torque	145
Exa 9.11	to find starting current and torque necessary external resistance and corresponding starting torque	146
Exa 9.12	find line current and starting torque with direct switching stator resistance starting autotransformer starting star delta starting autotransformer ratio give 1 pu . . .	146
Exa 9.13	to find resistance added to ckt	147
Exa 9.14	to find resistance added to ckt	148
Exa 9.15	to calculate the min resistance to be added and speed of the motor	149
Exa 9.17	to find the ratio of currents and torques at the starting V_2 by V_1	150
Exa 9.18	to calculate ratio of torques at starting and given slip	151
Exa 9.19	to compute acc time and value of rotor resistance	152
Exa 10.1	to compute the ratio of E_m by E_{mb} V_f by V_b T_f by T_b gross total torque T_f by total torque T_b by total torque	153

Exa 10.2	to calculate parameters of the ckt model line current power factor shaft torque and efficiency	154
Exa 10.3	to compute amplitudes of forward and backward stator mmf waves magnitude of auxillary current and its ph angle diff	155
Exa 10.4	to determine value of capacitor	156
Exa 10.5	to calculate starting torque and current value of run capacitor motor performance	157
Exa 10.6	to calculate starting torque and atarting current motor performance	159
Exa 12.1	calculate power fed to load	161
Exa 12.2	calculate firing angle value	161
Exa 12.3	calculate value of commutating capacitor	162

Chapter 2

Magnetic circuits and Induction

Scilab code Exa 2.1 calculating exciting current and corresponding flux linkages

```
1 // calculating exciting current and corresponding
   flux linkages
2
3 clc;
4 U_o=4*%pi*10^-7;
5 U_r=6000;
6 l_g=0.0006;
7 l_c=.40;
8 A_c=.04*.04;
9 B_c=1.2;
10 N=600;
11 function [i]=current(B_g)
12     i=(1/(U_o*N))*(((B_c*l_c)/U_r)+(B_g*l_g));
13 endfunction
14 disp(current(B_c), 'neglecting fringing , current (A)=')
   ;
15
16     phi=B_c*A_c;
17 disp(phi, 'flux (Wb)=');
18
```

```

19 function [lmda]=flux_linkage(phi)
20     lmda=N*phi;
21 endfunction
22 disp(flux_linkage(phi),'flux linkages(Wb-turns)=');
23
24 A_g=(.04+l_g)^2;
25 B_g=phi/A_g;
26
27 disp(current(B_g),'fringing taken into account,
    current(A)=');

```

Scilab code Exa 2.2 Calculation of current reqd to produce flux in the given magnetic circuit

```

1 //Calculation of current reqd to produce flux in the
    given magnetic circuit.
2
3 clc;
4 U_o=4*%pi*10^-7;
5 U_r=4000;
6 N=600;
7 //l_c=.30;
8 //l_g=.001;
9 dia=.02;
10 phi=.5*10^-3; //flux
11 A=(%pi/4)*dia^2;
12 function [i]=current(l_c,l_g)
13     R=((l_c/U_r)+l_g)/(U_o*A);
14     i=(phi*R)/N;
15 endfunction
16 disp(current(.30,0),'no air gap current(A)');
17 disp(current(.30,.001),'with air gap current(A)');
18
19 //B-H data
20 //H in AT/m      2500      3000      3500      4000

```

```

21 //B in T      1.55      1.59      1.6      1.615
22
23 B_g=phi/A;
24 disp(B_g, 'B(T) ');
25
26 H_g=B_g/U_o;
27
28 function [AT]=AT(H,l)
29     AT=H*l;
30 endfunction
31 AT_g=AT(H_g,.001);
32 disp(ceil(AT_g), 'AT_g ');
33
34 H_c=3000;
35 AT_c=AT(H_c,.30);
36 disp(AT_c, 'AT_c ');
37
38 i=(AT_g+AT_c)/N;
39 disp(i, 'from magnetisation data, current(A) ');

```

Scilab code Exa 2.3 Determination of mmf of the exciting coil

```

1 // Determination of mmf of the exciting coil
2
3 clc;
4 U_o=4*%pi*10^-7;
5 A1=.0001;
6 A2=.0002;
7 l1=.025*10^-2;
8 l2=.02*10^-2;
9 phi=.75*10^-3;
10 function [Re]=reluctance(l,U_r,A)
11     Re=l/(U_o*U_r*A);
12 endfunction
13

```

```

14 function [Ni]=mmf(R1,R2,R3)
15     Ni=phi*(R3+((R1*R2)/(R1+R2)));
16 endfunction
17 R_g1=reluctance(l1,1,A1);
18 R_g2=reluctance(l2,1,A1);
19 R_g3=reluctance(l2,1,A2);
20 disp(mmf(R_g1,R_g2,R_g3), 'when U_r=1,mmf(AT) ');
21 L1=l1*2*10^3;
22 L2=l2*10^3;
23 R_c1=reluctance(L1,5000,A1);
24 R_c2=reluctance(L1,5000,A1);
25 R_c3=reluctance(L2,5000,A2);
26 disp(mmf(R_c1+R_g1,R_c2+R_g2,R_c3+R_g3), 'when U_r
    =5000,mmf(AT) ');

```

Scilab code Exa 2.4 Exciting current calculation needed to setup reqd flux

```

1 // Exciting current calculation needed to setup reqd
  flux
2
3 clc;
4 U_o=4*%pi*10^-7;
5 A1=800*10^-6;
6 A2=600*10^-6;
7 l1=1*10^-3; //air gap length
8 l2=160*10^-3; //length of central limb
9 l3=400*10^-3; //length of side limb
10 phi=.8*10^-3;
11 N=500;
12 function [B]=fd(A)
13     B=phi/A;
14 endfunction
15
16 function [F]=mmf(l,B)
17     F=l/B;

```



```

18 endfunction
19 // air gap
20 B_g=fd(A1);
21 F_g=mmf(l1,B_g)/U_o; disp(F_g, 'F_g(AT) ');
22 // central limb
23 B_c=B_g;
24 F_c=mmf(l2,B_c)/10^-3; disp(F_c, 'F_c(AT) ');
25 // outer limb          flux is divided into
    half
26 B_o=fd(A2)/2;
27 F_o=mmf(l3,B_o)/(4*10^-3); disp(F_o, 'F_o(AT) ');
28 i=(F_g+F_c+F_o)/N;          // total mmf/no of
    turns
29 disp(i, 'exciting current (A) ');

```

Scilab code Exa 2.5 determination of excitation coil mmf

```

1 // determination of excitation coil mmf
2 clc;
3 U_o=4*%pi*10^-7;
4 A1=25*10^-4;
5 A2=12.5*10^-4;
6 A3=25*10^-4;
7 l1=.5;          //length of side limb(ab+cd)
8 l2=.2;          //length of central limb(ad)
9 l3=.5;          //length of side limb(dea)
10 l4=.25*10^-3;  //length of air gap
11 phi=.75*10^-3;
12 N=500;
13 function [B]=fd(A)
14     B=phi/A;
15     endfunction
16 function [F]=flux(B,l)
17     F=B*l/(U_o);
18     endfunction

```

```

19 function [f]=f1(H,l)
20 f=H*l;
21 endfunction
22 B_abcd=fd(A1);
23 F_bc=flux(B_abcd,l4);
24 disp(B_abcd,'B_abcd(T)');
25 H_ab=200; //for cast iron for
    B=0.3
26 F_abcd=f1(H_ab,l1);
27 F_ad=F_abcd+F_bc;
28 H_ad=F_ad/l2;
29 disp(H_ad,'H_ad(AT/m)');
30 B_ad=1.04 //for cast iron for
    H=800
31 phi_ad=B_ad*A2;
32 phi_dea=phi+phi_ad;
33 B_dea=phi_dea/A3;
34 H_dea=500 //for cast iron
    for B=.82
35 F_dea=H_dea*l3;
36 F=F_dea+F_ad;
37 disp(F,'reqd mmf(AT)');

```

Scilab code Exa 2.7 determination of self and mutual inductance bw 2 coils

```

1 //determination of self and mutual inductance b/w 2
  coils
2
3 clc;
4 U_o=4*%pi*10^-7;
5 U_r=1600;
6 A1=4*10^-4;
7 A2=4*10^-4;
8 A0=2*10^-4;

```

```

9 N1=500;
10 N2=1000;
11
12 l1=.01*((6+0.5+1)*2+(4+2));
13 l2=.01*((3+0.5+1)*2+(4+2));
14 l0=.01*(4+2);
15 function [R]=reluc(l,A)
16     R=1/(U_o*U_r*A);
17 endfunction
18 R1=reluc(l1,A1);
19 R2=reluc(l2,A2);
20 R0=reluc(l0,A0);
21
22 function [re]=re(r0,r1,r2)
23     re=r0+((r1*r2)/(r1+r2));
24 endfunction
25
26 disp('coil 1 excited with 1A');
27 R_1=re(R1,R0,R2);
28 phi1=N1/R_1;
29 phi2=phi1*R0/(R0+R2);
30 L11=N1*phi1;disp(L11,'self inductance(H)');
31 M21=N2*phi2;disp(M21,'mutual inductance(H)');
32 disp('coil 2 excited with 1A');
33 R_2=re(R2,R0,R1);
34 phi2=N2/R_2;
35 L22=N2*phi2;disp(L22,'self inductance(H)');
36 M12=M21;disp(M12,'mutual inductance(H)');

```

Scilab code Exa 2.8 determination of Rc Rg L Wf

```

1 //determination of R_c,R_g,L,W_f
2
3 clc;
4 U_o=4*%pi*10^-7;

```

```

5 U_r=6000;
6 l_g=0.0006;
7 l_c=.40;
8 A_c=.04*.04;
9 B_c=1.2;
10 N=600;
11 function [i]=current(B_g)
12     i=(1/(U_o*N))*(((B_c*l_c)/U_r)+(B_g*l_g));
13 endfunction
14 disp(current(B_c), 'neglecting fringing , current (A)=')
15     ;
16     phi=B_c*A_c;
17 disp(phi, 'flux (Wb)=');
18
19 function [lmda]=flux_linkage(phi)
20     lmda=N*phi;
21 endfunction
22 disp(flux_linkage(phi), 'flux linkages (Wb-turns)=');
23
24 function [R]=reluc(l,U,A)
25     R=1/(U_o*U*A);
26 endfunction
27 R_c=reluc(l_c,U_r,A_c);disp(R_c, 'R_c=');
28 R_g=reluc(l_g,1,A_c);disp(R_g, 'R_g=');
29
30 L=N^2/(R_c+R_g);
31 disp(L, 'coil inductance(H) ');
32
33 W_f=(N*phi)^2/(2*L);
34 disp(W_f, 'energy stored in the magnetic field(J)');

```

Scilab code Exa 2.9 calculation of hysteresis and eddy current losses

```
1 // calculation of hysteresis and eddy current losses
```

```
2
3 clc;
4 P1=1500;
5 f1=50;
6 P2=3000;
7 f2=75;
8 A=[1 50;1 75];           //P/f=A+B*f
9 B=[30;40];
10 v=A\B;
11
12 disp('at 50Hz');
13 P_h=v(1)*f1;disp(P_h,'hysterisis loss (W)');
14 P_e=v(2)*f1^2;disp(P_e,'eddy current loss (W)');
15
16 disp('at 75Hz');
17 P_h=v(1)*f2;disp(P_h,'hysterisis loss (W)');
18 P_e=v(2)*f2^2;disp(P_e,'eddy current loss (W)');
```

Chapter 3

Transformers

Scilab code Exa 3.1 To determine no load power factor core loss current and magnetising current and no load ckt parameters of transformer

```
1 // To determine no load power factor ,core loss
   current and magnetising current
2 // and no load ckt parameters of transformer
3
4 clc;
5 Pi=50;
6 V1=230;
7 Io=2;
8 pf=Pi/(V1*Io);disp(pf,'no load power factor ');
9 Im=Io*sind(acosd(pf));disp(Im,'magnetising current(A
   ) ');
10 Ii=Io*pf;disp(Ii,'core loss current(A) ');
11 Gi=Pi/V1^2;disp(Gi,'Gi(mho) ');
12 Bm=Im/V1;disp(Bm,'Bm(mho) ');
```

Scilab code Exa 3.2 To calculate no load current and its pf and no load power drawn from mains

```

1 // To calculate no load current and its pf and no
  load power drawn from mains
2
3 clc;
4 E=200;
5 f=50;
6 N1=150;           // no of turns
7 b1=.1;
8 b2=.05;
9 phi_max=E/(4.44*f*N1);
10 disp(phi_max, 'flux (Wb) ');
11 B_max=phi_max/(b1*b2);
12 disp(B_max, 'B_max(T) ');
13
14 H_max=250;       //According to B_max, H_max is 250
  AT/m
15 l_c=.2*(3.0+3.5); //length of core
16 AT_max=H_max*l_c;
17 disp(AT_max, 'AT_max ');
18 T_max=N1;
19 I_mmax=AT_max/T_max;
20 I_mrms=I_mmax/2.5;
21 disp(I_mrms, 'I_mrms(A) ');
22
23 v=2*(20*10*5)+2*(45*10*5);
24
25 d=.0079;        //density of core material
26 w=v*d;
27
28 cl=3;           //core loss/kg
29 closs=w*cl;
30 disp(closs, 'core loss (W) ');
31 I_i=closs/E;
32 disp(I_i, 'I_i (A) ');
33 function [r,pff]=rect2polar(x,y)
34     r=sqrt(x2+y2);
35     pff=cosd(atand(y/x));
36 endfunction

```

```

37 [I_o, pf]=rect2polar(I_i, -I_mmax);
38 disp(I_o, 'no load current(A)');
39 disp(pf, 'no load power factor');

```

Scilab code Exa 3.3 To calculate primary and secondary side impedances current and their pf and real power and calculate terminal voltage

```

1 // To calculate primary and secondary side impedences
  , current and their pf and real power
2 // and calculate terminal voltage
3
4 clc;
5 N_1=150;
6 N_2=75;
7
8 a=N_1/N_2;
9
10 Z_2=[5,30]; //polar (magnitude , phase
  diff)
11 disp(Z_2, 'secondary impedance(ohm)');
12 Z_1=[a^2*Z_2(1), Z_2(2)];
13 disp(Z_1, 'primary impedance(ohm)');
14
15 V_1=[200,0]; //polar (magnitde , phase
  diff)
16 V_2=[V_1(1)/a, V_1(2)];
17 disp(V_2, 'secondary terminal voltage(V)');
18
19 I_2(1)=V_2(1)/Z_2(1);
20 I_2(2)=V_2(2)-Z_2(2);
21 disp(I_2, 'I_2=');
22 pf=cosd(I_2(2));
23 disp(pf, 'pf lagging=');
24
25 I_1(1)=I_2(1)/a;

```



```

26 I_1(2)=I_2(2);
27 disp(I_1, 'I_1 (A) ');
28 pf=cosd(I_1(2));
29 disp(pf, 'pf lagging=');
30
31 P_2=V_2(1)*I_2(1)*cosd(I_2(2));
32 disp(P_2, 'secondary power output (W)=');
33 //P_1=primary power output
34 P_1=P_2 //as the
    transformer is lossless
35 disp(P_1, 'primary power output (W)=');

```

Scilab code Exa 3.4 To calculate primary current and its pf

```

1 // To calculate primary current and its pf
2
3 clc;
4
5 function [x,y]=polar2rect(r,theta)
6     x=r*cosd(theta);
7     y=r*sind(theta);
8 endfunction
9
10 function [r,theta]=rect2polar(x,y)
11     r=sqrt(x^2+y^2);
12     theta=atand(y/x);
13 endfunction
14
15 I_2=[10 -30];
16 [I_2r(1),I_2r(2)]=polar2rect(I_2(1),I_2(2));
17
18 I_0=[1.62 -71.5];
19 [I_0r(1),I_0r(2)]=polar2rect(I_0(1),I_0(2));
20
21 I_1r=I_0r+I_2r;

```

```

22
23 [I_1(1),I_1(2)]=rect2polar(I_1r(1),I_1r(2));
24 disp(I_1(1),'primary current(A)=');
25 pf=cosd(I_1(2));
26 disp(pf,'power factor=');

```

Scilab code Exa 3.5 Equivalent circuit referred to HV side LV side

```

1 // Equivalent circuit referred to(i)HV side (ii)LV
  side
2
3 clc;
4
5 N_1=2000;
6 N_2=200;
7
8 a=N_1/N_2;
9
10 Z_2=complex(.004,.005); //low voltage
    impedance
11 Z_2hv=a^2*Z_2;
12 disp(Z_2hv,'Z_2 referred to hv side(ohm)');
    //when referred to hv side
13
14 Y_0=complex(.002,-.015); //shunt branch
    admittance
15 Y_0hv=Y_0/a^2;
16 disp(Y_0hv,'Y_0 referred to hv side(mho)');
17
18 Z_1=complex(.42,.52); //low voltage
    impedance
19 Z_1lv=Z_1/a^2;
20 disp(Z_1lv,'Z_1 referred to lv side(ohm)');

```

Scilab code Exa 3.6 To find the voltage at the load end of the transformer when load is drawing transformer current

```
1 // To find the voltage at the load end of the
   transformer when load is drawing transformer
   current
2
3 clc;
4
5 I=20/2; //rated load current(hv
   side)
6
7 Z1=[.25,1.4]; //impedence of
   feeder (REAL,IMAGINERY)
8 Z2=[.82,1.02]; //impedence of
   transformer (REAL,IMAGINERY)
9
10 Z=Z1+Z2;
11 disp(Z, 'Z(ohm) ');
12
13 pf=.8;
14 phi=acosd(pf);
15
16 //from phasor diagram
17
18 R=Z(1);
19 X=Z(2);
20 AF=I*X*cosd(phi);
21 FE=I*R*sind(phi);
22 AE=AF-FE;
23 OA=2000;
24 OE=sqrt(OA^2-AE^2);
25
26 BD=I*R*cosd(phi);
```

```

27 DE=I*X*sind(phi);
28 BE=BD+DE;
29 V1=0E;    disp(V1, 'V1(V) ');
30 V2=V1-BE;    disp(V2, 'V2(V) ');
31
32 loadvol=V2/10;           //referred to
    LV side
33 disp(loadvol, 'load voltage(V) ');

```

Scilab code Exa 3.7 Approx equivalent ckt referred to hv and lv sides resp

```

1 // Approx equivalent ckt referred to hv and lv sides
    resp ,
2
3 clc;
4 //open ckt test data with HV side open
5 ocv=200;
6 oci=4;
7 ocp=120;
8 //short ckt test data with LV side open
9 scv=60;
10 sci=10;
11 scp=300;
12 //OC test(LV side)
13 Y_o=oci/ocv;    disp(Y_o, 'Y_o(mho) ');
14 G_i=ocp/ocv^2;  disp(G_i, 'G_i(mho) ');
15 B_m=sqrt(Y_o^2-G_i^2);  disp(B_m, 'B_m(mho) ');
16 //SC test(HV side)
17 Z=scv/sci;    disp(Z, 'Z(ohm) ');
18 R=scp/sci^2;  disp(R, 'R(ohm) ');
19 X=sqrt(Z^2-R^2);  disp(X, 'X(ohm) ');
20
21 N_H=2000;
22 N_L=200;
23 a=N_H/N_L;           //

```

```

        transformation ratio
24
25 //Equivalent ckt referred to HV side
26 G_iHV=G_i/a^2;          disp(G_iHV, 'G_i(HV)mho');
27 B_mHV=B_m/a^2;          disp(B_mHV, 'B_m(HV)mho');
28
29 //Equivalent ckt referred to LV side
30 RLV=R/a^2;              disp(RLV, 'R(LV)ohm');
31 XLV=X/a^2;              disp(XLV, 'X(LV)ohm');

```

Scilab code Exa 3.8 to calculate open ckt current power and pf when LV excited at rated voltage voltage at which HV side is excited ip power and its pf

```

1 // to calculate (a)open ckt current ,power and pf
  when LV excited at rated voltage
2 // (b) voltage at which HV side is excited , ip power
  and its pf
3
4 clc;
5 r=150000; //
  rating(VA)
6 V1=2400;
7 V2=240;
8 a=V1/V2;
9
10 R_1=.2;
11 X_1=.45;
12 R_i=10000;
13 R_2=2*10^-3;
14 X_2=4.5*10^-3;
15 X_m=1600;
16 //Referring the shunt parameters to LV side
17 R_iLV=R_i/a^2;
18 X_mLV=X_m/a^2;

```

```

19 I_oLV=[V2/100 V2/16];
20 I_o=sqrt(I_oLV(1)^2+I_oLV(2)^2);    disp(I_o, 'I_o (A)
    ');
21 pf=cosd(atan(I_oLV(2)/I_oLV(1)));    disp(pf, 'pf');
22 //equivalent series parameters referred to HVside
23 R=R_1+R_2*a^2;
24 X=X_1+X_2*a^2;
25 Z=complex(R,X);    disp(Z, 'Z(ohm) ');
26 z=[R X];
27 I_f1HV=r/V1;
28 V_scHV=I_f1HV*sqrt(R^2+X^2);
29 P_sc=I_f1HV^2*R;    disp(P_sc, 'P_sc (W) ');
30 pf_sc=cosd(atan(X/R));    disp(pf_sc, 'pf_sc ');

```

Scilab code Exa 3.10 To find exciting current and express impedance in pu in both HV and LV sides

```

1 //To find exciting current and express impedance in
  pu in both HV and LV sides
2
3 clc;
4
5 V_BHV=2000;
6 I_BHV=10;
7 Z_BHV=V_BHV/I_BHV;
8
9 V_BLV=200;
10 I_BLV=100;
11 Z_BLV=V_BLV/I_BLV;
12
13 I_o=3;
14 a=V_BHV/V_BLV;
15
16 I_oLV=I_o/100;    disp(I_oLV, 'I_o (LV) pu=');
17 I_oHV=I_o/(a*10);    disp(I_oHV, 'I_o (HV) pu=');

```

```

18
19 Z=complex(8.2,10.2);
20 ZHV=Z/Z_BHV;    disp(ZHV, 'Z(HV) pu= ');
21 z=Z/a^2;
22 ZLV=z/Z_BLV;    disp(ZLV, 'Z(LV) pu= ');

```

Scilab code Exa 3.11 o calculate efficiency of transformer

```

1 // To calculate efficiency of transformer
2
3 clc;
4
5 V_2=200;
6 I_2=100;
7 pf=.8;
8 P_o=V_2*I_2*pf;           //power output
9
10 P_i=120;
11 P_c=300;
12 k=1;
13 P_L=P_i+k^2*P_c;         //total losses
14
15 n=1-(P_L/(P_o+P_L));     disp(n*100, 'n(%) ');
16
17 K=sqrt(P_i/P_c);        //max efficiency
18
19 n_max=1-(2*P_i/(P_o*K+2*P_i)); //pf=.8
20 disp(n_max*100, 'n_max(%) ');

```

Scilab code Exa 3.13 comparing all day efficiencies for diff given load cycles

```

1 // Comparing all-day efficiencies for diff given
  load cycles
2
3 clc;
4
5 r=15; // kva rating
6 n_max=.98;
7 pf=1;
8 P_o=20;
9 P_i=r*(1-n_max)/2;
10 k=r*pf/P_o;
11 P_c=P_i/(k^2);
12 function [W_o,W_in]=power(P_o,h)
13     k=P_o/20;
14     P_c=P_i*P_o/r;
15     W_o=P_o*h;
16     W_in=(P_o+P_i+(k^2)*P_c)*h;
17 endfunction
18
19 //(a) full load of 20kva 12hrs/day and no load rest
  of the day
20 a=[20 12];
21 [W_oa(1),W_ina(1)]=power(a(1),a(2));
22 aa=[0 12];
23 [W_oa(2),W_ina(2)]=power(aa(1),aa(2));
24 disp(W_oa,'W_o(kWh) for a');
25 disp(W_ina,'W_in(kWh) for a');
26 n_ada=sum(W_oa)/sum(W_ina); disp(n_ada*100,'
  n_allday(a) in %age');
27
28 //(b) full load of 20kva 4hrs/day and .4 of full load
  rest of the day
29 b=[20 4];
30 [W_ob(1),W_inb(1)]=power(b(1),b(2));
31 bb=[8 20];
32 [W_ob(2),W_inb(2)]=power(bb(1),bb(2));
33 disp(W_ob,'W_o(kWh) for b');
34 disp(W_inb,'W_in(kWh) for b');

```



```

35 n_adb=sum(W_ob)/sum(W_inb);      disp(n_adb*100, '
    n_allday(b) in %age');

```

Scilab code Exa 3.14 To calculate volatage regulation volatage at load terminals and operating efficiency

```

1 // To calculate volatage regulation , volatage at
  load terminals and operating efficiency
2
3 clc;
4 S=20*1000;
5 V1=200;
6 V2=2000;
7 I1=S/V1;
8 I2=S/V2;
9 Rh=3;
10 Xh=5.2;
11 pf=0.8;
12 phi=acosd(pf);
13 Vha=V2+I2*(Rh*cosd(phi)+Xh*sind(phi));      //
    lagging
14 Vrega=(Vha-V2)*100/V2;      disp(Vrega, 'vol-reg
    lagging (%) ');
15 Vhb=V2+I2*(Rh*cosd(phi)-Xh*sind(phi));      //
    leading
16 Vregb=(Vhb-V2)*100/V2;      disp(Vregb, 'vol-reg
    leading (%) ');
17
18 V11=V2-I2*(Rh*cosd(phi)+Xh*sind(phi));
19 v1=V11/I2;      disp(v1, 'V_L(V) ');
20 ploss=120+10*10*3;
21 pop=v1*I1*cosd(phi);
22 eff=(1-(ploss/(ploss+pop)))*100;
23 disp(eff, ' eff (%) ');

```

Scilab code Exa 3.15 To determine voltage regulation and efficiency

```
1 // To determine voltage regulation and efficiency
2
3 clc;
4
5 r=150*1000; //rating in va
6 v1=2400;
7 v2=240;
8 a=v2/v1;
9 R_hv=.2+.002/a^2;
10 X_hv=.45+.0045/a^2;
11 I_2fl=r/v2;
12 pf=0.8 //lagging
13 phi=acosd(pf);
14 I_2=I_2fl*a;
15 vd=I_2*(R_hv*cosd(phi)+X_hv*sind(phi));
16 V2=v1;
17 vr=(vd/V2)*100; disp(vr, 'vol reg (%) ');
18 V1=v1+vd;
19 P_out=r*pf;
20 P_c=(I_2^2)*R_hv; //copper loss
21 P_i=(V1^2)/10000;
22 P_L=P_c+P_i;
23 n=P_out/(P_out+P_L); disp(n*100, 'eff (%) ');
24
25 I_o(1)=V1/(10*1000);
26 I_o(2)=-V1/(1.6*1000); //inductive effect
27 I2(1)=I_2*(cosd(phi));
28 I2(2)=I_2*(-sind(phi));
29 I_1=I_o+I2;
30 b=sqrt(I_1(1)^2+I_1(2)^2);
31 disp(b, 'I_1 (A) ');
32 pff=cosd(atan(I_1(2)/I_1(1)));
```

```
33 disp(pff, 'pf');
```

Scilab code Exa 3.16 to calculate voltage ratings kva ratings and efficiency of autotransformer

```
1 // to calculate voltage ratings ,kva ratings and
  efficiency of autotransformer
2
3 clc;
4
5 AB=200;
6 BC=2000;
7 V_1=BC;          disp(V_1, 'V_1(V) ');
8 V_2=AB+BC;      disp(V_2, 'V_2(V) ');
9 r=20000;        //rating of transformer
10 I_2=r/AB;
11 I_1=I_2+10;
12 rr=V_2*I_2/1000; //kva rating of
  autotransformer
13 disp(rr, 'kva rating ');
14 ri=V_1*(I_1-I_2)/1000; //kva inductive
15 rc=rr-ri;
16 disp(ri, 'kva transferred inductively ');
17 disp(rc, 'kva transferred conductively ');
18 W_c=120;        //core loss
19 W_cu=300;       //cu loss
20 W_t=W_c+W_cu;   //total loss
21 pf=0.8;
22 W=V_2*I_2*pf;   //full load output
23 n=1-(W_t/W);
24 disp(n*100, 'eff(%)');
```

Scilab code Exa 3.17 To determine the rating and full load efficiency of autotransformer

```
1 // To determine the rating and full load efficiency
  of autotransformer
2
3 clc;
4 //when used as transformer
5 v1=240;
6 v2=120;
7 r=12000;
8 I1=r/v1;
9 I2=r/v2;
10
11 //when connected as autotransformer
12 V1=240;
13 V2=v1+v2;
14 rr=I2*V2; disp(rr, 'rating of
  autotransformer (va) ');
15
16 pf=1;
17 P_o=r*pf; //output power
18 n=.962 //efficiency at upf
19 P_L=P_o*(1-n)/n;
20
21 pff=.85 //if pf=.85
22 Po=rr*pff;
23 nn=1/(1+P_L/Po); disp(nn*100, 'efficiency (%)
  at .85 pf is ');
```

Scilab code Exa 3.18 To calculate sec line voltage line current and output va

```
1 // To calculate sec. line voltage , line current and
  output va
```

```

2
3 clc;
4
5 disp('(a)Y/D conn');
6 V_LY=6600;
7 V_PY=V_LY/sqrt(3);
8 a=12;
9 V_PD=V_PY/a;
10 V_LD=V_PD;    disp(V_LD,'sec line voltage(V)');
11
12 I_PY=10;
13 I_PD=I_PY*a;
14 I_LD=I_PD*sqrt(3);    disp(I_LD,'sec. line current(A)
    ');
15 r=sqrt(3)*V_LD*I_LD;    disp(r,'output rating(va)');
16
17 disp('(b)D/Y conn');
18 I_LD=10;
19 I_PD=I_LD/sqrt(3);
20 I_LY=I_PD*a;    disp(I_LY,'sec. line current(A)
    ');
21 V_PD=6600;
22 V_PY=V_PD/a;
23 V_LY=V_PY*sqrt(3);    disp(V_LY,'sec line voltage(V)
    ');
24 r=sqrt(3)*V_LY*I_LY;    disp(r,'output rating(va)');

```

Scilab code Exa 3.19 To compute all the currents and voltages in all windings of Y D transformer

```

1 // To compute all the currents and voltages in all
    windings of Y/D transformer
2
3 clc;
4

```

```

5 S=complex(500,100);           //load is 500MW and 100
    MVar
6 s=abs(S);
7 r=s/3;           //MVA rating of each single ph
    transformer
8
9 V1=22;           //D side
10 V2=345;        //Y side
11 a=V2/(sqrt(3)*V1);           //voltage rating of each
    single phase
12 disp('Y side ');
13 V_A=(V2/sqrt(3))*complex(cosd(0),sind(0));
14 V_B=(V2/sqrt(3))*complex(cosd(-120),sind(-120));
15 V_C=(V2/sqrt(3))*complex(cosd(-240),sind(-240));
16
17 V_AB=V_A-V_B;     disp(V_AB, 'V_AB(V) ');
18 V_BC=V_B-V_C;     disp(V_BC, 'V_BC(V) ');
19 V_CA=V_C-V_A;     disp(V_CA, 'V_CA(V) ');
20
21 IA=S/(3*V_A);     disp(IA, 'IA(A) ');
22 IB=S/(3*V_B);     disp(IB, 'IB(A) ');
23 IC=S/(3*V_C);     disp(IC, 'IC(A) ');
24 disp('D side ');
25 V_ab=V_A/a;       disp(V_ab, 'V_ab(V) ');
26 V_bc=V_B/a;       disp(V_bc, 'V_bc(V) ');
27 V_ca=V_C/a;       disp(V_ca, 'V_ca(V) ');
28
29 I_ab=a*IA;
30 I_bc=a*IB;
31 I_ca=a*IC;
32 Ia=I_ab-I_bc;     disp(Ia, 'Ia(A) ');
33 Ib=I_bc-I_ca;     disp(Ib, 'Ib(A) ');
34 Ic=I_ca-I_ab;     disp(Ic, 'Ic(A) ');

```

Scilab code Exa 3.20 to find the load voltage when it draws rated current from transformer

```

1 // to find the load voltage when it draws rated
  current from transformer
2
3 clc;
4 // here pu method is used
5 r=20;           //kva rating of three 1-ph transformer
6 MVA_B=r*3/1000;
7 v2=2*sqrt(3);   //in kv voltage base on hv side
8 v1=.2;         //in kv voltage base on lv side
9
10 z1=complex(.0004,.0015); //feeder impedance
11 Z1=z1*MVA_B/v1^2;      // lv line (pu)
12 z2=complex(.13,.95);  //load impedance
13 Z2=z2*MVA_B/v2^2;     // hv line (pu)
14 z_T=complex(.82,1.02);
15 ZTY=z_T*MVA_B/v2^2;   // star side (pu)
16
17 Ztot=Z1+Z2+ZTY;
18 V1=1;               //sending end voltage [pu]
19 I1=1;               //rated current (pu)
20 pf=.8;
21 V2=V1-I1*(real(Ztot)*pf+imag(Ztot)*.6); //
  load voltage (pu)
22 V2v=V2*v1;
23 disp(V2v, 'load voltage (kv) ');

```

Scilab code Exa 3.21 to calculate fault current in feeder lines primary and secondary lines of receiving end transformers

```

1 // to calculate fault current in feeder lines , primary
  and secondary lines of receiving end
  transformers

```

```

2
3 clc;
4
5 r=60;           //kva rating of 3-ph common base
6 s=200;         //kva rating of 3ph transformer
7 //sending end
8 X_Tse=.06*r/s; //0.06= reactance of transformer
   based on its own rating
9 //in 2 kv feeder
10 V_B=2000/sqrt(3); //line to neutral
11 I_B=r*1000/(sqrt(3)*2000);
12 Z_B=V_B/I_B;
13 X_feeder=0.7/Z_B; //feeder reactance=0.7
14 //receiving end
15 X_Tre=0.0051;
16 X_tot=X_Tse+X_feeder+X_Tre;
17 V_se=20/20;
18 I_fc=V_se/X_tot; //feeder current
19
20 I_f=I_fc*I_B;    disp(I_f,'current in 2kv feeder(A) '
   );
21 I_t1=I_f/sqrt(3); disp(I_t1,'current in 2kv
   winding of transformer(A)');
22 I_t2=I_t1*10;   disp(I_t2,'current in 200kv winding
   of transformer(A)');
23 I_l=I_t2*sqrt(3); disp(I_l,'current at load
   terminals(A)');

```

Scilab code Exa 3.22 To calculate voltage and kva rating of 1ph transformer

```

1 // To calculate voltage and kva rating of 1-ph
   transformer
2
3 clc;

```



```

4
5 V_p=33;      //primary side voltage(V)
6 V_s=11;     //secondary side voltage(V)
7 V_p1=V_p/sqrt(3); //per ph primary side voltage(V
)
8 V_p2=V_s/sqrt(3); //per ph secondary side voltage
(V)
9
10 r=6000;    //kva rating 3-ph
11 s=r/3;    //per phase
12 disp('Y/Y conn');
13 disp(V_p1,'primary side ph voltage(V)');
14 disp(V_p2,'secondary side ph voltage(V)');
15 disp(s,'kva rating of transformer');
16
17 disp('Y/D conn');
18 disp(V_p1,'primary side ph voltage(V)');
19 disp(V_s,'secondary side ph voltage(V)');
20 disp(s,'kva rating of transformer');
21
22 disp('D/Y conn');
23 disp(V_p,'primary side ph voltage(V)');
24 disp(V_p2,'secondary side ph voltage(V)');
25 disp(s,'kva rating of transformer');
26
27 disp('D/D conn');
28 disp(V_p,'primary side ph voltage(V)');
29 disp(V_s,'secondary side ph voltage(V)');
30 disp(s,'kva rating of transformer');

```

Scilab code Exa 3.23 to calculate reactance in ohms line voltage kva rating series reactance for YY and YD conn

```

1 // to calculate (a)reactance in ohms(b)line voltage ,
   kva rating ,series reactance for Y/Y and Y/D

```

```

    conn
2
3  clc;
4  Xpu=0.12;    // of 1-ph transformer
5
6  function [X]=Xohm(kv,MVA)
7      X=(Xpu*kv^2)/MVA;
8  endfunction
9
10 disp('(a)');
11 MVAa=75*10^-3;
12 Vhv=6.6;
13 Vlv=.4;
14 Xhv=Xohm(Vhv,MVAa);    disp(Xhv,'X(ohm) of hv side')
    ;
15 Xlv=Xohm(Vlv,MVAa);    disp(Xlv,'X(ohm) of lv side')
    ;
16
17 disp('(b)');
18 disp('Y/Y');
19 MVAab=MVAa*3;
20 Vhv=6.6*sqrt(3);    disp(Vhv,'V_hv(kV)');
21 Vlv=.4*sqrt(3);    disp(Vlv,'V_lv(kV)');
22 Xhv=Xohm(Vhv,MVAab);    disp(Xhv,'X(ohm) of hv side')
    ;
23 Xlv=Xohm(Vlv,MVAab);    disp(Xlv,'X(ohm) of lv side')
    ;
24
25 disp('Y/D');
26 MVAab=MVAa*3;
27 Vhv=6.6*sqrt(3);    disp(Vhv,'V_hv(kV)');
28 Vlv=.4;    disp(Vlv,'V_lv(kV)');
29 Xhv=Xohm(Vhv,MVAab);    disp(Xhv,'X(ohm) of hv side')
    ;
30 Xlv=Xohm(Vlv,MVAab);    disp(Xlv,'X(ohm) of lv side')
    ;

```

Scilab code Exa 3.24 find how 2 transformers connected in parallel share the load

```

1 //find how 2 transformers connected in parallel
  share the load
2
3 clc;
4 Z1=complex(.012,.06);
5 Z2=2*complex(.014,.045);
6 Z=Z1+Z2;
7 r=800;           //kva rating
8 pf=.8;
9 S_L=r*(complex(pf,-1*sind(acosd(pf))));
10 S_1=S_L*Z2/Z;disp(S_1,'load by first transformer(kVA
  )');
11 S_2=S_L*Z1/Z;disp(S_2,'load by second transformer(
  kVA)');
12
13 S_2rated=300;
14 S_Lmax=S_2rated*abs(Z)/abs(Z1);
15 disp(S_Lmax,'max load by both transformer(kVA)');
16
17 r1=600;         //kva
18 V=440;
19 Z1actual=Z1*V/(r1*1000/V);
20 Z2actual=Z2*V/(r1*1000/V);
21 Zactual=Z1actual+Z2actual;
22 Z_Lact=V^2/(S_L*1000);
23
24 V1=445;
25 I1=(V1*Z2actual-10*Z_Lact)/(Z1actual*Z2actual+Z_Lact
  *Zactual);
26 I2=(V1*-1*Z1actual-10*Z_Lact)/(Z1actual*Z2actual+
  Z_Lact*Zactual);

```

```

27 S1=V*I1/1000;    disp(S1,'kVA of first transformer')
    ;
28 S2=V*I2/1000;    disp(S2,'kVA of second transformer'
    );
29 Pout=abs(S1)*cosd(atan2(imag(S1)/real(S1)))+abs(S2)*
    cosd(atan2(imag(S2)/real(S2)));
30 disp(Pout,'total output power(kW)');

```

Scilab code Exa 3.25 find pu value of the equivalent ckt steady state short ckt current and voltages

```

1 //find pu value of the equivalent ckt, steady state
  short ckt current and voltages
2
3 clc;
4 r=5;           //MVA rating
5 V_Bp=6.35;     //for primary
6 I_Bp=r*1000/V_Bp;
7 V_Bs=1.91;     //for secondary
8 I_Bs=r*1000/V_Bs;
9 //from resp tests
10 V1=.0787;
11 I1=.5;
12 V2=.1417;
13 I2=.5;
14 V3=.1212;
15 I3=.5;
16 X12=V1/I1;
17 X13=V2/I2;
18 X23=V3/I3;
19 X1=I1*(X12+X13-X23);
20 X2=I2*(X23+X12-X13);
21 X3=I3*(X13+X23-X12);
22 disp(X1,'X1(pu)');
23 disp(X2,'X2(pu)');

```

```

24 disp(X3, 'X3(pu) ');
25
26 V1=1;
27 I_sc=V1/X13;
28 I_scp=I_sc*I_Bp;    disp(I_scp, 'sc current primary
    side(A) ');
29 I_sct=I_sc*r*1000*1000/(400/sqrt(3));    disp(I_sct,
    'sc current tertiary side(A) ');
30 V_A=I_sc*X3;
31 V_Aact=V_A*1.91*sqrt(3);
32 disp(V_Aact, 'V_A(actual) line to line(kV) ');

```

Scilab code Exa 3.26 to calculate line currents of 3 ph side

```

1 // to calculate line currents of 3 ph side
2
3 clc;
4 N1=6600;
5 N2=100;
6 a=N1/N2;
7 b=(sqrt(3)/2)*a;
8 P=400;    //kW
9 pfa=.707;
10 pfb=1;
11 V=100;
12 Ia=P*1000/(V*pfa);
13 Ib=P*2*1000/(V*pfb);
14 I_A=Ia/b;disp(I_A, 'I_A (A) ');
15 I_BC=Ib/a;
16 I_B=I_BC-49.5*complex(pfa,pfa);    disp(abs(I_B), '
    I_B (A) ');
17 I_C=I_BC+49.5*complex(pfa,-1*pfa);disp(abs(I_C), 'I_C
    (A) ');

```

Scilab code Exa 3.27 to calculate magnitude and phase of secondary current

```
1 //to calculate magnitude and phase of secondary
  current
2
3 clc;
4 X1=505; //uohm
5 X2=551; //uohm
6 R1=109; //uohm
7 R2=102; //uohm
8 Xm=256; //mohm
9 I1=250; //A
10 I22=complex(0,Xm*1000)*I1/(complex(R1,X2+Xm*1000));
11 N1=250;
12 N2=5;
13 I2=I22*(N2/N1);
14 disp(abs(I2), 'current magnitude(A)');
15 disp(atand(imag(I2)/real(I2)), 'phase(degree)');
16 disp('now Rb is introduced in series');
17 Rbb=200; //uohm
18 Rb=(N2/N1)^2*Rbb;
19 I22=complex(0,Xm*1000)*I1/(complex((R1+Rb),X2+Xm
  *1000));
20 I2=I22*(N2/N1);
21 disp(abs(I2), 'current magnitude(A)');
22 disp(atand(imag(I2)/real(I2)), 'phase(degree)');
23 disp('no chnage as Rb is negligible');
```

Scilab code Exa 3.28 to calculate sec voltage magnitude and ph

```
1 //to calculate sec voltage magnitude and ph
```

```

2
3 clc;
4 a=6000/100;      //turn ratio
5 R1=780;
6 R2=907;
7 X1=975;
8 X2=1075;
9 Xm=443*1000;
10 disp('sec open');
11 //Zb=inf;
12 V1=6500;
13 V22=complex(0,Xm)*V1/complex(R1,Xm);
14 V2=V22/a;
15 disp(abs(V2),'voltage magnitude(V)');
16 disp(atand(imag(V2)/real(V2)),'phase(deg)');
17
18 disp('when Zb=Rb');
19 Rb=1;
20 Rbb=Rb*a^2;
21 Zm=complex(0,Xm/1000)*Rbb/complex(0,Xm/1000)+Rbb;
22 R=complex(R1/1000,X1/1000)+Zm;
23 Vm=Zm*V1/R;
24 V2=Vm/a;
25 disp(abs(V2),'voltage magnitude(V)');
26 disp(atand(imag(V2)/real(V2)),'phase(deg)');
27
28 disp('when Zb=jXb');
29 Rb=complex(0,1);
30 Rbb=Rb*a^2;
31 Zm=complex(0,Xm/1000)*Rbb/complex(0,Xm/1000)+Rbb;
32 R=complex(R1/1000,X1/1000)+Zm;
33 Vm=Zm*V1/R;
34 V2=Vm/a;
35 disp(abs(V2),'voltage magnitude(V)');
36 disp(atand(imag(V2)/real(V2)),'phase(deg)');

```

Scilab code Exa 3.29 to calculate L1 and L2 and coupling coefficient

```
1 //to calculate L1 and L2 and coupling coefficient
2
3 clc;
4 a=10;
5 V_p=200;
6 I_p=4;
7 Xm=V_p/I_p;
8 f=50;
9 L1=Xm/(2*%pi*f);disp(L1, 'L1(H) ');
10 V_s=1950;
11 w_max=V_s/(sqrt(2)*%pi*f);
12 M=w_max/(sqrt(2)*I_p);
13
14 v_s=2000;
15 i_s=.41;
16 w_max=sqrt(2)*i_s*M;
17 E1=sqrt(2)*%pi*f*w_max;
18 L2=v_s/(sqrt(2)*%pi*f*sqrt(2)*i_s);disp(L2, 'L2(H) ');
19 k=M/(sqrt(L1)*sqrt(L2));disp(k, 'coupling coeff');
```

Scilab code Exa 3.30 to calculate leakage inductance magnetising inductance mutual inductance and selfinductance

```
1 // to calculate leakage inductance , magnetising
   inductance ,mutual inductance and self-inductance
2
3 clc;
4 V1=2400;
5 V2=240;
6 a=V1/V2;
```



```

7 R1=.2;
8 X1=.45;
9 Rl=10000;
10 R2=2*10^-3;
11 X2=4.5*10^-3;
12 Xm=1600;
13 f=50;
14 l1=X1/(2*pi*f);disp(l1,'leakage inductance ie l1(H)
    ');
15 l2=X2/(2*pi*f);disp(l2,'l2(H) ');
16 Lm1=Xm/(2*pi*f);disp(Lm1,'magnetising inductance(H)
    ');
17 L1=Lm1+l1;disp(L1,'self-inductance ie L1(H) ');
18 M=Lm1/a;
19 L2=l2+M/a;disp(L2,'L2(H) ');
20 k=M/sqrt(L1*L2);disp(k,'coupling factor ');

```

Scilab code Exa 3.31 to calculate percentage voltage reg and efficiency

```

1 //to calculate %voltage reg and efficiency
2
3 clc;
4 P=500000;
5 V1=2200;
6 V2=1100;
7 V0=110;
8 I0=10;
9 P0=400;
10 Y0=I0/V0;
11 Gi=P0/(V0^2);
12 Bm=sqrt(Y0^2-Gi^2);
13 Vsc=90;
14 Isc=20.5;
15 Psc=808;
16 Z=Vsc/Isc;

```

```
17 R=Psc/Isc^2;
18 X=sqrt(Z^2-R^2);
19 TR=V1/V2;
20 Gi_HV=Gi/TR^2;
21 Bm_HV=Bm/TR^2;
22 R_LV=R/TR^2;
23 X_LV=X/TR^2;
24 I2=P/V2;
25 pf=.8;
26 Th=acos(pf);
27 dV=I2*(R_LV*cos(Th)+X_LV*sin(Th));
28 VR=(dV/V2)*100; disp(VR,'voltage regulation(%)');
29 Pi=P0;
30 Pc=Psc;
31 n=P*100/(P+Pi+Pc); disp(n,'eff(%)');
```

Chapter 5

Basic Concepts in Rotating Machines

Scilab code Exa 5.1 To calculate harmonic factor for stator

```
1 // To calculate harmonic factor for stator
2
3 clc;
4 S=36; //no of slots
5 q=3; //no of phases
6 p=4; //no of poles
7 m=S/(q*p); //slots/pole/phase
8 g=180*p/S; //gamma elec
9 function [k]=bfctr(n)
10     k=sind(m*n*g/2)/(m*sind(n*g/2));
11 endfunction
12
13 K_b=bfctr(1);
14 disp(K_b, 'K_b(fundamental) ');
15
16 K_b=bfctr(3);
17 disp(K_b, 'K_b(third harmonic) ');
18
19 K_b=bfctr(5);
```

```
20 disp(K_b, 'K_b(fifth harmonic)');
```

Scilab code Exa 5.2 to find the frequency and phase and line voltages

```
1 // to find the frequency and phase and line voltages
2
3 clc;
4 n=375; //speed in rpm
5 p=16; //no of poles
6 f=n*p/120;
7 disp(f, 'freq (Hz)');
8 S=144; //no of slots
9 c=10; //no of conductors/slot
10 t=S*c/2; //no of turns
11 ph=3;
12 N_ph=t/ph; //no of turns/ph
13 g=180*p/S; //slots angle
14 m=S/(p*ph); //slots/pole/phase
15 K_b=sind(m*g/2)/(m*sind(g/2)); //breadth factor
16 phi=0.04; //flux per pole
17 E_p=4.44*K_b*f*N_ph*phi;
18 disp(E_p, 'phase voltage(V)');
19 E_l=sqrt(3)*E_p;
20 disp(E_l, 'line voltage(V)');
```

Scilab code Exa 5.3 to find the phase and line voltages

```
1 // to find the phase and line voltages
2
3 clc;
4 f=50; //freq
5 n=600; //speed in rpm
6 p=120*f/n;
```

```

7 ph=3;
8 m=4;          //slots/pole/ph
9 S=p*ph*m;    //slots
10 t=12;       //turns per coil
11 N_ph=S*t/ph;
12 g=180*p/S;
13 K_b=sind(m*g/2)/(m*sind(g/2)); //breadth factor
14 cp=10;      //coil pitch
15 pp=S/cp;    //pole pitch
16 theta_sp=(pp-cp)*g; //short pitch angle
17 K_p=cosd(theta_sp/2);
18 phi=.035;
19 E_p=4.44*K_b*K_p*f*N_ph*phi;
20 disp(E_p, 'phase voltage (V) ');
21 E_l=sqrt(3)*E_p;
22 disp(E_l, 'line voltage (V) ');

```

Scilab code Exa 5.4 to calculate flux per pole

```

1 // to calculate flux/pole
2
3 clc;
4 S=42;
5 p=2;
6 ph=3;
7 m=S/(p*ph); //slots/pole/phase
8 g=180*p/S; //slots angle
9 K_b=sind(m*g/2)/(m*sind(g/2)); //breadth factor
10 cp=17;
11 pp=S/p;
12 theta_sp=(pp-cp)*g; //short pitch angle
13 K_p=cosd(theta_sp/2);
14 N_ph=S*2/(ph*p*2); //2 parallel paths
15 E_p=2300/sqrt(3);
16 phi=E_p/(4.44*K_b*K_p*f*N_ph);

```

```
17 disp(phi, 'flux/pole (Wb) ');
```

Scilab code Exa 5.5 to calculate useful flux per pole and ares of pole shoe

```
1 // to calculate useful flux/pole and ares of pole
  shoe
2
3 clc;
4 p=1500*1000; //power
5 v=600;
6 I_a=p/v;
7 cu=25*1000; //copper losses
8 R_a=cu/I_a^2;
9 E_a=v+I_a*R_a;
10 n=200;
11 Z=2500;
12 p=16;
13 A=16;
14 phi=E_a*60*A/(p*n*Z);
15 disp(phi, 'flux/pole (Wb) ');
16 fd=0.85; //flux density
17 a=phi/fd;
18 disp(a, 'area of pole shoe(m*m) ');
```

Scilab code Exa 5.6 To calculate em power developed mech power fed torque provided by primemover

```
1 // To calculate em power developed ,mech power fed ,
  torque provided by primemover
2
3 clc;
4 phi=32*10^-3; //flux/pole
5 n=1600; //speed in rpm
```

```

6 Z=728;           //no of conductors
7 p=4;
8 A=4;
9 E_a=phi*n*Z*(p/A)/60;
10 I_a=100;
11 P_e=E_a*I_a;
12 disp(P_e, 'electromagnetic power (W) ');
13 P_m=P_e;
14 disp(P_m, 'mechanical power (W) fed ');
15 w_m=2*pi*n/60;
16 T=P_m/w_m;
17 disp(T, 'primemover torque (Nm) ');

```

Scilab code Exa 5.9 To determine peak value of fundamental mmf

```

1 // To determine peak value of fundamental mmf
2
3 clc;
4 f=50;
5 n_s=300;
6 p=120*f/n_s;
7 P=400*1000; //power
8 V=3300;
9 I_L=P/(sqrt(3)*V);
10 I_P=I_L;
11 I_m=sqrt(2)*I_P; //max value of phase current
12 S=180;
13 g=180*p/S;
14 ph=3;
15 m=S/(p*ph); //slots/pole/phase
16 K_b=sind(m*g/2)/(m*sind(g/2)); //breadth factor
17 c=8; //conductors/1 coil side
18 N_ph=S*c/(ph*2); //turns/phase
19 F_m=(4/pi)*K_b*(N_ph/p)*I_m;
20 F_peak=(3/2)*F_m;

```

```
21 disp(F_peak, 'peak mmf(AT/pole)');
```

Scilab code Exa 5.10 to calculate field current and flux per pole and to calculate open ckt ph and line voltages and to calculate field current

```
1 // (a)to calculate field current and flux/pole(b)to
  calculate open ckt ph and line voltages
2 // (c)to calculate field current
3
4 clc;
5 B_peak=1.65;
6 g=.008;
7 u_o=4*%pi*10^-7;
8 P=4;
9 K_b=.957;
10 N_field=364/2;
11 I_f=B_peak*%pi*g*P/((4*u_o)*(K_b*N_field));
12 disp(I_f, 'field current(A)');
13 l=1.02; //rotor length
14 r=.41/2; //rotor radius
15 phi=(4/P)*B_peak*l*r;
16 disp(phi, 'flux/pole(Wb)');
17 N_ph=3*11*P/2;
18 ga=60/3; //slot angle
19 m=3;
20 f=50;
21 K_b=sind(m*ga/2)/(m*sind(ga/2)); //breadth factor
22 E_ph=sqrt(2)*%pi*K_b*f*N_ph*phi;
23 disp(E_ph, 'E_ph(V)');
24 E_line=sqrt(3)*E_ph;
25 disp(E_line, 'E_line(V)');
26 I_fnew=.75*I_f;
27 disp(I_fnew, 'I_f(new)(A)');
```

Scilab code Exa 5.11 to find fundamental mmf wave speed and its peak value

```
1 // to find fundamental mmf wave, speed and its peak
  value
2
3 clc;
4 p=4;
5 S=60;
6 g=180*p/S;
7 ph=3;
8 m=S/(p*ph); // slots/pole/phase
9 K_b=sind(m*g/2)/(m*sind(g/2)); //breadth factor
10 I_L=48;
11 I_P=I_L/sqrt(3);
12 I_Pmax=I_P*sqrt(2);
13 c=24; //conductors
14 N_ph=S*c/(ph*2); //turns/phase
15 F_m=(4/%pi)*K_b*(N_ph/p)*I_Pmax;
16 disp(F_m, 'F_m(AT/pole)');
17 F_peak=(3/2)*F_m;
18 disp(F_peak, 'F_peak(AT/pole)');
19 n=120*f/P;
20 disp(n, 'speed (rpm)');
```

Scilab code Exa 5.12 to calculate resultant air gap flux per pole

```
1 // to calculate resultant air gap flux/pole
2
3 clc;
4 F1=400;
5 F2=850;
```

```

6 a=123.6;
7 Fr=sqrt(F1^2+F2^2+2*F1*F2*cosd(a));
8 P=1.408*10^-4;           //permeance/pole
9 phi_r=P*Fr;
10 disp(phi_r, 'air gap flux/pole(Wb)');

```

Scilab code Exa 5.13 To calculate resultant AT per pole and peak air gap flux density rotor AT per pole stator AT and its angle with the resultant AT stator current

```

1 //To calculate resultant AT/pole and peak air gap
  flux density , rotor AT/pole , stator AT and its
  angle with the resultant AT, stator current
2
3 clc;
4 ph=3;
5 S=36;
6 c=8*2;
7 p=4;
8 f=50;
9 N_ph=S*c/(ph*2);           //turns/phase
10 ga=180*p/S;
11 m=S/(p*ph);           //slots/pole/phase
12 K_b=sind(m*ga/2)/(m*sind(ga/2));           //breadth factor
13 V_L=400;
14 V_ph=V_L/sqrt(3);
15 phi_r=V_ph/(4.44*K_b*f*N_ph);
16 disp(phi_r, 'phi_r (Wb/pole)');
17 D=.16;
18 l=0.12;
19 PA=%pi*l*D/4;           //pole area
20 B_rav=phi_r/PA;
21 B_rpeak=(%pi/2)*B_rav;
22 g=2*10^-3;
23 u_o=4*%pi*10^-7;

```

```

24 F_r=g*B_rpeak/u_o;
25 disp(F_r, 'F_r(AT/pole)');
26 T=60;           // torque (Nm)
27 d=26;
28 F2=T/((%pi/2)*(p/2)^2*phi_r*sind(d));
29 disp(F2, 'F2(AT/pole)');
30 F1=sqrt(F2^2+F_r^2-2*F2*F_r*sind(d));
31 disp(F1, 'F1(AT/pole)');
32 w=acosd((F1^2+F_r^2-F2^2)/(2*F1*F_r));
33 disp(w, 'angle(deg)');
34 K_w=K_b;
35 I_a=F1/((3/2)*(4*sqrt(2)/%pi)*K_w*(N_ph/p));
36 disp(I_a, 'I_a(A)');

```

Scilab code Exa 5.14 to determine in F2 peak rotor AT max torque ele ip at max torque for motoring mode and open ckt voltage for generating mode

```

1 //to determine in F2, peak rotor AT, max torque, ele
  i/p at max torque(motoring mode), open ckt voltage
  (generating mode)
2
3 clc;
4 disp('motoring mode');
5 K_w=.976;
6 N_pole=746;
7 p=4;
8 I_f=20;
9 F2=(4/%pi)*K_w*(N_pole/p)*I_f;
10 disp(F2, 'F2(AT)');
11 B_r=1.6;
12 D=.29;
13 l=.35;
14 T_max=(p/2)*(%pi*D*l/2)*F2*B_r;
15 disp(T_max, 'T_max');
16 f=50;

```

```

17 w_m=4*%pi*f/p;
18 P_in=T_max*w_m;
19 disp(P_in, 'P_in(W) ');
20
21 disp('generating mode');
22 m=S/(3*p);
23 ga=180*p/S;
24 K_b=sind(30)/(3*sind(15/2));
25 K_w=K_b;
26 u_o=4*%pi*10^-7;
27 phi_r=((2*D*l/p)*(u_o/g))*F2;
28 N_ph=20*p*4/2;
29 E_ph=4.44*K_b*f*N_ph*phi_r;
30 E_l=sqrt(3)*E_ph;
31 disp(E_l, 'E_l(V) ');

```

Scilab code Exa 5.15 to find motor speed

```

1 // to find motor speed
2
3 clc;
4 n=1500;           //speed of sync generator
5 p=4;
6 f=n*p/120;
7
8 p_im=6;
9 n_s=120*f/p_im;
10 s=0.05;         //slip
11 n_im=(1-s)*n_s;
12 disp(n_im, 'speed of induction motor(rpm) ');

```

Scilab code Exa 5.16 to find voltage available bw slip rings and its freq

```

1 //to find voltage available b/w slip rings and its
   freq
2
3 clc;
4 disp('(a)');
5 f=50;
6 p=6;
7 n_s=120*f/p;
8 n=-1000;
9 s=(n_s-n)/n_s;
10 f_s=f*s;
11 disp(f_s, 'slip freq(Hz)');
12 v2=100;
13 V2=s*v2;
14 disp(V2, 'slip ring voltage(V)');
15
16 disp('(b)');
17 n=1500;
18 s=(n_s-n)/n_s;
19 f_s=abs(f*s);
20 disp(f_s, 'slip freq(Hz)');
21 v2=100;
22 V2=s*v2;
23 disp(V2, 'slip ring voltage(V)');

```

Scilab code Exa 5.18 to find no of poles slip and freq of rotor currents at full load motor speed at twice of full load

```

1 //to find no of poles , slip and freq of rotor
   currents at full load , motor speed at twice of
   full load
2
3 clc;
4 n_s=600;
5 f=50;

```

```

6 P=120*f/n_s;
7 disp(p, 'no of poles ');
8 n=576;
9 s=(n_s-n)/n_s;
10 disp(s, 'slip ');
11 f2=s*f;
12 n_r=s*n_s;
13 disp(n_r, 'rotor speed wrt rotating field(rpm)');
14 ss=f2*s;
15 n=(1-ss)*n_s;
16 disp(n, 'motor speed(rpm)');
17 nn=528;
18 s_old=s;
19 s_new=(n_s-nn)/n_s;
20 fac=s_new/s_old;
21 disp(fac, 'factor is ');

```

Scilab code Exa 5.19 to calculate amplitude of travelling wave mmf peak value of air flux density velocity of wave current freq at some desired velocity

```

1 // to calculate amplitude of travelling wave mmf,
   peak value of air flux density , velocity of wave,
   current freq at some desired velocity
2
3 clc;
4 K_w=.925;
5 N_ph=48;
6 I=750/sqrt(2);
7 wndnglgth=2;
8 wavelgth=wndnglgth/0.5;
9 p=2*wavelgth;
10 F_peak=(3/2)*(4*sqrt(2)/%pi)*K_w*(N_ph/p)*I;
11 disp(F_peak, 'F_peak(A/m)');
12 g=.01;
13 u_o=4*%pi*10^-7;

```

```
14 B_peak=u_o*F_peak/g;
15 disp(B_peak, 'B_peak(T) ');
16 f=25;
17 B=.5;
18 v=f*B;      disp(v, 'velocity (m/s) ');
19 vv=72*10^3/3600;      //given velocity
20 f=vv/0.5;
21 disp(f, 'freq (Hz) ');
```

Chapter 7

DC Machines

Scilab code Exa 7.1 to calculate no of parrallel path

```
1 // to calculate no of parrallel path
2
3 clc;
4 S=12;           //no of commutator segments
5 P=4;
6 Y_cs=S/P;      //slots
7 Y_b=2*Y_cs+1;
8 y_f=Y_b-2;
9 disp(y_f, 'no of parralel path');
```

Scilab code Exa 7.2 to find spacing bw brushes

```
1 // to find spacing b/w brushes
2
3 clc;
4 S=22;
5 P=4;
6 Y_cs=floor(S/P);
```



```

7 U=6;           //coil sides/slot
8 Y_b=Y_cs*U+1;
9 y_f=Y_b-2;
10 n=(1/2)*U*S;      //no of commutator segments
11 A=4;           //no of brushes
12 sp=n/A;
13 disp(sp, 'spacing b/w adjacent brushes');

```

Scilab code Exa 7.3 to calculate relevant pitches for wave windings

```

1 //to calculate relevant pitches for wave windings
2
3 clc;
4 S=16;
5 P=6;
6 Y_cs=floor(S/P);
7 U=2;
8 Y_b=Y_cs*U+1;
9 C=16;
10 y_c=U*(C-1)/P;
11 y_f=2*y_c-Y_b;
12 disp(y_f, 'no of pitches');

```

Scilab code Exa 7.4 to find distance bw brushes

```

1 // to find distance b/w brushes
2
3 clc;
4 S=28;
5 P=4;
6 U=8;
7 c=U*S/2;
8 y_c=2*(c-1)/P;

```

```

9 Y_c=55;
10 C=(P/2)*Y_c+1;
11 Y_cs=floor(S/P);
12 Y_b=Y_cs*U+1;
13 y_f=2*Y_c-Y_b;
14 d=C/P;
15 disp(d, 'dis b/w brushes ');

```

Scilab code Exa 7.5 to find the torque and gross mech power developed

```

1 // to find the torque and gross mech power developed
2
3 clc;
4 D=.3;
5 l=.2;
6 p=4;
7 fd=.4; //flux density
8 phi=%pi*(D/p)*l*fd; //flux/pole
9 n=1500;
10 Z=400;
11 A=4;
12 E_a=phi*n*Z*(p/A)/60;
13 I_a=25;
14 mp=E_a*I_a;
15 disp(mp, 'gross mech power developed (W) ');
16 T=mp/(2*%pi*n/60);
17 disp(T, 'torque developed (Nm) ');

```

Scilab code Exa 7.6 to calculate ratio of generator speed to motor speed

```

1 // to calculate ratio of generator speed to motor
  speed
2

```

```

3  clc;
4  V=220;
5  P=4000;
6  I_a=P/V;
7  r_a=.4;           //armature resistance
8  E_ag=V+I_a*r_a;
9  E_am=V-I_a*r_a;
10 a=1.1;           //phi_m/phi_g
11 n=(E_ag/E_am)*a;
12 disp(n, 'n_g/n_m');

```

Scilab code Exa 7.7 to calculate speed of motor

```

1  // to calculate speed of motor
2
3  clc;
4  V=230;
5  R_f=115;         //field resistance
6  I_f=V/R_f;
7  P_g=100000;     //electric power (m/c running as
   generator)
8  I_L=P_g/V;
9  I_a=I_f+I_L;
10 R_a=.08;        //armature resitance
11 E_ag=V+I_a*R_a;
12 n_g=750;        //speed
13
14 P_m=9000;       //m/c running as motor
15 I_l=P_m/V;
16 I_A=I_l-I_f;
17 E_am=V-I_A*R_a;
18 n_m=(E_am/E_ag)*n_g;
19 disp(n_m, 'motor speed (rpm)');

```

Scilab code Exa 7.8 to calculate electromagnet power and torque

```
1 //to calculate electromagnet power and torque
2
3 clc;
4 E_a=250;
5 R_a=.05;
6 n=3000;
7 w_m=(n*2*%pi)/60;
8 disp('when terminal voltage is 255V');
9 V_t=255;
10 I_a=(V_t-E_a)/R_a;
11 P_in=E_a*I_a;
12 disp(P_in,'electromagnet power(W)');
13 T=P_in/w_m;
14 disp(T,'torque(Nm)');
15
16 disp('when terminal voltage is 248V');
17 V_t=248;
18 I_a=(E_a-V_t)/R_a;
19 P_in=E_a*I_a;
20 disp(P_in,'electromagnet power(W)');
21 T=P_in/w_m;
22 disp(T,'torque(Nm)');
```

Scilab code Exa 7.9 to calculate electromagnet power

```
1 //to calculate electromagnet power
2
3 clc;
4 n_f=3000;           //field speed
5 n_a=2950;          //armature speed
```

```

6 E=250;
7 E_a=E*(n_a/n_f);
8 V_t=250;
9 R_a=0.05;
10 I_a=(V_t-E_a)/R_a;
11 P_in=V_t*I_a;
12 disp(P_in, 'power (W) ');
13 P=E_a*I_a;
14 disp(P, 'electromagnetic power (W) ');

```

Scilab code Exa 7.10 to calculate cross and demagnetising turns per pole

```

1 // to calculate cross and demagnetising turns/pole
2
3 clc;
4 P=250000;
5 V=400;
6 I_a=P/V; //armature current
7 n=6; //no of parallel path
8 I_c=I_a/n; //conductor current
9 Z=720; //lap wound conductors
10 AT_a=(1/2)*Z*I_c/n;
11
12 B=2.5*n/2; //brush leadof 2.5 angular degrees
    (mech) from geo neutral
13 AT_c=AT_a*(1-(2*B)/180);
14 disp(AT_c, 'cross magnetising ampere turns(AT/pole)');
    ;
15 AT_d=AT_a*((2*B)/180);
16 disp(AT_d, 'demagnetising ampere turns(AT/pole)');

```

Scilab code Exa 7.11 to calculate no of conductors on each pole piece

```

1 //to calculate no of conductors on each pole piece
2
3 clc;
4 Z=256;
5 A=6;
6 P=6;
7 r=.71; //ratio of pole arc to pole pitch
8 N_cw=(Z/(2*A*P))*r;
9 N_cc=ceil(2*N_cw);
10 disp(N_cc,'compensating conductors/pole');

```

Scilab code Exa 7.12 to calculate no of turns reqd on each interpole

```

1 //to calculate no of turns reqd on each interpole
2
3 clc;
4 P=25000;
5 V=440;
6 I_a=P/V;
7 Z=846;
8 A=2;
9 P=4;
10 B_i=.5;
11 u_o=4*pi*10^-7;
12 l_gi=.003;
13 AT_i=((I_a*Z)/(2*A*P))+(B_i*l_gi)/u_o;
14 N_i=ceil(AT_i/I_a);
15 disp(N_i,'no of turns');

```

Scilab code Exa 7.13 to calculate mmf per pole and speed at no load in rpm

```

1 //to calculate mmf per pole and speed at no load(rpm
  )
2
3 clc;
4 ATppole=[1200 2400 3600 4800 6000];
5 V_i=[76 135 180 215 240];
6 plot(ATppole,V_i);
7 xlabel('AT/pole');
8 ylabel('E_a(V)');
9
10 V=240;
11 vd=25;           //voltage drop ie I_a*(R_a+R_se)
12 E_a=V-vd;
13 AT_netfl=4800;
14 AT_sefl=2400;
15 AT_sh=AT_sefl;
16
17 AT_senl=(3/25)*AT_sefl;
18 AT_sh=2400;           //no change
19 AT_netnl=AT_senl+AT_sh;
20 disp(AT_netnl,'mmf/pole on no load(AT)');
21 n=850;
22 E_a=148;           //from the magnetising curve
23 E_anl=240-3;
24 nnl=n*E_anl/E_a;
25 disp(nnl,'speed at no load(rpm)');

```

Scilab code Exa 7.14 to estimate at full load internal induced emf voltage drop caused y armature rxn and field current armature rxn demagnitisation

```

1 // to estimate at full load internal induced emf,
  voltage drop caused y armature rxn, and field
  current ~ armature rxn demagnitisation
2
3 clc;

```

```

4 I_f=[0 0.2 0.4 0.6 0.8 1 1.2 1.4];
5 Voc=[10 52 124 184 220 244 264 276];
6 plot(I_f,Voc);
7 xlabel('I_f(A)');
8 ylabel('Voc');
9
10 I_af1=50;
11 R_a=.3;
12 vd=I_af1*R_a;
13 V=240;
14 E_a=V+vd;
15 disp(E_a,'internal induced emf(V)');
16 V_oc=276; //from magnetising curve,I_f=1.4
17 V_d=V_oc-E_a;
18 disp(V_d,'armature rxn vol drop(V)');
19 I_f=0.36;
20 K_ar=I_f/I_af1;
21 disp(K_ar,'armature rxn demagnetisation');

```

Scilab code Exa 7.16 to calculate terminal voltage and rated output current and calculate no of series turns per pole

```

1 //to calculate terminal voltage and rated output
  current and calculate no of series turns/pole
2
3 clc;
4 P=100000;
5 V=200;
6 I_L=P/V;
7 I_f=5;
8 I_a=I_L+I_f;
9 I_se=I_a;
10 N_se=5;
11 N_f=1200;
12 I_feq=I_f+(N_se/N_f)*I_se;

```



```

13 n=1000;
14 E_a=225;
15 nn=950;
16 E_aa=E_a*(nn/n);
17 R_a=0.03;
18 R_se=0.004;
19 V_t=E_aa-I_a*(R_a+R_se);
20 disp(V_t, 'terminal voltage (V) ');
21 I_fd=0.001875*I_a;
22 V_t=200;
23 E_a=V_t+I_a*(R_a+R_se);
24 E_aa=E_a*(n/nn);
25 I_fnet=7.5;
26 N_f=1000;
27 N_se=ceil((I_fnet+I_fd-I_f)*(N_f/I_a));
28 disp(N_se, 'no of series turns/pole');

```

Scilab code Exa 7.21 to determine demagnetising AT per pole and no of series turns reqd

```

1 //to determine demagnetising AT/pole and no of
   series turns reqd
2
3 clc;
4 V_oc=[220 230 240 250 260 270];
5 I_f=[1 1.15 1.35 1.5 1.69 2.02];
6 plot(I_f,V_oc);
7 xlabel('I_f (A)');
8 ylabel('V_oc (V)');
9
10 V=240;
11 I_a=83.3;
12 R_a=.12;
13 E_a=V+I_a*R_a;
14 n=1150;

```

```

15 nn=1190;
16 Ea=E_a*(nn/n);
17 I_f=2.1;
18 I_fnet=1.65;
19 I_fd=I_f-I_fnet;
20 N_sf=550;           //shunt field turns/pole
21 AT_d=N_sf*I_fd;
22 disp(AT_d,'demagnetising AT_d/pole');
23
24 //at no load(1190rpm)
25 V_t=230;
26 I_f=1.43;
27 AT_f=N_sf*I_f;
28 R_f=V_t/I_f;
29
30 //at load(1150rpm)
31 I_L=I_a-(V/R_f);
32 V_a=(V+I_a*.045)/(1+(.045/R_f));
33 E_a=V_a+I_a*.12;
34 //consult mag field
35 Ea=E_a*(nn/n);
36 Ifn=1.675;        //needed
37 ATn=N_sf*Ifn;
38 If=V_a/R_f;
39 ATf=N_sf*If;
40
41 ATse=ATn+AT_d-AT_f;
42 I_L=I_a-If;
43 Nse=floor(ATse/I_L);
44 disp(Nse,'no of series turns/pole');

```

Scilab code Exa 7.22 to compute terminal voltage at rated voltage current

```

1 // to compute terminal voltage at rated voltage

```

```

        current
2
3  clc;
4  R_a=0.05;
5  R_se=.01;
6  N_f=1000;
7  N_se=3;
8  I_sf=5.6;           //shunt field current
9  I_L=200;
10 I_a=I_L+I_sf;
11 N=N_f*I_sf+I_a*N_se;           //excitation ampere
        turns
12 I_freq=N/N_f;
13
14 E_a=282;
15 n=1200;
16 nn=1150;
17 Ea=E_a*(nn/n);
18 V_t=Ea-I_a*(R_a+R_se);
19 disp(V_t, 'terminal voltage (V) ');

```

Scilab code Exa 7.23 to calculate no series turns

```

1 //to calculate no series turns
2
3  clc;
4  I_sf=5.6;
5  N_f=1000;
6  AT_f=I_sf*N_f;
7  I_a=205.6;
8  Z=400;
9  I_L=200;
10 AT_d=Z*(I_a/I_L);
11 V_t=250;
12 R_a=0.05;

```

```

13 R_se=.01;
14 E_a=V_t+I_a*(R_a+R_se);
15 n=1150;
16 nn=1200;
17 Ea=E_a*(nn/n);
18
19 I_fnet=6.2;
20 ATnet=I_fnet*N_f;
21
22 ATse=ATnet+AT_d-AT_f;
23 Nse=ceil(ATse/I_a);
24 disp(Nse,'no of series turns/pole');

```

Scilab code Exa 7.24 to find generator output

```

1 //to find generator output
2
3 clc;
4 P=20000;
5 V=250;
6 I_a=P/V;
7 R_a=.16;
8 vd=I_a*R_a;
9 function [P_o]=output(E_a)
10     V_t=E_a-vd;
11     P_o=I_a*V_t;
12     disp(P_o,'generator output (W) ');
13 endfunction
14 disp('at I_f=1A');
15 E_a=150;
16 P_o=output(E_a);
17 disp('at I_f=2A');
18 E_a=257.5;
19 P_o=output(E_a);
20 disp('at I_f=2.5A');

```

```

21 E_a=297.5;
22 P_o=output(E_a);
23
24 disp('at speed 1200rpm');
25 function [Ea]=ratio(E_a);
26     Ea=.8*E_a
27 endfunction
28 disp('at I_f=1A');
29 E_a=150;
30 Ea=ratio(E_a);
31 P_o=output(Ea);
32 disp('at I_f=2A');
33 E_a=257.5;
34 Ea=ratio(E_a);
35 P_o=output(Ea);
36 disp('at I_f=2.5A');
37 E_a=297.5;
38 Ea=ratio(E_a);
39 P_o=output(Ea);

```

Scilab code Exa 7.25 to find power to the load

```

1 //to find power to the load
2
3 clc;
4 R_L=3;
5 R_a=.16;
6 function [P_o]=output(E_a)
7     I_a=E_a/(R_a+R_L);
8     P_o=I_a^2*R_L;
9     disp(P_o,'power fed to the load(W)');
10 endfunction
11 disp('at I_f=1A');
12 E_a=150;
13 P_o=output(E_a);

```

```

14 disp('at I_f=2A');
15 E_a=257.5;
16 P_o=output(E_a);
17 disp('at I_f=2.5A');
18 E_a=297.5;
19 P_o=output(E_a);

```

Scilab code Exa 7.28 to compute the generator induced emf when fully loaded in long shunt compound and short shunt compound

```

1 //to compute the generator induced emf when fully
  loaded in long shunt compound and short shunt
  compound
2
3 clc;
4 P=75000;
5 V_t=250;
6 I_L=P/V_t;
7 R_a=.04;
8 R_se=.004;
9 R_f=100;
10 disp('case of long shunt');
11 I_f=V_t/R_f;
12 I_a=I_L+I_f;
13 V_b=2;
14 E_aLS=V_t+I_a*(R_a+R_se)+V_b;
15 disp(E_aLS,'generator induced emf(V)');
16
17 disp('case of short shunt');
18 V_b=V_t+I_L*R_se;
19 I_f=V_b/R_f;
20 I_a=I_L+I_f;
21 E_aSS=V_t+(I_a*R_a)+2;
22 disp(E_aSS,'generator induced emf(V)');
23

```

```
24 d=(E_aLS-E_aSS)*100/V_t;
25 disp(d,'percent diff');
```

Scilab code Exa 7.29 to find field current and field resistance at rated terminal voltage em power and torque

```
1 // to find field current and field resistance at
  rated terminal voltage , em power and torque
2
3 clc;
4 V_o=250; //no load voltage
5 I_f=1.5;
6 R_f=V_o/I_f; disp(R_f,'field resistance(ohm)');
7 P=25000;
8 V_t=220;
9 I_L=P/V_t;
10 I_a=I_L; disp(I_a,'field current(A)');
11 R_a=.1;
12 E_a=V_t+I_a*R_a;
13 I_f=1.1;
14 R_f=V_t/I_f; disp(R_f,'field resistance(ohm)');
15 I_a=I_L-I_f;
16 emp=E_a*I_a;
17 disp(emp,'em power(W)');
18 n=1600;
19 emt=emp/(n*2*%pi/60);
20 disp(emt,'torque(Nm)');
21 I_fa=1.25; //actual I_f
22 I_c=I_fa-I_f;
23 disp(I_c,'I_f needed to counter effect armature
  current');
```

Scilab code Exa 7.32 to determine the reduction of flux per pole due to armature rxn

```
1 //to determine the reduction of flux/pole due to
   armature rxn
2
3 clc;
4 V=250;
5 R_a=.7;
6 function [phi]=arxn(I_a,n)
7     phi=(V-I_a*R_a)/n;
8 endfunction
9
10 phinl=arxn(1.6,1250);
11 disp(phinl,'flux/pole no load');
12
13 phil=arxn(40,1150);
14 disp(phil,'flux/pole load');
15
16 d=(phinl-phil)*100/phinl;
17 disp(d,'reduction in phi due to armature rxn(%)');
```

Scilab code Exa 7.33 to determine internal em torque developed

```
1 //to determine internal em torque developed
2
3 clc;
4 V=250;
5 I_a=85;
6 R_a=.18;
7 E_a=V-I_a*R_a;
8 n=1100;
9 T=E_a*I_a/(n*2*%pi/60);
10 disp(T,'torque(Nm)');
11 T_1=.8*T;    disp(T_1,'new torque(Nm)');
```



```

12 //T=K_a '* K_f*I_f*I_a=K_a '* K_f*.8*I_f*I_a1      so
13 I_a1=I_a/.8;
14 E_a1=V-I_a1*R_a;
15 //E_a=K_a '* K_f*I_f*n
16 //E_a1=K_a '* K_f*.8*I_f*n1      so
17 n1=(E_a1/E_a)*n/.8
18 disp(n1, 'speed is (rpm) ');

```

Scilab code Exa 7.34 to determine speed calculate internal torque developed on load and no load

```

1 //to determine speed, calculate internal torque
  developed on load and no load
2
3 clc;
4 V=220;
5 R_f=110;
6 I_f=V/R_f;
7 I_L=5;
8 I_a0=I_L-I_f;
9 R_a=.25;
10 E_a0=V-I_a0*R_a;
11 n=1200;
12 T_0=(E_a0*I_a0)/(2*pi*n/60);
13 disp(T_0, 'torque at no load (Nm) ');
14
15 I_L=62;
16 I_a1=I_L-I_f;
17 E_a1=V-I_a1*R_a;
18 n1=(E_a1/E_a0)*n/.95;      disp(n1, 'speed (rpm) ');
19 T_1=(E_a1*I_a1)/(2*pi*n1/60);
20 disp(T_1-T_0, 'torque at on load (Nm) ');

```

Scilab code Exa 7.36 to sketch speed torque characteristics of the series motor connected to mains by calculating speed and torque values at diff values of armature current

```

1 //to sketch speed torque characteristics of
   the series motor connected to mains by
   calculating speed and torque values at diff
   values of armature current
2
3 clc;
4 Ise=[75 100 200 300 400];
5 V=250;
6 Ra=.08;
7 function [Ea]=Eaa(Ise)
8 Ea=V-Ra*Ise;
9 endfunction
10
11 Eav=[121.5 155 250 283 292];
12 n=1200;
13 function [nn]=speed(Ea,Eav)
14 nn=n*Ea/Eav;
15 endfunction
16 function [T]=torque(nn,Ea,Ise)
17 T=(60*Ea*Ise/(2*pi*nn));
18 endfunction
19
20 Ise=75;
21 Ea=Eaa(Ise);
22 Eav=121.5;
23 nn1=speed(Ea,Eav);
24 T1=torque(nn1,Ea,Ise);
25
26 Ise=100;
27 Ea=Eaa(Ise);
28 Eav=155;
29 nn2=speed(Ea,Eav);
30 T2=torque(nn2,Ea,Ise);
31

```

```

32 Ise=200;
33 Ea=Eaa(Ise);
34 Eav=250;
35 nn3=speed(Ea,Eav);
36 T3=torque(nn3,Ea,Ise);
37
38 Ise=300;
39 Ea=Eaa(Ise);
40 Eav=283;
41 nn4=speed(Ea,Eav);
42 T4=torque(nn4,Ea,Ise);
43
44 Ise=400;
45 Ea=Eaa(Ise);
46 Eav=292;
47 nn5=speed(Ea,Eav);
48 T5=torque(nn5,Ea,Ise);
49
50 nn=[nn1 nn2 nn3 nn4 nn5];disp(nn,'speed (rpm)');
51 T=[T1 T2 T3 T4 T5];disp(T,'torque (Nm)');
52
53 plot(T,nn);
54 xlabel('T(Nm)');
55 ylabel('n(rpm)');

```

Scilab code Exa 7.37 to determine the power delivered to the fan torque developed by the motor and calculate external resistance to be added to armature ckt

```

1 //to determine the power delivered to the fan ,torque
   developed by the motor and calculate external
   resistance to be added to armature ckt
2
3 clc;
4 V=220;

```

```

5 Ra=.6;
6 Rse=.4;
7 Ia=30;
8 Ea=V-(Ra+Rse)*Ia;
9 P=Ea*Ia;    disp(P, 'Power(W) ');
10 n=400;
11 w=2*pi*n/60;
12 T=P/w;    disp(T, 'torque(Nm) ');
13
14 nn=200;
15 T1=T*(nn/n)^2;
16 Iaa=Ia*nn/n;
17 w1=2*pi*nn/60;
18 P1=T1*w1;disp(P1, 'power developed when n=200 rpm((W)
    ) ');
19 Ea1=P1/Iaa;
20 Rext=(V-Ea1)/Iaa-(Ra+Rse);disp(Rext, 'external
    resistance(ohm) ');

```

Scilab code Exa 7.38 to determine the starting torque developed

```

1 // to determine the starting torque developed
2 clc;
3 P=180000;
4 V=600;
5 Ia=P/V;
6 Ra=.105;
7 Ea=V-Ia*Ra;
8 n=600;
9 nn=500;
10 Eaa=Ea*nn/n;
11 Iaa=282; //from magnetising curve
12 Iad=Ia-Iaa;
13 Ias=500; //at start
14 k=Iad/Ia^2;

```

```

15 Iae=Ias-Iad*k;
16 Eas=590; //from magnetising curve
17 Ts=Eas*Ias/(2*pi*nn/60); disp(Ts, 'T_start (Nm) ');

```

Scilab code Exa 7.39 to determine speed and mech power

```

1 //to determine speed and mech power
2
3 clc;
4 k=.2*10^-3;
5 Ia=250;
6 Iad=k*Ia^2;
7 Ianet=Ia-Iad;
8 Ea=428; //from magnetising curve
9 V=600;
10 Ra=.105;
11 Eaact=V-Ia*Ra;
12 n=500;
13 nn=n*Eaact/Ea; disp(nn, 'speed (rpm) ');
14 Pmech=Eaact*Ia; disp(Pmech, 'mech power developed (W) ');
    ;
15 T=Pmech/(2*pi*nn/60); disp(T, 'torque (Nm) ');

```

Scilab code Exa 7.40 to calculate the mmf per pole on no load and speed developed

```

1 //to calculate the mmf per pole on no load and speed
    developed
2
3 clc;
4 ATsefl=2400;
5 ATsenl=(3/25)*ATsefl;
6 ATsh=ATsefl;

```

```

7 ATnet=ATsenl+ATsh; disp(ATnet, 'mmf/pole(AT) ');
8 Ea=148; //from magnetising curve
9 V=240;
10 vd=3;
11 Eanl=V-vd;
12 n=850;
13 nnl=n*Eanl/Ea;
14 disp(nnl, 'speed(rpm) ');

```

Scilab code Exa 7.41 to calculate demagnetising ampeare turns em torque starting torque and no of turns of the series field

```

1 //to calculate demagnetising ampeare turns , em
   torque , starting torque and no of turns of the
   series field
2
3 clc;
4 P=10000;
5 Vt=240;
6 Ia=P/Vt;
7 If=.6;
8 Ra=.18;
9 Ri=0.025;
10 Ea=Vt-Ia*(Ra+Ri);
11 n=1218;
12 Eaa=Ea*Vt/Ea;
13 Iff=.548; //from n-If characteristics
14 Ifd=If-Iff;
15 N_s=2000; //shunt field turns
16 ATd=N_s*Ifd; disp(ATd, 'demagnetising ampere turns
   ');
17 T=Ea*Ia/(2*%pi*n/60); disp(T, 'torque(Nm) ');
18 Rf=320;
19 If=Vt/Rf;
20 ATd=165; //given

```

```

21 Ifd=ATd/N_s;
22 Ifnet=If-Ifd;
23 n=1150; //from n-If characteristics
24 //Ea=Ka*phi*w; Ka*phi=k
25 k=Vt/(2*pi*n/60);
26 Iastart=75;
27 Tstart=Iastart*k; disp(Tstart, 'starting torque (Nm) ');
28 n_0=1250;
29 Ea=240;
30 If=.56; //from n-If characteristics
31 n=1200;
32 Rse=.04;
33 R=Rse+Ra+Ri;
34 Eaa=Ea-Ia*R;
35 nn=n*Ea/Eaa;
36 Ifnet=.684; //from n-If characteristics
37 Ifd=Ifnet-If;
38 Nse=N_s*Ifd/Ia; disp(ceil(Nse), 'no of turns of
the series field ');

```

Scilab code Exa 7.42 to determine shunt field current of the motor demagnetising effect of armature rxn determine series field turns per pole speed of motor

```

1 //to determine shunt field current of the motor,
demagnetising effect of armature rxn, determine
series field turns/pole, speed of motor.
2
3 clc;
4 Voc=[180 200 220 240 250];
5 If=[1.18 1.4 1.8 2.4 2.84];
6 plot(If,Voc);
7 xlabel('If(A)');
8 ylabel('Voc(V)');
9 n_0=1350; //at no load

```

```

10 Vt=230;
11 Ea=Vt; //no voltage drop
12 If=1.08; //from occ characteristic
13 disp(If, 'If(A)');
14 n=1350;
15 Ia=56.5;
16 R=.15;
17 Ea=Vt-Ia*R;
18 Ifnet=1.8; //from occ characteristic
19 Ifact=2.08;
20 Ifd=Ifact-Ifnet;
21 N_s=1200; //shunt field turns
22 ATd=N_s*Ifd; disp(ATd, 'ATd');
23
24 Rf=.033;
25 Ea=Vt-Ia*(R+Rf);
26 n=1230;
27 nn=1350;
28 Eaa=Ea*nn/n;
29 Ifnet=2.41; ATnet=Ifnet*N_s;
30 If=1.08;
31 ATsh=If*N_s;
32 ATse=ATnet-ATsh+ATd;
33 Nse=ATse/Ia; disp(floor(Nse), 'series field turns'
);
34 Nse=25;
35 ATse=Nse*Ia;
36 ATnet=ATsh-ATd+ATse;
37 Ifnet=ATnet/N_s;
38 Rs=.025;
39 Eaa=226; //from occ
40 Eact=Vt-Ia*(R+Rs);
41 n=nn*Eact/Eaa; disp(n, 'speed(rpm)');

```

Scilab code Exa 7.43 to find the no of starter sections reqd and resistance of each section

```
1 //to find the no of starter sections reqd ,and
   resistance of each section
2
3 clc;
4 I1=55;
5 I2=35;
6 g=I1/I2;
7 V1=220;
8 R1=V1/I1;
9 Ra=.4;
10 n=log((R1/Ra)-g)+1;
11 disp((n), 'no of starter sections reqd ');
12
13 function [R]=res (re)
14     R=(1/g)*re;
15 endfunction
16 R_1=R1-res(R1);disp(R_1, 'R1(ohm) ');
17 R_2=res(R_1);disp(R_2, 'R2(ohm) ');
```

Scilab code Exa 7.44 to find the lower current limit motor speed at each stud

```
1 //to find the lower current limit , motor speed at
   each stud
2
3 clc;
4 Pop=25*1000;
5 Vt=230;
6 Ra=.12;
7 rf=120;
8 Nf1=2000;
9 Iafl=Pop/Vt;
```

```

10 Iamax=1.5*Iaf1;
11 k=5;
12 I1=Iamax;
13 R1=Vt/I1;
14 r=(R1/Ra)^(1/(k-1));
15 I2=I1/r;
16 function [R]=res (re)
17     R=(1/r)*re;
18 endfunction
19 R_1=R1-res(R1);disp(R_1, 'R1(ohm) ');
20 R_2=res(R_1);disp(R_2, 'R2(ohm) ');
21 R_3=res(R_2);disp(R_3, 'R3(ohm) ');
22 R_4=res(R_3);disp(R_4, 'R4(ohm) ');
23
24 Iaf1=103.7;
25 Ea=Vt-Iaf1*Ra;
26 Ka=Ea/Nf1;
27 function [n]=speed(r)
28     Ea=Vt-I2*r;
29     n=Ea/Ka;
30 endfunction
31 r1=R1;
32 n1=speed(r1);disp(n1, 'n1(rpm) ');
33 r2=r1-R_1;
34 n2=speed(r2);disp(n2, 'n2(rpm) ');
35 r3=r2-R_2;
36 n3=speed(r3);disp(n3, 'n3(rpm) ');
37 r4=r3-R_3;
38 n4=speed(r4);disp(n4, 'n4(rpm) ');

```

Scilab code Exa 7.45 to calculate the ratio of full load speed to no load speed

```

1 //to calculate the ratio of full load speed to no
  load speed

```

```

2
3 clc;
4 V=400;
5 Rf=200;
6 If=V/Rf;
7 Inl=5.6;
8 I_a0=Inl-If;
9 vd=2;      //voltage drop
10 Ra=.18;
11 E_a0=V-Ra*I_a0-vd;
12 Ifl=68.3;
13 Iaf1=Ifl-If;
14 E_af1=V-Ra*Iaf1-vd;
15 e=.03;    //armature rxn weakens the field by 3%
16 k=(E_af1/E_a0)*(1/(1-e));
17 disp(k, 'n_fl/n_nl');

```

Scilab code Exa 7.46 to calculate load torque motor speed and line current

```

1 //to calculate load torque , motor speed and line
   current
2
3 clc;
4 V=250;
5 Rf=41.67;
6 If1=V/Rf;
7 Ia=126;
8 Ia1=Ia-If1;
9 Ra=.03;
10 Ea1=V-Ra*Ia1;
11 n1=1105;    //rpm
12 w1=2*%pi*n1/60;
13 Ka=Ea1/(If1*w1);
14 T=Ka*If1*Ia1;

```

```

15 disp(T, 'torque (Nm) ');
16
17 If2=5;
18 Ia2=Ia1*(If1/If2);
19 I_L2=Ia2+2; disp(I_L2, 'motor current (A) initial ');
20 Ea2=V-Ra*Ia2;
21 w2=Ea2/(Ka*If2);
22
23 If1=6;
24 Voc1=267;
25 n=1200;
26 k1=Voc1/(2*pi*n/60); //k=Ka*phi
27 If1=5;
28 Voc2=250;
29 n=1200;
30 k2=Voc2/(2*pi*n/60); //k=Ka*phi
31 Ia2=Ia1*(k1/k2);
32 I_L2=Ia2+2; disp(I_L2, 'motor current (A) final ');
33 Ea2=V-Ra*Ia2;
34 w2=Ea2/k2;
35 disp(w2, 'motor speed (rad/s) ');

```

Scilab code Exa 7.47 to calculate armature current speed and value of external resistance in field ckt

```

1 //to calculate armature current ,speed and value of
  external resistance in field ckt
2
3 clc;
4 V=250;
5 Ia=5;
6 Ra=.6;
7 n=1000;
8 k=(V-Ia*Ra)/(2*pi*n/60);
9 T=100;

```

```

10 Ia=T/k; disp(Ia, 'armature current (A)');
11 w_m=(V-Ia*Ra)/k;
12 n=(60*w_m)/(2*pi); disp(n, 'speed (rpm)');
13
14 Rf=150;
15 If=V/Rf;
16 kk=k/If;
17 Iaa=44.8;
18 nn=1200;
19 Iff=(V-Iaa*Ra)/(kk*2*pi*nn/60);
20 Rftot=V/Iff;
21 Rfext=Rftot-Rf;
22 disp(Rfext, 'external resistance (ohm)');

```

Scilab code Exa 7.48 to determine speed and torque of the motor

```

1 //to determine speed and torque of the motor
2
3 clc;
4 Ra=0.035;
5 Rf=0.015;
6 V=220;
7 I=200;
8 Ea=V-I*(Ra+Rf);
9 disp('full field winding');
10 n=900;
11 nn=n*Ea/V; disp(nn, 'speed (rpm)');
12 T=(Ea*I/2)/(2*pi*nn/60); disp(T, 'torque (Nm)');
13 disp('field winding reduced to half');
14 Rse=Rf/2;
15 Rtot=Rse+Ra;
16 Ea=V-I*(Rtot);
17 Iff=I/2;
18 V=150; //from magnetisation characteristic
19 nn=n*Ea/V; disp(nn, 'speed (rpm)');

```

```

20 T=(Ea*I)/(2*pi*nn/60); disp(T, 'torque (Nm) ');
21
22 disp('divertor across series field ');
23 Ra=0.03;
24 Rse=.015;
25 Kd=1/((Rse/Ra)+1);
26 Ise=Kd*I;
27 V1=192;
28 I1=150;
29 V2=150;
30 I2=100;
31 v=V2+((V1-V2)/(I1-I2))*(Ise-I2);
32 R=(2/3)*Rse;
33 Ea=V-I*(Ra+R);
34 nn=n*Ea/v; disp(nn, 'speed (rpm) ');
35 T=(Ea*I)/(2*pi*nn/60); disp(T, 'torque (Nm) ');

```

Scilab code Exa 7.50 to determine speed regulation load speed and power regulation and compare power wasted in both cases

```

1 //to determine speed regulation , load speed and
   power regulation and compare power wasted in both
   cases
2
3 clc;
4 V=230;
5 Ra=2;
6 Ia=5;
7 Ea=V-Ia*Ra;
8 n=1250;
9 w=2*pi*n/60;
10 k=Ea/w; //k=Ka*phi
11 Re=15;
12 Ia0=1;
13 Ea=V-Ia0*(Ra+Re);

```

```

14 w0=Ea/k;
15 Ia=5;
16 Ea=V-Ia*(Ra+Re);
17 w=Ea/k;
18 wr=(w0-w)*100/w;
19 disp(wr, '(i) speed regulation (%) ');
20
21 R1=10;
22 R2=15;
23 B=R2/(R1+R2);
24 V_TH=V*B;
25 R_TH=R1*B;
26 Ea=V_TH-Ia0*(R_TH+Ra);
27 w0=Ea/k;
28 Ia=5;
29 Ea=V_TH-Ia*(R_TH+Ra);
30 w=Ea/k;
31 wr=(w0-w)*100/w;
32 disp(wr, '(ii) speed regulation (%) ');
33
34 Pe=Ia^2*Re;
35 disp(Pe, 'power loss by rheostat control (W) ');
36 Ra=2;
37 Ea=98;
38 Va=Ea+Ra*Ia;
39 P2=Va^2/R2;
40 I2=Va/R2;
41 I1=I2+Ia;
42 P1=I1^2*R1;
43 Pe=P1+P2;
44 disp(Pe, 'power loss by shunted armature control (W) ');
    ;

```

Scilab code Exa 7.52 to determine armature current

```

1 //to determine armature current
2
3 clc;
4 n1=1600;
5 Ia1=120;
6 n2=400;
7 Ia2=(n1*Ia1)/n2; //P=K*Ia*n
8 disp(Ia2, 'Ia (A) ');

```

Scilab code Exa 7.54 to find speed and ratio of mech op

```

1 //to find speed and ratio of mech o/p
2
3 clc;
4 V=400;
5 Ra=.25;
6 Ia1=25;
7 Ea1=V-Ra*Ia1;
8 n1=1200;
9 Rr=2.75;
10 Ia2=15;
11 Ea2=V-(Ra+Rr)*Ia2;
12 phi=.7; //phi=(phi(15)/phi(25))
13 n2=(Ea2/Ea1)*n1/phi;
14 disp(n2, 'speed (rpm) ');
15
16 Po2=Ea2*I2;
17 Po1=Ea1*I1;
18 disp(Po2/Po1, 'ratio of mech o/p');
19 Ia=120; //Ia is constant indep of speed
20 disp(Ia, 'Ia (A) ');

```

Scilab code Exa 7.55 to calculate the armature voltage reqd


```

1 //to calculate the armature voltage reqd
2
3 clc;
4 V=500;
5 Ra=.28;
6 Ia1=128;
7 Ea1=V-Ia1*Ra;
8 //(Vt2-.28*Ia2)-->n1/sqrt(2)      (i)
9 //Ea1-->n1      (ii)
10 Vt2=(Ea1/sqrt(2))+(Ia1*Ra);
11 disp(Vt2, 'armature voltage(V)');

```

Scilab code Exa 7.56 to find the range of generator field current motor current and speed

```

1 //to find the range of generator field current ,motor
   current and speed
2
3 clc;
4 If=[0 0.2 0.3 0.4 0.5 0.6 0.7 0.8 1 1.2];
5 Voc=[45 110 148 175 195 212 223 230 241 251];
6 plot(If,Voc);
7 xlabel('If(A)');
8 ylabel('Voc(V)');
9 Ifm=0.8;
10 Eam2=230; //at 1500rpm
11 n_m2=1500;
12 Ra=.5;
13 //n_m=300-1500rpm(range)
14 n_m1=300;
15 Eam1=Eam2*n_m1/n_m2;
16 P_mot=4500;
17 Ia1=P_mot/Eam1;
18 Eag1=Eam1+2*Ra*Ia1;
19 If1=.3-((.1/(148-110))*(148-Eag1));

```

```

20 disp(If1, 'lower limit of current(A)');
21
22 n_m2=1500;
23 Eam2=230;
24 P_mot=4500;
25 Ia2=P_mot/Eam2;
26 Eag2=Eam2+2*Ra*Ia2;
27 If2=1.2-(.2/(241-230)*(251-Eag2));
28 disp(If2, 'upper limit of current(A)');
29
30 Ifg=1;
31 Eag=241;
32 n=1500;
33 Pop=4500;
34 //((241-Eam)/(2*.5))*Eam=4500
35 //after solving
36 //Eam^2-241*Eam+4500=0
37 function [x]=quad(a,b,c)
38     d=sqrt(b^2-4*a*c);
39     x1=(-b+d)/(2*a);
40     x2=(-b-d)/(2*a);
41     if(x1<x2)
42         x=x2;
43     else
44         x=x1;
45     end
46 endfunction
47 Eam=quad(1,-241,4500);
48 Ifm=.2;
49 Eamm=110;
50 n_m=n*Eam/Eamm; disp(n_m, 'speed(rpm)');
51 Ia=(Eag-Eam)/(2*.5); disp(Ia, 'motor current(A)');

```

Scilab code Exa 7.57 to calculate mc eff as a generator and max eff when generating and motoring

```

1 //to calculate m/c eff as a generator and max eff
  when generating and motoring.
2
3 clc;
4 Pop=10*1000;
5 Vt=250;
6 Ra=.8;
7 Rf=275;
8 Ia=3.91;
9 Psh=Vt^2/Rf;
10 Prot=Vt*Ia-Ia^2*Ra;disp(Prot,'rotational loss (W)');
11
12 I1=Pop/Vt;
13 If=Vt/Rf;
14 Ia=I1+If;
15 Ploss=Prot+Psh+Ia^2*Ra;
16 Eff_gen=(1-Ploss/(Ploss+Pop))*100;disp(Eff_gen,'
  generator eff (%)');
17
18 Ia=I1-If;
19 Ploss=Prot+Psh+Ia^2*Ra;
20 Eff_motor=(1-Ploss/(Pop))*100;disp(Eff_motor,'motor
  eff (%)');
21
22 Ia=sqrt((Prot+Psh)/Ra);
23 Ploss_tot=2*(Prot+Psh);disp(Ploss_tot,'total loss (W)
  ');
24
25 I1=Ia-If;
26 Pout=Vt*I1;
27 Eff_gen_max=((1-Ploss_tot/(Ploss_tot+Pout)))*100;
28 disp(Eff_gen_max,'max generator eff (%)');
29
30 I1=Ia+If;
31 Pin=Vt*I1;
32 Eff_motor_max=((1-Ploss_tot/(Pin)))*100;disp(
  Eff_motor_max,'max motor eff (%)');

```

Scilab code Exa 7.59 to determine rotational loss no load armature current and speed and also find speed regulation and to calculate armature current for given em torque

```

1 //to determine rotational loss , no load armature
   current and speed and also find speed regulation
   and to calculate armature current for given em
   torque
2
3 clc;
4 Pout=60*1000;
5 eff=.85;
6 P_L=((1/eff)-1)*Pout;
7 Pin=Pout+P_L;
8 V=600;
9 I_L=Pin/V;
10 Rf=100;
11 If=V/Rf;
12 Ia=I_L-If;
13 Ra=.16;
14 Ea=V-Ia*Ra;
15 n=900;
16 Prot=P_L-Ia^2*Ra-V*If;disp(Prot,'rotational loss (W) '
   );
17
18 Iao=Prot/V;disp(Iao,'no load armature current (A)');
19 Eao=V;
20 n0=n*Eao/Ea;disp(n0,'no load speed (rpm)');
21 reg=(n0-n)*100/n;disp(reg,'speed regulation (%)');
22
23 K=Ea/(2*%pi*n/60); //K=Ka*phi
24 T=600;
25 Ia=T/K;disp(Ia,'reqd armature current (A)');

```

Scilab code Exa 7.60 to determine load torque and motor eff armature current for max motor eff and ots value

```
1 //to determine load torque and motor eff ,armature
   current for max motor eff and ots value
2
3 clc;
4 V=250;
5 Ia=35;
6 Ra=.5;
7 Ea=V-Ia*Ra;
8 Poutg=Ea*Ia;
9 Prot=500;
10 Pout_net=Poutg-Prot;
11 n=1250;
12 w=2*%pi*n/60;
13 T_L=Pout_net/w;disp(T_L, 'load torque (Nm) ');
14
15 Rf=250;
16 If=V/Rf;
17 I_L=If+Ia;
18 Pin=I_L*V;
19 eff=Pout_net*100/Pin;disp(eff, ' efficiency (%) ');
20
21 Pk=Prot+V*If;
22 Ia=sqrt(Pk/Ra);disp(Ia, 'armature current (A) ');
23 Tloss=2*Pk;
24 I_L=If+Ia;
25 Pin=I_L*V;
26 eff_max=1-(Tloss/Pin);disp(eff_max*100, 'max
   efficiency (%) ');
27
28 Ea1=V-Ia*Ra;
29 n1=n*Ea1/Ea;disp(n1, 'speed (rpm) ');
```

```

30 w=2*%pi*n1/60;
31 Poutg=Ea1*Ia;
32 Pout_net=Poutg-Prot;
33 T_L=Pout_net/w;disp(T_L,'load torque(Nm)');

```

Scilab code Exa 7.61 to calculate rotational loss armature resistance eff line current and speed

```

1 //to calculate rotational loss ,armature resistance ,
  eff,line current and speed
2
3 clc;
4 Pshaft=20000;
5 eff=.89;
6 P_L=((1/eff)-1)*Pshaft;
7 Pin=Pshaft+P_L;
8 V=250;
9 I_L=Pin/V;disp(I_L,'line current(A)');
10 Rf=125;
11 If=V/Rf;
12 Ia=I_L-If;
13
14 Ploss=P_L/2;
15 Ra=Ploss/Ia^2;disp(Ra,'armature resistance(ohm)');
16 Psh=V*If;
17 Prot=Ploss-Psh;disp(Prot,'rotational loss(W)');
18 Ea=V-I_L*Ra;
19 n=850;
20 Ia=100;
21
22 Pc=Ia^2*Ra;
23 P_L=Pc+Ploss;
24 Pin=V*I_L;
25 eff=(1-P_L/Pin)*100;
26 Ea1=V-Ia*Ra;

```

```
27 n1=n*Ea1/Ea;disp(n1,'speed (rpm)');
```

Scilab code Exa 7.62 to calculate eff of motor and generator

```
1 //to calculate eff of motor and generator
2
3 clc;
4 Iag=60;
5 Ia=15;
6 Iam=Iag+Ia;
7 Vt=250;
8 Ram=.2;
9 Rag=.2;
10 Pstray=.5*(Vt*Ia-Iam^2*Ram-Iag^2*Rag);
11 Ifm=2;
12 Pinm=Vt*(Iam+Ifm);
13 P_Lm=(Pstray+Vt*Ifm)+Iam^2*Ram;
14 eff_M=1-(P_Lm/Pinm);disp(eff_M*100,'efficiency of
    motor (%)');
15
16 Iag=60;
17 Ifg=2.5;
18 P_Lg=(Pstray+Vt*Ifg)+Iag^2*Rag;
19 Poutg=Vt*Iag;
20 eff_G=1-(P_Lg/(Poutg+P_Lg));disp(eff_G*100,'
    efficiency of generator (%)');
```

Scilab code Exa 7.63 to calculate torque constt value of rotational loss stalled torque and stalled current of motor armature current anad eff motor op and eff

```

1 //to calculaate torque constt,value of rotational
   loss ,stalled torque and stalled current of motor,
   armature current anad eff , motor o/p and eff
2
3 clc;
4 Vt=6;
5 Iao=.0145;
6 n=12125;
7 w=2*%pi*n/60;
8 Ra=4.2;
9 Ea=Vt-Iao*Ra;
10 Km=Ea/w;disp(Km,'torque constt');
11
12 Prot=Ea*Iao;disp(Prot,'rotational loss (W)');
13
14 Ia_stall=Vt/Ra;disp(Ia_stall,'stalled current(A)');
15 Tstall=Km*Ia_stall;disp(Tstall,'stalled torque(Nm)')
   ;
16
17 Poutg=1.6;
18 function [x]=quad(a,b,c)
19     d=sqrt(b^2-4*a*c);
20     x1=(-b+d)/(2*a);
21     x2=(-b-d)/(2*a);
22     if(x1>x2)
23         x=x2;
24     else
25         x=x1;
26     end
27 endfunction
28 //Ea*Ia=1.6;
29 //(Vt-Ra*Ia)*Ia=Poutg;
30 Ia=quad(Ra,-Vt,Poutg);
31 Ea=Vt-Ia*Ra;
32 wo=Ea/Km;
33 Proto=Prot*(w/wo)^2;
34 Pout_net=Poutg-Prot;
35 Pi=Vt*Ia;

```



```
36  eff=Pout_net/Pi;disp( eff*100, ' efficiency (%) ');
37
38  n1=10250;
39  w1=2*pi*n1/60;
40  Km=.004513;
41  Ea1=Km*w1;
42  Ia=(Vt-Ea1)/Ra;
43  Pout_gross=Ea1*Ia;
44  Prot1=Prot*(n1/n);
45  Pout_net=Pout_gross-Prot1;disp(Pout_net, 'o/p power (W
    ) ');
46  Pin=Vt*Ia;
47  eff=Pout_net/Pin;disp( eff*100, ' efficiency (%) ');
```

Chapter 8

Synchronous Machines

Scilab code Exa 8.2 to determine voltage regulation by mmf method

```
1 //to determine voltage regulation by mmf method
2
3 clc;
4 pf=0.85;
5 P=150*10^6;
6 V=13*1000;
7 Iarated=P/(sqrt(3)*pf*V);
8 If=750;
9 Ifocc=810;
10 B=acosd(pf);
11 Ff=sqrt((Ifocc+If*sind(B))^2+(If*cosd(B))^2);
12 Ef=16.3*1000;
13 vr=Ef/V-1;
14 disp(vr*100, 'voltage regulation (%)');
```

Scilab code Exa 8.3 to calculate syn chronous reactance leakage reactance voltage regulation

```

1 //to calculate syn chronous reactance ,leakage
   reactance ,voltage regulation
2
3 clc;
4 If=[50 75 100 125 150 162.5 200 250 300];
5 Voc=[6.2 8.7 10.5 11.6 12.8 13.7 14.2 15.2 15.9];
6 plot(If,Voc);
7 xlabel('If(A)');
8 ylabel('Voc(V)');
9
10 r=10*10^6; //rating
11 V=13000;
12 Ia=r/(sqrt(3)*V);
13 I_SC=688; //corresponding to V
14 Xs=V/(sqrt(3)*I_SC);disp(Xs,'sync reactance(ohm)');
15 V_a=1200;
16 Xl=V_a/(sqrt(3)*Ia);disp(Xl,'leakage reactance(ohm)');
17 Ifar=90;
18 Er=complex(V,sqrt(3)*Ia*Xl);
19 If=185; //corresponding to Er
20 Iff=sqrt((If+Ifar*sind(40.5))^2+(Ifar*cosd(40.5))^2);
21 Effic=15200; //corresponding to Iff
22 vr=(Effic/V-1)*100;disp(vr,'voltage regulation(%)');
23
24 Xsadj=Xs*complex(.8,-.6);j=sqrt(-1);
25 Ef=(V+sqrt(3)*Ia*Xsadj);
26 If=(150/13)*abs(Ef);
27 Vtoc=14800; //corresponding to If
28 vr=(Vtoc/V-1)*100;disp(vr,'voltage regulation(%)');

```

Scilab code Exa 8.6 to calculate the excitation emf

```

1 //to calculate the excitation emf

```

```

2
3 clc;
4 Vt=3300;
5 Xs=18/3;
6 pf=.707;
7 P=800*1000;
8 Ia=P/(sqrt(3)*Vt*pf);
9 a=Ia*Xs/sqrt(2);
10 b=Vt/sqrt(3);
11 Ef=sqrt((a+b)^2+a^2)*sqrt(3);
12 disp(Ef, 'excitation emf(V)(line)');

```

Scilab code Exa 8.7 to compute the max power and torque terminal voltage

```

1 //to compute the max power and torque ,terminal
   voltage
2
3 clc;
4 V=3300;
5 Vt=V/sqrt(3);
6 P=1000*10^3;
7 pf=1;
8 Ia=P/(V*sqrt(3)*pf);
9 Xsm=3.24;
10 j=sqrt(-1);
11 Efm=Vt-j*Ia*Xsm;
12 Efg=abs(Efm);
13 P_emax=3*Vt*Efg/Xsm;disp(P_emax, 'max power(W) ');
14 p=24;
15 f=50;
16 w_sm=(120*f*2*%pi)/(p*60);
17 Tmax=P_emax/w_sm;disp(Tmax, 'torque(Nm) ');
18
19 Xsg=4.55;

```

```

20 Efm=Vt-j*Ia*Xsg;
21 Efmm=abs(Efm);
22 X=Xsm+Xsg;
23 P_emax=3*Efg*Efmm/X;disp(P_emax,'max power (W)');
24 Tmax=P_emax/w_sm;disp(Tmax,'torque (Nm)');
25
26 d=90;
27 Efm=Efg*complex(cosd(0),sind(0));
28 Efg=Efmm*complex(cosd(d),sind(d));
29 Ia=(Efg-Efm)/(j*X);
30 v=j*Ia*Xsm;
31 Vt=Efm+j*Ia*Xsm;
32 disp(abs(Vt)*sqrt(3),'line voltage (V)');

```

Scilab code Exa 8.8 max power supplied power angle d corresponding field current

```

1 //max power supplied , power angle d, corresponding
  field current
2
3 clc;
4 j=sqrt(-1);
5 r=100*10^6; //va
6 V=11000;
7 P=100*10^6;
8 Ef=1; //pu
9 Vth=1; //pu
10 Xs=1.3; //pu
11 Xth=.24; //pu
12 P_emax=Ef*Vth/(Xs+Xth);disp(P_emax,'max power
  delivered (pu)');
13
14 Pe=1;
15 Vt=1;
16 d=asind(Pe*Xth/(Vt*Vth));disp(d,'power angle');

```

```

17 Vt=exp(j*d);
18 Ia=(Vt-Vth)/(j*Xth);
19 Ef=Vth+j*(Xs+Xth)*Ia;
20 Voc=11000;
21 If=256;
22 Ff=19150;
23 Iff=If*Ff/Voc;
24 disp(Iff, 'If(A) ');
25
26 Pe=0:0.01:0.8;
27 Vt=1+(0.24/1.54)*(1.54*Pe-1);
28 plot(Pe,Vt);
29 xlabel('load ');
30 ylabel('Vt(V) ');
31
32 Pe=0:0.01:0.8;
33 dl=asind(0.24*Pe);
34 Ef=1+(1.54/.24)*(exp(j*d1)-1);
35 If=(256/11)*Ef;
36 plot(Pe,abs(If));
37 xlabel('load ');
38 ylabel('excittion current ');

```

Scilab code Exa 8.9 to calculate the generator current and its pf

```

1 //to calculate the generator current and its pf
2
3 clc;
4 j=sqrt(-1);
5 X=.24;
6 r=400; //rating in MVA
7 rr=600; //rating in MVA
8 Pe=r/rr;
9 Vt=1;
10 Vth=1;

```

```

11 dl=asind(Pe*X/(Vt*Vth));
12 Ia=2*sind(dl/2)/X;
13 V=24000;
14 IaB=(rr/3)*10^6/(V/sqrt(3));
15 Iaa=Ia*IaB;disp(Iaa,'generating current(A)');
16 phi=dl/2;
17 pf= cosd(phi);disp(pf,'power factor');
18
19 Pe=1;
20 dl1=asind(Pe*X/(Vt*Vth));
21 Ia=2*sind(dl1/2)/X;
22 Iaa=Ia*IaB;disp(Iaa,'generating current(A)');
23 phi=dl1/2;
24 pf= cosd(phi);disp(pf,'power factor');
25 Ef=Vt+j*Ia*(complex(cosd(-phi),sind(-phi)))*X;
26 Eff=abs(Ef)*V;
27 dl2=atand(imag(Ef)/real(Ef));
28
29 Xth=.24;
30 Pe=abs(Ef)*Vth*sind(dl1+dl2)/(X+Xth);disp(Pe,'Pe(pu)
    ');

```

Scilab code Exa 8.10 to calculate armature resistance sync reactance full load stray load loss Rac Rdc various categories of losses at full load full load eff

```

1 //to calculate armature resistance , sync reactance ,
    full load stray load loss , Rac/Rdc, various
    categories of losses at full load ,full load eff
2
3 clc;
4 r=60*10^3;
5 Psc=3950;
6 Isc=108;
7 Raeff=Psc/(3*Isc^2);disp(Raeff,'effective armature

```

```

        resistance (ohm) ');
8  V=400;
9  Ifoc=2.85;
10 Ifsc=1.21;
11 I_SC=Isc*Ifoc/Ifsc;
12 Zs=(V/sqrt(3))/I_SC;
13 Xs=sqrt(Zs^2-Raeff^2); disp(Xs, 'sync reactance (ohm) ')
    ;
14
15 t1=25;
16 t2=75;
17 Rdc=0.075;
18 Radc=Rdc*((273+t2)/(273+t1));
19 Iarated=r/(sqrt(3)*V);
20 Psc=Psc*(Iarated/Isc)^2;
21 P=3*Iarated^2*Radc; disp(P, 'armature loss (W) ');
22 loss=Psc-P; disp(loss, 'loss (W) ');
23
24 a=Raeff/Radc; disp(a, 'Rac/Rdc ');
25
26 Pwf=900; disp(Pwf, 'windage and friction loss (W) ');
27 tloss=2440;
28 closs=tloss-Pwf; disp(closs, 'core loss (W) ');
29 If=3.1;
30 Rf=110;
31 Pcu=If^2*Rf; disp(Pcu, 'field cu loss (W) ');
32 disp(loss, 'stray load loss (W) ');
33 b=loss+Pcu+closs+Pwf+P;
34 disp(b, 'total loss (W) ');
35
36 pf=0.8;
37 op=r*pf;
38 ip=op+b;
39 eff=op/ip;
40 disp(eff, 'efficiency ');

```

Scilab code Exa 8.11 to calculate net power op eff line current and pf

```
1 //to calculate net power op,eff,line current and pf
2
3 clc;
4 j=sqrt(-1);
5 Zs=(1/3)*(.3+j*6);
6 phi=atand(imag(Zs)/real(Zs));
7 Vt=400/sqrt(3);
8 Ef=600/sqrt(3);
9 a=sqrt(Vt^2+Ef^2-2*Vt*Ef*cosd(phi));
10 Ia=a/abs(Zs);disp(Ia,'line current(A)');
11 B=acosd((Vt^2+a^2-Ef^2)/(2*Vt*a));
12
13 phi=90-(90-atand(imag(Zs)/real(Zs)))-B;disp(cosd(phi
    ),'pf');
14 Pein=Vt*Ia*cosd(phi);
15 Ra=.1;
16 b=Ia^2*Ra;
17 loss=2400;
18 Pmout=Pein-loss/3-b;disp(Pmout,'net power op(W)');
19 eff=Pmout/Pein;
20 disp(eff*100,'efficiency(%)');
```

Scilab code Exa 8.12 to find pf

```
1 //to find pf
2
3 clc;
4 j=sqrt(-1);
5 Zs=.8+j*5;
6 Vt=3300/sqrt(3);
```

```

7 Pein=800*10^3/3;      //per ph
8 pf=.8;
9 Qe=-Pein*tand(acosd(pf));
10 //a=Ef*sind(dl-a);
11 //b=Ef*cosd(dl-a);
12 a=((abs(Zs)/Vt)*(Pein-real(Zs)*(Vt/abs(Zs))^2));
13 b=((abs(Zs)/Vt)*(-Qe+imag(Zs)*(Vt/abs(Zs))^2));
14
15 Ef=sqrt(a^2+b^2);
16
17 Pein=(1200/3)*1000;
18 a=asind((abs(Zs)/(Vt*Ef))*(Pein-pf*(Vt/abs(Zs))^2));
19 Qe=imag(Zs)*(Vt/abs(Zs))^2-Ef*Vt*cosd(a)/abs(Zs);
20 pf=cosd(atan(Qe/Pein));
21 disp(pf, 'pf');

```

Scilab code Exa 8.13 to determine excitation emf torque angle stator current pf max power kVAR delivered

```

1 //to determine excitation emf, torque angle, stator
   current, pf, max power, kVAR delivered
2
3 clc;
4 j=sqrt(-1);
5 P=10000;
6 V=400;
7 Ia=P/(sqrt(3)*V);
8 pf=.8;
9 phi=acosd(pf);
10 Iaa=Ia*complex(cosd(-phi),sind(-phi));
11 Vt=V/sqrt(3);
12 X=16;
13 Ef=Vt+j*X*Iaa;
14 disp(abs(Ef), 'excitation emf(V)');
15 dl=atan(imag(Ef)/real(Ef));

```

```

16 disp(dl, 'torque angle ');
17
18 Pe=P*pf;
19 Eeff=abs(Ef)*1.2;
20 dl=(Pe/3)*X/(Eeff*Vt);
21 ta=asind(dl);
22 disp(ta, 'torque angle ');
23 Ia=(Eeff*complex(cosd(ta),sind(ta))-Vt)/(j*X);
24 disp(abs(Ia), 'stator current (A) ');
25 disp(cosd(-atand(imag(Ia)/real(Ia))), 'pf ');
26
27 Ef=413;
28 Pemax=Ef*Vt/X;
29 Ia=(Ef*complex(cosd(90),sind(90))-Vt)/(j*X);
30 disp(abs(Ia), 'stator current (A) ');
31 disp(cosd(-atand(imag(Ia)/real(Ia))), 'pf ');
32
33 Qe=(imag(Ia)/real(Ia))*Pe;disp(Qe, 'kVar delivered ');

```

Scilab code Exa 8.14 to calculate armature current pf power angle power shaft torques kVar

```

1 //to calculate armature current , pf ,power angle ,
   power , shaft torques ,kVar
2
3 clc;
4 j=sqrt(-1);
5 P=8000;
6 Prot=500;
7 Pmg=P+Prot;
8 Pein=Pmg;
9 Ef=750/sqrt(3);
10 Vt=231;
11 Xs=16;
12 dl=asind(Xs*(Pein/3)/(Ef*Vt));

```

```

13 Eff=Ef*complex(cosd(-dl),sind(-dl));
14 Ia=(Vt-Eff)/(j*Xs);
15 disp(abs(Ia),'armature current(A)');
16 disp(cosd(atan(imag(Ia)/real(Ia))), 'pf');
17 f=50;
18 p=4;
19 n_s=120*f/p;
20 w_s=2*%pi*n_s/60;
21 T=Pein/w_s;disp(T,'torque developed(Nm)');
22 T_s=P/w_s;disp(T_s,'shaft torques(Nm)');
23
24 Ef=600/sqrt(3);
25 Ia=(Vt-Eff)/(j*Xs);
26 rr=3*Vt*Ia/1000;
27 disp(rr,'kVar rating');
28 c=(abs(Ia)/Vt)/(2*%pi*f);
29 disp(-c,'capicator rating(F)');
30
31 Ef=300/sqrt(3);
32 Ia=(Vt-Eff)/(j*Xs);
33 rr=3*Vt*Ia/1000;
34 disp(-rr,'kVar rating');
35 L=(Vt/abs(rr))/(2*%pi*f);
36 disp(L,'inductor rating(H)');
37
38 Ia=j*2000/Vt;
39 Ef=Vt-j*Ia*Xs;
40 disp(abs(Ef)*sqrt(3),'excitation(V)');

```

Scilab code Exa 8.15 find the excitation emf mech power developed pf

```

1 //find the excitation emf,mech power developed ,pf
2
3 clc;
4 j=sqrt(-1);

```

```

5 V=6600;
6 Vt=V/sqrt(3);
7 r=4*10^6;
8 Ia=r/(sqrt(3)*V);
9 Xs=4.8;
10 //Vt^2+Ef^2-2*Vt*Efcosd(dl)=(Ia*Xs)^2
11 //after solving
12 //Ef^2-7.16*Ef+11.69=0;
13 function [x1,x2]=quad(a,b,c)
14     d=sqrt(b^2-4*a*c);
15     x1=(-b+d)/(2*a);
16     x2=(-b-d)/(2*a);
17 endfunction
18 [Ef1 Ef2]=quad(1,-7.16,11.69);
19 dl=20;
20 disp(Ef1,'excitation(kV)');
21 Pm=3*3.81*Ef1*sind(dl)/Xs;disp(Pm,'power developed(
    MW)');
22 pf1=Pm*10^6/(sqrt(3)*V*Ia);disp(pf1,'pf1');
23
24 disp(Ef2,'excitation(kV)');
25 Pm=3*3.81*Ef2*sind(dl)/Xs;disp(Pm,'power developed(
    MW)');
26 pf2=Pm*10^6/(sqrt(3)*V*Ia);disp(pf2,'pf2');

```

Scilab code Exa 8.16 to find power angle field current

```

1 //to find power angle ,field current
2
3 clc;
4 j=sqrt(-1);
5 V=400;
6 Vt=V/sqrt(3);
7 pf=1;
8 Ia=50;

```

```

9  Xs=1.3;
10 Ef=Vt-j*Ia*Xs;
11 disp(-atand(imag(Ef)/real(Ef)), 'power angle ');
12
13 Pm=Vt*Ia*pf;
14 pff=.8;
15 Ia=Pm/(Vt*pff);
16 ang=acosd(pff);
17 Eff=sqrt((Vt*cosd(ang))^2+(Vt*sind(ang)+Ia*Xs)^2);
18 If=.9;
19 Iff=If*Eff/abs(Ef);
20 disp(Iff, 'field current (A) ');

```

Scilab code Exa 8.17 to calculate motor eff excitation emf and power angle max power op corresponding net op

```

1 //to calculate motor eff, excitation emf and power
   angle, max power op, corresponding net op
2
3 clc;
4 j=sqrt(-1);
5 Sop=40*1000;
6 Vt=600;
7 Ra=.8;
8 Xs=8;
9
10 Pst=2000;
11 Pmnet=30*1000;
12 Pm_dev=Pst+Pmnet;
13 Ia=Sop/(sqrt(3)*Vt);
14 Poh=3*Ia^2*Ra;
15 Pin=Pm_dev+Poh;
16 eff=(1-(Poh+Pst)/Pin)*100; disp(eff, 'motor eff (%) ');
17
18 cos_phi=Pin/(sqrt(3)*Vt*Ia);

```

```

19 phi=acosd(cos_phi);
20 Ia=Ia*(cosd(phi)+j*sind(phi));
21 Vt=Vt/sqrt(3);
22 Za=Ra+Xs*j;
23 Ef=Vt-Ia*Za;
24 Ef_line=Ef*sqrt(3);disp(Ef_line,'excitation emf(V)')
    ;
25 delta=atand(imag(Ef)/real(Ef));disp(delta,'power
    angle(deg)');
26 IaRa=abs(Ia)*Ra;
27 IaXs=abs(Ia)*Xs;
28 AD=Vt*cosd(phi)-IaRa;
29 CD=Vt*sind(phi)+abs(Ia)*Xs;
30 Ef_mag=sqrt((abs(AD))^2+(abs(CD))^2);
31
32 Pm_out_gross=-((abs(Ef_mag))^2*Ra/(abs(Za))^2)+(Vt*
    abs(Ef_mag)/abs(Za));
33 disp(Pm_out_gross,'max power op(W)');
34 power_angle=atand(imag(Za)/real(Za));
35 disp(power_angle,'power angle(deg)');

```

Scilab code Exa 8.18 find the change in the power angle

```

1 //find the change in the power angle;
2
3 clc;
4 Pe=4000;
5 V=400';
6 pf=.8;d1=acosd(pf);
7 Ia=Pe/(sqrt(3)*V*pf);
8 Vt=V/sqrt(3);
9 Xs=25;
10 Ef=Vt+j*Ia*complex(cosd(-d1),sind(-d1))*Xs;
11 a=atand(imag(Ef)/real(Ef));
12

```

```

13 dl=asind((Pe/3)*Xs/(Vt*abs(Ef)));
14 ang=dl+a;
15 disp(ang,'change in power angle(deg)');

```

Scilab code Exa 8.19 to find no of poles MVA rating prime mover rating and op torque

```

1 //to find no of poles,MVA rating , prime mover rating
  and op torque
2
3 clc;
4 f=50;
5 n_s=100;
6 P=120*f/n_s;disp(P,'no of poles');
7 r=110; //MVA rating
8 pf=.8;
9 rr=r/pf;disp(rr,'MVA rating');
10 eff=.971;
11 rt=r/eff;disp(rt,'prime mover rating(MW)');
12 T_PM=rt*1000*60/(2*pi*n_s);disp(T_PM,'op torque(Nm)
  ');

```

Scilab code Exa 8.20 to determine the magnitude of Eg Em and min value of Em to remain mc in synchronism

```

1 //to determine the magnitude of Eg,Em and min value
  of Em to remain m/c in synchronism
2
3 clc;
4 j=sqrt(-1);
5 V_base=400;
6 kva_base=10;
7 MW_base=10;

```



```

8 Pm=8/10;
9 Vt=1;
10 pf=.8;
11 Ia=Pm/(Vt*pf);
12 Ia=Ia*complex(pf,sind(acosd(pf)));
13 Em=Vt-j*Ia*pf;
14 Emm=abs(Em)*V_base;
15 dl_m=atand(imag(Em)/real(Em));disp(dl_m,'dl_m(deg)')
    ;
16 Eg=Vt+j*Ia*(pf+.2);
17 Egg=abs(Eg)*V_base;
18 dl_g=atand(imag(Eg)/real(Eg));disp(dl_g,'dl_g(deg)')
    ;
19 dl_gm=dl_g-dl_m;disp(dl_gm,'relative angle(deg)');
20
21 dl_m=90;
22 Emmin=.8*.8/1;
23 disp(Emmin*V_base,'min value of Em(V)');

```

Scilab code Exa 8.21 to determine armature current pf power angle mech power developed and eff

```

1 //to determine armature current ,pf ,power angle ,mech
    power developed and eff
2
3 clc;
4 j=sqrt(-1);
5 Vt=3300/sqrt(3);
6 Ef=4270/sqrt(3);
7 Pein=750000/3;
8 Zs=.8+j*5.5;
9 a=90-atand(imag(Zs)/real(Zs));
10 dl=asind((Pein-real(Zs)*(Vt/abs(Zs))^2)/((Vt*Ef/abs(
    Zs))))+a;
11 disp(dl,'power angle(deg)');

```

```

12 b=Vt-Ef*complex(cosd(-dl),sind(-dl));
13 Ia=b/Zs;
14 disp(abs(Ia),'armature current(A)');
15 phi=atand(imag(Ia)/real(Ia));
16 disp(cosd(phi),'pf');
17 Ef=sqrt(3)*Ef*complex(cosd(-dl),sind(-dl));
18 Pm=sqrt(3)*abs(Ef)*abs(Ia)*cosd(dl+phi);
19 disp(Pm,'mech power developed(W)');
20 Pst=30000;
21 Pmnet=Pm-Pst;
22 eff=Pmnet/(Pein*3);disp(eff*100,'efficiency(%)');

```

Scilab code Exa 8.22 to find armature current power factor and power ip

```

1 //to find armature current ,power factor and power ip
2
3 clc;
4 j=sqrt(-1);
5 Vt=3300/sqrt(3);
6 Ef=4270/sqrt(3);
7 Pein=600000/3;
8 Zs=.8+j*5.5;
9 a=90-atand(imag(Zs)/real(Zs));
10 dl=asind((Pein+real(Zs)*(Ef/abs(Zs))^2)/((Vt*Ef/abs(
    Zs))))-a;
11 disp(dl,'power angle');
12 b=Vt-Ef*complex(cosd(-dl),sind(-dl));
13 Ia=b/Zs;
14 disp(abs(Ia),'armature current(A)');
15 phi=atand(imag(Ia)/real(Ia));
16 disp(cosd(phi),'pf');
17
18 Peinn=sqrt(3)*3300*abs(Ia)*cosd(phi);
19 disp(Peinn,'power ip(W)');
20 loss=Peinn-Pein*3;

```

```
21 disp(loss, 'ohmic loss (W)');
```

Scilab code Exa 8.23 to calculate pu adjusted sync reactance feild reactance reactive power op rotor power angle

```
1 //to calculate pu adjusted sync reactance , feild
  reactance , reactive power op, rotor power angle
2
3 clc;
4 j=sqrt(-1);
5 r=10*10^6;
6 V_SC=13.8*10^3;
7 Ia=r/(sqrt(3)*V_SC);
8 If=226;
9
10 Iff=842;
11 I_SC=Ia*Iff/If;
12 Xsadj=(V_SC/sqrt(3))/I_SC;
13
14 va_b=10*10^6;
15 v_b=13800;
16 Xspu=Xsadj*va_b/v_b^2;disp(Xspu, 'Xs(pu)');
17 Ra=.75;
18 Zs=Ra+j*Xsadj;
19 a=90-atand(imag(Zs)/real(Zs));
20
21 pf=.9;
22 phi=acosd(pf);
23 Pe=8.75*10^6;
24 Qe=Pe*tand(phi);
25 Vt=V_SC/sqrt(3);
26 Ia=(Pe/3)/(Vt*pf);
27 Ef=Vt+abs(Ia)*abs(Zs)*complex(cosd(90-a-phi),sind
  (90-a-phi));
28 Ef=abs(Ef)*sqrt(3);
```

```

29 If=Iff*Ef/V_SC;disp(If,'field current(A)');
30 loss=3*abs(Ia)^2*Ra;
31 Pmin=Pe+loss;disp(Pmin,'reactive power op(W)');
32
33 If=842;
34 Voc=7968;
35 Pmin=Pmin/3;
36 dl=asind((Pmin-real(Zs)*(Voc/abs(Zs))^2)/((Voc^2/abs
      (Zs))))+a;
37 disp(dl,'power angle');
38 Q=-((Voc/abs(Zs))^2*imag(Zs)+Voc^2*cosd(dl+a)/abs(Zs)
      );
39 disp(Q,'reactive power op(VAR)');

```

Scilab code Exa 8.25 to calculate the excitation emf power angle

```

1 //to calculate the excitation emf,power angle
2
3 clc;
4 Vt=1;
5 Ia=1;
6 pf=.8;phi=acosd(pf);
7 Iaa=Ia*complex(cosd(-phi),sind(-phi));
8 Xq=.5;
9 j=sqrt(-1);
10 Ef=Vt+j*Iaa*Xq;
11
12 dl=17.1;
13 w=phi+dl;
14 Id=Ia*sind(w);
15 Xd=.8;
16 CD=Id*(Xd-Xq);
17 Eff=abs(Ef)+CD;
18 Ef=Vt+j*Iaa*Xd;
19 disp(abs(Ef),'excitation emf(V)');

```

```
20 disp(atan(imag(Ef)/real(Ef)), 'power angle ');
```

Scilab code Exa 8.26 calculate excitation emf

```
1 //calculate excitation emf
2
3 clc;
4 V=3300;
5 Vt=V/sqrt(3);
6 pf=1;
7 phi=acosd(pf);
8 P=1500*1000;
9 Ia=P/(sqrt(3)*V*pf);
10 Xq=2.88;
11 Xd=4.01;
12 w=atan((Vt*0-Ia*Xq)/Vt);
13 dl=phi-w;
14 Id=Ia*sind(w);
15 Iq=Ia*cosd(w);
16 Ef=Vt*cosd(dl)-Id*Xd;
17 disp(Ef*sqrt(3), 'excitation emf(line)(V)');
```

Scilab code Exa 8.27 to calculate generator terminal voltage excitation emf power angle

```
1 //to calculate generator terminal voltage ,excitation
   emf, power angle
2
3 clc;
4 Xd=1.48;
5 Xq=1.24;
6 Xe=.1;
7 Xdt=Xd+Xe;
```

```

8 Xqt=Xq+Xe;
9
10 MVA=1;
11 Vb=1;
12 pf=.9;
13 phi=acosd(pf);
14 //(Vt*cosd(phi))^2+(Vt*sind(phi)+Ia*Xe)^2=Vb^2;
15 //after solving
16 //Vt^2-.0870*Vt-.99=0;
17 function [x]=quad(a,b,c)
18     d=sqrt(b^2-4*a*c);
19     x1=(-b+d)/(2*a);
20     x2=(-b-d)/(2*a);
21     if(x1<Vb)
22         x=x2;
23     else
24         x=x1;
25     end
26 endfunction
27 Vt=quad(1,-.0870,-.99);disp(Vt,'terminal voltage(V)');
28 //after solving
29 phi=20;
30
31 j=sqrt(-1);
32 Ia=1;
33 Iaa=Ia*complex(cosd(-phi),sind(-phi));
34 Ef=Vb+j*Iaa*Xqt;
35 Eff=abs(Ef);
36 dl=atand(imag(Ef)/real(Ef));disp(dl,'power angle');
37 w=dl+phi;
38 Id=Ia*sind(w);
39 Ef=Ef+Id*(Xdt-Xqt);
40 disp(abs(Ef),'excitation emf(V)');

```

Scilab code Exa 8.28 to find max pu power pu armature current pu reactive power

```
1 //to find max pu power, pu armature current, pu
   reactive power
2
3 clc;
4 Vt=1;
5 Xd=1.02;
6 Xq=.68;
7 Pmmax=Vt^2*(Xd-Xq)/(2*Xd*Xq);disp(Pmmax, 'max pu
   power ');
8 dl=.5*asind(Pmmax/(Vt^2*(Xd-Xq)/(2*Xd*Xq)));
9
10 Id=Vt*cosd(dl)/Xd;
11 Iq=Vt*cosd(dl)/Xq;
12 Ia=sqrt(Id^2+Iq^2);disp(Ia, 'armature current (pu) ');
13
14 Qe=Id*Vt*cosd(dl)+Iq*Vt*sind(dl);disp(Qe, 'reactive
   power (pu) ');
15
16 pf=cosd(atan(Qe/Pmmax));disp(pf, 'pf');
```

Scilab code Exa 8.29 to calculate power angle excitation emf field current

```
1 //to calculate power angle, excitation emf, field
   current
2
3 clc;
4 j=sqrt(-1);
5 MVA_b=300;
6 kV_b=22;
7
8 Pe=250/MVA_b;
9 pf=.85;
```

```

10 Vt=1;
11 Ia=Pe/(pf*Vt);
12 phi=acosd(pf);
13 Iaa=Ia*complex(cosd(-phi),sind(-phi));
14 Xq=1.16;
15 Xd=1.93;
16 Ef=Vt+j*Iaa*Xq;
17 dl=atand(imag(Ef)/real(Ef));disp(dl,'power angle');
18 w=phi+dl;
19 Id=abs(Iaa)*sind(w);
20 Ef=abs(Ef)+Id*(Xd-Xq);
21 disp(Ef*kV_b,'excitation emf(V)');
22
23 If=338;
24 If=If*Ef/1;disp(If,'field current(A)');

```

Scilab code Exa 8.30 to find max andmin pu field excitation

```

1 //to find max andmin pu field excitation
2
3 clc;
4 Xd=.71;
5 Xq=.58;
6 Xe=.08;
7 Xdt=Xd+Xe;
8 Xqt=Xq+Xe;
9
10 Pe=0;Vt=1;
11 dl=0;
12 phi=90;
13 Ia=1;
14 Iq=0;
15 Id=Ia;
16
17 Ef=Vt+Id*Xdt;

```



```

18 Ifmax=Ef;disp(Ifmax,'max field excitation(A)');
19
20
21 Ef=Vt-Id*Xdt;
22 Ifmin=Ef;disp(Ifmin,'min field excitation(A)');

```

Scilab code Exa 8.31 to calculate synchronising power and torque coeff per deg mech shift

```

1 //to calculate synchronising power and torque coeff/
  deg mech shift
2
3 clc;
4 V=11000;
5 Vt=V/sqrt(3);
6 P=6*10^6;
7 Ia=P/(sqrt(3)*V);
8 ohm_b=Vt/Ia;
9 Xs=.5;
10 Xss=Xs*ohm_b;
11
12 f=50;
13 P=8;
14 n_s=(120*f/P)*(2*pi/60);
15
16 Ef=Vt;
17 dl=0;
18 Psyn=(pi/15)*(Ef*Vt/Xss)*cosd(dl);disp(Psyn,'
  synchronising power(W)');
19 Tsyn=Psyn/n_s;disp(Tsyn,'torque coeff(Nm)');
20
21 pf=.8;
22 phi=acosd(pf);
23 Ef=Vt+j*Ia*Xss*complex(cosd(-phi),sind(-phi));
24 dl=atand(imag(Ef)/real(Ef));

```

```

25 Psyn=(%pi/15)*(abs(Ef)*Vt/Xss)*cosd(dl);disp(Psyn,'
    synchronising power(W)');
26 Tsyn=Psyn/n_s;disp(Tsyn,'torque coeff(Nm)');

```

Scilab code Exa 8.32 to calculate synchronising power per elec deg pu sync torque per mech deg

```

1 //to calculate synchronising power/elec deg,pu sync
    torque/mech deg
2
3 clc;
4 j=sqrt(-1);
5 Xd=.8;
6 Xq=.5;
7 Vt=1;
8 pf=.8;
9 phi=acosd(pf);
10 Ia=1*complex(cosd(phi),sind(phi));
11
12 Ef=Vt-j*Ia*Xq;
13 Eff=abs(Ef);
14 dl=atand(imag(Ef)/real(Ef));
15 w=-dl+phi;
16 Id=abs(Ia)*sind(w);
17 Ef=Eff+Id*(Xd-Xq);
18
19 Psyn=abs(Ef)*Vt*cosd(dl)/Xd+Vt^2*((Xd-Xq)/(Xd*Xq))*
    cosd(2*dl);
20 disp(Psyn*(%pi/180),'synchronising power(pu)/elec deg
    ');
21 f=50;
22 P=12;
23 n_s=(120*f/P)*(2*%pi/60);
24 Tsyn=Psyn/n_s;disp(Tsyn,'pu sync torque/mech deg');

```

Scilab code Exa 8.33 to calculate sync current power and torque

```
1 //to calculate sync current , power and torque
2
3 clc;
4 j=sqrt(-1);
5 P=12000;
6 V=400;
7 pf=.8;
8 Ia=P/(sqrt(3)*V*pf);
9 phi=acosd(pf);
10 Vt=V/sqrt(3);
11 Xs=2.5;
12 Ef=Vt-j*Ia*complex(cosd(phi),sind(phi))*Xs;
13 tandl=4;
14 Es=2*abs(Ef)*sind(tandl/2);
15 Is=Es/Xs;disp(Is,'sync current(A)');
16 dl=atand(imag(Ef)/real(Ef));
17 Ps=3*Vt*Is*cosd(dl+tandl/2);disp(Ps,'power(W)');
18 n_s=25*%pi;
19 T_s=Ps/n_s;
20 disp(T_s,'torque(Nm)');
```

Scilab code Exa 8.34 to calculate value of syncpower

```
1 //to calculate value of syncpower
2
3 clc;
4 V=6600;
5 E=V/sqrt(3);
6
7 P=12;
```

```

8 d1=1*P/2;
9
10 r=20000*10^3;
11 I=r/(sqrt(3)*V);
12 Xs=1.65;
13
14 Psy=d1*(%pi/180)*E^2/Xs;
15 disp(Psy, 'sync power(W) ');

```

Scilab code Exa 8.35 to determine op current and pf

```

1 //to determine op current and pf
2
3 clc;
4 P1=400*10^3;
5 P2=400*10^3;
6 P3=300*10^3;
7 P4=800*10^3;
8 pf1=1;
9 pf2=.85;
10 pf3=.8;
11 pf4=.7;
12 phi1=acosd(pf1);
13 phi2=acosd(pf2);
14 phi3=acosd(pf3);
15 phi4=acosd(pf4);
16 P=P1+P2+P3+P4;
17 Q1=P1*tand(phi1);
18 Q2=P2*tand(phi2);
19 Q3=P3*tand(phi3);
20 Q4=P4*tand(phi4);
21 Q=Q1+Q2+Q3+Q4;
22
23 I=100;
24 pf=.9;

```

```

25 V=6600;
26 P_A=sqrt(3)*V*I*pf;
27 P_B=P-P_A;
28 Q_A=P_A*tand(acosd(pf));
29 Q_B=Q-Q_A;
30 phi=atand(Q_B/P_B);
31 pf=cosd(phi);disp(pf,'pf');
32 I_B=P_B/(sqrt(3)*pf*V);disp(I_B,'op current (A)');

```

Scilab code Exa 8.36 to find the pf and current supplied by the mc

```

1 //to find the pf and current supplied by the m/c
2
3 clc;
4 P=50000;
5 pf=.8;
6 phi=acosd(pf);
7 Q=P*tand(phi);
8 P1=P/2;
9 pf1=.9;
10 phi1=acosd(pf1);
11 Q1=P1*tand(phi1);
12 P2=P/2;
13 Q2=Q-Q1;
14 phi2=atand(Q2/P2);
15 pf=cosd(phi2);disp(pf,'pf');
16 V_L=400;
17 I2=P2/(sqrt(3)*V_L*pf);disp(I2,'current supplied by
    m/c (A)');

```

Scilab code Exa 8.37 to find initial current current at the end of 2 cycles and at the end of 10s

```

1 //to find initial current ,current at the end of 2
   cycles and at the end of 10s
2
3 clc;
4 Ef=1;
5 Xd2=.2;
6 I2=Ef/Xd2;
7 r=100*106;
8 V=22000;
9 I_b=r/(sqrt(3)*V);
10 I2=I2*I_b;disp(I2,'initial current (A) ');
11
12 Xd1=.3;
13 I1=Ef/Xd1;
14 Xd=1;
15 I=Ef/Xd;
16
17 tau_dw=0.03;
18 tau_f=1;
19
20 function [a]=I_sc(t)
21     a=(I2-I1)*exp(-t/tau_dw)+(I1-I)*exp(-t/tau_f)+1;
22 endfunction
23 //2 cycles=0.04s
24 disp(I_sc(.2867)*I_b,'current at the end of 2 cycles
   (A) ');
25 disp(I_sc(10)*I_b,'current at the end of 10s(A) ');

```

Scilab code Exa 8.39 to calculate sync reactance voltage regulation torque angle ele power developed voltage and kva rating

```

1 //to calculate sync reactance ,voltage regulation ,
   torque angle , ele power developed , voltage and
   kva rating
2

```

```

3  clc;
4  r=1000*10^3;
5  V=6600;
6  Ia=r/(sqrt(3)*V);
7  pf=.75;
8  phi=-acosd(pf);
9  Vt=V/sqrt(3);
10 Ef=11400/sqrt(3);
11 //Ef*complex(cosd(dl),sind(dl))=Vt+j*Xs*Ia*complex(
    cosd(phi),sind(phi))
12 //after solving
13 //6.58*cosd(dl)=3.81+.058*Xs;
14 //6.58*sind(dl)=.0656*Xs;
15 //so after solving
16 //cosd(dl-phi)=.434;
17 dl=acosd(.434)+phi;
18
19 Xs=Ef*sind(dl)/65.6;disp(Xs,'sync reactance(ohm)');
20 vr=Ef*sqrt(3)/V-1;disp(vr,'voltage regulation(%)');
21 disp(dl,'torque angle(deg)');
22 P=3*Ef*Ia*cosd(dl-phi);disp(P,'ele power developed(W
    )');
23
24 volr=V/sqrt(3);disp(volr,'voltage rating(V)');
25 ir=Ia*sqrt(3);disp(ir,'current rating(A)');
26 r=sqrt(3)*volr*ir;disp(r,'VA rating');

```

Scilab code Exa 8.40 to determine mc and pf

```

1 //to determine m/c and pf
2
3 clc;
4 j=sqrt(-1);
5 P=230*10^6;
6 V=22000;

```

```

7 pf=1;
8 Ia=P/(sqrt(3)*V*pf);
9 Vt=V/sqrt(3);
10 Xs=1.2;
11 Ef=Vt+j*Xs*Ia;
12 //if Ef is inc by 30%
13 Ef=1.3*abs(Ef);
14
15 dl=asind((P/3)*Xs/(Ef*Vt));
16 Ia=((Ef*complex(cosd(dl),sind(dl)))-Vt)/(j*Xs);
17 disp(abs(Ia),'m/c current(A)');
18 disp(cosd(atan2(imag(Ia),real(Ia))), 'pf');
19
20 P=275*10^6;
21 dl=asind((P/3)*Xs/(Ef*Vt));
22 Ia=((Ef*complex(cosd(dl),sind(dl)))-Vt)/(j*Xs);
23 disp(abs(Ia),'m/c current(A)');
24 disp(cosd(atan2(imag(Ia),real(Ia))), 'pf');

```

Scilab code Exa 8.41 to calculate excitation emf torque angle eff shaft op

```

1 //to calculate excitation emf,torque angle , eff ,
   shaft op
2
3 clc;
4 j=sqrt(-1);
5 Va=.8;
6 Xa=5.5;
7 Xs=Va+j*Xa;
8 V=3300;
9 Ia=160;
10 pf=.8;
11 loss=30000;
12 phi=acosd(pf);
13 Ef=V/sqrt(3)-Xs*Ia*complex(cosd(-phi),sind(-phi));

```



```

    disp(abs(Ef), 'excitation emf(V)');
14 dl=atand(imag(Ef)/real(Ef)); disp(dl, 'torque angle(
    deg)');
15 P_mech=3*abs(Ef)*Ia*cosd(-phi-dl);
16 op_sft=P_mech-loss; disp(op_sft, 'shaft op(W)');
17 Pip=sqrt(3)*V*Ia*pf;
18 eff=op_sft/Pip; disp(eff*100, 'efficiency(%)');

```

Scilab code Exa 8.42 to caculate generator current pf real power excitation emf

```

1 //to caculate generator current ,pf , real power ,
    ecitation emf
2
3 clc;
4 r=500*10^6;
5 V=22000;
6 Ia=r/(sqrt(3)*V); disp(Ia, 'generator current(A)');
7 Vt=V/sqrt(3);
8 Zb=Vt/Ia;
9 MVA_b=500;
10 MW_b=500;
11 Xsg=1.57;
12 Xb=.4;
13 Xb=Xb/Zb;
14
15 rr=250;
16 rr=rr/MVA_b;
17 Vb=1;
18 Vt=1;
19 Ia=.5;
20 phi=asind(Xb*Ia/2);
21 pf=cosd(phi); disp(pf, 'pf');
22 Pe=rr*pf; disp(Pe, 'real power(pu)');
23 Eg=Vt+j*Xsg*rr**complex(cosd(-phi), sind(-phi));

```

```

24 Egg=abs(Eg)*V; disp(Egg, 'excitation emf(V) ');
25
26
27 rr=500;
28 rr=rr/MVA_b;
29 Vb=1;
30 Vt=1;
31 Ia=1;
32 phi=asind(Xb*Ia/2);
33 pf=cosd(phi); disp(pf, 'pf ');
34 Pe=rr*pf; disp(Pe, 'real power(pu) ');
35 Eg=Vt+j*Xsg*rr*complex(cosd(-phi), sind(-phi));
36 Egg=abs(Eg)*V; disp(Egg, 'excitation emf(V) ');

```

Scilab code Exa 8.43 to calculate pf angle torque angle equivalent capacitor and inductor value

```

1 //to calculate pf angle, torque angle, equivalent
  capacitor and inductor value
2
3 clc;
4 of1=250;
5 scr=.52; //short ckt ratio
6 of2=of1/scr;
7 r=25*10^6;
8 V=13000;
9 Ia=r/(sqrt(3)*V);
10 Isc=Ia*of1/of2;
11 Xs=V/(sqrt(3)*Isc);
12 Xb=V/(sqrt(3)*Ia);
13 Xsadj=Xs/Xb;
14
15 f=50;
16 If=200;
17 Ef=V*If/of1;

```

```

18 Vt=V/sqrt(3);
19 Ia=(Vt-Ef/sqrt(3))/Xs;
20 dl=0;disp(dl,'torque angle(deg)');
21 pf=90;disp(pf,'pf angle(deg)');
22 L=(V/(sqrt(3)*Ia))/(2*pi*f);
23 disp(L,'inductor value(H)');
24
25 If=300;
26 Eff=V*If/of1;
27 Vt=Ef/sqrt(3);
28 Ia=(Eff/sqrt(3)-Vt)/Xs;
29 dl=0;disp(dl,'torque angle(deg)');
30 pf=90;disp(pf,'pf angle(deg)');
31 c=1/((V/(Ia))*(2*pi*f));
32 disp(c,'capacitor value(F)');

```

Scilab code Exa 8.44 to determine X_s saturated scr X_s unsat and I_f generator current

```

1 //to determine  $X_s$ (saturated),scr, $X_s$ (unsat)and  $I_f$ ,
   generator current
2
3 clc;
4 MVA_b=400;
5 kV_b=22;
6 Ib=MVA_b/(sqrt(3)*kV_b);
7 ohm_b=kV_b/(sqrt(3)*Ib);
8
9 If=1120;
10 Voc=kV_b/sqrt(3);
11 Isc=13.2;
12 Xssat=Voc/Isc;disp(Xssat,' $X_s$ (saturated)(ohm)');
13 Xss=Xssat/ohm_b;disp(Xss,' $X_s$ (saturated)(pu)');
14 scr=1/Xss;disp(scr,'SCR');
15 Isc=Ib;

```

```

16 Voc=24.4/sqrt(3);
17 Xsunsat=Voc/Isc;disp(Xsunsat,'Xs(unsaturated)(ohm)')
    ;
18 Xsuns=Xsunsat/ohm_b;disp(Xsuns,'Xs(unsaturated)(pu)')
    );
19 Iff=If*scr;disp(Iff,'generator current(A)');

```

Scilab code Exa 8.45 find motor pf

```

1 //find motor pf
2
3 clc;
4 j=sqrt(-1);
5 V=6600;
6 Vt=V/sqrt(3);
7 pf=.8;
8 phi=acosd(pf);
9 P=800000;
10 Ia=P/(sqrt(3)*V*pf);
11 Zs=2+20*j;
12 Ef=Vt-Zs*Ia*complex(cosd(phi)+sind(phi));
13 Pip=1200*10^3;
14 theta=atand(imag(Zs)/real(Zs));
15 dl=acosd((real(Ef)^2*cosd(theta)/abs(Zs)-P/3)/(real(
    Ef)*abs(Ef)/abs(Zs)))-theta;
16
17 Ia=(real(Ef)-abs(Ef)*complex(cosd(-dl),sind(-dl)))/
    Zs;
18 phi=atand(imag(Ia)/real(Ia));
19 disp(cosd(phi),'pf');

```

Scilab code Exa 8.46 to find exciting emf neglecting saliency and accounting saliency

```

1 //to find exciting emf neglecting saliency and
   accounting saliency
2
3 clc;
4 j=sqrt(-1);
5 Xd=.12/3;
6 Xq=.075/3;
7
8 disp('neglecting saliency');
9 Xs=Xd;
10 V=440;
11 pf=.8;
12 phi=acosd(pf);
13 Vt=V/sqrt(3);
14 Ia=1000;
15 Ef=Vt+j*Xs*Ia*complex(cosd(-phi),sind(-phi));
16 disp(abs(Ef)*sqrt(3),'excitation emf(line)(V)');
17 disp('accounting saliency');
18 w=atand((Vt*sind(phi)+Ia*Xq)/(Vt*cosd(phi)));
19 dl=w-phi;
20 Ef=Vt*cosd(dl)+Ia*sind(dl)*Xd;
21 disp(abs(Ef)*sqrt(3),'excitation emf(line)(V)');

```

Scilab code Exa 8.47 calculate excitation emf max load motor supplies torque angle

```

1 //calculate excitation emf,max load motor supplies ,
   torque angle
2
3 clc;
4 Xd=23.2;
5 Xq=14.5;
6 V=6600;
7 pf=.8;
8 phi=acosd(pf);

```

```

 9 Vt=V/sqrt(3);
10 r=1500*1000;
11 Ia=r/(sqrt(3)*V)
12 w=atand((Vt*sind(-phi)-Ia*Xq)/(Vt*cosd(phi)));
13 dl=-phi-w;disp(dl,'torque angle');
14 Ef=Vt*cosd(dl)-Ia*sind(w)*Xd;
15 disp(Ef,'excitation emf(V)');
16
17 Pe=V^2*((Xd-Xq)/(2*Xd*Xq));disp(Pe,'load supplied(W)
    ');

```

Scilab code Exa 8.49 find no load freq setting sys freq at no load freq of swing generator system trip freq

```

1 //find no load freq setting ,sys freq ,at no load freq
  of swing generator , system trip freq
2
3 clc;
4 loadtot=260;
5 r=125;
6 pf=.84;
7 genfl=r*pf;
8 sld=75; //supply load
9 n=3; //no of generators
10 ls=loadtot-n*sld;
11 m=-5/genfl;
12 f=50;
13 ff=f-m*sld;disp(ff,'set freq(Hz)');
14 c=f-m*ls;disp(c,'set freq(Hz) supplied from swing
  generator');
15 nld=sld+50/4;
16 c=ff+m*nld;disp(c,'new system freq(Hz)');
17 rld=310-n*sld;
18 c=f-m*rld;disp(c,'set freq(Hz) of swing generator');
19 nld=310/n;

```

```
20 c=ff+m*nld;disp(c,'system trip freq(Hz)');
```

Chapter 9

Induction Machine

Scilab code Exa 9.1 to compute cu loss in rotoe windings input to the motor efficiency

```
1 // to compute cu loss in rotoe windings , input to
   the motor , efficiency
2
3 clc ;
4 f_s=120/60;           //cycles/min
5 f=50;
6 s=f_s/f;
7 n_s=1000;
8 n=(1-s)*n_s;
9 w=n*2*%pi/60;
10 T=160;
11 P=T*w;
12 T_L=10;
13 P_m=(T+T_L)*w;
14 cu=P_m*(s/(1-s));    disp(cu, 'rotor cu loss (W) ');
15
16 P_sl=800;           //stator loss
17 P_in=P_m+cu+P_sl;    disp(P_in, 'power i/p to motor (W
   ) ');
18
```



```

19 eff=P/P_in;
20 disp( eff*100, 'efficiency (%) ');

```

Scilab code Exa 9.2 to calculate torque resistance to be added to rotor ckt

```

1 //to calculate torque, resitance to be added to rotor
  ckt
2
3 clc;
4 f=50;
5 P=6;
6 n_s=120*f/P;
7 w_s=2*%pi*n_s/60;
8 n=875;
9 s_maxT=(n_s-n)/n_s;
10 R_2=.25;
11 X_2=R_2/s_maxT;
12 T_max=10;
13 //v=V/a
14 v=sqrt((T_max*w_s*X_2)/(3*.5));
15 T=((3)*v^2*(R_2/s))/(w_s*((R_2/s)^2+(X_2)^2));
16 disp(T, 'torque (Nm) ');
17
18 //from eqn (T_start/T_max)=(R2+Rext)*(X2/.5)/((R2+
  Rext)^2+X2^2)
19 //after solving
20 //Rt^2-6.67*Rt+4=0
21 function [x]=quad(a,b,c)
22     d=sqrt(b^2-4*a*c);
23     x1=(-b+d)/(2*a);
24     x2=(-b-d)/(2*a);
25     if(x1>x2)
26         x=x2;
27     else

```

```

28         x=x1;
29     end
30 endfunction
31 Rt=quad(1,-6.67,4);
32 r2=.25;
33 disp(Rt-r2,'external resistance (ohm)');

```

Scilab code Exa 9.3 to find slip at max torque full load slip and rotor current at starting

```

1 //to find slip at max torque ,full load slip and
  rotor current at starting
2
3 clc;
4 //Tfl=(3/w_s)*(V^2*Rs/s_fl)/((R2/s_fl)^2+X2^2);      (
  i)
5 //Ts=(3/w_s)*(V^2*R2)/(R2^2+X2^2);      (ii)
6 //Tmax=(3/w_s)*(.5*V^2)/X2^2;      (iii)
7 //Tmax/Ts=2;      k=R2/X2;      (iii)/(ii)and solving
8 //k^2-4*k+1=0;
9 function [x]=quad(a,b,c)
10     d=sqrt(b^2-4*a*c);
11     x1=(-b+d)/(2*a);
12     x2=(-b-d)/(2*a);
13     if(x1>x2)
14         x=x2;
15     else
16         x=x1;
17     end
18 endfunction
19 k=quad(1,-4,1);
20 disp(k,'s_max-T');
21
22 //((iii)/(i)and solving
23 //s_fl^2-1.072*s_fl+.072=0

```

```

24 s_fl=quad(1,-1.072,.072);
25 disp(s_fl,'s_fl');
26
27 //a=I2_start/I2_fullload
28 a=sqrt((k/s_fl)^2+1)/(k^2+1);
29 disp(a,'I2_start/I2_fullload');

```

Scilab code Exa 9.4 to calculate stator current pf net mech op torque motor performance

```

1 //to calculate stator current ,pf, net mech o/p,
   torque, motor performance
2
3 clc;
4 j=sqrt(-1);
5 Vt=400;
6 P=6;
7 f=50;
8 Inl=7.5;
9 Pnl=700;
10 disp('block rotor test results');
11 Vbr=150;
12 Ibr=35;
13 Pinbr=4000;
14 R1=.55; disp(R1,'R1(ohm)');
15 k=1/.5;
16 s=0.04;
17 Zbr=Vbr/(sqrt(3)*Ibr);
18 Rbr=Pinbr/(3*Ibr^2);
19 Xbr=sqrt(Zbr^2-Rbr^2);
20 X1=Xbr/(1+.5); disp(X1,'X1(ohm)');
21 X2=Xbr-X1; disp(X2,'X2(ohm)');
22 disp('no load test results');
23 Zo=Vt/(sqrt(3)*Inl);
24 Ro=Pnl/(3*Inl^2);

```

```

25 Xo=sqrt(Zo^2-Ro^2);
26 Xm=Xo-X1;disp(Xm,'Xm(ohm)');
27 R2=(Rbr-R1)*((Xm+X2)/Xm)^2;disp(R2,'R2(ohm)');
28 Zf=1/((1/(j*Xm))+1/((R2/s)+j*X2));
29 Rf=real(Zf);
30 Xf=imag(Zf);
31 Zin=R1+j*X1+Zf;
32 I1=Vt/(sqrt(3)*Zin);
33 Pin=sqrt(3)*Vt*abs(I1)*cosd(atan2(imag(I1),real(I1)))
    );disp(Pin,'Pin(W)');
34 Pg=3*abs(I1)^2*Rf;disp(Pg,'Pg(W)');
35 Pm=(1-s)*Pg;disp(Pm,'Pm(W)');
36 Prot=Pnl-3*Inl^2*R1;disp(Prot,'Prot(W)');
37 Pout=Pm-Prot;disp(Pout,'Pout(W)');
38 w_s=1000*2*pi/60;
39 Tnet=Pout/((1-s)*w_s);disp(Tnet,'Tnet(Nm)');
40 eff=Pout*100/Pin;disp(eff,'eff(%)');

```

Scilab code Exa 9.5 to determine ckt model parameters parameters of thevenin equivalent max torque and slip stator current pf and eff

```

1 //to determine ckt model parameters ,parameters of
   thevenin equivalent , max torque and slip , stator
   current , pf and eff
2
3 clc;
4 j=sqrt(-1);
5 //NL test
6 V=3300;
7 f=50;
8 Inl=5;
9 Po=2500;
10 Zo=V/(sqrt(3)*Inl);
11 Ro=Po/(3*Inl^2);disp(Ro,'Ro(ohm)');
12 Xo=sqrt(Zo^2-Ro^2);disp(Xo,'Xo(ohm)');

```

```

13 //BR test
14 V_BR=400;
15 I_BR=27;
16 ff=15;
17 P_BR=15000;
18 Z_BR=V_BR/(sqrt(3)*I_BR);
19 R_BR=P_BR/(3*I_BR^2);
20 X_BR=sqrt(Z_BR^2-R_BR^2);
21 x1=X_BR/2; //at 15 Hz
22 X1=x1*f/ff; //at 50Hz
23 disp(X1, 'X1(ohm)');
24 Xm=Xo-X1; disp(Xm, 'Xm(ohm)');
25 R1=3.75;
26 R2=(R_BR-R1)*((Xm+X1)/Xm)^2; disp(R2, 'R2(ohm)');
27
28 V_TH=(V/sqrt(3))*complex(cosd(0),sind(0))*complex(0,
    Xm)/complex(R1,X1+Xm);
29 disp(V_TH, 'V_TH(V)');
30 Z_TH=complex(0,Xm)*complex(R1,X1)/complex(R1,X1+Xm);
31 disp(real(Z_TH), 'R_TH(ohm)');
32 disp(imag(Z_TH), 'X_TH(ohm)');
33
34 a=(sqrt(real(Z_TH)^2+(X1+imag(Z_TH))^2));
35 s_max_T=R2/a;
36 n_s=1000;
37 Z_tot=complex(real(Z_TH)+a,X1+imag(Z_TH));
38 I2=abs(V_TH)/abs(Z_tot);
39 T_max=3*(I2^2)*R2/(s_max_T*(2*pi*n_s/60)); disp(
    T_max, 'T_max(Nm)');
40
41 Z_f=complex(0,Xm)*complex(81.25,X1)/complex(81.25,X1
    +Xm);
42 Z_in=Z_f+complex(R1,X1);
43 I1=V/(sqrt(3)*abs(Z_in));
44 pf=cosd(atan(imag(Z_in)/real(Z_in)));
45 s=.04;
46 Pmechg=(1-s)*3*I1^2*real(Z_f);
47 Prot=Po-Inl^2*R1;

```

```

48 Pip=sqrt(3)*V*I1*pf;
49 Pop=Pmechg-Prot;
50 eff=Pop/Pip;disp(eff,'efficiency');
51 Tint=Pmechg/((1-s)*2*%pi*n_s/60);disp(Tint,'internal
torque developed(Nm)');

```

Scilab code Exa 9.6 to calculate starting torque and current full load current pf torque internal and overall eff slip and max torque

```

1 //to calculate starting torque and current ,full load
current ,pf, torque , internal and overall eff ,
slip and max torque
2
3 clc;
4 R1=.3;
5 R2=.25;
6 X1=.6;
7 X2=.6;
8 Xm=35;
9 Prot=1500;
10 V=231;
11 Z_TH=complex(0,Xm)*complex(R1,X1)/complex(R1,X1+Xm);
12 V_TH=(V*complex(0,Xm))/complex(R1,X1+Xm);
13 n_s=1500;
14 w_s=2*%pi*n_s/60;
15
16 s=1;
17 Z_f=complex(0,Xm)*complex(R2,X2)/complex(R2,X2+Xm);
18 R_f=real(Z_f);
19 Z_in=Z_f+complex(R1,X1);
20 I1=V/abs(Z_in);disp(I1,'starting current(A)');
21 Tstart=3*I1^2*R_f/w_s;disp(Tstart,'starting torque(
Nm)');
22
23 n=1450;

```

```

24 s=1-n/n_s;
25 a=R2/s;
26 Z_f=complex(0,Xm)*complex(a,X2)/complex(a,X2+Xm);
27 R_f=real(Z_f);
28 Z_in=Z_f+complex(R1,X1);
29 I1=V/abs(Z_in);disp(I1,'full load current(A)');
30 pf=cosd(atan2(imag(Z_in)/real(Z_in)));disp(pf,'pf');
31 P_G=3*I1^2*R_f;
32 Popg=P_G*(1-s);
33 Pop=Popg-Prot;
34 Tnet=Pop/((1-s)*w_s);disp(Tnet,'net torque(Nm)');
35 Vt=400;
36 Pip=sqrt(3)*Vt*I1*pf;
37 eff=Pop/Pip;disp(eff*100,'efficiency(%)');
38 int_eff=Popg/Pip;disp(int_eff*100,'internal eff(%)')
    ;
39
40 s_max_T=1/(sqrt(real(Z_TH)^2+(imag(Z_TH)+X1)^2)/R2);
    disp(s_max_T,'max slip');
41 Z_tot=Z_TH+complex(R2/s_max_T,X2);
42 I2=abs(V_TH)/abs(Z_tot);
43 T_max=3*I2^2*(R2/s_max_T)/w_s;
44 disp(T_max,'max torque(Nm)');

```

Scilab code Exa 9.9 to determine the line current pf power ip shaft torque mech op and efficiency

```

1 //to determine the line current ,pf , power ip , shaft
    torque , mech op and efficiency
2
3 clc;
4 R1=1.4;
5 R2=.6;
6 X1=2;
7 X2=1;

```

```

8 Xm=50;
9 V=400;
10 Prot=275;
11 n_s=1000;
12 w_s=2*%pi*n_s/60;
13
14 disp('slip=0.03');
15 s=0.03;
16 I2=(V/sqrt(3))/complex(R1+R2/s,X1+X2);
17 Im=(V/sqrt(3))/(Xm*complex(cosd(90),sind(90)));
18 I1=Im+I2;
19 I_L=abs(I1);disp(I_L,'line current(A)');
20 pf=cosd(atan2(imag(I1)/real(I1)));disp(pf,'pf');
21 Pip=sqrt(3)*V*abs(I1)*cosd(atan2(imag(I1)/real(I1)))
    ;disp(Pip,'power i/p(W)');
22
23 P_G=3*abs(I2)^2*R2/s;
24 Pmechg=(1-s)*P_G;disp(Pmechg,'mech power op(W)');
25 Popnet=Pmechg-Prot;
26 Tnet=Popnet/(w_s*(1-s));disp(Tnet,'shaft torque(Nm)');
27
28 eff=Popnet/Pip;disp(eff,'efficiency');
29
30 disp('slip= -0.03');
31 s=-0.03;
32 I2=(V/sqrt(3))/complex(R1+R2/s,X1+X2);
33 Im=(V/sqrt(3))/(Xm*complex(cosd(90),sind(90)));
34 I1=-(Im+I2);
35 I_L=abs(I1);disp(I_L,'line current(A)');
36 pf=cosd(atan2(imag(I1)/real(I1)));disp(pf,'pf');
37 Pip=sqrt(3)*V*abs(I1)*cosd(atan2(imag(I1)/real(I1)))
    ;disp(Pip,'power i/p(W)');
38
39 P_G=3*abs(I2)^2*R2/s;
40 Pmechop=(1-s)*P_G;
41 Pmechipnet=-Pmechop;
42 Pmechipg=Pmechipnet+Prot;disp(Pmechipg,'mech power
    op(W)');

```



```

42 Tnet=Pmechipg/(ws*(1-s));disp(Tnet,'shaft torque(Nm
    )');
43 eff=Pip/Pmechipg;disp(eff,'efficiency');
44
45 disp('slip= 1.2');
46 s=1.2;
47 I2=(V/sqrt(3))/complex(R1+R2/s,X1+X2);
48 Im=(V/sqrt(3))/(Xm*complex(cosd(90),sind(90)));
49 I1=Im+I2;
50 I_L=abs(I1);disp(I_L,'line current(A)');
51 pf=cosd(atan2(imag(I1),real(I1)));disp(pf,'pf');
52 Pip=sqrt(3)*V*abs(I1)*pf;disp(Pip,'power i/p(W)');
53
54 P_G=3*abs(I2)^2*.5/s;
55 Pmechg=(1-s)*P_G;disp(Pmechg,'mech power op(W)');
56 Pmechabs=-Pmechg;
57 n=ns*(1-s);
58 w=2*pi*n/60;
59 Tnet=Pmechg/w;disp(Tnet,'torque developed(Nm)');
60 P=Pmechabs+Pip;disp(P,'power disipated(W)');

```

Scilab code Exa 9.10 to calculate max torque and slip starting torque

```

1 //to calculate max torque and slip , starting torque
2
3 clc;
4 k=5; //k=Is/Ifl
5 sfl=0.04;
6 smax_T=sqrt((sfl^2*(1-k^2))/((k*sfl)^2-1));disp(
    smax_T,'slip');
7 Tmax=.5*(smax_T^2+sfl^2)/(sfl*smax_T);disp(
    Tmax,'max torque(pu)');
8
9 Ts=k^2*sfl;disp(Ts,'starting torque(pu)');

```

Scilab code Exa 9.11 to find starting current and torque necessary external resistance and corresponding starting torque

```

1 //to find starting current and torque , necessary
   external resistance and corresponding starting
   torque
2
3 clc ;
4 f=50;
5 R2=.1;
6 X2=2*%pi*f*3.61*10^-3;
7 a=3.6;
8 R22=a^2*R2;
9 X22=a^2*X2;
10 V=3000;
11 n_s=1000;
12 w_s=2*%pi*n_s/60;
13 I_s=(V/sqrt(3))/sqrt(R22^2+X22^2);disp(I_s,'starting
   current (A)');
14 T_s=(3/w_s)*(V/sqrt(3))^2*R22/(R22^2+X22^2);disp(T_s
   ,'torque (Nm)');
15
16 Iss=30;
17 Rext=sqrt((V/sqrt(3)/Iss)^2-X22^2)-R22);
18 disp(Rext,'external resistance (ohm)');
19 T_s=(3/w_s)*(V/sqrt(3))^2*(R22+Rext)/((R22+Rext)^2+
   X22^2);disp(T_s,'torque (Nm)');

```

Scilab code Exa 9.12 find line current and starting torque with direct switching stator resistance starting autotransformer starting star delta starting autotransformer ratio give 1 pu

```

1 //find line current and starting torque with direct
  switching, stator resistance starting,
  autotransformer starting, star delta starting,
  autotransformer ratio give 1 pu
2
3 clc;
4 //I_s/I_fl=6;
5 s_fl=0.05;
6 disp('by direct switching');
7 Is=6;disp(Is,'line current (pu)');
8 T=Is^2*s_fl;disp(T,'torque (pu)');
9
10 disp('by stator resistance starting');
11 Is=2;disp(Is,'line current (pu)'); //given
12 T=Is^2*s_fl;disp(T,'torque (pu)');
13
14 disp('by autotransformer starting');
15 x=2/6;
16 Is_motor=2;
17 Is=Is_motor*x;disp(Is,'line current (pu)');
18 T=Is^2*s_fl;disp(T,'torque (pu)');
19
20 disp('by star delta starting');
21 Is=(1/3)*6;disp(Is,'line current (pu)');
22 T=Is^2*s_fl*3;disp(T,'torque (pu)');
23
24 disp('by autotransformer starting');
25 Ts=1;
26 x=sqrt(Ts/((6^2)*s_fl));disp(x,'x');

```

Scilab code Exa 9.13 to find resistance added to ckt

```

1 //to find resistance added to ckt
2
3 clc;

```

```

4 Rrot=.061;
5 R2=Rrot/2;
6 f=50;
7 P=12;
8 w_s=(120*f/P)*(2*pi/60);
9 s=0.045;
10 w=(1-s)*w_s;
11 P=200*10^3;
12 T_fan=P/w;
13 I2=sqrt(T_fan*w_s*s/(3*R2));
14 E2=I2*R2/s;
15 n=450;
16 ww=2*pi*n/60;
17 nn=500;
18 ss=(nn-n)/nn;
19 Tnew=T_fan*(ww/w)^2;
20 Rt=(3/w_s)*(E2*ss)^2/(ss*Tnew);
21 Rext=Rt-R2; disp(Rext, 'external resistance (ohm) ');

```

Scilab code Exa 9.14 to find resistance added to ckt

```

1 //to find resistance added to ckt
2
3 clc;
4 n_s=1500;
5 w_s=2*pi*n_s/60;
6 n=1250;
7 s=1-n/n_s;
8 //Im=(1/3)*(0.3+.25/s+j*1.83)ohm/ph
9 T=150;
10 V=440;
11 //T=(3/w_s)*(V^2*(R_2t/s))/((.1+(R_2t/s))^2+(X1+X2)^2);
12 //after solving R_2t^2-1.34*R_2t+0.093=0
13 function [x]=quad(a,b,c)

```

```

14     d=sqrt(b^2-4*a*c);
15     x1=(-b+d)/(2*a);
16     x2=(-b-d)/(2*a);
17     if(x1>x2)
18         x=x1;
19     else
20         x=x2;
21     end
22 endfunction
23 [x]=quad(1,-1.34,0.093);
24 Rext=x-0.083;disp(Rext,'external resistance (ohm)');

```

Scilab code Exa 9.15 to calculate the min resistance to be added and speed of the motor

```

1 //to calculate the min resistance to be added and
   speed of the motor
2
3 clc;
4 V=400;
5 a=2.5;
6 X2=.4;
7 R2=0.08;
8 n_s=750;
9 w_s=2*pi*n_s/60;
10 T=250;
11 //T=(3/w_s)*((V/sqrt(3))/a)*R2t/(R2t^2+X2^2);
12 //after solving
13 //R2t^2-1.304*R2t+0.16=0
14 function [x1,x2]=quad(a,b,c)
15     d=sqrt(b^2-4*a*c);
16     x1=(-b+d)/(2*a);
17     x2=(-b-d)/(2*a);
18 endfunction
19 [x1 x2]=quad(1,-1.304,0.16);

```

```

20     if (x1>x2)
21         R2t=x2;
22     else
23         R2t=x1
24     end
25 Rext=R2t-R2;
26 disp(Rext, 'external resistance (ohm) ');
27
28 //T=(3/w_s)*((V/sqrt(3))/a)*(R2t/s)/((R2t/s)^2+X2^2)
29 ;
30 //after solving
31 //((R2t/s)^2-1.304*(R2t/s)+0.16=0
32 [x1 x2]=quad(1,-1.304,0.16);
33 s=x2/x1;
34 n=n_s*(1-s);
35 disp(n, 'speed (rpm) ');
36
37 //T=(3/w_s)*((V/sqrt(3))/a)*(R2/s)/((R2/s)^2+X2^2);
38 //after solving
39 //((R2/s)^2-1.304*(R2/s)+0.16=0
40 [x1 x2]=quad(1,-1.304,0.16);
41 R2=0.08;
42 s1=R2/x1;
43 s2=R2/x2;
44 if (s1>s2)
45     ss=s2;
46 else
47     ss=s1
48 end
49 n=n_s*(1-ss);
50 disp(n, 'speed (rpm) ');

```

Scilab code Exa 9.17 to find the ratio of currents and torques at the starting V_2 by V_1

```

1 //to find the ratio of currents and torques at the
   starting ,V2/V1
2
3 clc;
4 f1=50;
5 f2=60;
6 f=f2/f1;
7 V=1;      //V=V2/V1
8 s_max_T=0.2;
9 //Is=I_s2/I_s1
10 Is=V*sqrt((s_max_T^2+1)/(s_max_T^2+f^2));
11 disp(Is,'ratio of currents at starting');
12 //Ts=T_s2/T_s1
13 Ts=V^2*((s_max_T^2+1)/(s_max_T^2+f^2));
14 disp(Ts,'ratio of torques at starting');
15 //Tmax=Tmax2/Tmax1
16 Tmax=V^2/f^2;
17 disp(Tmax,'ratio of max torques');
18 Vr=sqrt(1/sqrt((s_max_T^2+1)/(s_max_T^2+f^2)));
19 disp(Vr,'V2/V1');

```

Scilab code Exa 9.18 to calculate ratio of torques at starting and given slip

```

1 //to calculate ratio of torques at starting and at
   slip =0.05
2
3 clc;
4 R1=0.01;
5 X1=.5;
6 R2=0.05;
7 X2=.1;
8 Ts=((R1^2+X1^2)/(R2^2+X2^2))*(R2/R1);
9 disp(Ts,'Tso/Tsi');
10

```

```

11 s=0.05;
12 T=((R1/s)^2+X1^2)/((R2/s)^2+X2^2)*(R2/R1);
13 disp(T, 'To/Ti');

```

Scilab code Exa 9.19 to compute acc time and value of rotor resistance

```

1 //to compute acc time and value of rotor resistance
2
3 clc;
4 s=1-.96; //load is brought to .96 of n_s
5 s_max_T=sqrt((1-s^2)/(2*log(1/s)));
6 R=1.5;
7 R2_opt=R*s_max_T;disp(R2_opt, 'rotor resistance (ohm)');
8 n=1000;
9 w_s=2*pi*n/60;
10 V=415;
11 Tmax=(3/w_s)*(0.5*(V/sqrt(3))^2)/R;
12 J=11;
13 t_A=(J*w_s/(2*Tmax))*((1-s^2)/(2*s_max_T)+s_max_T*log(1/s));
14 disp(t_A, 'acc time (min)');

```

Chapter 10

Fractional Kilowatt Motors

Scilab code Exa 10.1 to compute the ratio of Emf by Emb Vf by Vb Tf by Tb gross total torque Tf by total torque Tb by total torque

```
1 // to compute the ratio of E_mf/E_mb, V_f/V_b, T_f/T_b
   , gross total torque, T_f/total torque, T_b/total
   torque
2
3 clc;
4 R_1m=3;
5 X_1m=5;
6 R_2=1.5;
7 X_2=2;
8 s=1-.97; //slip
9 a=complex(R_2/s, X_2);
10 b=complex(R_2/(2-s), X_2);
11 c=abs(a)/abs(b);
12 disp(c, 'E_mf/E_mb');
13 a=(1/2)*complex((R_1m+R_2/s), (X_1m+X_2));
14 b=(1/2)*complex((R_1m+R_2/(2-s)), (X_1m+X_2));
15 c=abs(a)/abs(b);
16 disp(c, 'V_f/V_b');
17 d=(2-s)/s;
18 disp(d, 'T_f/T_b');
```

```

19 Z_tot=a+b;
20 V=220;
21 I_m=V/abs(Z_tot);
22 P=6;
23 f=50;
24 n_s=120*f/P;
25 w_s=2*pi*n_s/60;
26 T_f=(I_m^2*R_2/(2*w_s))*(1/s);
27 T_b=(I_m^2*R_2/(2*w_s))*(1/(2-s));
28 T_tot=T_f-T_b;
29 disp(T_tot,'gross total torque(Nm)');
30 a=T_f/T_tot;
31 b=T_b/T_tot;
32 disp(a,'T_f/T_total');
33 disp(b,'T_b/T_total');

```

Scilab code Exa 10.2 to calculate parameters of the ckt model line current power factor shaft torque and efficiency

```

1 // to calculate parameters of the ckt model, line
   current, power factor, shaft torque and
   efficiency
2
3 clc;
4 V_0=215;
5 I_0=3.9;
6 P_0=185;
7 R_1=1.6;
8 V_sc=85;
9 I_sc=9.8;
10 P_sc=390;
11 X=(V_0/I_0)*2; //magnetisation reactance
12 phi_sc=acosd(P_sc/(V_sc*I_sc));
13 I_e=V_sc/complex(0,X);
14 I_SC=I_sc*complex(cosd(phi_sc*(-1)),sind(phi_sc*(-1))

```

```

    ));
15 I_m=I_SC-I_e;
16 Z=V_sc/I_m;
17 R_2=real(Z)-R_1; // real(Z)=R=R1+R2
18 disp(R_2, 'R_2(ohm) ');
19 disp(imag(Z), 'X_1+X_2(ohm) ');
20
21 n=1500; nn=1440;
22 s=(n-nn)/n;
23 a=1.55/s;
24 b=1.55/(2-s);
25 Z_ftot=(complex(0,X/2))*(complex(a+.8, imag(Z)/2))/((
    complex(0,X/2)+(complex(a+.8, imag(Z)/2)));
26 Z_btot=(complex(0,X/2))*(complex(b+.8, imag(Z)/2))/((
    complex(0,X/2)+(complex(b+.8, imag(Z)/2)));
27 Z_tot=Z_ftot+Z_btot;
28 I_m=V_0/Z_tot;
29 I_L=abs(I_m); disp(I_L, 'line current (A) ');
30 pf=cosd(atan2(real(I_m)/imag(I_m))); disp(pf, 'pf'
    );
31 P_in=V_0*I_L*pf;
32 I_mf=I_m*complex(0,X/2)/complex(39.55,59.12);
33 I_mb=I_m*complex(0,X/2)/complex(1.59,59.12);
34 T=(1/157.1)*(abs(I_mf)^2*38.75-abs(I_mb)^2*.79);
35 P_m=157.1*(1-s)*T;
36 P_L=185;
37 P_out=P_m-P_L;
38 eff=P_out/P_in; disp(eff*100, 'efficiency (%) ');
39 T_shaft=P_out/157.1; disp(T_shaft, 'shaft torque(
    Nm) ');

```

Scilab code Exa 10.3 to compute amplitudes of forward and backward stator mmf waves magnitude of auxiliary current and its ph angle diff

```
1 //to compute amplitudes of forward and backward
```

```

    stator mmf waves ,magnitude of auxillary current
    and its ph angle diff
2
3 clc;
4 N_m=80;
5 N_a=100;
6 I_m=15*complex(cosd(0),sind(0));
7 I_aa=7.5*complex(cosd(45),sind(45));
8 I_a=7.5*complex(cosd(60),sind(60));
9 F_m=N_m*I_m;
10 F_a=N_a*I_a;
11 F_aa=N_a*I_aa;    //mmf at 45 angle
12 F_f=(1/2)*(F_m+imult(F_aa));a=abs(F_f);
13 disp(a,'forward field(AT)');
14 F_b=(1/2)*(F_m-imult(F_aa));b=abs(F_b);
15 disp(b,'backward field(AT)');
16 //1200+100*I_a*complex(sind(a),cosd(a))=0
17 //equating real and imaginery parts
18 //100*I_a*cosd(a)=0;
19 a=90;
20 disp(a,'phase angle diff');
21 I_a=-1200/(100*sind(a)); disp(I_a,'auxillary
    current(A)');

```

Scilab code Exa 10.4 to determine value of capacitor

```

1 //to determine value of capacitor
2
3 clc;
4 f=50;
5 w=2*%pi*f;
6 Z_lm=complex(3,2.7);
7 Z_la=complex(7,3);
8 I_m=(-1)*atand(imag(Z_lm)/imag(Z_la));
9 a=90;

```

```

10 I_a=a+I_m;
11 c=1/(w*(real(Z_lm)-real(Z_la)*tand((-1)*I_a)));
12 disp(c, 'value of capacitor (F) ');

```

Scilab code Exa 10.5 to calculate starting torque and current value of run capacitor motor performance

```

1 //to calculate starting torque and current ,value of
  run capacitor ,motor performance
2
3 clc;
4 R_lm=4.2;
5 X_lm=11.3;
6 R_la=5.16;
7 X_la=12.1;
8 X=250;
9 a=1.05;
10 R_2=7.48;
11 X_2=7.2;
12 Z_f=(complex(0,X)*complex(R_2,X_2))/(complex(0,X)+
  complex(R_2,X_2));
13 c=314*70*10^-6;
14 Z_la=complex(R_la,X_la-1/c);
15 Z_lm=complex(R_lm,X_lm);
16 Z_12=(1/2)*(Z_la/(a^2)-(Z_lm));
17 V=220;
18 V_mf=(V/2)*complex(1,-1/a);
19 V_mb=(V/2)*complex(1,1/a);
20 Z=Z_lm+Z_f+Z_12;
21 I_mf=(V_mf*Z+V_mb*Z_12)/(Z^2-Z_12^2);
22 I_mb=(V_mb*Z+V_mf*Z_12)/(Z^2-Z_12^2);
23 n_s=1500;
24 w_s=2*%pi*n_s/60;
25 T_s=(2/w_s)*real(Z_f)*(abs(I_mf)^2+abs(I_mb)^2);disp
  (T_s, 'starting torque (Nm) ');

```

```

26 I_m=I_mf+I_mb;
27 I_a=imult(I_mf-I_mb)/a;
28 I_L=I_m+I_a;
29 disp(abs(I_L), 'I-L (start)(A)');
30
31 s=.04;
32 Z_f=(complex(0,X)*complex(R_2/s,X_2))/(complex(0,X)+
    complex(R_2/s,X_2));
33 Z_12=(-1/2)*complex(1,1/a)*(Z_lm+Z_f);
34 Z_1a=a^2*(2*Z_12+Z_lm);
35 Z=Z_1a-R_la-imult(X_la);
36 X_c=(-1)*imag(Z);
37 C=1/(314*X_c*10^-6);disp(C, 'value of run capacitor (
    uF)');
38
39 Z_f=(complex(0,X)*complex(R_2/s,X_2))/(complex(0,X)+
    complex(R_2/s,X_2));
40 Z_b=(complex(0,X)*complex(R_2/(2-s),X_2))/(complex
    (0,X)+complex(R_2/(2-s),X_2));
41 Z_la=complex(R_la,X_la)-imult(10^6/(314*C));
42 Z_12=(1/2)*((Z_la/(a^2))-complex(R_lm,X_lm));
43 Z1=Z_lm+Z_f+Z_12;
44 Z2=Z_lm+Z_b+Z_12;
45 I_mf=(V_mf*Z2+V_mb*Z_12)/(Z1*Z2-(Z_12)^2);
46 I_mb=(V_mb*Z1+V_mf*Z_12)/(Z1*Z2-(Z_12)^2);
47 T=(2/157.1)*((abs(I_mf)^2*real(Z_f))-(abs(I_mb)^2*
    real(Z_b)));
48 I_m=I_mf+I_mb;
49 I_a=imult(I_mf-I_mb)/a;
50 I_L=I_m+I_a;
51 I_l=abs(I_L); pf=1;
52 P_m=2*((abs(I_mf)^2*real(Z_f))-(abs(I_mb)^2*real(Z_b
    )))*(1-s);
53 P_L=45;
54 P_out=P_m-P_L;
55 P_in=I_l*V;
56 n=P_out/P_in;
57 disp(n, 'efficiency');

```

Scilab code Exa 10.6 to calculate starting torque and atarting current motor performance

```
1 //to calculate starting torque and atarting current ,
   motor performance
2
3 clc;
4 V_a=110*complex(cosd(90) ,sind(90));
5 V_m=220*complex(cosd(0) ,sind(0));
6 R_1=3;
7 R_2=2.6;
8 X_1=2.7;
9 X_2=2.7;
10 X=110;
11 V_f=(1/2)*(V_m-imult(V_a));
12 V_b=(1/2)*(V_m+imult(V_a));
13 Z_f=(complex(0,X)*complex(R_2,X_2))/(complex(0,X)+
   complex(R_2,X_2));
14 Z_b=Z_f;
15 Z_ftot=complex(R_1,X_1)+Z_f;
16 Z_btot=complex(R_1,X_1)+Z_b;
17 I_f=V_f/Z_ftot;
18 I_b=V_b/Z_btot;
19 T_s=(2/157)*real(Z_f)*(abs(I_f)^2-abs(I_b)^2);disp(
   T_s,'starting torque(Nm)');
20 I_m=I_f+I_b;
21 I_a=imult(I_f-I_b);disp(abs(I_a),'starting current(A
   )');
22 s=0.04;
23
24 Z_f=(complex(0,X)*complex(R_2/s,X_2))/(complex(0,X)+
   complex(R_2/s,X_2));
25 Z_b=(complex(0,X)*complex(R_2/(2-s),X_2))/(complex
   (0,X)+complex(R_2/(2-s),X_2));
```

```

26 Z_ftot=complex(R_1,X_1)+Z_f;
27 Z_btot=complex(R_1,X_1)+Z_b;
28 I_f=V_f/Z_ftot;
29 I_b=V_b/Z_btot;
30 w_s=157.1;
31 T_s=(2/157.1)*(abs(I_f)^2*real(Z_f)-abs(I_b)^2*real(
    Z_b));disp(T_s,'starting torque(Nm)');
32 I_m=I_f+I_b;m=atand(imag(I_m)/real(I_m));
33 I_a=imult(I_f-I_b);a=atand(imag(I_a)/real(I_a));
34 P_m=w_s*(1-s)*T_s;
35 P_L=200;
36 P_out=P_m-P_L;
37 P_min=V*abs(I_m)*cosd(m);
38 P_ain=V*abs(I_a)*cosd(a);
39 P_in=P_min+P_ain;
40 n=P_out/P_in;
41 disp(n,'efficiency');
42
43 r=Z_ftot/Z_btot; //r=V_mf/V_bf
44 //V_mf+V_bf=220
45 V_mf=220/(1+r);
46 V_mb=220-V_mf;
47 V_a=imult(V_mf-V_mb);
48 disp(abs(V_a),'V_a(V)');

```

Chapter 12

Motor Control by Static Power Convertors

Scilab code Exa 12.1 calculate power fed to load

```
1 //calculate power fed to load
2
3 clc;
4 V=100;
5 Va=(V/(sqrt(2)*%pi))*(2+1/sqrt(2));
6 Rd=10;
7 Pa=Va^2/Rd;
8 disp(Pa, 'load power (W)');
```

Scilab code Exa 12.2 calculate firing angle value

```
1 //calculate firing angle value
2
3 clc;
4 Po=15000;
5 Ro=1.5;
```

```
6 Va=sqrt(Po*Ro);
7 a=acosd((Va*2*pi/(3*sqrt(6)*V))-1);disp(a,'firing
   angle(deg)');
8 Ia=Va/Ro;
9 Ith=Ia/3;disp(Ith,'avg current through diodes(A)');
```

Scilab code Exa 12.3 calculate value of commutating capacitor

```
1 //calculate value of commutating capacitor
2
3 clc;
4 Iamax=100;
5 V=100;
6 f_max=400;
7 c=Iamax/(2*V*f_max);
8 disp(c,'value of commutating capacitor(F)');
```
