

Scilab Textbook Companion for  
Feedback Circuits And Operational Amplifiers  
by D. H. Horrocks<sup>1</sup>

Created by  
Naveen Varma Champathi  
B.Tech (pursuing)  
Electronics Engineering  
National Institute of Technology, Nagpur  
College Teacher  
Eswar Rao  
Cross-Checked by  
Aditya Sengupta, IIT Bombay

November 18, 2014

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Feedback Circuits And Operational Amplifiers

**Author:** D. H. Horrocks

**Publisher:** Chapman And Hall

**Edition:** 2

**Year:** 1990

**ISBN:** 0-412-34270-7

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
<b>2 GENERAL PROPERTIES OF FEEDBACK AMPLIFIERS</b>	<b>5</b>
<b>3 AMPLIFIERS WITHOUT FEEDBACK</b>	<b>8</b>
<b>4 FEEDBACK AMPLIFIER CIRCUITS</b>	<b>12</b>
<b>5 MORE ABOUT FEEDBACK AMPLIFIERS</b>	<b>16</b>
<b>6 THE OP AMPS BASIC IDEAS AND CIRCUITS</b>	<b>23</b>
<b>7 OP AMP NON IDEALITIES</b>	<b>25</b>
<b>8 SELECTED OP AMP APPLICATIONS</b>	<b>28</b>
<b>9 FURTHER OP AMP APPLICATIONS</b>	<b>31</b>

# List of Scilab Codes

Exa 2.1	feedback fraction . . . . .	5
Exa 2.2	Expected variations in closed loop gain . . . . .	6
Exa 3.1	Output voltage and gain of two stage amplifier . . . . .	8
Exa 3.2	single stage amplifier parameters . . . . .	9
Exa 3.3	Common mode rejection ratio and differential mode . . . . .	10
Exa 4.1	input resistance of a feedback amplifier . . . . .	12
Exa 4.2	input resistance of a feedback amplifier . . . . .	12
Exa 4.3	parameters of a feedback amplifier . . . . .	13
Exa 4.4	series voltage feedback circuit . . . . .	14
Exa 5.1	Voltage shunt feedback circuit . . . . .	16
Exa 5.2	amplifier parameters . . . . .	17
Exa 5.4	closed loop current gain input output resistance . . . . .	18
Exa 5.5	Voltage shunt feedback circuit . . . . .	20
Exa 5.6	feed back fraction . . . . .	22
Exa 6.1	design values of an inverting amplifier . . . . .	23
Exa 6.2	gain of a negative feedback amplifier . . . . .	23
Exa 6.4	non inverting amplifier . . . . .	24
Exa 7.1	Output voltage . . . . .	25
Exa 7.2	output offset voltage . . . . .	25
Exa 7.4	inverting voltage amplifier . . . . .	26
Exa 7.5	Full power bandwidth frequency . . . . .	27
Exa 8.1	basic differential amplifier . . . . .	28
Exa 8.2	Instrumental amplifier . . . . .	29
Exa 8.3	wein bridge oscillator . . . . .	29
Exa 9.1	Design of phase shifter . . . . .	31
Exa 9.2	design of non inverting amplifier . . . . .	32
Exa 9.3	low pass second order filter . . . . .	33

## Chapter 2

# GENERAL PROPERTIES OF FEEDBACK AMPLIFIERS

Scilab code Exa 2.1 feedback fraction

```
1 //example1:
2
3 printf(" Given:")
4 disp(" value of A=1000")//To display given values
5 A=1000
6 disp(" Magnitude of closed loop gain with feedback ,Af
   =10")
7 Af=10
8 disp(" Af=(A)/(1+A*b)")//standard formula for closed
   loop gain
9 disp(" b=((A/Af)-1)*(1/A)")
10 b=((A/Af)-1)*(1/A)
11 printf(' The value of b is %f',b)
12 //if ,A becomes 900 angle(-30 degrees)
13 A=900*cos(-%pi/6)+%i*900*sin(-%pi/6)
14 disp(" If ,A becomes 900 angle(-30 degrees)")
15 disp(" Af=(A)/((1+A*b))")//standard formula for
   closed loop gain
16 Af=(A)/((1+A*b))
```

```

17 r=real(Af)//To get real part of Af
18 i=imag(Af)//To get imaginary part of Af
19 printf(' The value of Af is (%f)+i(%f)',r,i)//to
    display value of Af
20 t=tan(i/r)//to get angle in radians of Af
21 t=t*180/%pi//to get angle in degrees
22 m=abs(Af)//to get magnitude of Af
23 printf('\n Af=%fangle(%f degrees)',m,t)
24 printf('\n Af=10.004angle(-0.32 degrees)')//rounding
    to 3 digits

```

---

### Scilab code Exa 2.2 Expected variations in closed loop gain

```

1 //To calculate the expected variations in closed
  loop gain
2 disp(" Given:")
3 disp(" Af=10+0.2% or 10-0.2%")//To display given
  values
4 disp(" -->Af=10 and dAf/Af=0.2%")
5 disp(" The available amplifiers are with gains
  50,500,5000")
6 disp(" dA/A=20%")
7 disp(" We have from formula")
8 disp(" dAf/Af=(1/(1+A*b))*(dA/A)")//standard formula
  for closed loop gain
9 disp(" let f=0.2%=(dAf/Af), a=20%=(dA/A), k=(1+A*b)")
10 disp(" Therefore we have:")
11 Af=10;
12 printf(" Af=%d\n", Af)
13 f=0.2/100;
14 printf(" f=%f\n", f)
15 a=20/100;
16 printf(" a=%f", a)
17 disp(" Therefore, the above formula becomes f=(1/k)*a"
  )

```

```

18 k=a/f
19 printf(" Therefore (1=A*b)>=%d, but ,A=(1+A*b)*Af" ,k)
20 l=k*Af//store partial value
21 disp("A>=k*Af")//given condition
22 printf(" Therefore we got the value of A to be >=%d"
    ,l)//display value of A
23 printf("\n Therefore A=5000 satisfies the obtained
    condition. Therefore A=5000 is most economical")
24 A=5000
25 b=((A/Af)-1)*(1/A)
26 printf(" The value of b is %f",b)
27 disp(" Pratical values of A are 4000 and 6000, since
    dA/A=(+-20%) and A=5000")
28 disp(" Therefore ")
29 Afmin=(4000/(1+(4000*b)))//to print result
30 Afmax=(6000/(1+(6000*b)))//to print result
31 printf(" Afmin=%1.3 f" ,Afmin)
32 devAfmin=(1-(Afmin/Af))*100;//deviation of Afmin
    from Af
33 printf("( %1.2 f percent low)",devAfmin)//to display
    deviation from original value
34 printf("\n Afmax=%2.3 f" ,Afmax)
35 devAfmax=(1-(Afmax/Af))*100;//deviation of Afmax
    from Af
36 dev=abs(devAfmax);//negative value of devAfmax
    indicates Afmax is greater than Af by abs(
    devAfmax)
37 printf("( %1.2 f percent high) ",dev)//to display
    deviation from original value

```

---



## Chapter 3

# AMPLIFIERS WITHOUT FEEDBACK

Scilab code Exa 3.1 Output voltage and gain of two stage amplifier

```
1 //example1:
2
3 printf(" Given:")
4 disp("The value of Rin=Rout=100kohms ,Rload=1kohm ,Kv
   =100")//To display given values
5 Rin=100//assigning given values
6 Rout=100
7 Rload=1
8 Kv=100
9 disp(" All resistances are in kohms")
10 disp("The whole two stage amplifier is fed by a
   generator having a voltage of Eg=1mV when no load
   and having self resistance Rg=20kohms")
11 Eg=(1/1000)//Eg converted to volts
12 Rg=20//all resistances are in kohms
13 disp(" Since amplifiers are identical")//given
14 disp(" Rin1=Rin")
15 disp(" Rin2=Rin")
16 disp(" Rout1=Rout")
```

```

17 disp(" Rout2=Rout")
18 Rin1=Rin//assigning given values
19 Rin2=Rin
20 Rout1=Rout
21 Rout2=Rout
22 disp(" Vout2 is given by equation")
23 disp(" Vout2=((Eg)*(Rin1/(Rg+Rin1)))*(Kv)*(Rin2/(
    Rout1+Rin2))*(Kv)*(Rload/(Rout2+Rload))")
24 Vout2=((Eg)*(Rin1/(Rg+Rin1)))*(Kv)*(Rin2/(Rout1+Rin2
    ))*(Kv)*(Rload/(Rout2+Rload))//equation for Vout2
25 printf(" Therefore Vout2=%f",Vout2)
26 disp(" Vin is given by equation ")
27 disp(" Vin=(Eg*(Rin1/Rg+Rin1))")
28 Vin=(Eg*(Rin1/(Rg+Rin1))//Equation for Vin
29 disp("Now overall gain ")
30 disp(" Av=(Vout2/Vin)")
31 Av=(Vout2/Vin)//Equation for Av
32 printf(" Therefore Vout2=%f and overall voltage gain
    Av=%f",Vout2,Av)//To print the required values.

```

---

### Scilab code Exa 3.2 single stage amplifier parameters

```

1
2 rin=10000;//in ohms
3 Kv=100;//constant for voltage-controlled voltage-
    source
4 rout=1000;//in ohms
5 //load resistance Rload
6 Rload=4000;//in ohms
7 C2=50*(10**-12);//in Farads
8 disp('Vout=Vin*(input voltage coupling)*Kv*(output
    voltage coupling)');
9 disp('(i)Mid band gain');
10 disp('Av=(Vout/Vin)=Kv*(Rload/(rout+Rload))');
11 Av=Kv*(Rload/(rout+Rload));

```

```

12 disp('(ii)For the upper half-power frequency');
13 disp('fu=(1/(2*%pi))*(1/(C2*(rout||Rload)))');
14 fu=(1/(2*%pi))*(1/(C2*((rout*Rload)/(rout+Rload))));
15 //Let coupling capacitance be C
16 disp('(iii)For coupling capacitance C ');
17 disp('fl=(1/(2*%pi))*(1/(C*rin))');
18 fl=10;//given lower half-power frequency fl
19 disp('C=1/(2*%pi*fl*rin)');
20 C=1/(2*%pi*fl*rin);
21 disp('RESULTS:\n');
22 printf('(i)Mid-band gain=%d\n',Av);
23 printf('(ii)Upper half-power frequency=%1.2f MHz\n',
    fu/(10**6));//fu divided by 10^6 to convert into
    MHz
24 printf('(iii)Coupling capacitance C for fl to be 10
    Hz is %1.2f uF\n',C*(10**6));// C multiplied by
    10^6 by convert to microFarads

```

---

### Scilab code Exa 3.3 Common mode rejection ratio and differential mode

```

1
2 disp(" given:")
3 disp("The voltage generated by an transducer which
    is connected to differential amplifier is Vdm=50
    mV ")
4 Vdm=50*(1/1000)//Vdm in volts
5 disp("Vcm=5V")
6 Vcm=5
7 disp("Vout should be equal to 10V")
8 Vout=10
9 disp("The unwanted output component owing to the
    common-mode input is to be less than 1% of the
    wanted component i.e Voutcm=1% of Voutdm")
10 Voutcm=(1/100)*10
11 printf(" Voutcm=%f",Voutcm)

```

```

12 disp("Let amplifier differential-mode gain be Adm")
13 disp("Vout,Admand Vdm are related as")
14 disp("Vout=Adm*Vdm------(1)")
15 disp("Adm=Vout/Vdm")
16 Adm=Vout/Vdm
17 printf(" Therefore amplifier differential-mode gain(
    Adm)=%d" ,Adm)
18 disp("Equation (1)can also be used for calculating
    unwanted output component")
19 disp("Unwanted components arise when operating in
    common-mode")
20 disp("Acm=Voutcm/Vcm")
21 Acm=Voutcm/Vcm
22 printf(" Common-mode gain Acm=%f" ,Acm)
23 disp("Now CMRR can be calculated using relation")
24 disp("CMRR=Adm/Acm")
25 CMRR=Adm/Acm
26 printf(" There fore CMRR of amplifier should be
    greater than or equal to %f" ,CMRR)
27 printf(" CMRR>=%d" ,CMRR)

```

---

## Chapter 4

# FEEDBACK AMPLIFIER CIRCUITS

Scilab code Exa 4.1 input resistance of a feedback amplifier

```
1 //input resistance in Kohm
2 Rin=1;
3 //voltage gain
4 Av=1000;
5 //feedback fraction
6 Bv=0.1;
7 //Let input resistance after feedback is applied be
  Zif
8 AB=Av*Bv;
9 Zif=Rin*(1+AB); //Zif in Kohms
10 printf("RESULTS:\n");
11 printf("Input resistance after feedback is applied
  Zif=%dKohms",Zif);
```

---

Scilab code Exa 4.2 input resistance of a feedback amplifier

```

1 //input impedance in ohms
2 Rin=10000;
3 //Trans-resistance in ohms
4 Rt=(10)^(5);
5 //feedback fraction Bg
6 Bg=(10)^(-3);
7 AB=Rt*Bg;
8 //input impedance after feedback is applied Zif in
  ohms
9 Zif=Rin/(1+AB);
10 printf("RESULTS:\n");
11 printf("Input impedance after feedback applied is
    Zif=%d Ohms",Zif);

```

---

**Scilab code Exa 4.3** parameters of a feedback amplifier

```

1 //Trans-resistance Rtf in Kohms
2 Rtf=(-10);
3 //given
4 R1=20;//in Kohms
5 R2=5;
6 Rc=1;
7 //transistor parameters in kohms
8 hie=1;
9 hfe=0.1;
10 //feedback fraction Bg
11 Bg=1/Rtf;
12 R=(-Rtf);
13 //input resistance ri in ohms
14 a=(R1*R2*hie)/((R1*R2)+(R1*hie)+(R2*hie));
15 ri=(a);
16 //Output resistance in ohms
17 ro=1000*Rc;
18 b=(R1*R2)/(R1+R2);
19 //let

```

```

20 i1=1;
21 ib=i1*b/(b+hie);
22 ic=hfe*ib;
23 //output voltage Vo
24 Vo=(-Rc*ic);
25 Rt=Vo/i1*1000;
26 //Feedback factor F
27 F=1+(Rt*Bg);
28 //closed loop gain Rtf
29 Rtf=Rt/F;
30 //closed loop input resistance rif
31 rif=ri/F;
32 //closed loop output resistance rof
33 rof=ro/F;
34 printf("RESULTS\n");
35 printf("closed-loop gain ,Rtf=%1.2fKohms\n",Rtf);
36 printf("closed-loop input resistance rif=%2.0f Ohms\n
n",1000*rif);//in ohms
37 printf("closed-loop output resistance rof=%d Ohms",
rof);

```

---

#### Scilab code Exa 4.4 series voltage feedback circuit

```

1 //caption:series voltage feedback circuit
2 //given in ohms
3 R1=10000;
4 R2=2000;
5 Rc=2000;
6 //transistor parameters in Ohms
7 hie=1000;//in ohms
8 hfe=100;
9 //loop gain Avf
10 Avf1=(R1+R2)/R2;//there is corrected equation.in
text book,it needs a correction
11 Bv=1/Avf1;

```

```

12 //forward voltage gain Av
13 Av=(0.5)*hfe*Rc/hie;
14 //feedback factor F
15 F=(1+Av*Bv);
16 //closed loop gain Avf
17 Avf=Av/F;
18 //input resistance ri
19 ri=2*hie;
20 //input resistance after feed back rif
21 rif=ri*F;
22 //output resistance ro
23 ro=Rc;
24 //output resistance after feedback rof
25 rof=ro/F;
26 printf("RESULTS\n");
27 printf("(i)voltage amplification Avf=%1.2f, This
    accords with the previous value of Avf=%d\n",Avf,
    Avf1);
28 printf("(ii)input resistance after feed back rif=%2
    .1fKohms\n",rif/1000);//to convert ohms to Kohms
29 printf("(iii)input resistance after feed back rof=
    %dKohms\n",rof);//to convert ohms to Kohms

```

---



## Chapter 5

# MORE ABOUT FEEDBACK AMPLIFIERS

Scilab code Exa 5.1 Voltage shunt feedback circuit

```
1 //caption:shunt voltage feedback circuit
2 //example5.1
3 printf(" Given :");
4 printf("R=10 Kohms ,\nR1=20Kohms ,\nR2=5Kohms ,\n hfe
   =100Kohms , hie=1Kohm ,\n Rc=1Kohm");
5 R=10000;
6 R1=20000; //in ohms
7 R2=5000;
8 Rc=1000;
9 hfe=100;
10 Bg=-1/R;
11 hie=1000;
12 printf(" Therefore Bg=%1.5 f\n",Bg);
13 printf("RT=input current coupling factor*- hfe*
   effective cdollector resistance\n");
14 printf("RT=(R1 || R2 || R) / ((R1 || R2 || R)+hfe) * hfe *(Rc || R)
   \n");
15 a=(R1*R2*R) / ((R1*R) + (R*R2) + (R1*R2));
16 b=(Rc*R) / (Rc+R);
```

```

17 RT=(-hfe*a*b)/(a+hie)/1000;
18 printf("RT=%2.1fKohms\n",RT);
19 c=1+(RT*1000*Bg);
20 d=(1/R1)+(1/R2)+(1/R)+(1/hie);
21 Zi=1/d;
22 Zo=b;
23 RTf=RT/c;
24 rif=Zi/c;
25 rof=Zo/c;
26 printf("RESULTS:\n");
27 printf("RT=%2.1fKohms\n",RT);
28 printf("Zi=%3.1fohms\n",Zi);
29 printf("Zo=%dohms\n",Zo);
30 printf("Closed-loop gain ,RTf=%1.2fKohms\n",RTf);
31 printf("Closed-loop input resistance ,rif=%dohms\n",
    rif);
32 printf("Closed-loop output resistance ,rof=%dohms\n",
    rof);

```

---

### Scilab code Exa 5.2 amplifier parameters

```

1 //caption:amplifier parameters
2 //given values of resistances
3 R1=10000;//in ohms
4 R2=2000;//in ohms
5 Rc=2000;//in ohms
6 hie=1000;//in ohms
7 hfe=100;
8 ri1=2*hie;
9 //unloaded feed-backfraction Bv
10 Bv=R2/(R1+R2);
11 disp("Av=ri1/(ri1+(R1||R2))*(Vo/Via)");
12 disp('Av=(1*hfe/2)*(ri1/(ri1+(R1||R2)))*(Rc||(R1+R2)
    )/hie');
13 Av=(1*hfe/2)*(ri1/(ri1+(R1*R2/(R1+R2))))*(Rc*(R1+R2)

```

```

    /(Rc+R1+R2))/hie;
14 C=1+(Av*Bv);
15 //open-loop input resistance ri
16 ri=ri1+(R1*R2/(R1+R2));
17 //open-loop output resistance ro
18 ro=Rc*(R1+R2)/(Rc+R1+R2);
19 //closed-loop gain ,Avf
20 disp('closed-loop gain , Avf=Av/C, where C=1+Av*Bv');
21 Avf=Av/C;
22 //closed-loop input resistance ,rif
23 disp('closed-loop input resistance , rif=ri*C');
24 rif=ri*C;
25 //closed-loop output resistance , rof
26 disp('closed-loop output resistance , rof=ro/C, where
    C=1+Av*Bv');
27 rof=ro/C;
28 printf("RESULTS:\n");
29 printf("Closed-loop gain ,Avf=%1.2f( previously 5.66)\n",Avf);
30 printf("Closed-loop input resistance ,rif=%2.1f Kohms
    (previously 35.3Kohms)\n",rif/1000);//divided by
    1000 to convert to Kohms
31 printf("Closed-loop output resistance ,rof=%3.0f Ohms
    (previously 113 ohms)\n",rof);

```

---

#### Scilab code Exa 5.4 closed loop current gain input output resistance

```

1
2 //example5.4
3 //Shunt circuit feedback configuration//given
4 R1=10000;//in ohms
5 R2=2000;//in ohms
6 Rc1=5000;//in ohms
7 hie=1000;//in ohms
8 hfe=100;

```

```

 9 //unloaded feedback fraction B1
10 B1=R2/(R1+R2);
11 disp('open loop forward current amplification A1=io/
      i ');
12 iia=1;//let
13 disp('ib=input-current coupling factor*iia ');
14 disp('ib=(R1+R2)*iia/(R1+R2+hie) ');
15 ib=(R1+R2)*iia/(R1+R2+hie);
16 disp('V2=(-hfe)*(Rc1||ri2)*ib ');
17 disp('ri2=hie+(1+hfe)*(R1||R2) ');
18 ri2=hie+(1+hfe)*(R1*R2/(R1+R2));
19 V2=(-hfe)*(Rc1*ri2/(Rc1+ri2))*ib;
20 disp('io/V2=C=-hfe/(hie+(1+hfe)*(R1||R2)) ');
21 C=-hfe/(hie+(1+hfe)*(R1*R2/(R1+R2)));
22 disp('Open loop current gain=A1=io/i=(ib/i)*(V2/ib)
      *(io/V2) ');
23 A1=(ib/iia)*(V2/ib)*(C);
24 disp('Open-loop input resistance , ri=(R1+R2)||hie ');
25 ri=(R1+R2)*hie/(R1+R2+hie);
26 disp('Open-loop output resistance ro as seen by the
      load resistance Rc2 is infinitely large since the
      load is in series with the infinitely large
      collector resistance of the transistor. ');
27 disp('Closed-loop current gain, A1f=A1/(1+A1*B1) ');
28 A1f=A1/(1+A1*B1);
29 disp(A1f);
30 disp('Closed-loop input resistance , rif=ri/(1+A1*B1) '
      );
31 rif=ri/(1+A1*B1);
32 disp(rif);
33 disp('Closed-loop output resistance , rof=ro(1+A1*B1) ,
      since ro is infinitely large ,the rof is also
      large infinitely .. ');
34 printf(" RESULTS:\n\n");
35 printf(" A1f=%1.2f ,\n\n",A1f);
36 printf(" rif=%2.1f ohms,\n\n",rif);//approximately
37 printf(" rof=infinite\n\n");

```

### Scilab code Exa 5.5 Voltage shunt feedback circuit

```
1 //important:In this example ro1 value is
   contradicting in text book,sometimes they used 1
   K0hm and sometimes 4Kohms,the code below used ro1
   =2KOhms as specified in question
2 //example5.5
3 //caption:Shunt voltage feedback circuit
4 //input resistance ri1
5 ri1=1000;//in ohms
6 //output resistance ro1
7 ro1=2000;//in ohms
8 //trans resistance Kr
9 Kr=-10^6;//in ohms
10 //Feedback resistor R
11 R=10000;//in ohms
12 //current source Jg
13 Jg=0.001;//in Amps
14 //source internal resistance rg
15 rg=2000;//in ohms
16 //load resistance rl
17 rl=5000;//in ohms
18 //unloaded feedback fraction
19 Bg=-1/R;
20 disp('Unloaded feedback fraction ,Bg=-1/R');
21 disp('open loop gain ,RTs=Vo/Jg=input current
   coupling factor*Kr*output voltage coupling factor
   ');
22 RTs=((rg*R/(rg+R))/(ri1+(rg*R/(rg+R))))*Kr*((rl*R/(
   rl+R))/(ro1+(rg*R/(rg+R))));
23 printf("RTs=%d ohms",RTs/1000);
24 disp('Open-loop input resistance ,ris=rg ||R|| ri1 ');
25 ris=rg*R*ri1/(rg*R+R*ri1+rg*ri1);
26 printf("\nris=%d ohms",ris);
```

```

27 disp('Open-loop output resistance , ros=ro1 || R || rl ');
28 ros=rl*R*ro1/(rl*R+R*ro1+rl*ro1);
29 printf(" ros=%d Ohms", ros);
30 disp(' Closed-loop gain , RTf=RTs/(1+RTs*Bg) ');
31 RTfs=RTs/(1+RTs*Bg);
32 printf("\nRTfs=%1.2 f Kohms", RTfs/1000);
33 disp(' Closed-loop input resistance , rifs=ris/(1+RTs*
      Bg) ');
34 rifs=ris/(1+RTs*Bg);
35 printf(" rifs=%d Ohms", rifs);
36 disp(' Closed-loop output resistance , rof=ros/(1+RTs*
      Bg) ');
37 rofs=ros/(1+RTs*Bg);
38 printf(" rofs=%2.1 f Ohms", rofs);
39 printf(" RESULTS:\n");
40 Vout=RTfs*Jg;
41 printf("\n(i)The output voltage=%1.2 f V", Vout);
42 disp(' rifs=rif*rg/(rif+rg)==>rif=rg*rifs/(rg-rifs) ')
      ;
43 rif=rg*rifs/(rg-rifs);
44 printf("\n(ii)The input resistance seen by the
      actual signal source is %2.1 f Ohms", rif);
45 disp(' rofs=rof*rl/(rof+rl)==>rof=rl*rofs/(rl-rofs) ')
      ;
46 rof=rl*rofs/(rl-rofs)
47 printf("\n(iii)The output resistance seen by the
      load is %2.1 f Ohms", rof);
48 printf("(iV)The closed-loop gain of the amplifier");
49 disp(' RTf=Vo/i1 , where ')
50 disp(' i1=current coupling factor*Jg=rg*Jg/(rg+rif) ')
      ;
51 RTf=(rg+rif)*RTfs/rg;
52 printf("(iV)The closed-loop gain of the amplifier
      circuit is %1.2 f Kohms", RTf/1000); //divided by
      1000 to convert ohms to Kohms.

```

---

Scilab code Exa 5.6 feed back fraction

```
1
2 //given
3 //current gain of transistor A
4 A=100;
5 //upper half-power frequency fh
6 fh=2*(10^6); //in Hz
7 //closed-loop current gain Acl
8 Acl=10;
9 //band width BW
10 BW=10*(10^6); //in Hz
11 //gain bandwidth product ABWp
12 ABWp=Acl*BW; //in Hz
13 //gain bandwidth product of transistor ABWpt
14 ABWpt=A*fh; //in Hz
15 printf("The gain bandwidth product of the transistor
        is %d*(10^8), which is greater the minimum
        required i.e. %d*(10^8) and therefore the
        transistor is suitable\n", ABWpt/(10^8), ABWp
        /(10^8))
16 disp(' Acl=A/(1+A*B) ==> B =(1/A)*(A/Acl-1)\n');
17 B =(1/A)*(A/Acl-1);
18 printf("Required value of B is %1.2f", B);
```

---

## Chapter 6

# THE OP AMPS BASIC IDEAS AND CIRCUITS

Scilab code Exa 6.1 design values of an inverting amplifier

```
1
2 R1=1;
3 //voltage gain of an inverting amplifier Av
4 Av=-100;
5 printf("Av=(-R2/R1)\nTherefore R2=-Av*R1");
6 R2=-Av*R1;
7 printf("\nRESULTS:\n");
8 printf("The design values are R1=%d Kohms and R2=%d
    Kohms",R1,R2);
```

---

Scilab code Exa 6.2 gain of a negative feedback amplifier

```
1
2 //Typical 741 type op-amp Differential gain A
3 A=200000;
4 R1=1; //in Kohms
```



```
5 R2=10;
6 //Circuit gain in negative feedback Av
7 Av=- (R2/R1)*(A*(R1/(R1+R2)))/(1+(A*(R1/(R1+R2)))));
8 printf("Circuit gain Av=%2.4f",Av);
```

---

#### Scilab code Exa 6.4 non inverting amplifier

```
1
2 Av=100;
3 printf("Av=1+(R1/R2)\n");
4 //Let R2=1 Kohms
5 R2=1; //in Kohms
6 printf("R1=(Av-1)*R2");
7 R1=(Av-1)*R2;
8 printf("\nRESULTS:\n");
9 printf("The design values are R1=%d Kohms and R2=%d
    Kohm",R1,R2);
```

---

# Chapter 7

## OP AMP NON IDEALITIES

Scilab code Exa 7.1 Output voltage

```
1
2 A=200000;
3 //Offset voltage Vos in mV
4 Vos=5;
5 //output voltage Vout=A*Vos in mV
6 printf("\nVout=A*Vos\n");
7 Vout=A*Vos;
8 printf("RESULTS:\n")
9 printf("The maximum output voltage Vout=%d V",Vout
    /1000);//in volts
```

---

Scilab code Exa 7.2 output offset voltage

```
1
2 printf("A=1+(R1/R2)\n");
3 A=10;
4 //out put voltage of an op-amp owing to voltage
    offset effects Vout
```

```

5 printf("Vout=-A*Vos");
6 Vos=5; //in mV
7 Vout=-A*Vos;
8 printf("\nRESULTS:\n");
9 printf("Output offset voltage is Vout=%d mV",Vout);

```

---

#### Scilab code Exa 7.4 inverting voltage amplifier

```

1 Av=-10;
2 disp('Av=-(R2/R1)*(A*B/1+A*B), where A-differential
      gain and B=R1/R1+R2');
3 disp('When A*B>>1,Av=-(R2/R1)=Av1');
4 Av1=Av;
5 disp('abs(A)>>1+(R2/R1)=1+abs(Av1)');
6 A=1+abs(Av1);
7 disp('Because the cross over point occurs at a
      significantly higher frequency than the dominant
      frequency at 10Hz');
8 disp('The phase angle of A is very close to -90
      degrees=%pi/2 radians');
9 disp('Using the j-notation the gain A at the
      crossover point is equal to %i*11');
10 A=%i*11;
11 disp('1+abs(Av1)=(R1+R2)/R1');
12 Av=(-10)*(A/(1+abs(Av1)))/(1+(A/(1+abs(Av1))));
13 Av2=abs(Av);
14 M=Av/Av2;
15 printf("The closed-loop gain at the cross over
      point is thus reduced by a factor %f and
      therefore point corresponds to upper half-power
      frequency which is 90KHz",M)
16 disp('Therefore fh=90KHz, fl=0KHz');
17 fh=90; //in KHz
18 fl=0; //in KHz
19 disp('Bandwidth BW=fh-fl');

```

```
20 BW=fh-f1;
21 printf(" RESULTS:\n");
22 printf(" The closed-loop bandwidth is %d KHz",BW);
```

---

### Scilab code Exa 7.5 Full power bandwidth frequency

```
1
2 SR=0.5*(10^6);
3 //given operating power supplies +-12V
4 printf("\nGiven operating power supplies +-12V\n");
5 printf("For 741 op-amp, the output can work typically
        to within 1V of the power supplies.\nSo, Vom=11V\n
        n");
6 Vom=11; //in volts
7 printf(" f=(1/(2*pi))*(SR/Vom)\n");
8 f=(1/(2*pi))*(SR/Vom);
9 printf("RESULTS:\n");
10 printf(" Full-power bandwidth frequency f=%d Hz",f);
```

---

## Chapter 8

# SELECTED OP AMP APPLICATIONS

Scilab code Exa 8.1 basic differential amplifier

```
1
2 Adm=100;
3 printf("Gain of an difference amplifier Adm=(1+(R2/
   R1))/(1+(R3/R4))\n");
4 printf("Let (R2/R1)=A and (R3/R4)=B\n");
5 printf("Therefore Adm=(1+A)/(1+B)\n");
6 printf("A=Adm,");
7 printf(" gives B=1/Adm\n");
8 A=Adm;
9 B=1/Adm;
10 printf("By suitable selection of resistors say R1=R2
   =1 Kohm");
11 R1=1; //in Kohm
12 R3=1;
13 R2=Adm*R1;
14 R4=Adm*R3;
15 printf("\nRESULTS:\n");
16 printf("Reasonable set of resistors R1=%d Kohm,R2=%d
   Kohms ,R3=%d Kohm,R4=%d Kohms." ,R1 ,R2 , R3 , R4 );
```

---

**Scilab code Exa 8.2** Instrumental amplifier

```
1
2 Adm=100;
3 printf("Adm=100=10*10, therefore it requires (R2/R1)
   =10 Kohms and (R4/R3)=10 Kohms\n");
4 printf("Therefore if R1=R3=10 Kohms, then R2=R4=100
   kohms\n");
5 R1=10; //in Kohms
6 R2=100;
7 R3=10;
8 R4=100;
9 printf("Adm=(1+2(Rb/Ra))*R4/R3\n");
10 printf("(Rb/Ra)=B\n");
11 printf("Adm=(1+2*B)*R4/R3\n");
12 B=((Adm/(R4/R3))-1)/2;
13 printf("Rb/Ra=%1.1f\n", B);
14 printf("If Ra=10 Kohms\n");
15 Ra=10; //in kohms
16 Rb=B*Ra;
17 printf("\nRESULTS:\n");
18 printf("The value of resistors are R1=%d Kohms, R2=%d
   Kohms, R3=%d Kohms, R4=%d Kohms, Ra=%d Kohms, Rb=%d
   Kohms", R1, R2, R3, R4, Ra, Rb);
```

---

**Scilab code Exa 8.3** wein bridge oscillator

```
1 //caption:wein bridge oscillator
2 //To design a wein bridge oscillator of frequency fo
   =10KHz
3 fo=10000; //in Hz
```

```

4 printf(" Capacitance C, Resistance R and Frequency fo
   are related as  $C \cdot R = 1 / (2 \cdot \pi \cdot f_o)$  \n");
5 printf(" If  $C \cdot R = A$  \n");
6 A = 1 / (2 * %pi * fo);
7 C = 0.01 * (10^-6); //in farads
8 R = A / C; //in ohms
9 B = R / 1000; //to convert to Kohms
10 printf(" Taking C=0.01 microfarad , we get R=%1.2 f
   Kohms \n", B); //in Kohms
11 printf(" Gain of a non-inverting amplifier should be
   3 i.e.  $A_v = 1 + (R_1 / R_2) = 3$  \n");
12 printf(" This gives  $(R_1 / R_2) = 2$ , by selecting R2=10
   Kohms, we get R1=20 Kohms \n");
13 R2 = 10;
14 R1 = 20; //in Kohms
15 printf(" The gain must be restricted between 2.8 to
   3.2, by selecting proper resistors Ra and Rb such
   that  $R_1 = R_a || R_b$  this can be achieved. \n");
16 printf(" These values of Ra and Rb comes out to be Ra
   =22Kohms and Rb=220Kohms \n");
17 printf(" RESULTS: \n");
18 printf(" design values are R=%1.2 f Kohms, C=0.01
   microFarad , Ra=22 Kohms, Rb=220 Kohms \n", B);

```

---

## Chapter 9

# FURTHER OP AMP APPLICATIONS

Scilab code Exa 9.1 Design of phase shifter

```
1 //caption:Design of phase shifter
2 //example9.1
3 disp(" Given frequency fo=10 KHz,Vrms=5 V, phi=10
      degrees\n");
4 disp(" Taking A=C3*R4\n");
5 phi=10;//in degrees
6 fo=1000;//in Hz
7 disp(" phi=180-2(atan(2*%pi*f*A))");
8 A=tan((180-10)*%pi/(180*2))/(2*fo*%pi);
9 printf(" Therefore A=C3*R4=%f sec.\n",A);
10 R4=10000;//let (in ohms)
11 printf("C3 and R4 values are selected such that
      their product equals or greater than %f, The
      above values are preferable for low cost and bias
      compensation",A);
12 C3=A/R4;
13 printf("\nC3=%f uF",C3*10^6);
14 disp("To lower the cost of design ,the preferred
      value is C31=0.22uF");
```



```

15 C31=0.22; //let Such that C31>C3
16 disp(" since ,C31*R4>A,C31 can be preferred")
17 printf(" Similarly , R1 and R2 values should be of
    Good matching to obtain accurate unity gain
    modulus ");
18 printf("RESULTS:\n");
19 printf(" (i) Resistors , R1=R2=10Kohms\n");
20 printf(" (iii) R4=%d Kohms\n",R4/1000); //divided by
    1000 to display in Kohms
21 printf(" (iii) Capacitor , C3=%1.2 f uF\n",C31);

```

---

#### Scilab code Exa 9.2 design of non inverting amplifier

```

1 //caption:design of non inverting amplifier
2 //to design a non inverting amplifier
3 //mid-band gain Av
4 Av=100;
5 //input impedance Zin
6 Zin=1000000; //in ohms
7 //cut-off frequencies fl1 and fl2
8 fl1=10; //in Hz
9 fl2=10; //in Hz
10 //From problem it follows
11 R3=Zin;
12 disp(' fl2 =1/(2*%pi*C2*R3) ');
13 disp(' C2=1/(2*%pi*fl2*R3) ');
14 C2=1/(2*%pi*fl2*R3);
15 disp(' Av=1+(R2/R1) ');
16 disp(' Bias compensation can also be obtained by
    taking R2=R3=1MHz ');
17 R2=R3;
18 disp(' R1=1/(Av-1)*R2 ');
19 R1=1/(Av-1)*R2;
20 printf(' R1=%1.1 f Kohms, preferred and standard value
    is 10Kohms\n',R1/1000);

```

```

21 R=R1;
22 R1=10000; //in ohms
23 disp('f11=1/(2*%pi*C1*R3)');
24 disp('C1=1/(2*%pi*f11*R3)');
25 C1=1/(2*%pi*f11*R1);
26 printf('RESULTS: Design summary\n');
27 printf('R1=%1.1f Kohms, preferred and standard value
        is 10Kohms\n',R/1000);
28 printf('R2=R3=%d Mohm\n',R3/10**6); //divided by 10^6
        to convert to Mohms
29 printf('C1=%1.2f uF but standard and preferred value
        is 2.2 uF\n',C1*(10**6));
30 printf('C2=%2.1f nF but standard and preferred value
        is 22 uF\n',C2*(10**9));

```

---

### Scilab code Exa 9.3 low pass second order filter

```

1 //caption:low pass second order filter
2 //to design a low pass second order filter
3 //since it is butterworth filter
4 Q=1/sqrt(2);
5 Wo=100; //in rad/sec.
6 H=-2;
7 bo=H;
8 a1=1/(Q*Wo);
9 a2=1/(Wo**2);
10 printf("It is convenient to choose R=100Kohms\n");
11 R=100; //in Kohms
12 R3=R;
13 R4=R;
14 R1=R4/(-bo);
15 a3=R3+R4+((R3*R4)/R1);
16 C5=(a1/a3)*(10**6); //in uF
17 C2=a2/(R3*R4*C5)*(10**9); //in nF
18 printf("RESULTS:\n");

```

```
19 printf("R=%dKohms, \ nR1=%dKohms, \ nR3=%dKohms, \ nR4=
    %dKohms, \ nC2=%1.3 f nF, \ nC5=%2.1 fuF" , R , R1 , R3 , R4 , C2
    , C5);
```

---