

Scilab Textbook Companion for  
Radio - Frequency And Microwave  
Communication Circuits  
by D. K. Mishra<sup>1</sup>

Created by  
Pralhad Das  
B.Tech  
Others  
IIT Bombay  
College Teacher  
Prabhu Ramchandran  
Cross-Checked by

May 23, 2016

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Radio - Frequency And Microwave Communication Circuits

**Author:** D. K. Mishra

**Publisher:** John Wiley & Sons Inc., New Jersey

**Edition:** 2

**Year:** 2004

**ISBN:** 0-471-47873-3

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
2 communication systems	5
3 transmission lines	18
4 electromagnetic fields and waves	27
5 resonant circuits	32
6 impedance matching networks	39
7 impedance transformers	44
8 two port networks	46
9 filter design	53
10 signal flow graphs and their applications	61
11 transistor amplifier design	64
12 oscillator design	69
13 detectors and mixers	77

# List of Scilab Codes

Exa 2.1	1	5
Exa 2.2	2	6
Exa 2.3	3	6
Exa 2.4	4	7
Exa 2.5	5	7
Exa 2.6	6	8
Exa 2.7	7	9
Exa 2.8	8	10
Exa 2.9	9	11
Exa 2.10	10	12
Exa 2.11	11	12
Exa 2.12	12	14
Exa 2.13	13	15
Exa 2.14	14	16
Exa 2.15	15	16
Exa 3.1	1	18
Exa 3.2	2	19
Exa 3.3	3	19
Exa 3.5	5	20
Exa 3.6	6	20
Exa 3.7	7	21
Exa 3.8	8	22
Exa 3.9	9	22
Exa 3.10	10	23
Exa 3.11	11	23
Exa 3.12	12	24
Exa 3.13	13	24
Exa 3.14	14	25

Exa 3.15	15	25
Exa 4.3	3	27
Exa 4.4	4	27
Exa 4.5	5	28
Exa 4.6	6	28
Exa 4.7	7	28
Exa 4.10	10	29
Exa 4.11	11	30
Exa 4.12	12	30
Exa 5.1	1	32
Exa 5.2	2	33
Exa 5.3	3	33
Exa 5.5	5	34
Exa 5.6	6	35
Exa 5.7	7	36
Exa 5.8	8	36
Exa 5.9	9	37
Exa 5.10	10	37
Exa 6.1	1	39
Exa 6.3	3	40
Exa 6.5	5	40
Exa 6.6	6	41
Exa 6.7	7	41
Exa 6.8	8	42
Exa 6.9	9	42
Exa 6.10	10	43
Exa 7.1	1	44
Exa 7.5	5	44
Exa 8.1	1	46
Exa 8.2	2	46
Exa 8.3	3	47
Exa 8.5	5	47
Exa 8.6	6	48
Exa 8.7	7	49
Exa 8.9	9	49
Exa 8.10	10	50
Exa 8.14	14	50
Exa 8.17	17	51

Exa 8.19	19	51
Exa 9.2	2	53
Exa 9.3	3	53
Exa 9.4	4	54
Exa 9.5	5	54
Exa 9.6	6	55
Exa 9.7	7	55
Exa 9.8	8	56
Exa 9.9	9	57
Exa 9.10	10	58
Exa 9.11	11	58
Exa 9.12	12	59
Exa 9.13	13	60
Exa 10.10	10	61
Exa 10.11	11	62
Exa 11.1	1	64
Exa 11.2	2	64
Exa 11.3	3	65
Exa 11.4	4	66
Exa 11.5	5	67
Exa 11.6	6	67
Exa 12.1	1	69
Exa 12.2	2	69
Exa 12.4	4	70
Exa 12.5	5	70
Exa 12.6	6	71
Exa 12.7	7	71
Exa 12.8	8	72
Exa 12.11	11	73
Exa 12.12	12	73
Exa 12.13	13	74
Exa 13.1	1	77
Exa 13.2	2	77
Exa 13.3	3	78
Exa 13.5	5	78

# Chapter 2

## communication systems

Scilab code Exa 2.1 1

```
1 // data given in question
2 // diameter of dish (m)
3 d=30;
4 //frequency of radiation (Hz)
5 f=4*10^9;
6 // speed of light(m/s)
7 c=3*10^8;
8 // efficiency of aperture
9 e=0.6;
10 //data print
11 printf("\nd=30 m\ tf=4 GHz\ te=0.6\n")
12 // equation and result
13 printf("\nresult:-")
14 wavelength=c/f
15 printf("\nwavelength of radiating signal=c/f= %.3 f m
    ",wavelength)
16 A=%pi*d^2/4
17 printf("\narea of aperture A=pi*d^2/4=%.4 f m^2",A)
18 G=4*pi*A*e/wavelength^2
19
20 printf("\nantenna gain G=4*pi*A*e/wavelength^2 =%.3 f
```



```

    ",G)
21 printf("=%0.0 f dB",10*log10(G))
22 BW=65*wavelength/d
23 printf("\nhalf power beam width BW=65*wavelength/d=%0
    .4 f degree",BW)

```

---

### Scilab code Exa 2.2 2

```

1 //impedance of transmission line
2 Za=73
3 //impedance of antenna
4 Zo=50
5 //radiation efficiency
6 ecd=1
7 I=integrate('(sin(x))^4','x',0,%pi)*2*%pi
8 Do=4*%pi/I
9 printf("\nDo=%0.4 f=%0.4 f dB",Do,10*log10(Do))
10 //voltage reflection coefficient
11 F=(Za-Zo)/(Za+Zo)
12 printf("\nvoltage reflection coefficient\nF=(Za-Zo)
    /(Za+Zo)=%f",F)
13 //mismatch efficiency of antenna
14 er=1-F^2
15 printf("\nmismatch efficiency of antenna\ner=1-F^2=%0
    .4 f=%0.4 f dB",er,10*log10(er))
16 //overall gain
17 Go=10*log10(Do)+10*log10(er)+10*log10(ecd)
18 printf("\noverall gain\nGo=Do+er+ecd=%0.4 f dB",Go)

```

---

### Scilab code Exa 2.3 3

```

1 printf("\nunit vector along the polarization of
    incident wave is ui=[1 0 0]")

```

```

2 ui=[1 0 0];
3 printf("\nunit vector along the antenna polarization
      ua=[1 1 0]*(1/sqrt(2))\n")
4 ua=[1 1 0]*(1/sqrt(2));
5 d=ui*ua'
6 printf("\npolarization loss factor |ui*ua|^2=%0.2f",d
      ^2)
7 printf("=%0.2f dB",10*log10(d^2))

```

---

#### Scilab code Exa 2.4 4

```

1 // data
2 // output of high power amplifier (W)
3 Pt=500;
4 //efficiency
5 e=0.8;
6 //gain of transmitting antenna(60dB=10^6)
7 G=10^6;
8 // data print
9 printf("\nPt=500 W\te=0.8\tG=60 dB\n")
10 //equations and result
11 printf("\nresult:-")
12 Pant=e*Pt
13 printf("\noutput power of antenna Pant=%0.2f W",Pant)
14 L=Pt/Pant
15 printf("\ninput/output power ratio L=Pt/Pant=%0.2f=%0
      .4f dB",L,10*log10(L))
16 EIRP=Pt*G/L
17 printf("\nEIRP =%0.4f dBw",10*log10(Pt)+10*log10(G)
      -10*log10(L))
18 printf("\nEIRP=Pt*G/L=%0.2e W",EIRP)

```

---

#### Scilab code Exa 2.5 5

```

1 // data in question
2 //distance of satellite from earth surface(m)
3 R=35860000;
4 //operating frequency of satellite(Hz)
5 f=4*10^9;
6 c=3*10^8;
7 //data print
8 printf("\nR=35,860 km\tf=4 GHz\n")
9 //equations and result
10 printf("\nresult:-")
11 wavelength=c/f
12 printf("\nwavelength of signal = c/f = %.3f m",
        wavelength)
13 space_loss_ratio=(wavelength/(4*pi*R))^2
14 printf("\nspace loss ratio=(wavelength/(4*pi*R))^2 =
        %.2e",space_loss_ratio)
15 printf(" = %.4f dB",10*log10(space_loss_ratio))

```

---

### Scilab code Exa 2.6 6

```

1 //date in question
2 //transmitting antenna gain (dB)
3 Gt=37
4 // ground station antenna gain (dB)
5 Gr=45.8
6 //frequency of signal
7 f=20*10^3
8 //distance from ground station
9 R=36941.031
10 //data print
11 printf("\nGt=37\tGr=45.8\tf=20GHz\tR=36941.031km\n")
12 //equation and result
13 printf("\nresult:-")
14 Pt=10*log10(2000)
15 printf("\npower transmitted\n\tPt=10*log10(2000)=%.4

```

```

    f dB\n",Pt)
16 Pr=Pt+Gt+Gr-20*log10(f*R)-32.4418 //Pt,Pr in dBm
    and Gt,Gr in dB f in MHz and R in km
17 printf("\npower received at earth station\n\tPr=Pt+
    Gt+Gr-20*log10(f*R)-32.4418=%f dBm",Pr)
18 Gt=0 //Gt in dB
19 Gr=0 //Gr in dB
20 Pr=Pt+Gt+Gr-20*log10(f*R)-32.4418
21 printf("\nif two antennas are isotropic \n\tPr=%f
    dBm=%.4emW",Pr,10^(Pr/10))

```

---

### Scilab code Exa 2.7 7

```

1 //data in question
2 // input power to the antenna(W)
3 Ps=2;
4 //reflection coefficient of transmitting antenna
5 Yt=0.1
6 //reflection coefficient of receiving antenna
7 Yr=0.2
8 //distance between two antennas
9 //consider
10 A=10^(-5)
11 R=100*(A)
12 //maximum directivity of receiving antenna(20 dB =
    10^(20/10))
13 Gr=10^(20/10)
14 //maximum directivity of transmitting antenna(16dB
    =10^(16/10))
15 Gt=10^(16/10)
16 //data print
17 printf("\nPs=2 W\tYt=0.1\tYr=0.2\tR=100 \tGr=20 dB\
    tGt=16 dB\n")
18 //equations and result
19 // power transmitted in the forward direction

```

```

20 printf("\nresult:-")
21 Pt = (1-Yt^2)*Ps
22 printf("\npower transmitted in the forward direction
        \n\tPt = (1-Yt^2)*Ps=%0.2 f W",Pt)
23 //Friis transmission equation
24 Pr=Pt*(A/(4*pi*R))^2*Gr*Gt
25 printf("\nFriis equation \n\tPr=Pt*(    /(4*pi*R))^2*
        Gr*Gt=%0fW",Pr)
26 printf(" =%0.0 f mW",Pr*1000)
27 //power delivered to receiver
28 Pd=(1-Yr^2)*Pr
29 printf("\npower delivered to receiver\n\tPd=(1-Yr^2)
        *Pr=%0.1 f mW",Pd*1000)

```

---

#### Scilab code Exa 2.8 8

```

1 //data in question
2 //power transmission(W)
3 Pt=25000
4 //operating frequency(Hz)
5 f=12*10^9
6 //gain of transmitter antenna(25dB)
7 Gt=10^(25/10)
8 //gain of receiver antenna(25dB)
9 Gr=10^(25/10)
10 //distance between two radars(m)
11 R=10000
12 //surface area of target radar(m^2)
13 A=8
14 c=3*10^8
15 //data print
16 printf("\nPt=25 kW\tf=12 GHz\tGt=Gr=25 dB\tR=10 km\
        tA=8 m^2\n")
17 //equation and result
18 printf("\nresult:-")

```

```

19 //wavelength L
20 L=c/f
21 printf("\nwavelength of signal L=c/f=%.3 f m",L)
22 Pr=Gr*Gt*Pt*A*L^2/(4*pi*(4*pi*R^2)^2)
23 printf("\nreceived power \nPr=Gr*Gt*Pt*A*L^2/(4*pi
      *(4*pi*R^2)^2)= %.2eW",Pr)
24 printf(" = %.2 f pW",Pr*10^12)

```

---

### Scilab code Exa 2.9 9

```

1 //data in question
2 //noise power at Th=290 K(dBm)
3 P1=-70
4 Th=290
5 //noise power at Tc=77 K(dBm)
6 P2=-75
7 Tc=77
8 //given noise temperature(K)
9 Ts=450
10 //frequency band B
11 B=1.5*10^9-500*10^6
12 //power gain of amplifier(10dB=10)
13 G=10
14 //boltzamn constant
15 k=1.38*10^(-23)
16 //data print
17 printf("\nP1=-70 dBm at Th=290 K\tP2=-75 dBm at Tc
      =77 K \tTs=450 K G=10\n")
18 //equation and result
19 printf("\nresult:-")
20 //Y-factor(Y=P1/P2 = (P1-P2)dBm)
21 Y=10^((P1-P2)/10)
22 printf("\n Y-factor = 10^((P1-P2)/10) = %.4 f",Y)
23 //equivalent noise temperature
24 Te=(Th-Y*Tc)/(Y-1)

```

```

25 printf("\nequivalent noise temperature\nTe=(Th-Y*Tc)
    /(Y-1)=%.2 f K",Te)
26 //noise power output of amplifier
27 Po=G*k*Ts*B+G*k*Te*B
28 printf("\nnoise power output\nPo=G*k*Ts*B+G*k*Te*B=%
    .4 e W",Po)
29 printf(" = %.4 f dBm\n",10*log10(Po*1000))

```

---

### Scilab code Exa 2.10 10

```

1 //data in question
2 //noise figure(dB)
3 NF=3.5
4 //band width(Hz)
5 B=(12-10)*10^9
6 //amplifier gain
7 G=10^(20/10)
8 To=290
9 k=1.38*10^-23
10 //data print
11 printf("\nNF=3.5 dB\tB=2 GHz \tG=20dB\n")
12 //equations and result
13 //noise factor
14 F=10^(NF/10)
15 printf("\nnoise factor\nF=10^(NF/10)=%f",F)
16 No=F*k*To*B*G
17 printf("\noutput noise power\nNo=F*k*To*B*G=%
    .4 e W",
    No)
18 printf(" = %.1 f dBm",10*log10(No*1000))

```

---

### Scilab code Exa 2.11 11

```

1 printf("\n\t(a) Find the noise figure of this
   cascaded system.")
2 printf("\n\t(b) What would be the noise figure if
   the amplifier were placed before the transmission
   line?\n")
3 // data in question
4 //ambient temperature(K)
5 Te=300
6 To=290
7 //noise temperature of amplifier(K)
8 Ta=150
9 k=1.38*10^-23
10 //band width(Hz)
11 B=100*10^6
12 //gain of amplifier
13 Gamp=10^(15/10)
14 // for transmission lines
15 Gline=1/10^0.2
16 //data print
17 printf("\nTe=300K\tTa=150K\tB=100MHz\tGamp=15dB\t
   tattenuation=2dB\n")
18 //equations and result
19 printf("\nresult:-")
20 //noise factor for amplifier
21 Famp=1+Ta/To
22 printf("\nFamp=1+Ta/To")
23 //noise for transmission lines
24 Fline=1+(1/Gline-1)*Te/To
25 printf("\nFline=1+(1/Gline-1)*Te/To")
26 Fcascaded=Fline+(Famp-1)/Gline
27 printf("\n(a)noise figure of cascaded system\n\t
   tFcascaded=Fline+(Famp-1)/Gline = %.4f",Fcascaded
   )
28 printf(" = %.4f dB",10*log10(Fcascaded))
29 Fcascaded=Famp+(Fline-1)/Gamp
30 printf("\n(b)if the amplifier is connected before
   the line\n\tFcascaded=Famp+(Fline-1)/Gamp = %.4f"
   ,Fcascaded)

```



```
31 printf(" = %.4f dB" ,10*log10(Fcascaded))
```

---

### Scilab code Exa 2.12 12

```
1 //data in question
2 //noise factor of A1
3 F1=10^(3/10)
4 //noise factor of A2
5 F2=10^(5/10)
6 //gain of amplifier A1
7 G1=10^(20/10)
8 //gain of amplifier A2
9 G2=10^(20/10)
10 //data print
11 printf("\nF1=3dB\tF2=5dB\tG1=G2=20dB\n")
12 //equation and result
13 printf("\nresult:-")
14 //overall gain of cascaded system
15 G=G1*G2
16 printf("\noverall gain of cascaded system\nG=G1*G2=
    %.2f",G)
17 printf(" = %.0f dB" ,10*log10(G))
18 //overall noise figure of cascaded system
19 F=F1+(F2-1)/G1
20 printf("\noverall noise of cascaded system\nF=F1+(F2
    -1)/G1 = %.6f",F) //some difference in result
    is due to approx in calculation
21 printf(" = %.3f dB" ,10*log10(F))
22 F=F2+(F1-1)/G2
23 printf("\noverall noise of cascaded system when
    order of amplifiers is changed\nF=F2+(F1-1)/G2 =
    %.6f",F)
24 printf(" = %.6f dB" ,10*log10(F))
```

---

### Scilab code Exa 2.13 13

```
1 //noise factor
2 F=10^(10/10)
3 //equation and result
4 printf("\nresult:-")
5 printf("\n(a)B=1MHz")
6 B=1
7 Pimds=-111+F+10*log10(B) //F in dB, B in MHz,
   Pidms in dBm
8 printf("\n\tPimds=-111+F+10*log10(B)\n\tPimds=%0.1 f
   dBm",Pimds)
9 printf(" = %0.2 e mW",10^(Pimds/10))
10 printf("\n(b)B=1GHz")
11 B=1000
12 Pimds=-111+F+10*log10(B) //F in dB, B in MHz,
   Pidms in dBm
13 printf("\n\tPimds=-111+F+10*log10(B)\n\tPimds=%0.1 f
   dBm",Pimds)
14 printf(" = %0.2 e mW",10^(Pimds/10))
15
16 printf("\n(c)B=10GHz")
17 B=10000
18 Pimds=-111+F+10*log10(B) //F in dB, B in MHz,
   Pidms in dBm
19 printf("\n\tPimds=-111+F+10*log10(B)\n\tPimds=%0.1 f
   dBm",Pimds)
20 printf(" = %0.2 e mW",10^(Pimds/10))
21 printf("\n(d)B=1kHz")
22 B=0.001
23 Pimds=-111+F+10*log10(B) //F in dB, B in MHz,
   Pidms in dBm
24 printf("\n\tPimds=-111+F+10*log10(B)\n\tPimds=%0.1 f
   dBm",Pimds)
```

```
25 printf(" = %.2 e mW" ,10^(Pimds/10))
```

---

#### Scilab code Exa 2.14 14

```
1 // data in question
2 //input signal(dBm)
3 Pin=-15
4 //intercept point of characteristic curve(dBm)
5 Pip=25
6 printf("\nPin=-15dBm\tPip=25dBm\n")
7 //equations and result
8 printf("\nresult:-")
9 Pimr=(Pin-Pip)*2 //Pimr in dB; Pin,Pip in dBm
10 printf("\nintermodulation ratio\nPimr=(Pin-Pip)*2 =%.
    .1 f dB",Pimr)
```

---

#### Scilab code Exa 2.15 15

```
1 //data in question
2 To=290
3 //bandwidth(Hz)
4 B=500*10^3
5 k=1.38*10^-23
6 //noise factor
7 F=10^(8/10)
8 //input power at IP
9 Pip=10
10 printf("\nB=500kHz\tF=8 dB\tPip=10 dBm")
11 //equations and result
12 Nf=k*To*B*F
13 printf("\nNf=k*To*B*F=%.4 e",Nf)
14 printf(" = %.2 f dBm",10*log10(Nf*1000))
15 Nf=10*log10(Nf*1000) //Nf in dBm
```

```
16 DR=2/3*(Pip-Nf) //DR in dB; Pip,Nf in dBm
17 printf("\ndynamic range\nDR=2/3*(Pip-Nf)=%.2 f dB" ,DR
    )
```

---

# Chapter 3

## transmission lines

Scilab code Exa 3.1 1

```
1 //resistance of line (ohm/m)
2 R=0.015
3 //operating frequency (Hz)
4 n=1.6*10^9
5 //angular frequency
6 w=2*%pi*n
7 //inductance of line (H/m)
8 L=0.002*10^(-6)
9 //conductance of line (S/m)
10 G=0.1*10^(-3)
11 //capacitance of line (F/m)
12 C=0.012*10^(-12)
13 printf("\nR=0.015ohm/m\tn=1.6GHz\tL=0.002uH/m\tG=0.1
        mS/m\tC=0.012pF/m\n")
14 //formulas and result
15 printf("\nimpedance Z=R+iwL=")
16
17 Y=complex(G,w*C) //admittance per unit length
18 Z=complex(R,w*L) //impedance per unit length
19 disp(Z)
20 printf("ohm/m\nadmittance Y=G+iwC=")
```

```

21 disp(Y)
22 printf("S/m\nZo=square root (Z/Y)=")
23 disp(sqrt(Z/Y))
24 printf("ohm")

```

---

### Scilab code Exa 3.2 2

```

1 //data
2 W=2*%pi*10^8 //rad/s
3 Vp=2.5*10^8 //m/s
4 Vin=75/(50+75)*3*complex(cos(0),sin(0)) //V
5 Iin=3/(50+75)*complex(cos(0),sin(0)) //A
6 //formula and result
7 printf("\nresult:--")
8 b=W/Vp
9 printf("\nB=%0.4 frad/m", b)
10 printf("\nV=1.8*cos(2*pi*10^8*t-0.8*pi*z)\ni=0.024*
    cos(2*pi*10^8*t-0.8*pi*z)")

```

---

### Scilab code Exa 3.3 3

```

1 //data
2 R=2 //ohm/m
3 G=0.5*10^(-3) //S/m
4 L=8*10^-9 //H/m
5 C=0.23*10^-12 //F/m
6 W=2*%pi*10^9 //Hz
7 Y=15.29*10^-4*exp(%i*1.2377)
8 Z=50.31*exp(%i*1.531)
9 //equation and result
10 printf("\nresult:--")
11 Zo=sqrt(complex(R,W*L)/complex(G,W*C))
12 y=sqrt(Z*Y)

```

```

13 a=real(y)
14 B=imag(y)
15 disp(Zo,"Zo=sqrt(complex(R,W*L)/complex(G,W*C))=")
16
17 disp(y,"y=sqrt(Z*Y)=")
18 printf("\na=%0.4fNp/m\nB=%0.4frad/m",a,B)

```

---

### Scilab code Exa 3.5 5

```

1 //data
2 lambda=1
3 Zin=150
4 ZL=300
5 //formula and result
6 Zo=sqrt(Zin*ZL)
7 printf("\nresult:-")
8 printf("\n(a)d=lambda/4=%0.2f m",lambda/4)
9 printf("\n(b)Zo=sqrt(Zin*ZL)=%0.3f ohm",sqrt(Zin*ZL))
10 printf("\n(c)FL=(ZL-Zo)/(ZL+Zo)=%0.4f", (ZL-Zo)/(ZL+Zo))

```

---

### Scilab code Exa 3.6 6

```

1 //data
2 Zin=45 //ohm
3 ZL=20 //ohm
4 b=0.5/2 //cm
5 Er=2.1
6 L=200*10^-9 //H
7 f=3*10^9 //Hz
8 C=55.63*Er*10^-12 //F
9 //formulas and result
10 printf("\nresult:-")

```

```

11 Zo=sqrt(Zin*ZL)
12 printf("\nZo=%0.0 f ohm",Zo)
13 k=30/sqrt(200*10^-9/(55.63*Er*10^-12))
14 a=b/exp(k)
15 printf("\na=%0f cm",a)
16 lambda=1/(f*sqrt(L*C))
17 printf("\nlambda=%0f m",lambda)
18 d=lambda/4
19 printf("\nd=%0f m =%0f cm",d,d*100)

```

---

### Scilab code Exa 3.7 7

```

1 //data
2 Zo1=80
3 ZL=50
4 h=1.6 //mm
5 Er=2.3
6 Zo=sqrt(Zo1*ZL)
7 A=1.4635
8 B=6.1739
9 qo=150
10 // formulas and result
11 printf("\nresult:-")
12 W=h*(2/%pi*(6.1739-1-log(2*6.1739-1)+(2.3-1)/(2*2.3)
    *(log(6.1739-1)+0.39-0.61/2.3)))
13 printf("\nW=%0.4 f mm",W)
14 F=(1+12*h/W)^(-1/2)
15 printf("\nF=%0.6 f",F)
16 Ee=(2.3+1)/2+(2.3-1)/2*0.383216-(2.3-1)/4.6*0.005/
    sqrt(2.0656)
17 printf("\nEe=%0.1 f",Ee)
18 F=4*h*sqrt(Er-1)/qo*(0.5+(1+2*log10(1+W/h))^2)
19 printf("\nF=%0f",F)
20 Ee=((sqrt(2.3)-sqrt(1.9))/(1+4*F^(-1.5))+sqrt(1.9))
    ^2

```



```

21 printf("\nEe(f)=%f",Ee)
22 q=3*10^8/(2*10^9*sqrt(1.9))
23 printf("\nq=%f m",q)
24 length_of_line=q/4
25 printf("\nlength of line=%f m",length_of_line)

```

---

### Scilab code Exa 3.8 8

```

1 Zo=50
2 C=100*10^(-12)
3 a=1.15*10^(-3)
4 //data print
5 printf("\nZo=50 ohm C=100pF/m a=0.01 dB/m\n")
6 //formula and result
7 L=C*Zo^2
8 R=a*sqrt(L/C)
9 G=R*C/L
10 vp=1/sqrt(L*C)
11 printf("\nresult:-")
12 printf("\n(a)R=a*sqrt(L/C)=%f ohm/m",a*sqrt(L/C))
13 printf("\n(b)L=C*Zo^2=%f e H/m",C*Zo^2)
14 printf("\n(c)G=R*C/L=%f e S/m",R*C/L)
15 printf("\n(d)vp=1/sqrt(L*C)=%f e m/s",1/sqrt(L*C))

```

---

### Scilab code Exa 3.9 9

```

1 //data
2 Zin=complex(30,60) //ohm
3 Zsc=%i*53.1 //ohm
4 Zoc=-48.3*i //ohm
5 //formula and result\
6 printf("\nresult:-")
7 Zo=sqrt(Zsc*Zoc)

```

```

8 printf("\nZo=%f ohm",Zo)
9 ZL=Zoc*(Zsc-Zin)/(Zin-Zoc)
10 disp(ZL,"ZL=")

```

---

### Scilab code Exa 3.10 10

```

1 //data
2 Zoc=-54.6*%i //ohm
3 Zsc=103*%i //ohm
4 d=1.5 //m
5 Zo=sqrt(Zoc*Zsc)
6 printf("\nZo=%f ohm",Zo)
7 //y=1/d*atanh(sqrt(Zsc/Zoc))
8 y=1/2/d*log(complex(1,1.8969)/complex(1,-1.8969))
9 printf("\ny=")
10 disp(y)
11 printf("1/m\nnegligible real part")
//real part
negligible

```

---

### Scilab code Exa 3.11 11

```

1 //data
2 W=2*%pi*26*10^6 //rad/s
3 Vp=200*10^6 //m/S
4 B=W/Vp
5 Zo=50 //ohm
6 Zs=50 //ohm
7 Vs=100 //volt
8 ZL=100+%i*50 //ohm
9 l=10 //m
10 //formulas and result
11 printf("\nresult:-")

```

```

12 printf("\nB=%f rad/m",B)
13 Zin=Zo*(ZL+%i*Zo*tan(B*l))/(Zo+%i*ZL*tan(B*l))
14 disp(Zin,"Zin=")
15 VA=Vs/(Zs+Zin)*Zin
16 disp(VA,"VA=")
17 ZTh=Zo*complex(Zs,Zo*tan(B*l))/complex(Zo,Zs*tan(B*l
    ))
18 disp(ZTh,"ZTh=")
19 Vin=50*exp(%i*(-8.168))
20 VTh=2*Vin
21 disp(VTh,"VTh=")
22 VL=VTh/(ZTh+ZL)*ZL
23 disp(VL,"VL=")
24 F=(complex(19.21,3.52)-50)/(complex(19.21,3.52)+50)
25 disp(F,"F=")
26 Z=10
27 VL=Vin*(exp(-%i*B*Z)+F*exp(%i*B*Z))
28 disp(VL,"VL=")

```

---

### Scilab code Exa 3.12 12

```

1 //data
2 R=250 //ohm
3 V250=60*sqrt(2)/11*exp(-%i*45/180*%pi) //volt
4 Pd=(real(V250)^2+imag(V250)^2)/(2*R)
5 printf("\nV250=")
6 disp(V250)
7 printf("\nPd=%f W",Pd)

```

---

### Scilab code Exa 3.13 13

```

1 //data
2 ZL=complex(73,-42.5)

```

```

3 Zo=complex(50,.01)
4 //formula and result
5 printf("\nresult:-")
6 F=(ZL-Zo)/(ZL+Zo)
7 p=sqrt(real(F)^2+imag(F)^2)
8 VSWR=(1+p)/(1-p)
9 disp(F,"F=")
10 printf("\nVSWR=%.4f",VSWR)

```

---

#### Scilab code Exa 3.14 14

```

1 //data
2 q=2 //m
3 B=%pi //rad/m
4 d1=.4 //m
5 Z2=1
6 S=2.4
7 //formula and result
8 printf("\nresult:-")
9 Z_L=complex(1,-S*tan(B*d1))/complex(S,-tan(B*d1))
10 disp(Z_L,"Z_L=")
11 disp(Z_L*100,"ZL=")

```

---

#### Scilab code Exa 3.15 15

```

1 //data
2 ZL=50+%i*100
3 Zo=50
4 Bl=%pi/2
5 //formula and result
6 printf("\nresult:-")
7 Z_in=Zo*(%i*Zo)/(%i*ZL)
8 F=(ZL-Zo)/(ZL+Zo)

```

```
9 x=sqrt(real(F)^2+imag(F)^2)
10 printf("\nx=%f",x)
11 VSWR=(1+x)/(1-x)
12 Z_L=ZL/Zo
13 printf("\nZ_in=")
14 disp(Z_in)
15 printf("\nF=")
16 disp(F)
17 printf("\nVSWR=%4 f",VSWR)
18 printf("\nZ_L=")
19 disp(Z_L)
```

---

# Chapter 4

## electromagnetic fields and waves

### Scilab code Exa 4.3 3

```
1 Eo=8.854*10^-12
2 uo=4*%pi*10^-7
3
4 W=2/sqrt(uo*Eo)
5 printf("\nW=%0.0e rad/s",W)
```

---

### Scilab code Exa 4.4 4

```
1 Q=[0:0.01:2*%pi]
2 q=[0:0.01:%pi]
3 k=integrate('60*%pi/sin(Q)*cos(%pi/2*cos(Q))^2', 'Q',
4             ,0,%pi/2)
5 printf("\nk=%0.2 f W",4*k*%pi)
```

---

### Scilab code Exa 4.5 5

```
1 B=2*%pi
2 C=3*10^8
3 lambda=2*%pi/B
4 f=C/lambda
5 W=2*%pi*f
6 uo=4*%pi*10^-7
7 k=2*%pi
8 n=W*uo/k
9 printf("\n(a) lambda=%0.0 f m\n(b) f=%0.0 e Hz\n(c) n=%0.4 f
      ohm", lambda, f, n)
```

---

### Scilab code Exa 4.6 6

```
1 uo=1.2567*10^-6
2 f=10^4
3 W=2*%pi*f
4 a=4
5 k=sqrt(W*uo*a/2)+sqrt(W*uo*a/2)*%i
6 B=real(k)
7 a=imag(k)
8 lambda=2*%pi/B
9 Vp=W/B
10 delta=1/a
11 disp(k, "k=")
12 printf("\nlambda=%f m\nVp=%0.4 e m/s\ndelta=%0.4 f m",
      lambda, Vp, delta)
```

---

### Scilab code Exa 4.7 7

```
1
2 ky=6
```

```

3 kz=8
4
5 kr=sqrt(ky^2+kz^2)
6 printf("\nkr=%0.0 f m^-1",kr)
7 //(a)
8 O=180/%pi*asin(ky/kr)
9 theta=(180-O)*%pi/180
10 Vr=3*10^8
11 printf("\n(a)\nO=%0.2 f degree",O)
12 //(b)
13 lr=2*%pi/kr
14 ly=2*%pi/ky
15 lz=2*%pi/kz
16 printf("\n(b)\nlr=%0.4 f m\nly=%0.4 f m\nlz=%0.4 f m",lr,
    ly,lz)
17 //(c)
18 W=Vr*kr
19 f=W/lr
20 Vpy=W/ky
21 Vpz=W/kz
22 printf("\n(c)\nW=%0.0 e rad/s\nf=%0.2 e Hz\nVpy=%0.1 e m/s
    \nVpz=%0.2 e m/s",W,f,Vpy,Vpz)
23 Ver=3*10^8
24 Vey=Ver*sin(theta)
25 Vez=Ver*cos(theta)
26 printf("\n(d)\nVey=%0.1 e m/s\nVez=%0.1 e m/s",Vey,Vez)

```

---

#### Scilab code Exa 4.10 10

```

1
2 Er=2.25
3 ur=1
4 W=10^9
5 p=0.2
6 uo=4*%pi*10^-7

```



```

7 Eo=8.854*10^-12
8 ko=W*sqrt(uo*Eo)
9 k2=W*sqrt(uo*Eo*Er)
10 n1=sqrt(uo/Eo)
11 n2=sqrt(uo/Eo/Er)
12 R=(n2-n1)/(n1+n2)
13 T=2*n2/(n1+n2)
14 VSWR=(1+p)/(1-p)
15 Pav=3.84^2/(2*n2)
16 printf("\nko=%0.4 f rad/m\nk2=%0.4 f rad/m\nn1=%0.4 f ohm\n
      nn2=%0.4 f ohm\nR=%0.2 f\nT=%0.2 f \nVSWR=%0.2 f\nPav=%0.4
      f W/m^2" , ko , k2 , n1 , n2 , R , T , VSWR , Pav)

```

---

#### Scilab code Exa 4.11 11

```

1
2 for m=1:1:3
3     qo=2.5*10^-2
4     fc=3*10^8*m/(9*10^-2)
5     qc=2*4.5*10^-2/m
6     printf("\nm=%0f\nfc=%0.4 e Hz\nlambdaC=%0.2 e m" , m , fc
      , qc)
7     printf("\nTM0=%0.4 e Hz" , fc)
8     q=qo/sqrt(1-(qo/qc)^2)
9     printf("\nlambda=%0.4 e m\n" , q)
10 end

```

---

#### Scilab code Exa 4.12 12

```

1
2 a=0.0158
3 b=0.0079
4 f=15.8*10^9

```

```

5 //TE10
6 m=1
7 n=0
8 fc=3*10^8*sqrt((m/2/a)^2+(n/2/b)^2)
9 printf("\n(a)\nfor TE10 \n\tfc=%0.4e Hz",fc)
10 Vp=3*10^8/sqrt(1-(fc/f)^2)
11 //TE20
12 m=2
13 n=0
14 fc=3*10^8*sqrt((m/2/a)^2+(n/2/b)^2)
15 printf("\nfor TE20 \n\tfc=%0.4e Hz",fc)
16 //TE01
17 m=0
18 n=1
19 fc=3*10^8*sqrt((m/2/a)^2+(n/2/b)^2)
20 printf("\nfor TE01 \n\tfc=%0.4e Hz",fc)
21 //TE11
22 m=1
23 n=1
24 fc=3*10^8*sqrt((m/2/a)^2+(n/2/b)^2)
25 printf("\nfor TE11 \n\tfc=%0.4e Hz",fc)
26 printf("\n(c)\nVp=%04e m/s",Vp)

```

---

# Chapter 5

## resonant circuits

Scilab code Exa 5.1 1

```
1
2 //data
3 f2=9 //MHz
4 f1=11 //MHz
5 R=50 //ohm
6 W1=2*%pi*11*10^6 //rad/s
7 W2=2*%pi*9*10^6 //rad/s
8 //formula and result
9 printf("\nresult:-")
10 Wo=sqrt(W1*W2)
11 fo=sqrt(f1*f2)
12 printf("\nWo=sqrt(W1*W2)\nfo=sqrt(f1*f2)=%.6 f MHz",
        fo)
13 L=R/(W1-W2)
14 printf("\nQ=Wo*L/R=Wo/(W1-W2)\nL=R/(W1-W2)=%.6 e H",L
        )
15 C=1/(L*Wo^2)
16 printf("\nWo=1/sqrt(L*C)\nC=1/(L*Wo^2)=%.6 e F",C)
```

---

### Scilab code Exa 5.2 2

```
1
2 //data
3 Lp=10^(-5) //H
4 Cp=10^(-11) //F
5 Rp=10^5 //ohm
6 RL=10^5 //ohm
7 //formula and result
8 printf("\nresult:-")
9 Wo=1/sqrt(Lp*Cp)
10 printf("\nWo=1/sqrt(Lp*Cp)=%.0 e rad/s",Wo)
11 Q=Rp/(Wo*Lp)
12 printf("\nQ=Rp/(Wo*Lp)=%.0 f",Q)
13 Qe=RL/(Wo*Lp)
14 printf("\nQe=RL/(Wo*Lp)=%.0 f",Qe)
15 QL=Q*Qe/(Q+Qe)
16 printf("\nQL=Q*Qe/(Q+Qe)=%.0 f",QL)
```

---

### Scilab code Exa 5.3 3

```
1
2 //data
3 R2=62.5*10^3 //ohm
4 E=1
5 L1=320*10^(-9) //H
6 L2=20*10^(-9) //H
7 //formula and result
8 printf("\nresult:-")
9 n=sqrt(E*L1/L2)
10 printf("\nn=sqrt(E*L1/L2)=%.0 f",n)
11 R1=n^(2)*R2
12 printf("\nZ1=n^2*Z2\nY1=Y2/n^2=1/n^2*complex(1/R2,W*
    C2)\n\nR1=n^2*R2=%.0 e ohm\n",R1)
13 C1=(6+1/4^2*30.7)*10^-12
```

```

14 printf("\nC1=%0.2 e F\n", C1)
15 Wo=1/sqrt(L1*C1)
16 printf("\nWo=1/sqrt(L1*C1)=%0.4 e rad/s\n", Wo)
17 fo=Wo/(2*pi)
18 printf("\nfo=Wo/(2*pi)=%0.2 e Hz\n", fo)
19 Q=R1/(Wo*L1)
20 printf("\nQ=R1/(Wo*L1)=%0.4 f", Q)

```

---

### Scilab code Exa 5.5 5

```

1
2 //data
3 a=0.455*10^-3 //m
4 b=1.499*10^-3 //m
5 W=2*pi*5*10^9 //rad/s
6 uo=4*pi*10^-7
7 q=5.813*10^7
8 Eo=8.854*10^-12
9 Er=2.08
10 d=0.0004
11 //formula and result
12 printf("\nresult:-")
13 Rs=sqrt(W*uo/2/q)
14 printf("\nRs=%f ohm", Rs)
15 ac=Rs*(1/a+1/b)/(2*log(b/a)*sqrt(uo/Eo))
16 printf("\nac=%f Np/m", ac)
17 ac=ac*sqrt(Er)
18 ad=W/2*sqrt(uo*Eo*Er)*(d)
19 Bo=2*pi*5*10^9/(3*10^8)
20 Bd=2*pi*5*10^9*sqrt(2.08)/(3*10^8)
21 a=0.058768
22 Qair=Bo/(2*a)
23 a=0.114963
24 Qteflon=Bd/(2*a)
25 printf("\n\twith teflon\n ac=%f Np/m\nad=%f Np/m\nBo

```

```
=%f rad/m\nBd=%f rad/m,\nQair=%f,\nQtflon=%f",ac
,ad,Bo,Bd,Qair,Qtflon)
```

---

### Scilab code Exa 5.6 6

```
1
2 Zo=50
3 Er=2.08
4 B=60*%pi^2/Zo/sqrt(Er)
5 c=3*10^8
6 f=2*10^9
7 Ee=1.7875
8 t=0.159*10^-6
9 a=5.813*10^7
10 fGHz=2
11 A=Zo/60*((Er+1)/2)^(1/2)+(Er-1)/(Er+1)*(0.23+0.11/Er
    )
12 printf("\nA=%0.4f\nB=%0.4f",A,B)
13 h=1.59*10^-3
14 if A>1.52 then
15     W=h*(8*exp(A)/(exp(2*A)-2))
16 else
17     W=h*(2/%pi*(B-1-log(2*B-1)+(Er-1)/2/Er*(log(B-1)
        +0.39-0.61/Er)))
18 end
19 printf("\nW=%0.6f cm",W)
20
21 Ere=0.5*(2.08+1+(2.08-1)/sqrt(1+12/3.192094))
    -(2.08-1)*0.0001/4.6/sqrt(3.1921)
22 printf("\nEre=%0.4f",Ere)
23 l=c/(2*f*sqrt(Ee))
24 printf("\nl=%0.6f m",l)
25 We=W/h+0.3979*t/h*(1+log(2*h/t))
26 printf("\nWe/h=%0.4f",We)
27 F=1+1/We*(1-1.25*t/(%pi*h)+1.25/%pi*log(2*h/t))
```

```

28 ac=44.1255*10^-5*F*Zo*Ere/h*sqrt(fGHz/a)*(We+0.667*
    We/(We+1.444))
29 printf("\nac=%0.4 f Np/m", ac)
30 del=0.00040
31 ad=10.4766*Er/(Er-1)*(Ere-1)/sqrt(Ere)*fGHz*tan(del)
32 printf("\nad=%0.4 f Np/m", ad)
33 B=2*pi/(2*1)
34 printf("\nB=%0.4 f rad/m", B)
35 Q=B/(2*(ac+ad))
36 printf("\nQ=%0.1 f", Q)

```

---

#### Scilab code Exa 5.7 7

```

1
2 a=2.286*10^-2
3 b=1.016*10^-2
4 f=9.379*10^9
5 c=1/2/sqrt((9379/300)^2-(1/2/a)^2)
6 printf("\nc=%0.5 f m = %0.4 f cm", c, c*100)

```

---

#### Scilab code Exa 5.8 8

```

1
2 //data
3 Er=2.05
4 ur=1
5 a=.016 //m
6 b=.0071 //m
7 c=.0156 //m
8 m=1
9 p=1
10 printf("\nresult:-")
11 fr=(300/sqrt(ur*Er))*sqrt((m/(2*a))^2+(p/(2*c))^2)

```

```
12 printf("\nfr=(300/sqrt(ur*Er))*sqrt((m/(2*a))^2+(p
    /(2*C))^2)\n =%.3e MHz",fr)
```

---

### Scilab code Exa 5.9 9

```
1
2 w=2*pi*5*10^9
3 u=4*pi*10^-7
4 a=5.8*10^7
5 r=sqrt((3.832^2+(pi/2)^2)/(5000*2*pi/300)^2)
6 h=2*r
7 del=sqrt(2/(w*u*a))
8 printf("\ndel=%.4e m",del)
9 Qc=47.7465*10^6/(9.3459*10^-7*5*10^9)*(3.832^2+(pi
    /2)^2)^1.5/((3.832^2+(pi/2)^2)+1)
10 printf("\nQc=%.2f",Qc)
```

---

### Scilab code Exa 5.10 10

```
1
2 fr=35*10^9
3 w=2*pi*fr
4 Es=9.9
5 Er=36
6 uo=4*pi*10^-7
7 Eo=8.8154*10^-12
8 z1=1.2892*10^8/(fr*sqrt(Es))
9 z2=1.2892*10^8/(fr*sqrt(Er))
10 r=0.835*10^-3
11 printf("\n1.2892*10^8/(fr*sqrt(Es))=%.3e m",z1)
12 printf("\n1.2892*10^8/(fr*sqrt(Er))=%.3e m",z2)
13 ko=w*sqrt(uo*Eo)
14 y=sqrt((ko*r)^2*(Er-1)-5.784)
```



```

15 printf("\ny=%0.3f", y)
16 k_ = 2.405/r + y / (2.405*r*(1+2.43/y+0.291*y))
17 printf("\nk_=%0.3e", k_)
18 a1 = sqrt(k_^2 - ko^2*Es)
19 a2 = sqrt(k_^2 - ko^2)
20 B = sqrt(ko^2*Er - k_^2)
21 printf("\na1=%0.3e\na2=%0.3e\nB=%0.3e", a1, a2, B)
22 d = 10^-3
23 t = .25*10^-3
24 h = 1/B*(atan(a1/(B*tanh(a1*t)))+atan(a2/(B*tanh(a2*d)
    )))
25 printf("\nh=%0.3e m", h)

```

---

# Chapter 6

## impedance matching networks

Scilab code Exa 6.1 1

```
1
2 //data
3 Zo=100
4 ZL=complex(50,-75)
5 B=2*%pi
6 XL=-0.75
7 RL=0.5
8 Y_L=Zo/ZL
9 //formulas and result
10 printf("\nresult:-")
11 G_L=real(Y_L)
12 B_L=imag(Y_L)
13 disp(Y_L,"Y_L=")
14 A=G_L*(G_L-1)+B_L^2
15 printf("\nA=%f",A)
16 ds=1/B*atan((XL+sqrt(XL^2-A*(1-RL)))/A)
17 printf("\nds=%f*lambda",ds) //
    calculation mistake in book
18 ds=1/B*atan((XL-sqrt(XL^2-A*(1-RL)))/A)
19 printf("\nds=%f*lambda",ds)
20 X_s=-1.2748
```

```

21 Ls=1/B*acot(X_s)
22 printf("\nLs=%f*lambda",Ls)
23 X_s=1.2748
24 Ls=1/B*acot(X_s)
25 printf("\nLs=%f*lambda",Ls)

```

---

### Scilab code Exa 6.3 3

```

1
2 FL=0.4*exp(-%i*30*%pi/180)
3 Fin=0.2*exp(%i*45*%pi/180)
4 Z_L=(1+FL)/(1-FL)
5 Z_in=(1+Fin)/(1-Fin)
6 Y_in=(1-Fin)/(1+Fin)
7 disp(Z_L,"Z_L=")
8 disp(Z_in,"Z_in=")
9 disp(Y_in,"Y_in=")
10 //Y_in=(1+%i*Z_L*tan(Bl))/(Z_L+%i*tan(Bl))
11 Y_in=1/Z_in
12 disp(Y_in,"Y_in=")

```

---

### Scilab code Exa 6.5 5

```

1
2 RL=50
3 Rs=75
4
5 R1=sqrt(Rs*(Rs-RL))
6 R2=sqrt(RL^2*Rs/(Rs-RL))
7 attenuation=20*log10(R2*RL/(R1*(R2+RL)+R2*RL))
8 printf("\nR1=%0.1f ohm\nR2=%0.1f ohm\nattenuation (dB)=
%0.2f dB",R1,R2,attenuation)

```

---

### Scilab code Exa 6.6 6

```
1
2 Rp=600
3 Rs=50
4 W=2*%pi*400*10^6
5 Q=sqrt(Rp/Rs-1)
6 Xs=Q*Rs
7 Xp=Rp/Q
8 Cs=1/W/Xs
9 Lp=Xp/W
10 Ls=Xs/W
11 Cp=1/W/Xp
12 printf("\nQ=%0.4 f\nXs=%0.4 f ohm\nXp=%0.4 f ohm\nCs=%0.2 e
    F\nLp=%0.3 e H\nLs=%0.3 e H\nCp=%0.2 e F" , Q , Xs , Xp , Cs , Lp
    , Ls , Cp)
```

---

### Scilab code Exa 6.7 7

```
1
2 Rp=600 //ohm
3 Rs=173.2 //ohm
4 Q=sqrt(Rp/Rs-1)
5 Xs=Q*Rs
6 Xp=Rp/Q
7 printf("\nQ=%0.4 f\nXs=%0.4 f ohm\nXp=%0.4 f ohm\n" , Q , Xs ,
    Xp)
8 Rp=173.2 //ohm
9 Rs=50 //ohm
10 Q=sqrt(Rp/Rs-1)
11 Xs=Q*Rs
12 Xp=Rp/Q
```

```
13 printf("\nQ=%0.4 f\nXs=%0.4 f ohm\nXp=%0.4 f ohm\n", Q, Xs ,  
Xp)
```

---

### Scilab code Exa 6.8 8

```
1  
2 f=500*10^6  
3 W=2*pi*f  
4 Rp=50  
5 Rs=10  
6 Q=sqrt(Rp/Rs-1)  
7 Xs=Q*Rs  
8 Xp=Rp/Q  
9 Ls=(Xs-10)/W  
10 Cp=1/W/Xp  
11 Cs=1/W/(Xs+10)  
12 Lp=Xp/W  
13 printf("\nQ=%0.0 f\nXs=%0.0 f ohm\nXp=%0.0 f ohm\nLs=%0.4 e  
H\nCp=%e F\nCs=%e F\nLp=%e H", Q, Xs, Xp, Ls, Cp, Cs, Lp  
)
```

---

### Scilab code Exa 6.9 9

```
1  
2 ZL=10^3/(8-%i*12)  
3 Rp=50  
4 W=2*pi*10^9  
5 Rs=real(ZL)  
6 Q=sqrt(Rp/Rs-1)  
7 Xs=Q*Rs  
8 Xc=Xs+imag(ZL)  
9 Xp=Rp/Q  
10 C=1/W/Xc
```

```

11 L=Xp/W
12 disp(ZL,"ZL=")
13 printf("\nQ=%0.4 f\nXs=%0.4 f ohm\nXp=%0.4 f ohm\nC=%0.4 e F
    \nL=%0.4 e H\n",Q,Xs,Xp,C,L)
14 printf("\nXs=57.6923 -21.0654 ohm\nXp=91.2909 ohm\nCp
    =1.7434 F")

```

---

### Scilab code Exa 6.10 10

```

1
2 W=2*%pi*10^9
3 Gs=0.02
4 Gp=0.008
5 Q=sqrt(Gs/Gp-1)
6 Bs=Gs/Q
7 Bp=Q*Gp
8 printf("\nQ=%0.4 f\nBs=%0.4 f S\nBp=%0.2 f S\n",Q,Bs,Bp)

```

---

# Chapter 7

## impedance transformers

Scilab code Exa 7.1 1

```
1
2 RL=100
3 Zo=50
4 PM=0.05
5 c=3*10^8
6 f=900*10^6
7 lambda=c/f
8 Z1=sqrt(RL*Zo)
9 l=lambda/4
10 fractional_bandwidth=2-4/%pi*acos(abs(2*PM*sqrt(Zo*
    RL)/(RL-Zo)/sqrt(1-PM^2)))
11 printf("\nZ1=%f ohm\nl=%0.4 f m\nfractional bandwidth=
    %0.7 f",Z1,l,fractional_bandwidth)
```

---

Scilab code Exa 7.5 5

```
1
2 delf=0.6
```

```

3 fo=1
4 Zo=100
5 Qz=acos(1/sqrt(2)*cos((2-delf/fo)/4*%pi))
6 Qm=acos(sqrt(2)*cos(Qz))
7 Z_L=5
8 k=sqrt((Z_L-1)^2/4/Z_L*cotg(Qz)^4)
9 Pm=sqrt(k^2/(1+k^2))
10 Z1=sqrt(((Z_L-1)^2/4/tan(Qz)^4+Z_L)^(1/2)+(Z_L-1)/2/
    tan(Qz)^2)
11 Z2=Z_L/Z1*Zo
12 Z_in=Z1^2/Z2^2*Z_L*10^4
13 F=(Z_in-1)/(Z_in+1)
14 printf("\nQz=%0.4f rad\nQm=%0.1f\nk=%0.4f\nPm=%0.4f\nZ_1
    =%0.2f ohm\nZ2=%0.2f ohm\nZ_in=%0.4f\nF=%0.4f", Qz, Qm,
    k, Pm, Z1, Z2, Z_in, F)

```

---



# Chapter 8

## two port networks

Scilab code Exa 8.1 1

```
1
2 I1=1
3 V1=6*I1
4 Z11=V1/I1
5 V2=6*I1
6 Z21=V2/I1
7 I2=1
8 V1=6*I2
9 Z12=V1/I2
10 V2=6*I2
11 Z22=V2/I2
12 A=[Z11 , Z12 ; Z21 , Z22]
13 printf("\nA=")
14 disp(A)
```

---

Scilab code Exa 8.2 2

```
1
```

```
2 I1=1
3 V1=12*I1
4 V2=0
5 Z21=V2/I1
6 Z11=V1/I1
7 I2=1
8 V2=3*I2
9 V1=0
10 Z12=V1/I2
11 V2=3*I2
12 Z22=V2/I2
13 A=[Z11 , Z12 ; Z21 , Z22]
14 printf("\nA=")
15 disp(A)
```

---

### Scilab code Exa 8.3 3

```
1
2 I1=1
3 V1=18*I1
4 V2=6*I1
5 Z11=V1/I1
6 Z21=V2/I1
7 I2=1
8 V2=9*I2
9 V1=6*I2
10 Z12=V1/I2
11 Z22=V2/I2
12 A=[Z11 , Z12 ; Z21 , Z22]
13 printf("\nA=")
14 disp(A)
```

---

### Scilab code Exa 8.5 5

```
1
2 V2=1
3 V1=1
4 V2=0
5 I1=0.05*V1
6 I2=-0.05*V1
7 Y11=I1/V1
8 Y21=I2/V1
9 I2=0.05*V2
10 I1=-0.05*V2
11 Y12=-0.05
12 Y22=0.05
13 A=[Y11 , Y12 ; Y21 , Y22]
14 printf("\nA=")
15 disp(A)
```

---

#### Scilab code Exa 8.6 6

```
1
2 V1=1
3 V2=1
4 I1=0.0225/0.325*V1
5 VN=I1/(0.2+0.025)
6 I2=-0.2*VN
7 Y11=I1/V1
8 Y21=I2/V1
9 I2=0.025/0.325*V2
10 VM=I2/(0.1+0.025)
11 I1=-0.1*VM
12 Y12=I1/V2
13 Y22=I2/V2
14 A=[Y11 , Y12 ; Y21 , Y22]
15 printf("\nA=")
16 disp(A)
```

---

### Scilab code Exa 8.7 7

```
1
2 V1=1
3 V2=1
4 I1=0.1192*V1
5 IN=0.05*I1/(0.05+(0.1*(0.2+0.025)/(0.1+0.2+0.025)))
6 IM=0.2*0.0692*V1/(0.2+0.025)
7 I2=-(IN+IM)
8 Y11=I1/V1
9 Y21=I2/V1
10 I2=(0.05+0.2*(0.1+0.025)/(0.2+0.1+0.025))*V2
11 IN=0.05*I2/(0.05+(0.2*(0.1+0.025)/(0.2+.1+0.025)))
12 IM=0.1*0.0769*V2/(0.1+0.025)
13 I1=-(IN+IM)
14 Y12=I1/V2
15 Y22=I2/V2
16 A=[Y11 , Y12 ; Y21 , Y22]
17 printf("\nA=")
18 disp(A)
```

---

### Scilab code Exa 8.9 9

```
1
2 I1=1
3 V1=14*I1
4 I2=-2/3*I1
5 h11=V1/I1
6 h21=I2/I1
7 V2=9*I2
8 V1=6*I2
9 h12=V1/V2
```

```
10 h22=I2/V2
11 A=[h11 , h12 ; h21 , h22]
12 printf("\nA=")
13 disp(A)
```

---

#### Scilab code Exa 8.10 10

```
1
2 I1=1
3 I2=-I1
4 V1=I1
5 B=-V1/I2
6 D=-I1/I2
7 V2=V1
8 I1=0
9 A=V1/V2
10 C=I1/V2
11 M=[A, B; C, D]
12 printf("\nA=")
13 disp(M)
```

---

#### Scilab code Exa 8.14 14

```
1
2 V1in=.5*(10*exp(%i*%pi/180*0)+50*.1*exp(%i*%pi
   /180*40))
3 disp(V1in)
4 V1ref=0.5*(10*exp(%i*%pi/180*0)-50*.1*exp(%i*%pi
   /180*40))
5 disp(V1ref)
6 V2in=0.5*(12*exp(%i*%pi/180*30)+50*.15*exp(%i*%pi
   /180*100))
7 disp(V2in)
```

```

8 V2ref=0.5*(12*exp(%i*%pi/180*30)-50*.15*exp(%i*%pi
  /180*100))
9 disp(V2ref)

```

---

### Scilab code Exa 8.17 17

```

1
2 n=10
3 S11=(n^2-1)/(n^2+1)
4 S21=2*n/(n^2+1)
5 S22=(1-n^2)/(1+n^2)
6 S12=2*n/(n^2+1)
7 A=[S11 , S12 ; S21 , S22]
8 disp(A)

```

---

### Scilab code Exa 8.19 19

```

1
2 Zo1=50
3 Zo2=50
4 Vs1=1
5 Vs2=1
6 Z1=%i*50+50*(-%i*25)/(50-%i*25)
7 S11=(Z1-Zo1)/(Z1+Zo1)
8 Z2=(50+%i*50)*(-%i*25)/(50+%i*50-25*%i)
9 S22=(Z2-Zo2)/(Z2+Zo2)
10 V2=(10-%i*20)/(50+%i*50+10-%i*20)*Vs1
11 S21=2*V2/Vs1
12 V2=(10-%i*30)/(50+10-%i*30)*Vs2
13 V1=50/(50+%i*50)*V2
14 S12=2*V1/Vs2
15 A=[S11 , S12 ; S21 , S22]
16 disp(A,"A=")

```



# Chapter 9

## filter design

### Scilab code Exa 9.2 2

```
1
2 foo=2.05*10^6
3 fc=2*10^6
4 Zo=75
5 Wc=2*pi*2*10^6
6 L=Zo/Wc*2
7 C=2/(Zo*Wc)
8 m=sqrt(1-(fc/foo)^2)
9 printf("\nm=%0.4 f",m)
10 printf("\nm*L/2=%0.2 e H",m*L/2)
11 printf("\nm*C=%0.3 e F",m*C)
12 printf("\n(1-m^2)*L/4/m=%0.2 e", (1-m^2)*L/4/m)
```

---

### Scilab code Exa 9.3 3

```
1
2 Zo=75
3 Wc=2*pi*2*10^6
```



```

4 foo=2.05*10^6
5 L=Zo/Wc*2
6 m=0.6
7 C=2/(Zo*Wc)
8 printf("\nm*L/2=%0.2 e H",m*L/2)
9 printf("\nm*C=%0.3 e F",m*C/2)
10 printf("\n(1-m^2)*L/4/m=%0.2 e", (1-m^2)*L/2/m)

```

---

#### Scilab code Exa 9.4 4

```

1
2 Zo=75
3 Wc=2*pi*2*10^6
4 foo=1.95*10^6
5 fc=2*10^6
6 L=Zo/Wc/2
7 C=1/2/(Zo*Wc)
8 m=sqrt(1-(foo/fc)^2)
9 printf("\nL=%0.3 e H",L)
10 printf("\nC=%0.3 e F",C)
11 printf("\nm=%0.4 f",m)
12 printf("\n2*C/m=%0.4 e F",2*C/m)
13 printf("\nL/m=%0.4 e H",L/m)
14 printf("\n4*m*C/(1-m^2)=%0.4 e F",4*m*C/(1-m^2))

```

---

#### Scilab code Exa 9.5 5

```

1
2 Le=3
3 E=10^(Le/10)-1
4 L=15
5 Wc=1
6 W=1.3*Wc

```

```

7 n=1/2*(log10(10^(L/10)-1)-log10(E))/log10(W/Wc)
8 m=acosh(sqrt(10^(0.1*L)-1))/acosh(W/Wc)
9 printf("\nn=%0.2 f",n)
10 printf("\nm=%0.3 f",m)

```

---

### Scilab code Exa 9.6 6

```

1
2 L=30
3 W=40*10^6
4 Wc=10*10^6
5 Le=3
6 E=10^(Le/10)
7 Zo=50
8 Wc=2*pi*10^6*10
9 L=Zo/Wc
10 C=2/(Zo*Wc)
11 n=1/2*(log10(10^(L/10)-1)-log10(E))/log10(W/Wc)
12 printf("\nn=%0.2 f",n)
13 printf("\ng1=%0.0 f\ng2=%0.0 f\ng3=%0.0 f",2*sin(pi/6),2*
    sin(pi/2),2*sin(pi*5/6))
14 printf("\n")
15 printf("\nL1=L3=%0.4 e H",L)
16 printf("\nC2=%0.3 e F",C)
17 Zo=50
18 Wc=2*pi*10^6*10
19 L=Zo*2/Wc
20 C=1/(Zo*Wc)
21 printf("\nL2=%0.4 e H",L)
22 printf("\nC1=C3=%0.4 e F",C)

```

---

### Scilab code Exa 9.7 7

```

1
2 Gr=0.01
3 m=acosh(sqrt(10^(0.1*L)-1)/sqrt(10^(0.1*Gr-1)))/
    acosh(W/Wc)
4 printf("\nm=%0.0 f\n",m)
5 m=3
6 E=log(coth(Gr/17.37))
7 X=sinh(E/2/m)
8 n=3
9 gp=1
10
11 for p=1:1:n
12     ap=sin((2*p-1)*%pi/2/m)
13     bp=X^2+sin(p*%pi/m)^2
14     printf("\nap=%0.4 f\nbp=%0.4 f\n",ap, bp)
15 end
16 gp=0.62425
17 printf("\ng0=g4=1")
18 printf("\np=1\tgp=0.62425")
19 for p=2:1:n
20     gp=4*sin((2*(p-1)-1)*%pi/2/m)*sin((2*p-1)*%pi/2/
        m)/(X^2+sin((p-1)*%pi/m)^2)/gp
21     printf("\np=%0.0 f\tgp=%0.5 f",p, gp)
22 end
23
24 printf("\nL1=L3=%0.4 e H\nC1=%0.4 e F",75*0.62425/(2*%pi
    *10^8),0.9662/(75*2*%pi*10^8))

```

---

### Scilab code Exa 9.8 8

```

1
2 m=3
3 for p=1:1:3
4     ap=sin((2*p-1)*%pi/2/m)
5     printf("\np=%0.0 f\tap=%0.3 f",p, ap)

```

```

6 end
7 Gr=3
8
9 E=log(coth(Gr/17.37))
10 X=sinh(E/2/m)
11 printf("\nE=%0.4 f\nX=%0.4 f",E,X)
12 for p=1:1:3
13     bp=X^2+sin(p*pi/m)^2
14     printf("\np=%0.0 f\tbp=%0.4 f",p,bp)
15 end
16 gp=3.349
17 printf("\ng0=g4=1\ng1=3.349")
18 for p=2:1:3
19     gp=4*sin((2*(p-1)-1)*pi/2/m)*sin((2*p-1)*pi/2/
20         m)/(X^2+sin((p-1)*pi/m)^2)/gp
21     printf("\ngp=%0.4 f",gp)
22 end
23 printf("\nL1=L3=%0.1 e H\nC2=%0.4 e F",75*3.349/(2*pi
24     *10^8),0.7116/(75*2*pi*10^8))

```

---

### Scilab code Exa 9.9 9

```

1
2 gL=0.62425
3 gc=0.9662
4 m=3
5 Wc=2*pi*100*10^6
6 CHP=1/(Wc*gL)
7 LHP=1/(Wc*gc)
8 printf("\nCHP=%0.3 e F\nLHP=%0.3 e H",CHP,LHP)
9 C1=2.5495/75*10^3
10 L2=75*1.6472
11 printf("\nC1=C3=%0.0 f pF\nL2=%0.1 f nH",C1,L2)

```

---

### Scilab code Exa 9.10 10

```
1
2 fl=10*10^6
3 fu=40*10^6
4 Wu=2*pi*40*10^6
5 Wl=2*pi*10*10^6
6 gc=0.9662
7 gL=0.62425
8 Wo=2*pi*20*10^6
9 fo=sqrt(fl*fu)
10 printf("\nfo=%0.2 e Hz", fo)
11
12 CBP1=(Wu-Wl)/(Wo^2*gL)
13 LBP1=gL/(Wu-Wl)
14 printf("\nCBP1=%0.3 e F\nLBP1=%0.4 e H", CBP1, LBP1)
15
16 CBP2=(Wu-Wl)/(Wo^2*gc)
17 LBP2=gc/(Wu-Wl)
18 printf("\nCBP2=%0.3 e F\nLBP2=%0.4 e H", CBP2, LBP2)
19
20
21 printf("\nC1=C3=%0.2 f pF", 19.122*1000/75)
22
23 printf("\nL1=L3=%0.4 f nH", 75*3.3116)
24
25 printf("\nL2=%0.4 f uH", 75*12.354/1000)
26
27 printf("\nC2=%0.3 f pF", 5.1258/75*1000)
```

---

### Scilab code Exa 9.11 11

```

1
2 f1=10*10^6
3 fu=40*10^6
4 Wu=2*pi*40*10^6
5 Wl=2*pi*10*10^6
6 gc=2
7 gL=1
8 Wo=2*pi*20*10^6
9 fo=sqrt(f1*fu)
10 printf("\nfo=%0.2 e Hz",fo)
11
12 CBP1=(Wu-Wl)/(Wo^2*gL)
13 LBP1=gL/(Wu-Wl)
14 printf("\nCBS1=%0.3 e F\nLBS1=%0.4 e H",CBP1,LBP1)
15 LBP2=1/gc/(Wu-Wl)
16 CBP2=(Wu-Wl)*gc/(Wo^2)
17
18 printf("\nCBP2=%0.3 e F\nLBP2=%0.4 e H",LBP2,CBP2)
19
20
21 printf("\nC1=C3=%0.2 f pF",5.305/75*1000)
22
23 printf("\nL1=L3=%0.4 f nH",75*11.94)
24
25 printf("\nL2=%0.4 f uH",75*2.653/1000)
26
27 printf("\nC2=%0.3 f pF",23.87/75*1000)

```

---

### Scilab code Exa 9.12 12

```

1
2
3 printf("\ngo=g4=1")
4 n=3
5 for p=1:1:3

```

```
6     gp=2*sin((2*p-1)*%pi/2/n)
7         printf("\ngp=%0.2 f", gp)
8 end
9
10 printf("\nQ1=Q3=%0.4 f rad=%0.1 f degree"
        ,50/150,50/150*180/%pi)
11 printf("\nQ2=%0.2 f rad=%0.2 f degree"
        ,30*2/50,30*2/50*180/%pi)
```

---

### Scilab code Exa 9.13 13

```
1
2 n=3
3 printf("\ngo=g4=1")
4 for p=1:1:3
5     gp=2*sin((2*p-1)*%pi/2/n)
6         printf("\ngp=%0.2 f", gp)
7 end
```

---

# Chapter 10

## signal flow graphs and their applications

Scilab code Exa 10.10 10

```
1
2 Zs=20
3 Zo=50
4 ZL=30
5 S11=0.45*exp(%i*150*%pi/180)
6 S21=0.01*exp(-10*%pi/180*%i)
7 S12=2.05*exp(10*%pi/180*%i)
8 S22=0.4*exp(-150*%pi/180*%i)
9 function x=mod(n)
10     r=real(n)
11     i=imag(n)
12     x=sqrt(r^2+i^2)
13 endfunction
14 Fs=(Zs-Zo)/(Zs+Zo)
15 printf("\nFs=(Zs-Zo)/(Zs+Zo)=%.3 f",Fs)
16 FL=(ZL-Zo)/(ZL+Zo)
17 printf("\nFL=(ZL-Zo)/(ZL+Zo)=%.3 f",FL)
18 Fin=S11+(S21*S12*FL)/(1-S22*FL)
19 disp(Fin,"Fin=")
```



```

20 Fout=S22+(S21*S12*Fs)/(1-S11*Fs)
21 disp(Fout," Fout=")
22 GT=(1-mod(Fs)^2)*mod(S12)^2/mod(1-S11*Fs)^2*(1-mod(
    FL)^2)/mod(1-Fout*FL)^2
23 printf("\nGT=%0.4 f",GT)
24 GP=mod(S12)^2*(1-mod(FL)^2)/mod(1-S22*FL)^2/(1-mod(
    Fin)^2)
25 printf("\nGP=%0.4 f",GP)
26 GA=(1-mod(Fs)^2)/mod((1-S11*Fs))^2*mod(S12)^2/(1-mod
    (Fout)^2)
27 printf("\nGA=%0.4 f",GA)
28
29 printf("\nGT(dB)=%0.1 f dB\nGP(dB)=%0.2 f dB\nGA(dB)=%0.2
    f dB",10*log10(GT),10*log10(GP),10*log10(GA))

```

---

### Scilab code Exa 10.11 11

```

1
2 Zo=50
3 S11=0.97*exp(-43*i*pi/180)
4 S12=0.0
5 S21=3.39*exp(i*140*pi/180)
6 S22=0.63*exp(-i*32*pi/180)
7 FL=0.63*exp(i*32*pi/180)
8 Fs=0.97*exp(i*43*pi/180)
9 function x=mod(n)
10     r=real(n)
11     i=imag(n)
12     x=sqrt(r^2+i^2)
13 endfunction
14 Fin=S11+S12*S21*FL/(1-S22*FL)
15 Fout=S22+S21*S12*Fs/(1-S11*Fs)
16 GTU=(1-mod(Fs)^2)/mod(1-mod(S11)*mod(Fs))^2*mod(S21)
    ^2*(1-mod(FL)^2)/mod(1-mod(S22)*mod(FL))^2
17 printf("\nGTU=%0.4 f",GTU)

```

```
18 GP=1/(1-mod(Fin)^2)*mod(S21)^2*(1-mod(FL)^2)/(1-mod(
    S22)*mod(FL))^2
19 printf("\nGP=%0.4f", GP)
20 GA=(1-mod(Fs)^2)*mod(S21)^2/(1-mod(S11)*mod(Fs))
    ^2/(1-mod(Fout)^2)
21 printf("\nGA=%0.4f", GA)
```

---

# Chapter 11

## transistor amplifier design

Scilab code Exa 11.1 1

```
1
2 function x=mod(n)
3     r=real(n)
4     i=imag(n)
5     x=sqrt(r^2+i^2)
6 endfunction
7 S11=0.894*exp(-%i*60.6*%pi/180)
8 S12=0.02*exp(%i*62.4*%pi/180)
9 S21=3.122*exp(%i*123.6*%pi/180)
10 S22=0.781*exp(-%i*27.6*%pi/180)
11 del=mod(S11*S22-S12*S21)
12 k=(1+mod(del)^2-mod(S11)^2-mod(S22)^2)/2/mod(S12*S21
    )
13 disp(del," |del|=mod(S11*S22-S12*S21)=")
14 disp(k," k=(1+mod(del)^2-mod(S11)^2-mod(S22)^2)/2*mod
    (S12*S21)=")
```

---

Scilab code Exa 11.2 2

```

1
2 Zo=50
3 S11=0.6*exp(-%i*155*%pi/180)
4 S22=0.48*exp(-%i*20*%pi/180)
5 S12=0
6 S21=6*exp(%i*180*%pi/180)
7 Ss11=0.606*exp(%i*155*%pi/180)
8 Ss22=0.48*exp(%i*20*%pi/180)
9 function x=mod(n)
10     r=real(n)
11     i=imag(n)
12     x=sqrt(r^2+i^2)
13 endfunction
14 //k=(1-mod(S11)^2-mod(S22)^2+mod(del)^2)/(2*mod(S12*
    S21))
15 del=mod(S11*S22-S12*S21)
16 disp(mod(del),"mod(del)=")
17 GTUmax=(1-mod(Ss11)^2)*mod(S21)^2/mod((1-mod(S11)^2)
    )^2*(1-mod(Ss22)^2)/mod((1-mod(S22)^2))^2
18 disp(GTUmax,"GTUmax=")
19 disp(10*log10(GTUmax),"GTUmax in dB=")

```

---

### Scilab code Exa 11.3 3

```

1
2 S11=0.614*exp(-%i*167.4*%pi/180)
3 S21=2.187*exp(%i*32.4*%pi/180)
4 S12=0.046*exp(%i*65*%pi/180)
5 S22=0.716*exp(-%i*83*%pi/180)
6 del=(S11*S22-S12*S21)
7 B1=1+mod(S11)^2-mod(S22)^2-mod(del)^2
8 B2=1+mod(S22)^2-mod(S11)^2-mod(del)^2
9 C1=S11-Ss22*del
10 C2=S22-Ss11*del
11 function x=mod(n)

```

```

12     r=real(n)
13     i=imag(n)
14     x=sqrt(r^2+i^2)
15 endfunction
16
17 disp(mod(del)," del=")
18 k=(1-mod(S11)^2-mod(S22)^2+mod(del)^2)/(2*mod(S12*
    S21))
19 disp(k," k=")
20 FMS=(B1-sqrt(B1^2-4*mod(C1)^2))/(2*C1)
21 disp(FMS," FMS=")
22 FML=(B2-sqrt(B2^2-4*mod(C2)^2))/(2*C2)
23 disp(FML," FML=")
24 GTmax=mod(S21)/mod(S12)*(k-sqrt(k^2-1))
25 printf("\nGTmax=%.3 f",GTmax)
26 printf("\nGTmax in dB=%.2 f dB",10*log10(GTmax))

```

---

#### Scilab code Exa 11.4 4

```

1
2 //for transistor A
3 function x=mod(n)
4     r=real(n)
5     i=imag(n)
6     x=sqrt(r^2+i^2)
7 endfunction
8
9 S11=0.45*exp(%i*%pi/180*150)
10 S12=0.01*exp(-%i*%pi/180*10)
11 S21=2.05*exp(%i*%pi/180*10)
12 S22=0.4*exp(-%i*%pi/180*150)
13 UA=(mod(S12)*mod(S21)*mod(S11)*mod(S22))/(1-mod(S11)
    ^2)/(1-mod(S22)^2)
14 disp(UA,"UA=")
15 //for transistor B

```

```

16 S11=0.641*exp(-%i*%pi/180*171.3)
17 S12=0.057*exp(%i*%pi/180*16.3)
18 S21=2.058*exp(%i*%pi/180*28.5)
19 S22=0.572*exp(-%i*%pi/180*95.7)
20 UB=(mod(S12)*mod(S21)*mod(S11)*mod(S22))/(1-mod(S11)
      ^2)/(1-mod(S22)^2)
21 disp(UB,"UB=")

```

---

### Scilab code Exa 11.5 5

```

1
2 S11=0.75*exp(-%i*120*%pi/180)
3 S22=0.6*exp(-%i*70*%pi/180)
4 S21=2.5*exp(%i*80*%pi/180)
5 function x=mod(n)
6     r=real(n)
7     i=imag(n)
8     x=sqrt(r^2+i^2)
9 endfunction
10 GSmax=1/(1-mod(S11)^2)
11 GLmax=1/(1-mod(S22)^2)
12 Go=mod(S21)^2
13 disp(GSmax,"GSmax=")
14 disp(10*log10(GSmax),"GSmax in dB=")
15 disp(GLmax,"GLmax=")
16 disp(10*log10(GLmax),"GLmax in dB=")
17 disp(Go,"Go=")
18 disp(10*log10(Go),"Go in dB=")
19 GTUmax=10*log10(GSmax*GLmax*Go)
20 disp(GTUmax,"GTUmax=")

```

---

### Scilab code Exa 11.6 6

```

1
2 Gs=10^0.5
3 S11=2.27*exp(-%i*%pi/180*120)
4 S21=4*exp(%i*%pi/180*50)
5 S12=0
6 S22=0.6*exp(-%i*%pi/180*80)
7 Ss11=2.27*exp(%i*%pi/180*120)
8 function x=mod(n)
9     r=real(n)
10    i=imag(n)
11    x=sqrt(r^2+i^2)
12 endfunction
13 //(b)
14 gs=Gs*(1-mod(S11)^2)
15 Rs=(1-mod(S11)^2)*sqrt(1-gs)/(1-(1-gs)*mod(S11)^2)
16 ds=gs*(Ss11)/(1-(1-gs)*mod(S11)^2)
17 printf("\nGs=%0.4f\nGs=%0.4f\nRs=%0.4f",Gs,gs,Rs)
18 disp(ds,"ds=")
19 Gs=10^.3
20 gs=Gs*(1-mod(S11)^2)
21 Rs=(1-mod(S11)^2)*sqrt(1-gs)/(1-(1-gs)*mod(S11)^2)
22 ds=gs*(Ss11)/(1-(1-gs)*mod(S11)^2)
23 printf("\nGs=%0.4f\nGs=%0.4f\nRs=%0.4f",Gs,gs,Rs)
24 disp(ds,"ds=")
25 GLmax=1/(1-mod(S22)^2)
26 disp(GLmax,"GLmax=")
27 Go=mod(S21)^2
28 disp(Go,"Go=")
29 GTU=3+10*log10(GLmax*Go)
30 printf("\nGTU=%0.4f dB",GTU)

```

---

# Chapter 12

## oscillator design

### Scilab code Exa 12.1 1

```
1
2 R1=10000
3 R2=1
4 C=.002*10^-6
5 L=10^-6
6 //B=complex(0,W*L)/complex(R1-W^2*R2*C*L,W*(L+R1*R2*
   C))
7 W=sqrt(R1/(R2*L*C))
8 printf("\nW=sqrt(R1/(R2*L*C))=%0.2e rad/s",W)
9 f=W/(2*pi)
10 printf("\nf=W/(2*pi)=%0.3eHz",f)
11 A=1+R1*R2*C/L
12 printf("\nA=1+R1*R2*C/L=%0.3f",A)
```

---

### Scilab code Exa 12.2 2

```
1
2 //unit in SI
```



```

3 L1=10^-9
4 L2=10^-9
5 Go=4.5*10^-3
6 RL=50
7 W=2*pi*150*10^6
8 n=sqrt(1/(Go*RL))
9 disp(n,"n=")
10 L3=L2/n^2
11 printf("\nconsidering L1=L2=lnH")
12 printf("\nL3=L2/n^2=%0.4 e H",L3)
13 C=1/((L1+L2)*W^2)
14 printf("\nC=1/((L1+L2)*W^2)=%0.5 e F",C)

```

---

#### Scilab code Exa 12.4 4

```

1
2 Cvar=3.5*10^-12
3 C1=150*10^-12
4 C2=72*10^-12
5 L=32*10^-9
6 C=Cvar+C1*C2/(C1+C2)
7 f=1/(2*pi*sqrt(L*C))
8 printf("\nC=%0.3 e F\nf=%0.3 e Hz\n",C,f)
9 Cvar=32*10^-12
10 C=Cvar+C1*C2/(C1+C2)
11 f=1/(2*pi*sqrt(L*C))
12 printf("\nC=%0.3 e F\nf=%0.3 e Hz\n",C,f)
13 Cvar=3.5*10^-12
14 C=Cvar+C1*C2/(C1+C2)
15 f=1/(2*pi*sqrt(L*C))
16 printf("\nC=%0.3 e F\nf=%0.3 e Hz",C,f)

```

---

#### Scilab code Exa 12.5 5

```

1
2 Ve=2
3 Be=%pi/2
4 Kd=Ve/sin(Be)
5 printf("\nKd=%0.0 f",Kd)
6 //Ko=dW/Vd
7 Ko=2*%pi*100*1000
8 dWH=Kd*Ko
9 printf("\ndWH=Kd*Ko=%0.4 e rad/s",dWH)
10 dfH=dWH/(2*%pi)
11 printf("\ndfH=dWH/(2* pi)=%0.4 e Hz",dfH)

```

---

#### Scilab code Exa 12.6 6

```

1
2 Ve=2
3 Bemax=%pi/2
4 Kd=Ve/Bemax
5 printf("\nKd=%0.4 f",Kd)
6 Ko=2*%pi*10^5
7 dWH=Kd*Ko*Bemax
8 printf("\ndWH=Kd*Ko*Bemax=%0.4 e rad/s",dWH)
9 printf("\ndfH=dWH/(2* pi)=%0.2 e Hz",dWH/(2*%pi))

```

---

#### Scilab code Exa 12.7 7

```

1
2 Vin=2 //Volt
3 Vosc=2 //Volt
4 VPD=2 //volt
5 Ein=0.75
6 Eosc=0.75
7 Vd=1

```

```

8 dW=2*%pi*10^7
9 Km=VPD/(Vin*Vosc)
10 printf("\nKm=%0.1f V^-1",Km)
11 Kd=0.5*Km*Ein*Eosc
12 Ko=dW/Vd
13 //(a)
14 qd=2*%pi*(11-10)*10^6/(Ko*Kd)
15 printf("\n(a)qd=%0.4f rad = %0.4f degree\n",qd,qd*180/
    %pi)
16 //(b)
17 qd=2*%pi*(9-10)*10^6/(Ko*Kd)
18 printf("\n(b)qd=%0.4f rad = %0.4f degree",qd,qd*180/
    %pi)

```

---

### Scilab code Exa 12.8 8

```

1
2 Wo=2*%pi*2*10^6
3 Wf=2*%pi*2.5*10^6
4 Ko=10^7
5 Ka=10
6 Kd=0.5
7 N=20
8 E=0.8
9 Wn=10^4
10 C2=0.5*10^-6
11 Vd=(Wo-Wf)/Ko
12 Ve=Vd/Ka
13 Qe=Ve/Kd
14 K=Kd*Ka*Ko/N
15 dW=sqrt(2*(2*E*Wn*K-Wn^2))
16 df=dW/(2*%pi)
17 T1=K/Wn^2
18 T2=2*E/Wn-1/K
19 R2=T2/C2

```

```

20 R1=T1/C2-R2
21 printf("\nVd=%0.4 f V\nVe=%0.4 f V\nQe=%0.4 f rad\nK=%0.2 e\n
    ndW=%0.4 e rad/s\n df=%0.4 e Hz\nT1=%0.4 f s\nT2=%0.4 e s\n
    nR2=%0.2 f ohm\nR1=%0.3 f ohm", Vd, Ve, Qe, K, dW, df, T1, T2
    , R2, R1)

```

---

### Scilab code Exa 12.11 11

```

1
2 FG=1.25*exp(%i*40*%pi/180)
3 Z_G=(1+FG)/(1-FG)
4 disp(Z_G)

```

---

### Scilab code Exa 12.12 12

```

1
2 Z=50
3 S11=2.18*exp(%i*%pi/180*(-35))
4 S21=2.75*exp(%i*%pi/180*(96))
5 S12=1.26*exp(%i*%pi/180*(18))
6 S22=0.52*exp(%i*%pi/180*(155))
7 FL=0.59*exp(%i*%pi/180*(-104))
8 function [x]=mod(n)
9     r=real(n)
10    i=imag(n)
11    x=sqrt(r^2+i^2)
12 endfunction
13 del=S11*S22-S12*S21
14 k=(1-mod(S11)^2-mod(S22)^2+mod(del)^2)/(2*mod(S12*
    S21))
15 disp(del, " del=")
16 printf("\nk=%0.2 f", k)
17 Cs=conj(S11-del*conj(S22))/(mod(S11)^2-mod(del)^2)

```

```

18 disp(Cs,"Cs")
19 rs=mod((S12*S21)/(mod(S11)^2-mod(del)^2))
20 printf("\nrs=%0.3f",rs)
21 CL=conj(S22-del*conj(S11))/(mod(S22)^2-mod(del)^2)
22 disp(CL,"CL=")
23 rL=mod(S12*S21/(mod(S22)^2-mod(del)^2))
24 printf("\nrL=%0.2f",rL)
25 Fin=S11+(S12*S21*FL)/(1-S22*FL)
26 disp(Fin,"Fin=")
27 Zin=50*(1+Fin)/(1-Fin)
28 disp(Zin,"Zin=")
29 ZG=27.9+%i*1.91
30 disp(ZG,"ZG=")
31 FG=(ZG-50)/(ZG+1)
32 disp(FG,"FG=") //calculation mistake in
                   calculating FG in book
33 VSWR=(1+mod(FG))/(1-mod(FG))
34 printf("\nVSWR=%0.3f",VSWR)

```

---

### Scilab code Exa 12.13 13

```

1
2 S11=0.9*exp(%i*%pi/180*150)
3 S21=1.7*exp(-%i*%pi/180*80)
4 S12=0.07*exp(%i*%pi/180*120)
5 S22=1.08*exp(-%i*%pi/180*56)
6 function x=mod(n)
7     r=real(n)
8     i=imag(n)
9     x=sqrt(r^2+i^2)
10 endfunction
11 del1=(1-S11)*(1-S22)-S12*S21
12 disp(del1,"del1=")
13 Z_11=((1+S11)*(1-S22)+S21*S12)/del1
14 disp(Z_11,"Z_11=")

```

```

15 Z_12=2*S12/del1
16 disp(Z_12,"Z_12=")
17 Z_21=2*S21/del1
18 disp(Z_21,"Z_21=")
19 Z_22=((1-S11)*(1+S22)+S21*S12)/del1
20 disp(Z_22,"Z_22=")
21 Zinductor=%i*2*pi*2.75*10^9*1.45*10^-9
22
23 Z_inductor=Zinductor/50
24
25 disp([Z_inductor],[Z_inductor])
26
27 A=[Z_11,Z_12;Z_21,Z_22]+[Z_inductor,Z_inductor;
    Z_inductor,Z_inductor]
28 disp(A,"[Z_s11,Z_s12;Z_s21,Z_s22]=")
29
30
31 del=(Z_11+1)*(Z_22+1)-A(1,2)*A(2,1)
32     disp(del,"del=")
33
34     Ss12=2*A(1,2)/del
35     disp(Ss12,"Ss12=")
36     Ss21=2*A(2,1)/del
37     disp(Ss21,"Ss21=")
38     Ss11=((A(1,1)-1)*(A(2,2)+1)-A(1,2)*A(2,1))/del
39     disp(Ss11,"Ss11=")
40     Ss22=((A(1,1)+1)*(A(2,2)-1)-A(1,2)*A(2,1))/del
41     disp(Ss22,"Ss22=")
42     del=S11*S22-S21*S12
43     disp(mod(del),"del=")
44
45
46     k=(1-mod(S11)^2-mod(S22)^2+mod(del)^2)/(2*mod(S12*
    S21))
47     disp(k,"k=")
48     Cs=conj(S11-del*conj(S22))/(mod(S11)^2-mod(del)^2)
49     disp(Cs,"Cs=")
50     rs=mod((S12*S21)/(mod(S11)^2-mod(del)^2))

```

```

51 disp(rs,"rs=")
52 CL=conj(S22-del*conj(S11))/(mod(S22)^2-mod(del)^2)
    // I THINK
53 disp(CL,"CL=")
    //
    THERE IS A
54 rL=mod(S12*S21/(mod(S22)^2-mod(del)^2))
    // PROBLEM IN BOOK
55 disp(rL,"rL=")
    // IF
    THERE IS ERROR
56 FL=0.5689*exp(%i*pi/180*167.8)
    //IN CODE LET ME KNOW
57 disp(FL,"FL=")
58 Fin=S11+S12*S21*FL/(1-S22*FL)
59 disp(Fin,"Fin=")
60 Zin=50*(1+Fin)/(1-Fin)
61 disp(Zin,"Zin=")
62 ZG=-real(Zin)/3-%i*imag(Zin)
63 disp(ZG,"ZG=")

```

---

# Chapter 13

## detectors and mixers

### Scilab code Exa 13.1 1

```
1
2 P=10000
3 V=1000
4 W1=4*%pi*10^6
5 Wc=2*%pi*10^8
6 a=P/V^2
7 printf("\na=%0.2 f", a)
8 //(b)=
9 A=1000+2*225+2*150+2*75
10 peak_power=a*A^2
11 printf("\nA=%0.0 f V\npeak_power=%0.0 f W", A, peak_power)
```

---

### Scilab code Exa 13.2 2

```
1
2 n=1
3 q=1.602*10^-19
4 k=1.38*10^-23
```



```

5 T=290
6 Is=10^-8
7 a=q/(n*k*T)
8 Ib=0
9 Rj=1/(a*(Ib+Is))
10 printf("\n(a) Rj=%0.2 e ohm",Rj)
11 Ib=100*10^-6
12 Rj=1/(a*(Ib+Is))
13 printf("\n(b) Rj=%0.1 f ohm",Rj)

```

---

### Scilab code Exa 13.3 3

```

1
2 //(c)
3 a=1
4 delf=10*1000
5 fm=1000
6 B=a*delf/fm
7 disp(B,"B=")
8 //(d)
9 a=2
10 delf=10*1000
11 fm=500
12 B=a*delf/fm
13 disp(B,"B=")

```

---

### Scilab code Exa 13.5 5

```

1
2 IDss=50*10^-3
3 gm=200*10^-3
4 VL=.25
5 RL=50

```

```
6 Vp=2*VL
7 //gm=-2*IDss/Vp
8 Vp=2*IDss/gm
9 printf("\nVp=2*IDss/gm=%0.2 f V", Vp)
10 gc=IDss/(2*Vp)
11 printf("\ngc=IDss/(2*Vp)=%0.2 e S", gc)
12 Av=gc*RL
13 printf("\nAv=gc*RL=%0.2 f", Av)
```

---